

Solutions Manual to Accompany  
**Fundamentals of Microelectronics, 1st Edition**

Book ISBN: 978-0-471-47846-1

Razavi

All materials copyrighted and published by John Wiley & Sons, Inc.

Not for duplication or distribution

2.1 (a)

$$\begin{aligned}k &= 8.617 \times 10^{-5} \text{ eV/K} \\n_i(T = 300 \text{ K}) &= 1.66 \times 10^{15} (300 \text{ K})^{3/2} \exp \left[ -\frac{0.66 \text{ eV}}{2 (8.617 \times 10^{-5} \text{ eV/K}) (300 \text{ K})} \right] \text{ cm}^{-3} \\&= \boxed{2.465 \times 10^{13} \text{ cm}^{-3}} \\n_i(T = 600 \text{ K}) &= 1.66 \times 10^{15} (600 \text{ K})^{3/2} \exp \left[ -\frac{0.66 \text{ eV}}{2 (8.617 \times 10^{-5} \text{ eV/K}) (600 \text{ K})} \right] \text{ cm}^{-3} \\&= \boxed{4.124 \times 10^{16} \text{ cm}^{-3}}\end{aligned}$$

Compared to the values obtained in Example 2.1, we can see that the intrinsic carrier concentration in Ge at  $T = 300 \text{ K}$  is  $\frac{2.465 \times 10^{13}}{1.08 \times 10^{10}} = 2282$  times higher than the intrinsic carrier concentration in Si at  $T = 300 \text{ K}$ . Similarly, at  $T = 600 \text{ K}$ , the intrinsic carrier concentration in Ge is  $\frac{4.124 \times 10^{16}}{1.54 \times 10^{15}} = 26.8$  times higher than that in Si.

(b) Since phosphorus is a Group V element, it is a donor, meaning  $N_D = 5 \times 10^{16} \text{ cm}^{-3}$ . For an n-type material, we have:

$$\begin{aligned}n &= N_D = \boxed{5 \times 10^{16} \text{ cm}^{-3}} \\p(T = 300 \text{ K}) &= \frac{[n_i(T = 300 \text{ K})]^2}{n} = \boxed{1.215 \times 10^{10} \text{ cm}^{-3}} \\p(T = 600 \text{ K}) &= \frac{[n_i(T = 600 \text{ K})]^2}{n} = \boxed{3.401 \times 10^{16} \text{ cm}^{-3}}\end{aligned}$$

2. (a) Mobility of electrons in Si =  $1350 \text{ cm}^2/\text{V}\cdot\text{s}$   
Mobility of holes in Si =  $480 \text{ cm}^2/\text{V}\cdot\text{s}$

$$\Rightarrow \text{velocity of electrons} = \mu_n E = \left(1350 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \left(\frac{0.1 \text{ V}}{\mu\text{m}}\right)$$
$$= 1.35 \cdot 10^4 \text{ m/s}$$

$$\text{velocity of holes} = \mu_p E = \left(480 \frac{\text{cm}^2}{\text{V}\cdot\text{s}}\right) \left(\frac{0.1 \text{ V}}{\mu\text{m}}\right)$$
$$= 4.8 \cdot 10^3 \text{ m/s}$$

(b) Given  $E = 0.1 \text{ V}/\mu\text{m}$  hole current negligible  
 $\mu_n = 1350 \text{ cm}^2/\text{V}\cdot\text{s}$   $\mu_p = 480 \text{ cm}^2/\text{V}\cdot\text{s}$

$$J_{\text{tot}} = 1 \text{ mA}/\mu\text{m}^2 = q [\mu_n n E + \mu_p p E] \approx q \mu_n n E$$

$$\therefore n = \frac{J_{\text{tot}}}{q \mu_n E} = \frac{1 \text{ mA}/\mu\text{m}^2}{(1.6 \cdot 10^{-19} \text{ C})(1350 \text{ cm}^2/\text{V}\cdot\text{s})(0.1 \text{ V}/\mu\text{m})}$$
$$= 4.6 \cdot 10^{17} \text{ cm}^{-3}$$

- 2.3 (a) Since the doping is uniform, we have no diffusion current. Thus, the total current is due only to the drift component.

$$\begin{aligned}
 I_{tot} &= I_{drift} \\
 &= q(n\mu_n + p\mu_p)AE \\
 n &= 10^{17} \text{ cm}^{-3} \\
 p &= n_i^2/n = (1.08 \times 10^{10})^2/10^{17} = 1.17 \times 10^3 \text{ cm}^{-3} \\
 \mu_n &= 1350 \text{ cm}^2/\text{V} \cdot \text{s} \\
 \mu_p &= 480 \text{ cm}^2/\text{V} \cdot \text{s} \\
 E &= V/d = \frac{1 \text{ V}}{0.1 \text{ } \mu\text{m}} \\
 &= 10^5 \text{ V/cm} \\
 A &= 0.05 \text{ } \mu\text{m} \times 0.05 \text{ } \mu\text{m} \\
 &= 2.5 \times 10^{-11} \text{ cm}^2
 \end{aligned}$$

Since  $n\mu_n \gg p\mu_p$ , we can write

$$\begin{aligned}
 I_{tot} &\approx qn\mu_n AE \\
 &= \boxed{54.1 \text{ } \mu\text{A}}
 \end{aligned}$$

- (b) All of the parameters are the same except  $n_i$ , which means we must re-calculate  $p$ .

$$\begin{aligned}
 n_i(T = 400 \text{ K}) &= 3.657 \times 10^{12} \text{ cm}^{-3} \\
 p &= n_i^2/n = 1.337 \times 10^8 \text{ cm}^{-3}
 \end{aligned}$$

Since  $n\mu_n \gg p\mu_p$  still holds (note that  $n$  is 9 orders of magnitude larger than  $p$ ), the hole concentration once again drops out of the equation and we have

$$\begin{aligned}
 I_{tot} &\approx qn\mu_n AE \\
 &= \boxed{54.1 \text{ } \mu\text{A}}
 \end{aligned}$$



2.4 (a) From Problem 1, we can calculate  $n_i$  for Ge.

$$\begin{aligned}
 n_i(T = 300 \text{ K}) &= 2.465 \times 10^{13} \text{ cm}^{-3} \\
 I_{tot} &= q(n\mu_n + p\mu_p)AE \\
 n &= 10^{17} \text{ cm}^{-3} \\
 p &= n_i^2/n = 6.076 \times 10^9 \text{ cm}^{-3} \\
 \mu_n &= 3900 \text{ cm}^2/\text{V} \cdot \text{s} \\
 \mu_p &= 1900 \text{ cm}^2/\text{V} \cdot \text{s} \\
 E &= V/d = \frac{1 \text{ V}}{0.1 \text{ } \mu\text{m}} \\
 &= 10^5 \text{ V/cm} \\
 A &= 0.05 \text{ } \mu\text{m} \times 0.05 \text{ } \mu\text{m} \\
 &= 2.5 \times 10^{-11} \text{ cm}^2
 \end{aligned}$$

Since  $n\mu_n \gg p\mu_p$ , we can write

$$\begin{aligned}
 I_{tot} &\approx qn\mu_nAE \\
 &= \boxed{156 \text{ } \mu\text{A}}
 \end{aligned}$$

(b) All of the parameters are the same except  $n_i$ , which means we must re-calculate  $p$ .

$$\begin{aligned}
 n_i(T = 400 \text{ K}) &= 9.230 \times 10^{14} \text{ cm}^{-3} \\
 p &= n_i^2/n = 8.520 \times 10^{12} \text{ cm}^{-3}
 \end{aligned}$$

Since  $n\mu_n \gg p\mu_p$  still holds (note that  $n$  is 5 orders of magnitude larger than  $p$ ), the hole concentration once again drops out of the equation and we have

$$\begin{aligned}
 I_{tot} &\approx qn\mu_nAE \\
 &= \boxed{156 \text{ } \mu\text{A}}
 \end{aligned}$$

2.5 Since there's no electric field, the current is due entirely to diffusion. If we define the current as positive when flowing in the positive  $x$  direction, we can write

$$I_{tot} = I_{diff} = AJ_{diff} = Aq \left[ D_n \frac{dn}{dx} - D_p \frac{dp}{dx} \right]$$

$$A = 1 \mu\text{m} \times 1 \mu\text{m} = 10^{-8} \text{ cm}^2$$

$$D_n = 34 \text{ cm}^2/\text{s}$$

$$D_p = 12 \text{ cm}^2/\text{s}$$

$$\frac{dn}{dx} = -\frac{5 \times 10^{16} \text{ cm}^{-3}}{2 \times 10^{-4} \text{ cm}} = -2.5 \times 10^{20} \text{ cm}^{-4}$$

$$\frac{dp}{dx} = \frac{2 \times 10^{16} \text{ cm}^{-3}}{2 \times 10^{-4} \text{ cm}} = 10^{20} \text{ cm}^{-4}$$


$$I_{tot} = (10^{-8} \text{ cm}^2) (1.602 \times 10^{-19} \text{ C}) [(34 \text{ cm}^2/\text{s}) (-2.5 \times 10^{20} \text{ cm}^{-4}) - (12 \text{ cm}^2/\text{s}) (10^{20} \text{ cm}^{-4})]$$

$$= \boxed{-15.54 \mu\text{A}}$$

b. Given Area = a

find total electrons stored.

$$n(x) = -\frac{N}{L}x + N$$

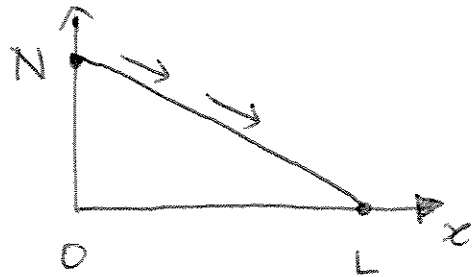

∴ total electrons stored


$$= \int a \cdot n(x) dx = \int_0^L a \left( -\frac{N}{L}x + N \right) dx$$

$$= aN \left( -\frac{x^2}{2L} + x \right) \Big|_0^L = \frac{aNL}{2}$$

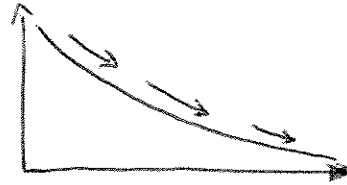7. Given Area = a

find total electrons stored.

$$n(x) = N \cdot \exp\left(\frac{-x}{L_d}\right)$$



∴ total electrons stored

$$= \int_0^{\infty} a \cdot n(x) \, dx = \int_0^{\infty} a \cdot N \cdot \exp\left(\frac{-x}{L_d}\right) \, dx$$

$$= aN \left( -L_d \cdot \exp\left(\frac{-x}{L_d}\right) \right) \Big|_0^{\infty} = aNL_d.$$

For the linear profile, the result depends on the length,  $L$ .

For the exponential profile, the result is constant (since  $L_d$  is constant.)

2.8 Assume the diffusion lengths  $L_n$  and  $L_p$  are associated with the electrons and holes, respectively, in this material and that  $L_n, L_p \ll 2 \mu\text{m}$ . We can express the electron and hole concentrations as functions of  $x$  as follows:

$$\begin{aligned}
 n(x) &= Ne^{-x/L_n} \\
 p(x) &= Pe^{(x-2)/L_p} \\
 \# \text{ of electrons} &= \int_0^2 an(x)dx \\
 &= \int_0^2 aNe^{-x/L_n} dx \\
 &= -aNL_n \left( e^{-x/L_n} \right) \Big|_0^2 \\
 &= -aNL_n \left( e^{-2/L_n} - 1 \right) \\
 \# \text{ of holes} &= \int_0^2 ap(x)dx \\
 &= \int_0^2 aPe^{(x-2)/L_p} dx \\
 &= aPL_p \left( e^{(x-2)/L_p} \right) \Big|_0^2 \\
 &= aPL_p \left( 1 - e^{-2/L_p} \right)
 \end{aligned}$$

Due to our assumption that  $L_n, L_p \ll 2 \mu\text{m}$ , we can write

$$\begin{aligned}
 e^{-2/L_n} &\approx 0 \\
 e^{-2/L_p} &\approx 0 \\
 \# \text{ of electrons} &\approx \boxed{aNL_n} \\
 \# \text{ of holes} &\approx \boxed{aPL_p}
 \end{aligned}$$

9. Drift is analogous to water flow in a river.

Water flows from top of mountain to bottom because of gravitational field; electron flows from one terminal to the other because of electric field.

<u>DRIFT</u>		<u>WATER FLOW</u>
electrons	↔	water
electric field	↔	gravitational field.
drift/current	↔	water flow

2.10 (a)

$$n_n = N_D = \boxed{5 \times 10^{17} \text{ cm}^{-3}}$$

$$p_n = n_i^2/n_n = \boxed{233 \text{ cm}^{-3}}$$

$$p_p = N_A = \boxed{4 \times 10^{16} \text{ cm}^{-3}}$$

$$n_p = n_i^2/p_p = \boxed{2916 \text{ cm}^{-3}}$$

(b) We can express the formula for  $V_0$  in its full form, showing its temperature dependence:

$$V_0(T) = \frac{kT}{q} \ln \left[ \frac{N_A N_D}{(5.2 \times 10^{15})^2 T^3 e^{-E_g/kT}} \right]$$

$$V_0(T = 250 \text{ K}) = \boxed{906 \text{ mV}}$$

$$V_0(T = 300 \text{ K}) = \boxed{849 \text{ mV}}$$

$$V_0(T = 350 \text{ K}) = \boxed{789 \text{ mV}}$$

Looking at the expression for  $V_0(T)$ , we can expand it as follows:

$$V_0(T) = \frac{kT}{q} [\ln(N_A) + \ln(N_D) - 2 \ln(5.2 \times 10^{15}) - 3 \ln(T) + E_g/kT]$$

Let's take the derivative of this expression to get a better idea of how  $V_0$  varies with temperature.

$$\frac{dV_0(T)}{dT} = \frac{k}{q} [\ln(N_A) + \ln(N_D) - 2 \ln(5.2 \times 10^{15}) - 3 \ln(T) - 3]$$

From this expression, we can see that if  $\ln(N_A) + \ln(N_D) < 2 \ln(5.2 \times 10^{15}) + 3 \ln(T) + 3$ , or equivalently, if  $\ln(N_A N_D) < \ln[(5.2 \times 10^{15})^2 T^3] - 3$ , then  $V_0$  will decrease with temperature, which we observe in this case. In order for this not to be true (i.e., in order for  $V_0$  to increase with temperature), we must have either very high doping concentrations or very low temperatures.

2.11 Since the p-type side of the junction is undoped, its electron and hole concentrations are equal to the intrinsic carrier concentration.

$$\begin{aligned}n_n &= N_D = 3 \times 10^{16} \text{ cm}^{-3} \\p_p &= n_i = 1.08 \times 10^{10} \text{ cm}^{-3} \\V_0 &= V_T \ln \left( \frac{N_D n_i}{n_i^2} \right) \\&= (26 \text{ mV}) \ln \left( \frac{N_D}{n_i} \right) \\&= \boxed{386 \text{ mV}}\end{aligned}$$



2.12 (a)


$$\begin{aligned}
C_{j0} &= \sqrt{\frac{q\epsilon_{\text{Si}}}{2} \frac{N_A N_D}{N_A + N_D} \frac{1}{V_0}} \\
C_j &= \frac{C_{j0}}{\sqrt{1 - V_R/V_0}} \\
N_A &= 2 \times 10^{15} \text{ cm}^{-3} \\
N_D &= 3 \times 10^{16} \text{ cm}^{-3} \\
V_R &= -1.6 \text{ V} \\
V_0 &= V_T \ln\left(\frac{N_A N_D}{n_i^2}\right) = 701 \text{ mV} \\
C_{j0} &= 14.9 \text{ nF/cm}^2 \\
C_j &= 8.22 \text{ nF/cm}^2 \\
&= \boxed{0.082 \text{ fF/cm}^2}
\end{aligned}$$

(b) Let's write an equation for  $C'_j$  in terms of  $C_j$  assuming that  $C'_j$  has an acceptor doping of  $N'_A$ .

$$\begin{aligned}
C'_j &= 2C_j \\
\sqrt{\frac{q\epsilon_{\text{Si}}}{2} \frac{N'_A N_D}{N'_A + N_D} \frac{1}{V_T \ln(N'_A N_D/n_i^2) - V_R}} &= 2C_j \\
\frac{q\epsilon_{\text{Si}}}{2} \frac{N'_A N_D}{N'_A + N_D} \frac{1}{V_T \ln(N'_A N_D/n_i^2) - V_R} &= 4C_j^2 \\
q\epsilon_{\text{Si}} N'_A N_D &= 8C_j^2 (N'_A + N_D) (V_T \ln(N'_A N_D/n_i^2) - V_R) \\
N'_A [q\epsilon_{\text{Si}} N_D - 8C_j^2 (V_T \ln(N'_A N_D/n_i^2) - V_R)] &= 8C_j^2 N_D (V_T \ln(N'_A N_D/n_i^2) - V_R) \\
N'_A &= \frac{8C_j^2 N_D (V_T \ln(N'_A N_D/n_i^2) - V_R)}{q\epsilon_{\text{Si}} N_D - 8C_j^2 (V_T \ln(N'_A N_D/n_i^2) - V_R)}
\end{aligned}$$

We can solve this by iteration (you could use a numerical solver if you have one available). Starting with an initial guess of  $N'_A = 2 \times 10^{15} \text{ cm}^{-3}$ , we plug this into the right hand side and solve to find a new value of  $N'_A = 9.9976 \times 10^{15} \text{ cm}^{-3}$ . Iterating twice more, the solution converges to  $N'_A = 1.025 \times 10^{16} \text{ cm}^{-3}$ . Thus, we must increase the  $N_A$  by a factor of  $N'_A/N_A = 5.125 \approx \boxed{5}$ .

B.

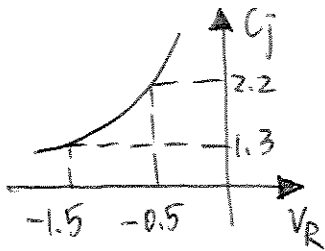

$$\frac{C_{j0}}{\sqrt{1 + \frac{0.5}{V_0}}} = 2.2 \quad \text{--- ①}$$

$$\frac{C_{j0}}{\sqrt{1 + \frac{1.5}{V_0}}} = 1.3 \quad \text{--- ②}$$

$$\text{①} \div \text{②} : \quad \frac{1 + \frac{1.5}{V_0}}{1 + \frac{0.5}{V_0}} = \left(\frac{2.2}{1.3}\right)^2 \Rightarrow V_0 = 0.0365 \text{ V}$$

Substitute  $V_0$  into ①:

$$C_{j0} = 2.2 \sqrt{1 + \frac{0.5}{V_0}} \approx 8.43 \text{ fF}/\mu\text{m}^2$$

$$\begin{aligned} \Rightarrow \frac{N_A N_D}{N_A + N_D} &= (C_{j0})^2 \cdot V_0 \cdot \frac{2}{\epsilon_{\text{eff}}} \\ &= \left(8.43 \frac{\text{fF}}{\mu\text{m}^2}\right)^2 \times (0.0365 \text{ V}) \cdot \frac{2}{\epsilon_{\text{eff}}} \approx 3.13 \cdot 10^{11} \text{ cm}^{-3} \end{aligned}$$

Fix a value for  $N_A > \frac{N_A N_D}{N_A + N_D} \cong \eta$

$$\begin{aligned} N_A = 2 \cdot 10^{18} \text{ cm}^{-3} &\Rightarrow N_D = \frac{\eta N_A}{N_A - \eta} \\ &= \frac{(3.13 \cdot 10^{17} \text{ cm}^{-3})(2 \cdot 10^{18} \text{ cm}^{-3})}{(2 \cdot 10^{18} - 3.13 \cdot 10^{17}) \text{ cm}^{-3}} \\ &\approx 3.71 \cdot 10^{17} \text{ cm}^{-3} \end{aligned}$$

14 (a) In forward bias,  $I_D = 1 \text{ mA}$ ,  $V_D = 750 \text{ mV}$


$$\begin{aligned}\therefore I_S &\approx I_D e^{-\frac{V_D}{V_T}} = (1 \text{ mA}) \exp[-750 \text{ mV}/26 \text{ mV}] \\ &= 2.97 \cdot 10^{-16} \text{ A}\end{aligned}$$

(b) Since  $I_S \propto \text{Area}$ , doubling area implies doubling  $I_S$ . From (a),

$$I_D = 1 \text{ mA} = 2 \times I_S e^{\frac{V_D}{V_T}}$$

$$\begin{aligned}\therefore V_D &= V_T \ln\left(\frac{I_D}{2I_S}\right) = (26 \text{ mV}) \ln\left(\frac{1 \text{ mA}}{2 \cdot 2.97 \cdot 10^{-16} \text{ A}}\right) \\ &= 0.732 \text{ V}\end{aligned}$$

15 (a)

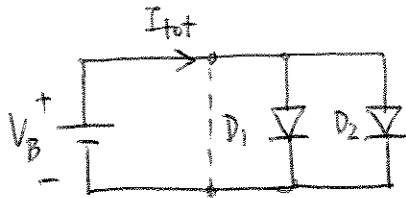

$$I_{tot} = I_{D_1} + I_{D_2} = I_{S_1} (e^{V_B/V_T} - 1) + I_{S_2} (e^{V_B/V_T} - 1)$$

$$= (I_{S_1} + I_{S_2}) (e^{V_B/V_T} - 1)$$

Therefore, the parallel combination operates as an exponential device, with an equivalent saturation current of  $I_{S_1} + I_{S_2}$ .

(b) By KVL,  $V_{D_1} = V_{D_2}$

$$\Rightarrow V_T \ln\left(\frac{I_{D_1}}{I_{S_1}}\right) = V_T \ln\left(\frac{I_{D_2}}{I_{S_2}}\right)$$


$$\text{Also, } I_{tot} = I_{D_1} + I_{D_2} \Rightarrow I_{D_2} = I_{tot} - I_{D_1}$$

$$\therefore V_T \ln\left(\frac{I_{D_1}}{I_{S_1}}\right) = V_T \ln\left(\frac{I_{tot} - I_{D_1}}{I_{S_2}}\right)$$

$$\Rightarrow I_{D_1} = I_{tot} \left( \frac{I_{S_1}}{I_{S_1} + I_{S_2}} \right)$$

$$\Rightarrow I_{D_2} = I_{tot} \left( \frac{I_{S_2}}{I_{S_1} + I_{S_2}} \right)$$

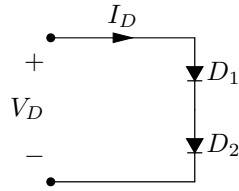2.16 (a) The following figure shows the series diodes.



Let  $V_{D1}$  be the voltage drop across  $D_1$  and  $V_{D2}$  be the voltage drop across  $D_2$ . Let  $I_{S1} = I_{S2} = I_S$ , since the diodes are identical.


$$\begin{aligned} V_D &= V_{D1} + V_{D2} \\ &= V_T \ln \left( \frac{I_D}{I_S} \right) + V_T \ln \left( \frac{I_D}{I_S} \right) \\ &= 2V_T \ln \left( \frac{I_D}{I_S} \right) \\ I_D &= I_S e^{V_D/2V_T} \end{aligned}$$

Thus, the diodes in series act like a single device with an exponential characteristic described by  $I_D = I_S e^{V_D/2V_T}$ .

(b) Let  $V_D$  be the amount of voltage required to get a current  $I_D$  and  $V'_D$  the amount of voltage required to get a current  $10I_D$ .

$$\begin{aligned} V_D &= 2V_T \ln \left( \frac{I_D}{I_S} \right) \\ V'_D &= 2V_T \ln \left( \frac{10I_D}{I_S} \right) \\ V'_D - V_D &= 2V_T \left[ \ln \left( \frac{10I_D}{I_S} \right) - \ln \left( \frac{I_D}{I_S} \right) \right] \\ &= 2V_T \ln(10) \\ &= \boxed{120 \text{ mV}} \end{aligned}$$

17.

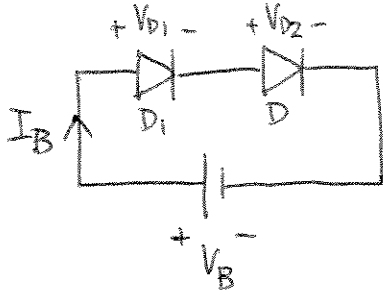

Find  $I_B$ ,  $V_{D1}$ ,  $V_{D2}$  in terms of  $V_B$ ,  $I_1$ ,  $I_{S2}$

$$\text{By KVL, } V_B = V_{D1} + V_{D2} = V_T \ln\left(\frac{I_B}{I_{S1}}\right) + V_T \ln\left(\frac{I_B}{I_{S2}}\right)$$


$$\Rightarrow V_B = V_T \ln\left(\frac{I_B^2}{I_{S1} I_{S2}}\right)$$

$$\therefore I_B = \sqrt{I_{S1} I_{S2} \cdot \exp\left(\frac{V_B}{V_T}\right)} = \sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)$$

$$\begin{aligned} V_{D1} &= V_T \ln\left(\frac{I_B}{I_{S1}}\right) = V_T \ln\left(\frac{\sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)}{I_{S1}}\right) \\ &= V_T \ln\left(\sqrt{\frac{I_{S2}}{I_{S1}}}\right) + \frac{V_B}{2} \end{aligned}$$

$$\begin{aligned} V_{D2} &= V_T \ln\left(\frac{I_B}{I_{S2}}\right) = V_T \ln\left(\frac{\sqrt{I_{S1} I_{S2}} \cdot \exp\left(\frac{V_B}{2V_T}\right)}{I_{S2}}\right) \\ &= V_T \ln\left(\sqrt{\frac{I_{S1}}{I_{S2}}}\right) + \frac{V_B}{2} \end{aligned}$$

18.

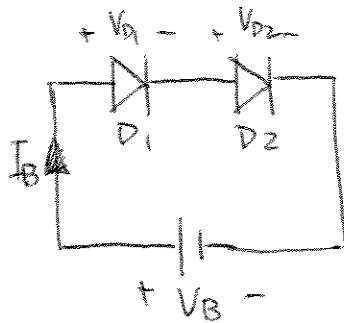

$$V_B = V_T \ln \frac{I_B}{I_{S1}} + V_T \ln \frac{I_B}{I_{S2}} = V_T \ln \left( \frac{I_B^2}{I_{S1} I_{S2}} \right)$$

$$\Rightarrow I_B = \sqrt{I_{S1} I_{S2}} \cdot \exp \frac{V_B}{2V_T}$$

Increase  $I_B$  by 10 times:

$$I_{B, \text{new}} = 10 I_B$$

$$\begin{aligned} \Rightarrow V_{B, \text{new}} &= V_T \ln \left( \frac{I_{B, \text{new}}^2}{I_{S1} I_{S2}} \right) = V_T \ln \left[ \frac{(10 I_B)^2}{I_{S1} I_{S2}} \right] \\ &= V_T \ln \left( \frac{I_B^2}{I_{S1} I_{S2}} \right) + V_T \ln 100 \\ &= V_B + V_T \ln 100 \approx V_B + 0.120 \text{ V} \end{aligned}$$

$\therefore V_B$  increases by 0.120 V.



$$\begin{aligned}
 V_X &= I_X R_1 + V_{D1} \\
 &= I_X R_1 + V_T \ln \left( \frac{I_X}{I_S} \right) \\
 I_X &= \frac{V_X}{R_1} - \frac{V_T}{R_1} \ln \left( \frac{I_X}{I_S} \right)
 \end{aligned}$$

For each value of  $V_X$ , we can solve this equation for  $I_X$  by iteration. Doing so, we find


$$\begin{aligned}
 I_X(V_X = 0.5 \text{ V}) &= 0.435 \text{ } \mu\text{A} \\
 I_X(V_X = 0.8 \text{ V}) &= 82.3 \text{ } \mu\text{A} \\
 I_X(V_X = 1 \text{ V}) &= 173 \text{ } \mu\text{A} \\
 I_X(V_X = 1.2 \text{ V}) &= 267 \text{ } \mu\text{A}
 \end{aligned}$$

Once we have  $I_X$ , we can compute  $V_D$  via the equation  $V_D = V_T \ln(I_X/I_S)$ . Doing so, we find

$$\begin{aligned}
 V_D(V_X = 0.5 \text{ V}) &= \boxed{499 \text{ mV}} \\
 V_D(V_X = 0.8 \text{ V}) &= \boxed{635 \text{ mV}} \\
 V_D(V_X = 1 \text{ V}) &= \boxed{655 \text{ mV}} \\
 V_D(V_X = 1.2 \text{ V}) &= \boxed{666 \text{ mV}}
 \end{aligned}$$

As expected,  $V_D$  varies very little despite rather large changes in  $I_D$  (in particular, as  $I_D$  experiences an increase by a factor of over 3,  $V_D$  changes by about 5%). This is due to the exponential behavior of the diode. As a result, a diode can allow very large currents to flow once it turns on, up until it begins to overheat.

20.

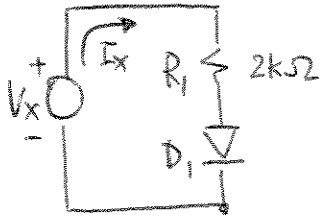

Since  $I_{s1} \propto \text{Area}$ ,  $I_{D1}$  becomes:

$$I_{D1} = \frac{10 \times (2 \cdot 10^{-15} \text{ A})}{I_{s1}'} \left( e^{\frac{V_{D1}}{V_T}} - 1 \right)$$

$V_x = 0.8 \text{ V}$  Suppose  $D_1$  is on. Assume  $V_{D1} = 0.7 \text{ V}$

$$V_{D1} = 0.7 \text{ V} \Rightarrow I_x = \frac{V_x - V_{D1}}{R_1} = \frac{0.1 \text{ V}}{2 \text{ k}\Omega} = 0.05 \text{ mA}$$

$$\begin{aligned} \Rightarrow V_{D1} &= V_T \ln\left(\frac{I_x}{I_{s1}'}\right) = (0.026 \text{ V}) \ln\left(\frac{0.05 \text{ mA}}{20 \cdot 10^{-15} \text{ A}}\right) \\ &= 0.563 \text{ V} \end{aligned}$$

$$V_{D1} = 0.563 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.563) \text{ V}}{2 \text{ k}\Omega} = 0.12 \text{ mA}$$

$$\Rightarrow V_{D1} = (0.026 \text{ V}) \ln\left(\frac{0.12 \text{ mA}}{20 \cdot 10^{-15} \text{ A}}\right) \approx 0.585 \text{ V}$$

$$V_{D1} = 0.585 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.585) \text{ V}}{2 \text{ k}\Omega} = 0.11 \text{ mA}$$

$$\Rightarrow V_{D1} = (0.026 \text{ V}) \ln\left(\frac{0.11 \text{ mA}}{20 \cdot 10^{-15} \text{ A}}\right) \approx 0.583 \text{ V}$$

$$V_{D1} = 0.583 \text{ V} \Rightarrow I_x = \frac{(0.8 - 0.583) \text{ V}}{2 \text{ k}\Omega} = 0.11 \text{ mA}$$

$$\Rightarrow V_{D1} = 0.583 \text{ V}$$

$$\therefore V_{D1} \approx 0.583 \text{ V}$$

$$I_x \approx 0.11 \text{ mA}$$

$V_x = 1.2 \text{ V}$  Suppose  $D_1$  is on. Use results from previous calculations as starting point.

$$V_{D_1} = 0.583 \text{ V} \Rightarrow I_x = \frac{(1.2 - 0.583) \text{ V}}{2 \text{ k}\Omega} = 0.31 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.31 \text{ mA}}{20 \times 10^{-15} \text{ A}}\right) \approx 0.610 \text{ V}$$

$$V_{D_1} = 0.610 \text{ V} \Rightarrow I_x = \frac{(1.2 - 0.610) \text{ V}}{2 \text{ k}\Omega} = 0.30 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.30 \text{ mA}}{20 \times 10^{-15} \text{ A}}\right) \approx 0.609 \text{ V}$$

$$V_{D_1} = 0.609 \text{ V} \Rightarrow I_x = \frac{(1.2 - 0.609) \text{ V}}{2 \text{ k}\Omega} = 0.30 \text{ mA}$$


$$\Rightarrow V_{D_1} = 0.609 \text{ V}$$

$$\therefore V_{D_1} \approx 0.609 \text{ V}$$

$$I_x \approx 0.30 \text{ mA}$$

By increasing the cross-section area of  $D_1$ , intuitively this means  $D_1$  can conduct same amount of current with less  $V_{D_1}$ . The results have shown that in this problem,  $V_{D_1}$  is less and  $I_x$  is more.

21.

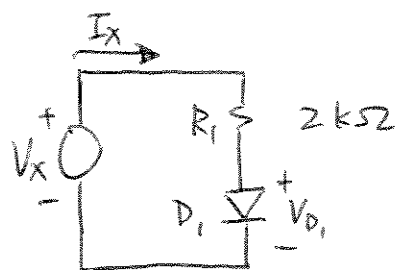Given: @  $V_x = 2V$ ,  $V_{D_1} = 850mV$ 

$$\Rightarrow I_x = \frac{V_x - V_{D_1}}{R_1} = 0.58 \text{ mA}$$

$$\begin{aligned} \therefore I_s &= \frac{I_x}{(e^{V_{D_1}/V_T} - 1)} \approx I_x \exp[-V_{D_1}/V_T] \\ &= (0.58 \text{ mA}) \exp[-0.85/0.026] \approx 3.64 \cdot 10^{-18} \text{ A} \end{aligned}$$

2.22


$$V_X/2 = I_X R_1 = V_{D1} = V_T \ln(I_X/I_S)$$

$$I_X = \frac{V_T}{R_1} \ln(I_X/I_S)$$

$$I_X = 367 \mu\text{A} \text{ (using iteration)}$$

$$\begin{aligned} V_X &= 2I_X R_1 \\ &= \boxed{1.47 \text{ V}} \end{aligned}$$

23.

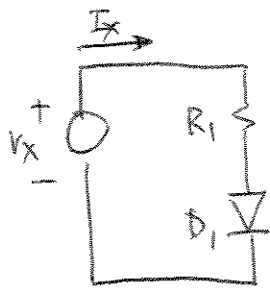

$$\text{Given } V_x = 1V \Rightarrow I_x = 0.2\text{mA}$$

$$V_x = 2V \Rightarrow I_x = 0.5\text{mA}$$

Find  $R_1$  and  $I_s$ .

$$\text{By KVL, } V_{D_1} = V_x - I_x R_1 = V_T \ln\left(\frac{I_x}{I_s}\right)$$

$$\Rightarrow 1 - (0.2\text{mA})R_1 = (0.026\text{V}) \ln\left(\frac{0.2\text{mA}}{I_s}\right) \quad \text{--- (1)}$$

$$2 - (0.5\text{mA})R_1 = (0.026\text{V}) \ln\left(\frac{0.5\text{mA}}{I_s}\right) \quad \text{--- (2)}$$

$$\text{(2) - (1) : } 1 - (0.3\text{mA})R_1 = (0.026\text{V}) \ln\left(\frac{0.5}{0.2}\right)$$

$$\Rightarrow R_1 = \frac{1 - (0.026) \ln\left(\frac{0.5}{0.2}\right)}{0.3\text{mA}} = 3.25\text{ k}\Omega$$

Substitute  $R_1$  into (1):

$$I_s = I_x \cdot \exp\left[-\frac{V_x - I_x R_1}{V_T}\right]$$


$$= (0.2\text{mA}) \exp\left[-\frac{1 - (0.2\text{mA})(3.25\text{k})}{0.026}\right] \approx 2.94 \cdot 10^{-10}\text{A}$$

$$\therefore R_1 \approx 3.25\text{ k}\Omega$$

$$I_s \approx 2.94 \cdot 10^{-10}\text{A}$$

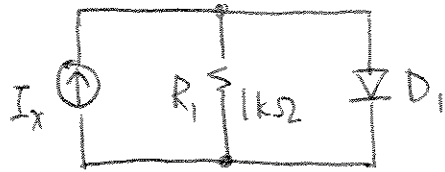24.

Given  $I_s = 3 \cdot 10^{-16} \text{ A}$ ,  
find  $V_{D_1}$ .



$$\text{By KCL, } I_x = \frac{V_{D_1}}{R_1} + I_{D_1} = \frac{V_T}{R_1} \ln\left(\frac{I_{D_1}}{I_s}\right) + I_{D_1}$$

Since  $I_x$ ,  $V_T$ ,  $R_1$  and  $I_s$  are known, this can be solved directly with special programs or graphing calculators. However, this can be also solved by iterations. Assume a  $V_{D_1}$ , calculate  $I_{D_1}$ , and re-iterate on  $V_{D_1}$ .

Assume  $V_{D_1} = 0.7 \text{ V}$  as starting point.

$$\boxed{I_x = 1 \text{ mA}}$$

$$V_{D_1} = 0.7 \text{ V} \Rightarrow I_{D_1} = I_x - \frac{V_{D_1}}{R_1} = 1 \text{ mA} - \frac{0.7 \text{ V}}{1 \text{ k}\Omega} = 0.3 \text{ mA}$$

$$\begin{aligned} \Rightarrow V_{D_1} &= V_T \ln\left(\frac{I_x}{I_s}\right) \\ &= (0.026 \text{ V}) \ln\left(\frac{0.3 \text{ mA}}{3 \cdot 10^{-16} \text{ A}}\right) \approx 0.718 \text{ V} \end{aligned}$$

$$V_{D_1} = 0.718 \text{ V} \Rightarrow I_{D_1} = 1 \text{ mA} - \frac{0.718 \text{ V}}{1 \text{ k}\Omega} = 0.28 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln\left(\frac{0.28 \text{ mA}}{3 \cdot 10^{-16} \text{ A}}\right) \approx 0.717 \text{ V}$$

$$V_{D_1} = 0.717 \text{ V} \Rightarrow I_{D_1} = 1 \text{ mA} - \frac{0.717 \text{ V}}{1 \text{ k}\Omega} = 0.28 \text{ mA}$$

$$\Rightarrow V_{D_1} = 0.717 \text{ V}$$

$$\therefore V_{D_1} \approx 0.717 \text{ V.}$$

$I_X = 2 \text{ mA}$  Assume  $V_{D_1} = 0.717 \text{ V}$  from previous result.

$$V_{D_1} = 0.717 \text{ V} \Rightarrow I_{D_1} = 2 \text{ mA} - \frac{0.717 \text{ V}}{1 \text{ k}\Omega} = 1.28 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln \left( \frac{1.28 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.756 \text{ V}$$

$$V_{D_1} = 0.756 \text{ V} \Rightarrow I_{D_1} = 2 \text{ mA} - \frac{0.756 \text{ V}}{1 \text{ k}\Omega} = 1.24 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln \left( \frac{1.24 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.755 \text{ V}$$

$$V_{D_1} = 0.755 \text{ V} \Rightarrow I_{D_1} = 2 \text{ mA} - \frac{0.755 \text{ V}}{1 \text{ k}\Omega} = 1.24 \text{ mA}$$

$$\Rightarrow V_{D_1} = 0.755 \text{ V}$$

$$\therefore V_{D_1} = 0.755 \text{ V}$$



$I_x = 4 \text{ mA}$  Assume  $V_{D_1} = 0.755 \text{ V}$  from previous result.

$$V_{D_1} = 0.755 \text{ V} \Rightarrow I_{D_1} = 4 \text{ mA} - \frac{0.755 \text{ V}}{1 \text{ k}\Omega} = 3.25 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln \left( \frac{3.25 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.780 \text{ V}$$


$$V_{D_1} = 0.780 \text{ V} \Rightarrow I_{D_1} = 4 \text{ mA} - \frac{0.780 \text{ V}}{1 \text{ k}\Omega} = 3.22 \text{ mA}$$

$$\Rightarrow V_{D_1} = (0.026 \text{ V}) \ln \left( \frac{3.22 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.780 \text{ V}$$

$\therefore V_{D_1} \approx 0.780 \text{ V}$ .

Note: As  $I_x$  increases,  $I_{D_1}$  increases, while  $(V_{D_1}/R_1)$  stays relatively the same. Because of the exponential characteristic, the diode, once on, will absorb as much current as necessary to satisfy KCL.

25.

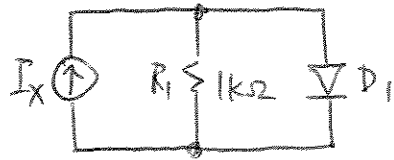


Given  $I_{D_1} = 0.5 \text{ mA}$  when  $I_x = 1.3 \text{ mA}$ , find  $I_s$ .

$$\begin{aligned} \text{This means } V_{D_1} &= (I_x - I_{D_1}) R_1 \\ &= (0.8 \text{ mA}) 1k\Omega = 0.8 \text{ V} \end{aligned}$$

$$\begin{aligned} \Rightarrow I_s &= I_{D_1} \cdot \exp[-V_{D_1}/V_T] \\ &= (0.5 \text{ mA}) \exp[-0.8 \text{ V}/0.026 \text{ V}] \\ &\approx 2.17 \cdot 10^{-17} \text{ A} \end{aligned}$$

26

Given  $I_{R_1} = I_x/2$   
 $I_s = 3 \cdot 10^{-16} \text{ A}$

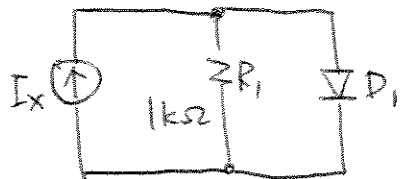find  $I_x$ .

$$V_{D_1} = \frac{I_x}{2} \cdot R_1 = V_T \ln \left( \frac{I_x/2}{I_s} \right)$$

This can be solved directly with special programs or graphing calculators. Alternatively, one can solve this iteratively by hand.

Assume  $V_D = 0.8 \text{ V}$ .

$$V_D = 0.8 \text{ V} \Rightarrow \left( \frac{I_x}{2} \right) = \frac{V_D}{R_1} = \frac{0.8 \text{ V}}{1 \text{ k}\Omega} = 0.8 \text{ mA}$$

$$\Rightarrow V_D = V_T \ln \left( \frac{I_x/2}{I_s} \right) = (0.026 \text{ V}) \ln \left( \frac{0.8 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right)$$

$$\approx 0.744 \text{ V}$$

$$V_D = 0.744 \text{ V} \Rightarrow \frac{I_x}{2} = \frac{0.744 \text{ V}}{1 \text{ k}\Omega} = 0.744 \text{ mA}$$


$$\Rightarrow V_D = (0.026 \text{ V}) \ln \left( \frac{0.744 \text{ mA}}{3 \cdot 10^{-16} \text{ A}} \right) \approx 0.742 \text{ V}$$

$$V_D = 0.742V \Rightarrow I_x/2 = \frac{0.742V}{1k\Omega} = 0.742 \text{ mA}$$

$$\Rightarrow V_D = (0.026V) \ln\left(\frac{0.742 \text{ mA}}{3 \cdot 10^{-16} \text{ A}}\right) \approx 0.742V$$

$$\therefore I_x = 2(0.742 \text{ mA}) = 1.48 \text{ mA}$$

27.

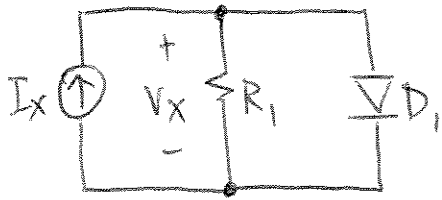

Given  $I_x = 1\text{mA} \rightarrow V_x = 1.2\text{V}$   
 $I_x = 2\text{mA} \rightarrow V_x = 1.8\text{V}$

find  $R_1$  and  $I_s$ .

$$I_{D_1} = I_x - V_x/R_1 \quad (\text{KCL})$$

$$\text{By KVL, } V_x = V_T \ln\left(\frac{I_{D_1}}{I_s}\right) = V_T \ln\left(\frac{I_x - V_x/R_1}{I_s}\right)$$

$$\Rightarrow (1.2\text{V}) = (0.026\text{V}) \ln\left[\frac{(1\text{mA}) - (1.2\text{V})/R_1}{I_s}\right] \quad \text{--- ①}$$

$$(1.8\text{V}) = (0.026\text{V}) \ln\left[\frac{(2\text{mA}) - (1.8\text{V})/R_1}{I_s}\right] \quad \text{--- ②}$$


$$\text{②} - \text{①}: 0.6\text{V} = (0.026\text{V}) \ln\left(\frac{2\text{mA} - 1.8\text{V}/R_1}{1\text{mA} - 1.2\text{V}/R_1}\right)$$

$$\Rightarrow R_1 = \frac{1.2 \cdot \exp\left[\frac{0.6}{0.026}\right] - 1.8}{1\text{mA} \cdot \exp\left[\frac{0.6}{0.026}\right] - 2\text{mA}} \approx 1.2\text{ k}\Omega$$

$$I_s = I_D \exp\left[-\frac{V_x}{V_T}\right] = \left(2\text{mA} - \frac{1.8\text{V}}{1.2\text{k}\Omega}\right) \exp\left[-\frac{1.8\text{V}}{0.026\text{V}}\right]$$

$$\approx 4.29 \cdot 10^{-34}\text{ A.}$$

28.

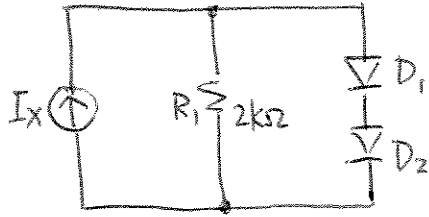

Given  $D_1 = D_2$  with  
 $I_s = 5 \cdot 10^{-16} \text{ A}$

Find  $V_{R_1}$  for  $I_x = 2 \text{ mA}$ .

Current through the diodes =  $I_D$   
 $= I_x - \frac{V_{R_1}}{R_1}$  where  $V_{R_1}$  = voltage across  $R_1$

$$\Rightarrow V_{R_1} = 2 \cdot V_T \ln\left(\frac{I_D}{I_s}\right) = 2 \left[ V_T \ln\left(\frac{I_x}{I_s} - \frac{V_{R_1}}{I_s R_1}\right) \right]$$

This can be solved directly with special programs or graphing calculators or by hand iteratively.

Assume a  $V_{R_1}$ , calculate  $I_D$ , and re-iterate on new  $V_{R_1} = (2 \times V_{D_1})$ . From experience, most diodes conduct at  $V_D \approx 0.7 \text{ V}$ . Assume  $V_{R_1} = 1.4 \text{ V}$ .

$$V_{R_1} = 1.4 \text{ V} \Rightarrow I_D = I_x - \frac{V_{R_1}}{R_1} = 2 \text{ mA} - \frac{1.4 \text{ V}}{2 \text{ k}\Omega} = 1.3 \text{ mA}$$

$$\Rightarrow V_{R_1} = 2 V_T \ln\left(\frac{I_D}{I_s}\right)$$

$$= 2(0.026 \text{ V}) \ln\left(\frac{1.3 \text{ mA}}{5 \cdot 10^{-16} \text{ A}}\right) \approx 1.49 \text{ V}$$

$$V_{R_1} = 1.49V \Rightarrow I_D = 2mA - \frac{1.49}{2k\Omega} = 1.26mA$$


$$\Rightarrow V_{R_1} = 2(0.026V) \ln\left(\frac{1.26mA}{5 \cdot 10^{-16}A}\right) \approx 1.48V$$

$$V_{R_1} = 1.48V \Rightarrow I_D = 2mA - \frac{1.48V}{2k\Omega} = 1.26mA$$

$$\Rightarrow V_{R_1} = 1.48V$$

∴ voltage across  $R_1 = 1.48V$

29.

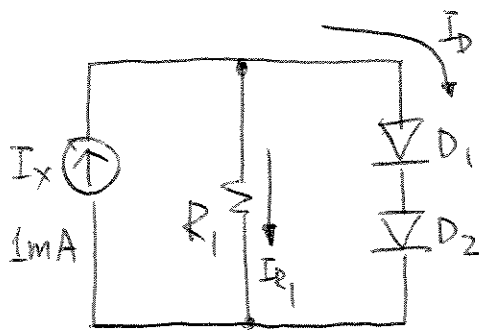

Given  $I_{R_1} = 0.5\text{ mA}$ ,  
 $I_s = 5 \cdot 10^{-16}\text{ A}$  for  
 each diode.

Find  $R_1$ .

$$\text{By KCL, } I_D = I_x - I_{R_1} = 0.5\text{ mA}$$


$$\Rightarrow V_{D_1} = V_{D_2} = V_T \ln\left(\frac{I_D}{I_s}\right) = 0.026 \ln\left(\frac{0.5\text{ mA}}{5 \cdot 10^{-16}\text{ A}}\right)$$

$$\approx 0.718\text{ V}$$

$$\therefore R_1 = \frac{V_{R_1}}{I_{R_1}} = \frac{2V_{D_1}}{I_{R_1}} = \frac{2(0.718\text{ V})}{0.5\text{ mA}} = 2.87\text{ k}\Omega$$




30.

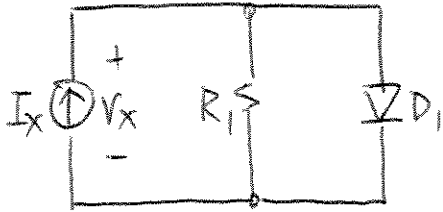

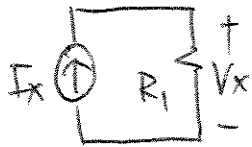
(a) Constant-voltage model:

Consider, first, the extreme cases: when  $D_1$  is off, we have the following:




This implies  $V_x$  is linearly proportional to  $I_x$

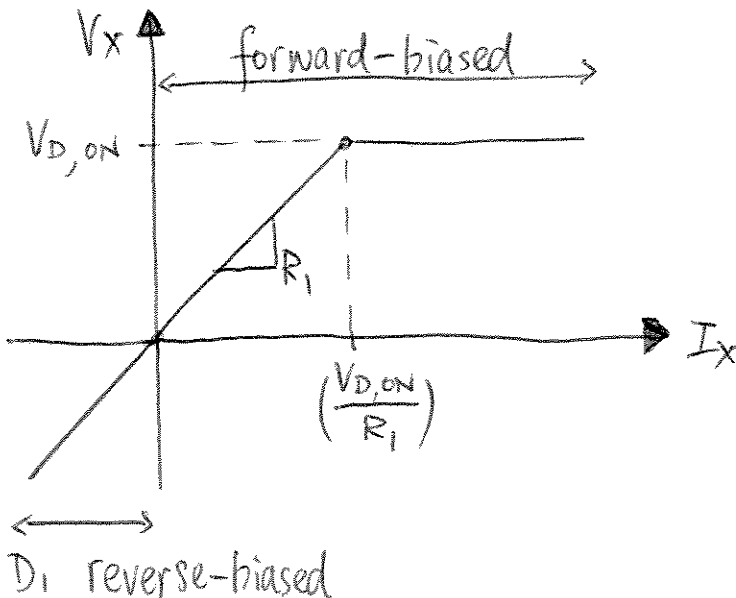When  $D_1$  is on,  $V_x$  is fixed (by KVL) by  $D_1$  ( $= V_{D,ON}$ ). This implies that any additional current from  $I_x$  cannot flow through  $R_1$ , which means  $D_1$  will absorb all the currents to satisfy KVL.



(b) exponential model :

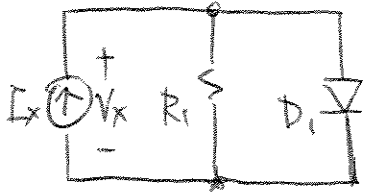

Assume  $I_s$  negligible.


When  $D_1$  is off, most of  $I_x$  flows through  $R_1$ . When  $D_1$  is on,  $V_{D_1}$  ( $= V_x$ ) follows this relationship:

$$V_{D_1} = V_x = V_T \ln\left(\frac{I_{D_1}}{I_s}\right) = V_T \ln\left(\frac{I_x - \frac{V_x}{R_1}}{I_s}\right)$$

$$\Rightarrow I_x = I_s \exp(V_x/V_T) + V_x/R_1$$


$$\approx I_s \exp(V_x/V_T) \quad \text{when } D_1 \text{ is forward-biased } (V_x > V_T)$$

i.e.  $V_x \approx V_T \ln(I_x/I_s)$

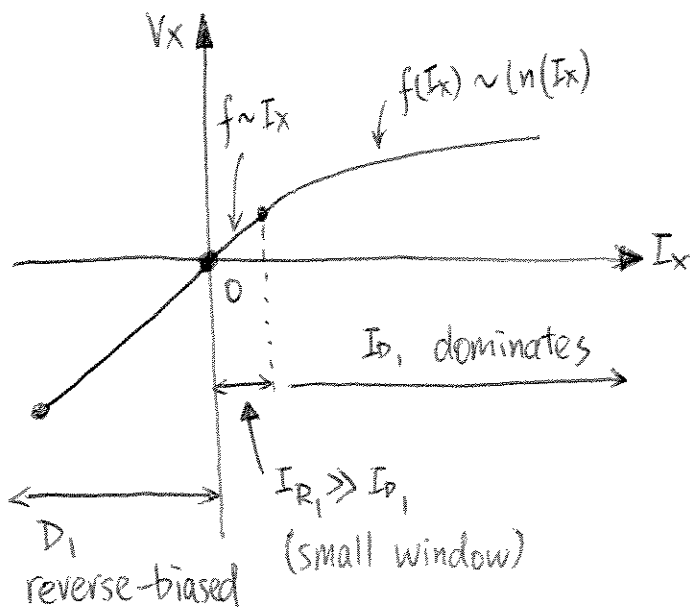

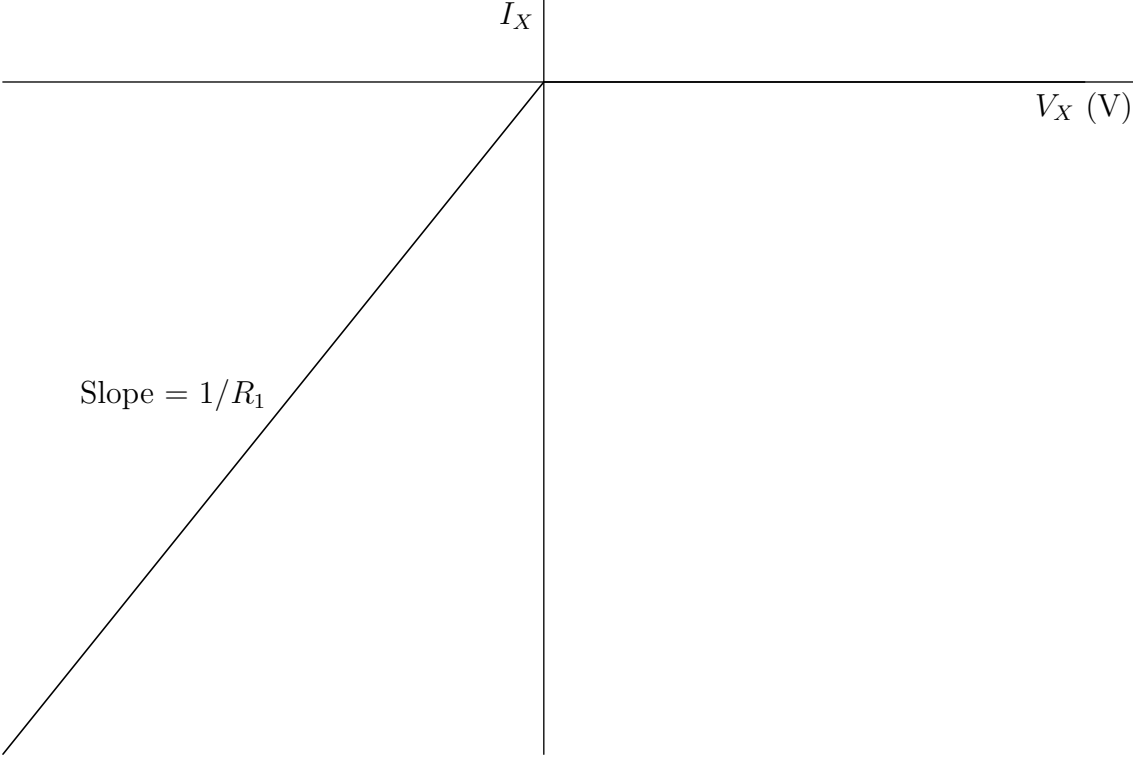3.1 (a)


$$I_X = \begin{cases} \frac{V_X}{R_1} & V_X < 0 \\ 0 & V_X > 0 \end{cases}$$



3.2

$$I_X = \begin{cases} \frac{V_X}{R_1} & V_X < 0 \\ 0 & V_X > 0 \end{cases}$$


Plotting  $I_X(t)$ , we have

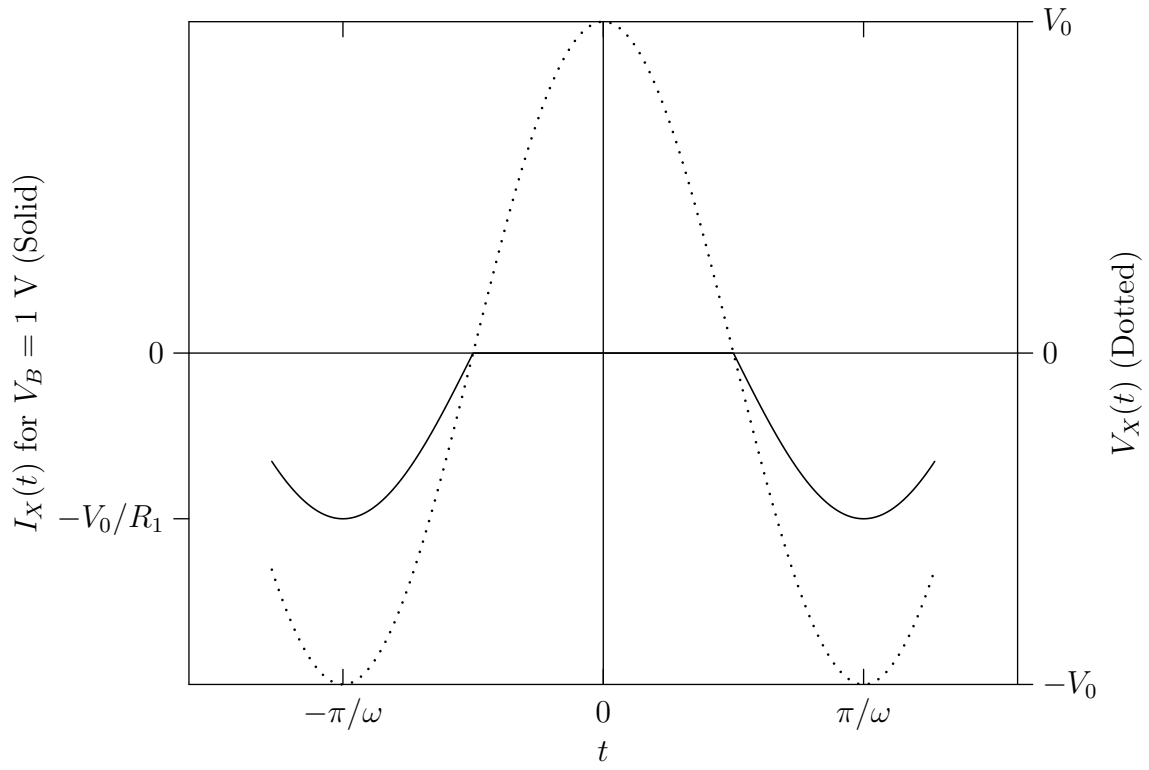

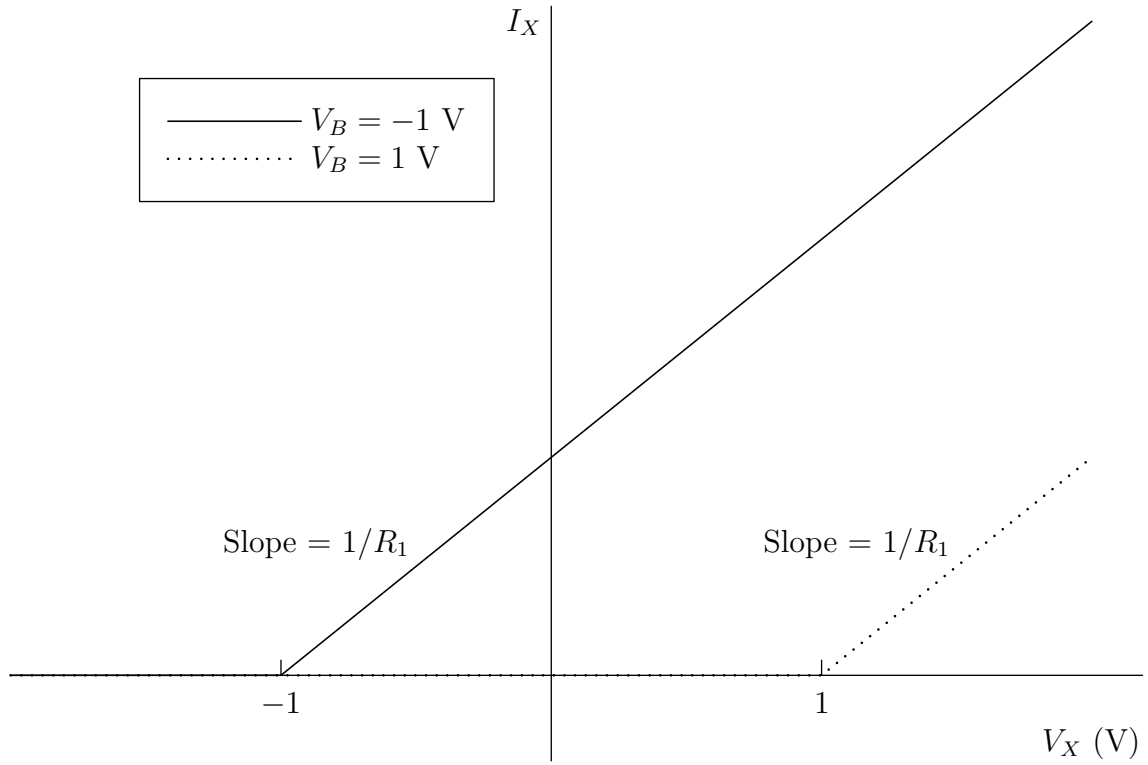3.3

$$I_X = \begin{cases} 0 & V_X < V_B \\ \frac{V_X - V_B}{R_1} & V_X > V_B \end{cases}$$


Plotting  $I_X$  vs.  $V_X$  for  $V_B = -1$  V and  $V_B = 1$  V, we get:



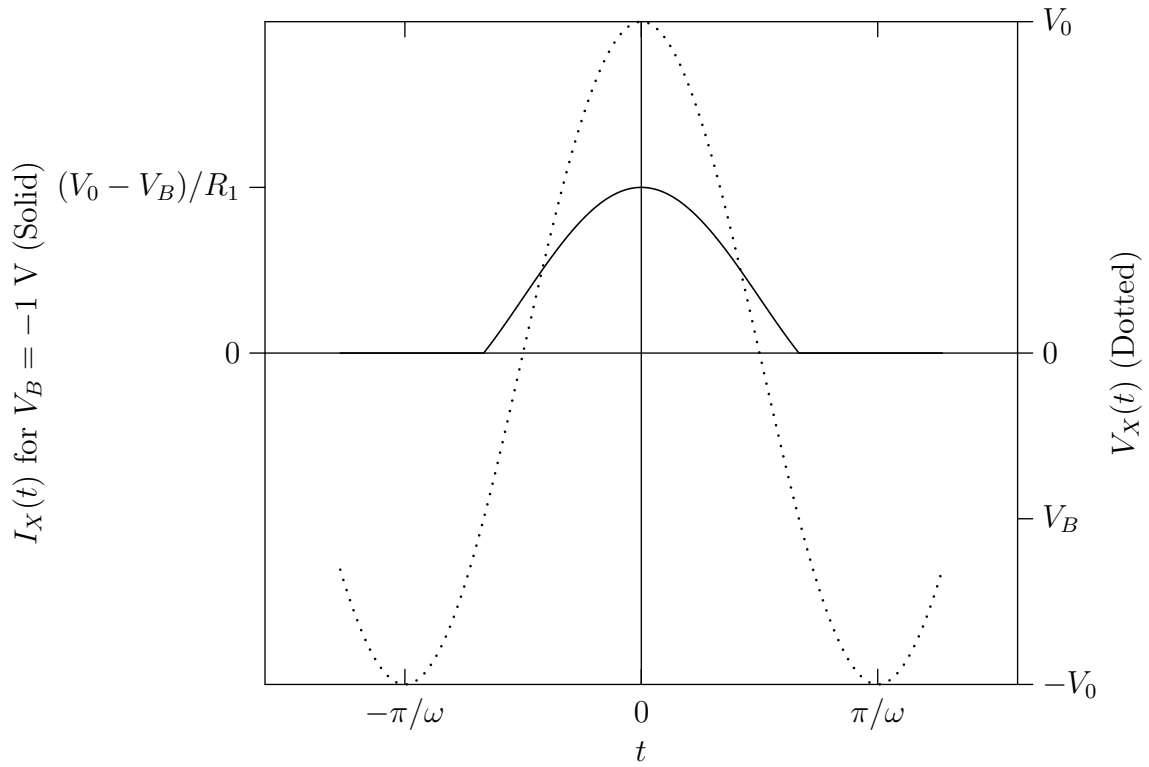
3.4

$$I_X = \begin{cases} 0 & V_X < V_B \\ \frac{V_X - V_B}{R_1} & V_X > V_B \end{cases}$$

Let's assume  $V_0 > 1$  V. Plotting  $I_X(t)$  for  $V_B = -1$  V, we get



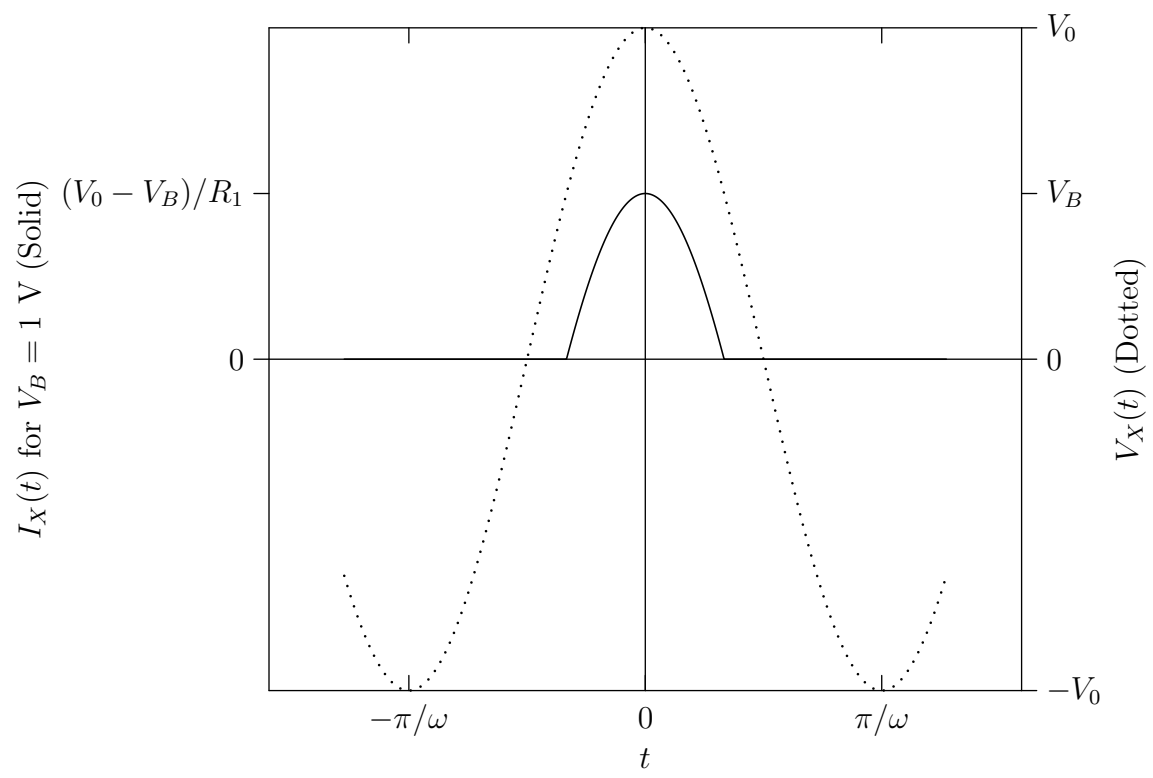
Plotting  $I_X(t)$  for  $V_B = 1$  V, we get



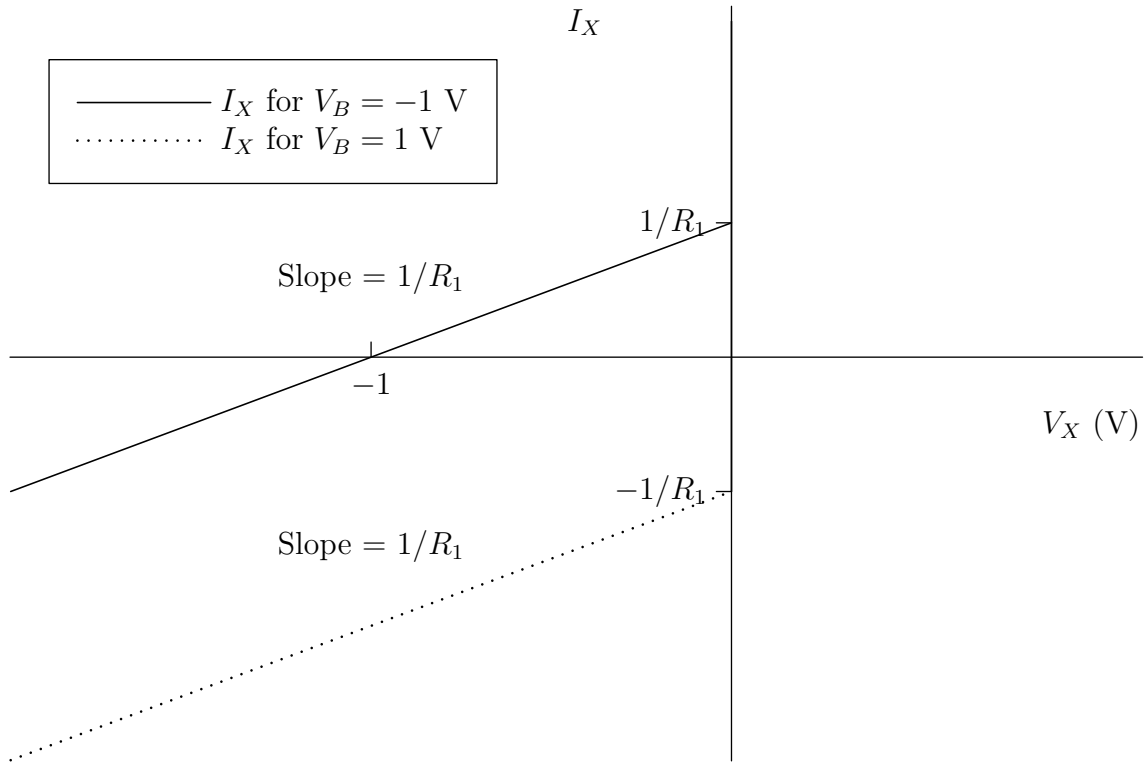3.5

$$I_X = \begin{cases} \frac{V_X - V_B}{R_1} & V_X < 0 \\ \infty & V_X > 0 \end{cases}$$

Plotting  $I_X$  vs.  $V_X$  for  $V_B = -1$  V and  $V_B = 1$  V, we get:






3.6 First, note that  $I_{D1} = 0$  always, since  $D_1$  is reverse biased by  $V_B$  (due to the assumption that  $V_B > 0$ ). We can write  $I_X$  as

$$I_X = (V_X - V_B)/R_1$$

Plotting this, we get:

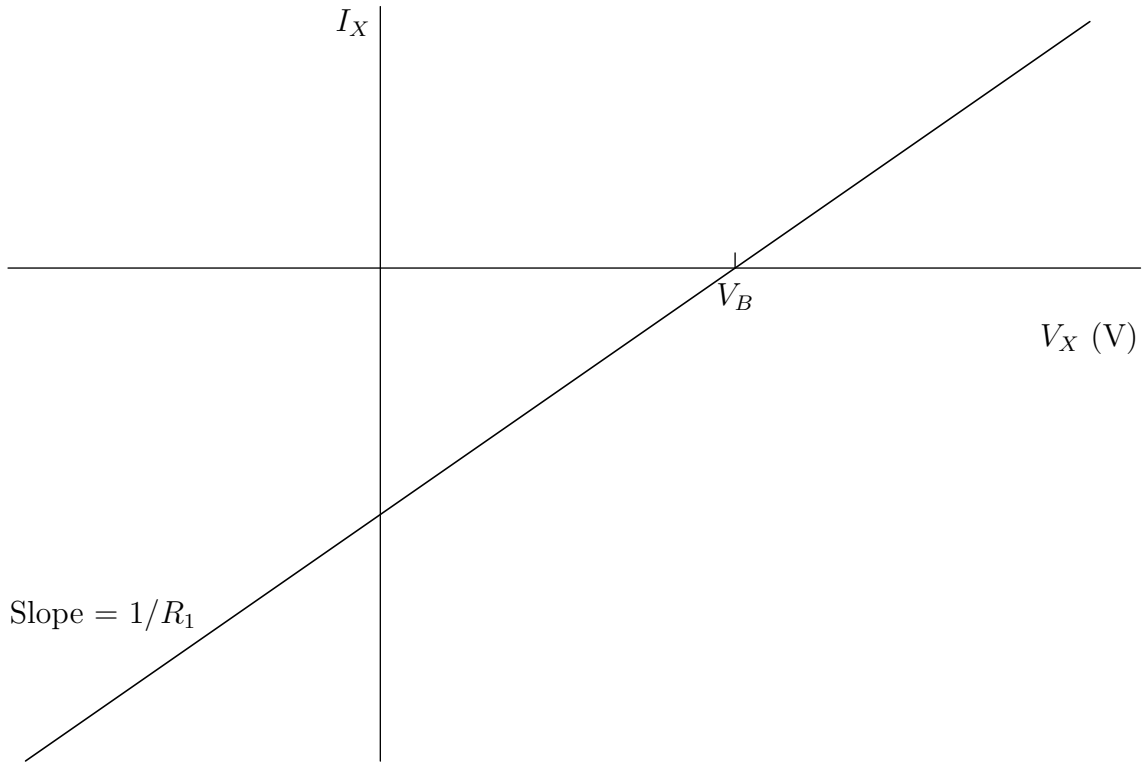


3.7


$$I_X = \begin{cases} \frac{V_X - V_B}{R_1} & V_X < V_B \\ \frac{V_X - V_B}{R_1 \parallel R_2} & V_X > V_B \end{cases}$$

$$I_{R1} = \frac{V_X - V_B}{R_1}$$

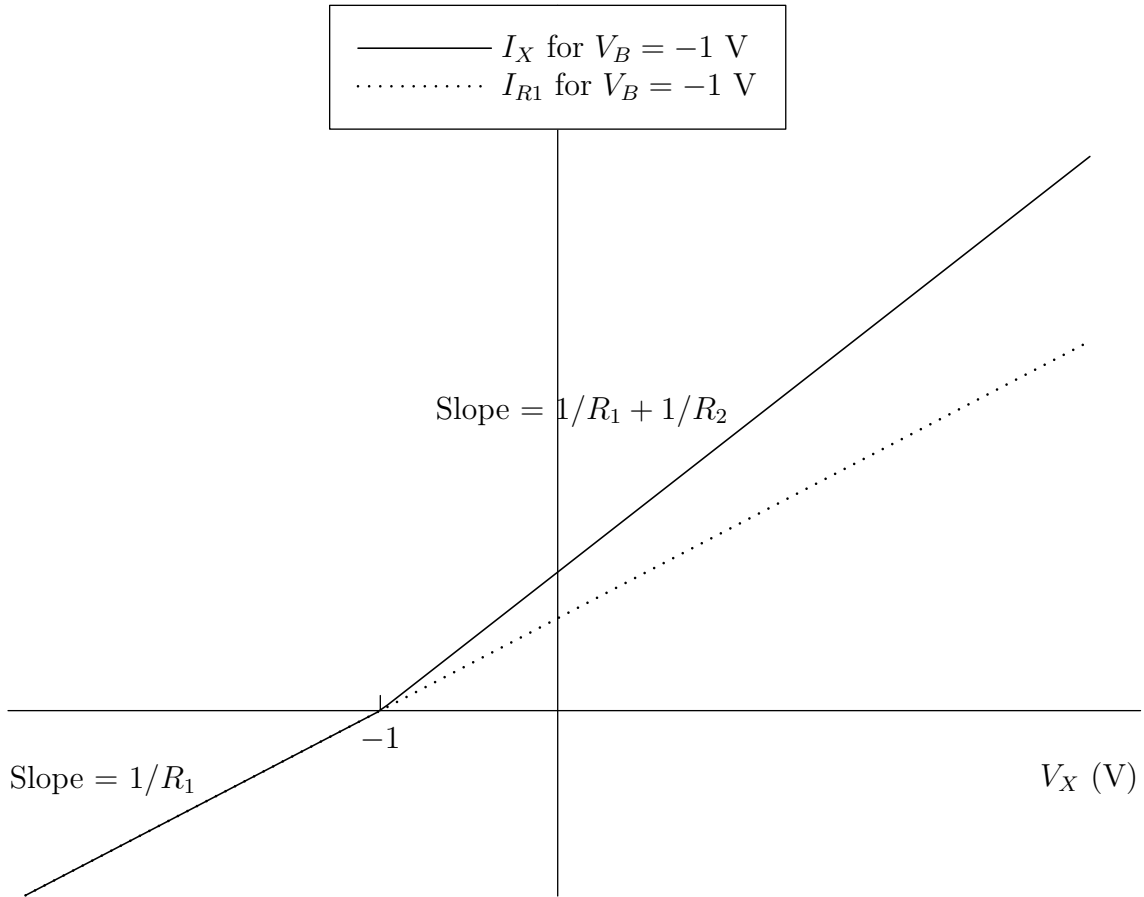Plotting  $I_X$  and  $I_{R1}$  for  $V_B = -1$  V, we get:



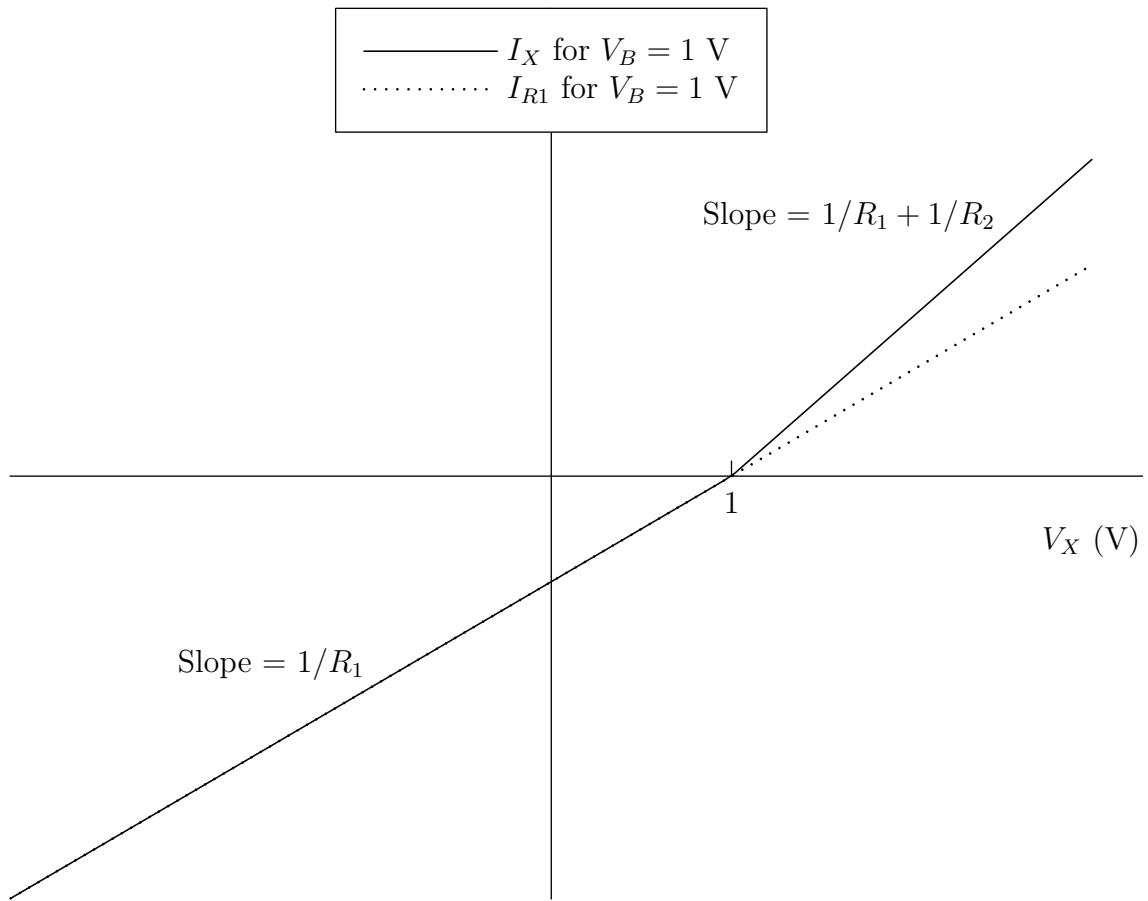Plotting  $I_X$  and  $I_{R1}$  for  $V_B = 1$  V, we get:




3.8


$$I_X = \begin{cases} 0 & V_X < \frac{V_B}{R_1+R_2} R_1 \\ \frac{V_X}{R_1} + \frac{V_X-V_B}{R_2} & V_X > \frac{V_B}{R_1+R_2} R_1 \end{cases}$$

$$I_{R1} = \begin{cases} \frac{V_B}{R_1+R_2} & V_X < \frac{V_B}{R_1+R_2} R_1 \\ \frac{V_X}{R_1} & V_X > \frac{V_B}{R_1+R_2} R_1 \end{cases}$$

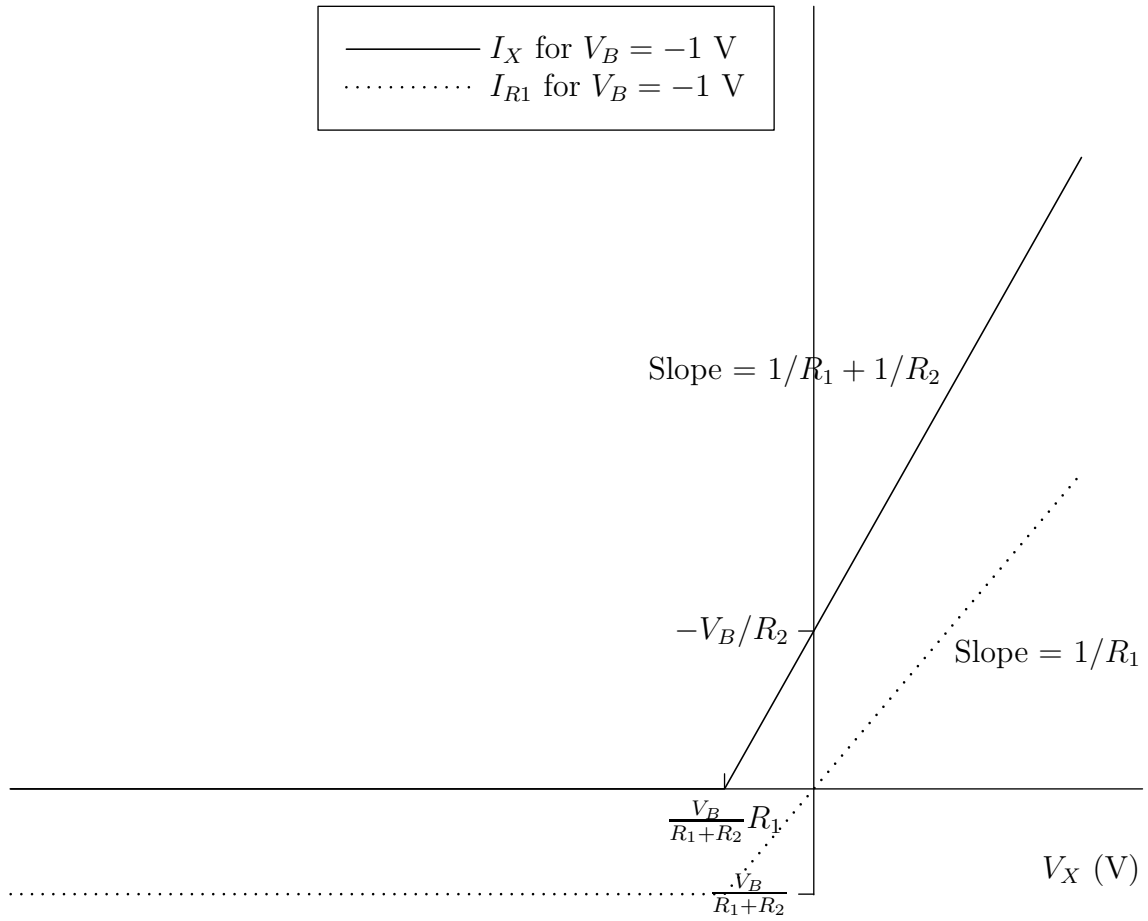Plotting  $I_X$  and  $I_{R1}$  for  $V_B = -1$  V, we get:




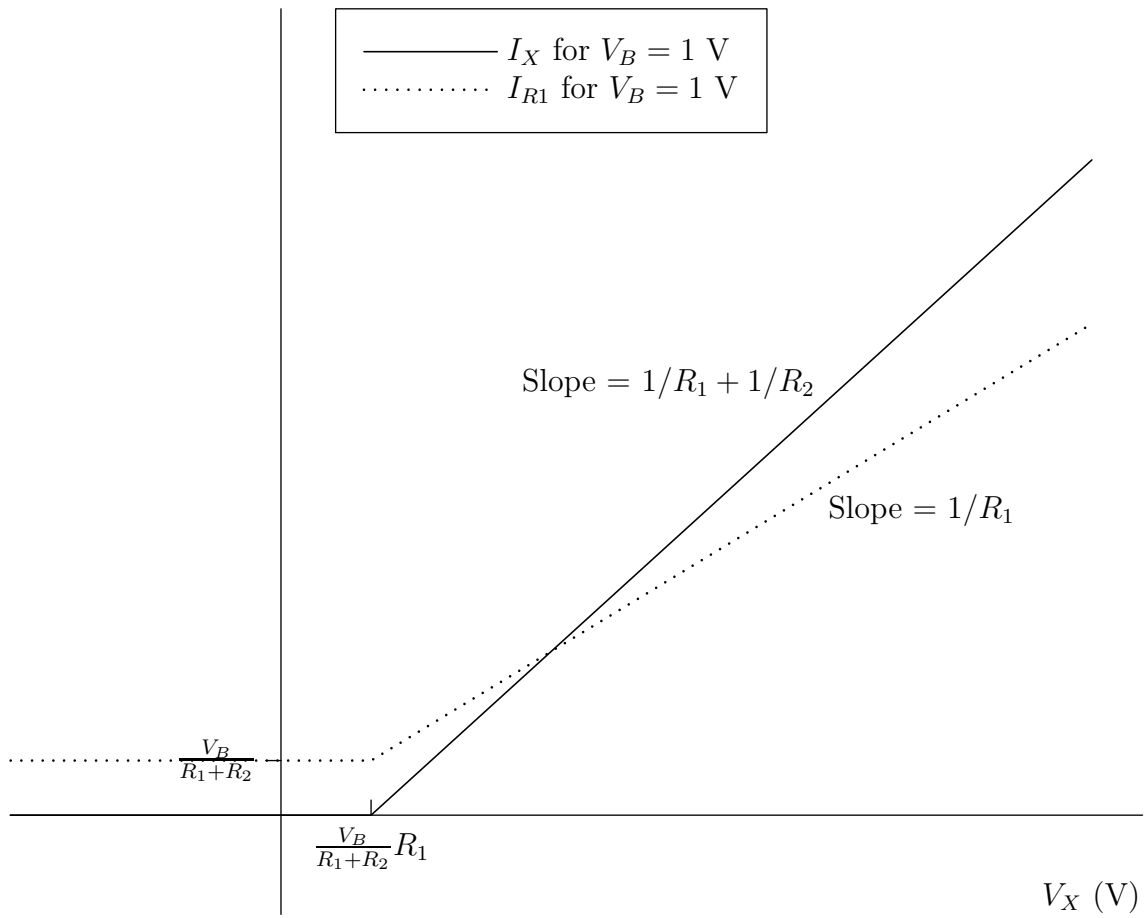Plotting  $I_X$  and  $I_{R1}$  for  $V_B = 1$  V, we get:



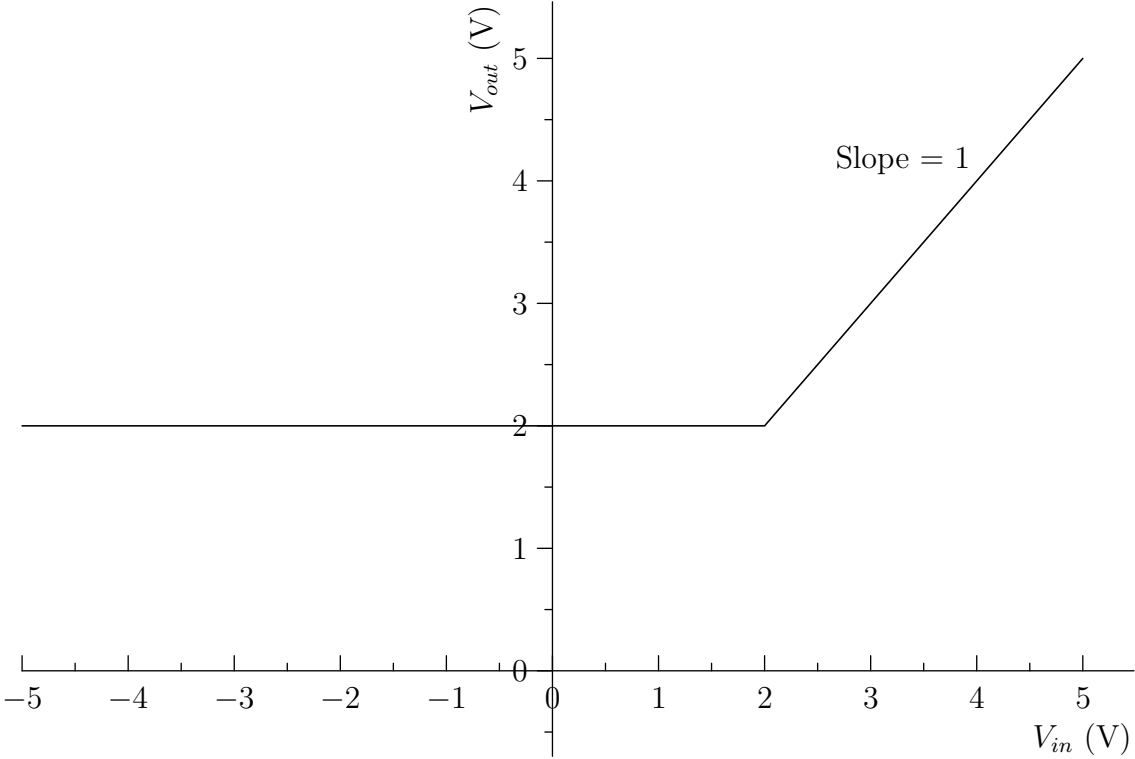
3.9 (a)

$$V_{out} = \begin{cases} V_B & V_{in} < V_B \\ V_{in} & V_{in} > V_B \end{cases}$$




(b)
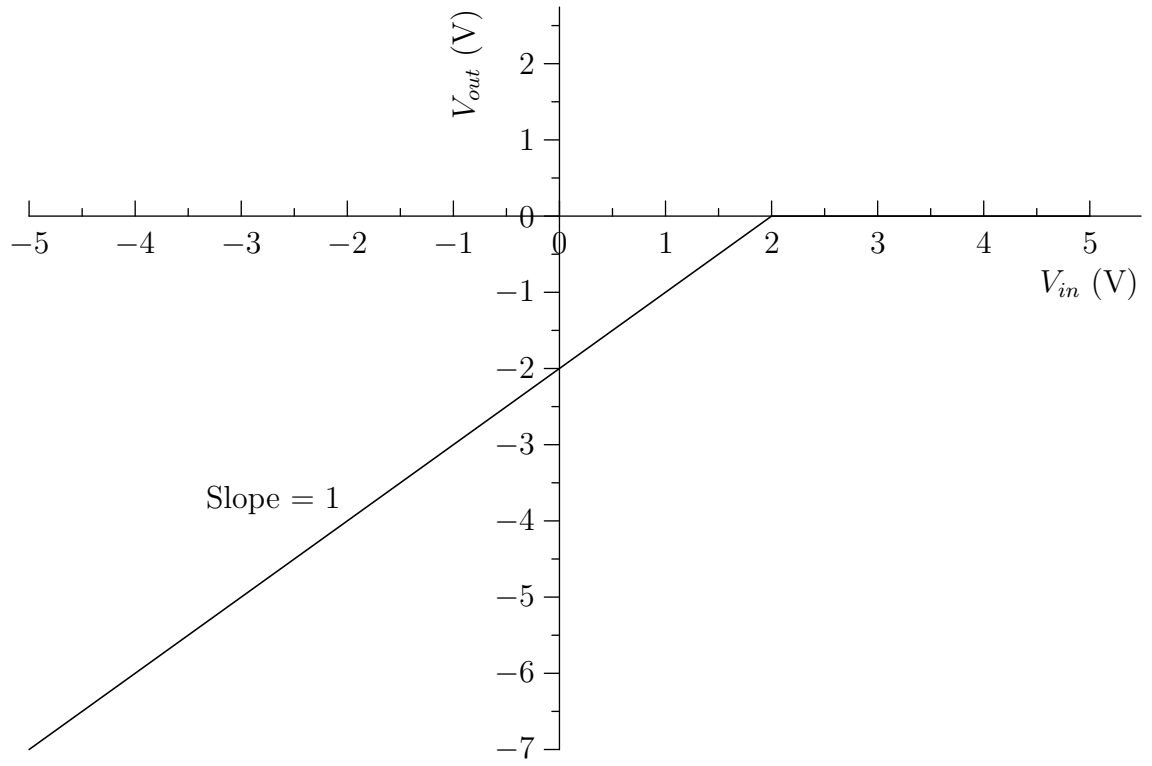
$$V_{out} = \begin{cases} V_{in} - V_B & V_{in} < V_B \\ 0 & V_{in} > V_B \end{cases}$$




(c)

$$V_{out} = V_{in} - V_B$$

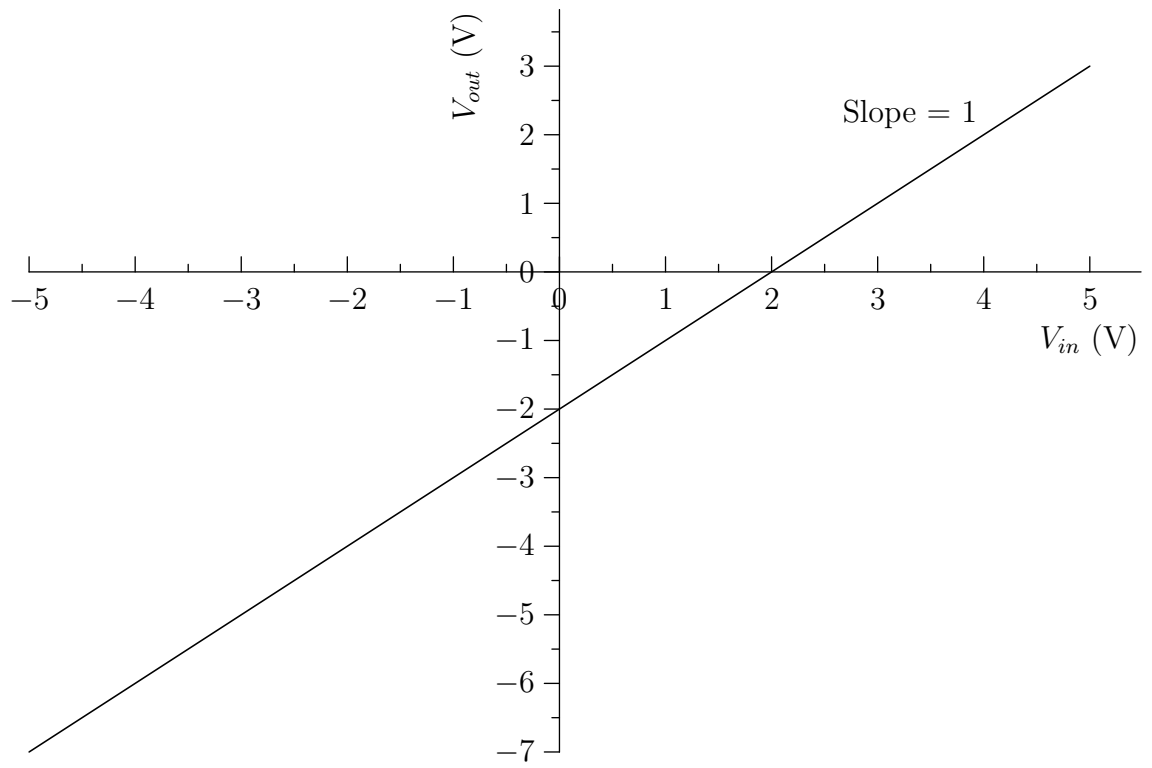

(d)

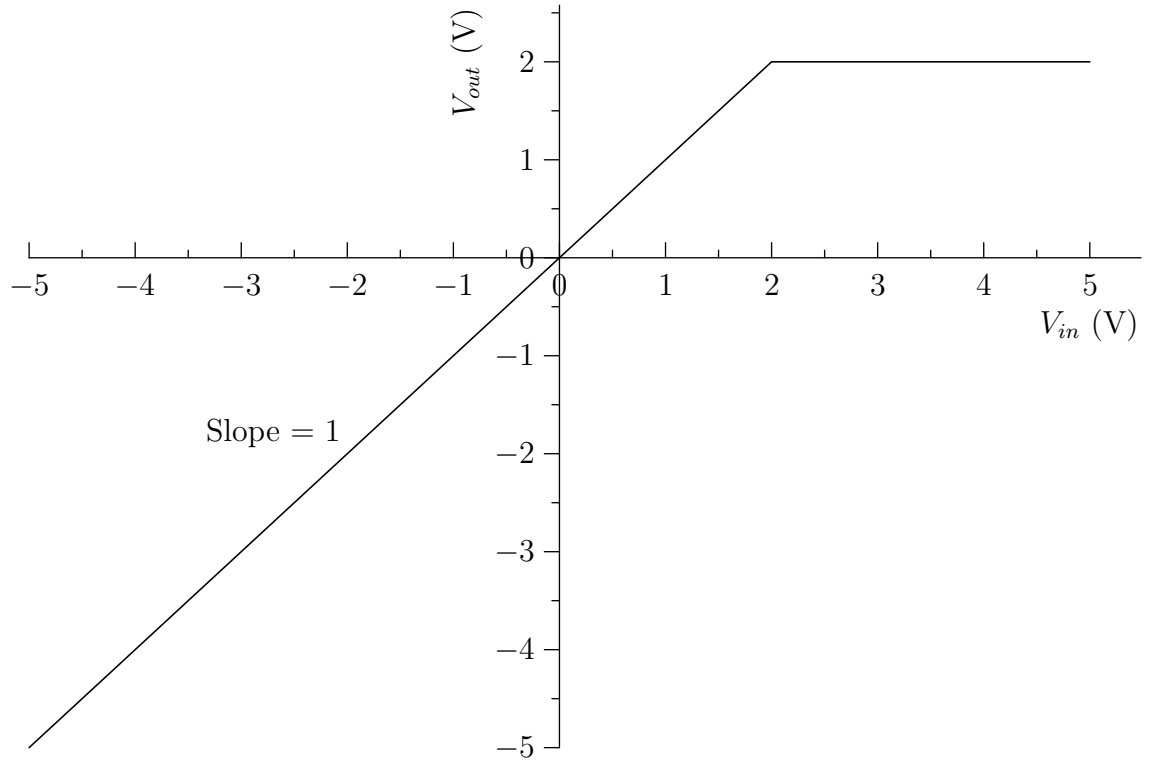
$$V_{out} = \begin{cases} V_{in} & V_{in} < V_B \\ V_B & V_{in} > V_B \end{cases}$$




(e)
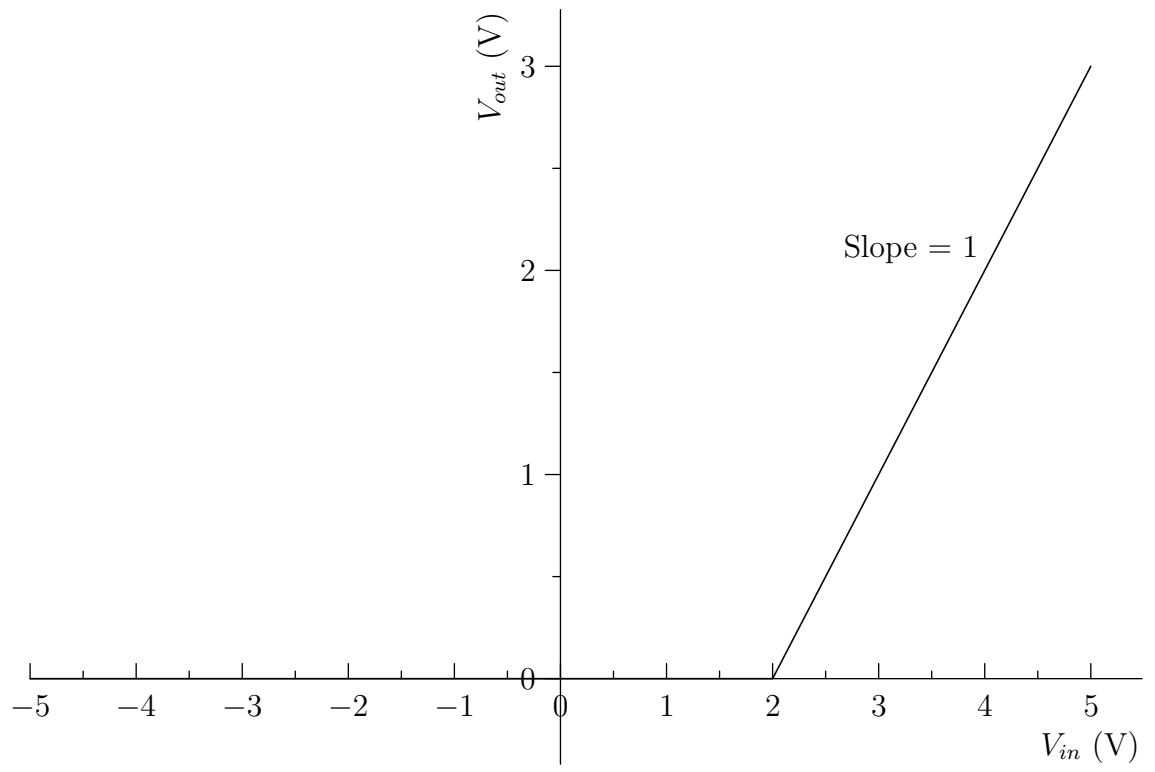
$$V_{out} = \begin{cases} 0 & V_{in} < V_B \\ V_{in} - V_B & V_{in} > V_B \end{cases}$$







(10) a/

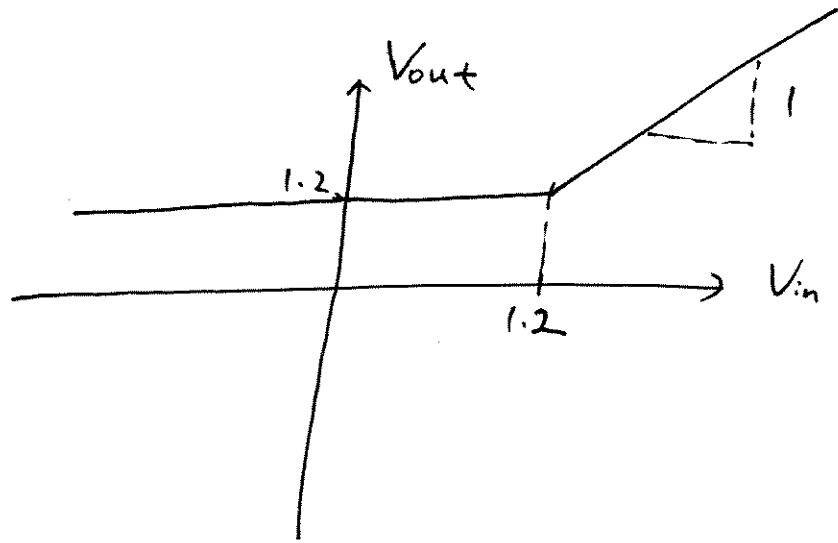


b/

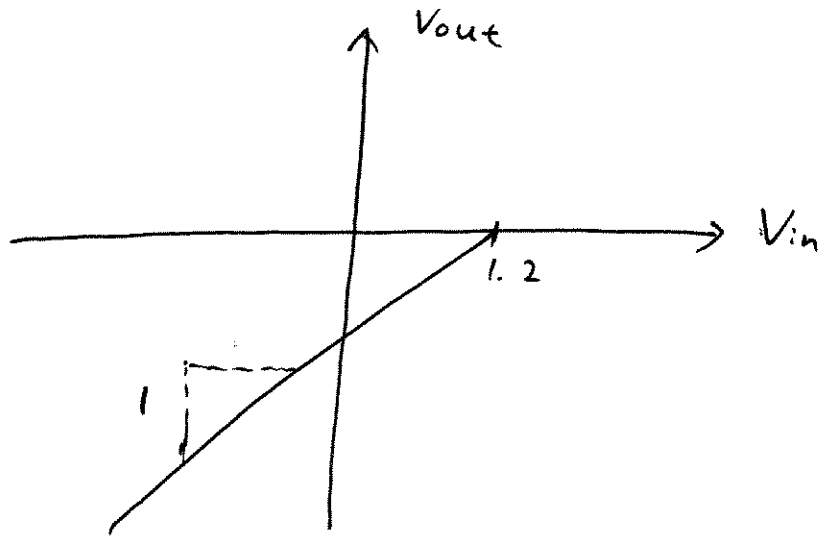


c/

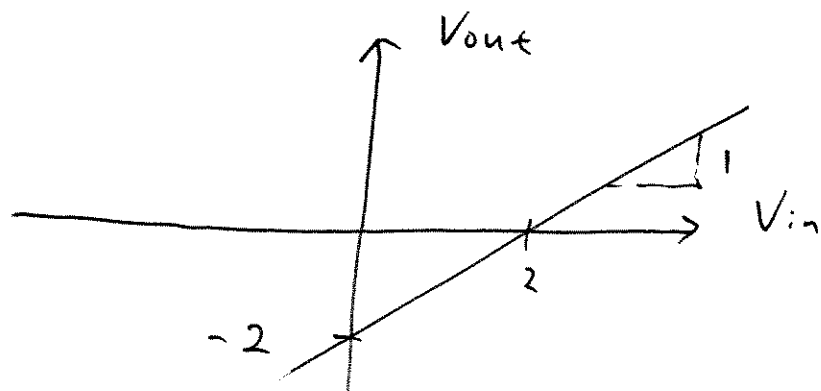

d)

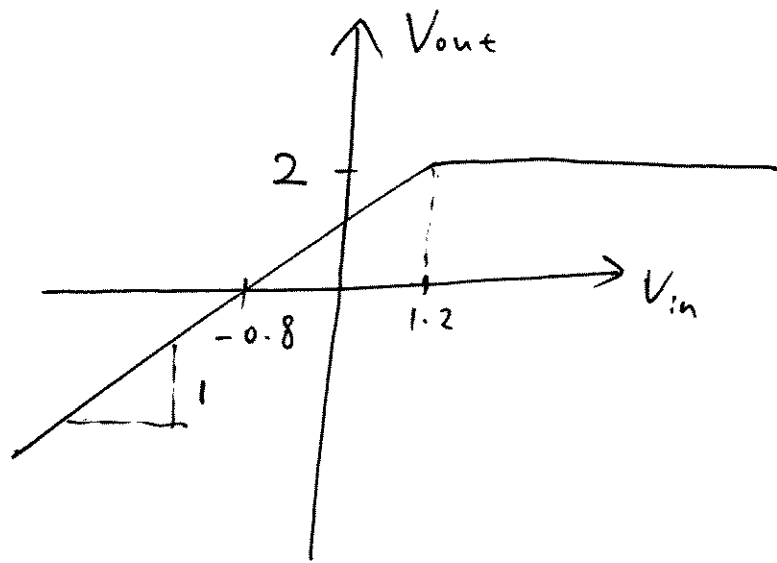


e)

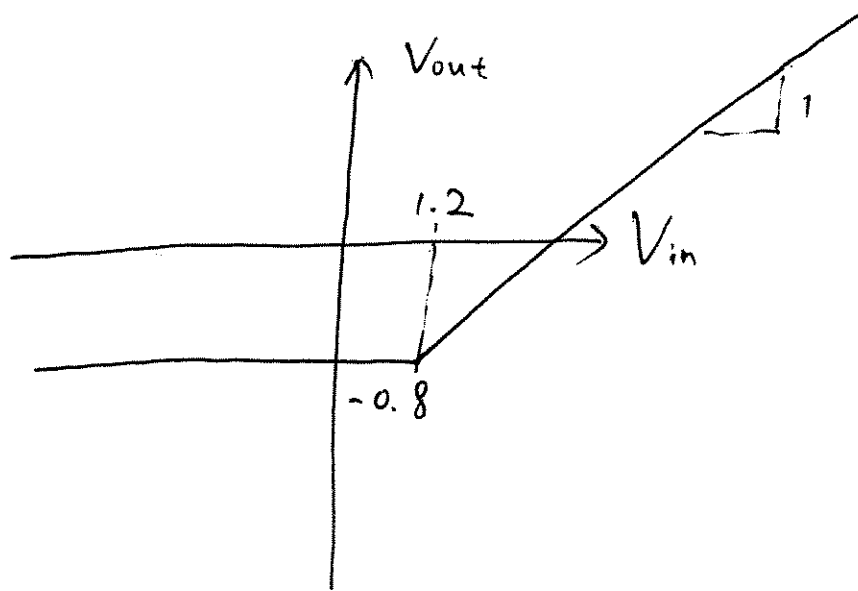

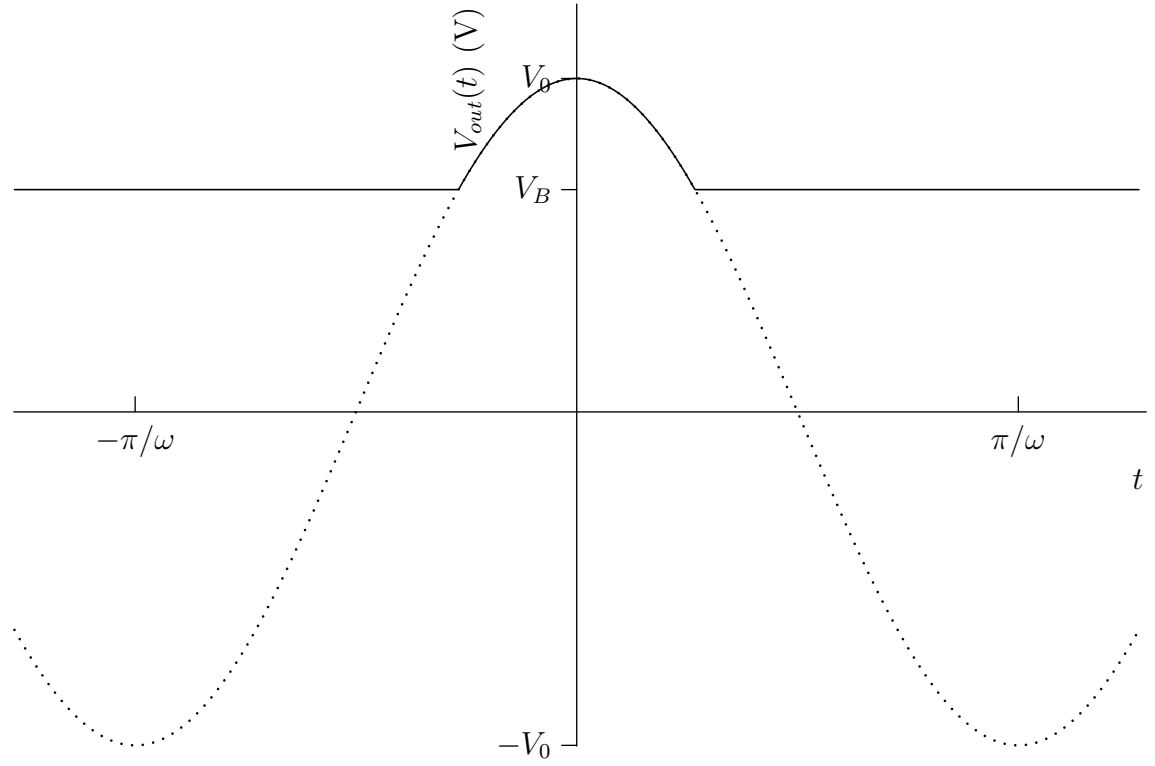3.11 For each part, the dotted line indicates  $V_{in}(t)$ , while the solid line indicates  $V_{out}(t)$ . Assume  $V_0 > V_B$ .


(a)

$$V_{out} = \begin{cases} V_B & V_{in} < V_B \\ V_{in} & V_{in} > V_B \end{cases}$$




(b)
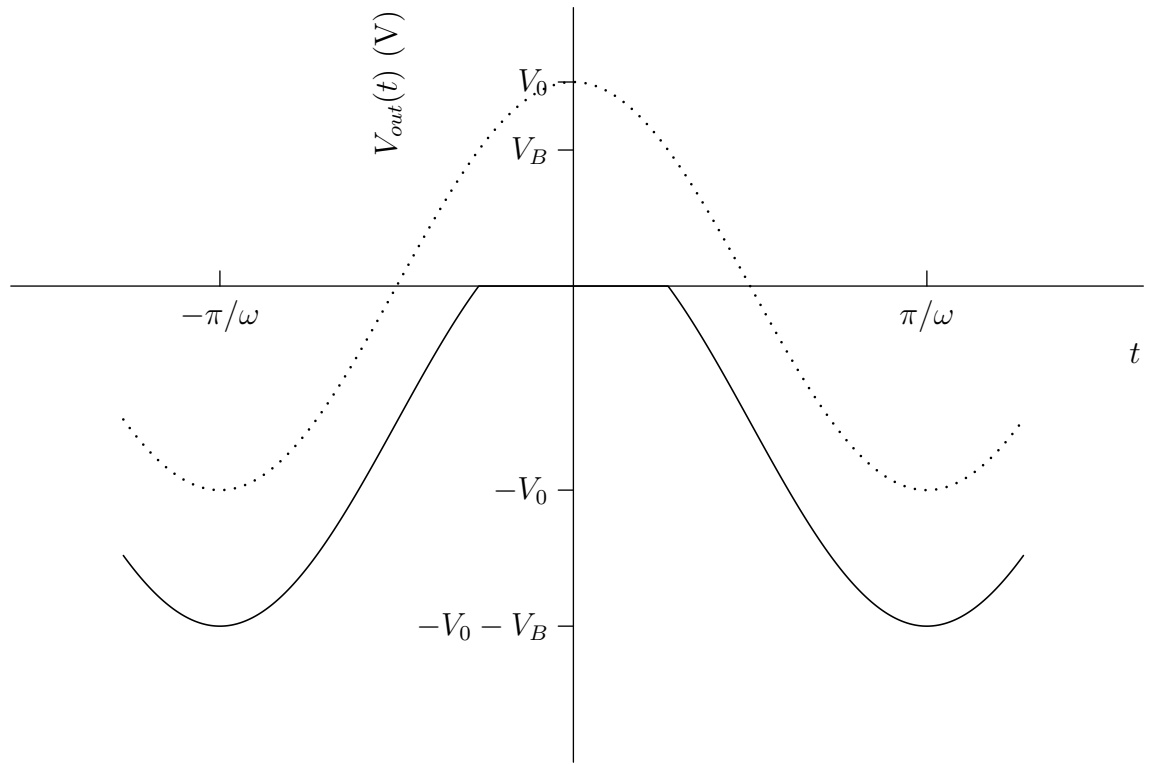
$$V_{out} = \begin{cases} V_{in} - V_B & V_{in} < V_B \\ 0 & V_{in} > V_B \end{cases}$$




(c)

$$V_{out} = V_{in} - V_B$$

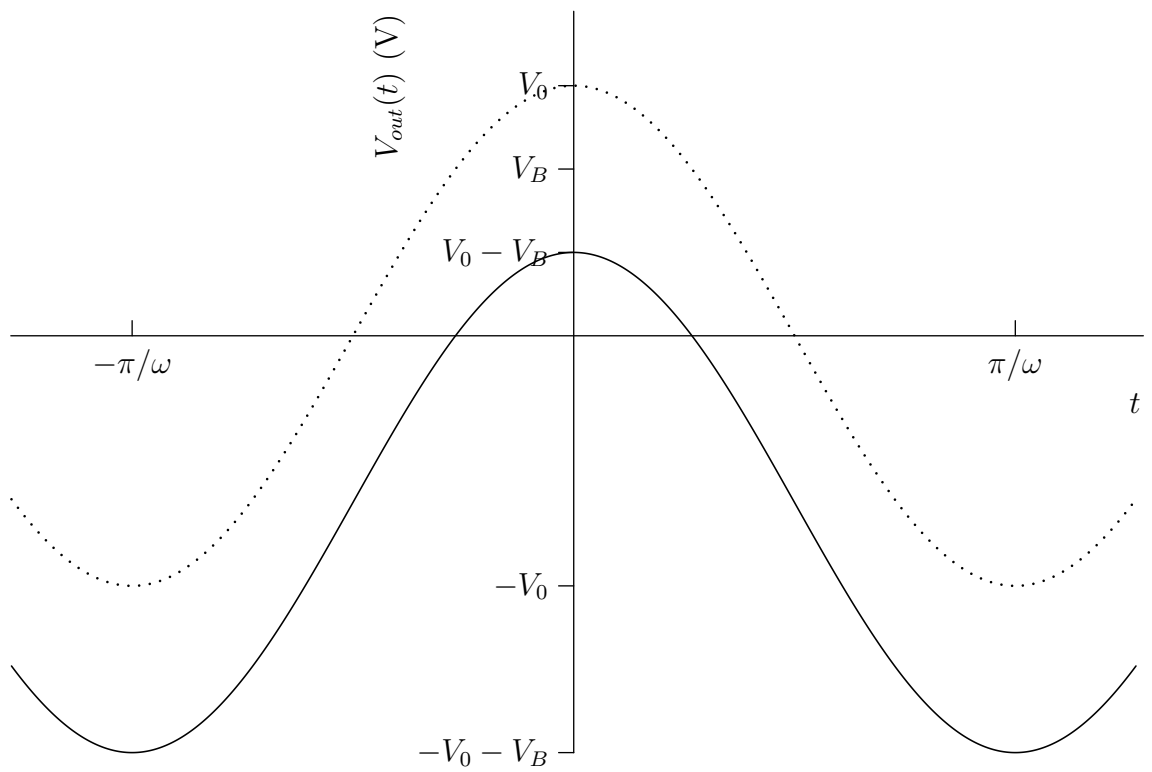


(d)
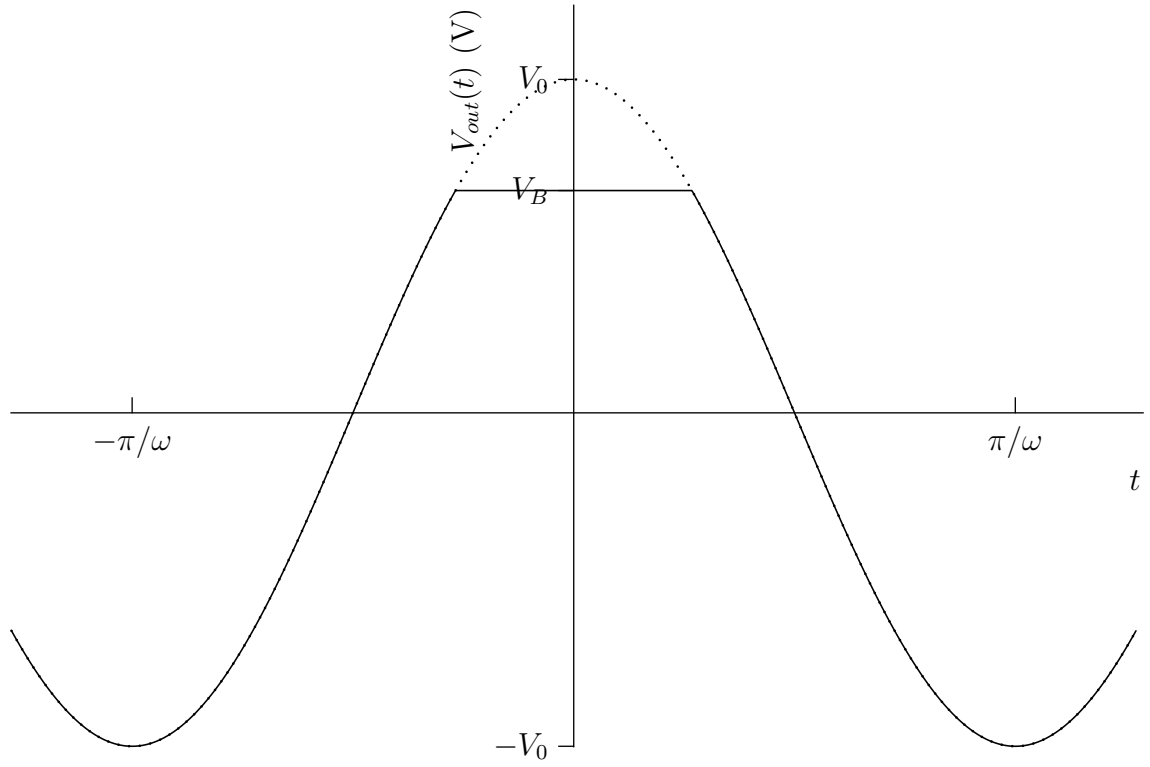
$$V_{out} = \begin{cases} V_{in} & V_{in} < V_B \\ V_B & V_{in} > V_B \end{cases}$$



(e)

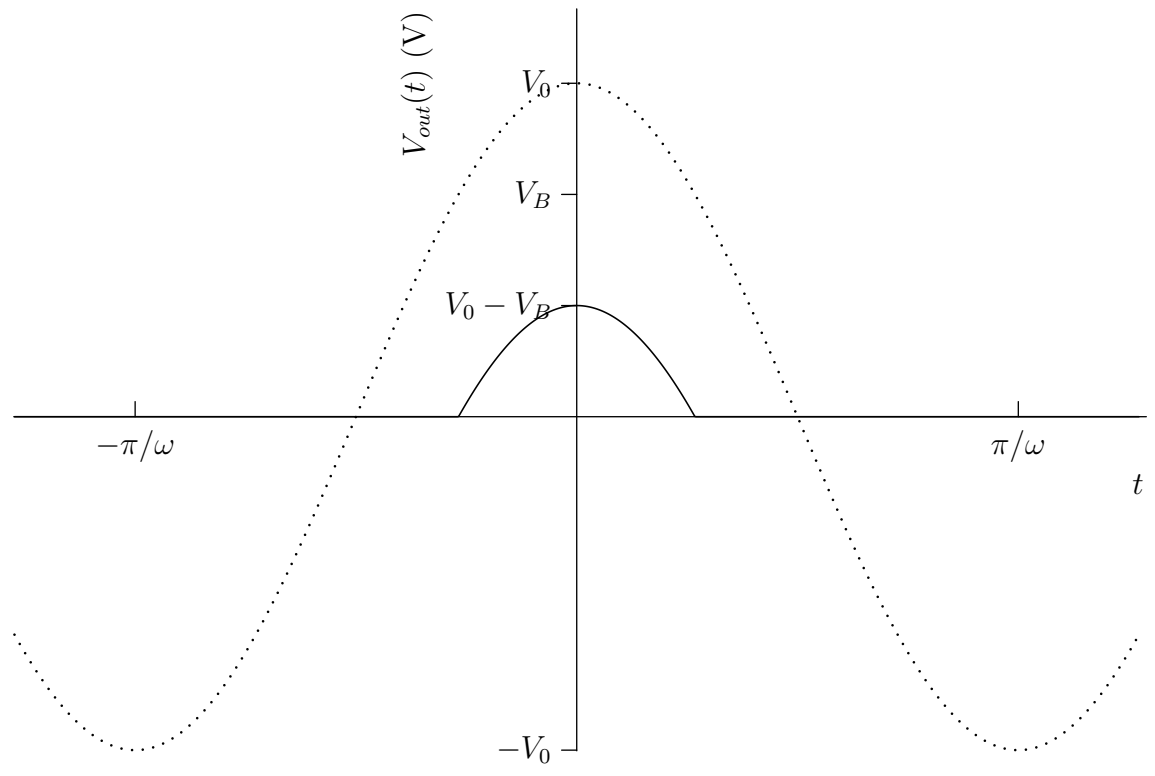
$$V_{out} = \begin{cases} 0 & V_{in} < V_B \\ V_{in} - V_B & V_{in} > V_B \end{cases}$$



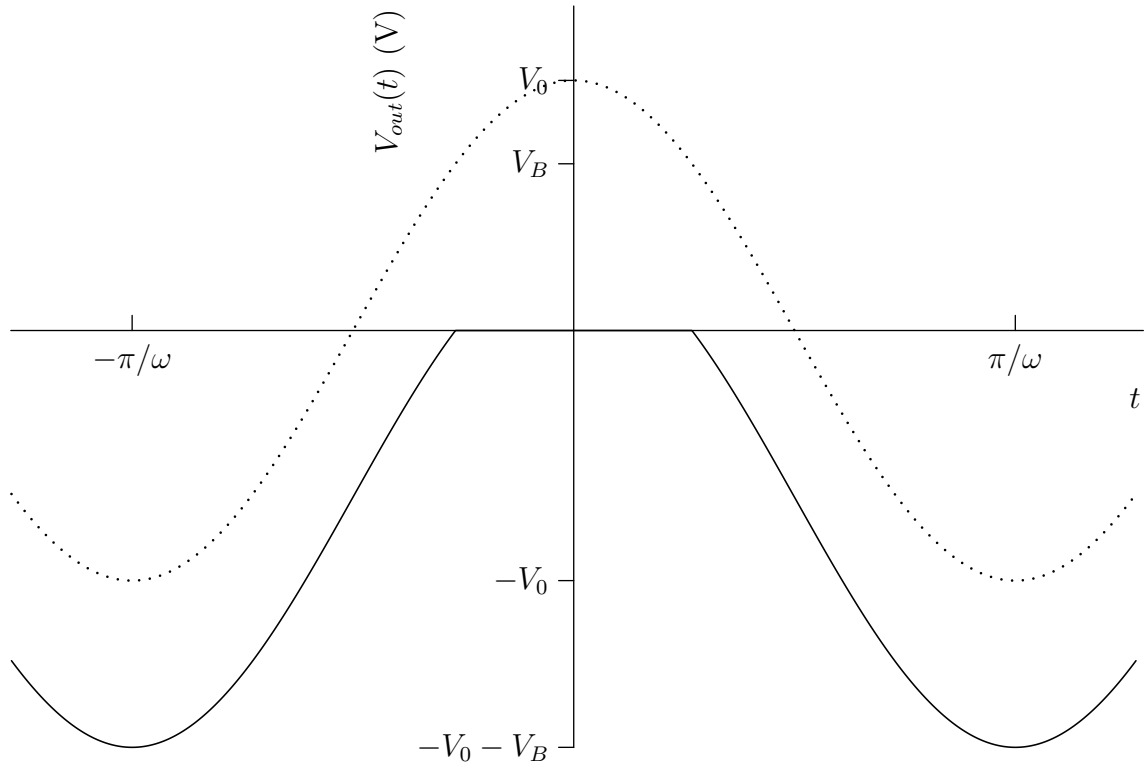3.12 For each part, the dotted line indicates  $V_{in}(t)$ , while the solid line indicates  $V_{out}(t)$ . Assume  $V_0 > V_B$ .

(a)


$$V_{out} = \begin{cases} V_{in} - V_B & V_{in} < V_B \\ 0 & V_{in} > V_B \end{cases}$$



(b)

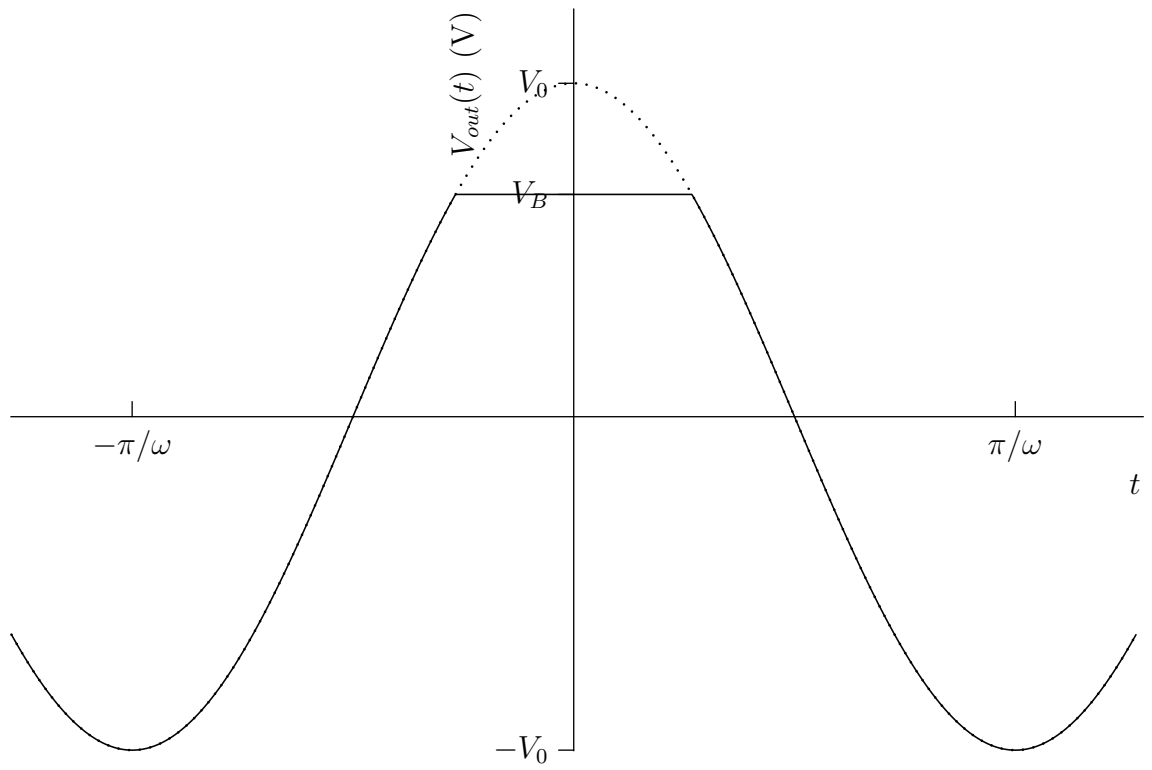
$$V_{out} = \begin{cases} V_{in} & V_{in} < V_B \\ V_B & V_{in} > V_B \end{cases}$$






(c)
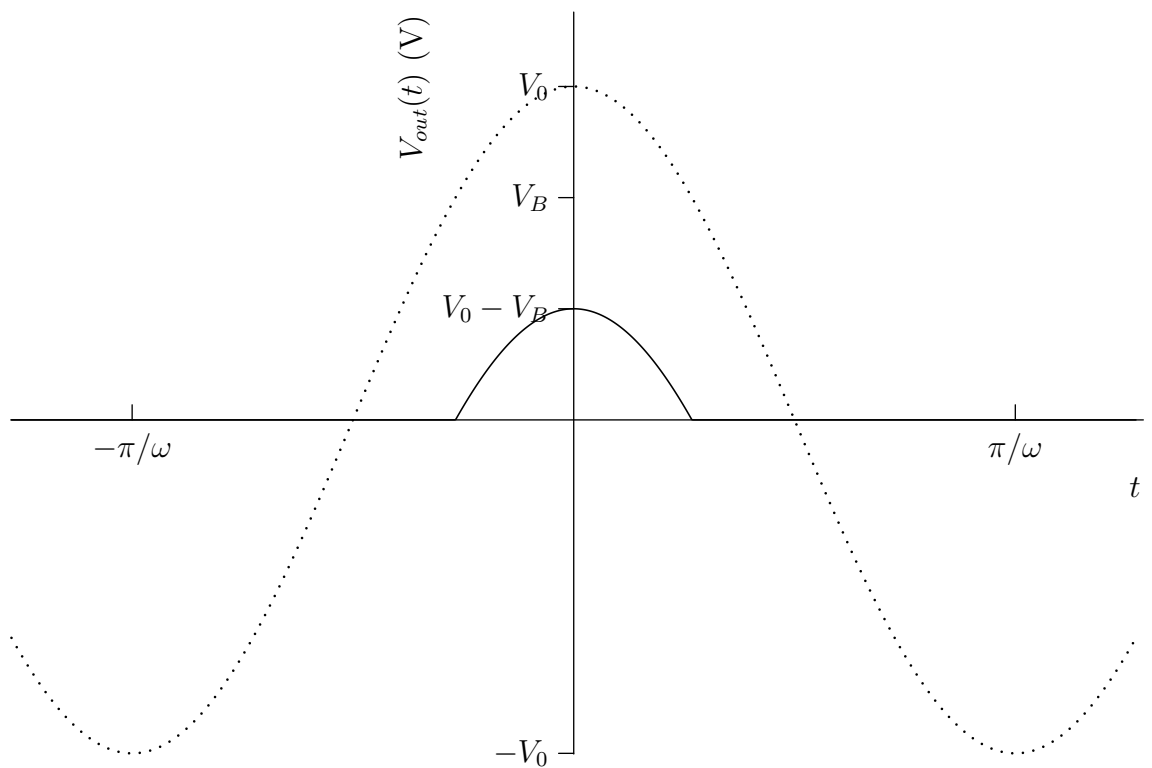
$$V_{out} = \begin{cases} 0 & V_{in} < V_B \\ V_{in} - V_B & V_{in} > V_B \end{cases}$$




(d)

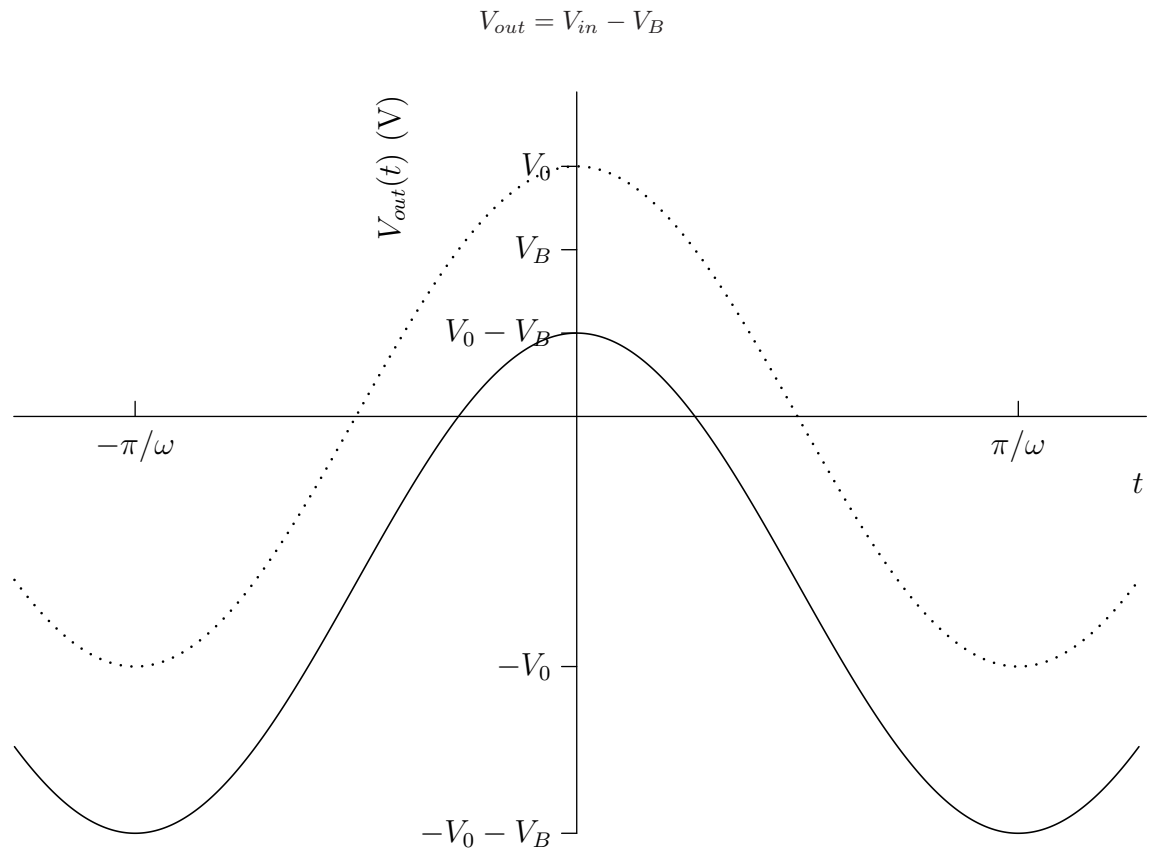


(e)

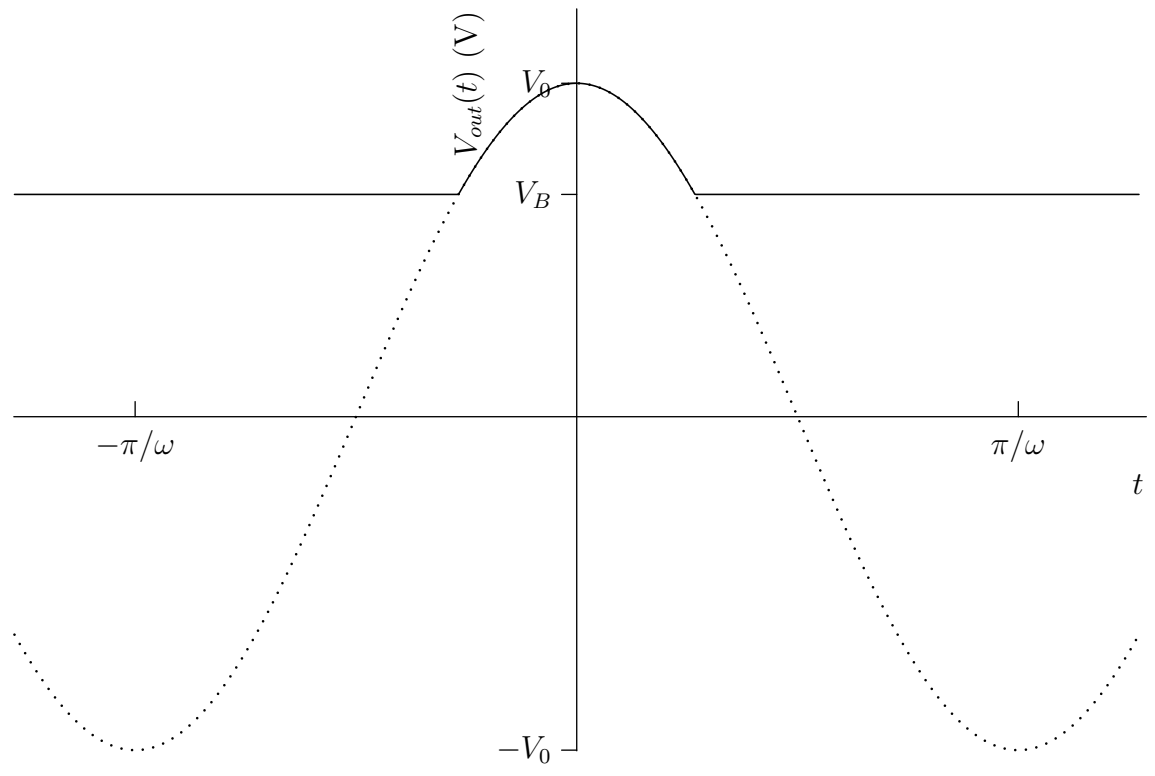
$$V_{out} = \begin{cases} V_B & V_{in} < V_B \\ V_{in} & V_{in} > V_B \end{cases}$$




⑬ a)

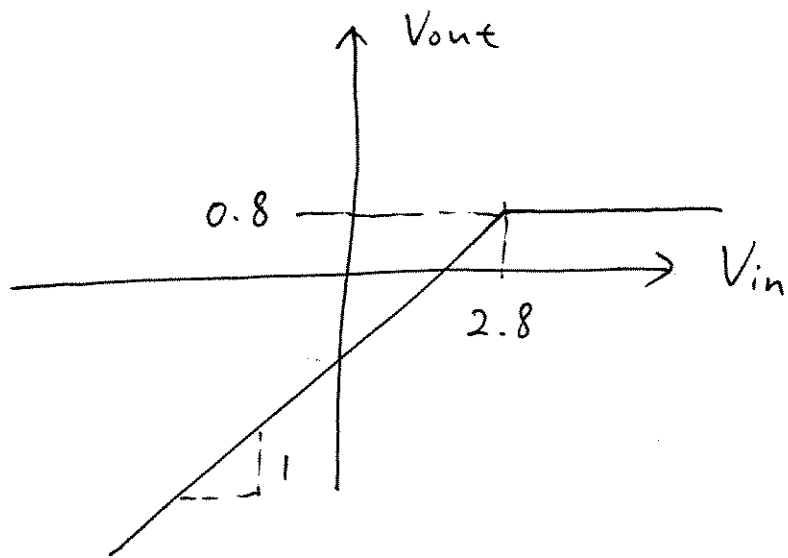


b)

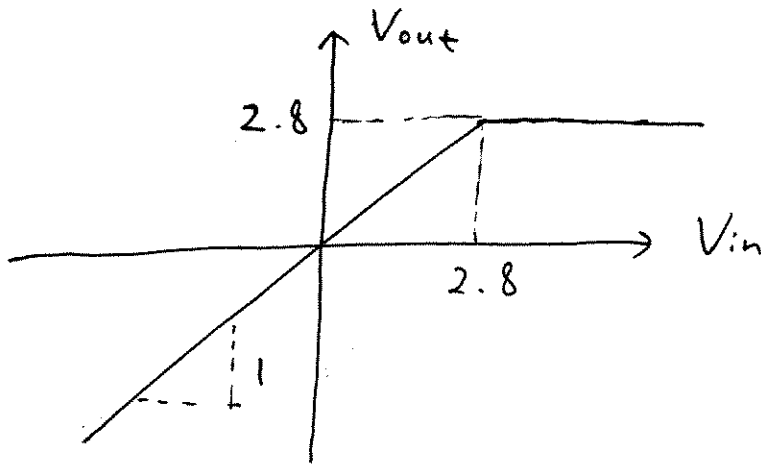


c)

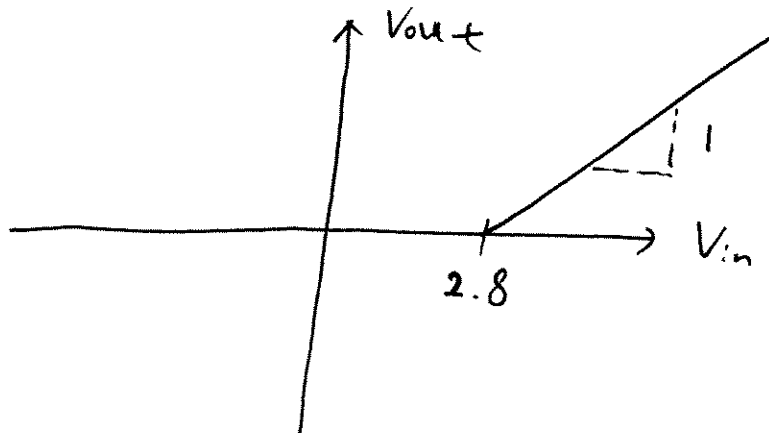


d)

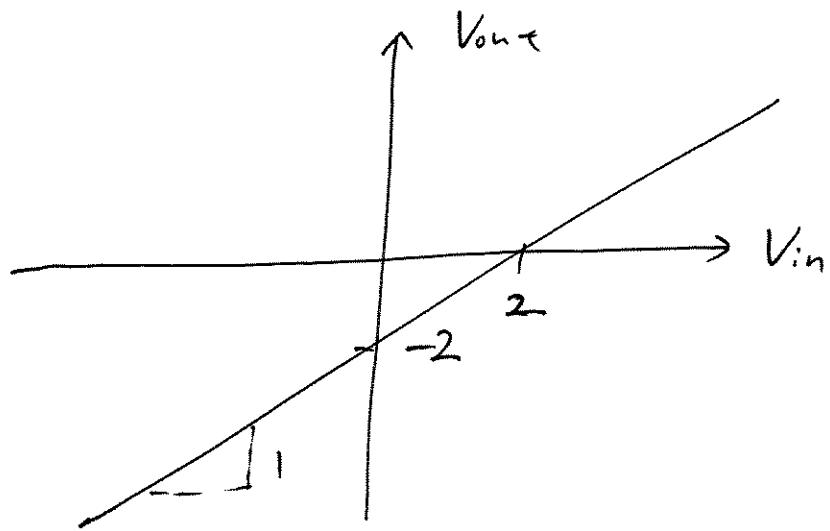


e)

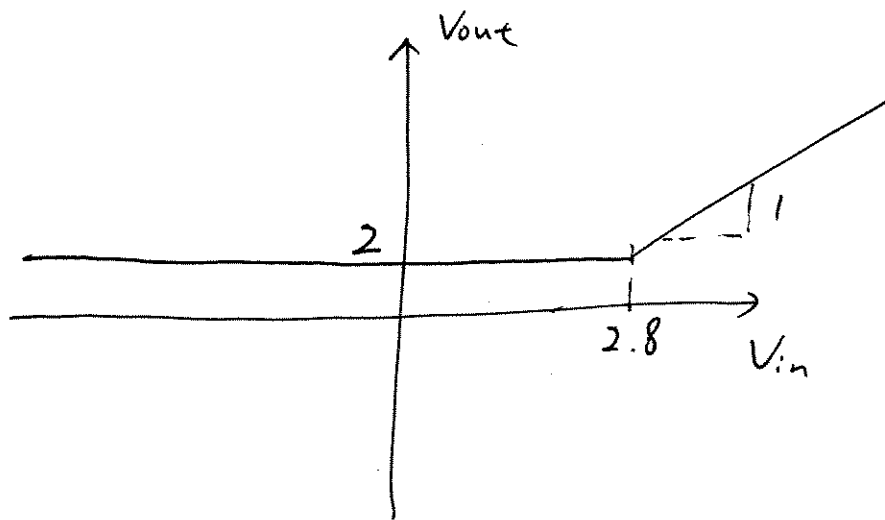


(14) a)

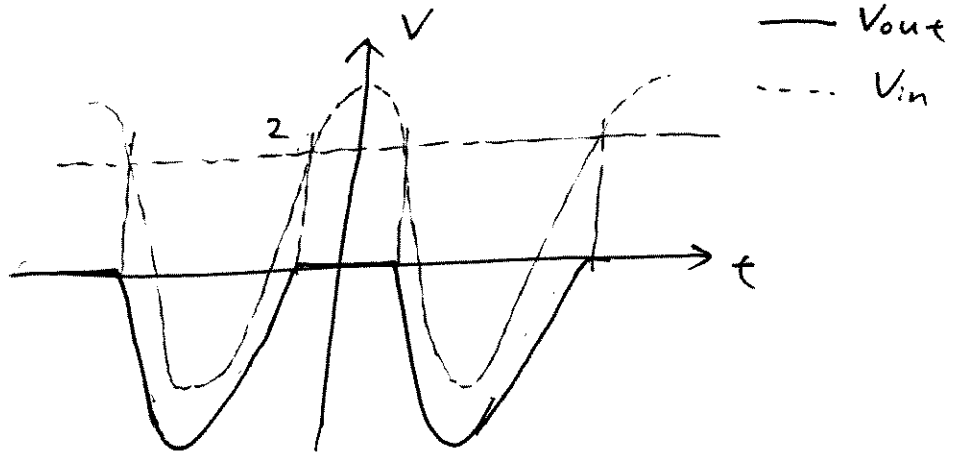


b)

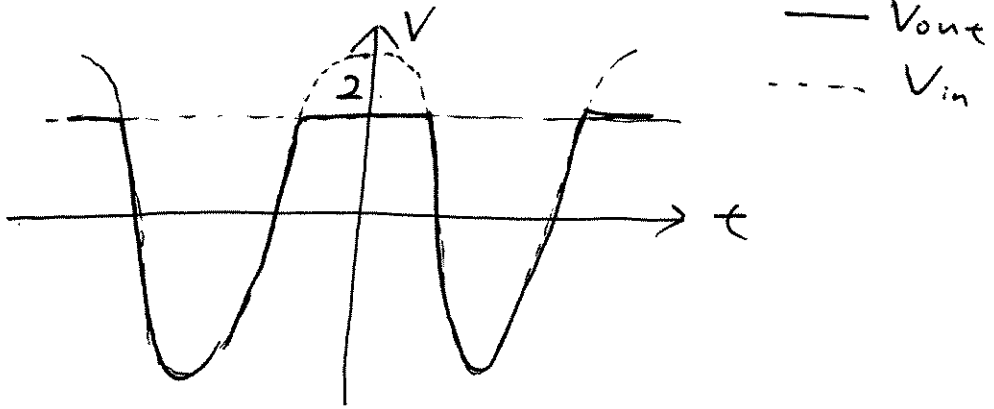


c)

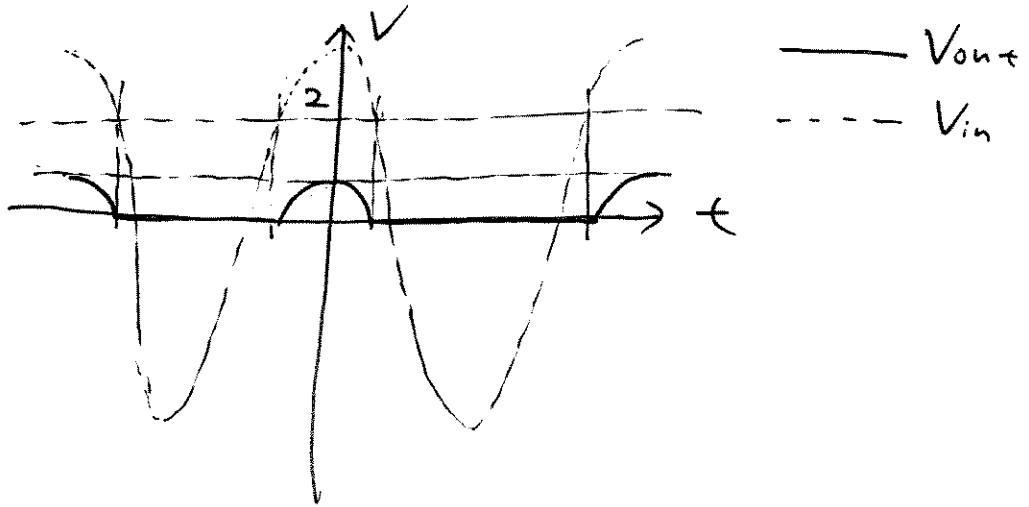


d)

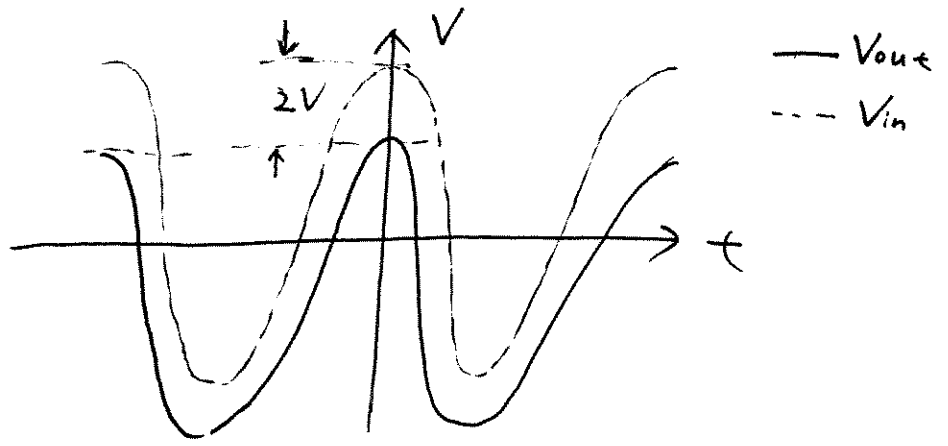


e)

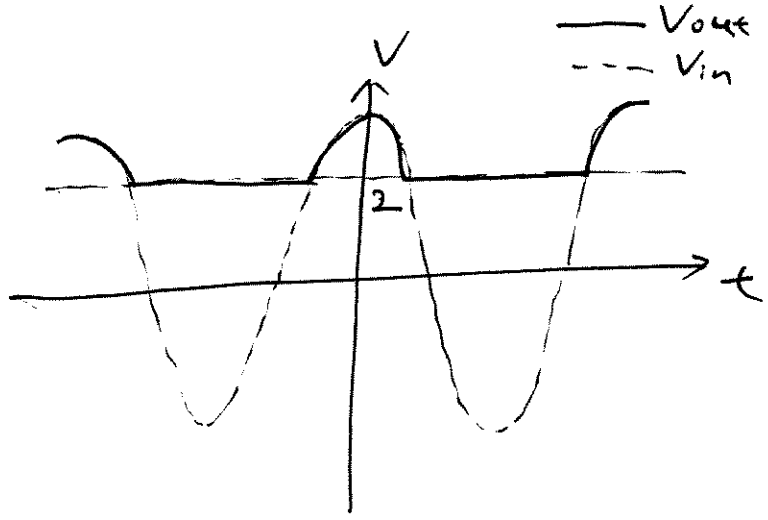


(15) a)

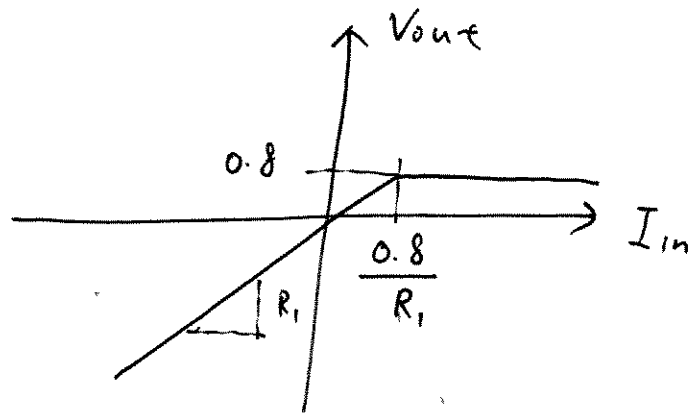


b)

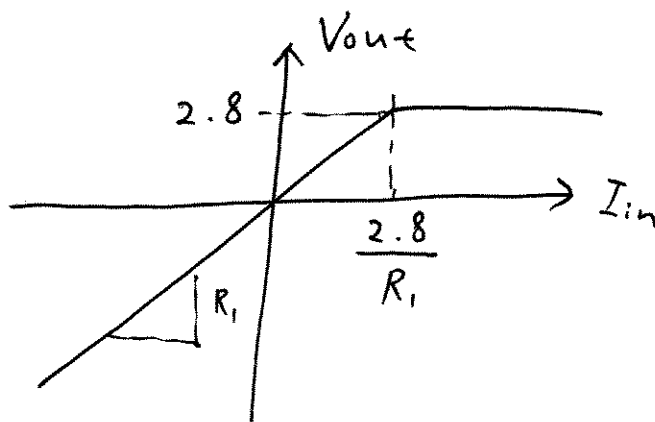

c)

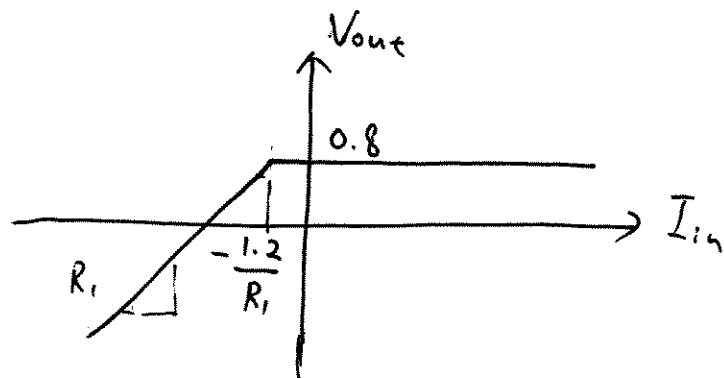


d)

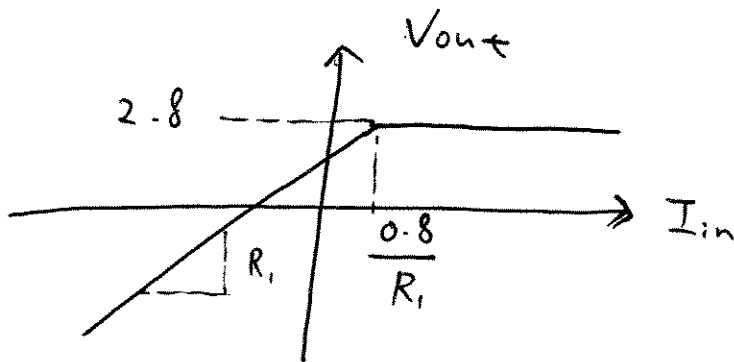



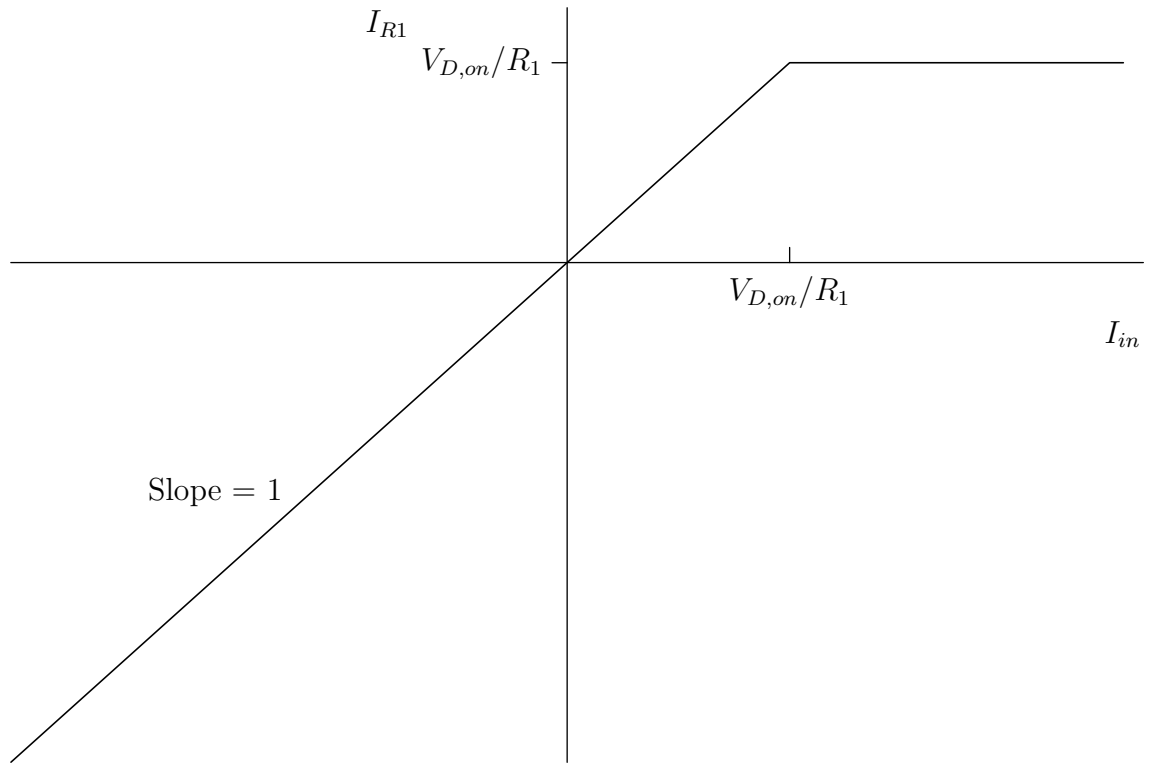
3.16 (a)

$$I_{R1} = \begin{cases} I_{in} & I_{in} < \frac{V_{D,on}}{R_1} \\ \frac{V_{D,on}}{R_1} & I_{in} > \frac{V_{D,on}}{R_1} \end{cases}$$




(b)
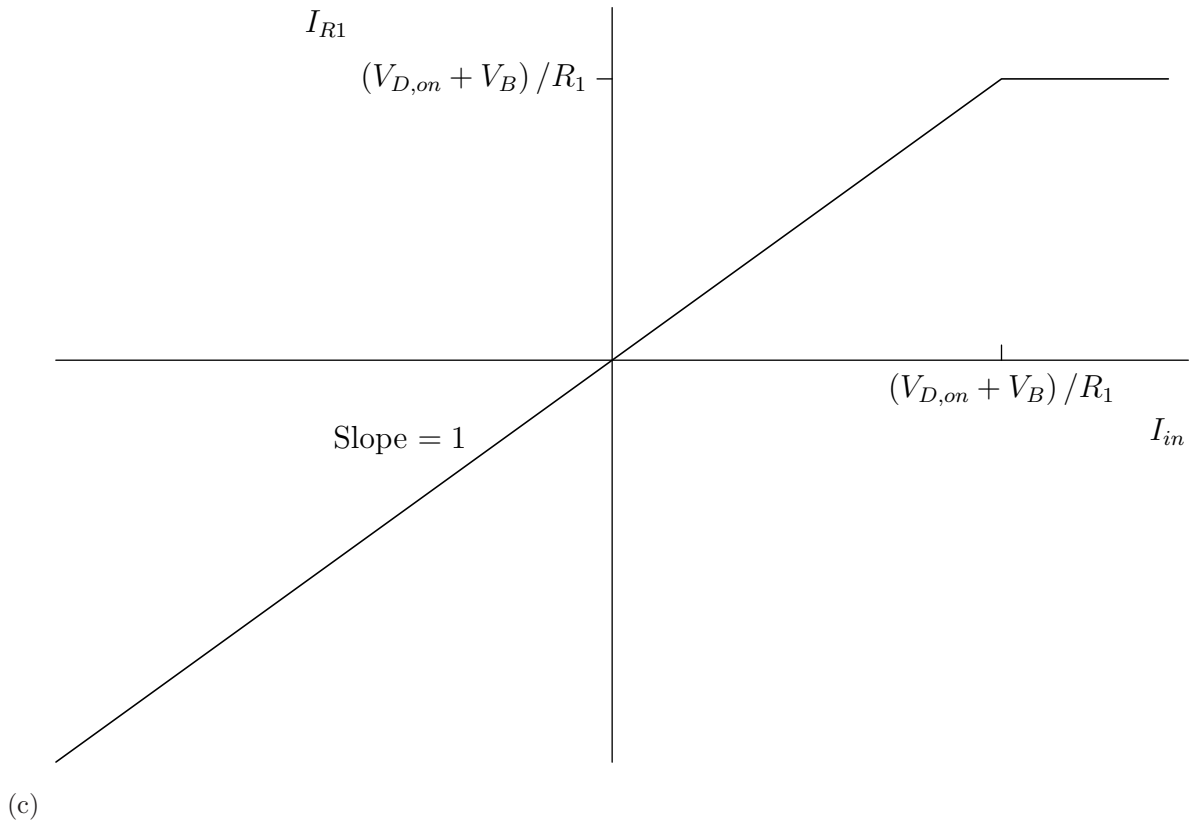
$$I_{R1} = \begin{cases} I_{in} & I_{in} < \frac{V_{D,on} + V_E}{R_1} \\ \frac{V_{D,on} + V_E}{R_1} & I_{in} > \frac{V_{D,on} + V_E}{R_1} \end{cases}$$



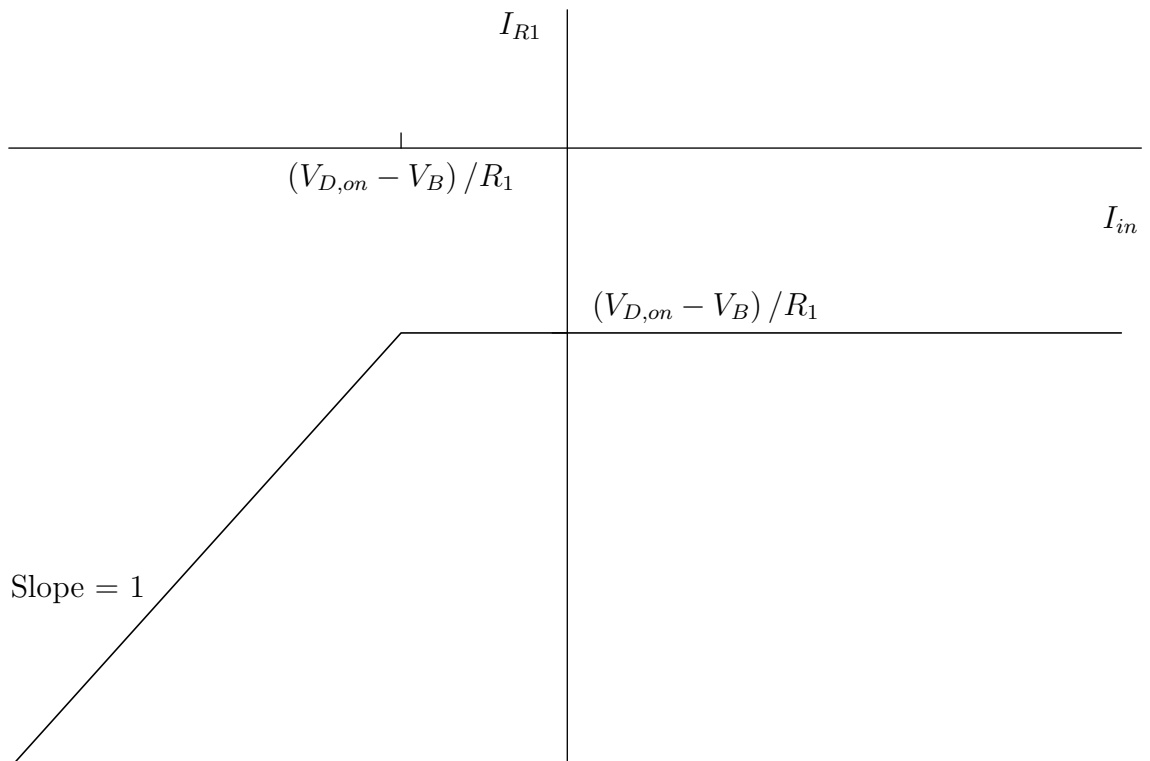
$$I_{R1} = \begin{cases} I_{in} & I_{in} < \frac{V_{D,on} - V_B}{R_1} \\ \frac{V_{D,on} - V_B}{R_1} & I_{in} > \frac{V_{D,on} - V_B}{R_1} \end{cases}$$




(d)
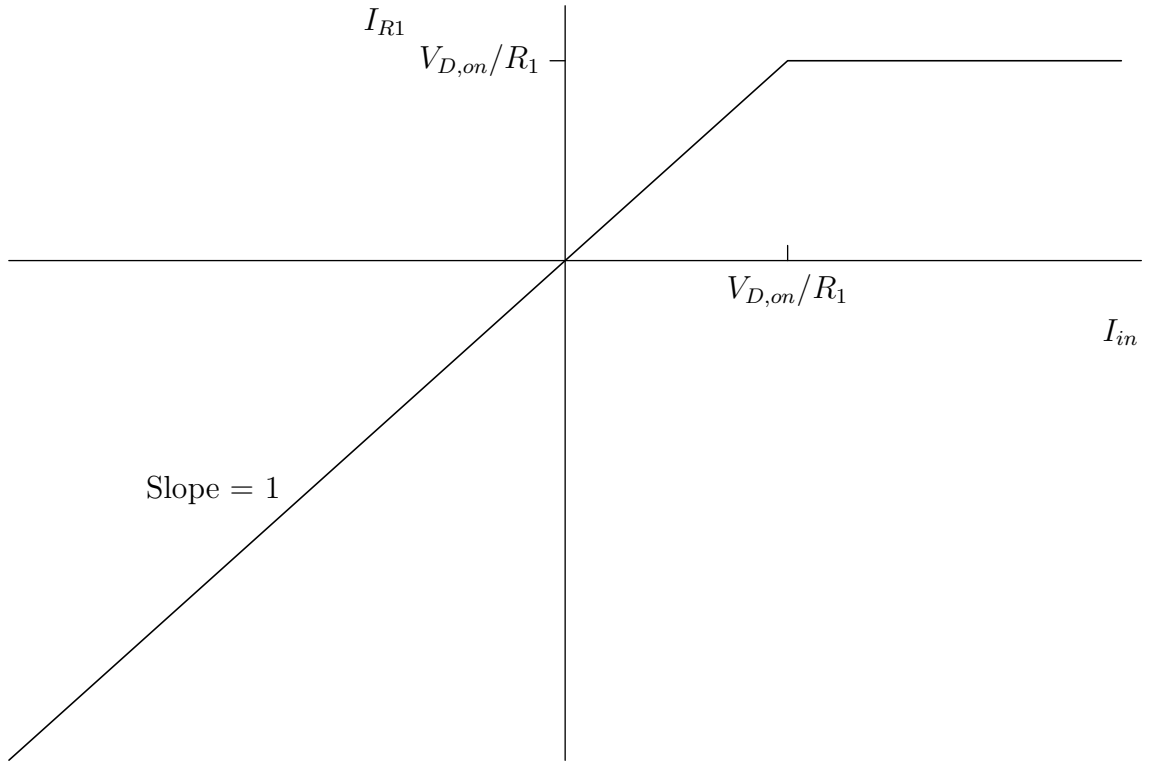
$$I_{R1} = \begin{cases} I_{in} & I_{in} < \frac{V_{D,on}}{R_1} \\ \frac{V_{D,on}}{R_1} & I_{in} > \frac{V_{D,on}}{R_1} \end{cases}$$



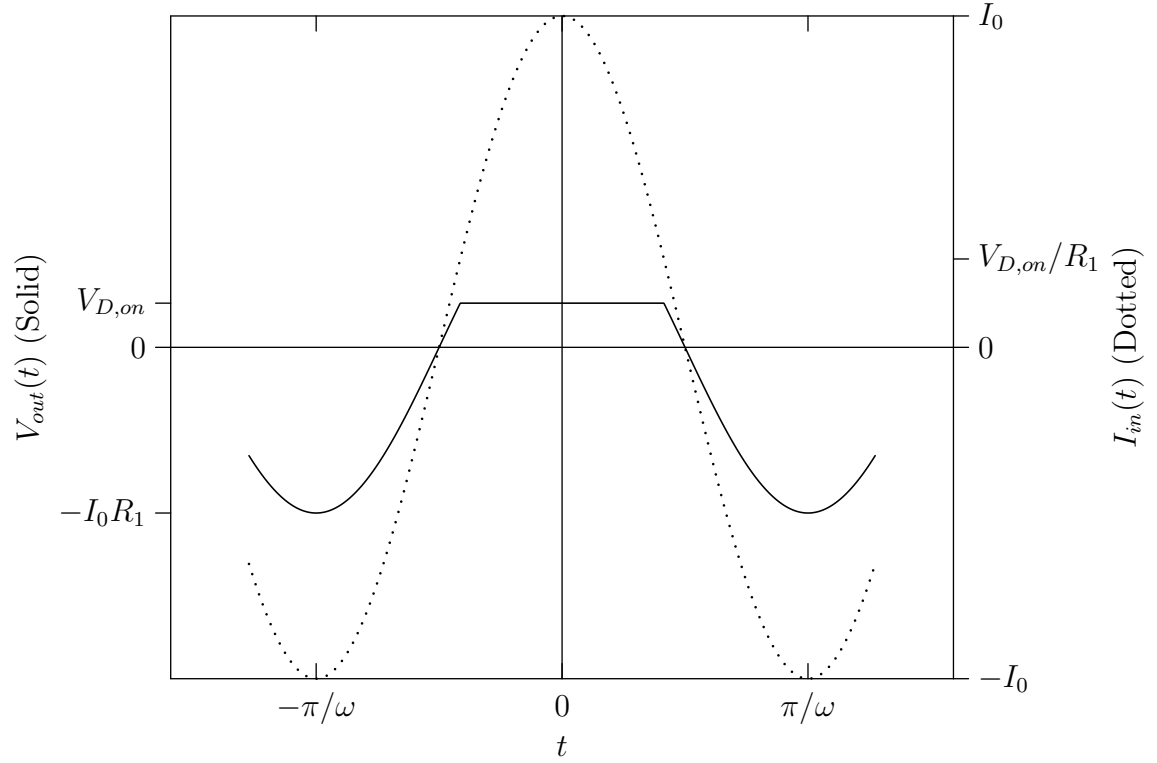
3.17 (a)

$$V_{out} = \begin{cases} I_{in}R_1 & I_{in} < \frac{V_{D,on}}{R_1} \\ V_{D,on} & I_{in} > \frac{V_{D,on}}{R_1} \end{cases}$$




(b)
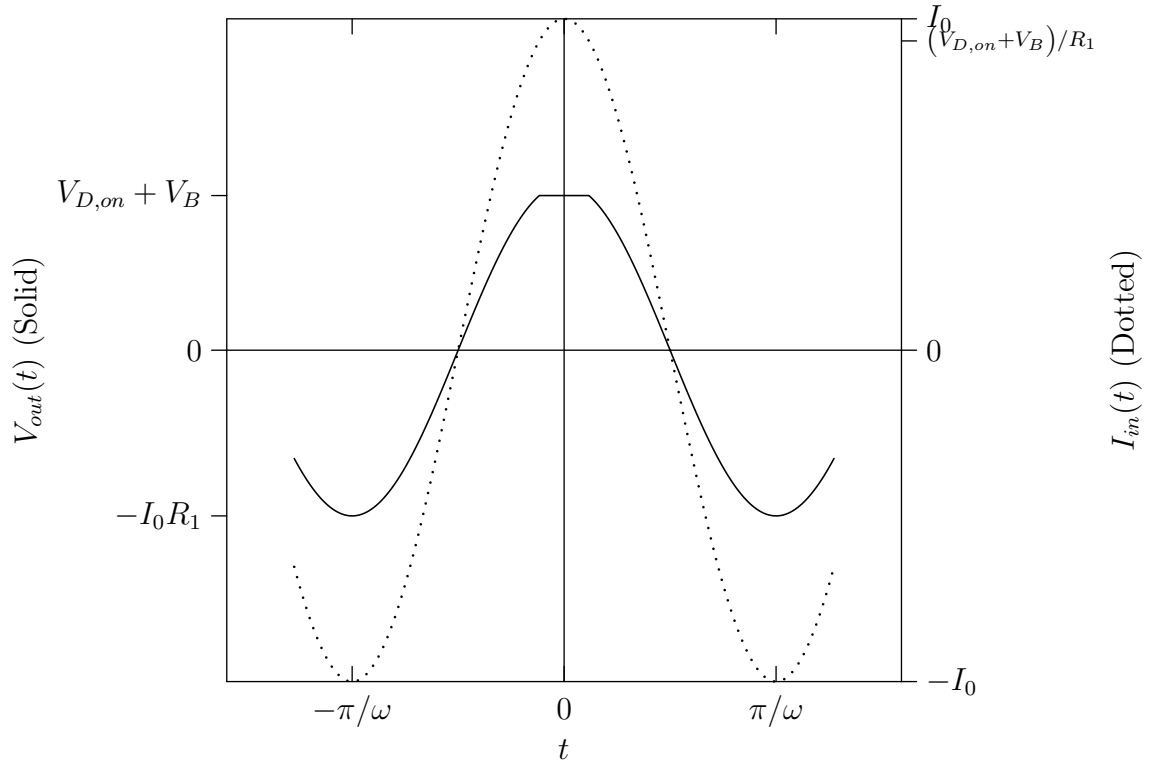
$$V_{out} = \begin{cases} I_{in}R_1 & I_{in} < \frac{V_{D,on} + V_B}{R_1} \\ V_{D,on} + V_B & I_{in} > \frac{V_{D,on} + V_B}{R_1} \end{cases}$$




(c)
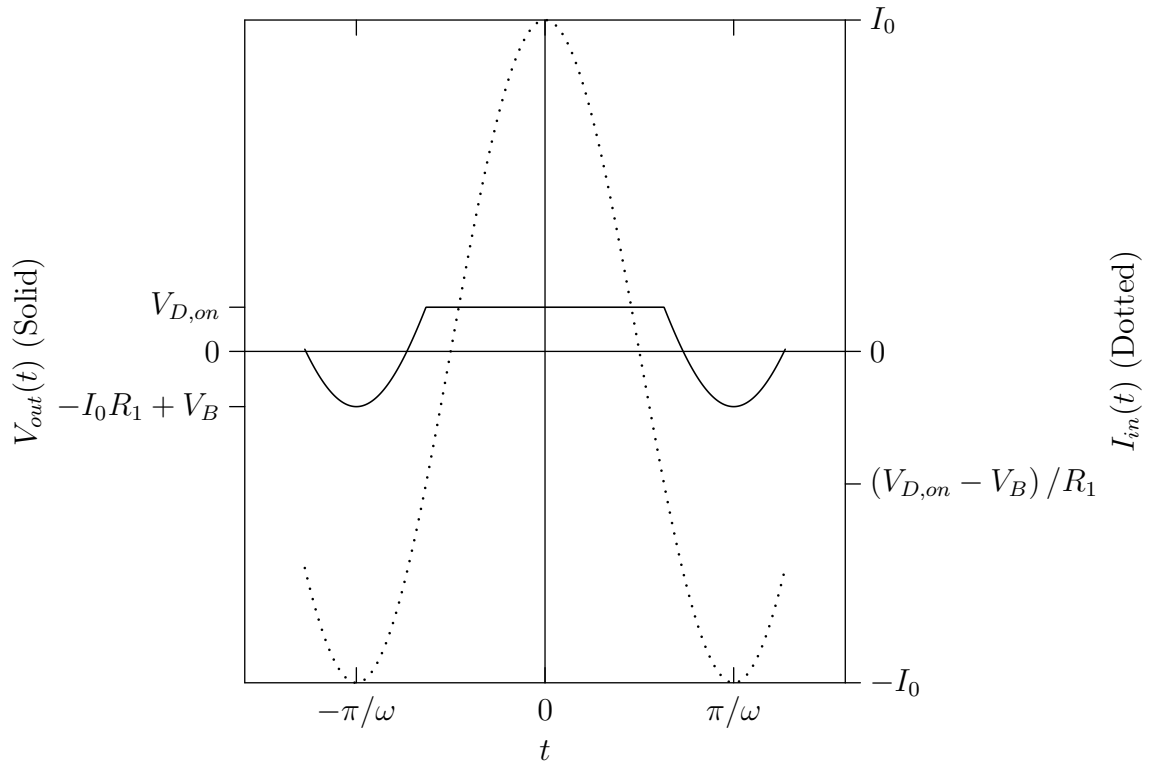
$$V_{out} = \begin{cases} I_{in} R_1 + V_B & I_{in} < \frac{V_{D,on} - V_B}{R_1} \\ V_{D,on} & I_{in} > \frac{V_{D,on} - V_B}{R_1} \end{cases}$$




(d)
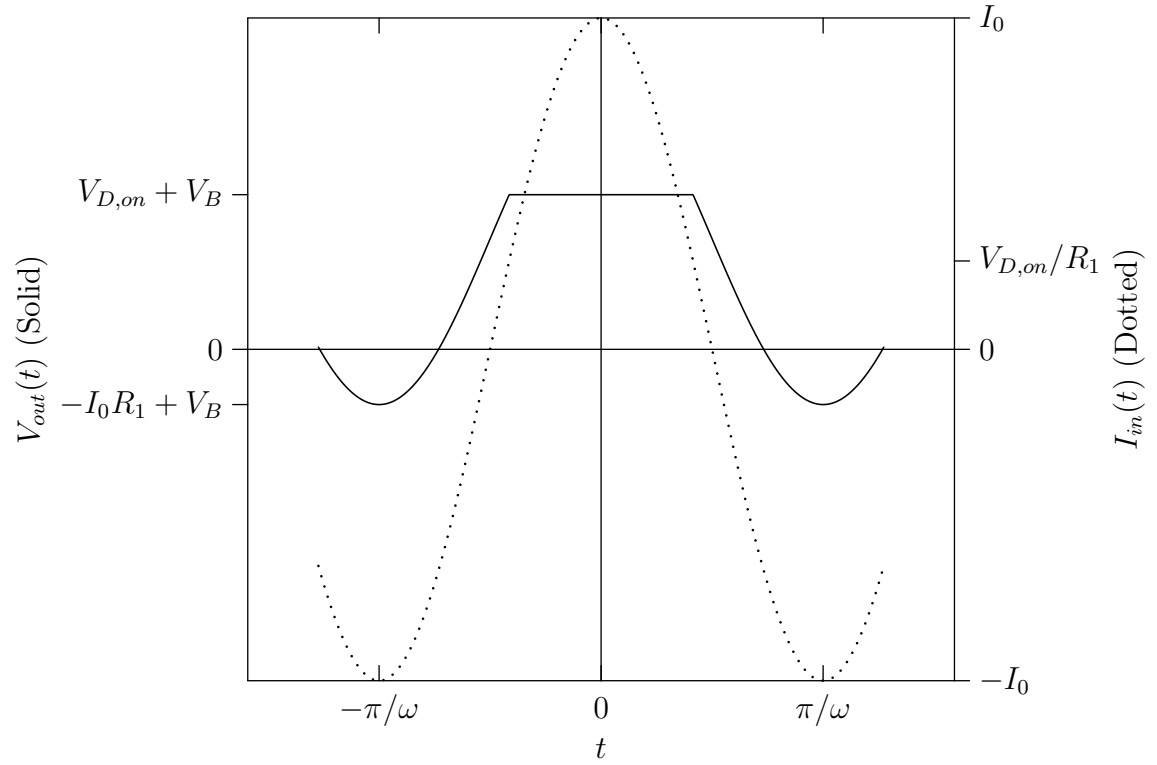
$$V_{out} = \begin{cases} I_{in}R_1 + V_B & I_{in} < \frac{V_{D,on}}{R_1} \\ V_{D,on} + V_B & I_{in} > \frac{V_{D,on}}{R_1} \end{cases}$$




18


a)

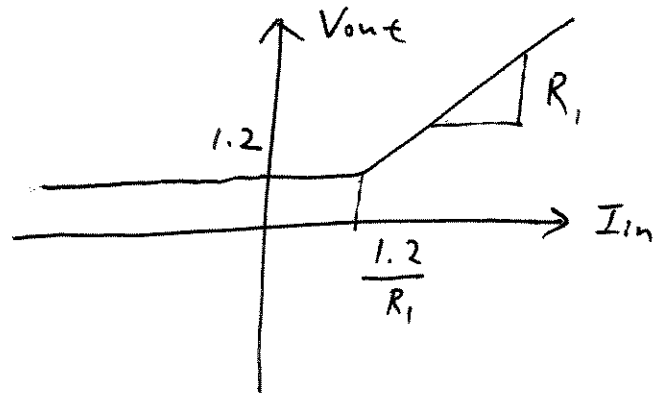


b)

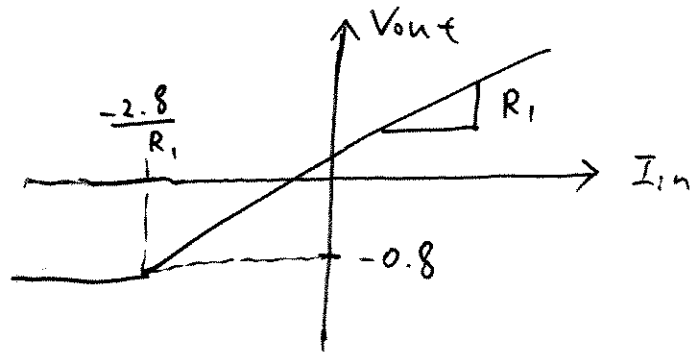


c)

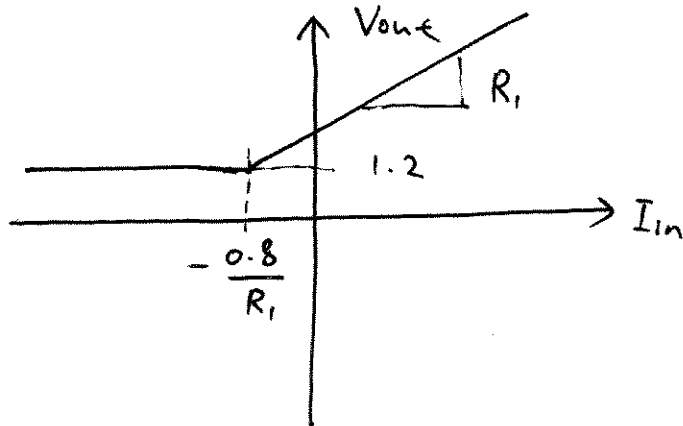


(19) a)

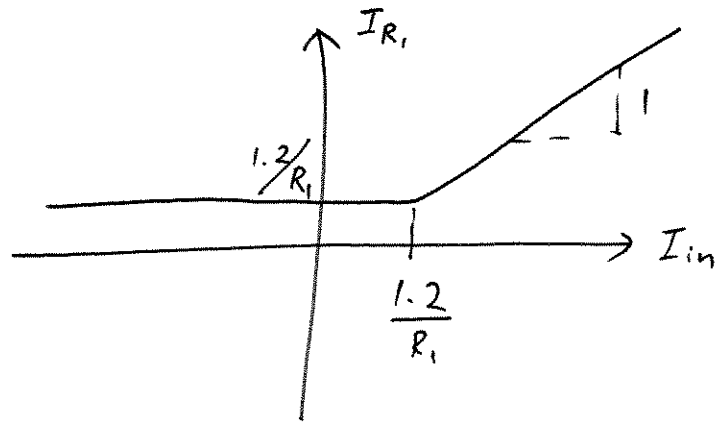

b)

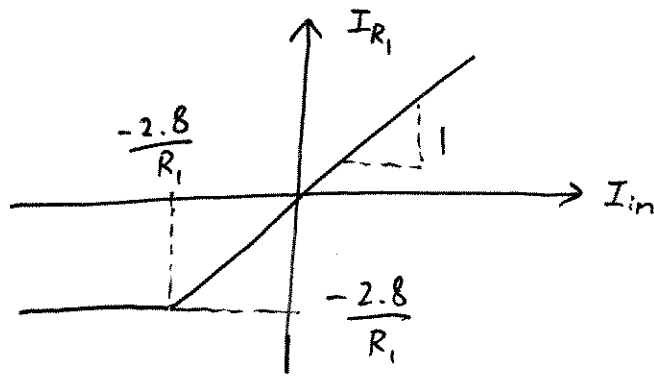


c)

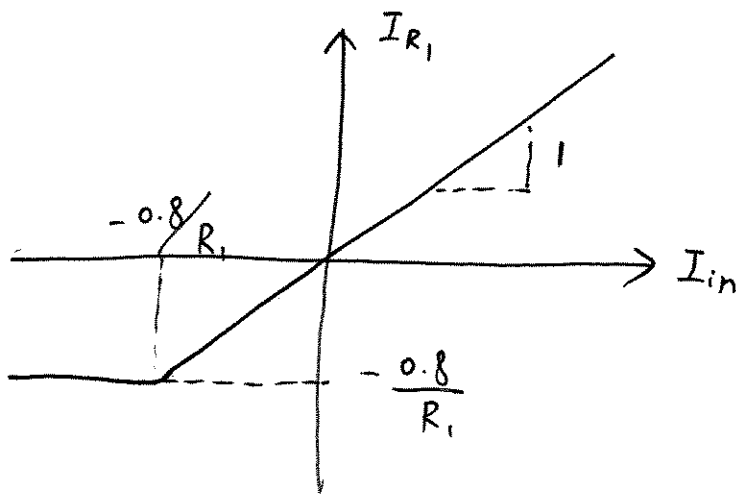



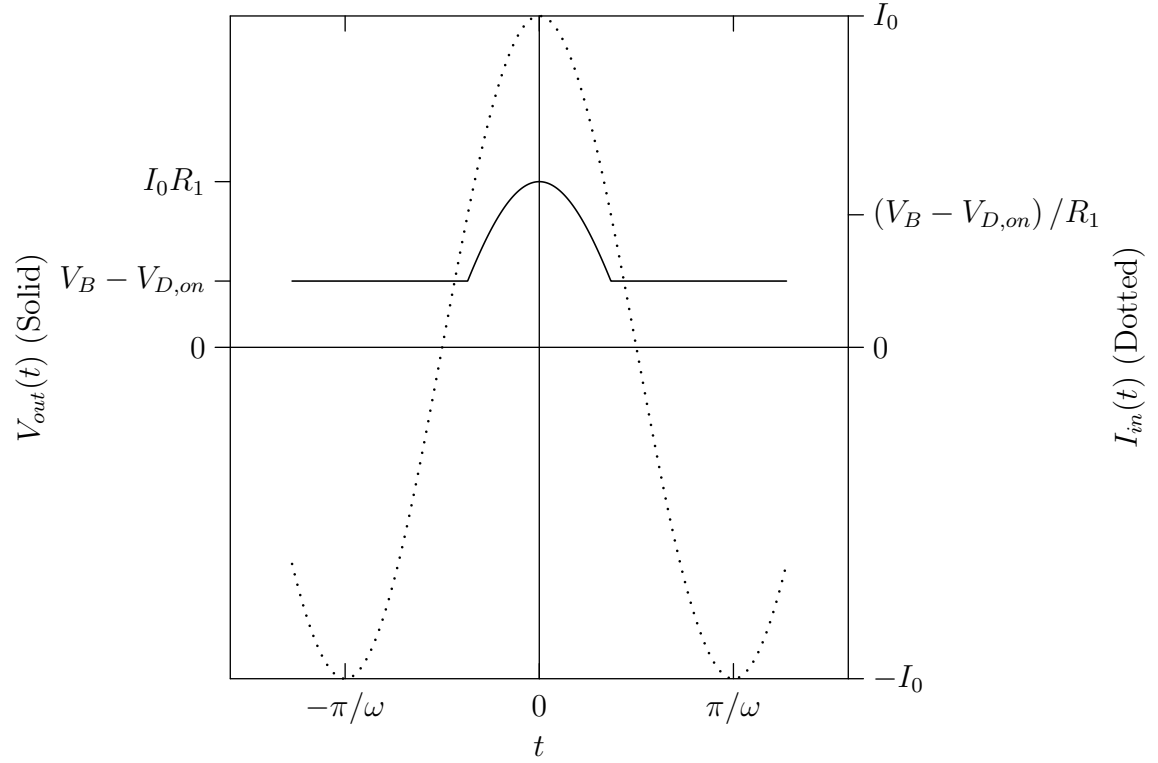
3.20 (a)

$$V_{out} = \begin{cases} I_{in} R_1 & I_{in} > \frac{V_B - V_{D,on}}{R_1} \\ V_B - V_{D,on} & I_{in} < \frac{V_B - V_{D,on}}{R_1} \end{cases}$$




(b)
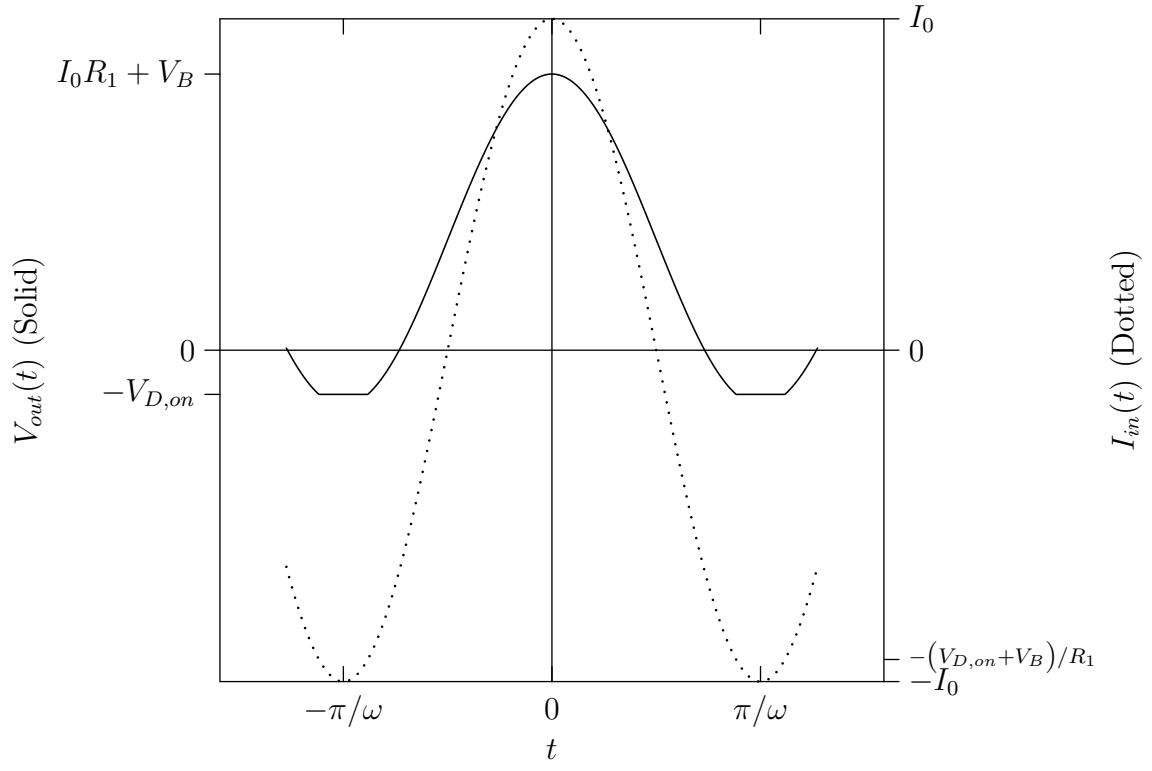
$$V_{out} = \begin{cases} I_{in} R_1 + V_B & I_{in} > -\frac{V_{D,on} + V_B}{R_1} \\ -V_{D,on} & I_{in} < -\frac{V_{D,on} + V_B}{R_1} \end{cases}$$




(c)

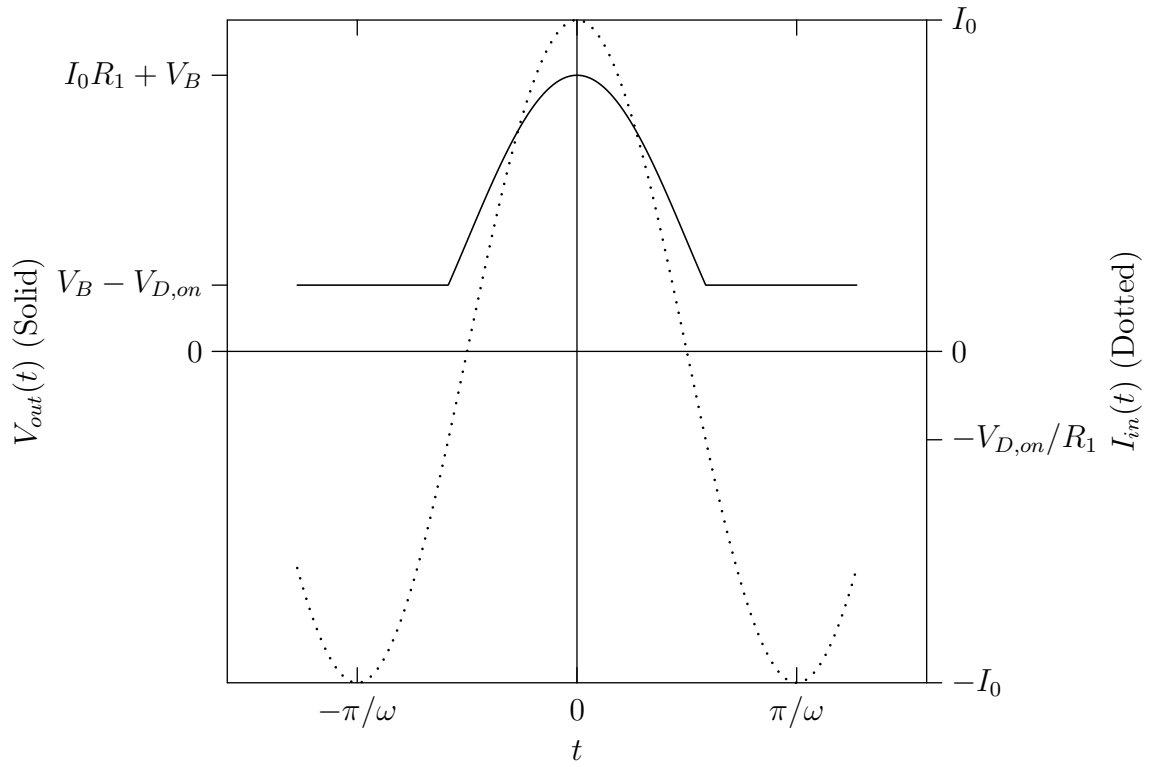
$$V_{out} = \begin{cases} I_{in} R_1 + V_B & I_{in} > -\frac{V_{D,on}}{R_1} \\ V_B - V_{D,on} & I_{in} < -\frac{V_{D,on}}{R_1} \end{cases}$$




(21) a)

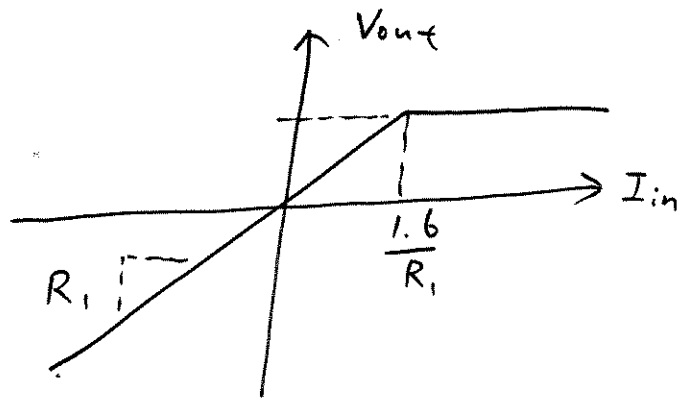


b)




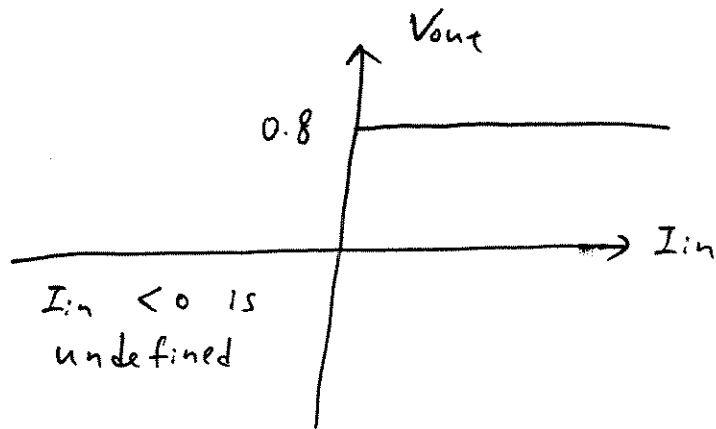


c)

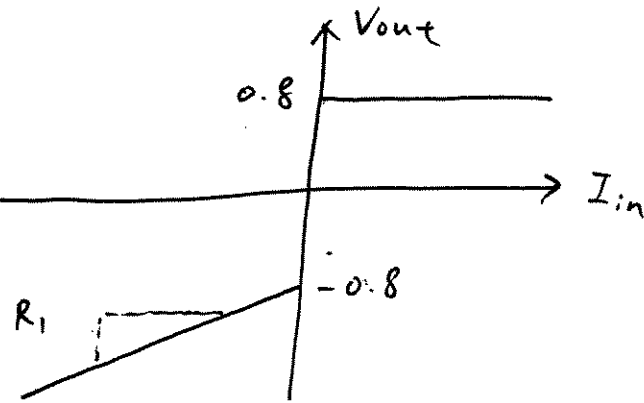


d)

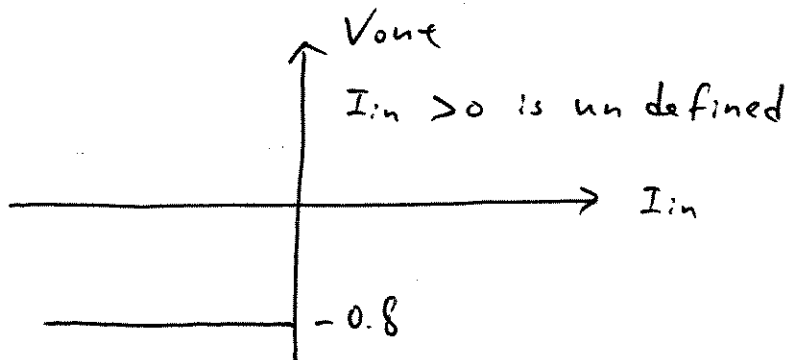

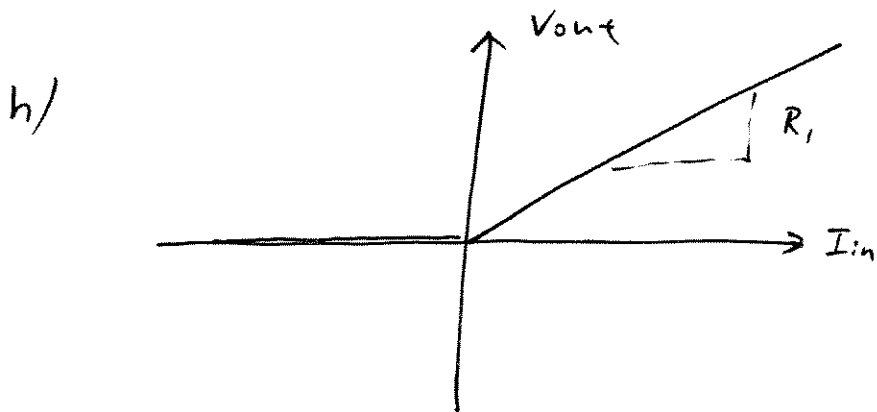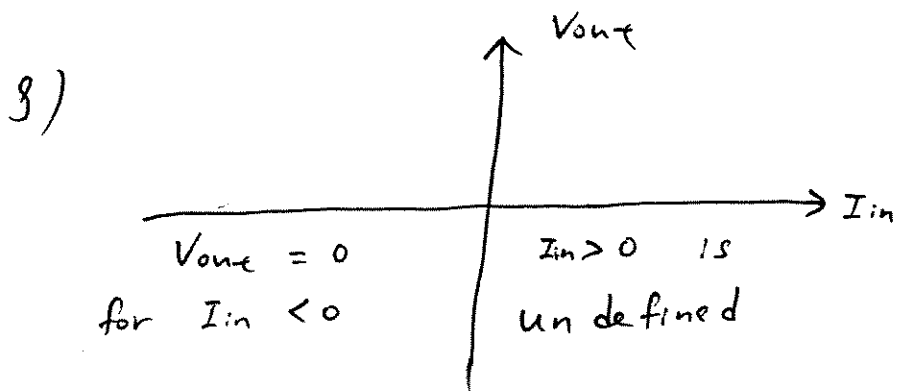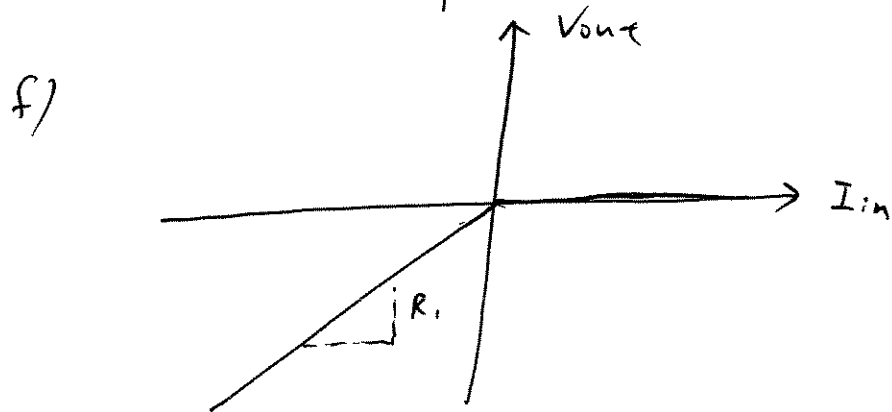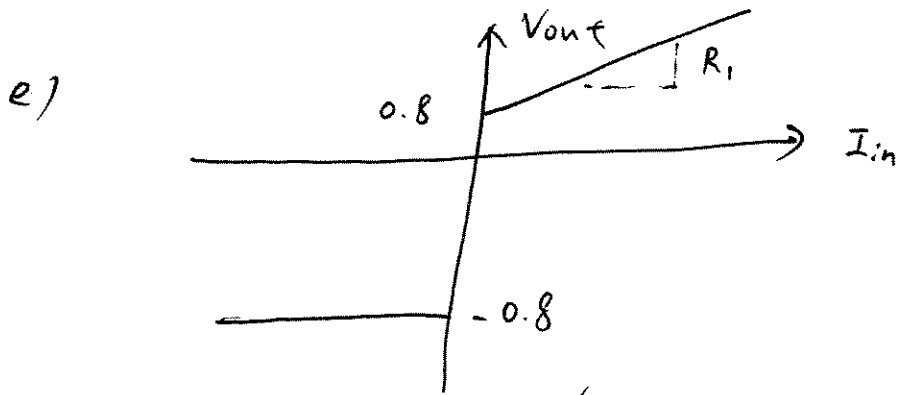


22


a)

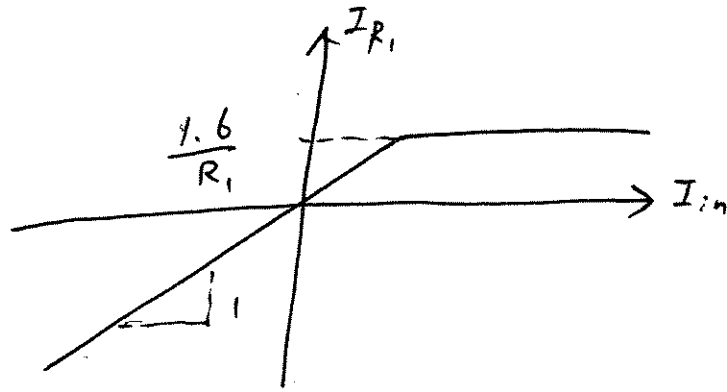


b)

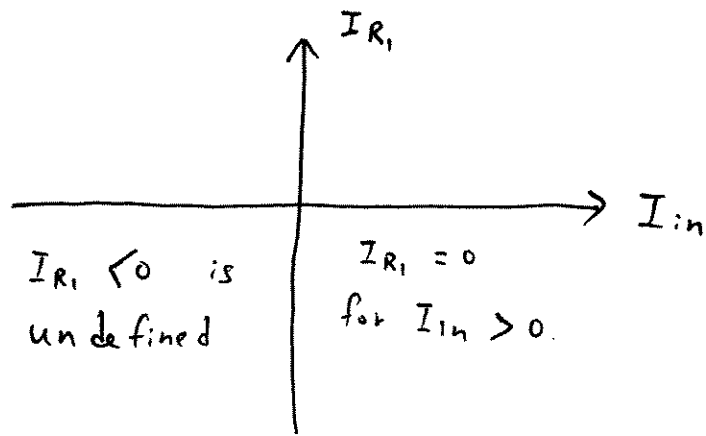


c)

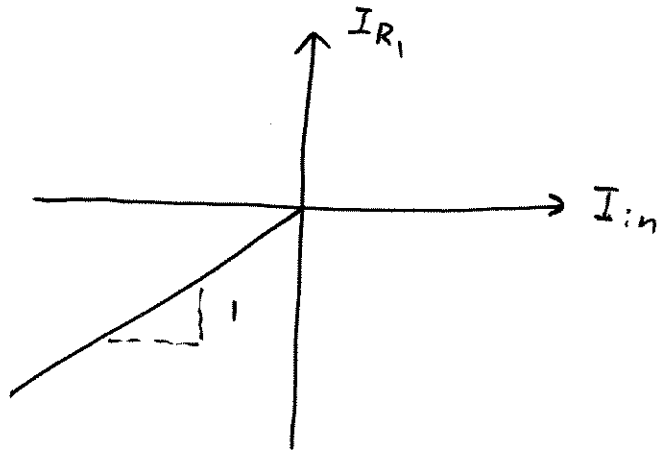


d)

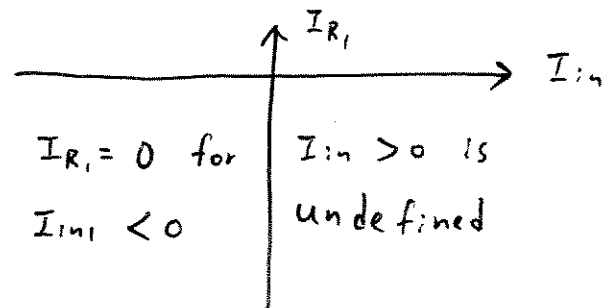


e)

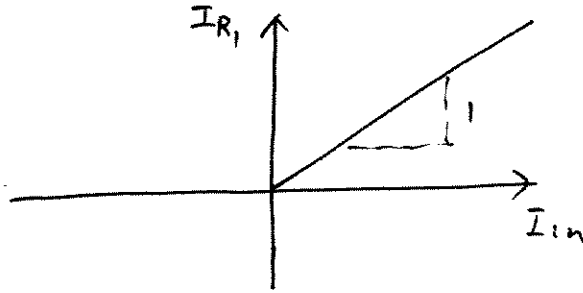


f)

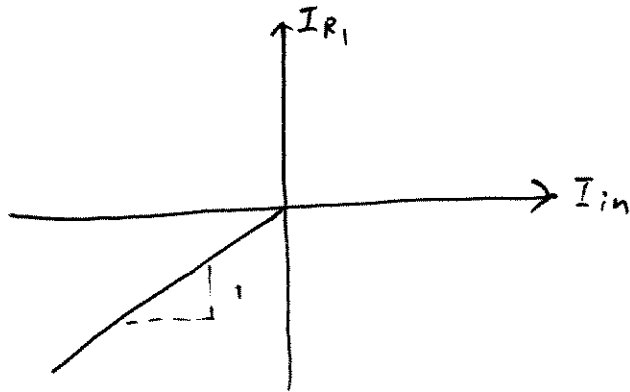

g)

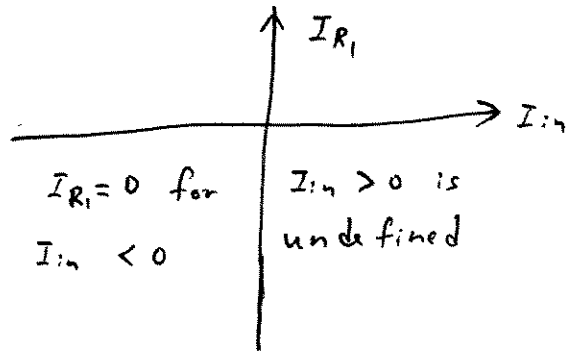


h)

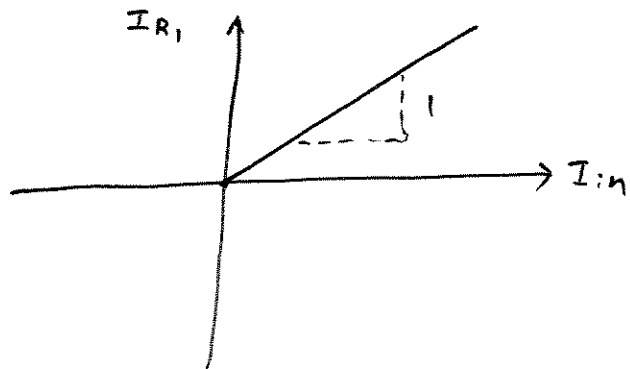

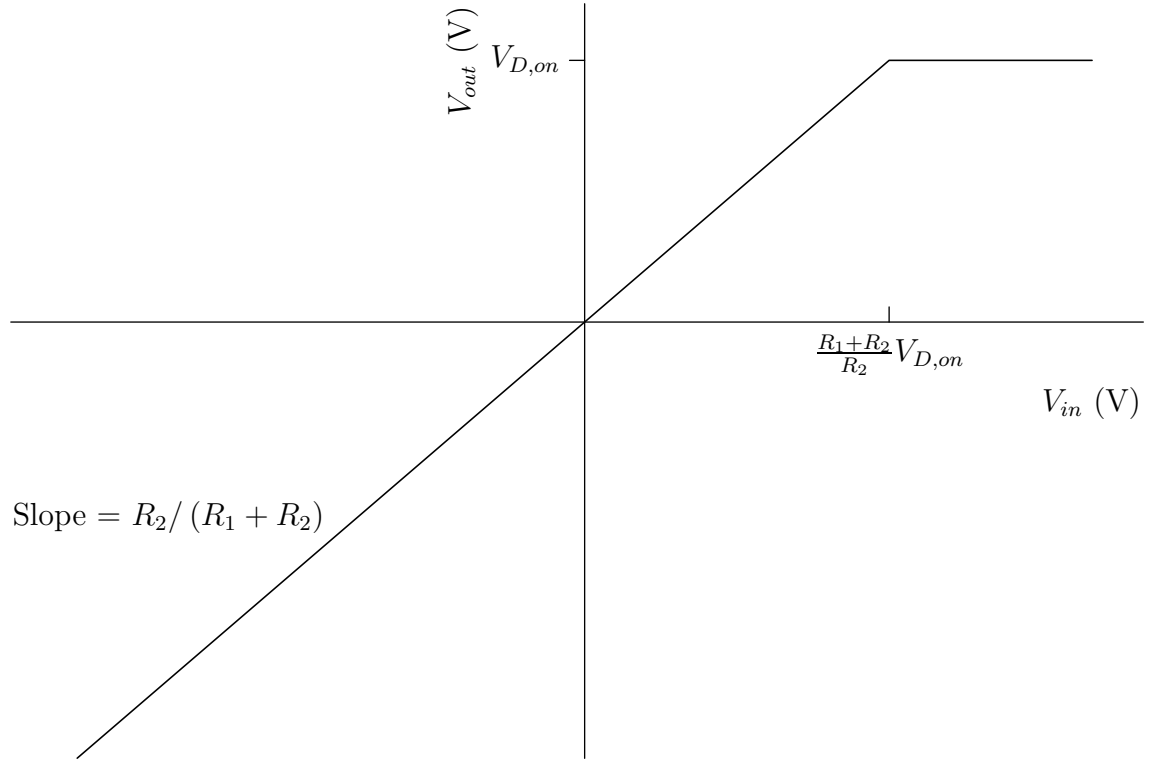
3.23 (a)

$$V_{out} = \begin{cases} \frac{R_2}{R_1+R_2} V_{in} & V_{in} < \frac{R_1+R_2}{R_2} V_{D,on} \\ V_{D,on} & V_{in} > \frac{R_1+R_2}{R_2} V_{D,on} \end{cases}$$



(b)
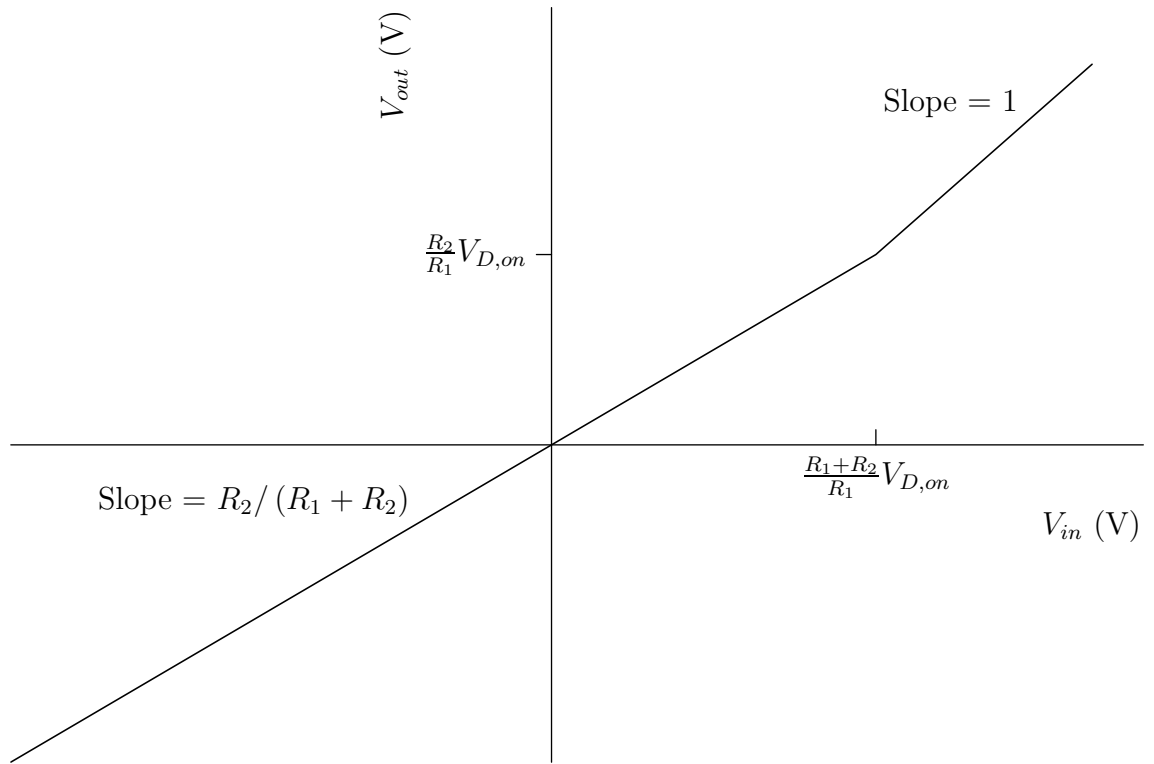
$$V_{out} = \begin{cases} \frac{R_2}{R_1+R_2} V_{in} & V_{in} < \frac{R_1+R_2}{R_1} V_{D,on} \\ V_{in} - V_{D,on} & V_{in} > \frac{R_1+R_2}{R_1} V_{D,on} \end{cases}$$






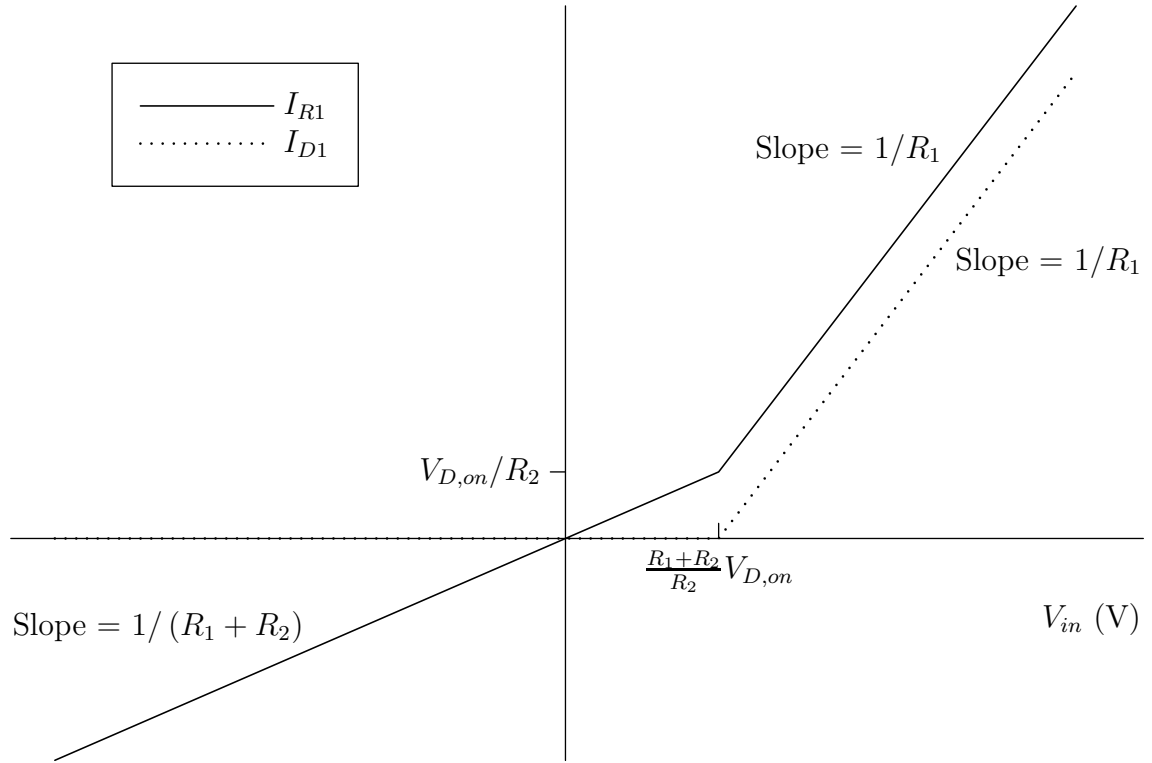3.24 (a)

$$I_{R1} = \begin{cases} \frac{V_{in}}{R_1+R_2} & V_{in} < \frac{R_1+R_2}{R_2} V_{D,on} \\ \frac{V_{in}-V_{D,on}}{R_1} & V_{in} > \frac{R_1+R_2}{R_2} V_{D,on} \end{cases}$$


$$I_{D1} = \begin{cases} 0 & V_{in} < \frac{R_1+R_2}{R_2} V_{D,on} \\ \frac{V_{in}-V_{D,on}}{R_1} - \frac{V_{D,on}}{R_2} & V_{in} > \frac{R_1+R_2}{R_2} V_{D,on} \end{cases}$$



(b)


$$I_{R1} = \begin{cases} \frac{V_{in}}{R_1+R_2} & V_{in} < \frac{R_1+R_2}{R_1} V_{D,on} \\ \frac{V_{D,on}}{R_1} & V_{in} > \frac{R_1+R_2}{R_1} V_{D,on} \end{cases}$$
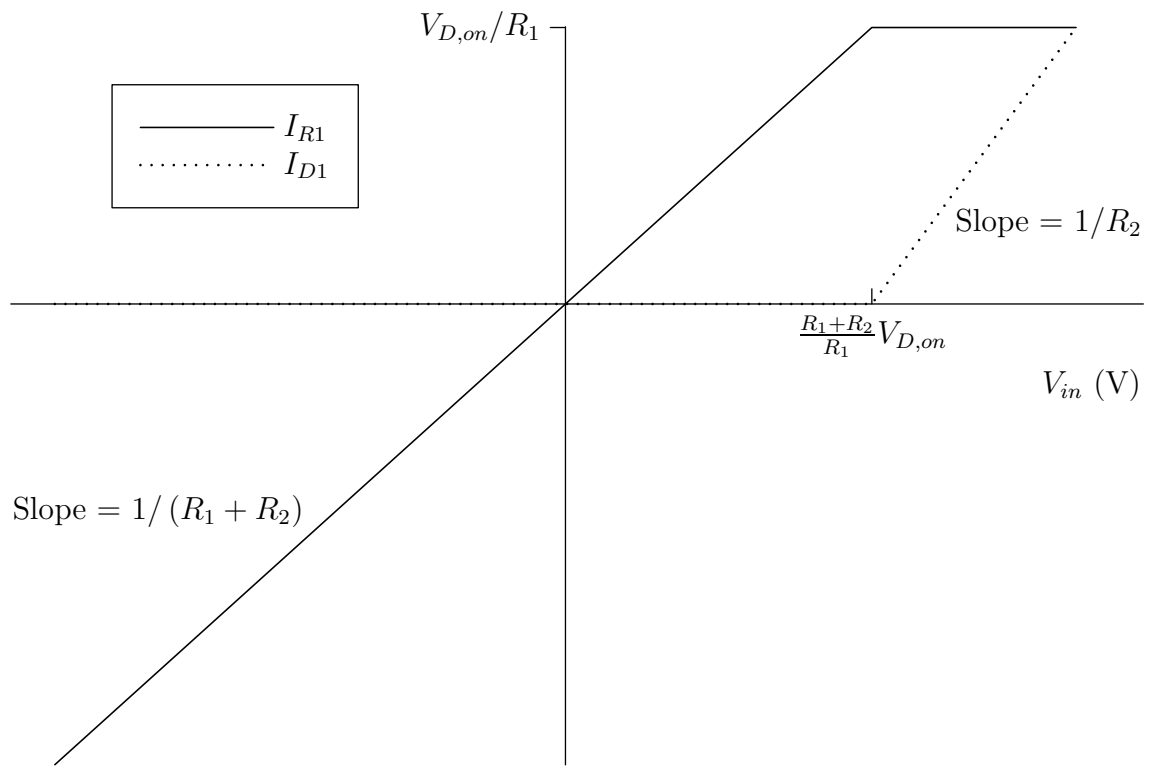
$$I_{D1} = \begin{cases} 0 & V_{in} < \frac{R_1+R_2}{R_1} V_{D,on} \\ \frac{V_{in}-V_{D,on}}{R_2} - \frac{V_{D,on}}{R_1} & V_{in} > \frac{R_1+R_2}{R_1} V_{D,on} \end{cases}$$



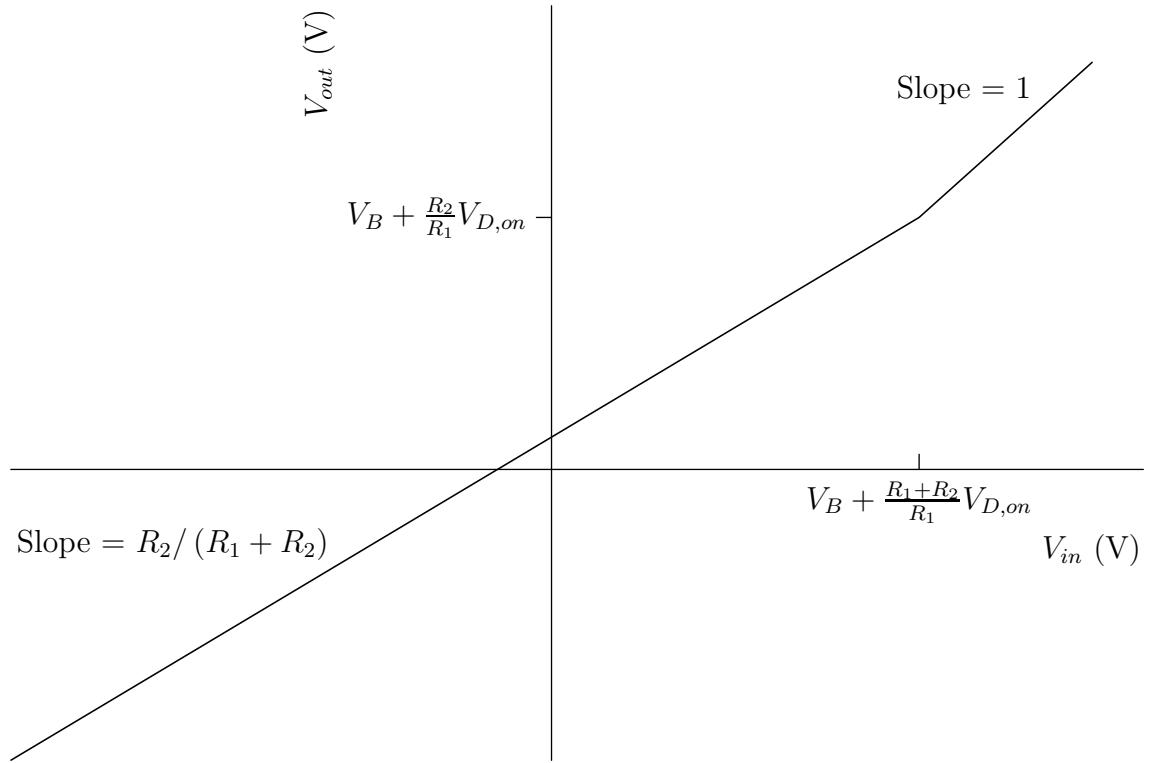
3.25 (a)

$$V_{out} = \begin{cases} V_B + \frac{R_2}{R_1+R_2} (V_{in} - V_B) & V_{in} < V_B + \frac{R_1+R_2}{R_1} V_{D,on} \\ V_{in} - V_{D,on} & V_{in} > V_B + \frac{R_1+R_2}{R_1} V_{D,on} \end{cases}$$




(b)
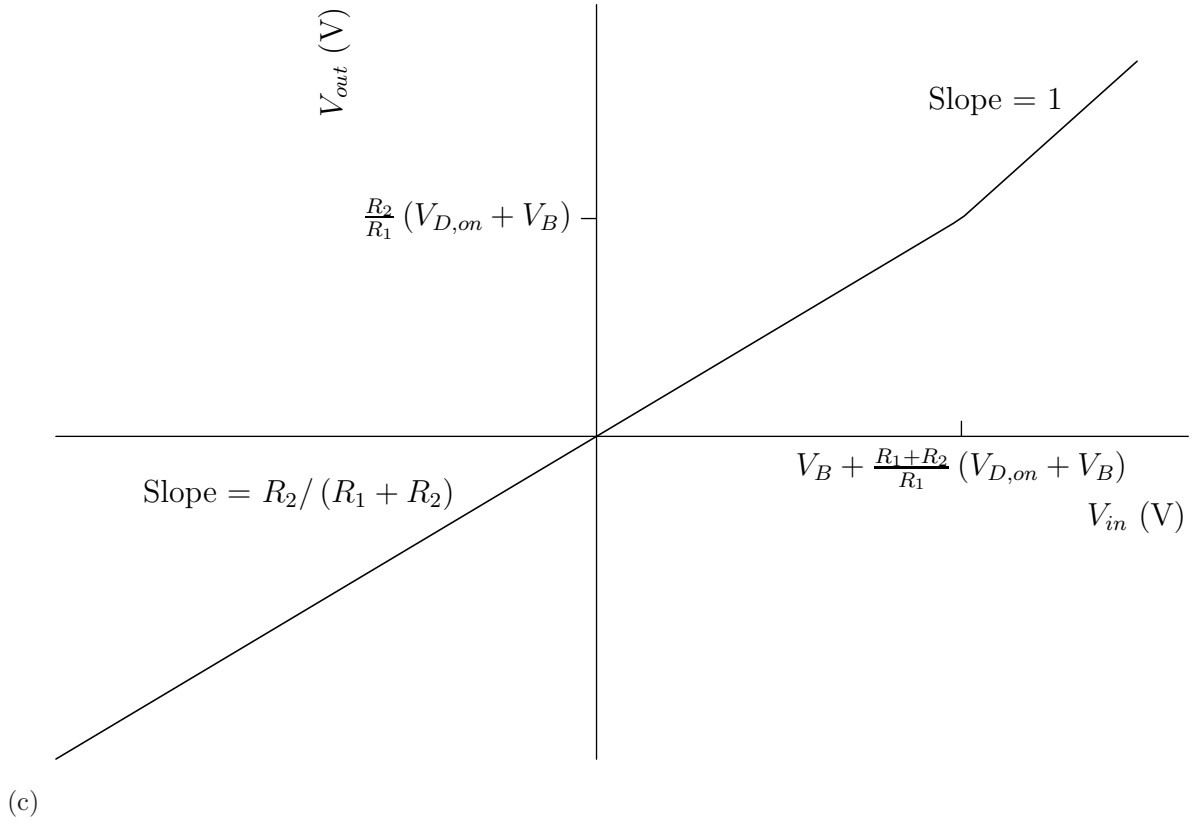
$$V_{out} = \begin{cases} \frac{R_2}{R_1+R_2} V_{in} & V_{in} < \frac{R_1+R_2}{R_1} (V_{D,on} + V_B) \\ V_{in} - V_{D,on} - V_B & V_{in} > \frac{R_1+R_2}{R_1} (V_{D,on} + V_B) \end{cases}$$



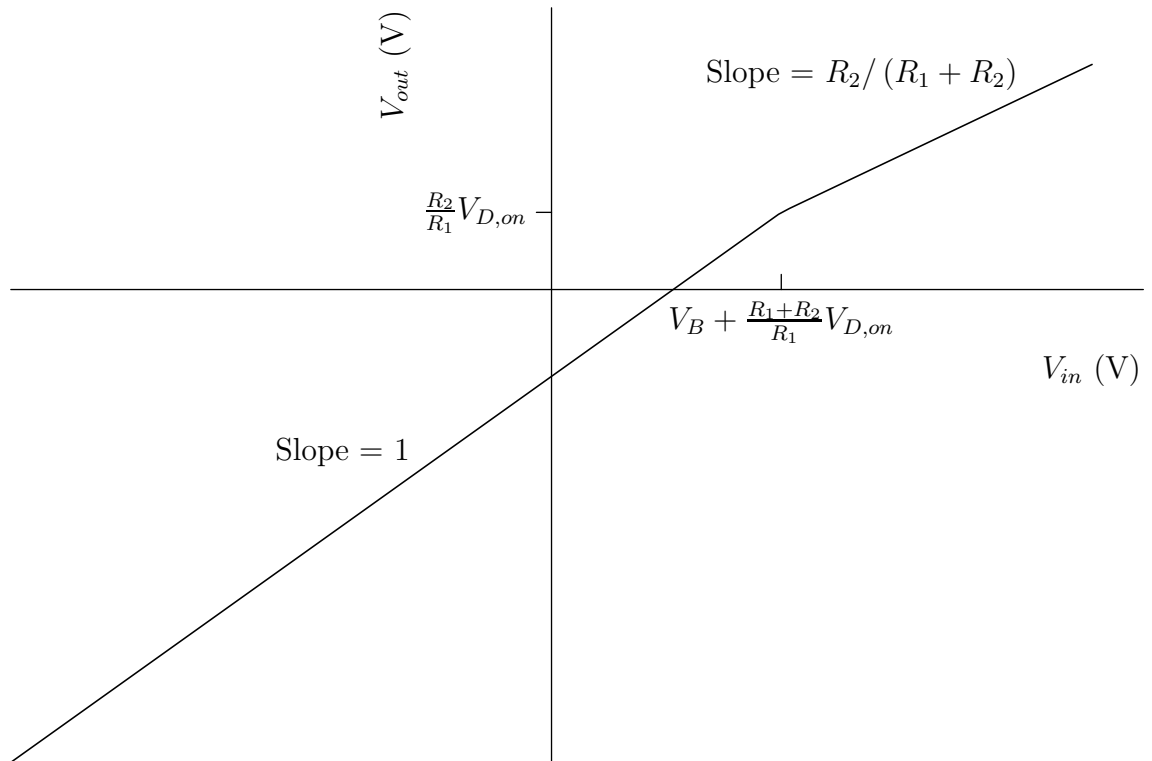
$$V_{out} = \begin{cases} \frac{R_2}{R_1 + R_2} (V_{in} - V_B) & V_{in} > V_B + \frac{R_1 + R_2}{R_1} V_{D,on} \\ V_{in} + V_{D,on} - V_B & V_{in} < V_B + \frac{R_1 + R_2}{R_1} V_{D,on} \end{cases}$$



(d)

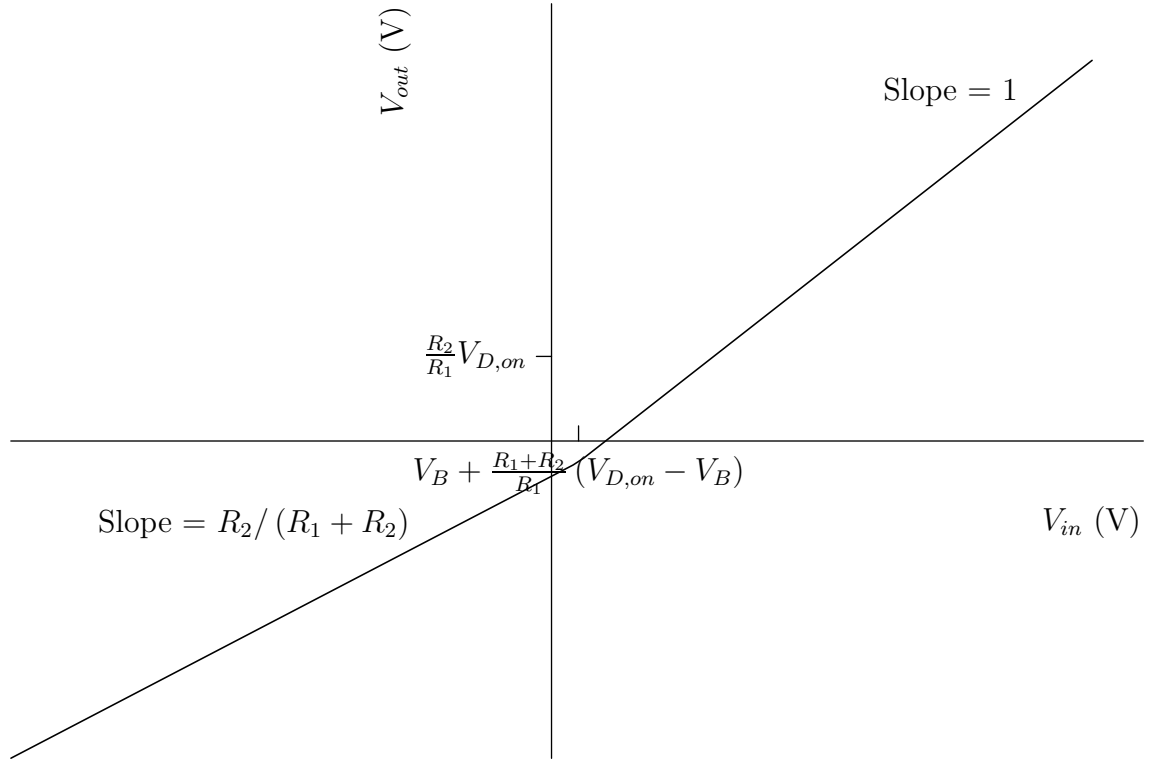
$$V_{out} = \begin{cases} \frac{R_2}{R_1+R_2} (V_{in} - V_B) & V_{in} < V_B + \frac{R_1+R_2}{R_1} (V_{D,on} - V_B) \\ V_{in} - V_{D,on} & V_{in} > V_B + \frac{R_1+R_2}{R_1} (V_{D,on} - V_B) \end{cases}$$



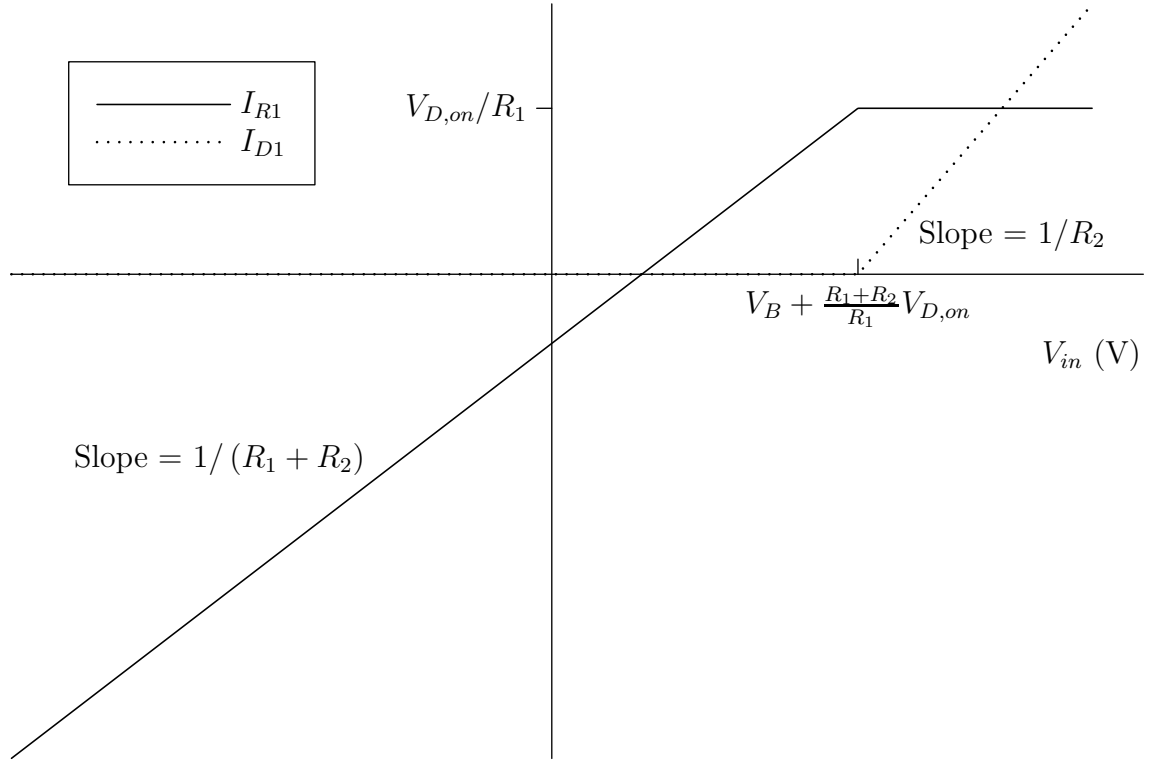3.26 (a)

$$I_{R1} = \begin{cases} \frac{V_{in} - V_B}{R_1 + R_2} & V_{in} < V_B + \frac{R_1 + R_2}{R_1} V_{D,on} \\ \frac{V_{D,on}}{R_1} & V_{in} > V_B + \frac{R_1 + R_2}{R_1} V_{D,on} \end{cases}$$


$$I_{D1} = \begin{cases} 0 & V_{in} < V_B + \frac{R_1 + R_2}{R_1} V_{D,on} \\ \frac{V_{in} - V_{D,on} - V_B}{R_2} - \frac{V_{D,on}}{R_1} & V_{in} > V_B + \frac{R_1 + R_2}{R_1} V_{D,on} \end{cases}$$



(b)


$$I_{R1} = \begin{cases} \frac{V_{in}}{R_1 + R_2} & V_{in} < \frac{R_1 + R_2}{R_1} (V_{D,on} + V_B) \\ \frac{V_{D,on} + V_B}{R_1} & V_{in} > \frac{R_1 + R_2}{R_1} (V_{D,on} + V_B) \end{cases}$$
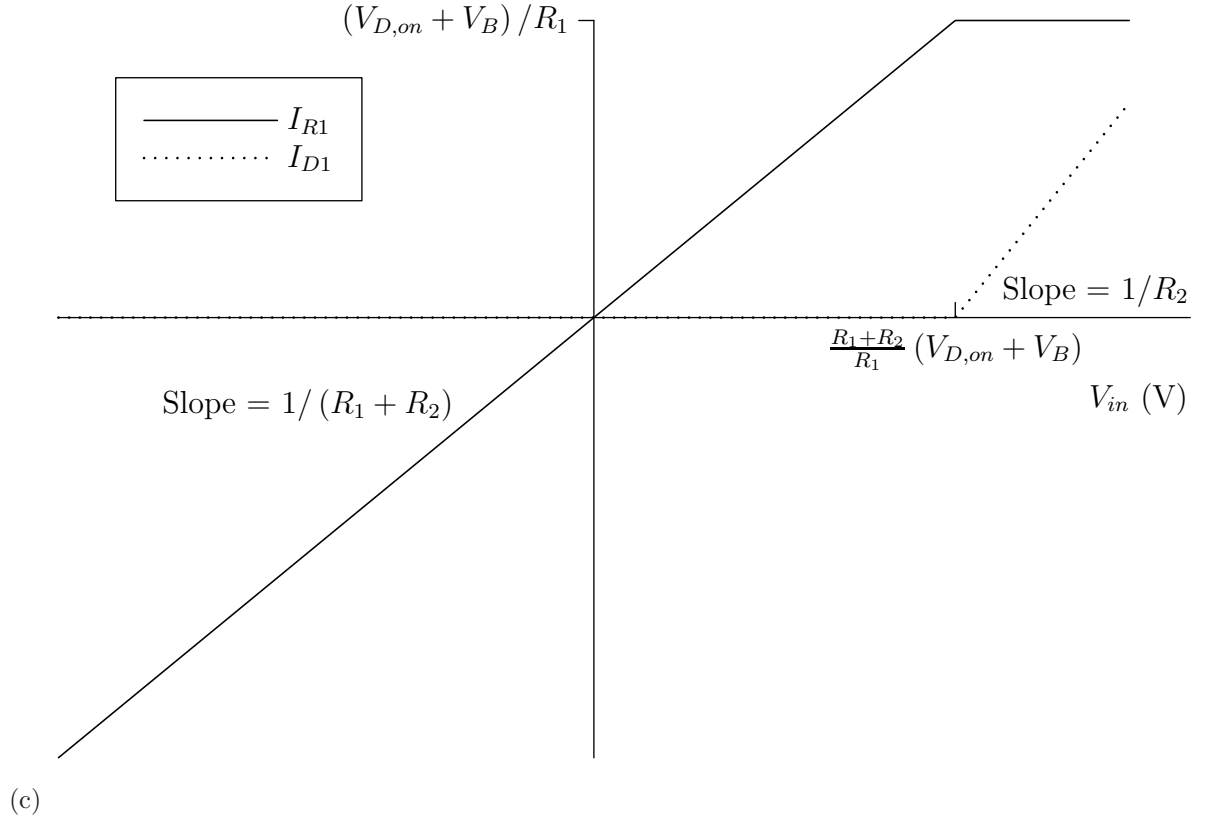
$$I_{D1} = \begin{cases} 0 & V_{in} < \frac{R_1 + R_2}{R_1} (V_{D,on} + V_B) \\ \frac{V_{in} - V_{D,on} - V_B}{R_2} - \frac{V_{D,on} + V_B}{R_1} & V_{in} > \frac{R_1 + R_2}{R_1} (V_{D,on} + V_B) \end{cases}$$



$$I_{R1} = \begin{cases} \frac{V_{in} - V_B}{R_1 + R_2} & V_{in} > V_B - \frac{R_1 + R_2}{R_1} V_{D,on} \\ -\frac{V_{D,on}}{R_1} & V_{in} < V_B - \frac{R_1 + R_2}{R_1} V_{D,on} \end{cases}$$
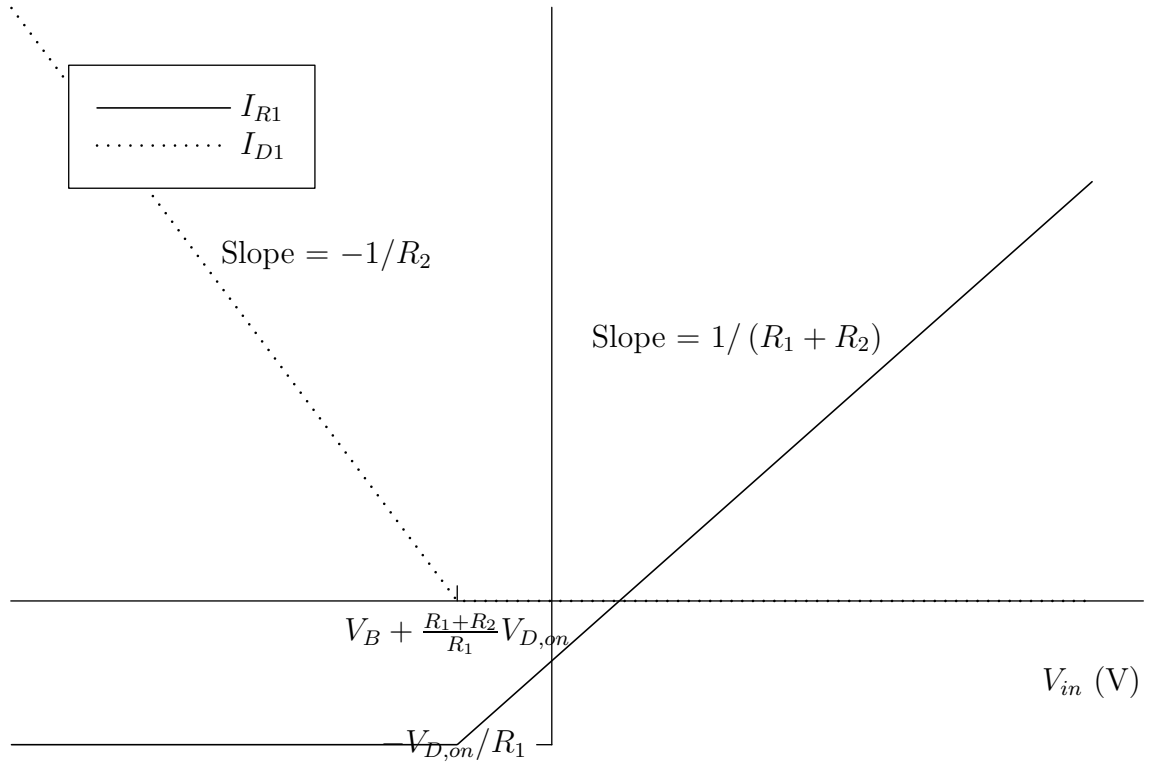
$$I_{D1} = \begin{cases} 0 & V_{in} > V_B - \frac{R_1 + R_2}{R_1} V_{D,on} \\ -\frac{V_{in} + V_{D,on} + V_B}{R_2} - \frac{V_{D,on}}{R_1} & V_{in} < V_B - \frac{R_1 + R_2}{R_1} V_{D,on} \end{cases}$$




(d)

$$I_{R1} = \begin{cases} \frac{V_{in} - V_B}{R_1 + R_2} & V_{in} < V_B + \frac{R_1 + R_2}{R_1} (V_{D,on} - V_B) \\ \frac{V_{D,on} - V_B}{R_1} & V_{in} > V_B + \frac{R_1 + R_2}{R_1} (V_{D,on} - V_B) \end{cases}$$

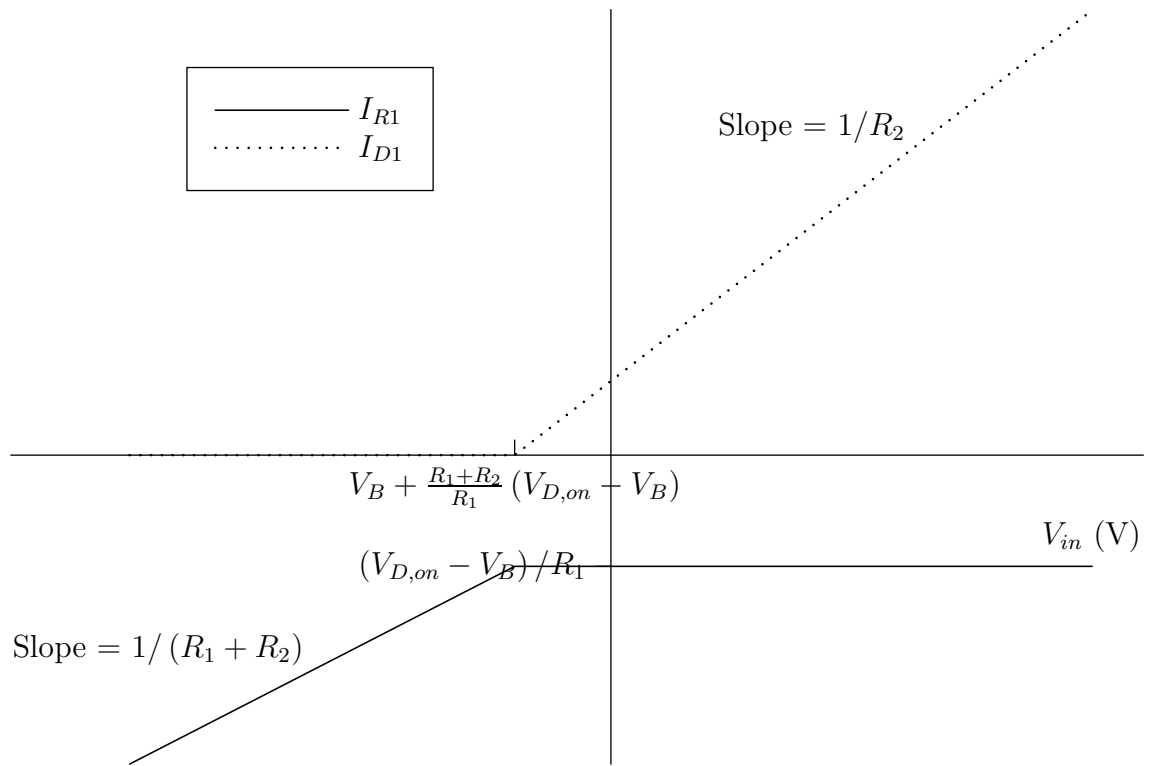
$$I_{D1} = \begin{cases} 0 & V_{in} < V_B + \frac{R_1 + R_2}{R_1} (V_{D,on} - V_B) \\ \frac{V_{in} - V_{D,on}}{R_2} - \frac{V_{D,on} - V_B}{R_1} & V_{in} > V_B + \frac{R_1 + R_2}{R_1} (V_{D,on} - V_B) \end{cases}$$





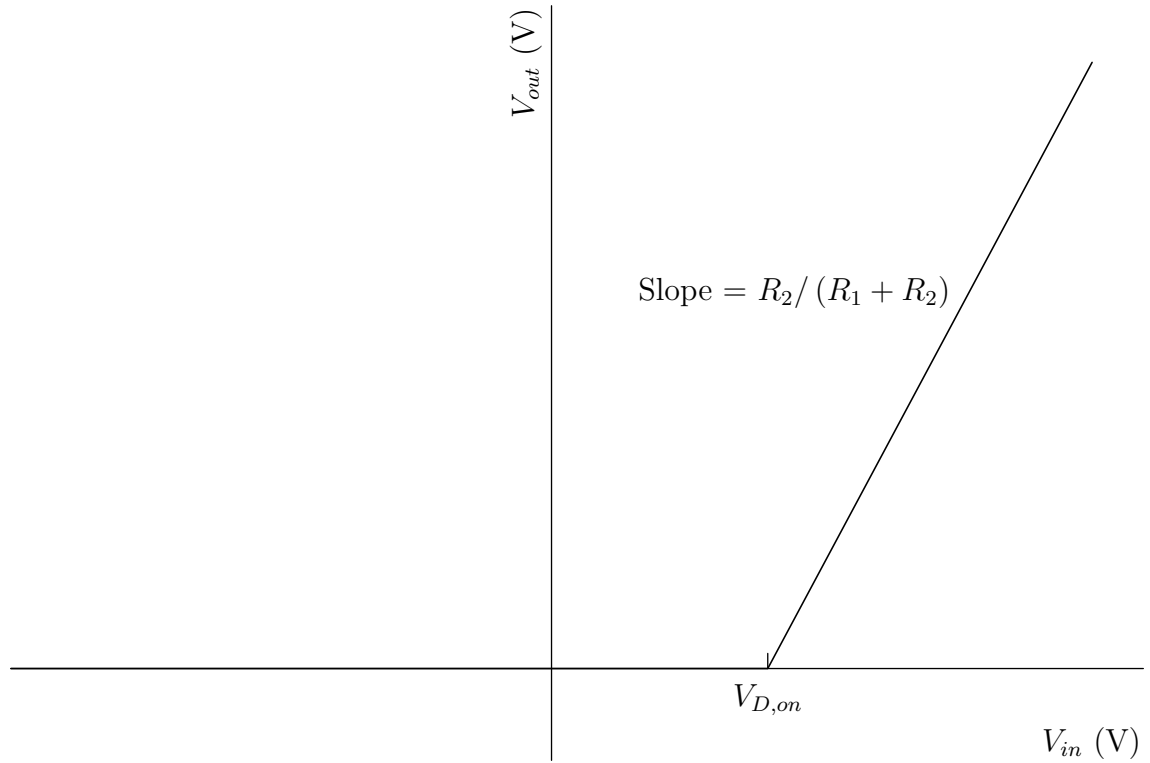
3.27 (a)

$$V_{out} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{R_2}{R_1+R_2} (V_{in} - V_{D,on}) & V_{in} > V_{D,on} \end{cases}$$




(b)
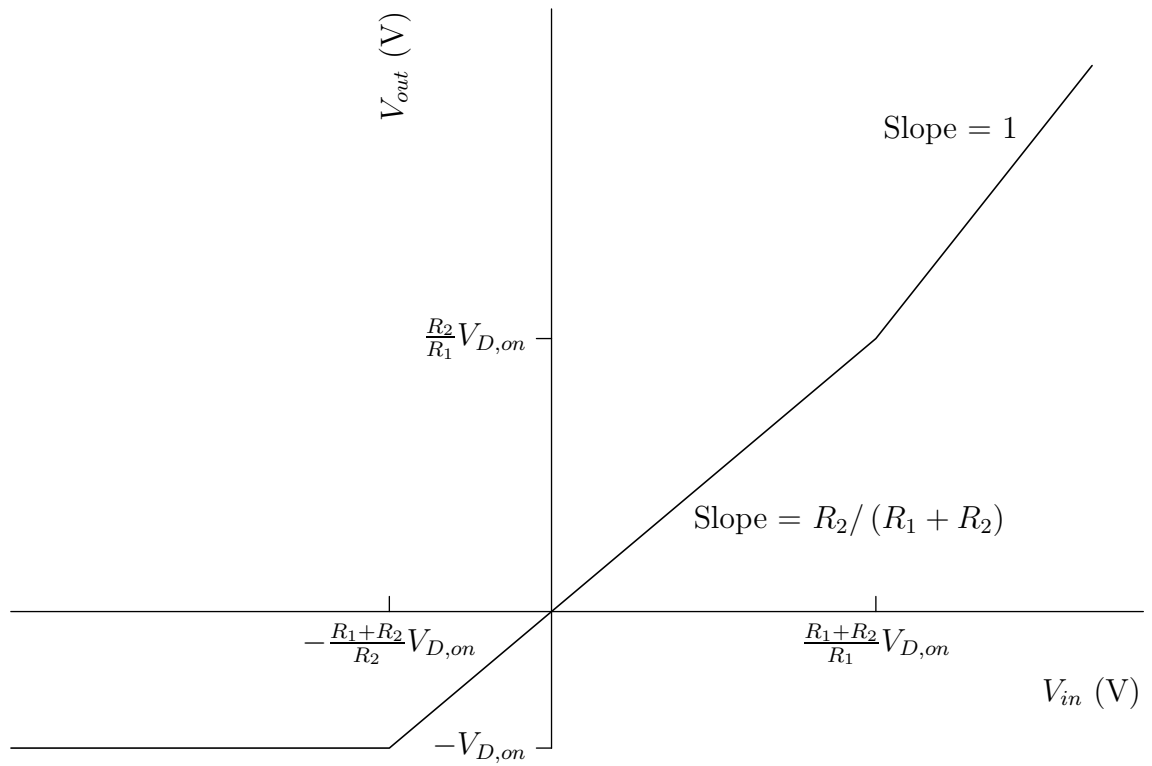
$$V_{out} = \begin{cases} -V_{D,on} & V_{in} < -\frac{R_1+R_2}{R_2} V_{D,on} \\ \frac{R_2}{R_1+R_2} V_{in} & -\frac{R_1+R_2}{R_2} V_{D,on} < V_{in} < \frac{R_1+R_2}{R_1} V_{D,on} \\ V_{in} - V_{D,on} & V_{in} > \frac{R_1+R_2}{R_1} V_{D,on} \end{cases}$$




(c)
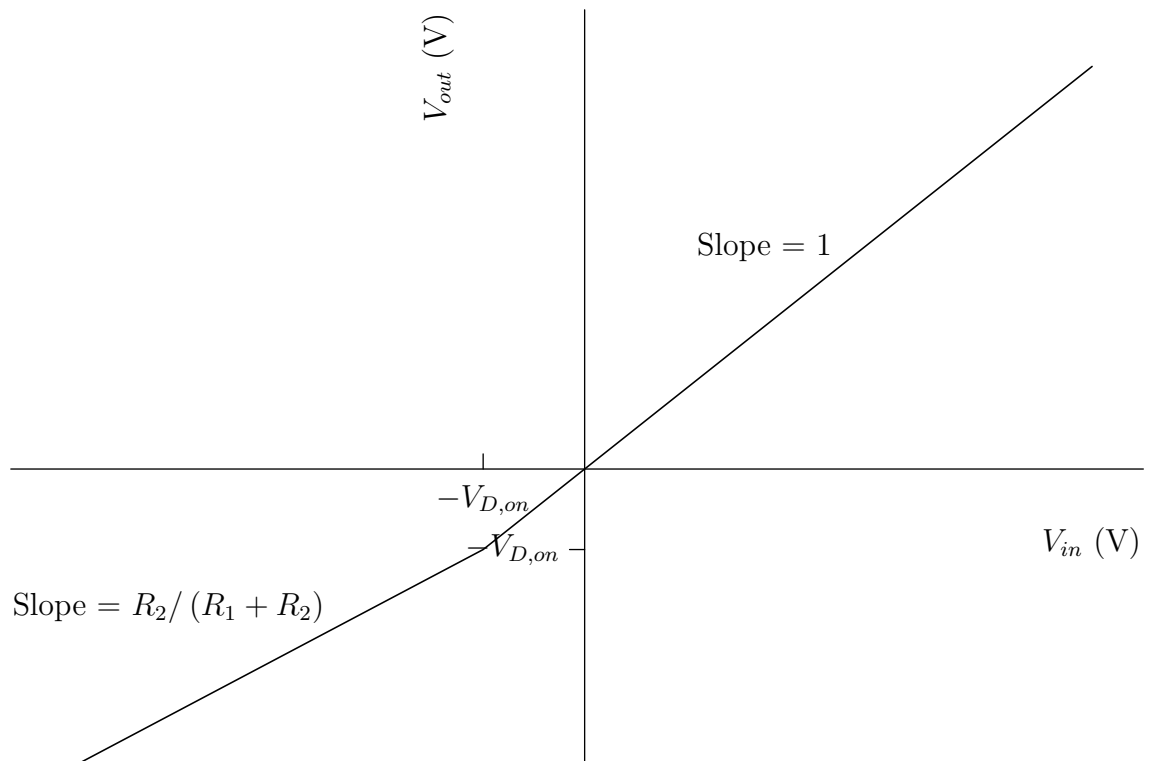
$$V_{out} = \begin{cases} \frac{R_2}{R_1+R_2} (V_{in} + V_{D,on}) - V_{D,on} & V_{in} < -V_{D,on} \\ V_{in} & V_{in} > -V_{D,on} \end{cases}$$




(d)
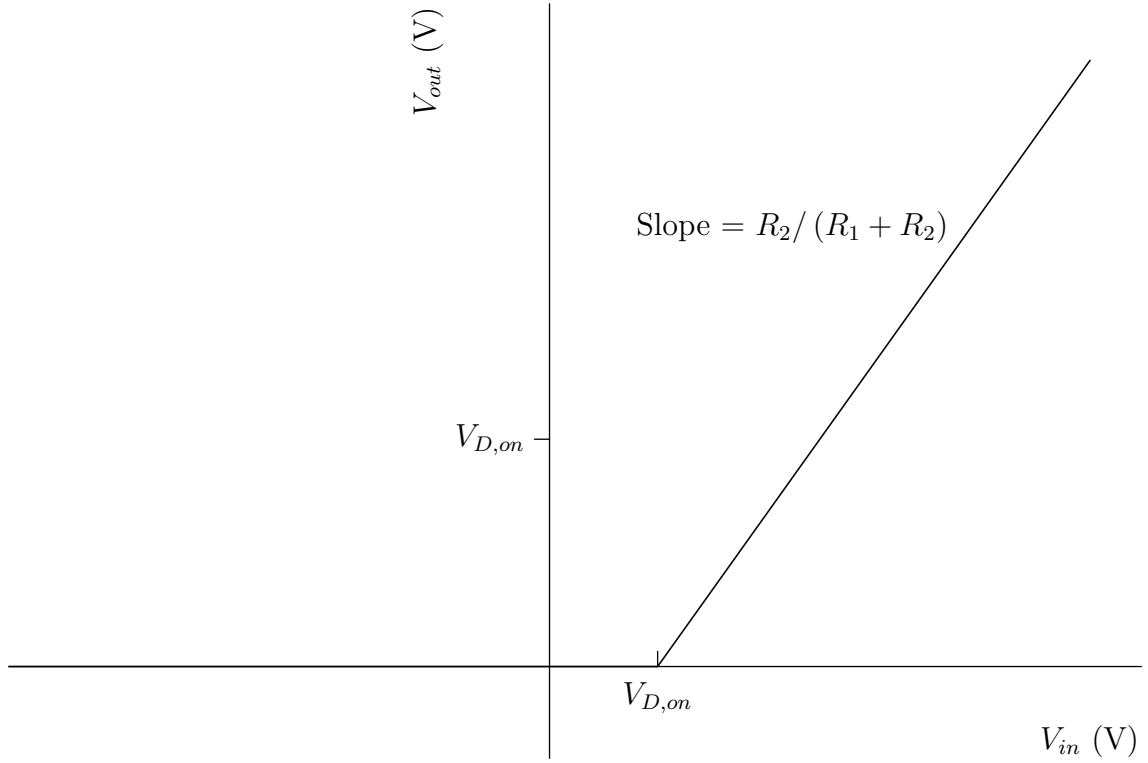
$$V_{out} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{R_2}{R_1+R_2} (V_{in} - V_{D,on}) & V_{in} > V_{D,on} \end{cases}$$



(e)

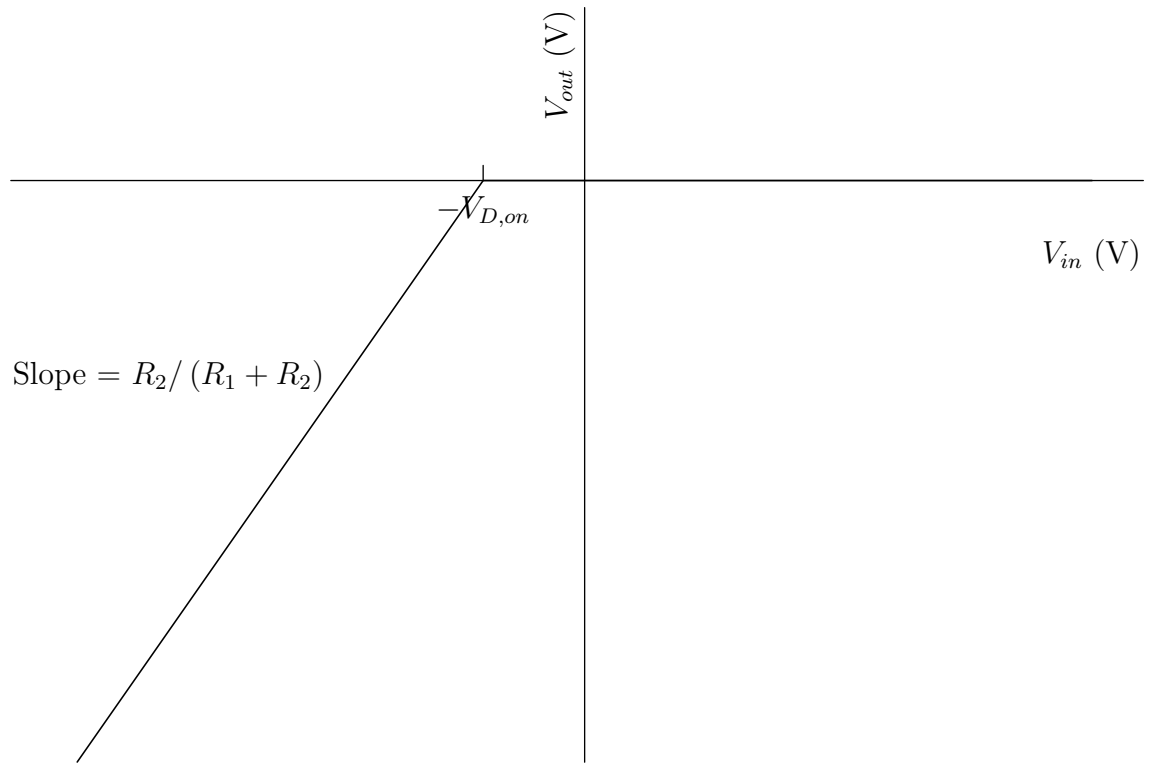
$$V_{out} = \begin{cases} \frac{R_2}{R_1+R_2} (V_{in} + V_{D,on}) & V_{in} < -V_{D,on} \\ 0 & V_{in} > -V_{D,on} \end{cases}$$



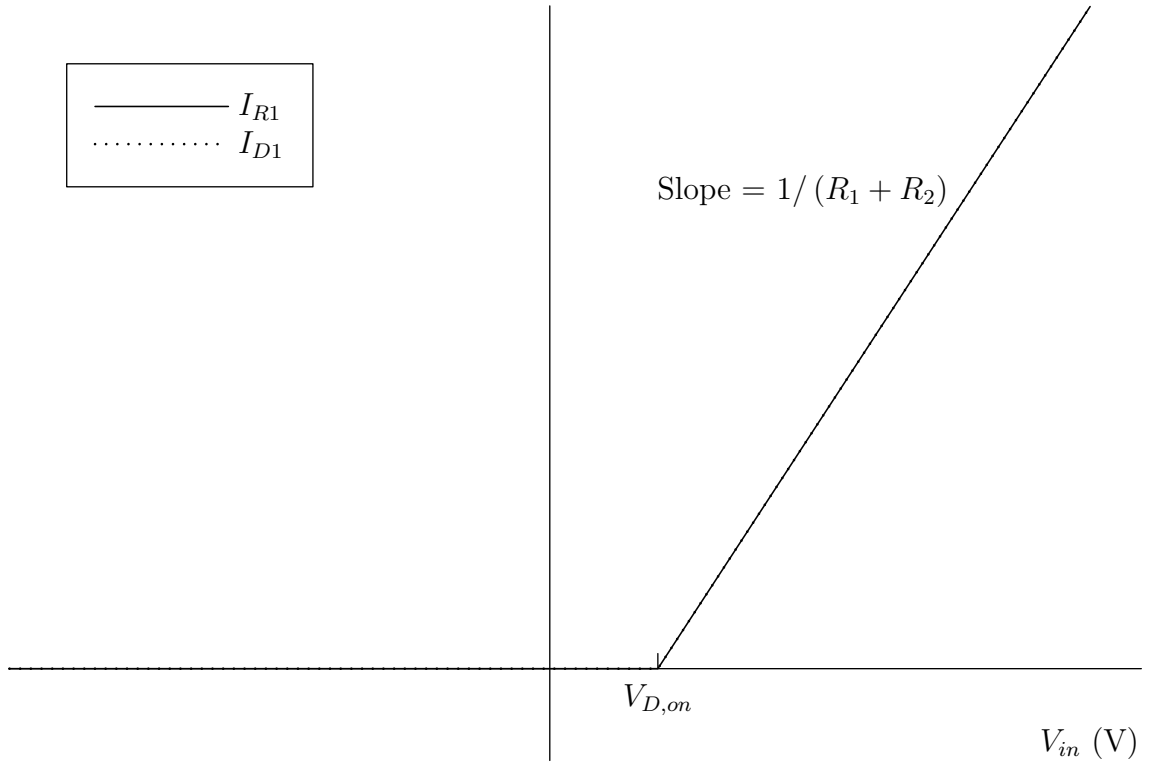3.28 (a)

$$I_{R1} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{in} > V_{D,on} \end{cases}$$


$$I_{D1} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{in} > V_{D,on} \end{cases}$$



(b)

$$I_{R1} = \begin{cases} \frac{V_{in} + V_{D,on}}{R_1} & V_{in} < -\frac{R_1 + R_2}{R_2} V_{D,on} \\ \frac{V_{in}}{R_1 + R_2} & -\frac{R_1 + R_2}{R_2} V_{D,on} < V_{in} < \frac{R_1 + R_2}{R_1} V_{D,on} \\ \frac{V_{D,on}}{R_1} & V_{in} > \frac{R_1 + R_2}{R_1} V_{D,on} \end{cases}$$

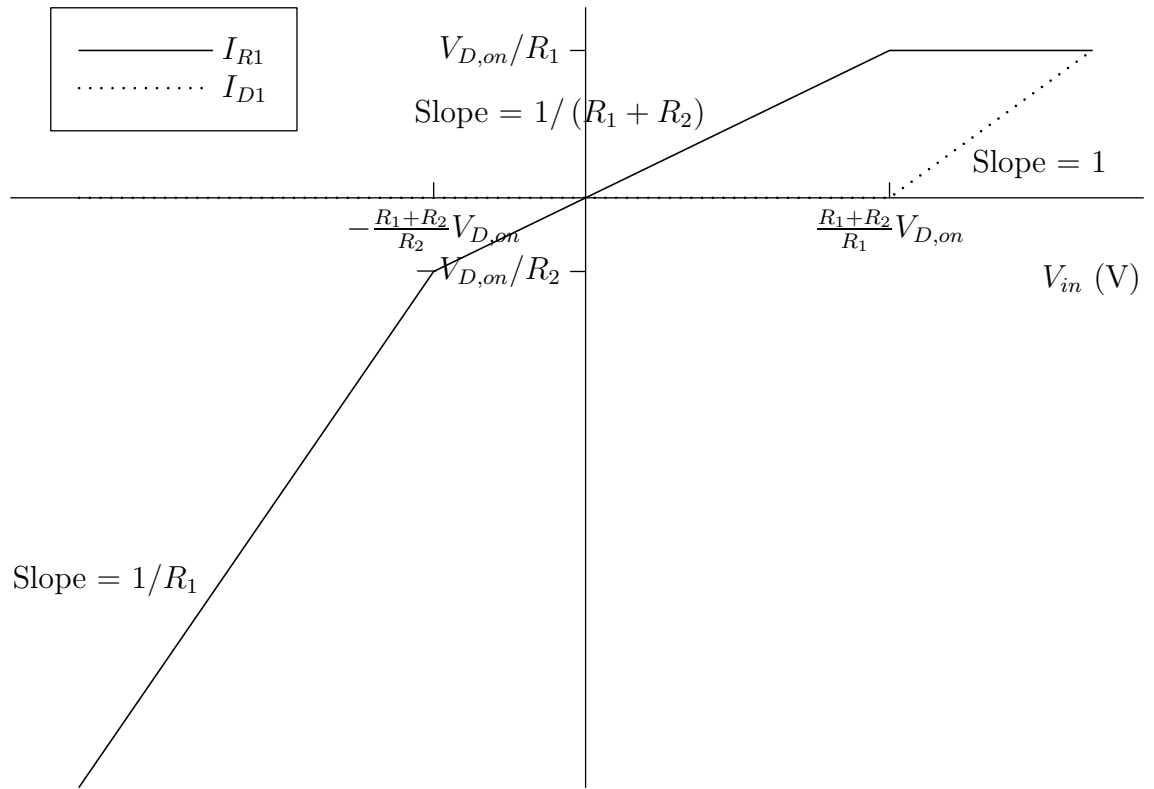
$$I_{D1} = \begin{cases} 0 & V_{in} < -\frac{R_1 + R_2}{R_2} V_{D,on} \\ 0 & -\frac{R_1 + R_2}{R_2} V_{D,on} < V_{in} < \frac{R_1 + R_2}{R_1} V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_2} - \frac{V_{D,on}}{R_1} & V_{in} > \frac{R_1 + R_2}{R_1} V_{D,on} \end{cases}$$



(c)

$$I_{R1} = \begin{cases} \frac{V_{in} + V_{D,on}}{R_1 + R_2} & V_{in} < -V_{D,on} \\ 0 & V_{in} > -V_{D,on} \end{cases}$$
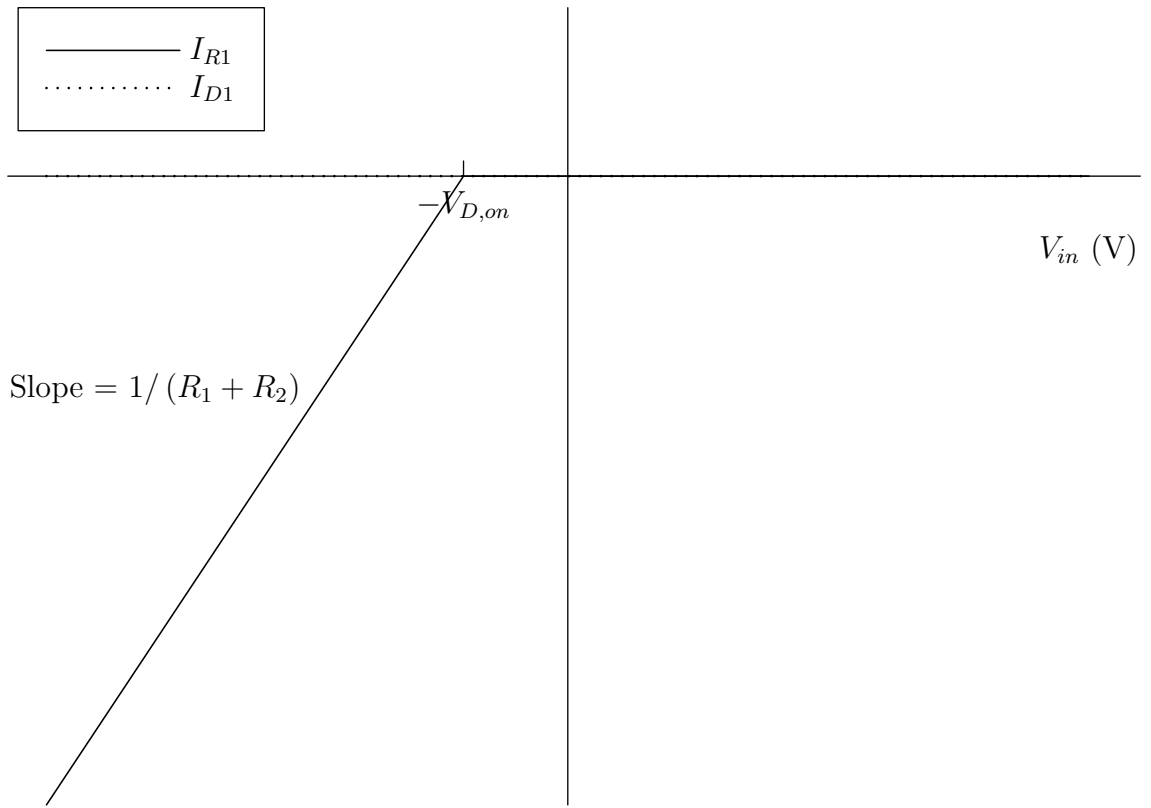
$$I_{D1} = \begin{cases} 0 & V_{in} < -V_{D,on} \\ 0 & V_{in} > -V_{D,on} \end{cases}$$




(d)

$$I_{R1} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{in} > V_{D,on} \end{cases}$$
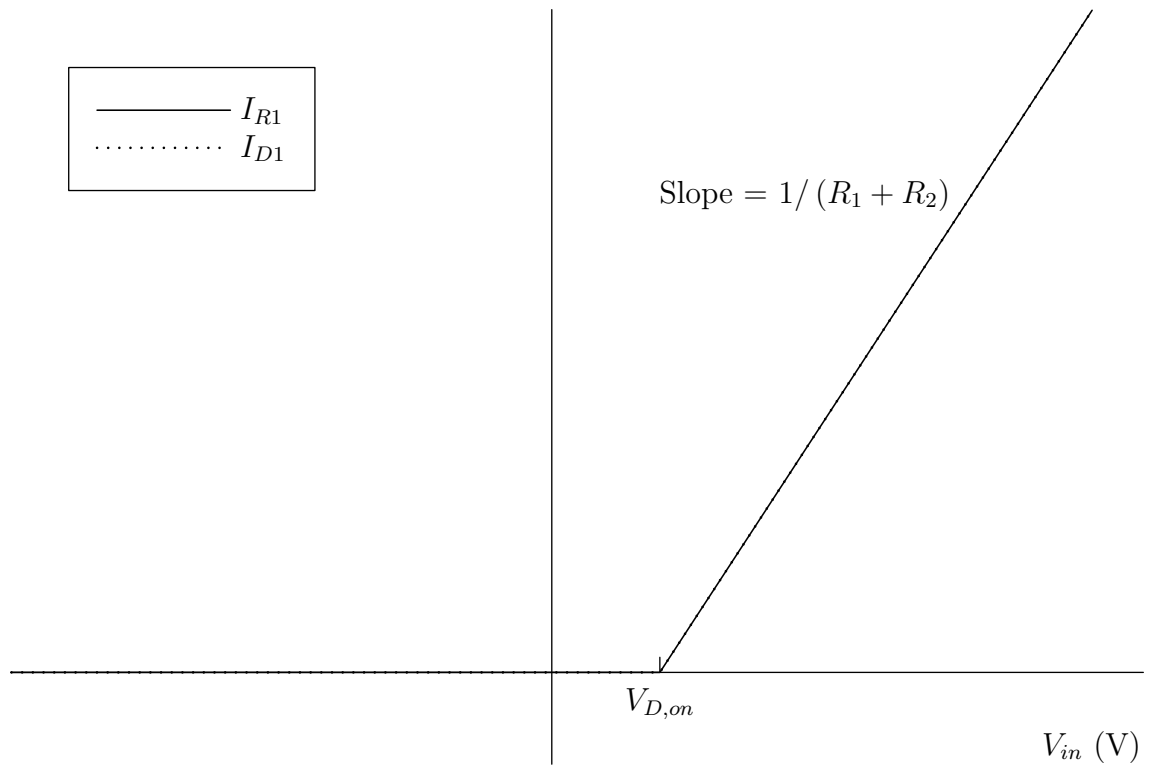
$$I_{D1} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{in} > V_{D,on} \end{cases}$$






(e)


$$I_{R1} = \begin{cases} \frac{V_{in} + V_{D,on}}{R_1 + R_2} & V_{in} < -V_{D,on} \\ 0 & V_{in} > -V_{D,on} \end{cases}$$
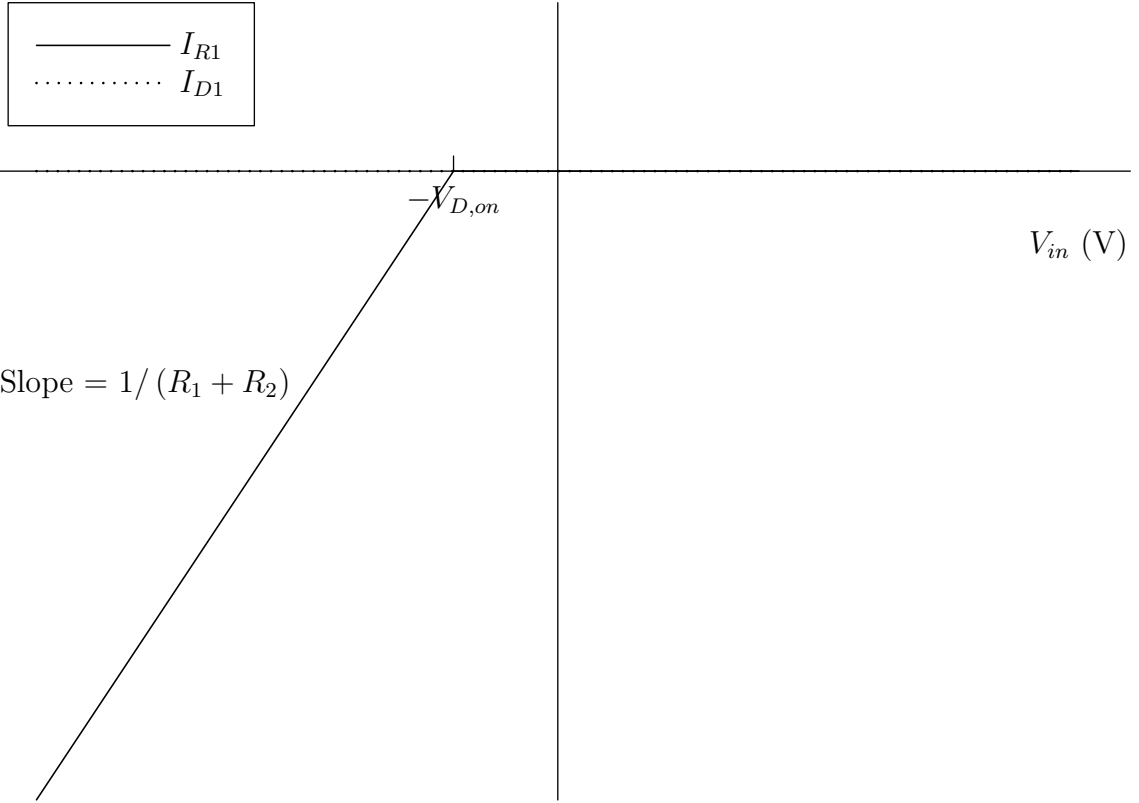
$$I_{D1} = \begin{cases} 0 & V_{in} < -V_{D,on} \\ 0 & V_{in} > -V_{D,on} \end{cases}$$



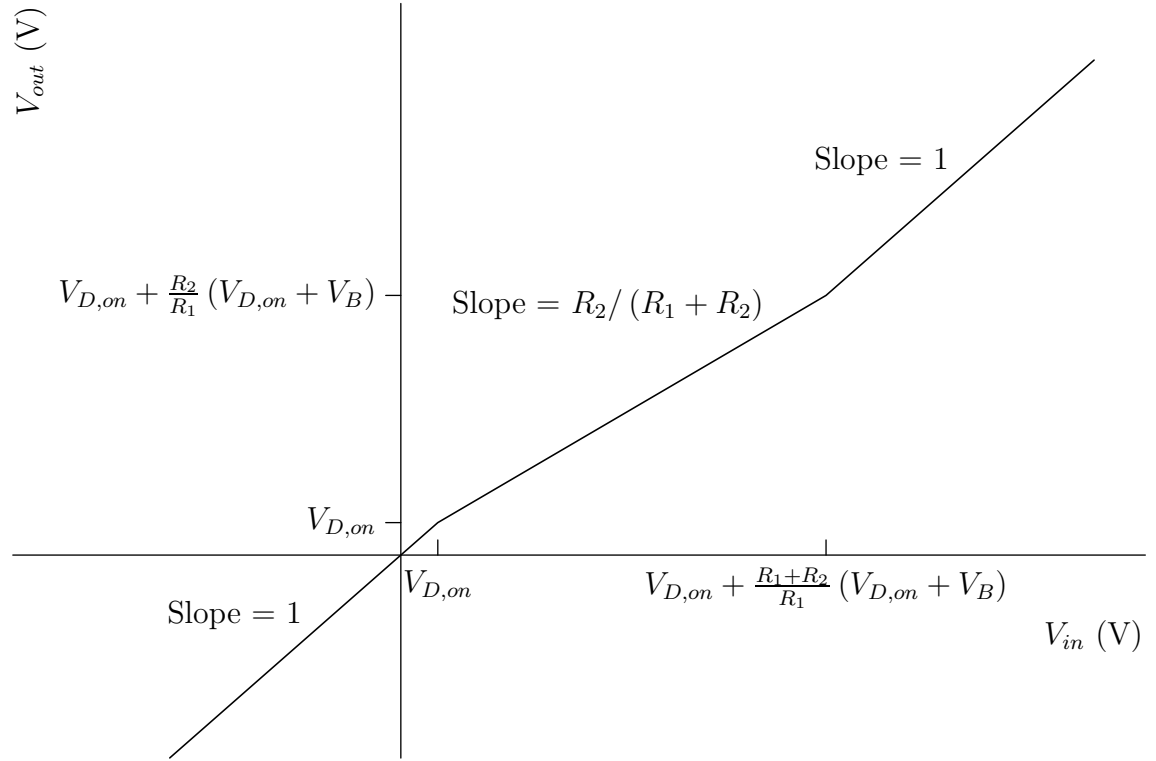
3.29 (a)

$$V_{out} = \begin{cases} V_{in} & V_{in} < V_{D,on} \\ V_{D,on} + \frac{R_2}{R_1+R_2} (V_{in} - V_{D,on}) & V_{D,on} < V_{in} < V_{D,on} + \frac{R_1+R_2}{R_1} (V_{D,on} + V_B) \\ V_{in} - V_{D,on} - V_B & V_{in} > V_{D,on} + \frac{R_1+R_2}{R_1} (V_{D,on} + V_B) \end{cases}$$




(b)
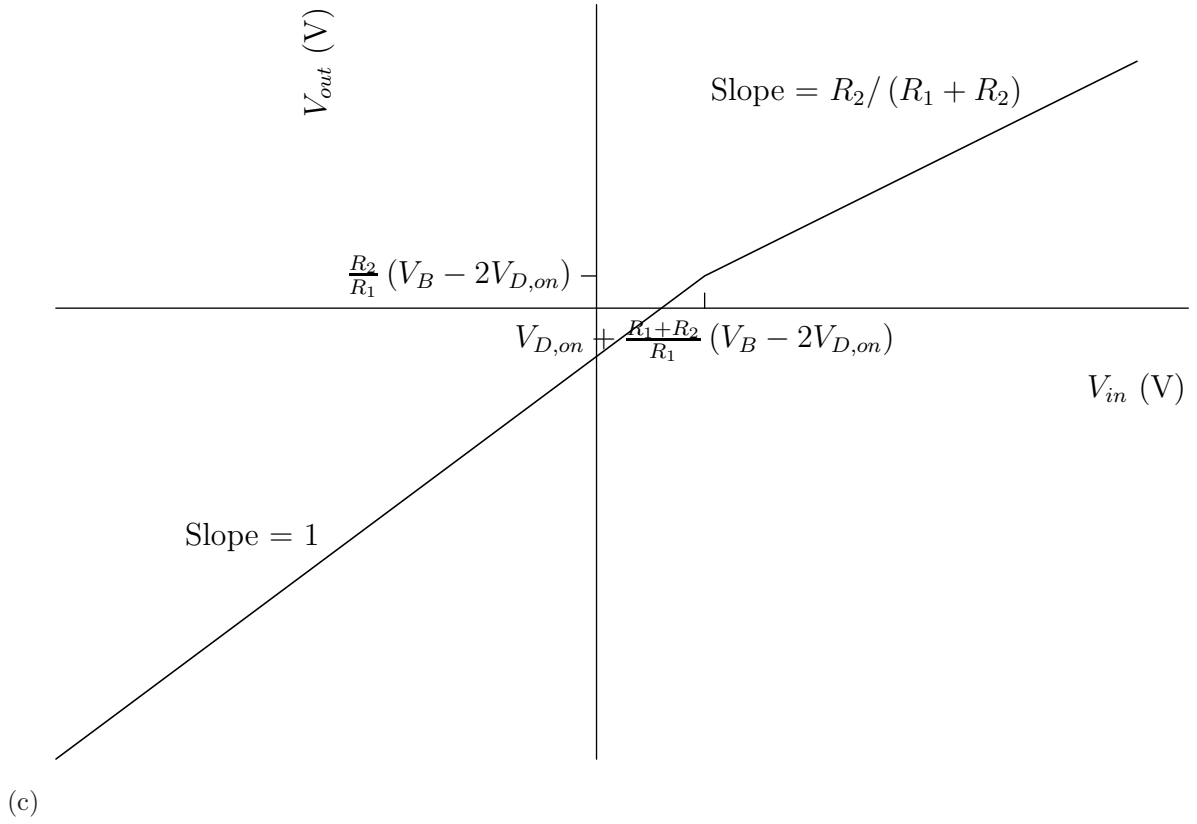
$$V_{out} = \begin{cases} V_{in} + V_{D,on} - V_B & V_{in} < V_{D,on} + \frac{R_1+R_2}{R_1} (V_B - 2V_{D,on}) \\ \frac{R_2}{R_1+R_2} (V_{in} - V_{D,on}) & V_{in} > V_{D,on} + \frac{R_1+R_2}{R_1} (V_B - 2V_{D,on}) \end{cases}$$



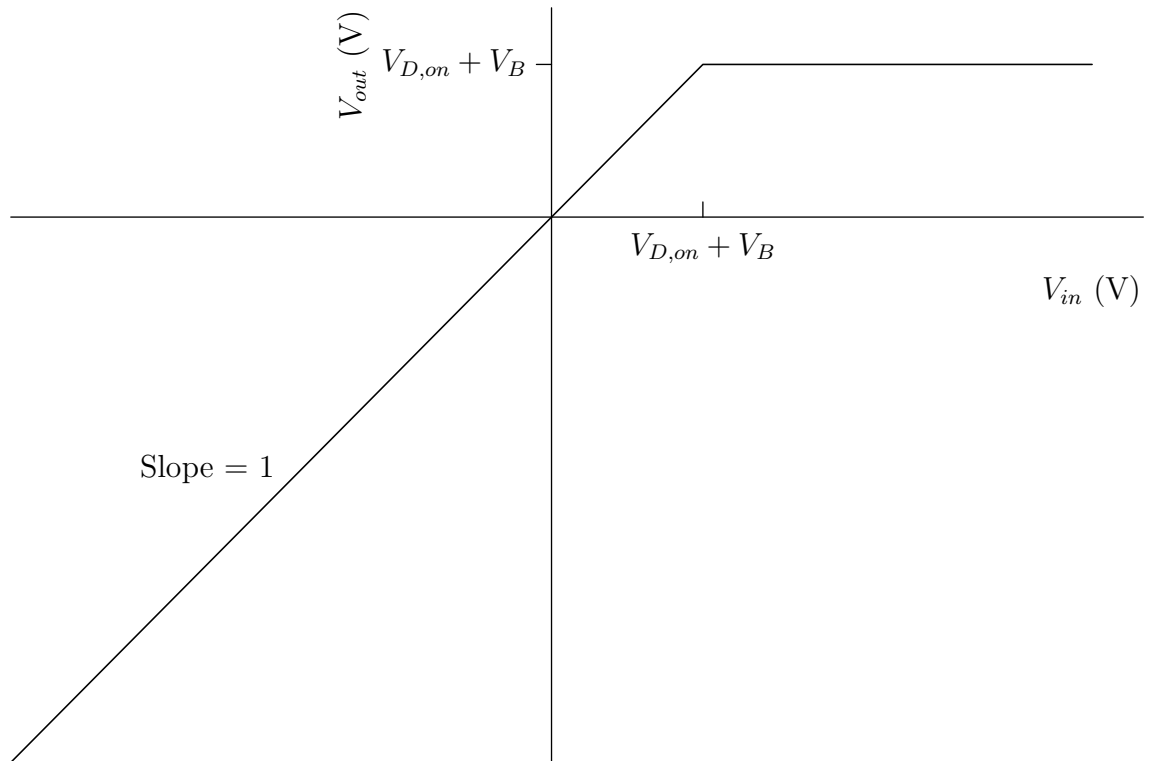
$$V_{out} = \begin{cases} V_{in} & V_{in} < V_{D,on} + V_B \\ V_{D,on} + V_B & V_{in} > V_{D,on} + V_B \end{cases}$$



(d)

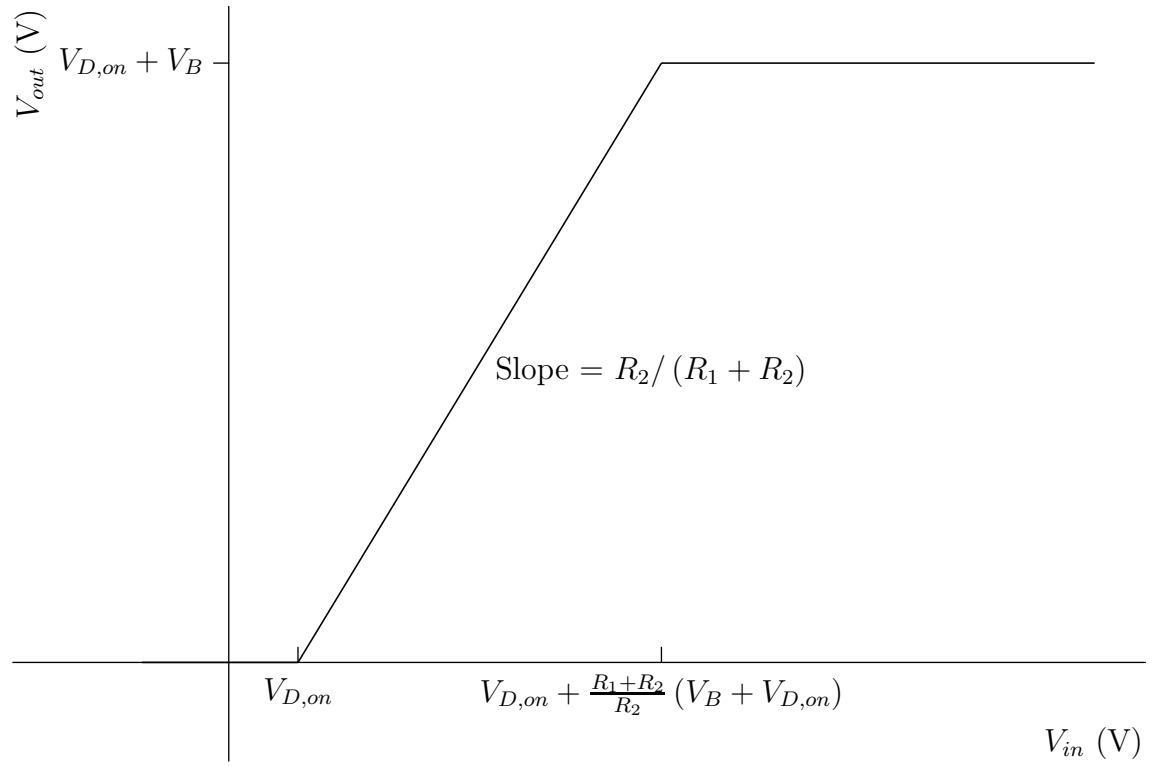
$$V_{out} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{R_2}{R_1+R_2} (V_{in} - V_{D,on}) & V_{D,on} < V_{in} < V_{D,on} + \frac{R_1+R_2}{R_2} (V_B + V_{D,on}) \\ V_{D,on} + V_B & V_{in} > V_{D,on} + \frac{R_1+R_2}{R_2} (V_B + V_{D,on}) \end{cases}$$



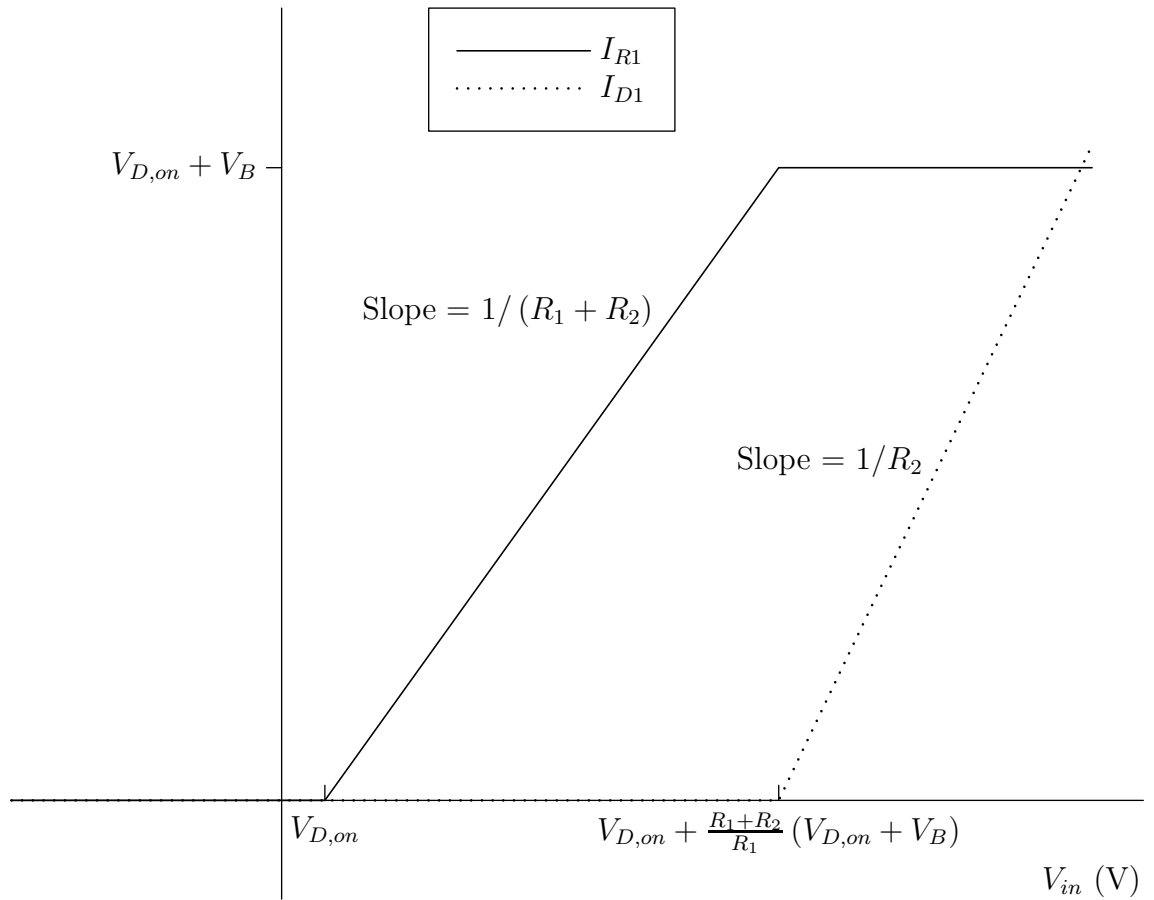3.30 (a)


$$I_{R1} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{D,on} < V_{in} < V_{D,on} + \frac{R_1 + R_2}{R_1} (V_{D,on} + V_B) \\ \frac{V_{D,on} + V_B}{R_1} & V_{in} > V_{D,on} + \frac{R_1 + R_2}{R_1} (V_{D,on} + V_B) \end{cases}$$

$$I_{D1} = \begin{cases} 0 & V_{in} < V_{D,on} + \frac{R_1 + R_2}{R_1} (V_{D,on} + V_B) \\ \frac{V_{in} - 2V_{D,on} - V_B}{R_2} - \frac{V_{D,on} + V_B}{R_1} & V_{in} > V_{D,on} + \frac{R_1 + R_2}{R_1} (V_{D,on} + V_B) \end{cases}$$



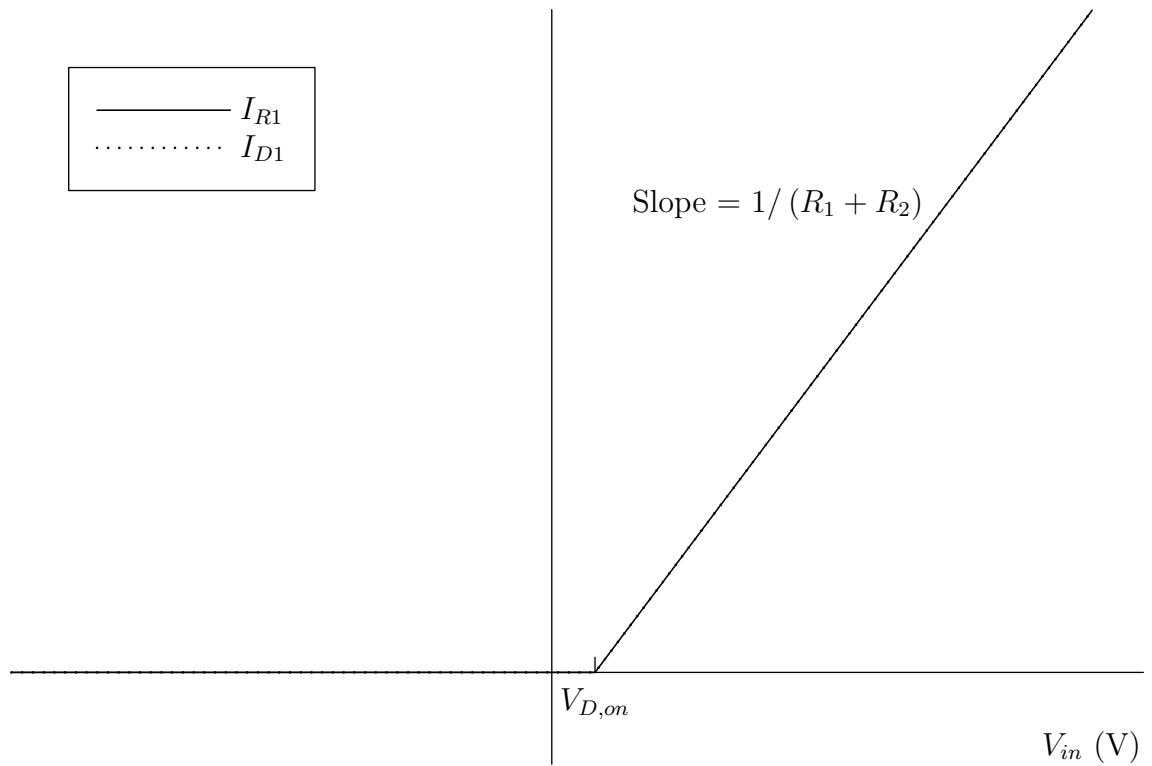
(b) If  $V_B < 2V_{D,on}$ :

$$I_{R1} = I_{D1} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{in} > V_{D,on} \end{cases}$$



If  $V_B > 2V_{D,on}$ :

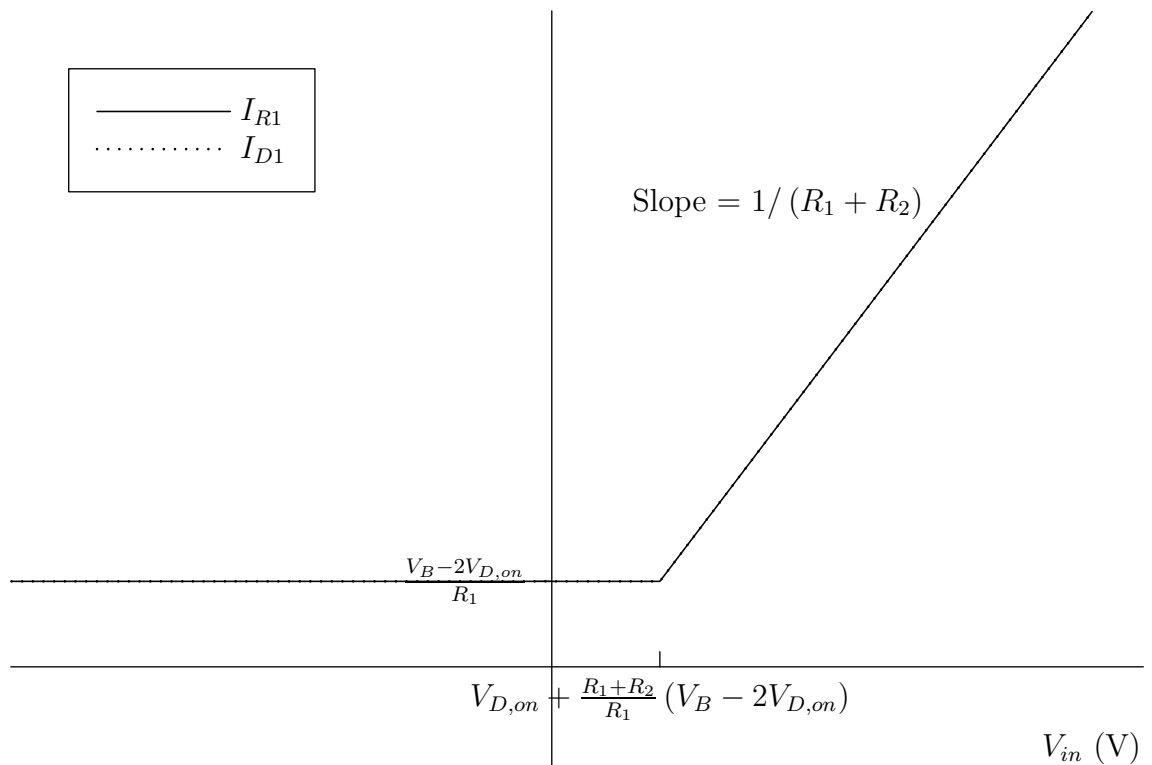
$$I_{R1} = I_{D1} = \begin{cases} \frac{V_B - 2V_{D,on}}{R_1} & V_{in} < V_{D,on} + \frac{R_1 + R_2}{R_1} (V_B - 2V_{D,on}) \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{in} > V_{D,on} + \frac{R_1 + R_2}{R_1} (V_B - 2V_{D,on}) \end{cases}$$



(c)

$$I_{R1} = \begin{cases} 0 & V_{in} < V_{D,on} + V_B \\ \frac{V_{in} - V_{D,on} - V_B}{R_1} & V_{in} > V_{D,on} + V_B \end{cases}$$
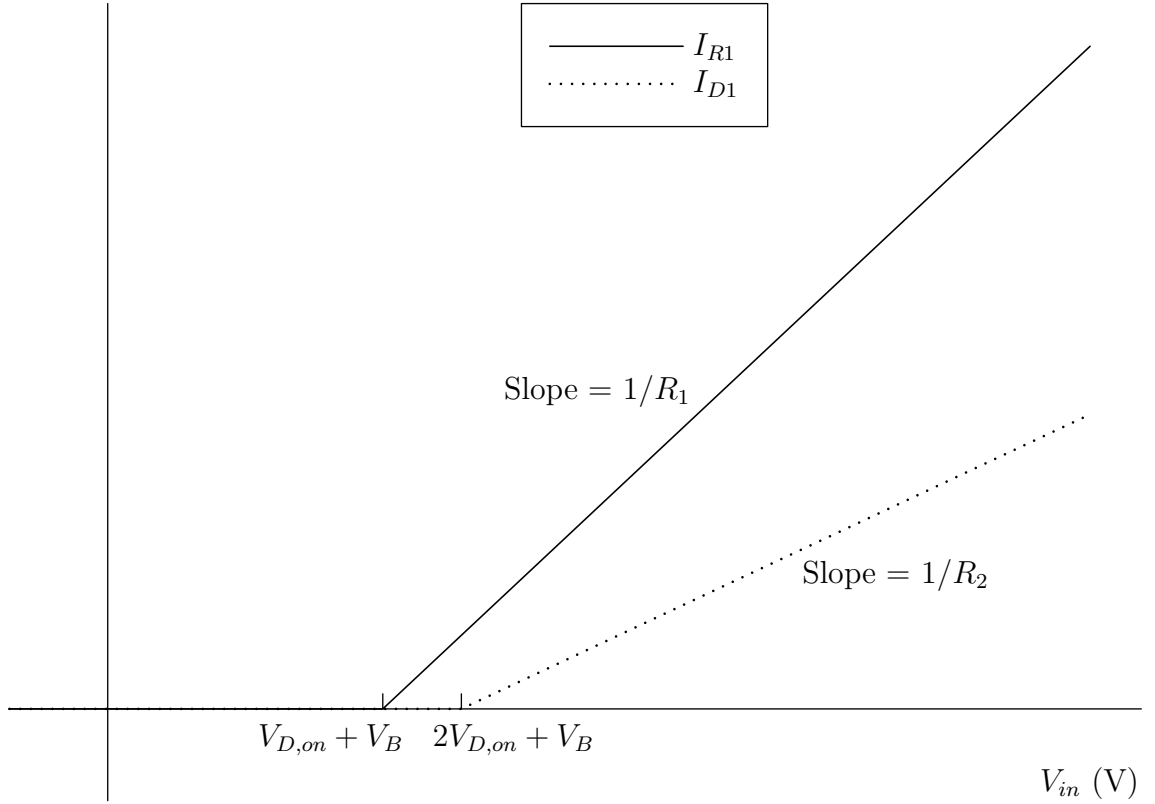
$$I_{D1} = \begin{cases} 0 & V_{in} < V_{D,on} + V_B \\ 0 & V_{D,on} + V_B < V_{in} < 2V_{D,on} + V_B \\ \frac{V_{in} - 2V_{D,on} - V_B}{R_2} & V_{in} > 2V_{D,on} + V_B \end{cases}$$




(d)

$$I_{R1} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{D,on} < V_{in} < V_{D,on} + \frac{R_1 + R_2}{R_2} (V_B + V_{D,on}) \\ \frac{V_{in} - 2V_{D,on} - V_B}{R_1} & V_{in} > V_{D,on} + \frac{R_1 + R_2}{R_2} (V_B + V_{D,on}) \end{cases}$$
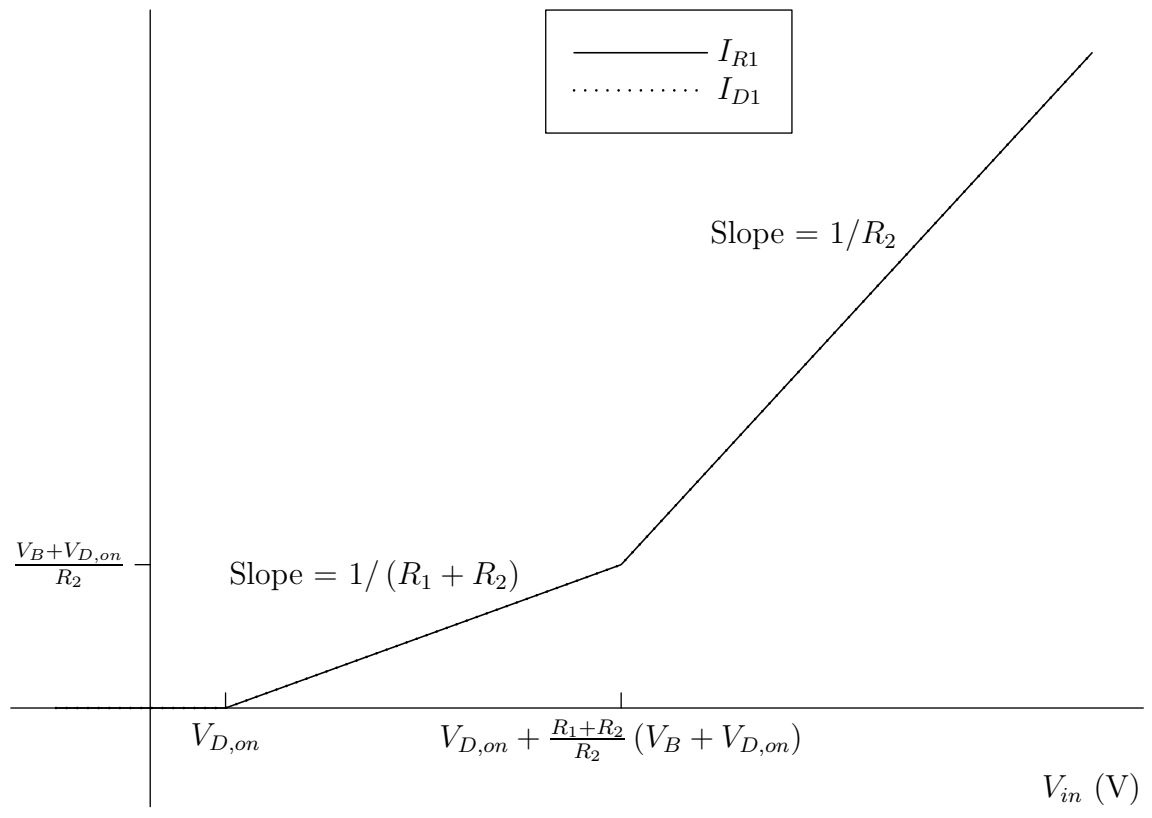
$$I_{D1} = \begin{cases} 0 & V_{in} < V_{D,on} \\ \frac{V_{in} - V_{D,on}}{R_1 + R_2} & V_{D,on} < V_{in} < V_{D,on} + \frac{R_1 + R_2}{R_2} (V_B + V_{D,on}) \\ \frac{V_{in} - 2V_{D,on} - V_B}{R_1} & V_{in} > V_{D,on} + \frac{R_1 + R_2}{R_2} (V_B + V_{D,on}) \end{cases}$$





3.31 (a)

$$I_{D1} = \frac{V_{in} - V_{D,on}}{R_1} = 1.6 \text{ mA}$$

$$r_{d1} = \frac{V_T}{I_{D1}} = 16.25 \Omega$$

$$\Delta V_{out} = \frac{R_1}{r_d + R_1} \Delta V_{in} = \boxed{98.40 \text{ mV}}$$

(b)

$$I_{D1} = I_{D2} = \frac{V_{in} - 2V_{D,on}}{R_1} = 0.8 \text{ mA}$$

$$r_{d1} = r_{d2} = \frac{V_T}{I_{D1}} = 32.5 \Omega$$

$$\Delta V_{out} = \frac{R_1 + r_{d2}}{R_1 + r_{d1} + r_{d2}} \Delta V_{in} = \boxed{96.95 \text{ mV}}$$

(c)

$$I_{D1} = I_{D2} = \frac{V_{in} - 2V_{D,on}}{R_1} = 0.8 \text{ mA}$$

$$r_{d1} = r_{d2} = \frac{V_T}{I_{D1}} = 32.5 \Omega$$

$$\Delta V_{out} = \frac{r_{d2}}{r_{d1} + R_1 + r_{d2}} \Delta V_{in} = \boxed{3.05 \text{ mV}}$$

(d)

$$I_{D2} = \frac{V_{in} - V_{D,on}}{R_1} - \frac{V_{D,on}}{R_2} = 1.2 \text{ mA}$$

$$r_{d2} = \frac{V_T}{I_{D2}} = 21.67 \Omega$$

$$\Delta V_{out} = \frac{R_2 \parallel r_{d2}}{R_1 + R_2 \parallel r_{d2}} \Delta V_{in} = \boxed{2.10 \text{ mV}}$$

3.32 (a)

$$\Delta V_{out} = \Delta I_{in} R_1 = \boxed{100 \text{ mV}}$$

(b)

$$\begin{aligned} I_{D1} &= I_{D2} = I_{in} = 3 \text{ mA} \\ r_{d1} &= r_{d2} = \frac{V_T}{I_{D1}} = 8.67 \text{ } \Omega \\ \Delta V_{out} &= \Delta I_{in} (R_1 + r_{d2}) = \boxed{100.867 \text{ mV}} \end{aligned}$$

(c)

$$\begin{aligned} I_{D1} &= I_{D2} = I_{in} = 3 \text{ mA} \\ r_{d1} &= r_{d2} = \frac{V_T}{I_{D1}} = 8.67 \text{ } \Omega \\ \Delta V_{out} &= \Delta I_{in} r_{d2} = \boxed{0.867 \text{ mV}} \end{aligned}$$

(d)


$$\begin{aligned} I_{D2} &= I_{in} - \frac{V_{D,on}}{R_2} = 2.6 \text{ mA} \\ r_{d2} &= \frac{V_T}{I_{D2}} = 10 \text{ } \Omega \\ \Delta V_{out} &= \Delta I_{in} (R_2 \parallel r_{d2}) = \boxed{0.995 \text{ mV}} \end{aligned}$$


$$\textcircled{33} \text{ a) } \quad i_{r_1} = i_{in} \\ = 0.1 \text{ mA}$$

$$\text{b) } \quad i_{r_1} = i_{in} \\ = 0.1 \text{ mA}$$

$$\text{c) } \quad i_{r_1} = i_{in} \\ = 0.1 \text{ mA}$$
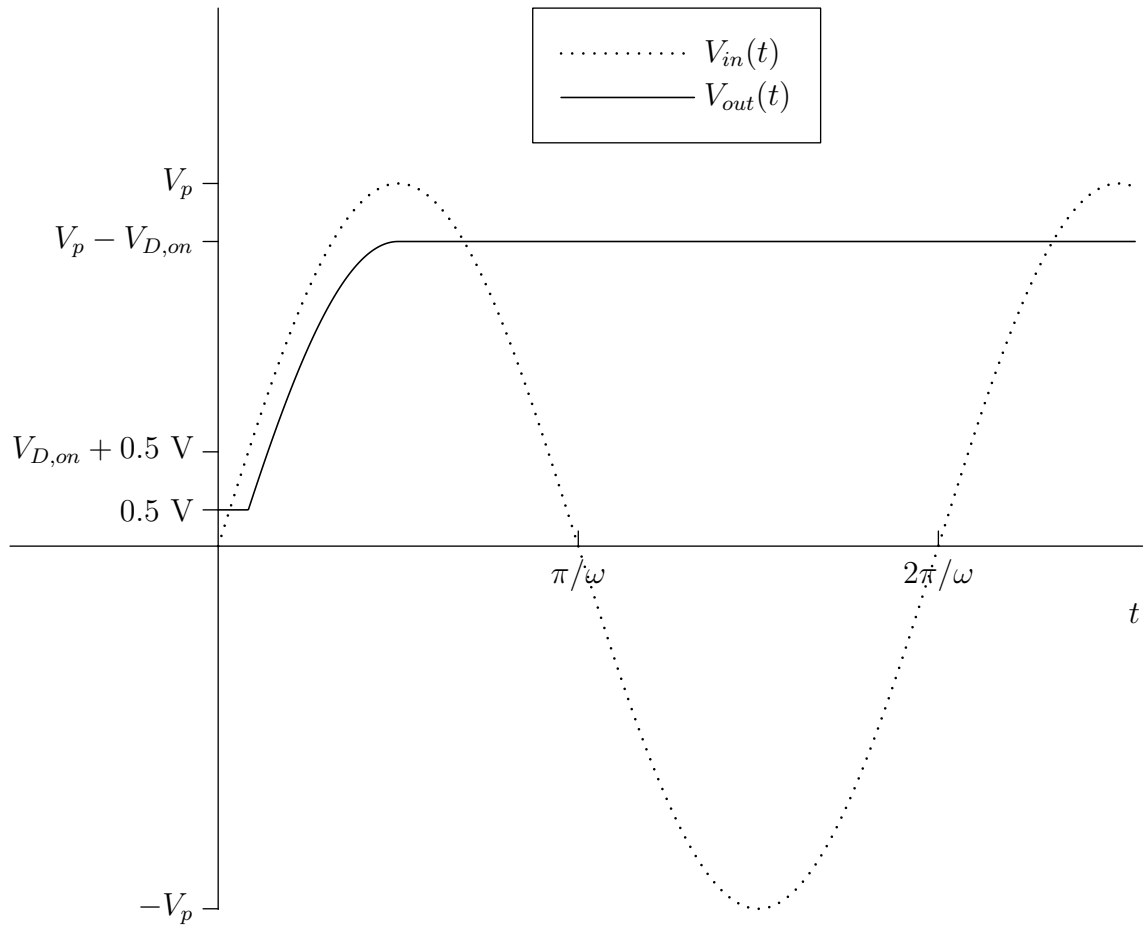
$$\text{d) } \quad i_{r_1} = i_{in} \\ = 0.1 \text{ mA}$$



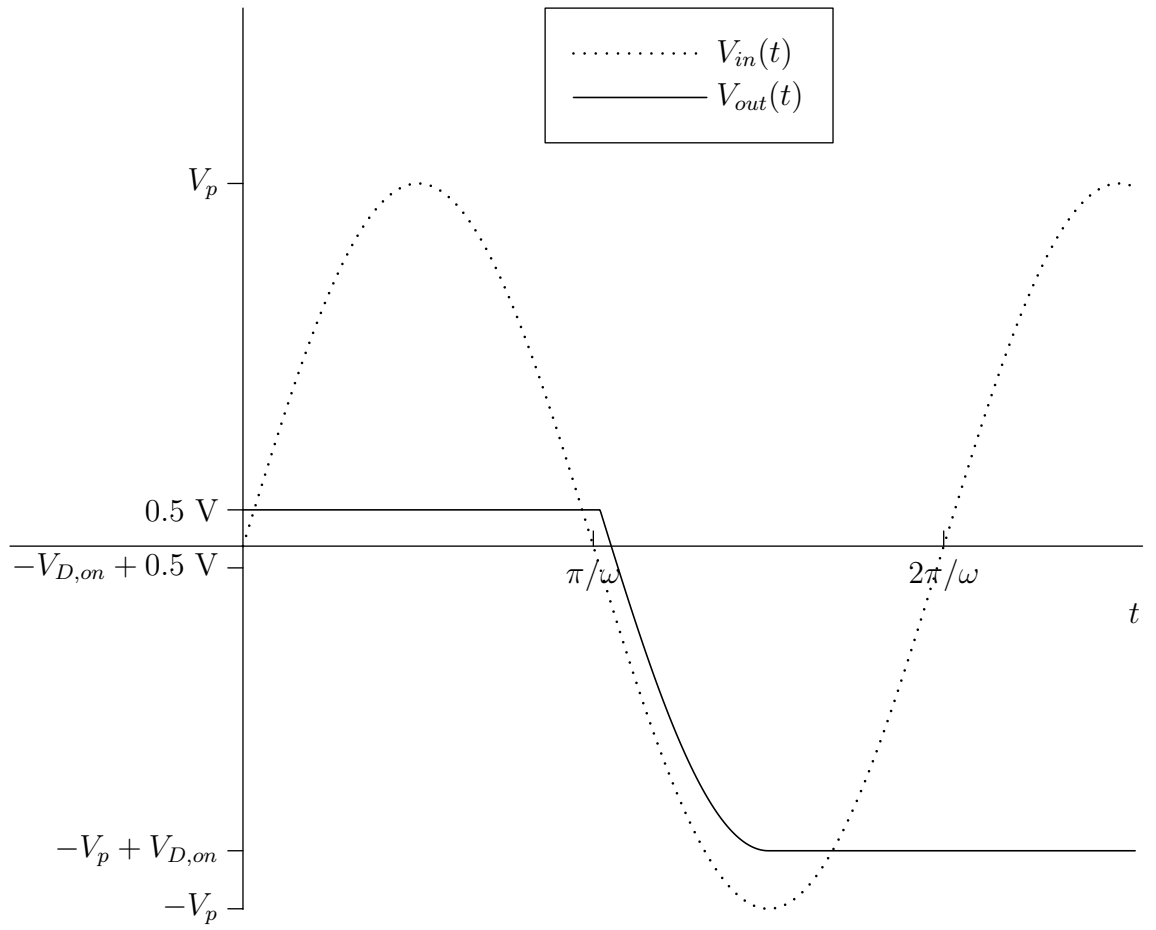

3.36

$$V_R \approx \frac{V_p - V_{D,on}}{R_L C_1 f_{in}}$$

$$V_p = 3.5 \text{ V}$$

$$R_L = 100 \Omega$$

$$C_1 = 1000 \mu\text{F}$$

$$f_{in} = 60 \text{ Hz}$$

$$V_R = \boxed{0.45 \text{ V}}$$

3.37

$$V_R = \frac{I_L}{C_1 f_{in}} \leq 300 \text{ mV}$$


$$f_{in} = 60 \text{ Hz}$$

$$I_L = 0.5 \text{ A}$$


$$C_1 \geq \frac{I_L}{(300 \text{ mV}) f_{in}} = \boxed{27.78 \text{ mF}}$$



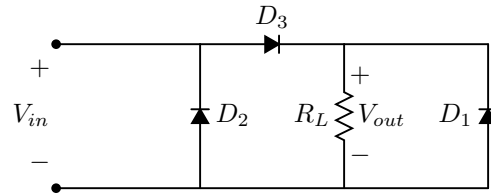
3.38 Shorting the input and output grounds of a full-wave rectifier shorts out the diode  $D_4$  from Fig. 3.38(b). Redrawing the modified circuit, we have:



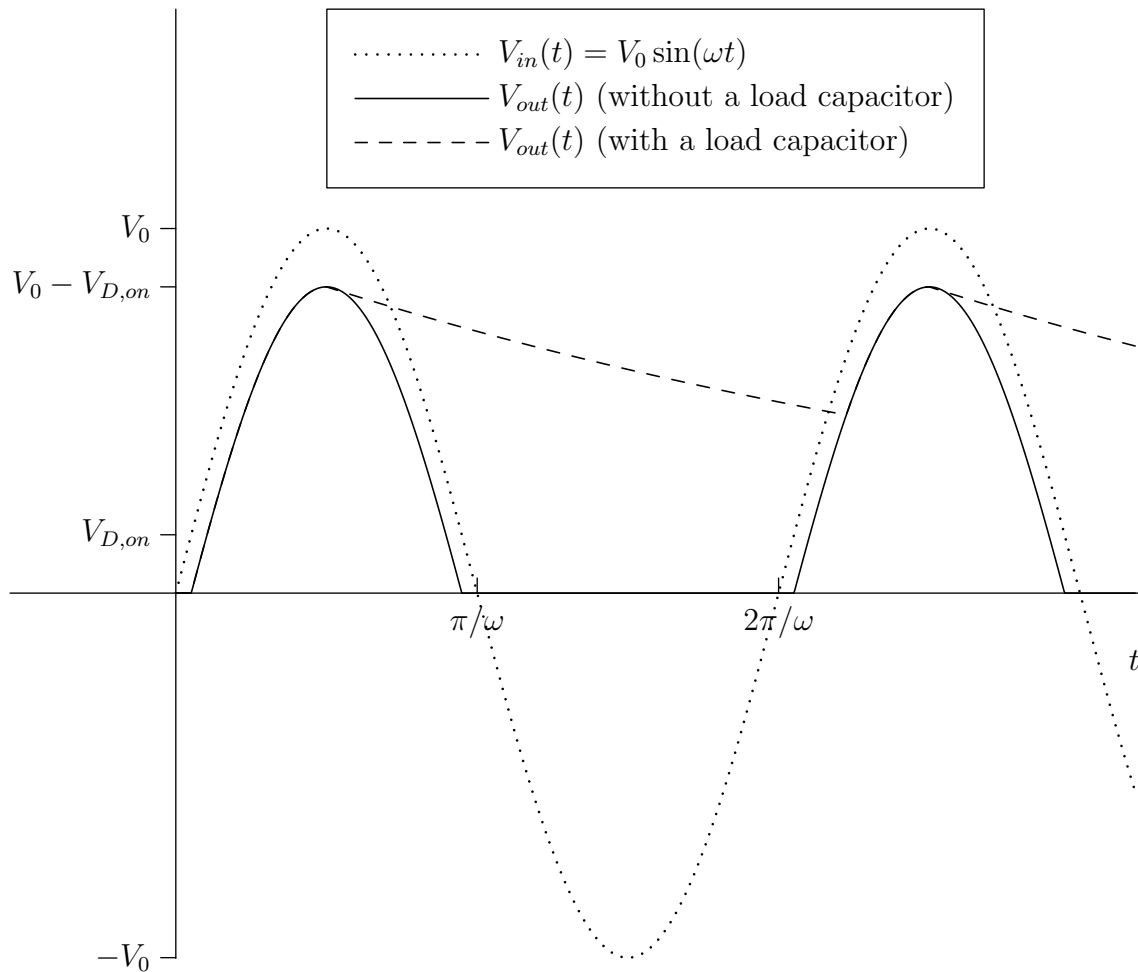On the positive half-cycle,  $D_3$  turns on and forms a half-wave rectifier along with  $R_L$  (and  $C_L$ , if included). On the negative half-cycle,  $D_2$  shorts the input (which could cause a dangerously large current to flow) and the output remains at zero. Thus, the circuit behaves like a half-wave rectifier. The plots of  $V_{out}(t)$  are shown below.



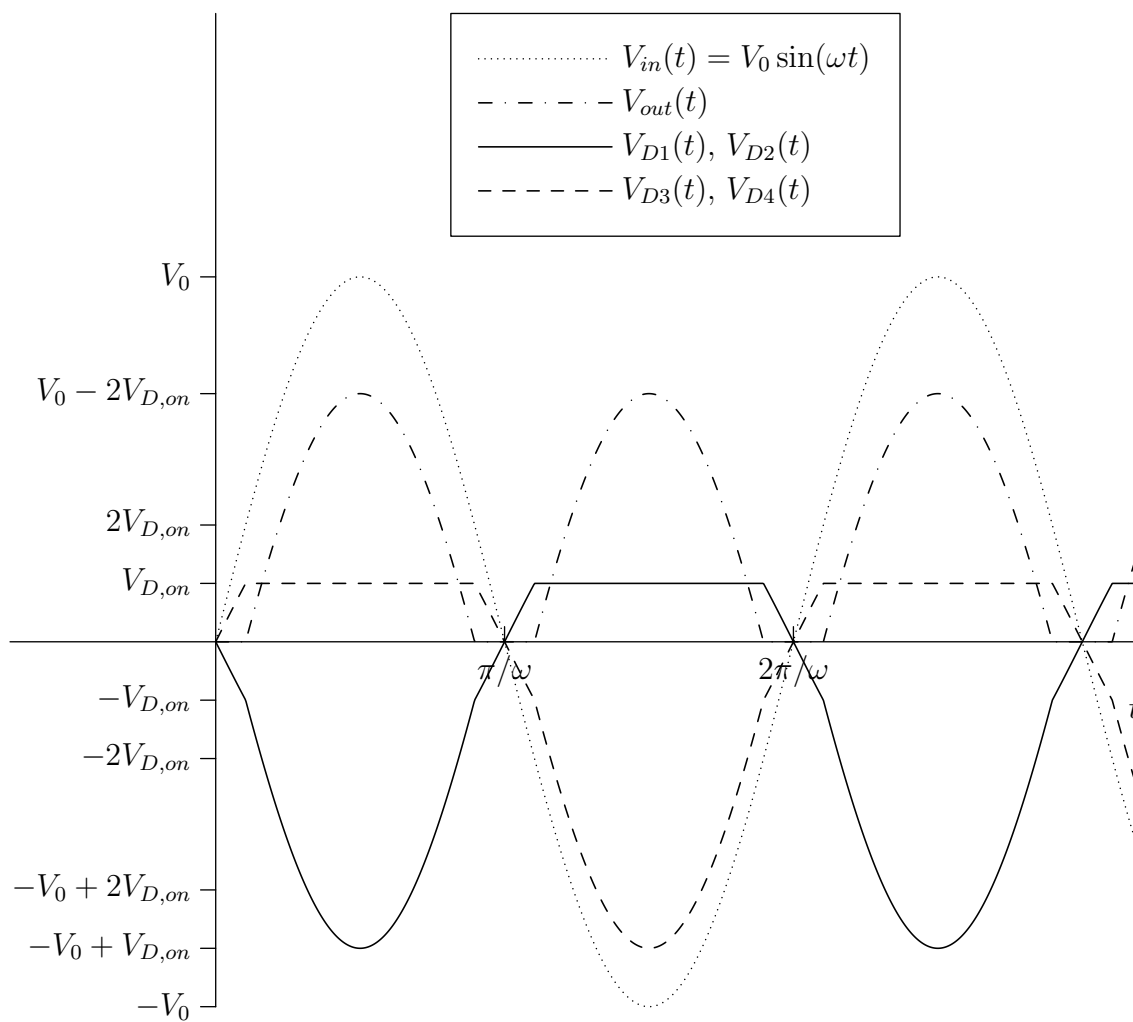3.39 Note that the waveforms for  $V_{D1}$  and  $V_{D2}$  are identical, as are the waveforms for  $V_{D3}$  and  $V_{D4}$ .




3.40 During the positive half-cycle,  $D_2$  and  $D_3$  will remain reverse-biased, causing  $V_{out}$  to be zero as no current will flow through  $R_L$ . During the negative half-cycle,  $D_1$  and  $D_3$  will short the input (potentially causing damage to the devices), and once again, no current will flow through  $R_L$  (even though  $D_2$  will turn on, there will be no voltage drop across  $R_L$ ). Thus,  $V_{out}$  always remains at zero, and the circuit fails to act as a rectifier.


④ Using Eq. (3.94),

$$\begin{aligned}V_R &\approx \frac{1}{2} \cdot \frac{V_P - 2 V_{P,ON}}{R_L C_1 f_{in}} \\&= \frac{1}{2} \cdot \frac{3 - 2 \times 0.8}{30 \times 1000 \times 10^{-6} \times 60} \\&= 0.389V\end{aligned}$$

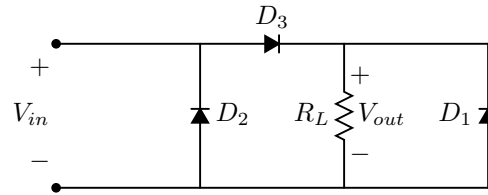3.42 Shorting the negative terminals of  $V_{in}$  and  $V_{out}$  of a full-wave rectifier shorts out the diode  $D_4$  from Fig. 3.38(b). Redrawing the modified circuit, we have:




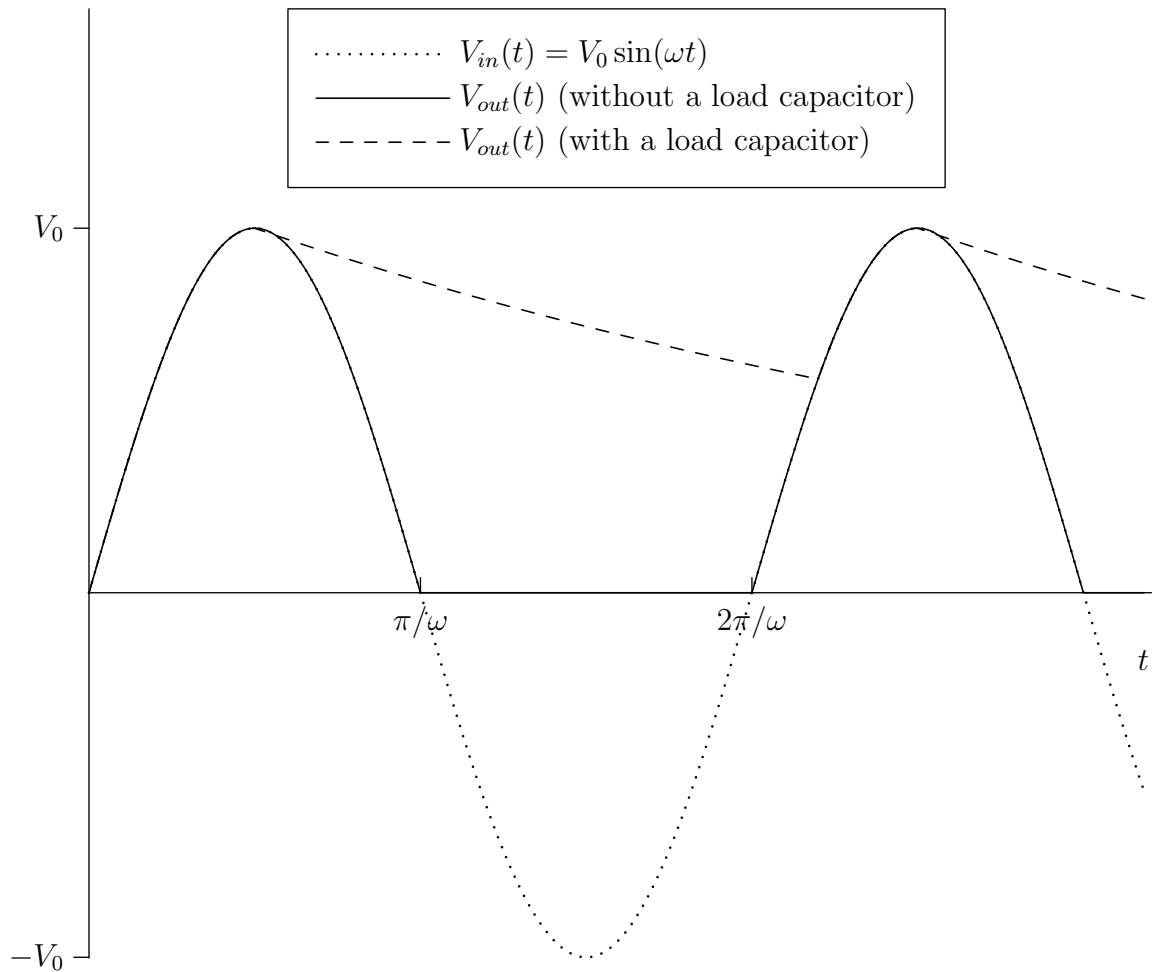On the positive half-cycle,  $D_3$  turns on and forms a half-wave rectifier along with  $R_L$  (and  $C_L$ , if included). On the negative half-cycle,  $D_2$  shorts the input (which could cause a dangerously large current to flow) and the output remains at zero. Thus, the circuit behaves like a half-wave rectifier. The plots of  $V_{out}(t)$  are shown below.



(43)

The circuit can be simplified as:

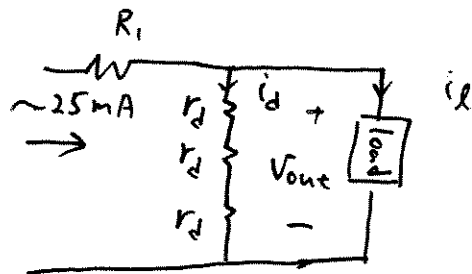

First, find  $r_d$ :

$$r_d = \frac{V_T}{I_D} \quad (\text{from eq. 3.60})$$

$$= \frac{26\text{mV}}{5\text{mA}}$$

$$= 5.2\ \Omega$$

Since  $i_L = +1\text{mA}$ .

$$i_d = -1\text{mA}.$$

$\therefore$  change in  $V_{out}$ ,

$$\text{ie. } V_{out} = (-1\text{mA})(3 \times 5.2)$$

$$= -15.6\text{mV}$$

- 3.44 (a) We know that when a capacitor is discharged by a constant current at a certain frequency, the ripple voltage is given by  $\frac{I}{Cf_{in}}$ , where  $I$  is the constant current. In this case, we can calculate the current as approximately  $\frac{V_p - 5V_{D,on}}{R_1}$  (since  $V_p - 5V_{D,on}$  is the voltage drop across  $R_1$ , assuming  $R_1$  carries a constant current). This gives us the following:

$$V_R \approx \frac{1}{2} \frac{V_p - 5V_{D,on}}{R_L C_1 f_{in}}$$

$$V_p = 5 \text{ V}$$

$$R_L = 1 \text{ k}\Omega$$

$$C_1 = 100 \text{ }\mu\text{F}$$

$$f_{in} = 60 \text{ Hz}$$

$$V_R = \boxed{166.67 \text{ mV}}$$


- (b) The bias current through the diodes is the same as the bias current through  $R_1$ , which is  $\frac{V_p - 5V_{D,on}}{R_1} = 1 \text{ mA}$ . Thus, we have:

$$r_d = \frac{V_T}{I_D} = 26 \text{ }\Omega$$

$$V_{R,load} = \frac{3r_d}{R_1 + 3r_d} V_R = \boxed{12.06 \text{ mV}}$$

$$I_{D1} = \begin{cases} 0 & V_{in} < V_{D,on} + V_{B1} \\ \frac{V_{in} - V_{D,on} - V_{B1}}{R_1} & V_{in} > V_{D,on} + V_{B1} \end{cases}$$
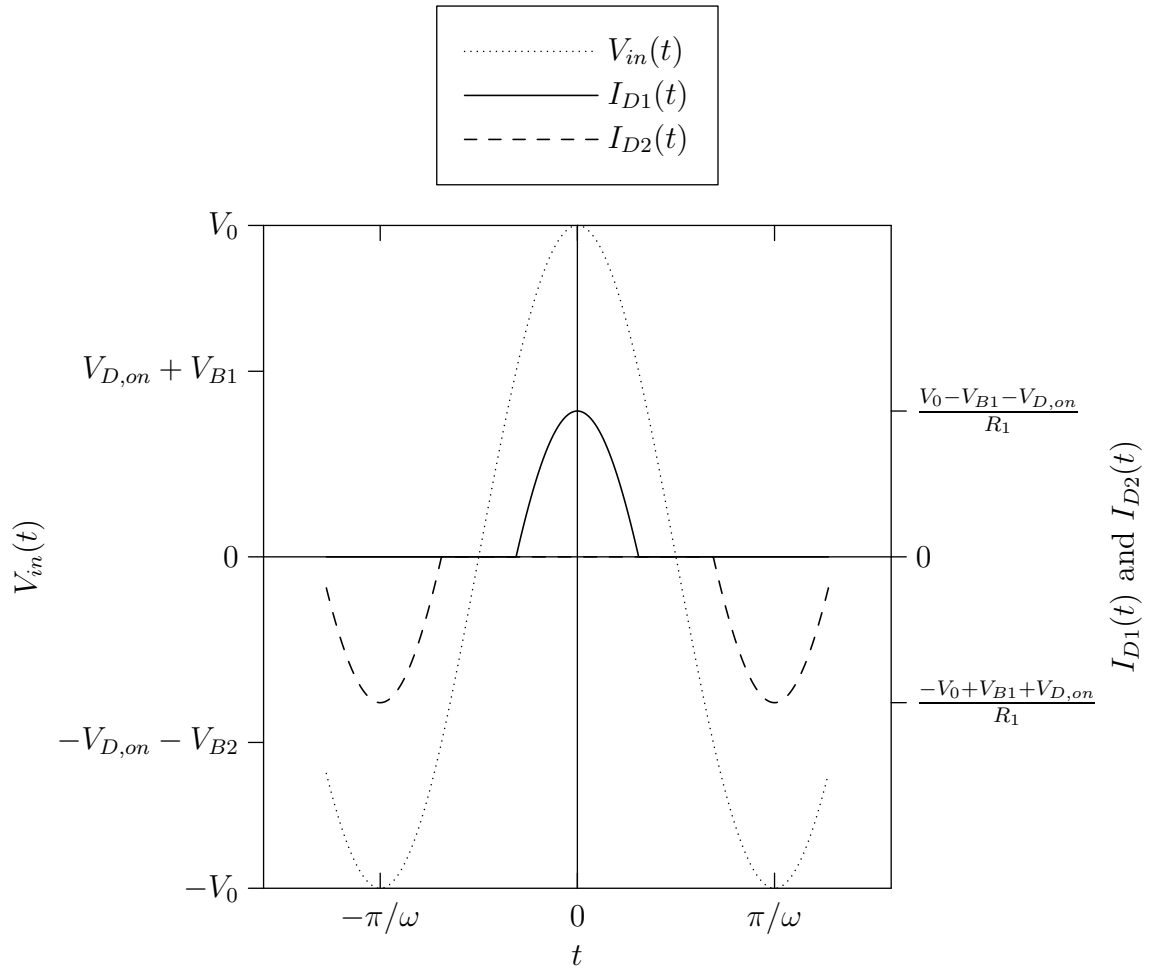
$$I_{D2} = \begin{cases} \frac{V_{in} + V_{D,on} + V_{B2}}{R_1} & V_{in} < -V_{D,on} - V_{B2} \\ 0 & V_{in} > -V_{D,on} - V_{B2} \end{cases}$$





(46) With positive threshold = + 2.2V,

$$\begin{aligned}V_{B1} &= 2.2 - 0.8 \\ &= +1.4V\end{aligned}$$

With negative threshold = -1.9V,

$$\begin{aligned}-V_{B2} &= -1.9 + 0.8 \\ &= -1.1V.\end{aligned}$$

$$V_{B2} = 1.1V$$

To meet the maximum current criterion,

Since  $I_{R1} = I_{D1}$  or  $I_{D2}$ ,

$I_{D1}$  or  $I_{D2}$  is at max when

$I_{R1}$  is at max.

$I_{R1}$  is at max when  $|V_R|$  is max,


$$\begin{aligned}\text{ie. } |V_R| &= 5 - 1.9 \\ &= 3.1V.\end{aligned}$$

Since  $I_{R1} \leq 2 \text{ mA}$ .

$$R_1 \geq \frac{3.1}{2 \text{ mA}}, \text{ ie. } R_1 \geq 1550\Omega$$

(47)

The required circuit is:

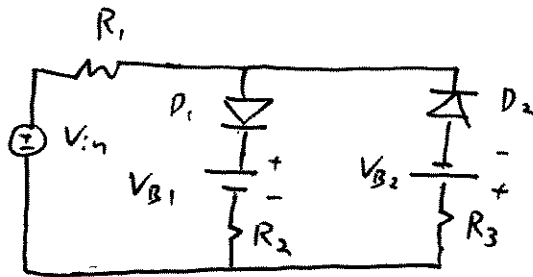

Similar to Example 3.34,

$$\begin{aligned} V_{B1} &= V_{B2} = (2 - 0.8) \text{ V} \\ &= 1.2 \text{ V} \end{aligned}$$

To find  $R_2$ ,


For  $V_{in} > 2 \text{ V}$ ,  $\frac{V_{out}}{V_{in}}$  has a slope of 0.5.

This implies  $R_2 = R_1$   
( $R_1$  and  $R_2$  forms a volt. divider).

Similarly,  $R_3 = R_1$ .


Thus, set  $R_1 = R_2 = R_3 = 1 \text{ k}\Omega$ .

The resulting circuit is:

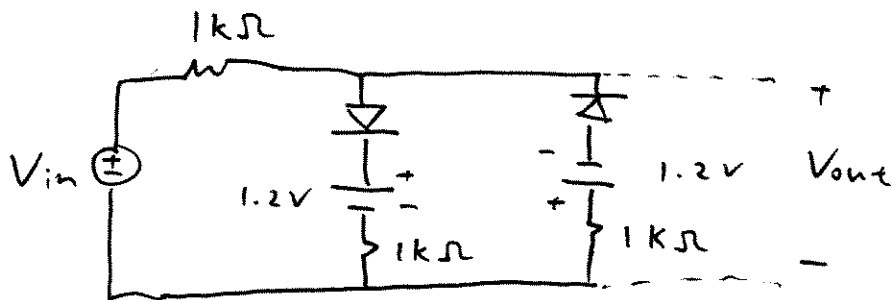


(48) For  $|V_{in}| < 4V$ , the  $V_{out} - V_{in}$  characteristic is similar to prob. (47).

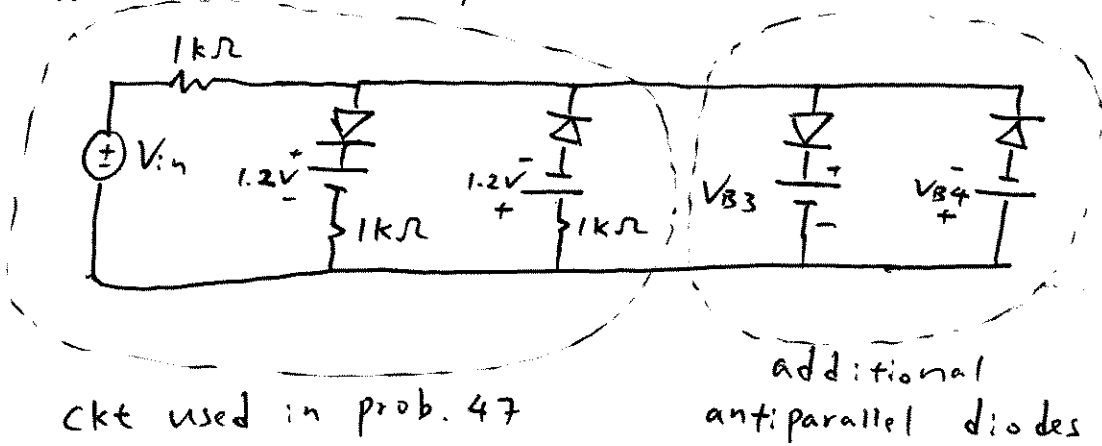To get voltage limiting characteristic for  $V_{in} > 4V$ , and  $V_{in} < -4V$ , we can shunt the circuit used in prob(47) with two anti parallel diodes as below:




$$V_{B3} = V_{B4} = 4 - 0.8 = 3.2V$$

Resulting circuit is:

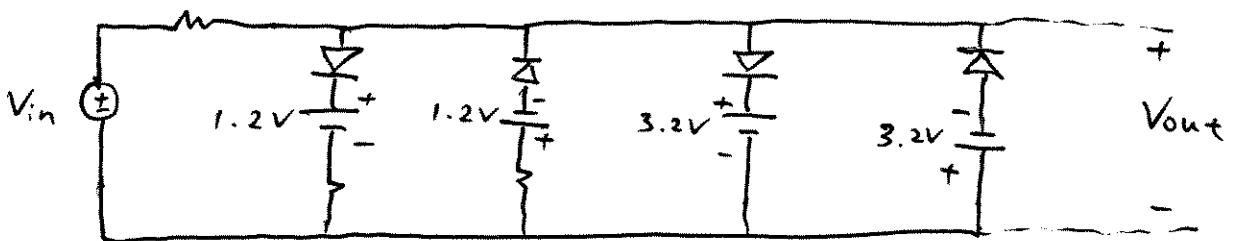


49

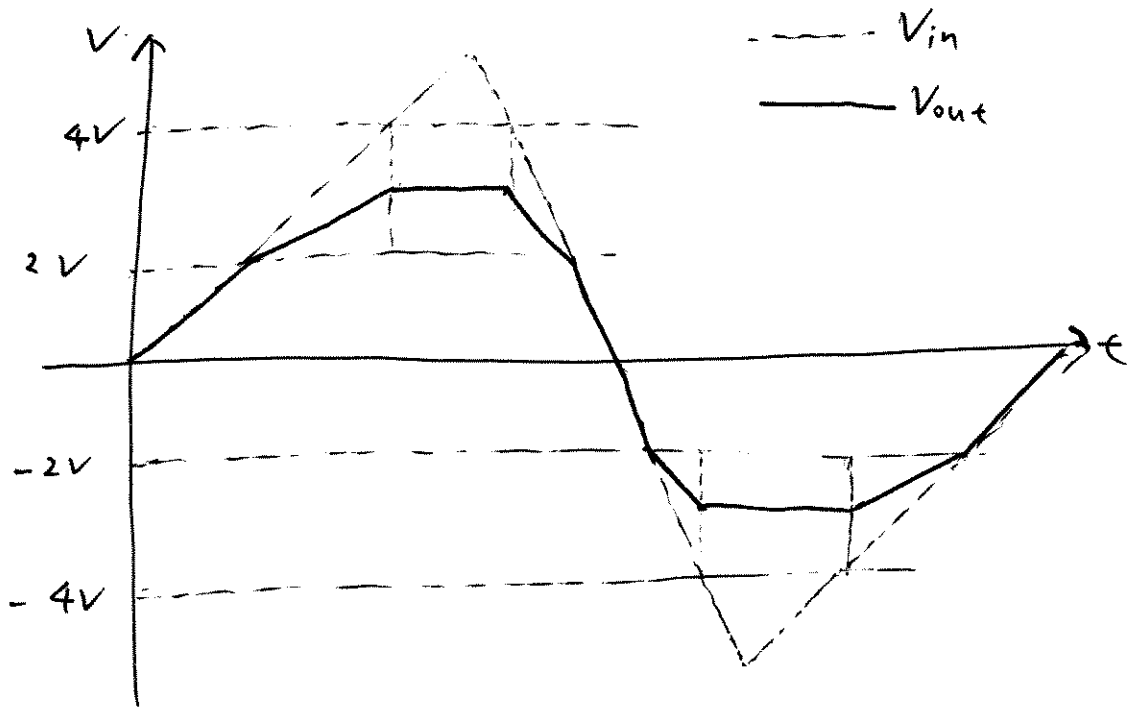


To get a better approximate of a sinusoid, the slope of the input-output characteristic should decrease more gradually from 1 to 0 through more sections.

eg :

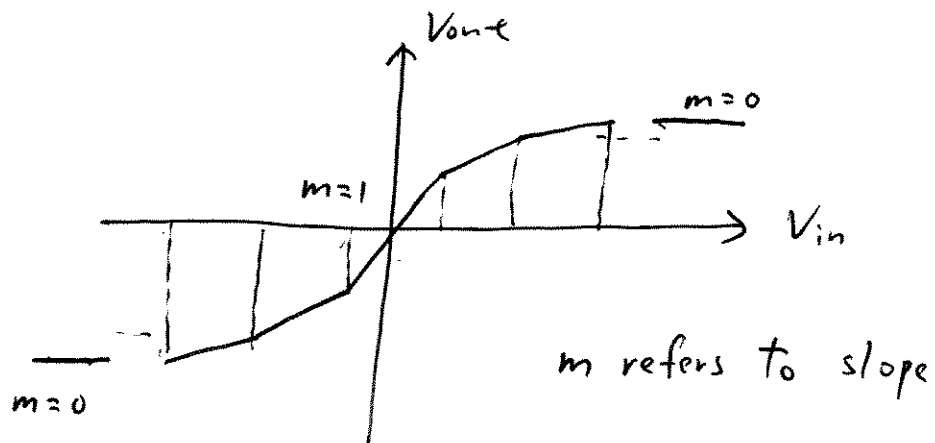

## chapter 4

4.1

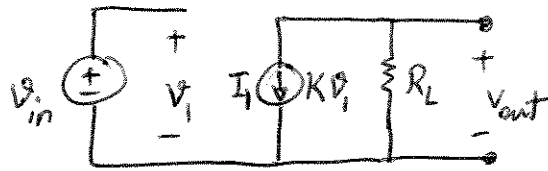

$$K = 20 \text{ mA/V}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = 15 \quad V_{in} = V_1$$


$$V_{out} = -I_1 R_L = -K R_L V_{in}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = -K R_L \Rightarrow \left| \frac{V_{out}}{V_{in}} \right| = K R_L$$

$$\Rightarrow K R_L = 15 \Rightarrow R_L = \frac{15}{20 \text{ mA/V}} = 750 \Omega$$

$$\boxed{R_L = 750 \Omega}$$

4.2

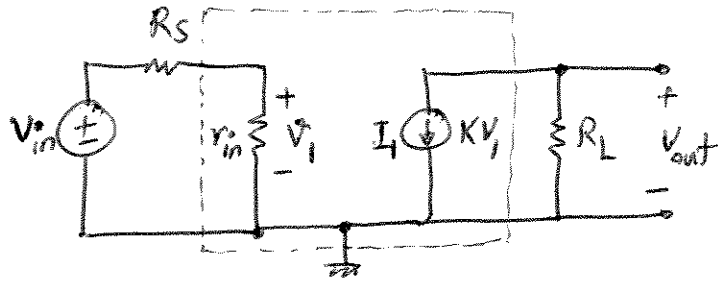

$$\frac{V_{out}}{V_{in}} = ?$$

$$V_1 = \frac{r_{in}}{r_{in} + R_S} V_{in}$$

$$I_1 = K V_1$$

$$V_{out} = -R_L I_1$$

$$\left. \begin{array}{l} V_1 = \frac{r_{in}}{r_{in} + R_S} V_{in} \\ I_1 = K V_1 \\ V_{out} = -R_L I_1 \end{array} \right\} \Rightarrow V_{out} = -K R_L V_1 \Rightarrow V_{out} = -K R_L \frac{r_{in}}{r_{in} + R_S} V_{in}$$

$$\Rightarrow A_V = \frac{V_{out}}{V_{in}} = -K R_L \frac{r_{in}}{r_{in} + R_S}$$

4.3 From solution for problem 4.2,

$$a > 0$$


$$b > 0$$

$$x \gg 0$$

$$A_v = -KR_L \frac{r_{in}}{r_{in} + R_S}$$

$$\begin{array}{l} r_{in} = a/x \\ K = bx \end{array} \rightarrow A_v = -bx R_L \frac{a/x}{a/x + R_S} = -bR_L \frac{a}{\frac{a}{x} + R_S}$$
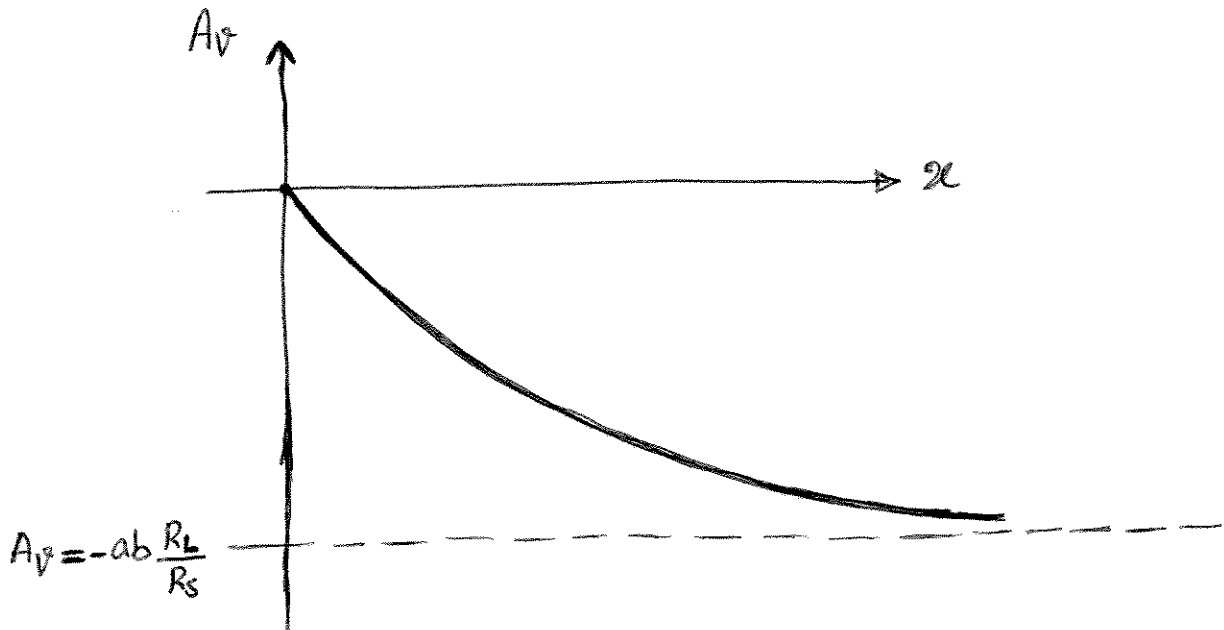
$$\Rightarrow A_v = -bR_L \left( \frac{x}{1 + \frac{R_S}{a} x} \right)$$




4.4 According to Equation (4.8), we have

$$I_C = \frac{A_E q D_n n_i^2}{N_B W_B} \left( e^{V_{BE}/V_T} - 1 \right)$$
$$\propto \frac{1}{W_B}$$

We can see that if  $W_B$  increases by a factor of two, then  $I_C$  decreases by a factor of two.



4.5

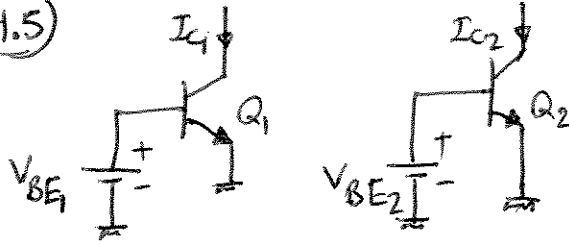

$$V_T = 26 \text{ mV}$$

$$I_{C1} = I_{C2}$$

$$V_{BE1} - V_{BE2} = 20 \text{ mV}$$

$$I_C = \frac{A_E q D_n n_i^2}{N_E W_B} \left( e^{\frac{V_{BE}}{V_T}} - 1 \right) \quad \text{equation (4.8) page 136}$$

$$\Rightarrow I_C \approx \frac{A_E q D_n n_i^2}{N_E W_B} e^{\frac{V_{BE}}{V_T}} \quad A_E \equiv \text{Cross Section}$$

if  $I_{C1} = I_{C2}$

$$\Rightarrow \frac{A_{E1} q D_n n_i^2}{N_E W_B} e^{\frac{V_{BE1}}{V_T}} = \frac{A_{E2} q D_n n_i^2}{N_E W_B} e^{\frac{V_{BE2}}{V_T}}$$

$$\Rightarrow \frac{A_{E2}}{A_{E1}} = \frac{e^{\frac{V_{BE1}}{V_T}}}{e^{\frac{V_{BE2}}{V_T}}}$$

$$\Rightarrow \frac{A_{E2}}{A_{E1}} = e^{\frac{(V_{BE1} - V_{BE2})}{V_T}} = e^{\frac{20 \text{ mV}}{26 \text{ mV}}}$$

$$\Rightarrow \boxed{\frac{A_{E2}}{A_{E1}} = e^{\frac{20}{26}} \approx 2.16}$$

$$\textcircled{6a} \quad I_x = 1^{\text{mA}} \Rightarrow I_{Q_1} = I_{Q_2} = 0.5^{\text{mA}}$$

$$I_{Q_1} = I_{S_1} e^{\frac{V_{BE1}}{V_T}} \Rightarrow 5 \times 10^{-4} = 3 \times 10^{-16} e^{\frac{V_B}{26 \text{mV}}}$$

$$\Rightarrow V_B = 26^{\text{mV}} \ln\left(\frac{5}{3} \times 10^{12}\right) \Rightarrow$$

$$\boxed{V_B \approx 731.7^{\text{mV}}}$$

$$\textcircled{6b} \quad I_y = I_{S_3} e^{\frac{V_B}{V_T}}$$

$$\Rightarrow I_{S_3} = I_y e^{-\frac{V_B}{V_T}} = 2.5 \times 10^{-3} \times e^{-\frac{V_B}{26 \text{mV}}} = 2.5 \times 10^{-3} \times \frac{1}{\frac{5}{3} \times 10^{12}}$$

$$\Rightarrow \boxed{I_{S_3} = 1.5 \times 10^{-15} \text{ A}}$$

$$\textcircled{7a} \quad I_x = I_1 + I_2$$

$$\Rightarrow I_x = I_{s1} e^{\frac{V_B}{V_T}} + I_{s2} e^{\frac{V_B}{V_T}} \Rightarrow I_x = (I_{s1} + I_{s2}) e^{\frac{V_B}{V_T}}$$

$$\Rightarrow V_B = V_T \ln \left( \frac{I_x}{I_{s1} + I_{s2}} \right) \xrightarrow{I_{s1} = 2I_{s2}} \boxed{V_B = V_T \ln \left( \frac{I_x}{\frac{3}{2} I_{s1}} \right)}$$

$$V_B = 26 \times 10^{-3} \ln \left( \frac{1.2 \times 10^{-3}}{\frac{3}{2} \times 5 \times 10^{-16}} \right) \Rightarrow \boxed{V_B \approx 730.6 \text{ mV}}$$

$\textcircled{7b}$  Transistors at the edge of the active mode  $\Rightarrow V_C = V_B$   
applying KVL, we have:

$$V_{CC} = R_C I_x + V_B \Rightarrow \boxed{R_C = \frac{V_{CC} - V_B}{I_x}}$$

$$\Rightarrow R_C = \frac{2.5 - 0.73}{1.2 \times 10^{-3}}$$

$$\Rightarrow \boxed{R_C \approx 1475 \Omega}$$

8a) Same as 7a,

$$V_B \approx 730.6 \text{ mV}$$

8b) According to 7b,

$$R_C = \frac{V_{CC} - V_B}{I_X} = \frac{1.5 - 0.73}{1.2 \times 10^{-3}}$$

$$\Rightarrow R_C \approx 642 \Omega$$

④  $Q_1$  is at the edge of the active region  $\Rightarrow V_C = V_B$


applying KVL, we have:

$$V_{CC} = R_C I_C + V_C$$

$$\xrightarrow{V_C = V_B} V_{CC} = R_C I_C + V_B$$

$$\Rightarrow V_{CC} = R_C I_S e^{\frac{V_B}{V_T}} + V_B$$
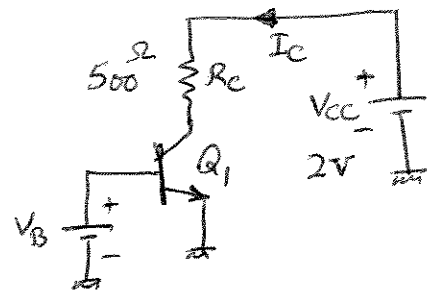
$$\Rightarrow 500 \Omega \times 5 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}} + V_B = 2 \text{ V}$$



Using numerical methods or simply, trial & error:

$$\boxed{V_B \approx 760 \text{ mV}}$$

⑩  $Q_1$  at the edge of saturation  $\Rightarrow V_C = V_B$



Hence:  $V_{CC} = R_C I_C + V_B$

$\Rightarrow V_{CC} = R_C I_S e^{\frac{V_B}{V_T}} + V_B$

$I_S = 3 \times 10^{-16} \text{ A}$

$V_{CC} = 3 \times 10^{-13} e^{\frac{V_B}{V_T}} + V_B$

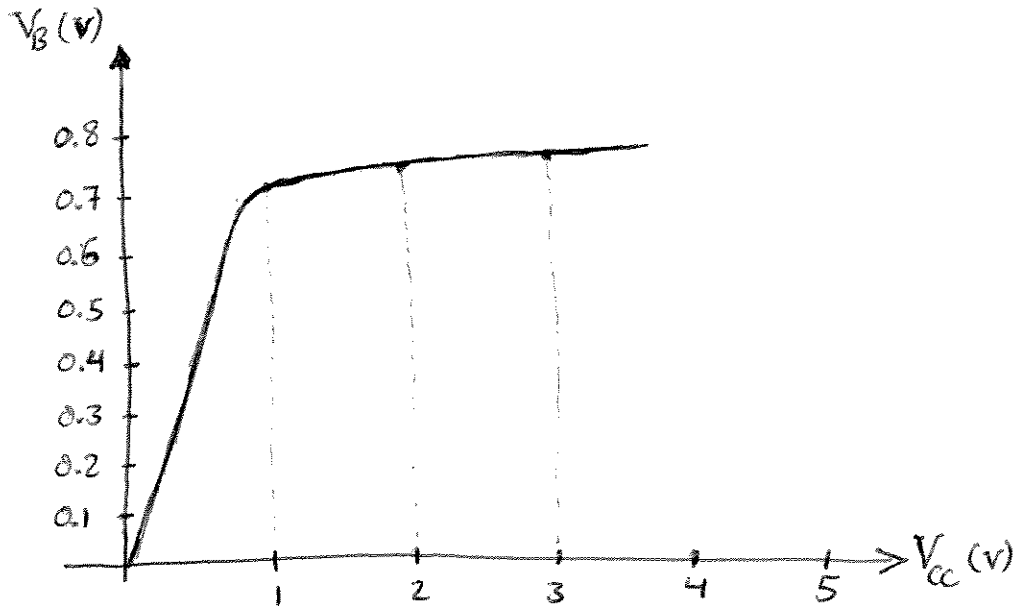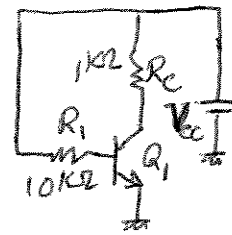
with  $V_{CC} = 2 \text{ V}$   $V_B \approx 755 \text{ mV}$



4.11

$$\begin{aligned}V_{BE} &= 1.5 \text{ V} - I_E(1 \text{ k}\Omega) \\ &\approx 1.5 \text{ V} - I_C(1 \text{ k}\Omega) \text{ (assuming } \beta \gg 1) \\ &= V_T \ln \left( \frac{I_C}{I_S} \right) \\ I_C &= 775 \text{ }\mu\text{A} \\ V_X &\approx I_C(1 \text{ k}\Omega) \\ &= \boxed{775 \text{ mV}}\end{aligned}$$

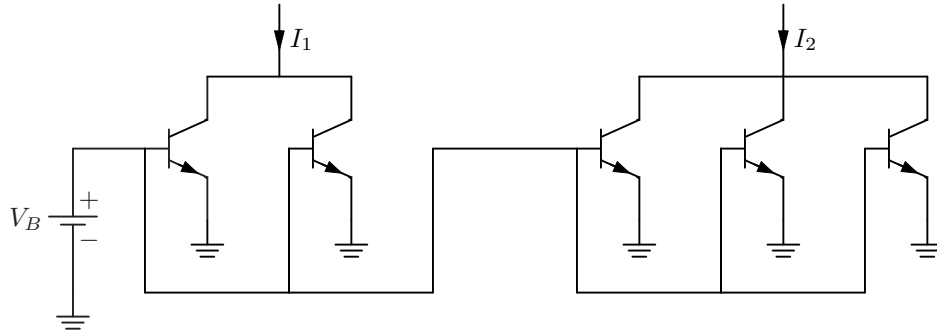4.12 Since we have only integer multiples of a unit transistor, we need to find the largest number that divides both  $I_1$  and  $I_2$  evenly (i.e., we need to find the largest  $x$  such that  $I_1/x$  and  $I_2/x$  are integers). This will ensure that we use the fewest transistors possible. In this case, it's easy to see that we should pick  $x = 0.5$  mA, meaning each transistor should have 0.5 mA flowing through it. Therefore,  $I_1$  should be made up of  $1 \text{ mA}/0.5 \text{ mA} = 2$  parallel transistors, and  $I_2$  should be made up of  $1.5 \text{ mA}/0.5 \text{ mA} = 3$  parallel transistors. This is shown in the following circuit diagram.



Now we have to pick  $V_B$  so that  $I_C = 0.5$  mA for each transistor.

$$\begin{aligned}
 V_B &= V_T \ln \left( \frac{I_C}{I_S} \right) \\
 &= (26 \text{ mV}) \ln \left( \frac{5 \times 10^{-4} \text{ A}}{3 \times 10^{-16} \text{ A}} \right) \\
 &= \boxed{732 \text{ mV}}
 \end{aligned}$$



⑬ Using the same technique as in <sup>problem</sup> 12, we have:

$$\frac{n_1}{I_1} = \frac{n_2}{I_2} = \frac{n_3}{I_3}$$

$$\Rightarrow \frac{n_1}{0.2} = \frac{n_2}{0.3} = \frac{n_3}{0.45} \Rightarrow \boxed{\frac{n_1}{4} = \frac{n_2}{6} = \frac{n_3}{9}}$$

So let's choose  $\begin{cases} n_1 = 4 \\ n_2 = 6 \\ n_3 = 9 \end{cases}$


Hence,

$$I_1 = n_1 I_s e^{\frac{V_B}{V_T}} \Rightarrow 0.2 \times 10^{-3} = 4 \times 3 \times 10^{-16} e^{\frac{V_B}{26 \text{ mV}}}$$

$$\Rightarrow \boxed{V_B \approx 672 \text{ mV}}$$

⑭ From KVL,

$$V_B = R_1 I_B + V_{BEQ_1}$$

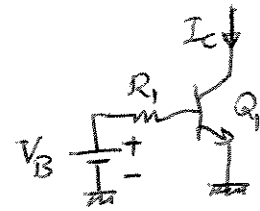

$$I_B = \frac{I_C}{\beta} = \frac{1 \text{ mA}}{100} \Rightarrow \boxed{I_B = 10^{-5} \text{ A}}$$

$$V_{BEQ_1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \times 10^{-3} \ln\left(\frac{10^{-3}}{7 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{BEQ_1} \approx 727.7 \text{ mV}}$$

Therefore,

$$V_B = R_1 I_B + V_{BEQ_1}$$


$$\approx 10 \text{ k}\Omega \times 10^{-5} \text{ A} + 728 \times 10^{-3}$$

$$\Rightarrow V_B \approx 0.1 + 0.728 \Rightarrow \boxed{V_B \approx 0.828 \text{ V}}$$

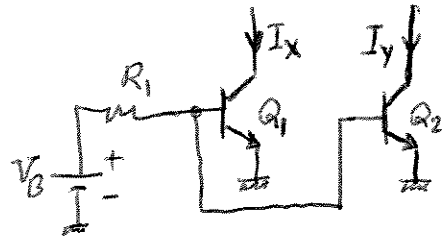4.15

$$\begin{aligned}\frac{V_B - V_{BE}}{R_1} &= I_B \\ &= \frac{I_C}{\beta} \\ I_C &= \frac{\beta}{R_1} [V_B - V_T \ln(I_C/I_S)] \\ I_C &= \boxed{786 \mu\text{A}}\end{aligned}$$

$$\textcircled{16} \begin{cases} I_x = I_{S1} \exp\left(\frac{V_{BE1}}{V_T}\right) \\ I_y = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right) \\ V_{BE1} = V_{BE2} = V_{BE} \end{cases}$$



$$\Rightarrow \frac{I_x}{I_y} = \frac{I_{S1}}{I_{S2}} = \frac{2I_{S2}}{I_{S2}} \Rightarrow \boxed{\frac{I_x}{I_y} = 2} \begin{cases} I_x = \beta_1 I_{B1} \\ I_y = \beta_2 I_{B2} \\ \beta_1 = \beta_2 \end{cases}$$

$$\Rightarrow \boxed{\frac{I_{B1}}{I_{B2}} = \frac{I_x}{I_y} = 2}$$

Applying KVL:

$$V_B = R_1 (I_{B1} + I_{B2}) + V_{BE}$$

$$V_{BE} = V_{BE1} = V_T \ln\left(\frac{I_x}{I_{S1}}\right) = 26 \text{ mV} \ln\left(\frac{1 \text{ mA}}{4 \times 10^{-16}}\right) \approx 742 \text{ mV}$$

$$I_{B1} = \frac{I_x}{\beta} \xrightarrow{\beta=100} I_{B1} = \frac{1 \text{ mA}}{100} = 10 \mu\text{A}$$

$$\frac{I_{B1}}{I_{B2}} = 2 \longrightarrow I_{B2} = \frac{I_{B1}}{2} = \frac{10 \mu\text{A}}{2} \Rightarrow I_{B2} = 5 \mu\text{A}$$

$$\text{Hence: } V_B = 5 \times 10^3 \Omega (10 \mu\text{A} + 5 \mu\text{A}) + 0.742 \text{ V}$$

$$= 0.075 + 0.742 \Rightarrow \boxed{V_B = 0.817 \text{ V}}$$

4.17 First, note that  $V_{BE1} = V_{BE2} = V_{BE}$ .

$$\begin{aligned}V_B &= (I_{B1} + I_{B2})R_1 + V_{BE} \\&= \frac{R_1}{\beta}(I_X + I_Y) + V_T \ln(I_X/I_{S1}) \\I_{S2} &= \frac{5}{3}I_{S1} \\ \Rightarrow I_Y &= \frac{5}{3}I_X \\V_B &= \frac{8R_1}{3\beta}I_X + V_T \ln(I_X/I_{S1}) \\I_X &= \boxed{509 \mu\text{A}} \\I_Y &= \boxed{848 \mu\text{A}}\end{aligned}$$

⑮ Since Transistor is in Forward active region,


No change across  $V_{BE}$



No change in  $I_B$



No change in  $I_C$

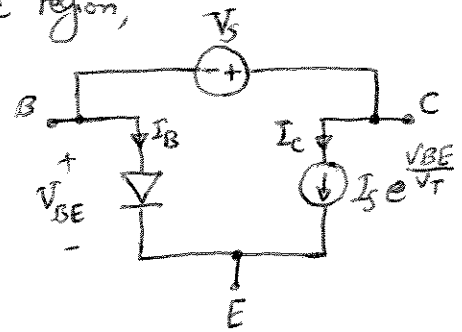

$$\textcircled{19} \quad g_m = \frac{I_c}{V_T}$$

$$\Rightarrow g_m = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_T} \Rightarrow \boxed{V_{BE} = V_T \ln\left(\frac{g_m V_T}{I_S}\right)}$$

$$\begin{array}{l} I_S = 6 \times 10^{-16} \text{ A} \\ g_m = \frac{1}{13 \Omega} \end{array} \rightarrow V_{BE} = 26 \text{ mV} \cdot \ln\left(\frac{\frac{1}{13 \Omega} \times 26 \times 10^{-3}}{6 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{BE} \approx 750 \text{ mV}}$$

20

$$g_m = \frac{I_c}{V_T}$$

$$\Delta g_m = \frac{\Delta I_c}{V_T} = \frac{1}{V_T} \Delta \left( I_s e^{\frac{V_{BE}}{V_T}} \right) \approx \frac{I_s}{V_T^2} e^{\frac{V_{BE}}{V_T}} \Delta V_{BE}$$

$$\Rightarrow \boxed{\Delta g_m \approx \frac{I_c}{V_T^2} \Delta V_{BE}}$$

$$\Rightarrow \Delta g_m \approx \frac{g_m}{V_T} \Delta V_{BE}$$

$$\Rightarrow \boxed{\frac{\Delta g_m}{g_m} \approx \frac{1}{V_T} \Delta V_{BE}}$$

$$\left. \frac{\Delta g_m}{g_m} \right|_{I_c=1\text{mA}}^{\text{max}} 0.1 \Rightarrow \Delta V_{BE, \text{max}} = 0.1 V_T$$

$$\Rightarrow \boxed{\Delta V_{BE} \leq 2.6 \text{ mV}}$$




4.21 (a)

$$\begin{aligned}
 V_{BE} &= \boxed{0.8 \text{ V}} \\
 I_C &= I_S e^{V_{BE}/V_T} \\
 &= \boxed{18.5 \text{ mA}} \\
 V_{CE} &= V_{CC} - I_C R_C \\
 &= \boxed{1.58 \text{ V}}
 \end{aligned}$$

$Q_1$  is operating in forward active. Its small-signal parameters are

$$\begin{aligned}
 g_m &= I_C/V_T = \boxed{710 \text{ mS}} \\
 r_\pi &= \beta/g_m = \boxed{141 \Omega} \\
 r_o &= \boxed{\infty}
 \end{aligned}$$

The small-signal model is shown below.

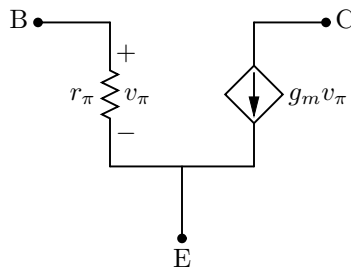


(b)

$$\begin{aligned}
 I_B &= 10 \mu\text{A} \\
 I_C &= \beta I_B = \boxed{1 \text{ mA}} \\
 V_{BE} &= V_T \ln(I_C/I_S) = \boxed{724 \text{ mV}} \\
 V_{CE} &= V_{CC} - I_C R_C \\
 &= \boxed{1.5 \text{ V}}
 \end{aligned}$$

$Q_1$  is operating in forward active. Its small-signal parameters are

$$\begin{aligned}
 g_m &= I_C/V_T = \boxed{38.5 \text{ mS}} \\
 r_\pi &= \beta/g_m = \boxed{2.6 \text{ k}\Omega} \\
 r_o &= \boxed{\infty}
 \end{aligned}$$

The small-signal model is shown below.

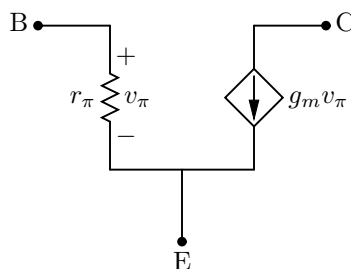


(c)

$$I_E = \frac{V_{CC} - V_{BE}}{R_C} = \frac{1 + \beta}{\beta} I_C$$
$$I_C = \frac{\beta}{1 + \beta} \frac{V_{CC} - V_T \ln(I_C/I_S)}{R_C}$$
$$I_C = \boxed{1.74 \text{ mA}}$$
$$V_{BE} = V_T \ln(I_C/I_S) = \boxed{739 \text{ mV}}$$
$$V_{CE} = V_{BE} = \boxed{739 \text{ mV}}$$

$Q_1$  is operating in forward active. Its small-signal parameters are

$$g_m = I_C/V_T = \boxed{38.5 \text{ mS}}$$
$$r_\pi = \beta/g_m = \boxed{2.6 \text{ k}\Omega}$$
$$r_o = \boxed{\infty}$$

The small-signal model is shown below.

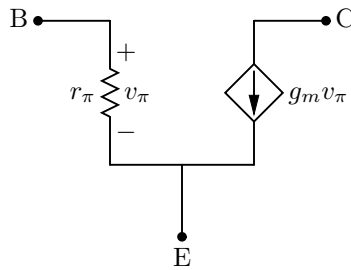


4.22 (a)

$$\begin{aligned}
 I_B &= 10 \mu\text{A} \\
 I_C &= \beta I_B = \boxed{1 \text{ mA}} \\
 V_{BE} &= V_T \ln(I_C/I_S) = \boxed{739 \text{ mV}} \\
 V_{CE} &= V_{CC} - I_E(1 \text{ k}\Omega) \\
 &= V_{CC} - \frac{1 + \beta}{\beta}(1 \text{ k}\Omega) \\
 &= \boxed{0.99 \text{ V}}
 \end{aligned}$$

$Q_1$  is operating in forward active. Its small-signal parameters are

$$\begin{aligned}
 g_m &= I_C/V_T = \boxed{38.5 \text{ mS}} \\
 r_\pi &= \beta/g_m = \boxed{2.6 \text{ k}\Omega} \\
 r_o &= \boxed{\infty}
 \end{aligned}$$

The small-signal model is shown below.

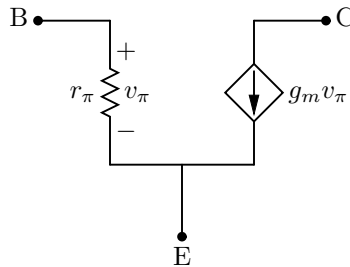


(b)

$$\begin{aligned}
 I_E &= \frac{V_{CC} - V_{BE}}{1 \text{ k}\Omega} = \frac{1 + \beta}{\beta} I_C \\
 I_C &= \frac{\beta}{1 + \beta} \frac{V_{CC} - V_T \ln(I_C/I_S)}{1 \text{ k}\Omega} \\
 I_C &= \boxed{1.26 \text{ mA}} \\
 V_{BE} &= V_T \ln(I_C/I_S) = \boxed{730 \text{ mV}} \\
 V_{CE} &= V_{BE} = \boxed{730 \text{ mV}}
 \end{aligned}$$

$Q_1$  is operating in forward active. Its small-signal parameters are

$$\begin{aligned}
 g_m &= I_C/V_T = \boxed{48.3 \text{ mS}} \\
 r_\pi &= \beta/g_m = \boxed{2.07 \text{ k}\Omega} \\
 r_o &= \boxed{\infty}
 \end{aligned}$$

The small-signal model is shown below.

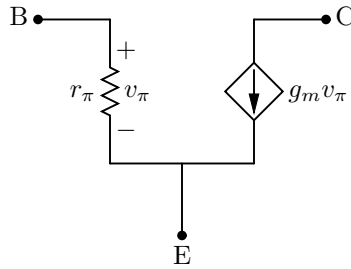

(c)

$$I_E = 1 \text{ mA}$$

$$I_C = \frac{\beta}{1 + \beta} I_E = \boxed{0.99 \text{ mA}}$$

$$V_{BE} = V_T \ln(I_C/I_S) = \boxed{724 \text{ mV}}$$

$$V_{CE} = V_{BE} = \boxed{724 \text{ mV}}$$


$Q_1$  is operating in forward active. Its small-signal parameters are

$$g_m = I_C/V_T = \boxed{38.1 \text{ mS}}$$

$$r_\pi = \beta/g_m = \boxed{2.63 \text{ k}\Omega}$$

$$r_o = \boxed{\infty}$$

The small-signal model is shown below.

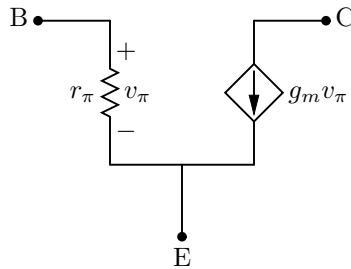

(d)

$$I_E = 1 \text{ mA}$$

$$I_C = \frac{\beta}{1 + \beta} I_E = \boxed{0.99 \text{ mA}}$$

$$V_{BE} = V_T \ln(I_C/I_S) = \boxed{724 \text{ mV}}$$

$$V_{CE} = V_{BE} = \boxed{724 \text{ mV}}$$


$Q_1$  is operating in forward active. Its small-signal parameters are

$$g_m = I_C/V_T = \boxed{38.1 \text{ mS}}$$

$$r_\pi = \beta/g_m = \boxed{2.63 \text{ k}\Omega}$$

$$r_o = \boxed{\infty}$$


The small-signal model is shown below.

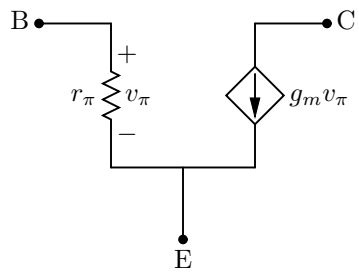

$$(23) \quad I_C = I_S \exp\left(\frac{V_{BE}}{nV_T}\right) \quad I_C = \beta I_B$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{1}{nV_T} I_S \exp\left(\frac{V_{BE}}{nV_T}\right) = \frac{I_C}{nV_T}$$

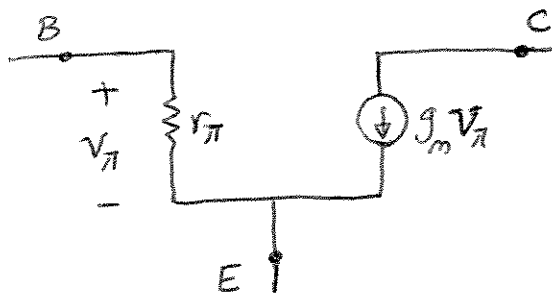
$$r_{\pi} = \frac{\partial V_{BE}}{\partial I_B} = \frac{\partial V_{BE}}{\frac{1}{\beta} \partial I_C} = \frac{\beta}{g_m} = \frac{n\beta V_T}{I_C}$$



$$(24) \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right), \quad I_C = \alpha I_B^2 \Rightarrow \frac{\partial I_B}{\partial I_C} = \frac{1}{2\sqrt{\alpha I_C}}$$

$$g_m = \frac{\partial I_C}{\partial V_{BE}} = \frac{I_S}{V_T} \exp\left(\frac{V_{BE}}{V_T}\right) = \frac{I_C}{V_T}$$
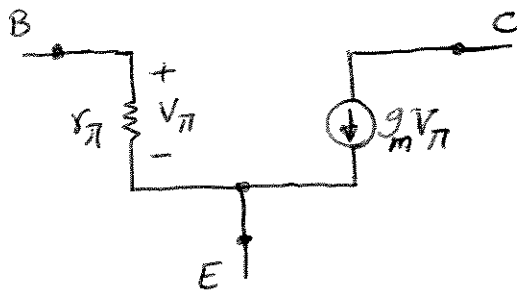
$$r_{\pi} = \frac{\partial V_{BE}}{\partial I_B} = \frac{\partial V_{BE}}{\frac{1}{2\sqrt{\alpha I_C}} \partial I_C} = \frac{2\sqrt{\alpha I_C}}{g_m} = \frac{2\sqrt{\alpha I_C}}{\frac{I_C}{V_T}} = 2V_T \sqrt{\frac{\alpha}{I_C}}$$



$$\textcircled{25} \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] \quad V_{BE} \text{ is Constant}$$

$$\Delta I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} \Delta V_{CE}$$

$$\Rightarrow \frac{\Delta I_C}{I_C} = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} \cdot \Delta V_{CE}}{I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]} = \frac{\Delta V_{CE}}{V_A + V_{CE}}$$

$$\frac{\Delta I_C}{I_{C_{\min}}} < 0.05 \Rightarrow \frac{\Delta V_{CE}}{V_A + V_{CE_{\min}}} < 0.05$$

$$\Rightarrow 20 \Delta V_{CE} < V_A + V_{CE_{\min}}$$

$$\left. \begin{array}{l} \Delta V_{CE} = 2 \text{ V} \\ V_{CE_{\min}} = 1 \text{ V} \end{array} \right\} \Rightarrow 40 < V_A + 1 \Rightarrow \boxed{V_A > 39 \text{ V}}$$



26

$$a) I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) = 5 \times 10^{-17} \exp\left(\frac{800 \text{ mV}}{26 \text{ mV}}\right) \approx \boxed{1.15 \text{ mA}}$$

$$V_X = V_{CC} - R_C I_C = 2.5 \text{ V} - 1 \text{ k}\Omega \times 1.15 \text{ mA}$$

$$\boxed{V_X = 1.35 \text{ V}}$$

Transistor is in Forward Active Region

$$b) I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$

$$\Rightarrow I_C = 5 \times 10^{-17} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5 \text{ V}}\right] \quad \text{equation 1}$$

$$\text{Also we know: } V_X = V_{CC} - R_C I_C \Rightarrow I_C = \frac{V_{CC} - V_X}{R_C} \quad \text{equation 2}$$

$$\text{equations 1, 2} \Rightarrow \frac{V_{CC} - V_X}{R_C} = 5 \times 10^{-17} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5}\right]$$


$$\Rightarrow V_X + 5 \times 10^{-14} \exp\left(\frac{800}{26}\right) \left[1 + \frac{V_X}{5}\right] = 2.5$$

$$\Rightarrow 1.2306 V_X \approx 1.347$$

$$\Rightarrow \boxed{V_X \approx 1.095 \text{ V}} \quad \text{equation 1} \Rightarrow \boxed{I_C \approx 1.406 \text{ mA}}$$

Transistor is in Forward Active Region

(27)

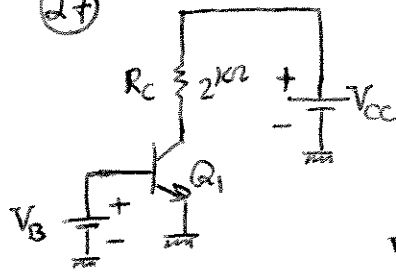

$$I_S = 1 \times 10^{-17} \text{ A} \quad V_A = 5 \text{ V}$$

Applying KVL:

$$V_{CC} = R_C I_C + V_{CE}$$

$$\Rightarrow V_{CC} = R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right] + V_{CE}$$

$V_{BE}$  Constant  $\Rightarrow$

$$\Delta V_{CC} = \left[ R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right) \frac{1}{V_A} + 1 \right] \cdot \Delta V_{CE} \quad \text{equation 1}$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left[1 + \frac{V_{CE}}{V_A}\right] \Rightarrow \Delta I_C = I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A} \Delta V_{CE}$$

$$\Rightarrow \Delta V_{CE} = \frac{1}{I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}} \cdot \Delta I_C \quad \text{equation 2}$$

equations 1, 2  $\Rightarrow$


$$\Delta I_C = \frac{I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}}{1 + R_C I_S e^{\frac{V_{BE}}{V_T}} \times \frac{1}{V_A}} \cdot \Delta V_{CC}$$

$$\Rightarrow \Delta I_C = \frac{I_S \exp\left(\frac{V_{BE}}{V_T}\right)}{V_A + R_C I_S \exp\left(\frac{V_{BE}}{V_T}\right)} \cdot \Delta V_{CC} = \frac{1}{r_o + R_C} \cdot \Delta V_{CC}$$

could also be obtained using small signal model

$$\Rightarrow \Delta I_C = \frac{2.31 \times 10^{-4}}{5 + \frac{0.4613}{0.001}} \times 0.5 \Rightarrow \Delta I_C \approx 0.021 \text{ mA}$$

(28)

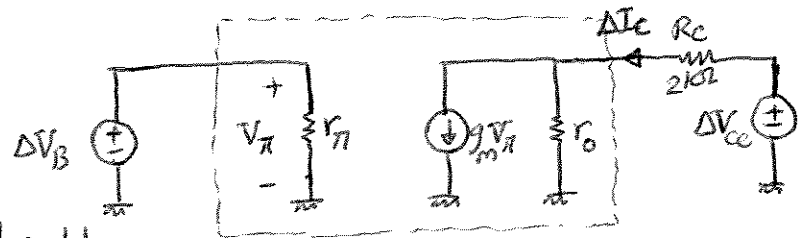

We use small signal model,

Assuming that the required  $\Delta V_B$  is small enough.

Applying superposition,

$$\Delta I_C = \left( \frac{1}{r_o + R_C} \right) \Delta V_{CC} + \left( \frac{g_m r_o}{r_o + R_C} \right) \Delta V_B$$

$$\Delta I_C = 0 \Rightarrow \boxed{\Delta V_B = -\frac{1}{g_m r_o} \Delta V_{CC}}$$


$$\Delta V_B = -\frac{1}{\frac{I_C}{V_T} \cdot \frac{V_A}{I_C}} \Delta V_{CC} \Rightarrow \Delta V_B = -\frac{V_T}{V_A} \Delta V_{CC}$$

$$\Rightarrow \Delta V_B = -\frac{26 \times 10^{-3}}{5} \times (3 - 2.5)$$

$$\Rightarrow \boxed{\Delta V_B = -2.6 \text{ mV}}$$

which is small enough

for small signal model

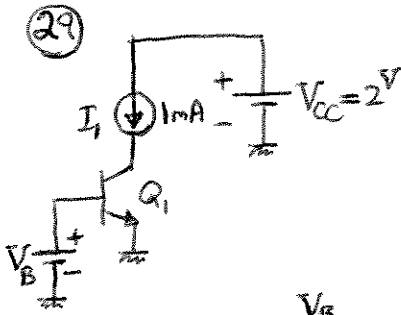

$$I_S = 3 \times 10^{-17} \text{ A}$$

$$a) I_C = I_S e^{\frac{V_B}{V_T}} \Rightarrow V_B = V_T \ln\left(\frac{I_C}{I_S}\right) = 26^{\text{mV}} \ln\left(\frac{10^{-3}}{3 \times 10^{-17}}\right)$$

$$\Rightarrow \boxed{V_B \approx 809.6 \text{ mV}}$$

$$b) I_C = I_S e^{\frac{V_B}{V_T}} \left(1 + \frac{V_{CE}}{V_A}\right)$$

$$10^{-3} = 3 \times 10^{-17} e^{\frac{V_B}{V_T}} \left(1 + \frac{1.5}{5}\right) \Rightarrow e^{\frac{V_B}{V_T}} = \frac{10}{3.9}$$

$$\Rightarrow V_B = 26^{\text{mV}} \ln\left(\frac{10}{3.9}\right) \Rightarrow \boxed{V_B \approx 802.8 \text{ mV}}$$

$$\textcircled{30} \quad I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \left[1 + \frac{V_{CE}}{V_A}\right]$$

$$r_o^{-1} = \frac{dI_C}{dV_{CE}} = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \cdot \frac{1}{V_A} \approx \frac{I_C}{V_A} \quad \Rightarrow \quad r_o \approx \frac{V_A}{I_C}$$


$$r_o > 10^4 \Omega \quad \Rightarrow \quad \frac{V_A}{I_C} > 10^4 \Omega$$

$$\Rightarrow V_A > 10^4 \Omega \times 2^{\text{mA}}$$

$$\Rightarrow \boxed{V_A > 20 \text{ V}}$$

$$\begin{aligned}
 I_C &= I_S e^{V_{BE}/V_T} \left( 1 + \frac{V_{CE}}{V_A} \right) \\
 I_{C,Total} &= n I_C \\
 &= n I_S e^{V_{BE}/V_T} \left( 1 + \frac{V_{CE}}{V_A} \right) \\
 g_{m,Total} &= \frac{\partial I_C}{\partial V_{BE}} \\
 &= n \frac{I_S}{V_T} e^{V_{BE}/V_T} \\
 &\approx n \frac{I_C}{V_T} \\
 &= n g_m \\
 &= \boxed{n \times 0.4435 \text{ S}} \\
 I_{B,Total} &= \frac{1}{\beta} I_{C,Total} \\
 r_{\pi,Total} &= \left( \frac{\partial I_{B,Total}}{\partial V_{BE}} \right)^{-1} \\
 &\approx \left( \frac{I_{C,Total}}{\beta V_T} \right)^{-1} \\
 &= \left( \frac{n I_C}{\beta V_T} \right)^{-1} \\
 &= \frac{r_{\pi}}{n} \\
 &= \boxed{\frac{225.5 \Omega}{n}} \quad (\text{assuming } \beta = 100) \\
 r_{o,Total} &= \left( \frac{\partial I_{C,Total}}{\partial V_{CE}} \right)^{-1} \\
 &\approx \left( \frac{I_{C,Total}}{V_A} \right)^{-1} \\
 &= \frac{V_A}{n I_C} \\
 &= \frac{r_o}{n} \\
 &= \boxed{\frac{693.8 \Omega}{n}}
 \end{aligned}$$

The small-signal model is shown below.

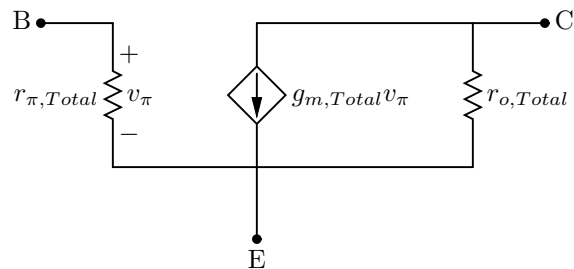

4.32 (a)


$$\begin{aligned}V_{BE} &= V_{CE} \text{ (for } Q_1 \text{ to operate at the edge of saturation)} \\V_T \ln(I_C/I_S) &= V_{CC} - I_C R_C \\I_C &= 885.7 \mu\text{A} \\V_B = V_{BE} &= \boxed{728.5 \text{ mV}}\end{aligned}$$

(b) Let  $I'_C$ ,  $V'_B$ ,  $V'_{BE}$ , and  $V'_{CE}$  correspond to the values where the collector-base junction is forward biased by 200 mV.

$$\begin{aligned}V'_{BE} &= V'_{CE} + 200 \text{ mV} \\V_T \ln(I'_C/I_S) &= V_{CC} - I'_C R_C + 200 \text{ mV} \\I'_C &= 984.4 \mu\text{A} \\V'_B &= 731.3 \text{ mV}\end{aligned}$$

Thus,  $V_B$  can increase by  $V'_B - V_B = \boxed{2.8 \text{ mV}}$  if we allow soft saturation.

33

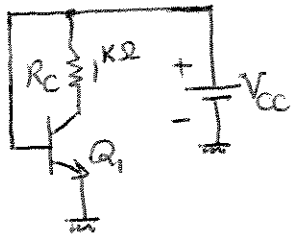

$$I_S = 7 \times 10^{-16} \text{ A}, \quad V_A = \infty$$
$$\Downarrow$$
$$r_o = \infty$$

Applying KVL,

$$V_{CC} = R_C I_C + V_{CE} \xrightarrow{V_{CE} = V_{BE} - 0.2 \text{ V}} R_C I_C + V_{BE} - 0.2 \text{ V} = V_{CC}$$

$$\Rightarrow R_C I_S e^{\frac{V_{BE}}{V_T}} + V_{BE} - 0.2 \text{ V} = V_{CC}$$

$$\xrightarrow{V_{BE} = V_{CC}} R_C I_S e^{\frac{V_{CC}}{V_T}} + V_{CC} - 0.2 = V_{CC}$$

$$\Rightarrow R_C I_S e^{\frac{V_{CC}}{V_T}} = 0.2 \text{ V}$$

$$\Rightarrow 1 \text{ k}\Omega \times 7 \times 10^{-16} e^{\frac{V_{CC}}{26 \text{ mV}}} = 0.2 \text{ V}$$


$$\Rightarrow \boxed{V_{CC} \approx 686 \text{ mV}}$$



4.34

$$\begin{aligned}V_{BE} &= V_{CC} - I_B R_B \\V_T \ln(I_C/I_S) &= V_{CC} - I_C R_B/\beta \\I_C &= 1.67 \text{ mA} \\V_{BC} &= V_{CC} - I_B R_B - (V_{CC} - I_C R_C) \\&< 200 \text{ mV} \\I_C R_C - I_B R_B &< 200 \text{ mV} \\R_C &< \frac{200 \text{ mV} + I_B R_B}{I_C} \\&= \frac{200 \text{ mV} + I_C R_B/\beta}{I_C} \\R_C &< \boxed{1.12 \text{ k}\Omega}\end{aligned}$$

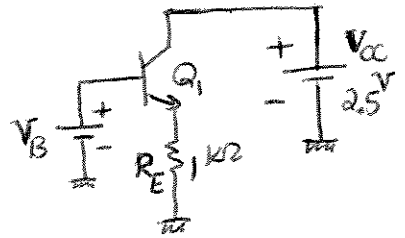35)  $I_S = 5 \times 10^{-16} \text{ A}$ ,  $V_A = \infty \Rightarrow r_o = \infty$



Soft saturation  $\Rightarrow V_{BC} = 200 \text{ mV}$

$\Rightarrow V_B = V_C + 0.2 \text{ V} \Rightarrow \boxed{V_B = 2.7 \text{ V}}$

Applying KVL  $\Rightarrow V_B = V_{BE} + R_E I_E \xrightarrow{I_E \approx I_C} V_B = V_{BE} + R_E I_C$

$\Rightarrow V_{BE} + 1 \text{ k} \times I_S e^{\frac{V_{BE}}{V_T}} = 2.7 \text{ V}$


$\Rightarrow V_{BE} + 5 \times 10^{-13} e^{\frac{V_{BE}}{V_T}} = 2.7 \text{ V} \Rightarrow \boxed{V_{BE} \approx 754 \text{ mV}}$

$I_C = I_S e^{\frac{V_{BE}}{V_T}} = 5 \times 10^{-16} e^{\frac{0.754}{0.026}} \Rightarrow \boxed{I_C \approx 2 \text{ mA}}$

$$\textcircled{36} \quad \beta = 100, \quad V_A = \infty \Rightarrow r_o = \infty$$

$$V_{BC} = 0.2 \text{ V} \Rightarrow R_p I_C = 0.2 \text{ V}$$
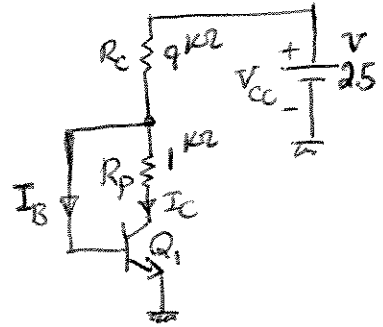
$$\Rightarrow \boxed{I_C = \frac{0.2 \text{ V}}{R_p}}$$



$$V_{BE} = V_{CC} - R_c (I_B + I_C)$$

$$\stackrel{\beta=100}{\Rightarrow} V_{BE} = V_{CC} - \frac{\beta+1}{\beta} R_c I_C \Rightarrow \boxed{V_{BE} = V_{CC} - \frac{\beta+1}{\beta} \frac{R_c \times 0.2}{R_p}}$$

$$I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \Rightarrow I_S = I_C \exp\left(-\frac{V_{BE}}{V_T}\right)$$

$$\Rightarrow \boxed{I_S = \frac{0.2}{R_p} \exp\left[\frac{0.2}{V_T} \cdot \frac{\beta+1}{\beta} \cdot \frac{R_c}{R_p} - \frac{V_{CC}}{V_T}\right]}$$

$$\stackrel{\beta=100}{\Rightarrow} \boxed{I_S \approx \frac{0.2}{R_p} \exp\left[\frac{0.2}{V_T} \frac{R_c}{R_p} - \frac{V_{CC}}{V_T}\right]}$$

$$\Rightarrow \boxed{I_S \approx 4.06 \times 10^{-16} \text{ A}}$$


$$\textcircled{37} \quad I_{S_1} = 3I_{S_2} = 6 \times 10^{-16} \text{ A}$$

$$I_1 = I_{S_1} \exp\left(\frac{V_{EB_1}}{V_T}\right) = 6 \times 10^{-16} \exp\left(\frac{300}{26}\right) \Rightarrow \underline{I_1 \approx 6.155 \times 10^{-11} \text{ A}}$$

$$I_2 = I_{S_2} \exp\left(\frac{V_{EB_2}}{V_T}\right) = 2 \times 10^{-16} \exp\left(\frac{820}{26}\right) \Rightarrow \underline{I_2 \approx 10 \text{ mA}}$$

$$I_X = I_1 + I_2 \Rightarrow \boxed{I_X \approx 10 \text{ mA}}$$
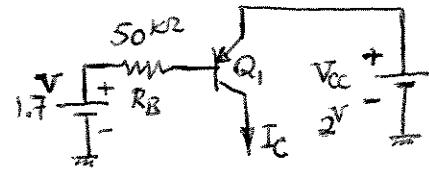
$$(38) \quad I_S = 2 \times 10^{-17} \text{ A} \quad \beta = 100$$



Applying KVL,

$$V_{CC} = V_{EB} + R_B I_B + 1.7 \text{ V}$$

$$\Rightarrow 2 \text{ V} = V_{EB} + R_B \frac{I_C}{\beta} + 1.7 \text{ V}$$

$$\Rightarrow 0.3 \text{ V} = V_{EB} + \frac{50 \text{ k}\Omega}{100} I_C$$

$$\Rightarrow 0.3 \text{ V} = V_{EB} + 500 \times I_S e^{\frac{V_{EB}}{V_T}}$$


$$\Rightarrow 0.3 \text{ V} = V_{EB} + 10^{-14} e^{\frac{V_{EB}}{26 \text{ mV}}} \Rightarrow \boxed{V_{EB} \approx 0.3 \text{ V}}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow I_C = 2 \times 10^{-17} e^{\frac{300}{26}}$$

$$\Rightarrow \boxed{I_C \approx 2.05 \times 10^{-12} \text{ A}}$$

③⑨  $I_C = 3\text{mA}$  ,  $\beta = 100$  ,  $R_B = 23\text{k}\Omega$

Applying KVL,

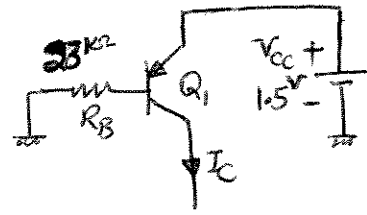

$$V_{CC} = V_{EB} + R_B I_B \Rightarrow V_{CC} = V_{EB} + R_B \frac{I_C}{\beta}$$

$$\Rightarrow -I_C \frac{R_B}{\beta} + V_{CC} = V_{EB}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}}$$

$$\Rightarrow I_S = I_C e^{\frac{-V_{EB}}{V_T}}$$


$$\Rightarrow I_S = I_C e^{\frac{1}{V_T} \left( \frac{R_B I_C}{\beta} - V_{CC} \right)}$$

$$\Rightarrow I_S \approx 8.85 \times 10^{-17} \text{ A}$$

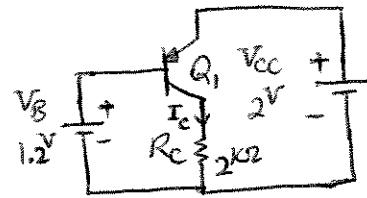40) At the edge of active  $\Rightarrow V_{BC} = 0$

$$I_C = \frac{V_B - V_{BC}}{R_C} = \frac{V_B}{R_C}$$

$$\Rightarrow I_C = \frac{1.2\text{V}}{2\text{k}\Omega} \Rightarrow \boxed{I_C \approx 0.6\text{ mA}}$$



$$I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right) \Rightarrow I_S = I_C \exp\left(-\frac{V_{EB}}{V_T}\right)$$

$$\Rightarrow I_S = 0.6 \times 10^{-3} \exp\left(-\frac{800}{26}\right)$$


$$\Rightarrow \boxed{I_S \approx 2.6 \times 10^{-17}\text{ A}}$$

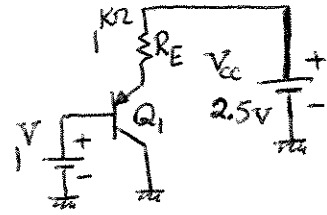4.41

$$\begin{aligned}V_{EB} &= V_{EC} \text{ (for } Q_1 \text{ to operate at the edge of saturation)} \\V_{CC} - I_B R_B &= V_{CC} - I_C R_C \\I_C R_B / \beta &= I_C R_C \\R_B / \beta &= R_C \\\beta &= R_B / R_C \\&= \boxed{100}\end{aligned}$$



$$(42) I_S = 3 \times 10^{-17} \text{ A}$$



Applying KVL,

$$V_{CC} = R_E I_E + V_{EB} + 1 \text{ V} \quad \xrightarrow{I_E = I_C} \quad V_{CC} = R_E I_C + V_{EB} + 1 \text{ V}$$

$$\Rightarrow 2.5 = 1 \text{ k}\Omega \times 3 \times 10^{-17} e^{\frac{V_{EB}}{26 \text{ mV}}} + V_{EB} + 1 \text{ V}$$

$$\Rightarrow V_{EB} + 3 \times 10^{-14} e^{\frac{V_{EB}}{26 \text{ mV}}} = 1.5 \text{ V}$$

$$\Rightarrow \boxed{V_{EB} \approx 800.5 \text{ mV}}$$

$$I_C = I_S e^{\frac{V_{EB}}{V_T}} = 3 \times 10^{-17} e^{\frac{800.5}{26}} \Rightarrow \boxed{I_C \approx 0.705 \text{ mA}}$$

④  $I_S = 3 \times 10^{-17} \text{ A}$ ,  $\beta = 100$ ,  $V_A = \infty \Rightarrow r_o = \infty$


a)  $V_{EB} = 2.5 - 1.7 = 0.8 \text{ V}$

$I_C = I_S \exp\left(\frac{V_{EB}}{V_T}\right) = 3 \times 10^{-17} \exp\left(\frac{0.8}{26}\right) \Rightarrow I_C \approx 0.692 \text{ mA}$

$V_{EC} = V_{CC} - R_C I_C = 2.5 - 1 \times 0.692 \Rightarrow V_{EC} \approx 1.808 \text{ V}$

$g_m = \frac{I_C}{V_T} = \frac{0.692 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m \approx 26.6 \text{ mS}$

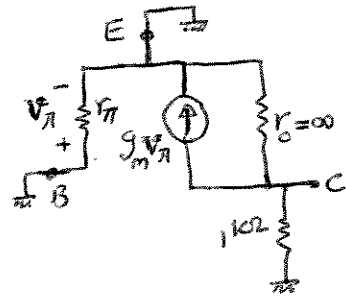$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{26.6 \times 10^{-3}} \Rightarrow r_{\pi} \approx 3.76 \text{ k}\Omega$



b)  $V_{EB} = V_T \ln\left(\frac{I_C}{I_S}\right) \Rightarrow V_{EB} = V_T \ln\left(\frac{\beta I_B}{I_S}\right)$


$\Rightarrow V_{EB} = 26 \text{ mV} \times \ln\left(\frac{100 \times 20 \times 10^{-6}}{3 \times 10^{-17}}\right)$

$\Rightarrow V_{EB} \approx 827.6 \text{ mV}$

$I_C = \beta I_B \Rightarrow I_C = 2 \text{ mA}$

$V_{EC} = V_{CC} - R_C I_C = 2.5 - 0.5 \times 2 \Rightarrow V_{EC} = 1.5 \text{ V}$

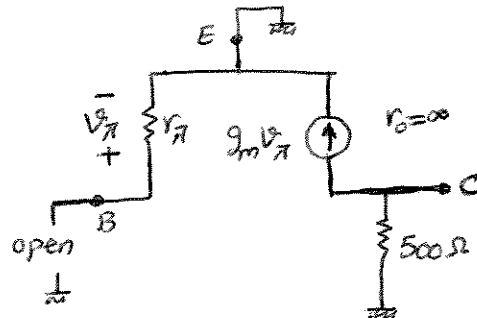$g_m = \frac{I_C}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_m \approx 77 \text{ mS}$        $r_{\pi} = \frac{\beta}{g_m} \Rightarrow r_{\pi} \approx 1.3 \text{ k}\Omega$



43) Continued .....

c) Applying KVL,

$$V_{cc} = V_{EB} + (I_C + I_B) \times 2^{k\Omega} \approx V_{EB} + 2^{k\Omega} \times I_C$$


$$\Rightarrow V_{EB} + 2^{k\Omega} \times I_S e^{\frac{V_{EB}}{V_T}} = V_{cc}$$

$$\Rightarrow V_{EB} + 6 \times 10^{-14} e^{\frac{V_{EB}}{26^{mV}}} = 2.5^V \Rightarrow \boxed{V_{EB} \approx 805^{mV}}$$

$$I_C = \frac{V_{cc} - V_{EB}}{R} = \frac{2.5 - 0.805}{2^{k\Omega}} \Rightarrow \boxed{I_C \approx 847.5 \mu A}$$

$$g_m = \frac{I_C}{V_T} = \frac{0.8475 \times 10^{-3}}{0.026} \Rightarrow \boxed{g_m \approx 32.6 \text{ mS}}$$
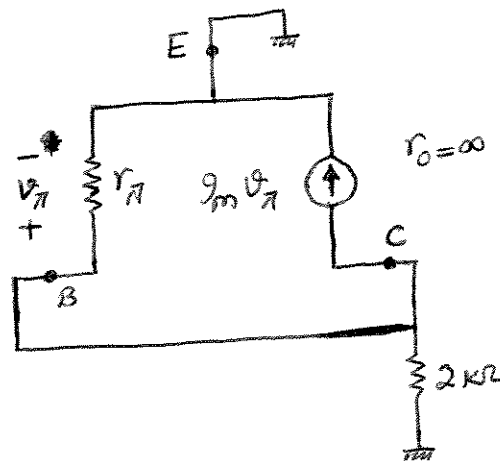
$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{32.6 \times 10^{-3}} \Rightarrow \boxed{r_{\pi} \approx 3068 \Omega}$$




4.44 (a)

$$\begin{aligned}
 I_B &= 2 \mu\text{A} \\
 I_C &= \beta I_B \\
 &= \boxed{200 \mu\text{A}} \\
 V_{EB} &= V_T \ln(I_C/I_S) \\
 &= \boxed{768 \text{ mV}} \\
 V_{EC} &= V_{CC} - I_E(2 \text{ k}\Omega) \\
 &= V_{CC} - \frac{1 + \beta}{\beta} I_C(2 \text{ k}\Omega) \\
 &= \boxed{2.1 \text{ V}}
 \end{aligned}$$

$Q_1$  is operating in forward active. Its small-signal parameters are

$$\begin{aligned}
 g_m &= I_C/V_T = \boxed{7.69 \text{ mS}} \\
 r_\pi &= \beta/g_m = \boxed{13 \text{ k}\Omega} \\
 r_o &= \boxed{\infty}
 \end{aligned}$$

The small-signal model is shown below.

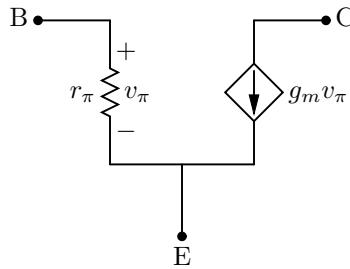


(b)

$$\begin{aligned}
 I_E &= \frac{V_{CC} - V_{EB}}{5 \text{ k}\Omega} \\
 \frac{1 + \beta}{\beta} I_C &= \frac{V_{CC} - V_T \ln(I_C/I_S)}{5 \text{ k}\Omega} \\
 I_C &= \boxed{340 \mu\text{A}} \\
 V_{EB} &= \boxed{782 \text{ mV}} \\
 V_{EC} = V_{EB} &= \boxed{782 \text{ mV}}
 \end{aligned}$$

$Q_1$  is operating in forward active. Its small-signal parameters are

$$\begin{aligned}
 g_m &= I_C/V_T = \boxed{13.1 \text{ mS}} \\
 r_\pi &= \beta/g_m = \boxed{7.64 \text{ k}\Omega} \\
 r_o &= \boxed{\infty}
 \end{aligned}$$

The small-signal model is shown below.

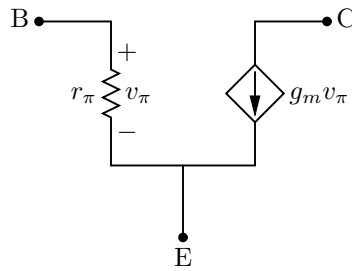

(c)

$$I_E = \frac{1 + \beta}{\beta} I_C = 0.5 \text{ mA}$$

$$I_C = \boxed{495 \text{ } \mu\text{A}}$$

$$V_{EB} = \boxed{971 \text{ mV}}$$

$$V_{EC} = V_{EB} = \boxed{971 \text{ mV}}$$


$Q_1$  is operating in forward active. Its small-signal parameters are

$$g_m = I_C / V_T = \boxed{19.0 \text{ mS}}$$

$$r_\pi = \beta / g_m = \boxed{5.25 \text{ k}\Omega}$$


$$r_o = \boxed{\infty}$$

The small-signal model is shown below.

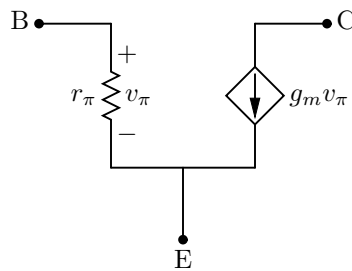

45)  $I_S = 5 \times 10^{-17} \text{ A}$

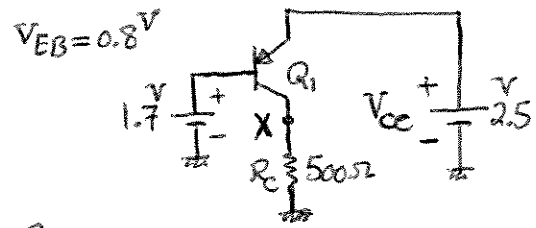a)  $V_A = \infty \Rightarrow r_o = \infty$



$$I_c = I_S e^{\frac{V_{EB}}{V_T}} \Rightarrow I_c = 5 \times 10^{-17} e^{\frac{0.8}{0.026}} \Rightarrow \boxed{I_c = 1.15 \text{ mA}}$$

$$V_x = R_c I_c = 0.5 \times 1.15 \text{ mA} \Rightarrow \boxed{V_x = 0.58 \text{ V}}$$

b)  $V_A = 6 \text{ V}$

$$I_c = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{EC}}{V_A} \right), \quad V_{EC} = V_{CC} - R_c I_c$$

$$\Rightarrow I_c = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{CC} - R_c I_c}{V_A} \right)$$

$$\Rightarrow I_c = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{CC}}{V_A} \right) - \frac{I_S R_c}{V_A} e^{\frac{V_{EB}}{V_T}} I_c$$

$$\Rightarrow \boxed{I_c = \frac{I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{CC}}{V_A} \right)}{1 + \frac{I_S R_c}{V_A} e^{\frac{V_{EB}}{V_T}}} = \frac{5 \times 10^{-17} e^{\frac{0.8}{0.026}} \left( 1 + \frac{2.5}{6} \right)}{1 + \frac{5 \times 10^{-17} \times 0.5}{6} e^{\frac{0.8}{0.026}}}}$$

$$\Rightarrow \boxed{I_c = 1.49 \text{ mA}} \quad V_x = R_c I_c = 500 \times 1.49 \times 10^{-3} \Rightarrow \boxed{V_x = 0.745 \text{ V}}$$

$$(46) \quad r_o = 60 \text{ k}\Omega, \quad I_C = 2 \text{ mA}$$

$$r_o = \frac{V_A}{I_C} \Rightarrow 60 \times 10^3 \Omega = \frac{V_A}{2 \times 10^{-3} \text{ A}} \Rightarrow \boxed{V_A = 120 \text{ V}}$$

$$\textcircled{47} \quad r_o = 60 \text{ k}\Omega, \quad I_C = 1 \text{ mA}$$

$$r_o = \frac{V_A}{I_C} \Rightarrow \boxed{V_A = r_o \cdot I_C} \Rightarrow \boxed{V_A \propto I_C}$$

$$\Rightarrow V_A = 60 \text{ k}\Omega \times 1 \text{ mA}$$


$$\Rightarrow \boxed{V_A = 60 \text{ V}}$$

$V_A$  is half the value in <sup>problem</sup> 46 as  $V_A$  is proportional to  $I_C$ .



48)  $V_A = 5\text{V}$

a) At the edge of active mode

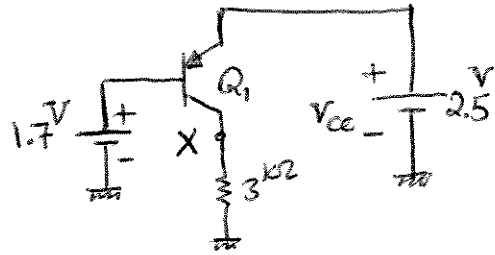

$$\Rightarrow V_X = V_B = 1.7\text{V}$$

$$I_C = \frac{V_X}{R_C} = \frac{1.7\text{V}}{3\text{k}\Omega} \Rightarrow I_C \approx 0.567\text{mA}$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \left(1 + \frac{V_{CE}}{V_A}\right) \Rightarrow I_S = \frac{I_C e^{-\frac{V_{BE}}{V_T}}}{1 + \frac{V_{CE}}{V_A}}$$

$$I_S = \frac{0.567 \times 10^{-3} e^{-\frac{800}{26}}}{1 + \frac{2.5 - 1.7}{5}} \Rightarrow I_S \approx 2.118 \times 10^{-17}\text{A}$$

b)  $V_A = \infty$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}} \Rightarrow I_S = I_C e^{-\frac{V_{BE}}{V_T}}$$

$$I_S = 0.567 \times 10^{-3} e^{-\frac{800}{26}} \Rightarrow I_S \approx 2.457 \times 10^{-17}\text{A}$$


$I_S$  increases

4.49 The direction of current flow in the large-signal model (Fig. 4.40) indicates the direction of positive current flow when the transistor is properly biased.

The direction of current flow in the small-signal model (Fig. 4.43) indicates the direction of positive change in current flow when the base-emitter voltage  $v_{be}$  increases. For example, when  $v_{be}$  increases, the current flowing into the collector increases, which is why  $i_c$  is shown flowing into the collector in Fig. 4.43. Similar reasoning can be applied to the direction of flow of  $i_b$  and  $i_e$  in Fig. 4.43.

⑤  $I_S = 6 \times 10^{-16} \text{ A}$ ,  $V_A = 5 \text{ V}$ ,  $I_1 = 2 \text{ mA}$

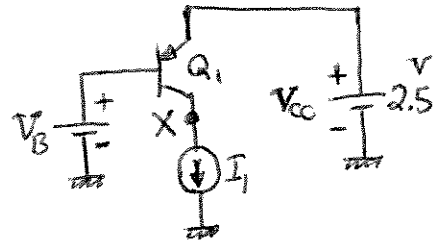a)  $I_C = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{EC}}{V_A} \right)$



$\Rightarrow V_{EB} = V_T \ln \left( \frac{I_C}{I_S \left( 1 + \frac{V_{EC}}{V_A} \right)} \right)$

$V_{EC} = V_{CC} - V_X$   
 $V_{EB} = V_{CC} - V_B$

$$V_B = V_{CC} - V_T \ln \left( \frac{I_C}{I_S \left( 1 + \frac{V_{CC} - V_X}{V_A} \right)} \right)$$

$\Rightarrow V_B = 2.5 - 0.026 \ln \left( \frac{2 \times 10^{-3}}{6 \times 10^{-16} \left( 1 + \frac{2.5 - 1}{5} \right)} \right) \Rightarrow V_B \approx 1.757 \text{ V}$

b)  $I_C = I_S e^{\frac{V_{EB}}{V_T}} \left( 1 + \frac{V_{EC}}{V_A} \right) \Rightarrow 1 + \frac{V_{EC}}{V_A} = \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}}$

$V_{EC} = V_{CC} - V_X$   
 $V_{EB} = V_{CC} - V_B$

$$V_X = V_{CC} - V_A \left( \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} - 1 \right)$$

$\Delta V_X \approx \frac{dV_X}{dV_{EB}} \Delta V_{EB} \Rightarrow \Delta V_X \approx \frac{V_A}{V_T} \cdot \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} \Delta V_{EB}$


$\Delta V_{EB} = -\Delta V_B$

$$\Delta V_X \approx -\frac{V_A}{V_T} \cdot \frac{I_C}{I_S} e^{-\frac{V_{EB}}{V_T}} \Delta V_B$$

$\Rightarrow \Delta V_X \approx -\frac{5}{0.026} \times \frac{2 \times 10^{-3}}{6 \times 10^{-16}} \exp \left( -\frac{2.5 - 1.757}{0.026} \right) \times 0.1 \times 10^{-3} \Rightarrow \Delta V_X \approx -24.9 \text{ mV}$

50) Continued .....

c)

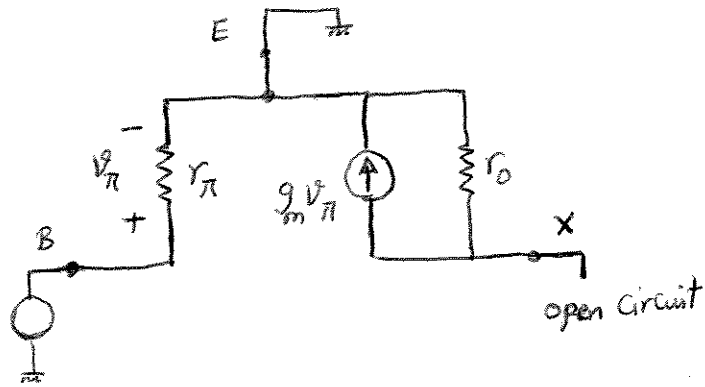


$$r_o = \frac{V_A}{I_C} = \frac{5\text{V}}{2\text{mA}} \Rightarrow \boxed{r_o \approx 2.5\text{ k}\Omega}$$

$$g_m = \frac{I_C}{V_T} = \frac{2\text{mA}}{0.026\text{V}} \Rightarrow \boxed{g_m \approx 76.9\text{ mS}}$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{\frac{2}{26}} \Rightarrow \boxed{r_{\pi} = 1.3\text{ k}\Omega}$$

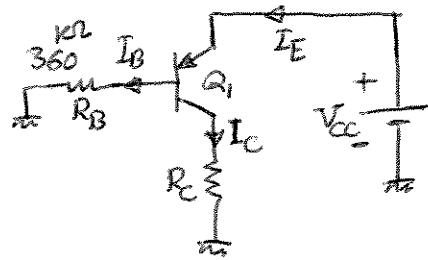⑤  $\beta = 100, V_A = \infty \Rightarrow r_o = \infty$   
 $R_B = 360 \text{ k}\Omega$



a) given:  $V_C = V_B + 0.2 \text{ V}$

$$\Rightarrow R_C I_C = R_B I_B + 0.2 \text{ V}$$

$$\Rightarrow R_C I_C = R_B \frac{I_C}{\beta} + 0.2 \text{ V} \Rightarrow \boxed{I_C = \frac{0.2 \text{ V}}{R_C - \frac{R_B}{\beta}}} \Rightarrow \boxed{I_C = 0.5 \text{ mA}}$$

$$I_C = I_S e^{+\frac{V_{EB}}{V_T}} \Rightarrow I_S = I_C e^{-\frac{V_{EB}}{V_T}} \Rightarrow I_S = I_C e^{-\left(\frac{V_{CC} - R_B I_B}{V_T}\right)}$$

$$\Rightarrow \boxed{I_S = \left(\frac{0.2}{R_C - \frac{R_B}{\beta}}\right) \exp\left[-\frac{1}{V_T} \left(V_{CC} - R_B \times \frac{0.2 \text{ V}}{\beta \left(R_C - \frac{R_B}{\beta}\right)}\right)\right]}$$

$$\Rightarrow \boxed{I_S \approx 10^{-15} \text{ A} = 1 \text{ fA}}$$

b)  $g_m = \frac{I_C}{V_T}$

$$\Rightarrow \boxed{g_m = \frac{0.2 \text{ V}}{V_T \left(R_C - \frac{R_B}{\beta}\right)}} \Rightarrow \boxed{g_m \approx 19.23 \text{ mS}}$$

$$\textcircled{52} \quad I_S = 5 \times 10^{-16} \text{ A}, \quad \beta = 100, \quad V_A = \infty \Rightarrow r_o = \infty$$

$$\text{a) } V_{EB} = 0 \Rightarrow Q_1 \text{ is off} \quad I_C = 0$$

$$\text{b) } I_B = 0 \Rightarrow Q_1 \text{ is off}$$

$$\text{c) Applying KVL: } V_{CC} = V_{EB} + 1 \text{ k}\Omega \times I_C$$

$$\Rightarrow V_{EB} + 1 \text{ k}\Omega \times I_S e^{\frac{V_{EB}}{V_T}} \approx V_{CC} \Rightarrow V_{EB} + 5 \times 10^{-13} e^{\frac{V_{EB}}{26 \text{ mV}}} \approx 2.5 \text{ V}$$

$$\Rightarrow \boxed{V_{EB} \approx 751 \text{ mV}} \quad I_C = 5 \times 10^{-16} e^{\frac{0.751}{0.026}} \Rightarrow \boxed{I_C \approx 1.8 \text{ mA}}$$

With this current, transistor is saturated. Note  $V_B < V_C$  Always

$$\text{d) } V_{BC} = 0 \Rightarrow \text{Transistor is at the edge of saturation}$$

$$\text{e) } I_C \approx 0.5 \text{ mA} \Rightarrow V_{EB} = V_T \ln\left(\frac{I_C}{I_S}\right) = 26 \text{ mV} \ln\left(\frac{0.5 \text{ mA}}{5 \times 10^{-16}}\right)$$

$$\Rightarrow \boxed{V_{EB} \approx 718 \text{ mV}}$$

$$V_{\text{collector}} = 500 \Omega \times I_C \Rightarrow \boxed{V_C = 0.25 \text{ V}}$$

As  $V_B = 0$ ,  $V_C = 0.25 \text{ V} \Rightarrow$  Transistor is soft saturated

4.53 (a)

$$V_{CB2} < 200 \text{ mV}$$

$$I_{C2}R_C < 200 \text{ mV}$$

$$I_{C2} < 400 \text{ } \mu\text{A}$$

$$\begin{aligned} V_{EB2} &= V_{E2} \\ &= V_T \ln(I_{C2}/I_{S2}) \\ &< 741 \text{ mV} \end{aligned}$$

$$\frac{\beta_2}{1 + \beta_2} I_{E2} R_C < 200 \text{ mV}$$

$$\frac{\beta_2}{1 + \beta_2} \frac{1 + \beta_1}{\beta_1} I_{C1} R_C < 200 \text{ mV}$$

$$I_{C1} < 396 \text{ } \mu\text{A}$$

$$\begin{aligned} V_{BE1} &= V_T \ln(I_{C1}/I_{S1}) \\ &< 712 \text{ mV} \end{aligned}$$

$$V_{in} = V_{BE1} + V_{EB2}$$

$$< \boxed{1.453 \text{ V}}$$

(b)

$$I_{C1} = 396 \text{ } \mu\text{A}$$

$$I_{C2} = 400 \text{ } \mu\text{A}$$

$$g_{m1} = \boxed{15.2 \text{ mS}}$$

$$r_{\pi1} = \boxed{6.56 \text{ k}\Omega}$$


$$r_{o1} = \boxed{\infty}$$

$$g_{m2} = \boxed{15.4 \text{ mS}}$$

$$r_{\pi2} = \boxed{3.25 \text{ k}\Omega}$$

$$r_{o2} = \boxed{\infty}$$


The small-signal model is shown below.

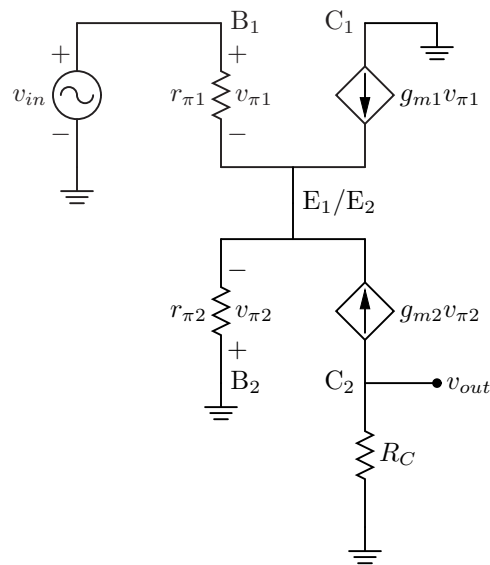

54)  $I_{S1} = 3I_{S2} = 5 \times 10^{-16} \text{ A}$ ,  $\beta_1 = 100$ ,  $\beta_2 = 50$ ,  $V_A = \infty$

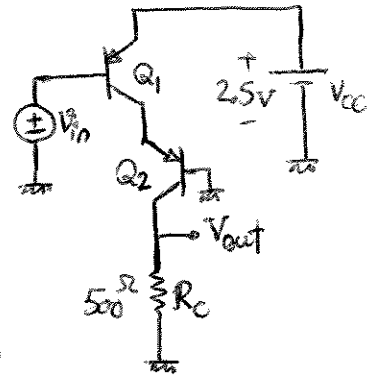a)  $V_{B2} = \phi$   $\xrightarrow[\text{Forward biased by } 200\text{mV}]{Q_2 \text{ Base-Collector}}$   $V_{C2} = 0.2 \text{ V}$

$\Rightarrow I_{C2} = \frac{V_{C2\text{max}}}{R_c} = \frac{0.2 \text{ V}}{500 \Omega} \Rightarrow \boxed{I_{C2} = 0.4 \text{ mA}}$



As shown:  $I_{C1} \approx I_{C2}$  (Note:  $I_{C1} = I_{E2} = \frac{\beta_2 + 1}{\beta_2} I_{C2}$  precisely)

$I_{C1} \approx I_{S1} e^{\frac{V_{EB1}}{V_T}} \Rightarrow V_{EB1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) \Rightarrow V_{CC} - V_{in} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)$


$\Rightarrow \boxed{V_{in} = V_{CC} - V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right)} \Rightarrow V_{in} = 2.5 - 0.026 \ln\left(\frac{4 \times 10^{-4}}{5 \times 10^{-16}}\right)$

$\Rightarrow \boxed{V_{in} = 1.787 \text{ V}}$  This is minimum acceptable  $V_{in}$

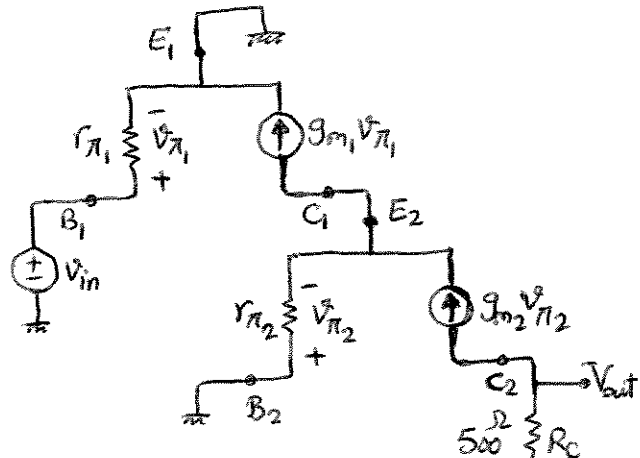b)  $g_{m1} = \frac{I_{C1}}{V_T} \approx \frac{0.4 \text{ mA}}{26 \text{ mV}}$

$g_{m2} = \frac{I_{C2}}{V_T} = \frac{0.4 \text{ mA}}{26 \text{ mV}}$

$\Rightarrow \boxed{g_{m1} = g_{m2} \approx 15.4 \text{ mS}}$



$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{100}{\frac{0.4}{26}} \Rightarrow \boxed{r_{\pi 1} = 6.5 \text{ k}\Omega}$

$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = \frac{50}{\frac{0.4}{26}} = \boxed{3.25 \text{ k}\Omega}$

$V_{EB2} = V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right) = 26 \text{ mV} \ln\left(\frac{0.4 \times 10^{-3}}{5 \times 10^{-16}}\right) \Rightarrow \boxed{V_{EB2} \approx 741 \text{ mV}} \Rightarrow \boxed{V_{EC1} \approx 1.759 \text{ V}}$

$Q_1$  in active mode




4.55 (a)

$$\begin{aligned}
 V_{BC2} &< 200 \text{ mV} \\
 V_{BE2} - (V_{CC} - I_{C2}R_C) &< 200 \text{ mV} \\
 V_T \ln(I_{C2}/I_{S2}) + I_{C2}R_C - V_{CC} &< 200 \text{ mV} \\
 I_{C2} &< 3.80 \text{ mA} \\
 V_{BE2} &< 799.7 \text{ mV} \\
 I_{E1} = \frac{1 + \beta_1}{\beta_1} I_{C1} = I_{B2} = I_{C2}/\beta_2 \\
 I_{C1} &< 75.3 \text{ } \mu\text{A} \\
 V_{BE1} &< 669.2 \text{ mV} \\
 V_{in} = V_{BE1} + V_{BE2} \\
 &< \boxed{1.469 \text{ V}}
 \end{aligned}$$

(b)

$$\begin{aligned}
 I_{C1} &= 75.3 \text{ } \mu\text{A} \\
 I_{C2} &= 3.80 \text{ mA} \\
 g_{m1} &= \boxed{2.90 \text{ mS}} \\
 r_{\pi 1} &= \boxed{34.5 \text{ k}\Omega} \\
 r_{o1} &= \boxed{\infty} \\
 g_{m2} &= \boxed{146.2 \text{ mS}} \\
 r_{\pi 2} &= \boxed{342 \text{ }\Omega} \\
 r_{o2} &= \boxed{\infty}
 \end{aligned}$$

The small-signal model is shown below.

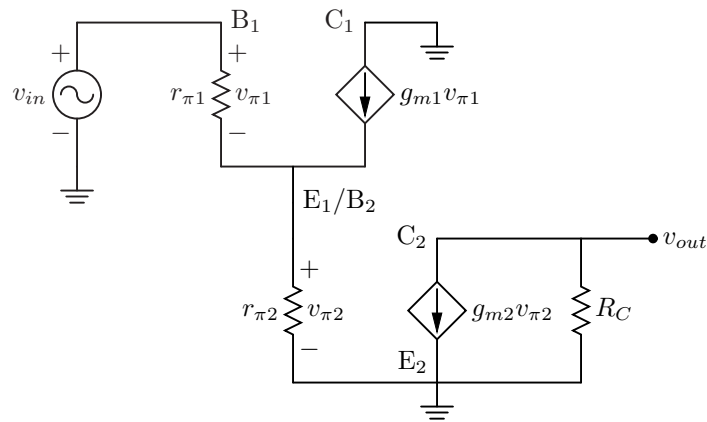


56)  $I_{S1} = 2I_{S2} = 6 \times 10^{-17} \text{ A}$ ,  $\beta_1 = 80$ ,  $\beta_2 = 100$

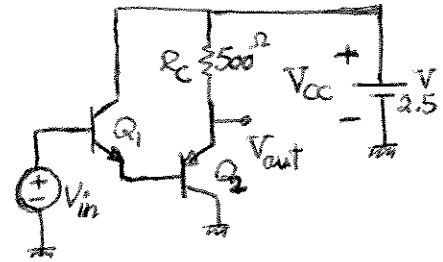a)  $I_{C2} = 2 \text{ mA}$

$$V_{EB2} = V_T \ln \frac{I_{C2}}{I_{S2}} = 26 \text{ mV} \ln \left( \frac{2 \times 10^{-3}}{3 \times 10^{-17}} \right) \approx 827.6 \text{ mV}$$

$$V_{BE1} = V_T \ln \frac{I_{C1}}{I_{S1}} = 26 \text{ mV} \ln \left( \frac{2 \times 10^{-3}}{6 \times 10^{-17}} \right) \approx 689.9 \text{ mV}$$



$$V_{in} = V_{CC} - R_C I_{C2} - V_{EB2} + V_{BE1} = 2.5 - 0.5 \times 2 - 0.8276 + 0.6899$$

$$\Rightarrow V_{in} = 1.362 \text{ V}$$


b)  $g_{m2} = \frac{I_{C2}}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_{m2} \approx 76.9 \text{ mS}$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{2 \text{ mA}}{26 \text{ mV}} \Rightarrow g_{m2} \approx 76.9 \mu\text{S}$$

$$r_{\pi 1} = \frac{\beta_1}{g_{m1}} = \frac{80}{1/1300}$$


$$\Rightarrow r_{\pi 1} = 104 \text{ k}\Omega$$
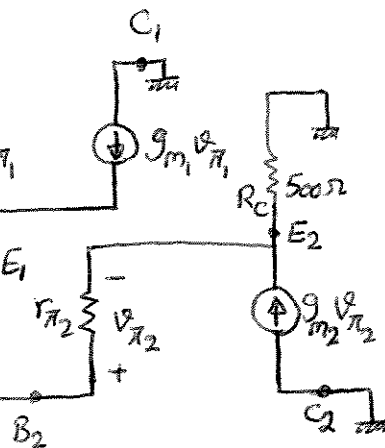
$$r_{\pi 2} = \frac{\beta_2}{g_{m2}} = \frac{100}{2/26} \Rightarrow r_{\pi 2} = 1300 \Omega$$



$$V_A = \infty \Rightarrow r_o = \infty$$


1)

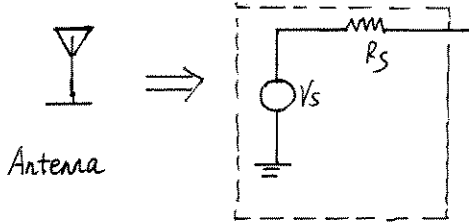

Thevenin Equivalent:

$$V_s = V_0 \cos \omega t$$

$$R_s = R_{out}$$

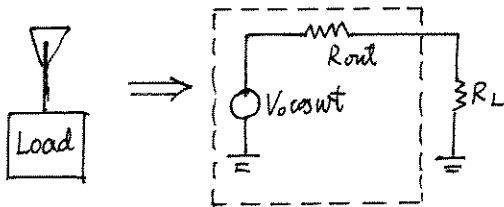

Average power delivered to load =  $(I_{RMS})^2 R_L$ ,

$$I_{RMS} = \frac{V_{RMS}}{R_{out} + R_L}, \quad V_{RMS} = \frac{V_0}{\sqrt{2}} \Rightarrow I_{RMS} = \frac{V_0}{\sqrt{2}(R_{out} + R_L)}$$

$$\text{Average power} = (I_{RMS})^2 R_L = \frac{V_0^2 R_L}{2(R_{out} + R_L)^2} \quad (\text{Eq. 1})$$

Plot of Average Power

When  $R_L$  is small, Eq. 1 is small.

When  $R_L$  is large, Eq. 1 is also small.


So for some  $R_L$  between zero and infinity, the average power will reach its peak. Let's take the derivative of Eq. 1 with respect to  $R_L$  to find the optimum  $R_L$ .

$$\frac{\partial}{\partial R_L} \left[ \frac{V_0^2 R_L}{2(R_{out} + R_L)^2} \right] = \frac{V_0^2}{2(R_{out} + R_L)^2} - \frac{V_0^2 R_L}{(R_{out} + R_L)^3}$$


Setting it to zero and solve for  $R_L$

$$\frac{V_0^2}{2(R_{out} + R_L)^2} = \frac{V_0^2 R_L}{(R_{out} + R_L)^3} \Rightarrow \frac{(R_{out} + R_L)}{2} = R_L$$

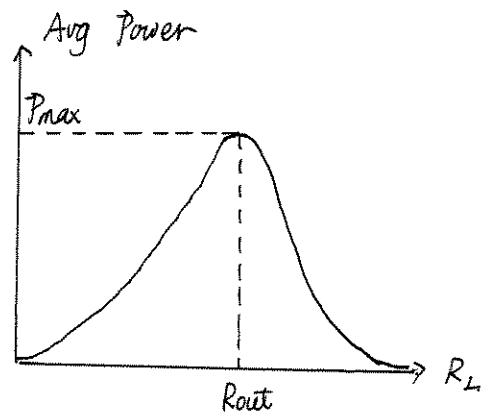
$$\Rightarrow R_{out} + R_L = 2R_L \Rightarrow R_L = R_{out}$$



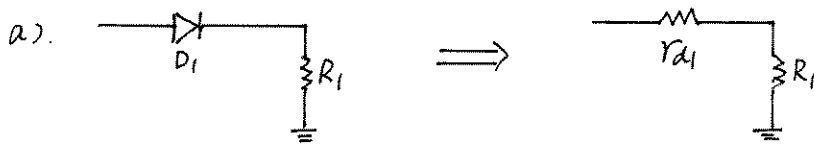
2) In small signal operation, a diode can be replaced by a linear resistor if charges are small.



$$R_{in} = r_{d1} + R_1$$

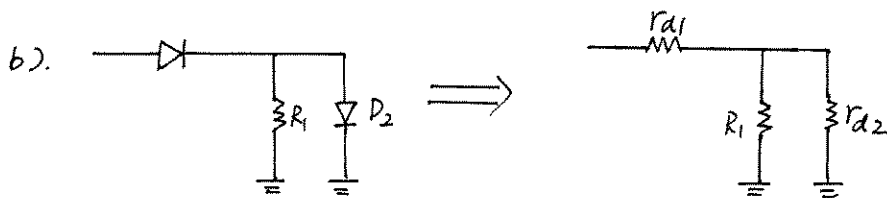

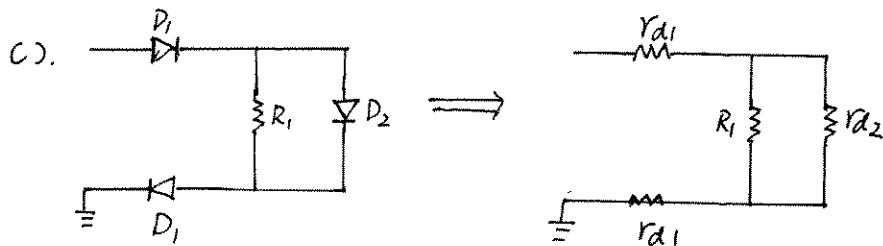
$$R_{in} = r_{d1} + R_1 // r_{d2} \quad ( // \text{ means in parallel } )$$




$$R_{in} = 2r_{d1} + R_1 // r_{d2}$$

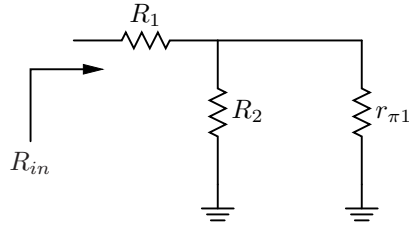- 5.3 (a) Looking into the base of  $Q_1$  we see an equivalent resistance of  $r_{\pi 1}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = R_1 + R_2 \parallel r_{\pi 1}$$

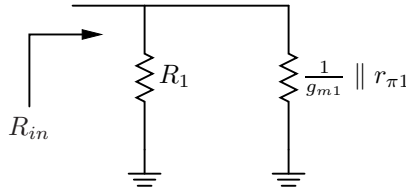- (b) Looking into the emitter of  $Q_1$  we see an equivalent resistance of  $\frac{1}{g_{m1}} \parallel r_{\pi 1}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = R_1 \parallel \left( \frac{1}{g_{m1}} \parallel r_{\pi 1} \right)$$

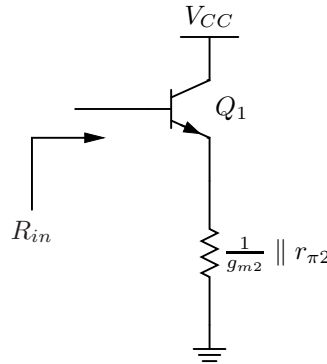- (c) Looking down from the emitter of  $Q_1$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

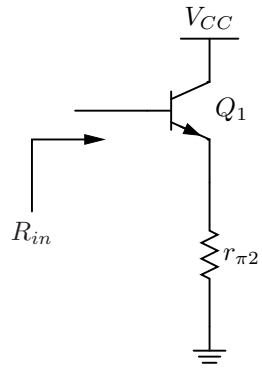- (d) Looking into the base of  $Q_2$  we see an equivalent resistance of  $r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = r_{\pi 1} + (1 + \beta_1)r_{\pi 2}$$

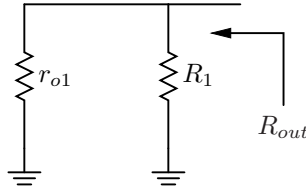- 5.4 (a) Looking into the collector of  $Q_1$  we see an equivalent resistance of  $r_{o1}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = r_{o1} \parallel R_1$$

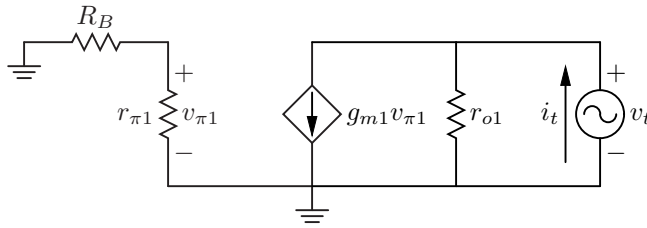- (b) Let's draw the small-signal model and apply a test source at the output.




$$i_t = g_{m1}v_{\pi 1} + \frac{v_t}{r_{o1}}$$

$$v_{\pi 1} = 0$$

$$i_t = \frac{v_t}{r_{o1}}$$


$$R_{out} = \frac{v_t}{i_t} = r_{o1}$$

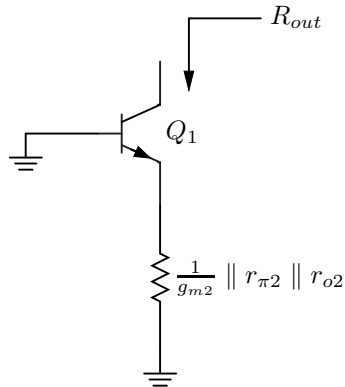- (c) Looking down from the emitter of  $Q_1$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1}) \left( r_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

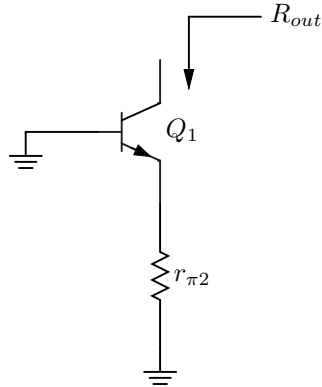
- (d) Looking into the base of  $Q_2$  we see an equivalent resistance of  $r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = \boxed{r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi 1} \parallel r_{\pi 2})}$$




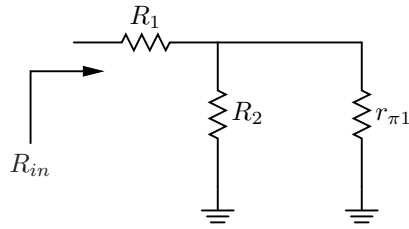- 5.5 (a) Looking into the base of  $Q_1$  we see an equivalent resistance of  $r_{\pi 1}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :



$$R_{in} = R_1 + R_2 \parallel r_{\pi 1}$$

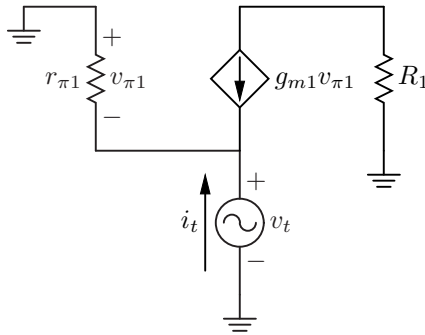- (b) Let's draw the small-signal model and apply a test source at the input.



$$i_t = -\frac{v_{\pi 1}}{r_{\pi 1}} - g_{m1}v_{\pi 1}$$


$$v_{\pi 1} = -v_t$$

$$i_t = \frac{v_t}{r_{\pi 1}} + g_{m1}v_t$$

$$i_t = v_t \left( g_{m1} + \frac{1}{r_{\pi 1}} \right)$$


$$R_{in} = \frac{v_t}{i_t} = \frac{1}{g_{m1}} \parallel r_{\pi 1}$$

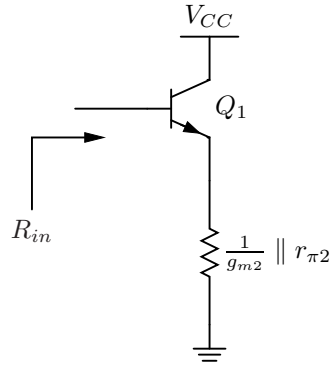- (c) From our analysis in part (b), we know that looking into the emitter we see a resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2}$ . Thus, we can draw the following equivalent circuit for finding  $R_{in}$ :



$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

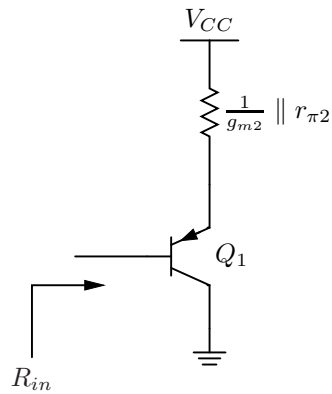
- (d) Looking up from the emitter of  $Q_1$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :



$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$


- (e) We know that looking into the base of  $Q_2$  we see  $R_{in} = r_{\pi 2}$  if the emitter is grounded. Thus, transistor  $Q_1$  does not affect the input impedance of this circuit.

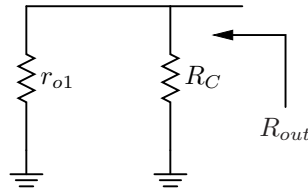- 5.6 (a) Looking into the collector of  $Q_1$  we see an equivalent resistance of  $r_{o1}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = R_C \parallel r_{o1}$$

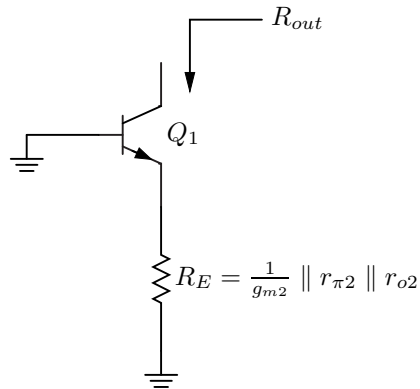- (b) Looking into the emitter of  $Q_2$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1}) \left( r_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

5.7 (a)

$$\begin{aligned}V_{CC} - I_B(100 \text{ k}\Omega) &= V_{BE} = V_T \ln(I_C/I_S) \\V_{CC} - \frac{1}{\beta}I_C(100 \text{ k}\Omega) &= V_T \ln(I_C/I_S) \\I_C &= \boxed{1.754 \text{ mA}} \\V_{BE} &= V_T \ln(I_C/I_S) = \boxed{746 \text{ mV}} \\V_{CE} &= V_{CC} - I_C(500 \text{ }\Omega) = \boxed{1.62 \text{ V}}\end{aligned}$$

$Q_1$  is operating in forward active.

(b)

$$\begin{aligned}I_{E1} &= I_{E2} \Rightarrow V_{BE1} = V_{BE2} \\V_{CC} - I_{B1}(100 \text{ k}\Omega) &= 2V_{BE1} \\V_{CC} - \frac{1}{\beta}I_{C1}(100 \text{ k}\Omega) &= 2V_T \ln(I_{C1}/I_S) \\I_{C1} = I_{C2} &= \boxed{1.035 \text{ mA}} \\V_{BE1} = V_{BE2} &= \boxed{733 \text{ mV}} \\V_{CE2} = V_{BE2} &= \boxed{733 \text{ mV}} \\V_{CE1} &= V_{CC} - I_C(1 \text{ k}\Omega) - V_{CE2} \\&= \boxed{733 \text{ mV}}\end{aligned}$$

Both  $Q_1$  and  $Q_2$  are at the edge of saturation.

(c)

$$\begin{aligned}V_{CC} - I_B(100 \text{ k}\Omega) &= V_{BE} + 0.5 \text{ V} \\V_{CC} - \frac{1}{\beta}I_C(100 \text{ k}\Omega) &= V_T \ln(I_C/I_S) + 0.5 \text{ V} \\I_C &= \boxed{1.262 \text{ mA}} \\V_{BE} &= \boxed{738 \text{ mV}} \\V_{CE} &= V_{CC} - I_C(1 \text{ k}\Omega) - 0.5 \text{ V} \\&= \boxed{738 \text{ mV}}\end{aligned}$$

$Q_1$  is operating at the edge of saturation.


5.8 See Problem 7 for the derivation of  $I_C$  for each part of this problem.

(a)

$$I_{C1} = 1.754 \text{ mA}$$

$$g_{m1} = I_{C1}/V_T = \boxed{67.5 \text{ mS}}$$
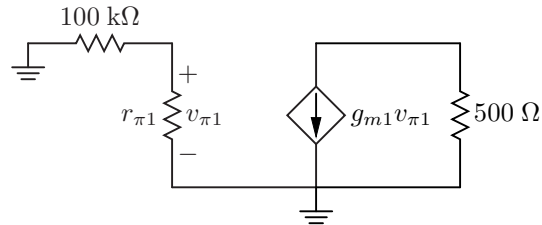
$$r_{\pi 1} = \beta/g_{m1} = \boxed{1.482 \text{ k}\Omega}$$




(b)

$$I_{C1} = I_{C2} = 1.034 \text{ mA}$$

$$g_{m1} = g_{m2} = I_{C1}/V_T = \boxed{39.8 \text{ mS}}$$
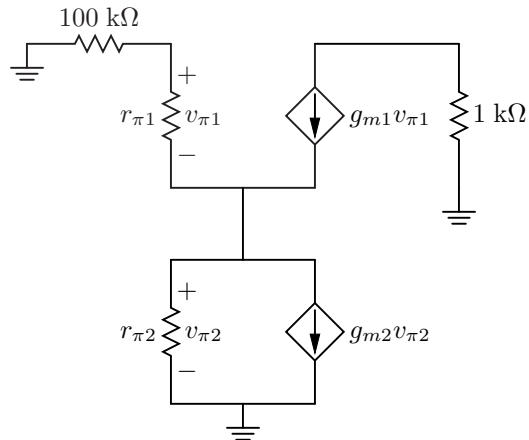
$$r_{\pi 1} = r_{\pi 2} = \beta/g_{m1} = \boxed{2.515 \text{ k}\Omega}$$




(c)

$$I_{C1} = 1.26 \text{ mA}$$

$$g_{m1} = I_{C1}/V_T = \boxed{48.5 \text{ mS}}$$
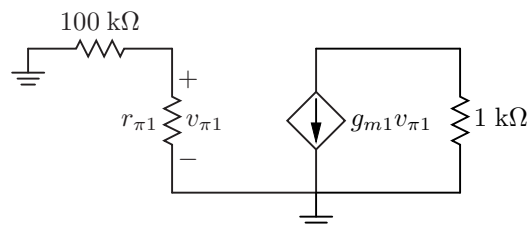
$$r_{\pi 1} = \beta/g_{m1} = \boxed{2.063 \text{ k}\Omega}$$



5.9 (a)

$$\frac{V_{CC} - V_{BE}}{34 \text{ k}\Omega} - \frac{V_{BE}}{16 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$I_C = \beta \frac{V_{CC} - V_T \ln(I_C/I_S)}{34 \text{ k}\Omega} - \beta \frac{V_T \ln(I_C/I_S)}{16 \text{ k}\Omega}$$

$$I_C = \boxed{677 \text{ }\mu\text{A}}$$

$$V_{BE} = \boxed{726 \text{ mV}}$$

$$V_{CE} = V_{CC} - I_C(3 \text{ k}\Omega) = \boxed{468 \text{ mV}}$$

$Q_1$  is in soft saturation.

(b)

$$I_{E1} = I_{E2}$$

$$\Rightarrow I_{C1} = I_{C2}$$

$$\Rightarrow V_{BE1} = V_{BE2} = V_{BE}$$

$$\frac{V_{CC} - 2V_{BE}}{9 \text{ k}\Omega} - \frac{2V_{BE}}{16 \text{ k}\Omega} = I_{B1} = \frac{I_{C1}}{\beta}$$

$$I_{C1} = \beta \frac{V_{CC} - 2V_T \ln(I_{C1}/I_S)}{9 \text{ k}\Omega} - \beta \frac{2V_T \ln(I_{C1}/I_S)}{16 \text{ k}\Omega}$$

$$I_{C1} = I_{C2} = \boxed{1.72 \text{ mA}}$$

$$V_{BE1} = V_{BE2} = V_{CE2} = \boxed{751 \text{ mV}}$$

$$V_{CE1} = V_{CC} - I_{C1}(500 \text{ }\Omega) - V_{CE2} = \boxed{890 \text{ mV}}$$

$Q_1$  is in forward active and  $Q_2$  is on the edge of saturation.

(c)

$$\frac{V_{CC} - V_{BE} - 0.5 \text{ V}}{12 \text{ k}\Omega} - \frac{V_{BE} + 0.5 \text{ V}}{13 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$I_C = \beta \frac{V_{CC} - V_T \ln(I_C/I_S) - 0.5 \text{ V}}{12 \text{ k}\Omega} - \beta \frac{V_T \ln(I_C/I_S) + 0.5 \text{ V}}{13 \text{ k}\Omega}$$

$$I_C = \boxed{1.01 \text{ mA}}$$

$$V_{BE} = \boxed{737 \text{ mV}}$$

$$V_{CE} = V_{CC} - I_C(1 \text{ k}\Omega) - 0.5 \text{ V} = \boxed{987 \text{ mV}}$$

$Q_1$  is in forward active.


5.10 See Problem 9 for the derivation of  $I_C$  for each part of this problem.

(a)

$$I_C = 677 \mu\text{A}$$

$$g_m = I_C/V_T = \boxed{26.0 \text{ mS}}$$
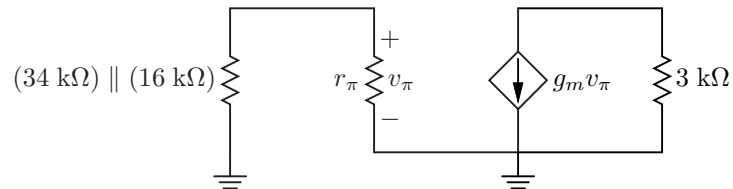
$$r_\pi = \beta/g_m = \boxed{3.84 \text{ k}\Omega}$$




(b)

$$I_{C1} = I_{C2} = 1.72 \text{ mA}$$

$$g_{m1} = g_{m2} = I_{C1}/V_T = \boxed{66.2 \text{ mS}}$$
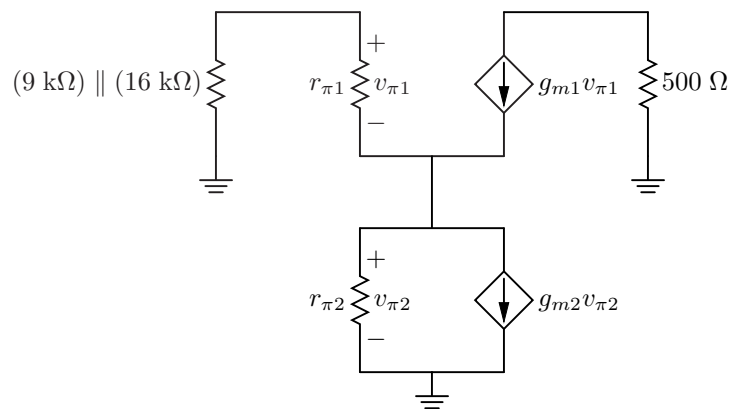
$$r_{\pi1} = r_{\pi2} = \beta/g_{m1} = \boxed{1.51 \text{ k}\Omega}$$




(c)

$$I_C = 1.01 \text{ mA}$$

$$g_m = I_C/V_T = \boxed{38.8 \text{ mS}}$$
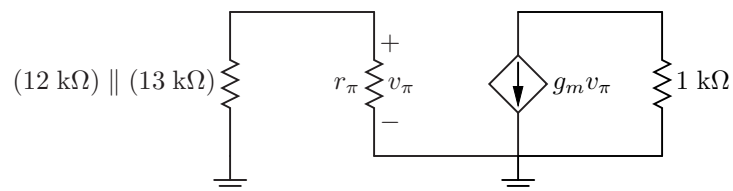
$$r_\pi = \beta/g_m = \boxed{2.57 \text{ k}\Omega}$$



5.11 (a)

$$V_{CE} \geq V_{BE} \text{ (in order to guarantee operation in the active mode)}$$

$$V_{CC} - I_C(2 \text{ k}\Omega) \geq V_{BE}$$

$$V_{CC} - I_C(2 \text{ k}\Omega) \geq V_T \ln(I_C/I_S)$$

$$I_C \leq 886 \text{ }\mu\text{A}$$

$$\frac{V_{CC} - V_{BE}}{R_B} - \frac{V_{BE}}{3 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$\frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \frac{V_T \ln(I_C/I_S)}{3 \text{ k}\Omega} = \frac{I_C}{\beta}$$

$$R_B \left( \frac{I_C}{\beta} + \frac{V_T \ln(I_C/I_S)}{3 \text{ k}\Omega} \right) = V_{CC} - V_T \ln(I_C/I_S)$$

$$R_B = \frac{V_{CC} - V_T \ln(I_C/I_S)}{\frac{I_C}{\beta} + \frac{V_T \ln(I_C/I_S)}{3 \text{ k}\Omega}}$$

$$R_B \geq \boxed{7.04 \text{ k}\Omega}$$

(b)

$$\frac{V_{CC} - V_{BE}}{R_B} - \frac{V_{BE}}{3 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$I_C = \beta \frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \beta \frac{V_T \ln(I_C/I_S)}{3 \text{ k}\Omega}$$



$$I_C = 1.14 \text{ mA}$$

$$V_{BE} = 735 \text{ mV}$$

$$V_{CE} = V_{CC} - I_C(2 \text{ k}\Omega) = 215 \text{ mV}$$
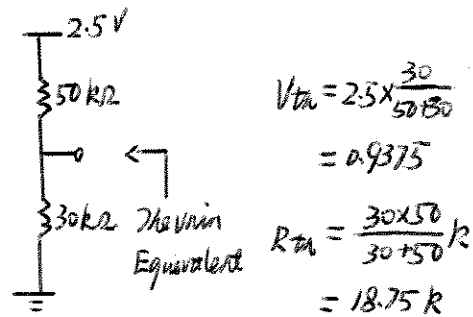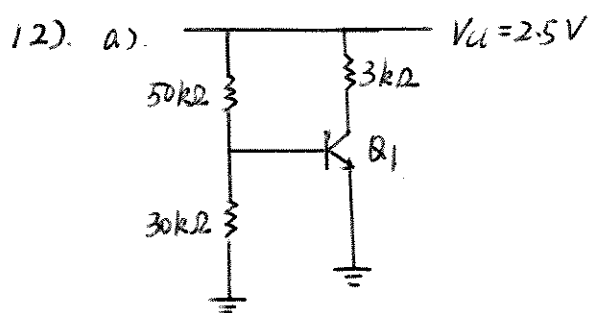
$$V_{BC} = V_{BE} - V_{CE} = \boxed{520 \text{ mV}}$$





Since  $I_C = 0.5 \text{ mA}$ ,  $I_B = \frac{I_C}{\beta} = 0.005 \text{ mA}$ .

$$I_B = \frac{V_{th} - V_{BE}}{R_{th}} \Rightarrow V_{BE} = V_{th} - I_B \cdot R_{th} = 0.84375$$

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)} \Rightarrow I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = 4.03 \times 10^{-15} \text{ (mA)}$$

b). At the edge of saturation means  $V_{BE} - V_{CE} = 0$ .

(soft saturation not allowed)

$$V_{CE} = 2.5 - I_C \cdot (3k), \text{ in which } I_C = \beta I_B = \beta \left( \frac{V_{th} - V_{BE}}{R_{th}} \right)$$

$$\text{SO } V_{BE} = 2.5 - \beta \left( \frac{V_{th} - V_{BE}}{R_{th}} \right) \cdot (3k)$$

Solve this equation:

$$V_{BE} = 0.83.$$

$$I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = \frac{\beta \left( \frac{V_{th} - V_{BE}}{R_{th}} \right)}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = 7.84 \times 10^{-15} \text{ (mA)}$$

5.13 We know the input resistance is  $R_{in} = R_1 \parallel R_2 \parallel r_\pi$ . Since we want the minimum values of  $R_1$  and  $R_2$  such that  $R_{in} > 10 \text{ k}\Omega$ , we should pick the maximum value allowable for  $r_\pi$ , which means picking the minimum value allowable for  $g_m$  (since  $r_\pi \propto 1/g_m$ ), which is  $g_m = 1/260 \text{ S}$ .

$$g_m = \frac{1}{260} \text{ S}$$

$$I_C = g_m V_T = 100 \text{ }\mu\text{A}$$

$$V_{BE} = V_T \ln(I_C/I_S) = 760 \text{ mV}$$

$$I_B = \frac{I_C}{\beta} = 1 \text{ }\mu\text{A}$$

$$\frac{V_{CC} - V_{BE}}{R_1} - \frac{V_{BE}}{R_2} = I_B$$

$$R_1 = \frac{V_{CC} - V_{BE}}{I_B + \frac{V_{BE}}{R_2}}$$

$$r_\pi = \frac{\beta}{g_m} = 26 \text{ k}\Omega$$

$$R_{in} = R_1 \parallel R_2 \parallel r_\pi$$

$$= \left( \frac{V_{CC} - V_{BE}}{I_B + \frac{V_{BE}}{R_2}} \right) \parallel R_2 \parallel r_\pi$$

$$> 10 \text{ k}\Omega$$

$$R_2 > \boxed{23.57 \text{ k}\Omega}$$

$$R_1 > \boxed{52.32 \text{ k}\Omega}$$

5.14

$$\begin{aligned}g_m &= \frac{I_C}{V_T} \geq \frac{1}{26} \text{ S} \\r_\pi &= \frac{\beta}{g_m} = 2.6 \text{ k}\Omega \\R_{in} &= R_1 \parallel R_2 \parallel r_\pi \\&\leq r_\pi\end{aligned}$$

According to the above analysis,  $R_{in}$  cannot be greater than 2.6 k $\Omega$ . This means that the requirement that  $R_{in} \geq 10 \text{ k}\Omega$  cannot be met. Qualitatively, the requirement for  $g_m$  to be large forces  $r_\pi$  to be small, and since  $R_{in}$  is bounded by  $r_\pi$ , it puts an upper bound on  $R_{in}$  that, in this case, is below the required 10 k $\Omega$ .

$$\begin{aligned}
R_{out} &= R_C = R_0 \\
A_v &= -g_m R_C = -g_m R_0 = -\frac{I_C}{V_T} R_0 = -A_0 \\
I_C &= \frac{A_0}{R_0} V_T \\
r_\pi &= \beta \frac{V_T}{I_C} = \beta \frac{R_0}{A_0} \\
V_{BE} &= V_T \ln(I_C/I_S) = V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right) \\
\frac{V_{CC} - V_{BE}}{R_1} - \frac{V_{BE}}{R_2} &= I_B = \frac{I_C}{\beta} \\
R_1 &= \frac{V_{CC} - V_{BE}}{\frac{I_C}{\beta} + \frac{V_{BE}}{R_2}} \\
R_{in} &= R_1 \parallel R_2 \parallel r_\pi \\
&= \left( \frac{V_{CC} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)}{\frac{I_C}{\beta} + \frac{V_T}{R_2} \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)} \right) \parallel R_2 \parallel \beta \frac{R_0}{A_0}
\end{aligned}$$

In order to maximize  $R_{in}$ , we can let  $R_2 \rightarrow \infty$ . This gives us

$$R_{in,max} = \boxed{\left( \frac{V_{CC} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)}{\beta \frac{I_C}{\beta}} \right) \parallel \beta \frac{R_0}{A_0}}$$

5.16 (a)

$$\begin{aligned}
 I_C &= 0.25 \text{ mA} \\
 V_{BE} &= 696 \text{ mV} \\
 \frac{V_{CC} - V_{BE} - I_E R_E}{R_1} - \frac{V_{BE} + I_E R_E}{R_2} &= I_B = \frac{I_C}{\beta} \\
 R_1 &= \frac{V_{CC} - V_{BE} - \frac{1+\beta}{\beta} I_C R_E}{\frac{I_C}{\beta} + \frac{V_{BE} + \frac{1+\beta}{\beta} I_C R_E}{R_2}} \\
 &= \boxed{22.74 \text{ k}\Omega}
 \end{aligned}$$

(b) First, consider a 5 % increase in  $R_E$ .

$$\begin{aligned}
 R_E &= 210 \Omega \\
 \frac{V_{CC} - V_{BE} - I_E R_E}{R_1} - \frac{V_{BE} + I_E R_E}{R_2} &= I_B = \frac{I_C}{\beta} \\
 \frac{V_{CC} - V_T \ln(I_C/I_S) - \frac{1+\beta}{\beta} I_C R_E}{R_1} - \frac{V_T \ln(I_C/I_S) + \frac{1+\beta}{\beta} I_C R_E}{R_2} &= I_B = \frac{I_C}{\beta} \\
 I_C &= 243 \mu\text{A} \\
 \frac{I_C - I_{C,nom}}{I_{C,nom}} \times 100 &= \boxed{-2.6 \%}
 \end{aligned}$$

Now, consider a 5 % decrease in  $R_E$ .

$$\begin{aligned}
 R_E &= 190 \Omega \\
 I_C &= 257 \mu\text{A} \\
 \frac{I_C - I_{C,nom}}{I_{C,nom}} \times 100 &= \boxed{+2.8 \%}
 \end{aligned}$$

5.17

$$V_{CE} \geq V_{BE} \text{ (in order to guarantee operation in the active mode)}$$

$$V_{CC} - I_C R_C \geq V_T \ln(I_C/I_S)$$

$$I_C \leq 833 \mu\text{A}$$

$$\frac{V_{CC} - V_{BE} - I_E R_E}{30 \text{ k}\Omega} - \frac{V_{BE} + I_E R_E}{R_2} = I_B = \frac{I_C}{\beta}$$

$$R_2 = \frac{V_{BE} + I_E R_E}{\frac{V_{CC} - V_{BE} - I_E R_E}{30 \text{ k}\Omega} - \frac{I_C}{\beta}}$$
$$= \frac{V_T \ln(I_C/I_S) + \frac{1+\beta}{\beta} I_C R_E}{\frac{V_{CC} - V_T \ln(I_C/I_S) - \frac{1+\beta}{\beta} I_C R_E}{30 \text{ k}\Omega} - \frac{I_C}{\beta}}$$

$$R_2 \leq \boxed{20.66 \text{ k}\Omega}$$

5.18 (a) First, note that  $V_{BE1} = V_{BE2} = V_{BE}$ , but since  $I_{S1} = 2I_{S2}$ ,  $I_{C1} = 2I_{C2}$ . Also note that  $\beta_1 = \beta_2 = \beta = 100$ .


$$I_{B1} = \frac{I_{C1}}{\beta} = \frac{V_{CC} - V_{BE} - (I_{E1} + I_{E2})R_E}{R_1} - \frac{V_{BE} + (I_{E1} + I_{E2})R_E}{R_2}$$

$$I_{C1} = \beta \frac{V_{CC} - V_T \ln(I_{C1}/I_{S1}) - \frac{3}{2} \frac{1+\beta}{\beta} I_{C1} R_E}{R_1} - \frac{V_T \ln(I_{C1}/I_{S1}) + \frac{3}{2} \frac{1+\beta}{\beta} I_{C1} R_E}{R_2}$$


$$I_{C1} = \boxed{707 \mu\text{A}}$$

$$I_{C2} = \frac{I_{C1}}{2} = \boxed{354 \mu\text{A}}$$

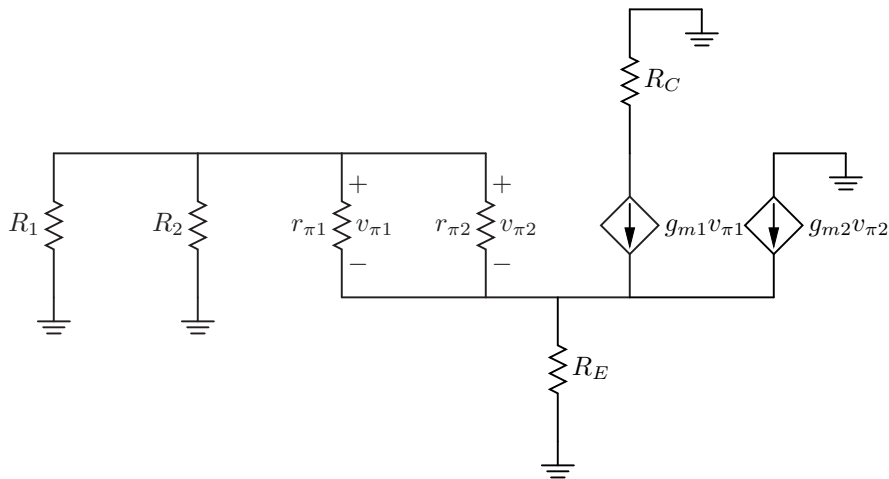(b) The small-signal model is shown below.



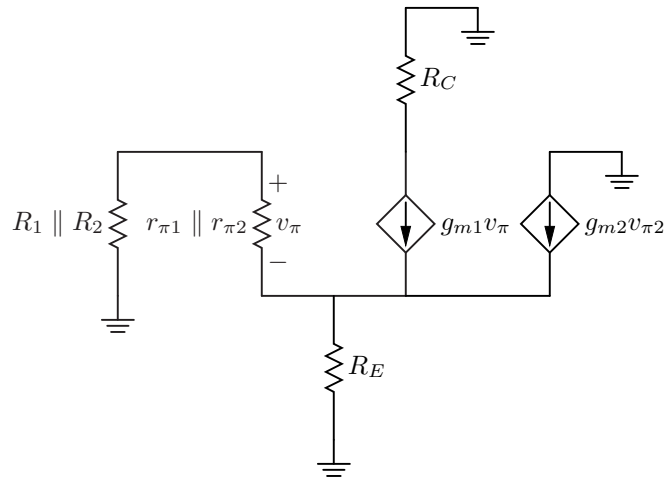We can simplify the small-signal model as follows:



$$g_{m1} = I_{C1}/V_T = \boxed{27.2 \text{ mS}}$$

$$r_{\pi1} = \beta_1/g_{m1} = \boxed{3.677 \text{ k}\Omega}$$

$$g_{m2} = I_{C2}/V_T = \boxed{13.6 \text{ mS}}$$

$$r_{\pi2} = \beta_2/g_{m2} = \boxed{7.355 \text{ k}\Omega}$$



5.19 (a)

$$I_{E1} = I_{E2} \Rightarrow V_{BE1} = V_{BE2}$$

$$\frac{V_{CC} - 2V_{BE1}}{9 \text{ k}\Omega} - \frac{2V_{BE1}}{16 \text{ k}\Omega} = I_{B1} = \frac{I_{C1}}{\beta_1}$$

$$I_{C1} = \beta_1 \frac{V_{CC} - 2V_T \ln(I_{C1}/I_{S1})}{9 \text{ k}\Omega} - \beta_1 \frac{2V_T \ln(I_{C1}/I_{S1})}{16 \text{ k}\Omega}$$


$$I_{C1} = I_{C2} = \boxed{1.588 \text{ mA}}$$

$$V_{BE1} = V_{BE2} = V_T \ln(I_{C1}/I_{S1}) = \boxed{754 \text{ mV}}$$

$$V_{CE2} = V_{BE2} = \boxed{754 \text{ mV}}$$

$$V_{CE1} = V_{CC} - I_{C1}(100 \Omega) - V_{CE2} = \boxed{1.587 \text{ V}}$$

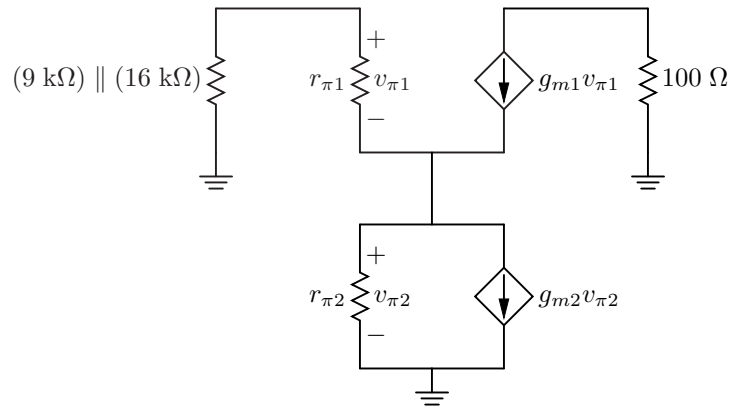
(b) The small-signal model is shown below.



$$g_{m1} = g_{m2} = \frac{I_{C1}}{V_T} = \boxed{61.1 \text{ mS}}$$

$$r_{\pi 1} = r_{\pi 2} = \frac{\beta_1}{g_{m1}} = \boxed{1.637 \text{ k}\Omega}$$

20)

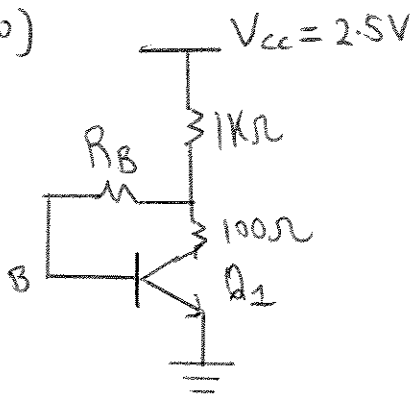

$$I_C = 1\text{mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.750\text{V}$$

$$V_B = 2.5 - (I_E (1k\Omega) + I_B R_B) = 0.750\text{V}$$

$$I_E = 1.01\text{mA}$$


$$I_B = 0.01\text{mA}$$

$$V_B = 2.5 - 1.01 - 0.01 R_B = 0.750$$

$$0.74 = 0.01 R_B$$

$$R_B = 74k\Omega$$

21)

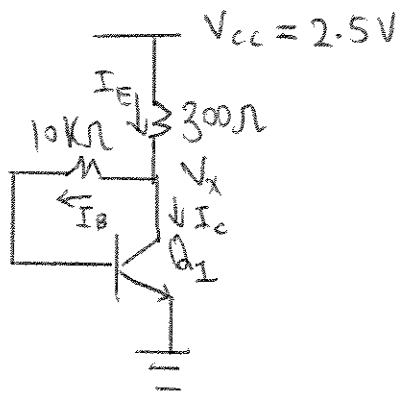

$$V_X = 1.1V$$

$$\beta = 100$$

$$I_S = ?$$

$$I_E = I_B + I_C$$

$$I_E = \frac{2.5 - 1.1}{300\Omega} = 4.67 \text{ mA}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_E = \frac{I_C}{\beta} + I_C = 4.67 \text{ mA}$$

$$I_C = 4.624 \text{ mA}$$

$$I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}}, \quad V_{BE} = 1.1 - \frac{4.624(10K)}{100} = 0.6376V$$

$$I_S = 1.035 \times 10^{-10} \text{ mA}$$

$$I_S = 1.035 \times 10^{-13} \text{ A}$$

5.22

$$\begin{aligned}V_{CC} - I_E(500 \Omega) - I_B(20 \text{ k}\Omega) - I_E(400 \Omega) &= V_{BE} \\V_{CC} - \frac{1+\beta}{\beta}I_C(500 \Omega + 400 \Omega) - \frac{1}{\beta}I_C(20 \text{ k}\Omega) &= V_T \ln(I_C/I_S) \\I_C &= \boxed{1.584 \text{ mA}} \\V_{BE} = V_T \ln(I_C/I_S) &= \boxed{754 \text{ mV}} \\V_{CE} = V_{CC} - I_E(500 \Omega) - I_E(400 \Omega) \\&= V_{CC} - \frac{1+\beta}{\beta}I_C(500 \Omega + 400 \Omega) = \boxed{1.060 \text{ V}}\end{aligned}$$

$Q_1$  is operating in forward active.

$$V_{BC} \leq 200 \text{ mV}$$

$$V_{CC} - I_E(1 \text{ k}\Omega) - I_B R_B - (V_{CC} - I_E(1 \text{ k}\Omega) - I_C(500 \text{ }\Omega)) \leq 200 \text{ mV}$$

$$I_C(500 \text{ }\Omega) - I_B R_B \leq 200 \text{ mV}$$

$$I_B R_B \geq I_C(500 \text{ }\Omega) - 200 \text{ mV}$$

$$V_{CC} - I_E(1 \text{ k}\Omega) - I_B R_B = V_{BE} = V_T \ln(I_C/I_S)$$


$$V_{CC} - \frac{1+\beta}{\beta} I_C(1 \text{ k}\Omega) - I_C(500 \text{ }\Omega) + 200 \text{ mV} \leq V_T \ln(I_C/I_S)$$

$$I_C \geq 1.29 \text{ mA}$$

$$R_B \geq \frac{I_C(500 \text{ }\Omega) - 200 \text{ mV}}{\frac{I_C}{\beta}}$$

$$\geq \boxed{34.46 \text{ k}\Omega}$$

24). a).

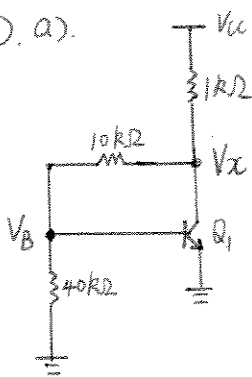

$$I_S = 8 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = \infty$$

$$V_C = 2.5 - \left( \frac{I_C}{\alpha} + \frac{V_B}{40k} \right) \cdot 1k$$

$$V_C = \left( \frac{V_B}{40k} + 2I_B \right) 10k + V_B = \left( \frac{V_B}{40k} + \frac{I_C}{\beta} \right) 10k + V_B$$

$$\text{Equating } V_C \Rightarrow 2.5 - \left( V_B + \frac{V_B \cdot 1k}{40k} + \frac{V_B \cdot 10k}{40k} \right) = \frac{I_C}{\alpha} \cdot 1k + \frac{I_C}{\beta} \cdot 10k.$$

$$\Rightarrow I_C = \frac{2.5 - 1.275V_B}{\frac{1k}{\alpha} + \frac{10k}{\beta}}$$

Guess  $V_B = 0.8$

$$I_C = \frac{1.48}{\frac{1k}{0.99} + \frac{10k}{100}} = 1.33 \text{ mA}$$

Then

$$V_B = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.732, \text{ not } 0.8.$$

Reiterate

$$I_C = \frac{1.5667}{1.11} = 1.4113 \text{ mA}$$

$$V_B = V_T \ln \left( \frac{I_C}{I_S} \right) = 0.733$$

So  $V_B$  converges to 0.73V


$$I_C = 1.41 \text{ mA}$$

$$I_B = 14.1 \mu\text{A}$$

$$V_{CE} = 2.5 \text{ V} - \left( \frac{1.41}{0.99} + \frac{0.73}{40} \right) \times 1 \text{ V} = 1.06 \text{ V}.$$

$$V_{BE} = 0.73 \text{ V}$$

24 b) Small Signal

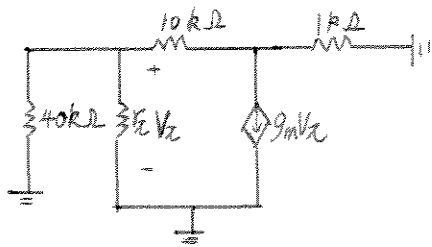


$$g_m = \frac{I_C}{V_T} = 0.054 \text{ S}$$

$$r_c = \frac{\beta}{g_m} = 1844 \Omega$$

5.25 (a)

$$\begin{aligned}
 I_{C1} &= 1 \text{ mA} \\
 V_{CC} - (I_{E1} + I_{E2})(500 \Omega) &= V_T \ln(I_{C2}/I_{S2}) \\
 V_{CC} - \left( \frac{1+\beta}{\beta} I_{C1} + \frac{1+\beta}{\beta} I_{C2} \right) (500 \Omega) &= V_T \ln(I_{C2}/I_{S2}) \\
 I_{C2} &= 2.42 \text{ mA} \\
 V_B - (I_{E1} + I_{E2})(500 \Omega) &= V_T \ln(I_{C1}/I_{S1}) \\
 V_B - \left( \frac{1+\beta}{\beta} I_{C1} + \frac{1+\beta}{\beta} I_{C2} \right) (500 \Omega) &= V_T \ln(I_{C1}/I_{S1}) \\
 V_B &= \boxed{2.68 \text{ V}}
 \end{aligned}$$

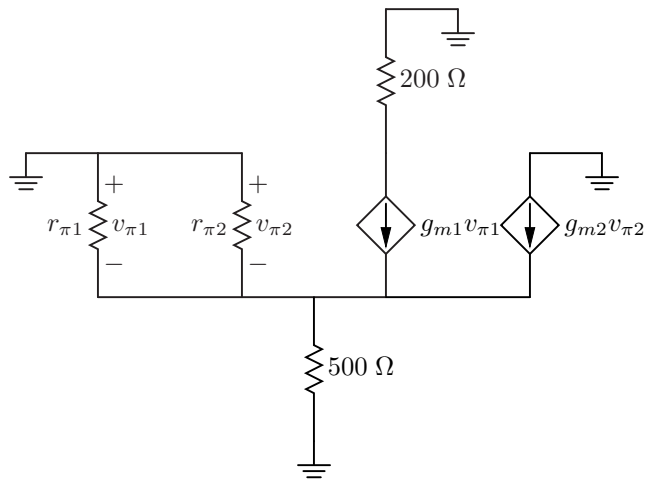(b) The small-signal model is shown below.



$$\begin{aligned}
 g_{m1} &= I_{C1}/V_T = \boxed{38.5 \text{ mS}} \\
 r_{\pi 1} &= \beta_1/g_{m1} = \boxed{2.6 \text{ k}\Omega} \\
 g_{m2} &= I_{C2}/V_T = \boxed{93.1 \text{ mS}} \\
 r_{\pi 2} &= \beta_2/g_{m2} = \boxed{1.074 \text{ k}\Omega}
 \end{aligned}$$



5.26 (a)

$$\begin{aligned}
 V_{CC} - I_B(60 \text{ k}\Omega) &= V_{EB} \\
 V_{CC} - \frac{1}{\beta_{pnp}} I_C(60 \text{ k}\Omega) &= V_T \ln(I_C/I_S) \\
 I_C &= \boxed{1.474 \text{ mA}} \\
 V_{EB} &= V_T \ln(I_C/I_S) = \boxed{731 \text{ mV}} \\
 V_{EC} &= V_{CC} - I_C(200 \Omega) = \boxed{2.205 \text{ V}}
 \end{aligned}$$

$Q_1$  is operating in forward active.


(b)

$$\begin{aligned}
 V_{CC} - V_{BE1} - I_{B2}(80 \text{ k}\Omega) &= V_{EB2} \\
 V_{CC} - V_T \ln(I_{C1}/I_S) - I_{B2}(80 \text{ k}\Omega) &= V_T \ln(I_{C2}/I_S) \\
 I_{C1} &= \frac{\beta_{npn}}{1 + \beta_{npn}} I_{E1} \\
 &= \frac{\beta_{npn}}{1 + \beta_{npn}} I_{E2} \\
 &= \frac{\beta_{npn}}{1 + \beta_{npn}} \cdot \frac{1 + \beta_{pnp}}{\beta_{pnp}} I_{C2} \\
 V_{CC} - V_T \ln\left(\frac{\beta_{npn}}{1 + \beta_{npn}} \cdot \frac{1 + \beta_{pnp}}{\beta_{pnp}} \cdot \frac{I_{C2}}{I_S}\right) - \frac{1}{\beta_{pnp}} I_{C2}(80 \text{ k}\Omega) &= V_T \ln(I_{C2}/I_S) \\
 I_{C2} &= \boxed{674 \mu\text{A}} \\
 V_{BE2} &= V_T \ln(I_{C2}/I_S) = \boxed{711 \text{ mV}} \\
 I_{C1} &= \boxed{680 \mu\text{A}} \\
 V_{BE1} &= V_T \ln(I_{C1}/I_S) = \boxed{711 \text{ mV}} \\
 V_{CE1} &= V_{BE1} = \boxed{711 \text{ mV}} \\
 V_{CE2} &= V_{CC} - V_{CE1} - I_{C2}(300 \Omega) \\
 &= \boxed{1.585 \text{ V}}
 \end{aligned}$$

$Q_1$  is operating on the edge of saturation.  $Q_2$  is operating in forward active.

5.27 See Problem 26 for the derivation of  $I_C$  for each part of this problem.

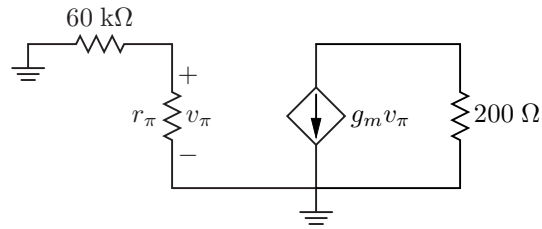(a) The small-signal model is shown below.




$$I_C = 1.474 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \boxed{56.7 \text{ mS}}$$

$$r_\pi = \frac{\beta}{g_m} = \boxed{1.764 \text{ k}\Omega}$$

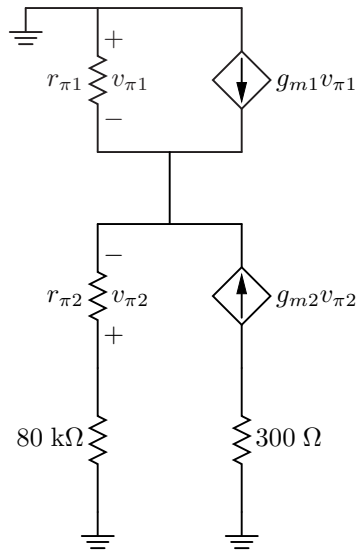(b) The small-signal model is shown below.



$$I_{C1} = 680 \text{ }\mu\text{A}$$

$$g_{m1} = \frac{I_{C1}}{V_T} = \boxed{26.2 \text{ mS}}$$


$$r_{\pi1} = \frac{\beta_{npn}}{g_{m1}} = \boxed{3.824 \text{ k}\Omega}$$

$$I_{C2} = 674 \text{ }\mu\text{A}$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \boxed{25.9 \text{ mS}}$$

$$r_{\pi2} = \frac{\beta_{pnp}}{g_{m2}} = \boxed{1.929 \text{ k}\Omega}$$

28)

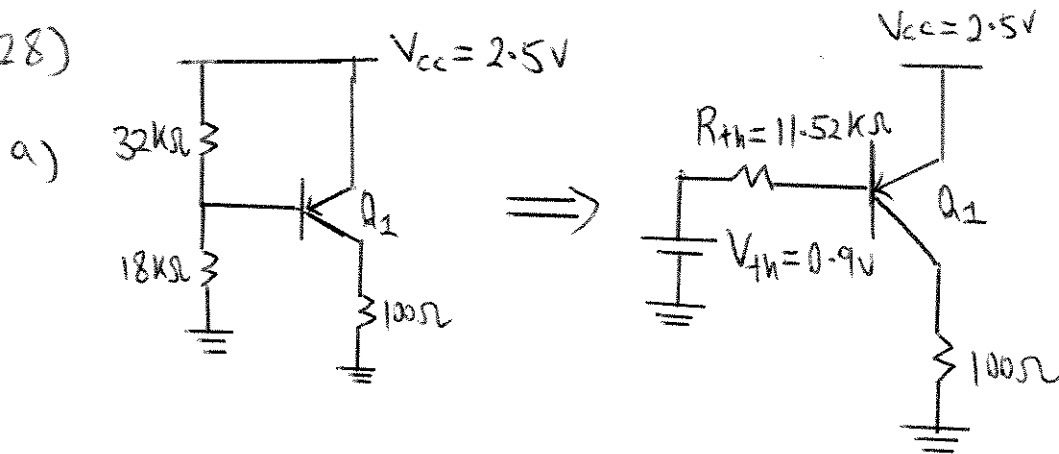

$$I_c = \beta_{npn} \left( \frac{2.5 - |V_{BE}| - V_{th}}{R_{th}} \right)$$

Guess  $|V_{BE}| = 0.7V$ ,  $I_c = 3.91mA$

$$|V_{BE}| = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.757V$$

Reiterate,  $|V_{BE}| = 0.757V$ ,  $I_c = 3.66mA$

$$|V_{BE}| = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.755V$$

Reiterate,  $|V_{BE}| = 0.755V$ ,  $I_c = 3.67mA$

$$|V_{BE}| = V_T \ln \left( \frac{I_c}{I_s} \right) = 0.755V, \text{ converged!!}$$

$$V_c = (3.67mA)(0.1k\Omega) = 0.367V, \quad V_B = 2.5 - 0.755 = 1.745V$$


$Q_1$  in forward active.

Bias point:

$$I_c = 3.67mA \quad |V_{BE}| = 0.755$$

$$I_B = 73.4\mu A \quad |V_{CE}| = 2.5 - 0.367 = 2.133V$$

28)  
b)

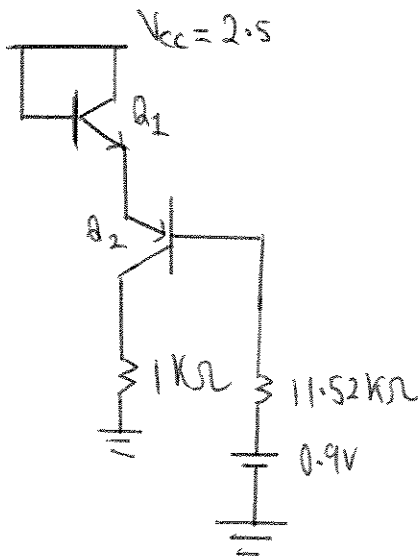

$$I_{c2} = \frac{(2.5 - (V_{BE1} + V_{BE2}) - 0.9)}{11.52 \text{ k}} \cdot 50$$

$$I_{c1} = I_{c2} (1.00997)$$

(From  $\beta$  relation)

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right)$$

$$|V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right)$$

Guess,  $V_{BE1} = V_{BE2} = 0.7 \text{ V}$

$$I_{c2} = 0.868 \text{ mA}, \quad I_{c1} = 0.877 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right) = 0.718 \text{ V}, \quad |V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right) = 0.717 \text{ V}$$

Reiterate,  $V_{BE1} = 0.718 \text{ V}, \quad |V_{BE2}| = 0.717 \text{ V}$

$$I_{c2} = 0.716 \text{ mA}, \quad I_{c1} = 0.723 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right) = 0.713 \text{ V}, \quad |V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right) = 0.712 \text{ V}$$

Reiterate,  $V_{BE1} = 0.713 \text{ V}, \quad |V_{BE2}| = 0.712 \text{ V}$

$$I_{c2} = 0.760 \text{ mA}, \quad I_{c1} = 0.767 \text{ mA}$$

$$V_{BE1} = 0.714 \text{ V}, \quad |V_{BE2}| = 0.714 \text{ V}$$

28)

b)

$$\text{Reiterate, } V_{BE1} = 0.714 \text{ V, } |V_{BE2}| = 0.714 \text{ V}$$

$$I_{C2} = 0.747 \text{ mA, } I_{C1} = 0.754 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.714 \text{ V,}$$

$$|V_{BE2}| = 0.714 \text{ V}$$

$$V_{B2} = \frac{(0.747 \text{ mA})(11.52 \text{ k}\Omega) + 0.9}{50} = 1.07 \text{ V}$$

$$V_{C2} = (0.747 \text{ mA})(1 \text{ k}\Omega) = 0.747 \text{ V}$$

Q<sub>2</sub> is in forward-active region. Q<sub>1</sub> is always in forward-active region.

Bias point:

$$V_{BE1} = 0.714 \text{ V}$$

$$I_{C1} = 0.754 \text{ mA}$$

$$I_{B1} = 7.54 \mu\text{A}$$

$$V_{CE1} = 0.714 \text{ V}$$

$$|V_{BE2}| = 0.714 \text{ V}$$


$$I_{C2} = 0.747 \text{ mA}$$

$$I_{B2} = 14.94 \mu\text{A}$$


$$|V_{CE2}| = 2.5 - 0.714 - 0.747 = 1.039 \text{ V}$$

29)

a)

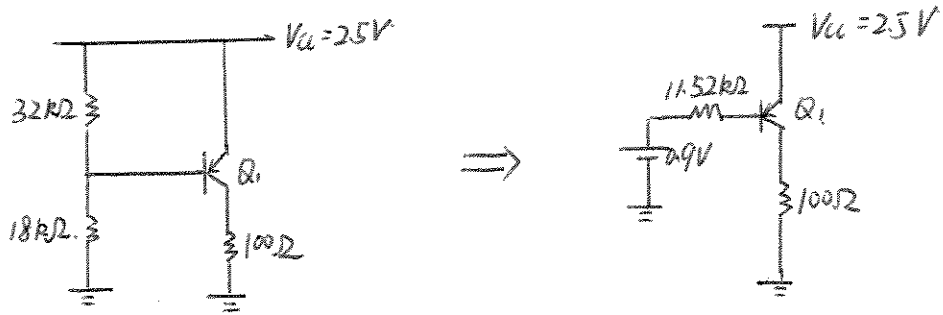


Small Signal:

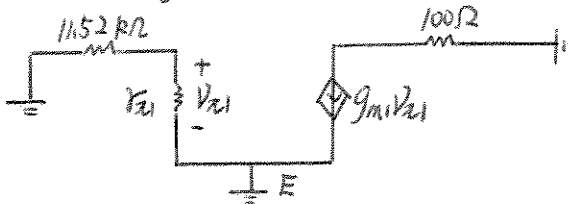

$$g_{m1} = \frac{3.67 \text{ mA}}{26 \text{ mV}} = 0.141 \text{ S}$$

$$r_{21} = \frac{50}{0.141} \Omega = 354.2 \Omega$$

b)

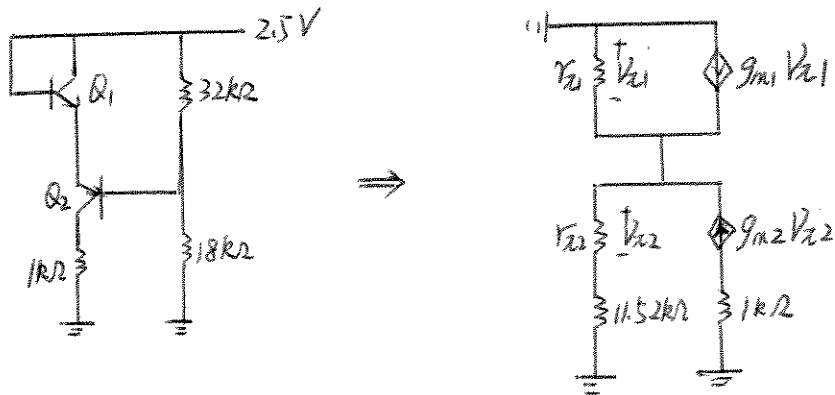

$$g_{m1} = 0.029 \text{ S}$$

$$r_{21} = 3448.3 \Omega$$

$$g_{m2} = 0.0287 \text{ S}$$

$$r_{22} = 17403 \Omega$$

$$V_{CC} - I_C(1 \text{ k}\Omega) = V_{EC} = V_{EB} \text{ (in order for } Q_1 \text{ to operate at the edge of saturation)}$$

$$= V_T \ln(I_C/I_S)$$

$$I_C = 1.761 \text{ mA}$$

$$V_{EB} = 739 \text{ mV}$$

$$\frac{V_{CC} - V_{EB}}{R_B} - \frac{V_{EB}}{5 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$R_B = 9.623 \text{ k}\Omega$$

First, let's consider when  $R_B$  is 5 % larger than its nominal value.

$$R_B = 10.104 \text{ k}\Omega$$

$$\frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \frac{V_T \ln(I_C/I_S)}{5 \text{ k}\Omega} = \frac{I_C}{\beta}$$

$$I_C = 1.411 \text{ mA}$$

$$V_{EB} = 733 \text{ mV}$$

$$V_{EC} = V_{CC} - I_C(1 \text{ k}\Omega) = 1.089 \text{ V}$$

$$V_{CB} = \boxed{-355 \text{ mV}} \text{ (the collector-base junction is reverse biased)}$$

Now, let's consider when  $R_B$  is 5 % smaller than its nominal value.

$$R_B = 9.142 \text{ k}\Omega$$

$$\frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \frac{V_T \ln(I_C/I_S)}{5 \text{ k}\Omega} = \frac{I_C}{\beta}$$

$$I_C = 2.160 \text{ mA}$$

$$V_{EB} = 744 \text{ mV}$$

$$V_{EC} = V_{CC} - I_C(1 \text{ k}\Omega) = 340 \text{ mV}$$

$$V_{CB} = \boxed{405 \text{ mV}} \text{ (the collector-base junction is forward biased)}$$

5.31

$$\frac{V_{BC} + I_C(5 \text{ k}\Omega)}{10 \text{ k}\Omega} - \frac{V_{CC} - V_{BC} - I_C(5 \text{ k}\Omega)}{10 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$V_{BC} = 300 \text{ mV}$$

$$I_C = 194 \text{ }\mu\text{A}$$

$$V_{EB} = V_T \ln(I_C/I_S) = 682 \text{ mV}$$

$$V_{CC} - I_E R_E - I_C(5 \text{ k}\Omega) = V_{EC} = V_{EB} + 300 \text{ mV}$$

$$V_{CC} - \frac{1+\beta}{\beta} I_C R_E - I_C(5 \text{ k}\Omega) = V_{EB} + 300 \text{ mV}$$

$$R_E = \boxed{2.776 \text{ k}\Omega}$$

Let's look at what happens when  $R_E$  is halved.

$$R_E = 1.388 \text{ k}\Omega$$

$$\frac{V_{CC} - I_E R_E - V_{EB}}{10 \text{ k}\Omega} - \frac{V_{CC} - (V_{CC} - I_E R_E - V_{EB})}{10 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$\beta \frac{V_{CC} - \frac{1+\beta}{\beta} I_C R_E - V_T \ln(I_C/I_S)}{10 \text{ k}\Omega} - \beta \frac{V_{CC} - \left( V_{CC} - \frac{1+\beta}{\beta} I_C R_E - V_T \ln(I_C/I_S) \right)}{10 \text{ k}\Omega} = I_C$$

$$I_C = 364 \text{ }\mu\text{A}$$

$$V_{EB} = 698 \text{ }\mu\text{V}$$

$$V_{EC} = 164 \text{ }\mu\text{V}$$

Thus, when  $R_E$  is halved,  $Q_1$  operates in deep saturation.



5.32

$$V_{CC} - I_B(20 \text{ k}\Omega) - I_E(1.6 \text{ k}\Omega) = V_{BE} = V_T \ln(I_C/I_S)$$


$$V_{CC} - \frac{I_C}{\beta}(20 \text{ k}\Omega) - \frac{1+\beta}{\beta}I_C(1.6 \text{ k}\Omega) = V_{BE} = V_T \ln(I_C/I_S)$$

$$I_S = \frac{I_C}{e^{[V_{CC} - \frac{I_C}{\beta}(20 \text{ k}\Omega) - \frac{1+\beta}{\beta}I_C(1.6 \text{ k}\Omega)]/V_T}}$$

$$I_C = 1 \text{ mA}$$

$$I_S = \boxed{3 \times 10^{-14} \text{ A}}$$

33)

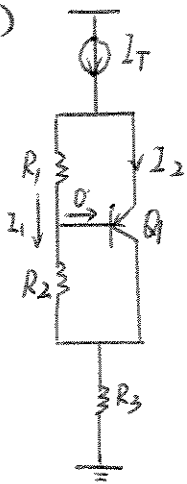

If Base current is neglected,  $I_C = I_E$


$$I_1 = \frac{V_E - V_C}{R_1 + R_2}$$

$$|V_{BE}| = I_1 R_1 = \frac{V_E - V_C}{R_1 + R_2} R_1 = \frac{|V_{CE}|}{R_1 + R_2} R_1$$

$$\text{So } \frac{|V_{CE}|}{|V_{BE}|} = \frac{R_1 + R_2}{R_1}$$

Let  $A = \frac{R_1 + R_2}{R_1}$ ,  $|V_{CE}| = A |V_{BE}|$ , thus  $|V_{BE}|$  is multiplied.

34)

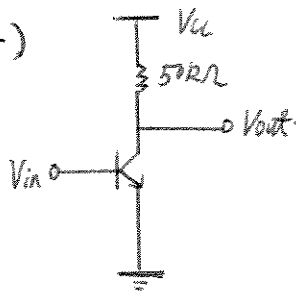

$$A_V = g_m R_C = 20$$


$$\frac{I_C R_C}{V_T} = 20 \Rightarrow I_C = \frac{20 V_T}{R_C}$$

$$I_C = 0.0104 \text{ mA}$$

$$V_{CC} - (50 \text{ k}\Omega) (0.0104 \text{ mA}) = V_{BE}$$

$$\Rightarrow V_{CC} - 50 \times 0.0104 \text{ V} = 0.8 \text{ V}$$

$$\Rightarrow V_{CC} = 1.32 \text{ V}$$

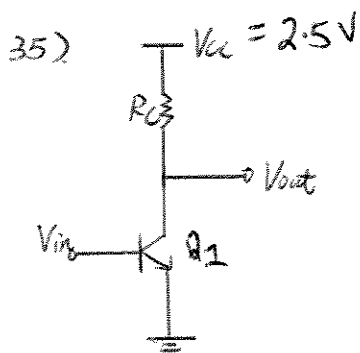

$$V_A = 10V, r_o = \frac{V_A}{I_C}, g_m = \frac{I_C}{V_T}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = g_m (R_C // r_o) = g_m \left( \frac{R_C r_o}{R_C + r_o} \right) = \frac{R_C V_A}{V_T \left( R_C + \frac{V_A}{I_C} \right)}$$

As the equation above shows, a large gain means a large  $I_C$ . However, a large  $I_C$  will drive  $Q_1$  into saturation. So a tradeoff must be made. The maximum limit for  $I_C$  is when it drives  $Q_1$  into the edge of saturation, namely,  $V_{BE} = V_{CE}$ .


$$V_{CE} = V_{CC} - I_C (1K)$$

$$V_{BE} = 0.8V, V_{CC} = 2.5V$$

$$0.8 = 2.5 - I_C 1K$$

$$I_C = 1.7mA$$

36)

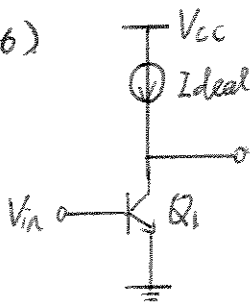


$$A_v = 50$$

$$R_{out} = R_o = 10k\Omega$$

$$A_v = g_m R_{out} = \frac{I_c}{V_T} R_{out} = 50$$

$$I_c = 50 \left( \frac{V_T}{R_{out}} \right) = 0.13mA$$

37).

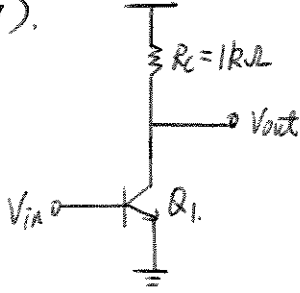

$$I_c = I_s \exp\left(\frac{V_{BE}}{2V_T}\right)$$

$$g_m = \frac{\partial I_c}{\partial V_{BE}} = \frac{I_c}{2V_T}$$

$$R_{out} = R_c$$

$$\left|\frac{V_{out}}{V_{in}}\right| = g_m R_{out} = \frac{I_c R_c}{2V_T} = \frac{(1mA)(1k\Omega)}{(2)(0.026V)} = 19.23$$

5.38 (a)

$$A_v = -g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

(b)

$$A_v = -g_{m1} \left( R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$


(c)

$$A_v = -g_{m1} \left( R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

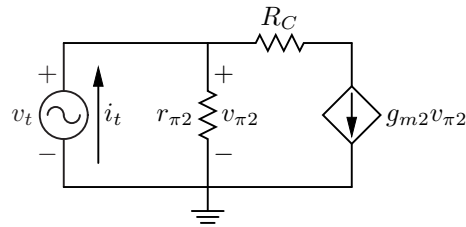(d) Let's determine the equivalent resistance seen looking up from the output by drawing a small-signal model and applying a test source.



$$i_t = \frac{v_{\pi 2}}{r_{\pi 2}} + g_{m2}v_{\pi 2}$$

$$v_{\pi 2} = v_t$$

$$i_t = v_t \left( \frac{1}{r_{\pi 2}} + g_{m2} \right)$$


$$\frac{v_t}{i_t} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$A_v = -g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

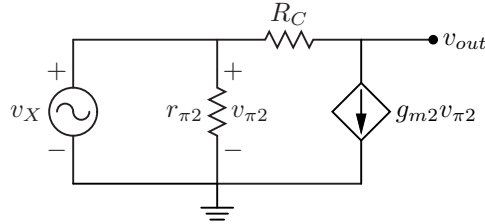- (e) From (d), we know the gain from the input to the collector of  $Q_1$  is  $-g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$ . If we find the gain from the collector of  $Q_1$  to  $v_{out}$ , we can multiply these expressions to find the overall gain. Let's draw the small-signal model to find the gain from the collector of  $Q_1$  to  $v_{out}$ . I'll refer to the collector of  $Q_1$  as node  $X$  in the following derivation.




$$\begin{aligned} \frac{v_X - v_{out}}{R_C} &= g_{m2}v_{\pi 2} \\ v_{\pi 2} &= v_X \\ \frac{v_X - v_{out}}{R_C} &= g_{m2}v_X \\ v_X \left( \frac{1}{R_C} - g_{m2} \right) &= \frac{v_{out}}{R_C} \\ \frac{v_{out}}{v_X} &= 1 - g_{m2}R_C \end{aligned}$$

Thus, we have

$$A_v = \boxed{-g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right) (1 - g_{m2}R_C)}$$

$$R_{in} = \boxed{r_{\pi 1}}$$

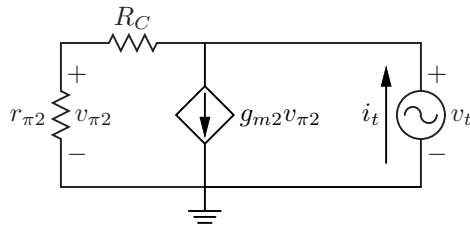To find the output resistance, let's draw the small-signal model and apply a test source at the output. Note that looking into the collector of  $Q_1$  we see infinite resistance, so we can exclude it from the small-signal model.





$$\begin{aligned}
i_t &= g_{m2}v_{\pi2} + \frac{v_{\pi2}}{r_{\pi2}} \\
v_{\pi2} &= \frac{r_{\pi2}}{r_{\pi2} + R_C}v_t \\
i_t &= \left(g_{m2} + \frac{1}{r_{\pi2}}\right) \frac{r_{\pi2}}{r_{\pi2} + R_C}v_t \\
R_{out} &= \frac{v_t}{i_t} \\
&= \boxed{\left(\frac{1}{g_{m2}} \parallel r_{\pi2}\right) \frac{r_{\pi2} + R_C}{r_{\pi2}}}
\end{aligned}$$

5.39 (a)

$$A_v = -g_{m1} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$$

(b)

$$A_v = -g_{m1} \left[ r_{o1} \parallel \left( R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right) \right]$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = r_{o1} \parallel \left( R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$


(c)

$$A_v = -g_{m1} \left[ r_{o1} \parallel \left( R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right) \right]$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = r_{o1} \parallel \left( R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

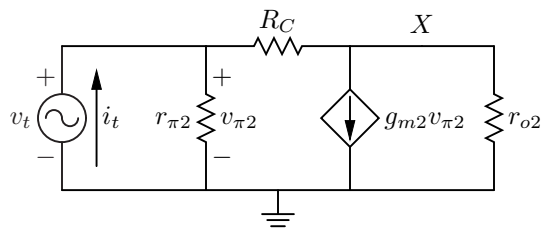(d) Let's determine the equivalent resistance seen looking up from the output by drawing a small-signal model and applying a test source.



$$\begin{aligned}
i_t &= \frac{v_{\pi 2}}{r_{\pi 2}} + \frac{v_t - v_X}{R_C} \\
\frac{v_X - v_t}{R_C} + g_{m2}v_{\pi 2} + \frac{v_X}{r_{o2}} &= 0 \\
v_{\pi 2} &= v_t \\
v_X \left( \frac{1}{R_C} + \frac{1}{r_{o2}} \right) &= v_t \left( \frac{1}{R_C} - g_{m2} \right) \\
v_X &= v_t \left( \frac{1}{R_C} - g_{m2} \right) (r_{o2} \parallel R_C) \\
i_t &= \frac{v_t}{r_{\pi 2}} + \frac{v_t}{R_C} - \frac{1}{R_C} v_t \left( \frac{1}{R_C} - g_{m2} \right) (r_{o2} \parallel R_C) \\
&= v_t \left[ \frac{1}{r_{\pi 2}} + \frac{1}{R_C} - \frac{1}{R_C} \left( \frac{1}{R_C} - g_{m2} \right) (r_{o2} \parallel R_C) \right] \\
&= v_t \left[ \frac{1}{r_{\pi 2}} + \frac{1}{R_C} + \left( g_{m2} - \frac{1}{R_C} \right) \frac{r_{o2}}{r_{o2} + R_C} \right] \\
\frac{v_t}{i_t} &= r_{\pi 2} \parallel R_C \parallel \left[ \frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right]
\end{aligned}$$


$$A_v = -g_{m1} \left( r_{o1} \parallel r_{\pi 2} \parallel R_C \parallel \left[ \frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right] \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = r_{o1} \parallel r_{\pi 2} \parallel R_C \parallel \left[ \frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right]$$

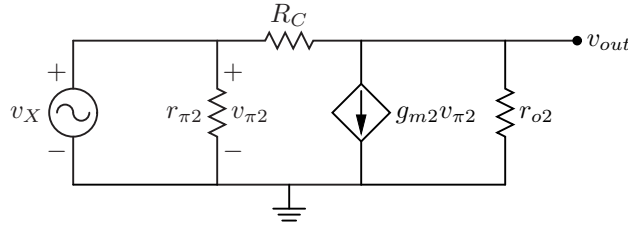(e) From (d), we know the gain from the input to the collector of  $Q_1$  is  $-g_{m1} \left( r_{o1} \parallel r_{\pi 2} \parallel R_C \parallel \left[ \frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right] \right)$ .

If we find the gain from the collector of  $Q_1$  to  $v_{out}$ , we can multiply these expressions to find the overall gain. Let's draw the small-signal model to find the gain from the collector of  $Q_1$  to  $v_{out}$ . I'll refer to the collector of  $Q_1$  as node  $X$  in the following derivation.




$$\begin{aligned} \frac{v_{out} - v_X}{R_C} + g_{m2}v_{\pi 2} + \frac{v_{out}}{r_{o2}} &= 0 \\ v_{\pi 2} &= v_X \\ \frac{v_{out} - v_X}{R_C} + g_{m2}v_X + \frac{v_{out}}{r_{o2}} &= 0 \\ v_{out} \left( \frac{1}{R_C} + \frac{1}{r_{o2}} \right) &= v_X \left( \frac{1}{R_C} - g_{m2} \right) \\ \frac{v_{out}}{v_X} &= \left( \frac{1}{R_C} - g_{m2} \right) (R_C \parallel r_{o2}) \end{aligned}$$

Thus, we have

$$A_v = \boxed{-g_{m1} \left( r_{o1} \parallel r_{\pi 2} \parallel R_C \parallel \left[ \frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right] \right) \left( \frac{1}{R_C} - g_{m2} \right) (R_C \parallel r_{o2})}$$

$$R_{in} = \boxed{r_{\pi 1}}$$

To find the output resistance, let's draw the small-signal model and apply a test source at the output. Note that looking into the collector of  $Q_1$  we see  $r_{o1}$ , so we replace  $Q_1$  in the small-signal model with this equivalent resistance. Also note that  $r_{o2}$  appears from the output to ground, so we can remove it from this analysis and add it in parallel at the end to find  $R_{out}$ .

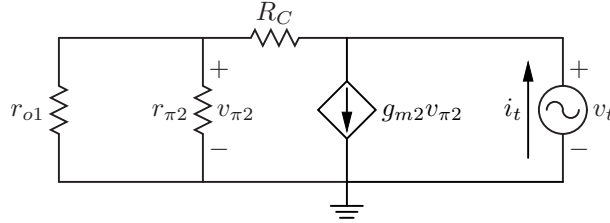

$$\begin{aligned} i_t &= g_{m2}v_{\pi 2} + \frac{v_{\pi 2}}{r_{\pi 2} \parallel r_{o1}} \\ v_{\pi 2} &= \frac{r_{\pi 2} \parallel r_{o1}}{r_{\pi 2} \parallel r_{o1} + R_C} v_t \\ i_t &= \left( g_{m2} + \frac{1}{r_{\pi 2} \parallel r_{o1}} \right) \frac{r_{\pi 2} \parallel r_{o1}}{r_{\pi 2} \parallel r_{o1} + R_C} v_t \\ R_{out} &= r_{o2} \parallel \frac{v_t}{i_t} \\ &= \boxed{r_{o2} \parallel \left[ \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o1} \right) \frac{r_{\pi 2} \parallel r_{o1} + R_C}{r_{\pi 2} \parallel r_{o1}} \right]} \end{aligned}$$

40)

Gain of a degenerated CE stage ( $V_A = \infty$ )

$$A_v = \frac{-R_c}{\frac{1}{g_m} + R_E} = \frac{-R_c g_m}{1 + R_E g_m}$$

$$\frac{\partial A_v}{\partial I_c} = R_c \left( \frac{g_m R_E}{(1 + R_E g_m)^2} \frac{\partial g_m}{\partial I_c} - \frac{\partial g_m / \partial I_c}{1 + g_m R_E} \right)$$

$$\frac{\partial g_m}{\partial I_c} = \frac{1}{V_T} = \frac{1}{26 \text{ mV}} = 38.46 \left( \frac{1}{\text{V}} \right)$$

a)  $g_m R_E = 3$

$$\frac{\partial A_v}{\partial I_c} = R_c (-2.404) \quad , \quad \partial I_c = 0.1 I_c$$

$$\partial A_v = -R_c I_c (0.24)$$

$$\text{Relative change in gain} = \frac{\partial A_v}{A_v} = \frac{-0.24 (R_c I_c)}{-\frac{R_c I_c}{V_T (1 + R_E g_m)}} = 2.5\%$$

40)


$$b) g_m R_E = 7$$

$$\frac{\partial A_v}{\partial I_c} = -R_c \cdot 0.6$$

$$\partial A_v = -R_c I_c (0.06)$$

Relative change in gain
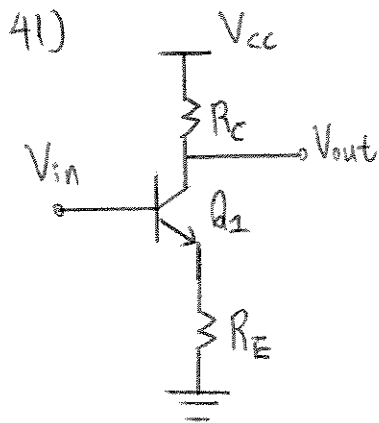
$$\frac{\partial A_v}{A_v} = \frac{-0.06 (R_c I_c)}{\frac{-R_c I_c}{V_T (1 + R_E g_m)}} = 1.25\%$$



$$V_A = \infty$$

$$R_C I_C = 20 V_T$$

$$R_E I_C = 5 V_T$$


$$|A_v| = \frac{R_C}{R_E + \frac{1}{g_m}} = \frac{R_C}{R_E + \frac{V_T}{I_C}} = \frac{R_C I_C}{R_E I_C + V_T}$$

Assume  $\beta$  is large, so  $I_C = I_E$ .

$$R_C I_C = 20 V_T, \quad R_E I_C = 5 V_T$$

$$|A_v| = \frac{20 V_T}{5 V_T + V_T} = \frac{20 V_T}{6 V_T} = 3.33$$

42)

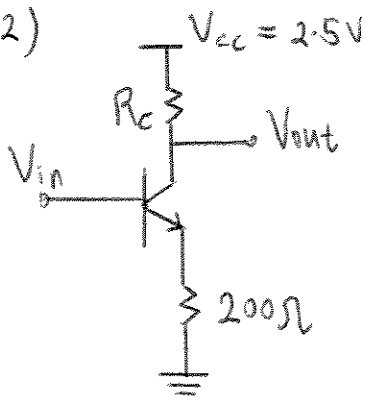

$$|A_v| = \frac{R_c I_c}{R_E I_c + V_T} = 10$$

Edge of Saturation

$$V_{CE} = V_{BE} = 2.5 - I_c (R_c + R_E)$$

$$V_{BE} = 0.8 \text{ V} \Rightarrow I_c R_c = 1.7 - I_c 0.2 \quad (\text{operating point})$$

$$|A_v| = 10 \Rightarrow R_c I_c = 10 (R_E I_c + V_T) \quad (\text{Gain Equation})$$

Equating the two equations above  $\Rightarrow$ 

$$1.7 - 0.2 I_c = 2 I_c + 0.26 \Rightarrow I_c = 0.655 \text{ mA}$$

Check for  $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_0}\right) = 0.725$ , not 0.8, Reiterate

$$I_c R_c = 1.775 - I_c 0.2 \quad (\text{operating point})$$

$$I_c R_c = 2 I_c + 0.26 \quad (\text{Gain equation})$$

Equating the two equations  $\Rightarrow I_c = 0.689 \text{ mA}$ Check for  $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_0}\right) = 0.727 \text{ V}$ , iterate 1 more time

$$I_c R_c = 1.773 - I_c 0.2 \quad (\text{operating point})$$

$$I_c R_c = 2 I_c + 0.26 \quad (\text{Gain equation})$$



42)

Equating the two equations  $\Rightarrow I_c = 0.688 \text{ mA}$

Check for  $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.727 \text{ V}$ , converged

$$I_c = 0.688 \text{ mA}$$

$$R_c = \frac{2I_c + 0.26}{I_c} = \frac{(2 \times 0.688) + 0.26}{0.688}$$

$$R_c = 2.38 \text{ k}\Omega$$

$$R_{in} = r_{\pi} + (1 + \beta) R_E$$

$$R_{in} = \frac{\beta}{g_m} + (101)(0.2) = 24.0 \text{ k}\Omega$$

$$\begin{aligned}
 A_v &= -\frac{R_C}{\frac{1}{g_m} + (200 \Omega)} \\
 &= -\frac{R_C}{\frac{V_T}{I_C} + (200 \Omega)} \\
 &= -100
 \end{aligned}$$



$$R_C = 100 \frac{V_T}{I_C} + 100(200 \Omega)$$

$$I_C R_C - I_E(200 \Omega) = V_{CE} = V_{BE} = V_T \ln(I_C/I_S)$$

$$I_C \left( 100 \frac{V_T}{I_C} + 100(200 \Omega) \right) - \frac{1 + \beta}{\beta} I_C(200 \Omega) = V_T \ln(I_C/I_S)$$

We can see that this equation has no solution. For example, if we let  $I_C = 0$ , we see that according to the left side, we should have  $V_{BE} = 2.6$  V, which is clearly an infeasible value. Qualitatively, we know that in order to achieve a large gain, we need a large value for  $R_C$ . However, increasing  $R_C$  will result in a smaller value of  $V_{CE}$ , eventually driving the transistor into saturation. When  $A_v = -100$ , there is no value of  $R_C$  that will provide such a large gain without driving the transistor into saturation.

44)  $V_A = \infty$

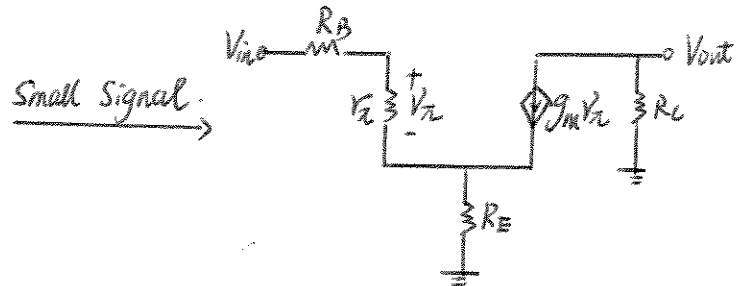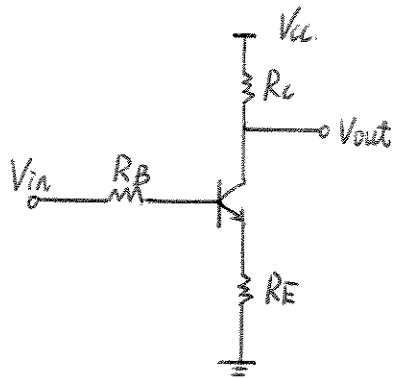


$$V_{out} = -g_m V_e R_C$$

$$V_e = \frac{V_{in} r_e}{R_B + r_e + (\beta + 1) R_E}$$


$$V_{out} = \frac{-g_m r_e R_C V_{in}}{R_B + r_e + (\beta + 1) R_E} = \frac{-\beta R_C V_{in}}{R_B + r_e + (\beta + 1) R_E} = \frac{-R_C V_{in}}{\frac{R_B}{\beta} + \frac{1}{g_m} + \frac{\beta + 1}{\beta} R_E}$$

$$\frac{V_{out}}{V_{in}} \approx \frac{-R_C}{\frac{R_B}{\beta + 1} + \frac{1}{g_m} + R_E}$$

45)

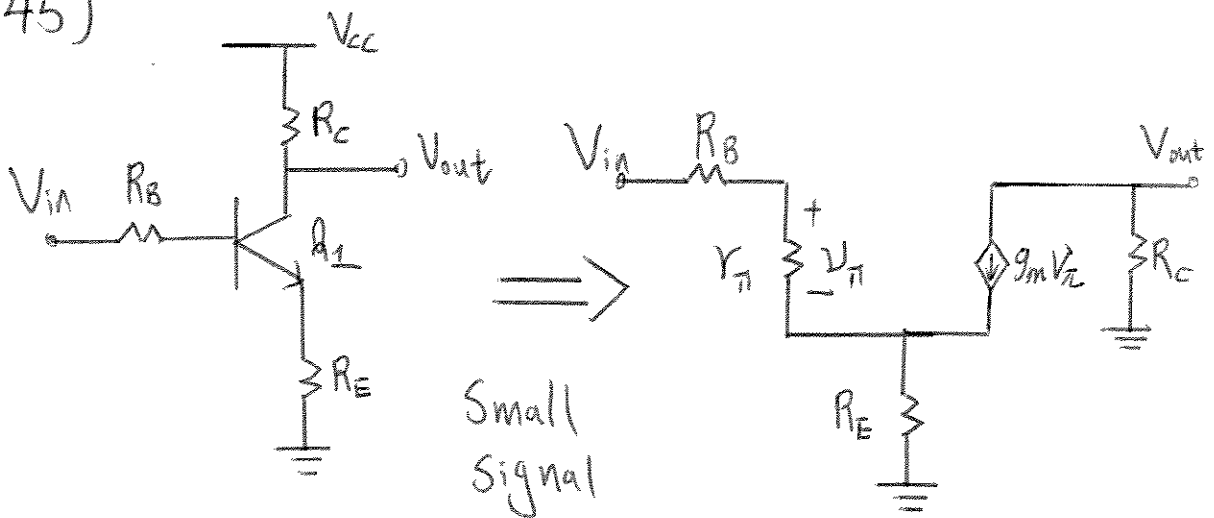

$R_{out}$  Calculation:

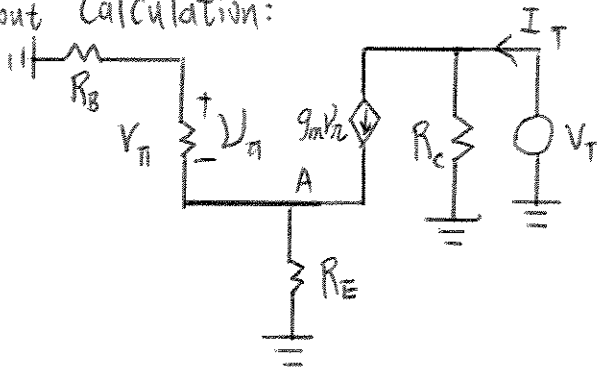

$$V_A = g_m V_{\pi} (R_E \parallel R_B + r_{\pi}) \quad (1)$$

$$V_{\pi} = -\frac{V_A r_{\pi}}{r_{\pi} + R_B} \Rightarrow V_A = -\frac{V_{\pi} (r_{\pi} + R_B)}{r_{\pi}} \quad (2)$$

The only possible solution for 1) and 2) is  $V_{\pi} = V_A = 0$ ,  
 since 1) is positive and 2) is negative.

$$V_{\pi} = 0 \Rightarrow g_m V_{\pi} \Rightarrow 0 \Rightarrow \frac{V_T}{I_T} = R_C$$

Therefore,  $R_{out} = R_C$

5.46 (a)

$$A_v = -\frac{R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1)R_E$$

$$R_{out} = R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

(b)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{out} = R_C$$

(c)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{out} = R_C$$

(d)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{R_B}{1 + \beta_1}}$$

$$R_{in} = R_B + r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{out} = R_C$$

(e)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{R_B}{1 + \beta_1}}$$

$$R_{in} = R_B + r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{out} = R_C$$

5.47 (a)

$$A_v = -\frac{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) R_E$$

$$R_{out} = R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

(b)

$$A_v = -\frac{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E} \cdot \frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

$$= -\frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) R_E$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

(c)

$$A_v = -\frac{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m3}} \parallel r_{\pi 3}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m3}} \parallel r_{\pi 3} \right)$$

$$R_{out} = R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$


(d)

$$A_v = -\frac{R_C \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) R_E$$


$$R_{out} = R_C \parallel r_{\pi 2}$$

48).

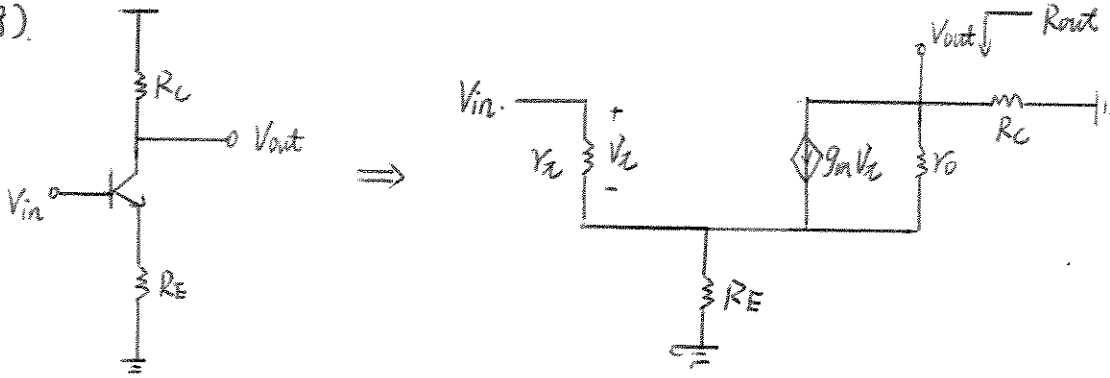

$$R_{out} = R_c \parallel R_{eq}$$

Solve for  $R_{eq}$ .

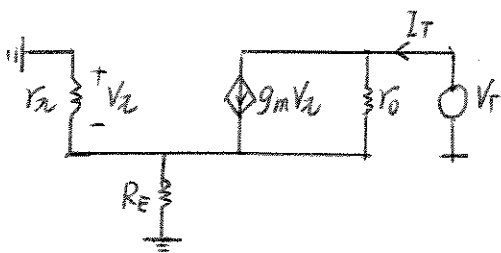

$$I_T = g_m V_{\pi} + \frac{(V_T + V_{\pi})}{r_o}$$

$$V_{\pi} = -I_T (r_{\pi} \parallel R_E)$$

$$I_T = -g_m I_T (r_{\pi} \parallel R_E) + \frac{(V_T - I_T (r_{\pi} \parallel R_E))}{r_o}$$

$$\frac{V_T}{I_T} = r_o \left( 1 + \frac{(r_{\pi} \parallel R_E)}{r_o} \right) + g_m (r_{\pi} \parallel R_E)$$


$$\frac{V_T}{I_T} = r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$

$$R_{eq} = r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$

$$R_{out} = R_c \parallel r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$


$$R_{out} \approx R_c \parallel r_o (1 + g_m (r_{\pi} \parallel R_E)) \quad \text{since } g_m r_o \gg 1$$

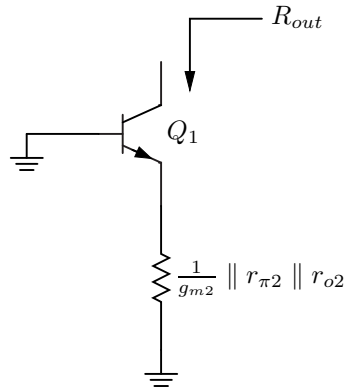- 5.49 (a) Looking into the emitter of  $Q_2$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1}) \left( r_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

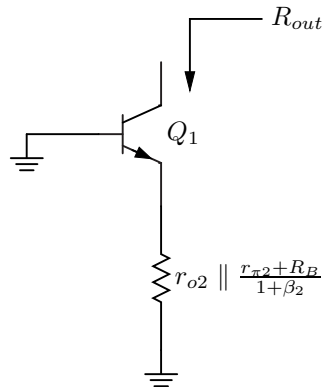
- (b) Looking into the emitter of  $Q_2$  we see an equivalent resistance of  $r_{o2} \parallel \frac{r_{\pi 2} + R_B}{1 + \beta_2}$  ( $r_{o2}$  simply appears in parallel with the resistance seen when  $V_A = \infty$ ), so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1}) \left( r_{\pi 1} \parallel r_{o2} \parallel \frac{r_{\pi 2} + R_B}{1 + \beta_2} \right)$$

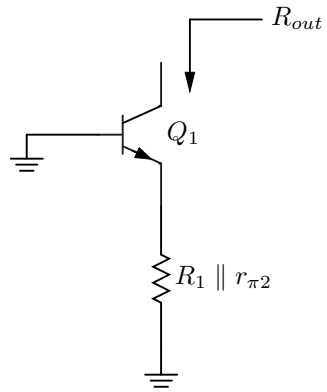
- (c) Looking down from the emitter of  $Q_1$  we see an equivalent resistance of  $R_1 \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :






$$R_{out} = \boxed{r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi 1} \parallel R_1 \parallel r_{\pi 2})}$$

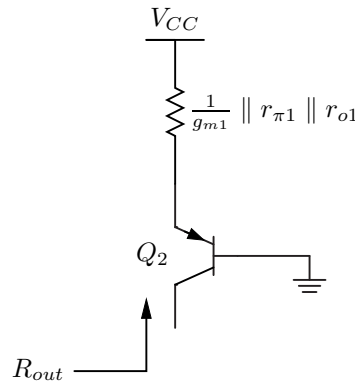- 5.50 (a) Looking into the emitter of  $Q_1$  we see an equivalent resistance of  $\frac{1}{g_{m1}} \parallel r_{\pi1} \parallel r_{o1}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = \boxed{r_{o2} + (1 + g_{m2}r_{o2}) \left( r_{\pi2} \parallel \frac{1}{g_{m1}} \parallel r_{\pi1} \parallel r_{o1} \right)}$$

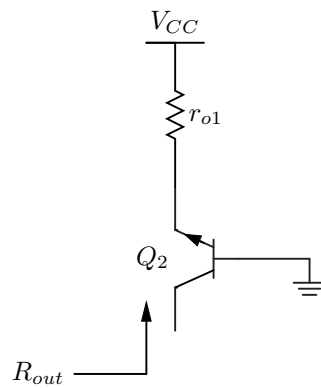- (b) Looking into the emitter of  $Q_1$  we see an equivalent resistance of  $r_{o1}$ , so we can draw the following equivalent circuit for finding  $R_{out}$ :



$$R_{out} = \boxed{r_{o2} + (1 + g_{m2}r_{o2}) (r_{\pi2} \parallel r_{o1})}$$

Comparing this to the solution to part (a), we can see that the output resistance is larger because instead of a factor of  $1/g_{m1}$  dominating the parallel resistors in the expression,  $r_{\pi2}$  dominates (assuming  $r_{o1} \gg r_{\pi2}$ ).

$$51). r_2 = \beta V_T / I_C.$$

$$R_{in} = r_2 \parallel R_B = \frac{\frac{\beta V_T}{I_C} R_B}{\frac{\beta V_T}{I_C} + R_B} = \frac{V_T R_B}{V_T + \frac{I_C}{\beta} R_B} = \frac{V_T R_B}{V_T + 2R_B}$$

$$\text{Since } I_B R_B \gg V_T \Rightarrow R_{in} \approx \frac{V_T R_B}{I_B R_B} = \frac{V_T}{I_B} = \frac{V_T}{\frac{I_C}{\beta}} = \frac{\beta V_T}{I_C} \approx r_2$$

$$\text{So } R_{in} = r_2 \parallel R_B \approx r_2.$$

5.52 (a)

$$\begin{aligned}
 V_{CC} - I_B(100 \text{ k}\Omega) - I_E(100 \text{ }\Omega) &= V_{BE} = V_T \ln(I_C/I_S) \\
 V_{CC} - \frac{1}{\beta}I_C(100 \text{ k}\Omega) - \frac{1+\beta}{\beta}I_C(100 \text{ }\Omega) &= V_T \ln(I_C/I_S) \\
 I_C &= 1.6 \text{ mA} \\
 A_v &= -\frac{1 \text{ k}\Omega}{\frac{1}{g_m} + 100 \text{ }\Omega} \\
 g_m &= 61.6 \text{ mS} \\
 A_v &= \boxed{-8.60}
 \end{aligned}$$

(b)

$$\begin{aligned}
 V_{CC} - I_B(50 \text{ k}\Omega) - I_E(2 \text{ k}\Omega) &= V_T \ln(I_C/I_S) \\
 I_C &= 708 \text{ }\mu\text{A} \\
 A_v &= -\frac{1 \text{ k}\Omega}{\frac{1}{g_m} + \frac{(1 \text{ k}\Omega)\|(50 \text{ k}\Omega)}{1+\beta}} \\
 g_m &= 27.2 \text{ mS} \\
 A_v &= \boxed{-21.54}
 \end{aligned}$$

(c)

$$\begin{aligned}
 I_B &= \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE} - I_E(2.5 \text{ k}\Omega)}{14 \text{ k}\Omega} - \frac{V_{BE} + I_E(2.5 \text{ k}\Omega)}{11 \text{ k}\Omega} \\
 I_C &= \beta \frac{V_{CC} - V_T \ln(I_C/I_S) - \frac{1+\beta}{\beta}I_C(2.5 \text{ k}\Omega)}{14 \text{ k}\Omega} - \beta \frac{V_T \ln(I_C/I_S) + \frac{1+\beta}{\beta}I_C(2.5 \text{ k}\Omega)}{11 \text{ k}\Omega} \\
 I_C &= 163 \text{ }\mu\text{A} \\
 A_v &= -\frac{10 \text{ k}\Omega}{\frac{1}{g_m} + 500 \text{ }\Omega + \frac{(1 \text{ k}\Omega)\|(14 \text{ k}\Omega)\|(11 \text{ k}\Omega)}{1+\beta}} \\
 g_m &= 6.29 \text{ mS} \\
 A_v &= \boxed{-14.98}
 \end{aligned}$$

5.53 (a)

$$\begin{aligned}I_C &= \frac{V_{CC} - 1.5 \text{ V}}{R_C} \\&= 4 \text{ mA} \\V_{BE} &= V_T \ln(I_C/I_S) = 832 \text{ mV} \\I_B &= \frac{V_{CC} - V_{BE}}{R_B} = 66.7 \text{ }\mu\text{A} \\ \beta &= \frac{I_C}{I_B} = \boxed{60}\end{aligned}$$

(b) Assuming the speaker has an impedance of  $8 \text{ }\Omega$ , the gain of the amplifier is

$$\begin{aligned}A_v &= -g_m (R_C \parallel 8 \text{ }\Omega) \\&= -\frac{I_C}{V_T} (R_C \parallel 8 \text{ }\Omega) \\&= \boxed{-1.19}\end{aligned}$$

Thus, the circuit provides greater than unity gain.

5.54 (a)

$$A_v = g_m R_C$$

$$g_m = \frac{I_C}{V_T} = 76.9 \text{ mS}$$

$$A_v = \boxed{38.46}$$

$$R_{in} = \frac{1}{g_m} \parallel r_\pi$$


$$r_\pi = \frac{\beta}{g_m} = 1.3 \text{ k}\Omega$$

$$R_{in} = \boxed{12.87 \Omega}$$

$$R_{out} = R_C = \boxed{500 \Omega}$$


- (b) Since  $A_v = g_m R_C$  and  $g_m$  is fixed for a given value of  $I_C$ ,  $R_C$  should be chosen as large as possible to maximize the gain of the amplifier.  $V_b$  should be chosen as small as possible to maximize the headroom of the amplifier (since in order for  $Q_1$  to remain in forward active, we require  $V_b < V_{CC} - I_C R_C$ ).

55)  $V_A = \infty$

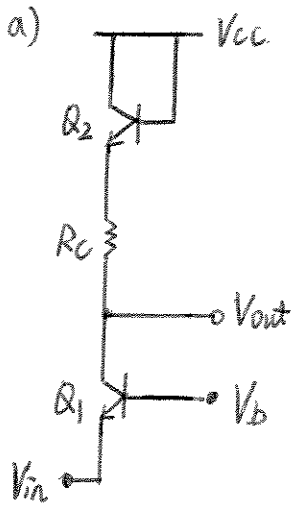


$$|A_v| = \frac{R_c + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}}}$$
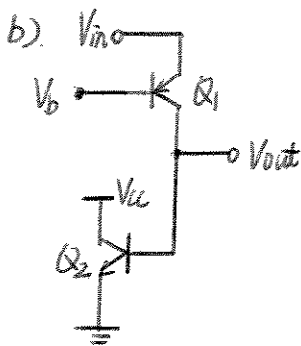
$$= g_{m1} (R_c + \frac{1}{g_{m2}} \parallel r_{\pi 2})$$



$$|A_v| = \frac{r_{\pi 2}}{\frac{1}{g_{m1}}} = g_{m1} r_{\pi 2}$$

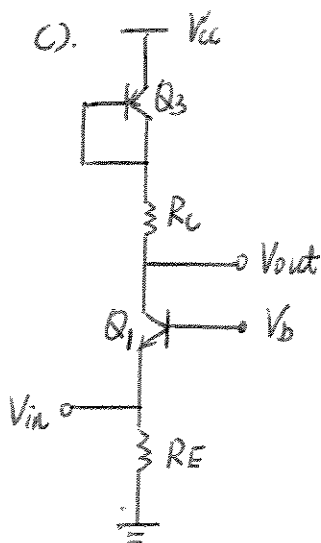


$$|A_v| = \frac{R_c + \frac{1}{g_{m3}} \parallel r_{\pi 3}}{\frac{1}{g_{m1}}}$$

$$= g_{m1} (R_c + \frac{1}{g_{m3}} \parallel r_{\pi 3})$$

55).

d).

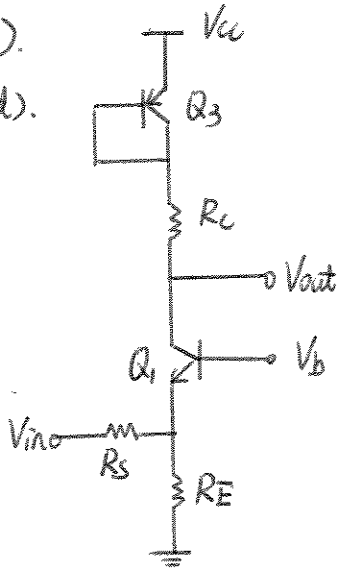


$$|A_v| = \left| \frac{V_{out}}{V_A} \right| \left| \frac{V_A}{V_{in}} \right|$$

$$= \left[ g_{m1} \left( R_C + \frac{1}{g_{m3} \parallel R_{L3}} \right) \right] \left( \frac{R_E \parallel \frac{1}{g_{m1}}}{R_E \parallel \frac{1}{g_{m1}} + R_S} \right)$$




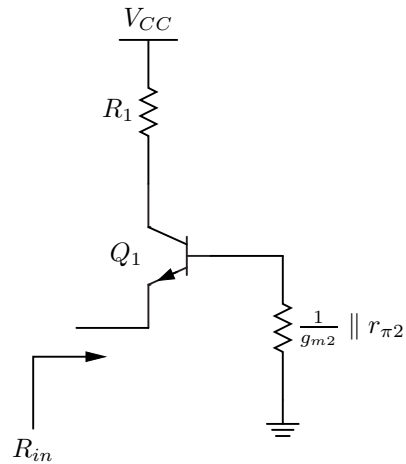- 5.56 (a) Looking into the emitter of  $Q_2$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = \frac{r_{\pi 1} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{1 + \beta_1}$$

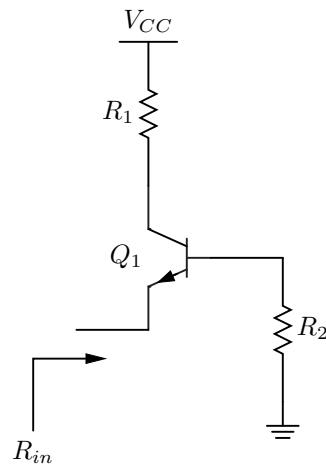- (b) Looking right from the base of  $Q_1$  we see an equivalent resistance of  $R_2$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = \frac{r_{\pi 1} + R_2}{1 + \beta_1}$$

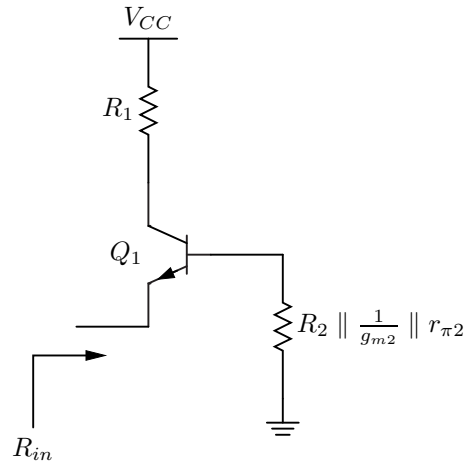- (c) Looking right from the base of  $Q_1$  we see an equivalent resistance of  $R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = \frac{r_{\pi 1} + R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{1 + \beta_1}$$

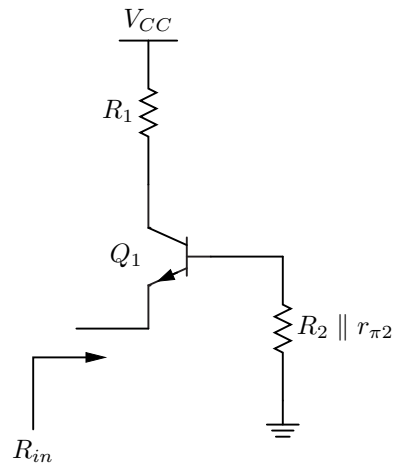- (d) Looking right from the base of  $Q_1$  we see an equivalent resistance of  $R_2 \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :



$$R_{in} = \frac{r_{\pi 1} + R_2 \parallel r_{\pi 2}}{1 + \beta_1}$$

57)

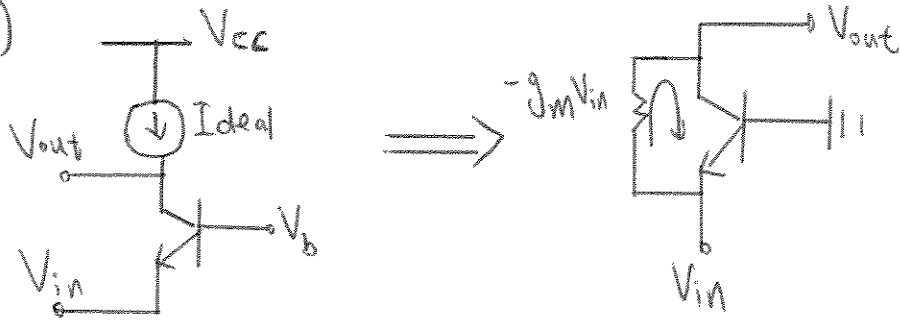

Since an ideal current source is an open circuit, the signal current produced by the transistor has nowhere to go but  $R_o$ .

$$\text{So } V_{out} = -(g_m(0 - V_{in}))R_o + V_{in}$$

$$V_{out} = g_m R_o V_{in} + V_{in}$$

$$V_{out} = V_{in}(g_m R_o + 1)$$

$$\frac{V_{out}}{V_{in}} = 1 + g_m R_o$$

5.58 (a)

$$I_B = \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE} - I_E(400 \Omega)}{13 \text{ k}\Omega} - \frac{V_{BE} + I_E(400 \Omega)}{12 \text{ k}\Omega}$$
$$I_C = \beta \frac{V_{CC} - V_T \ln(I_C/I_S) - \frac{1+\beta}{\beta} I_C(400 \Omega)}{13 \text{ k}\Omega} - \beta \frac{V_T \ln(I_C/I_S) + \frac{1+\beta}{\beta} I_C(400 \Omega)}{12 \text{ k}\Omega}$$
$$I_C = \boxed{1.02 \text{ mA}}$$
$$V_{BE} = V_T \ln(I_C/I_S) = \boxed{725 \text{ mV}}$$
$$V_{CE} = V_{CC} - I_C(1 \text{ k}\Omega) - I_E(400 \Omega) = \boxed{1.07 \text{ V}}$$

$Q_1$  is operating in forward active.


(b)

$$A_v = g_m(1 \text{ k}\Omega)$$

$$g_m = 39.2 \text{ mS}$$

$$A_v = \boxed{39.2}$$

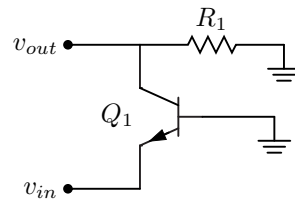5.61 For small-signal analysis, we can draw the following equivalent circuit.



$$A_v = \boxed{g_m R_1}$$
$$R_{in} = \boxed{\frac{1}{g_m} \parallel r_\pi}$$
$$R_{out} = \boxed{R_1}$$

59)

$$C_B = 0$$

a) Since  $C_B$  was not considered during DC analysis, it has no effect on operating point analysis. So it is still the same as 58).


$$V_{BE} = 0.725 \text{ V}$$

$$I_C = 1.0163 \text{ mA}$$

$$I_B = 10.163 \mu\text{A}$$

$$V_{CE} = 1.07 \text{ V}$$

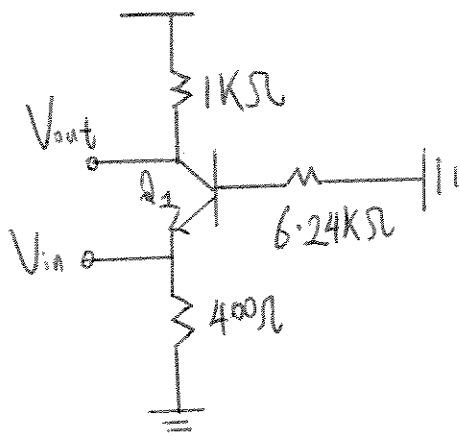b) Since capacitor is frequency dependent, the circuit's AC analysis will be different.




$$|A_v| = \frac{1\text{k}}{\frac{1}{g_m} + \frac{6.24\text{k}\Omega}{\beta + 1}} = 11.4$$

$$R_{in} = 400\Omega \parallel \left( \frac{1}{g_m} + \frac{6.24\text{k}\Omega}{\beta + 1} \right)$$

$$R_{in} = 71.7\Omega$$

$$R_{out} = 1\text{k}\Omega$$

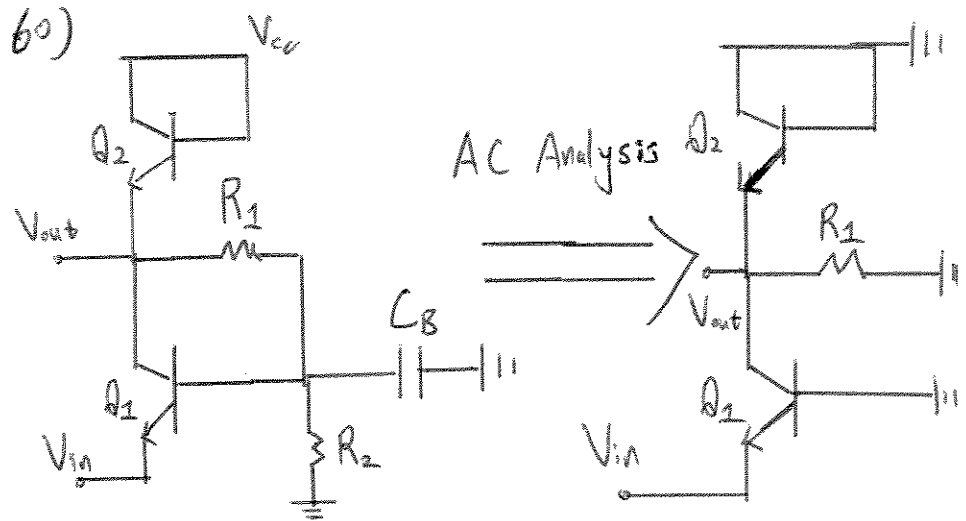Note:  $6.24\text{k}\Omega$  is  $R_{THEV}$   
of  $13\text{k}\Omega$  and  $12\text{k}\Omega$   
combination.




$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_1 \approx \frac{1}{g_{m2}} \parallel R_1$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_1 \right) \approx g_{m1} \left( \frac{1}{g_{m2}} \parallel R_1 \right)$$

$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \approx \frac{1}{g_{m1}}$$

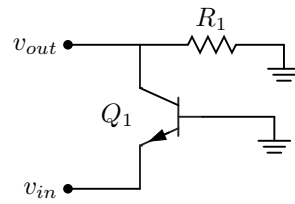
5.61 For small-signal analysis, we can draw the following equivalent circuit.



$$A_v = \boxed{g_m R_1}$$
$$R_{in} = \boxed{\frac{1}{g_m} \parallel r_\pi}$$
$$R_{out} = \boxed{R_1}$$



62)

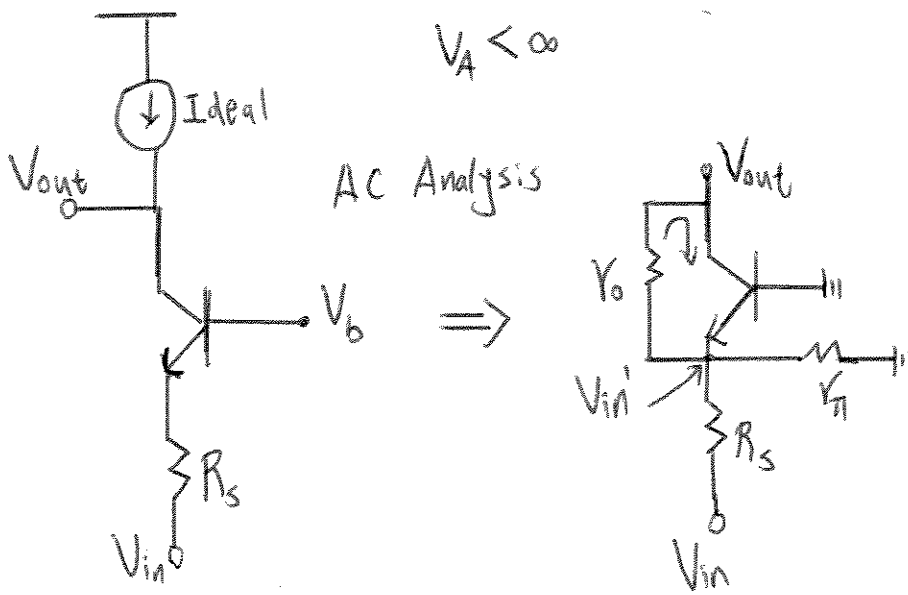

$$A_v = \frac{V_{out}}{V_{in}} = \left( \frac{V_{in'}}{V_{in}} \right) \left( \frac{V_{out}}{V_{in'}} \right), \quad \left( \frac{V_{in'}}{V_{in}} \right) = \frac{r_{\pi}}{r_{\pi} + R_s}$$

Since  $V_{out}$  is float, so looking at emitter and  $r_o$ , we will see an infinite impedance.

$$\frac{V_{out}}{V_{in'}} \Rightarrow -g_m (-V_{in'}) r_o + V_{in'} = V_{out} \Rightarrow \frac{V_{out}}{V_{in'}} = (g_m r_o + 1)$$

$$A_v = (g_m r_o + 1) \left( \frac{r_{\pi}}{r_{\pi} + R_s} \right)$$


5.63 Since  $I_{S1} = 2I_{S2}$  and they're biased identically, we know that  $I_{C1} = 2I_{C2}$ , which means  $g_{m1} = 2g_{m2}$ .

$$\frac{v_{out1}}{v_{in}} = g_{m1}R_C = 2g_{m2}R_C$$

$$\frac{v_{out2}}{v_{in}} = g_{m2}R_C$$

$$\Rightarrow \boxed{\frac{v_{out1}}{v_{in}} = 2 \frac{v_{out2}}{v_{in}}}$$

64)

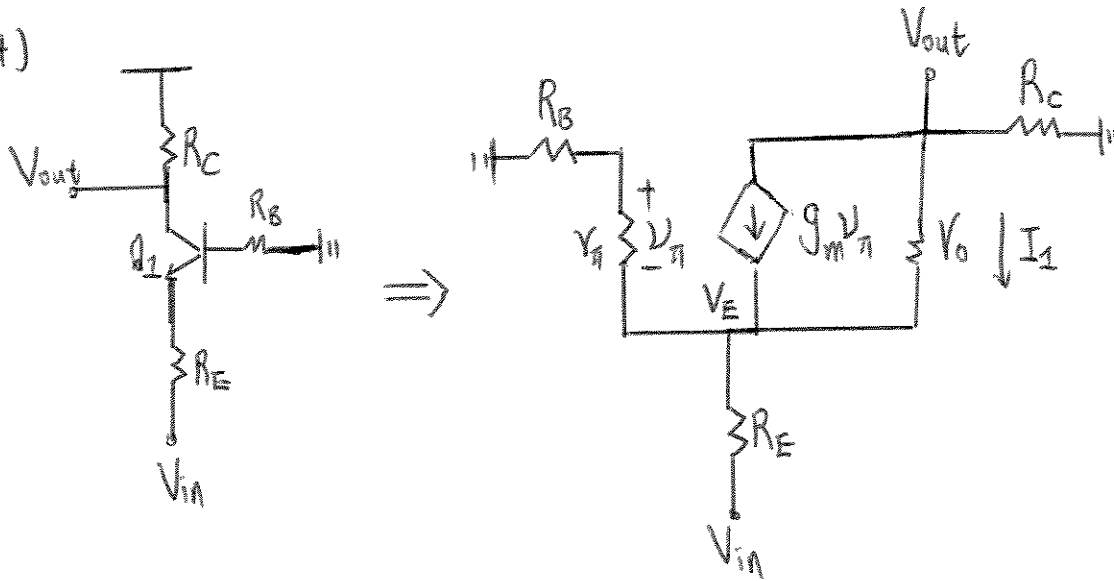

$$V_{out} = -(I_1 + g_m v_\pi) R_C, \quad I_1 = \frac{V_{out} - V_E}{Y_o}$$

$$V_{out} = -\left(\frac{V_{out} - V_E}{Y_o} + g_m v_\pi\right) R_C, \quad V_E = -\frac{g_m v_\pi}{\beta} (r_\pi + R_B)$$

$$V_{out} = -\left(\frac{V_{out} + \frac{g_m v_\pi (r_\pi + R_B)}{\beta}}{Y_o} + g_m v_\pi\right) R_C$$

Rearranging

$$v_\pi = \frac{-(1 + \frac{R_C}{Y_o}) V_{out}}{\frac{g_m (r_\pi + R_B) R_C}{\beta Y_o} + g_m R_C} = A V_{out}$$

Summing the voltage at node E.

$$V_E - \left( \left(1 + \frac{1}{\beta}\right) g_m v_\pi + \frac{V_{out} - V_E}{Y_o} \right) R_E = V_{in} \quad (1)$$

64) Writing  $V_E$  in terms of  $V_{\pi}$ , and  $V_{\pi}$  in terms of  $V_{out}$

1) becomes

$$-\frac{g_m A V_{out}}{\beta} (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) - \left(1 + \frac{1}{\beta}\right) g_m A V_{out} R_E - \frac{V_{out} R_E}{Y_0} = V_{in}$$


Solving  $V_{out} / V_{in} \Rightarrow$

$$\frac{V_{out}}{V_{in}} = \frac{1}{-\frac{g_m A}{\beta} (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) - \left(1 + \frac{1}{\beta}\right) g_m A R_E - \frac{R_E}{Y_0}}$$

substituting A into equation

$$\frac{V_{out}}{V_{in}} = \frac{g_m (Y_{\pi} + R_B) R_C + g_m R_C}{g_m \left(1 + \frac{R_E}{Y_0}\right) (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) + \left(1 + \frac{1}{\beta}\right) g_m \left(1 + \frac{R_C}{Y_0}\right) R_E - \frac{R_E}{Y_0} \left(\frac{g_m (Y_{\pi} + R_B) R_C}{\beta Y_0} + g_m R_C\right)}$$

65)

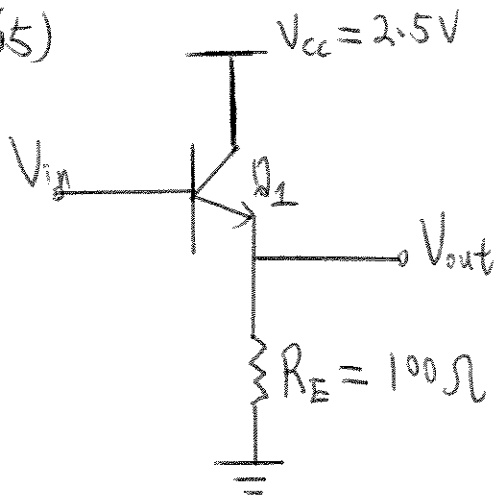

$$R_E = 100\Omega$$

$$V_A = \infty$$

$$|A_v| = 0.8$$


$$|A_v| = \frac{R_E}{R_E + \frac{1}{g_m}} = \frac{R_E I_c}{R_E I_c + V_T} = 0.8$$

$$\Rightarrow R_E I_c = 0.8(R_E I_c + V_T), \quad R_E = 100\Omega$$

$$\Rightarrow 0.1 I_c = 0.08 I_c + 0.0208 \Rightarrow 0.02 I_c = 0.0208$$

$$\Rightarrow I_c = 1.04 \text{ mA}$$

6b)

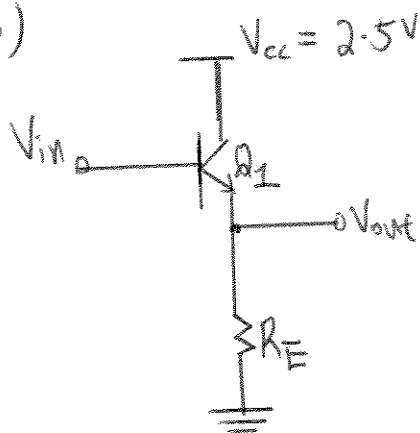

$$|A_v| > 0.9$$

$$R_{in} > 10\text{K}\Omega$$

$$|A_v| = \frac{R_E I_C}{R_E I_C + V_T} > 0.9 \Rightarrow R_E I_C > 0.9 [R_E I_C + V_T]$$

$$\Rightarrow R_E I_C > 9V_T = 234\text{mV}, \text{ Let } R_E I_C = 240\text{mV}$$

$$R_{in} = r_{\pi} + (1 + \beta) R_E > 10\text{K} \Rightarrow 100V_T + (101)R_E I_C > 10\text{K}\Omega I_C$$

substituting  $R_E I_C = 240\text{mV} \Rightarrow I_C < 2.684\text{mA}$

$$\text{Choose } I_C \text{ to be } 2.5\text{mA} \Rightarrow R_E = 96\Omega$$

To Verify:


$$R_{in} = \frac{100(0.026)}{2.5} + (101)0.096 = 10.74\text{K}\Omega$$

$$|A_v| = \frac{(0.096)(2.5)}{(0.096)(2.5) + 0.026} = 0.902$$

5.67

$$\begin{aligned}R_{out} &= \frac{r_{\pi} + R_S}{1 + \beta} \\&= \frac{\beta V_T / I_C + R_S}{1 + \beta} \\&\leq 5 \Omega \\I_C &= \frac{\beta}{1 + \beta} I_E = \frac{\beta}{1 + \beta} I_1 \\ \frac{\frac{\beta(1+\beta)V_T}{\beta I_1} + R_S}{1 + \beta} &= \frac{\frac{(1+\beta)V_T}{I_1} + R_S}{1 + \beta} \\&\leq 5 \Omega \\I_1 &\geq \boxed{8.61 \text{ mA}}\end{aligned}$$

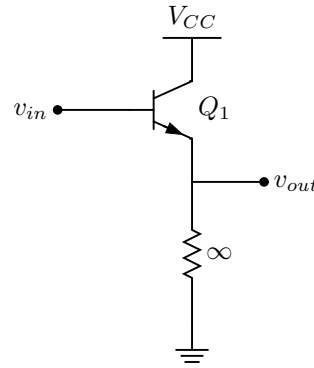- 5.68 (a) Looking into the collector of  $Q_2$  we see an equivalent resistance of  $r_{o2} = \infty$ , so we can draw the following equivalent circuit:




$$A_v = \boxed{1}$$

$$R_{in} = \boxed{\infty}$$

$$R_{out} = \boxed{\frac{1}{g_{m1}} \parallel r_{\pi 1}}$$

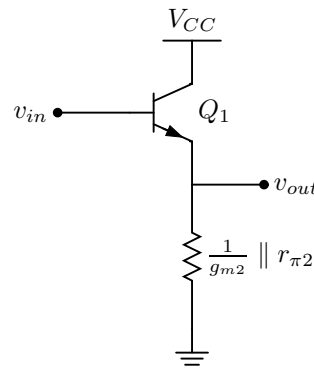- (b) Looking down from the emitter of  $Q_1$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit:




$$A_v = \boxed{\frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}}$$

$$R_{in} = \boxed{r_{\pi 1} + (1 + \beta_1) \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)}$$

$$R_{out} = \boxed{\frac{1}{g_{m1}} \parallel r_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

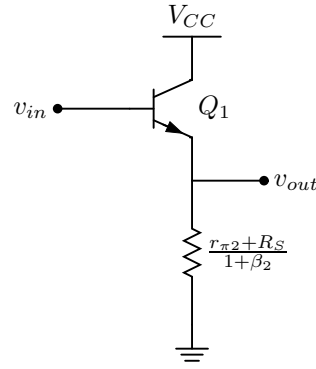- (c) Looking into the emitter of  $Q_2$  we see an equivalent resistance of  $\frac{r_{\pi 2} + R_S}{1 + \beta_2}$ , so we can draw the following equivalent circuit:






$$A_v = \frac{\frac{r_{\pi 2} + R_S}{1 + \beta_2}}{\frac{1}{g_{m1}} + \frac{r_{\pi 2} + R_S}{1 + \beta_2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( \frac{r_{\pi 2} + R_S}{1 + \beta_2} \right)$$

$$R_{out} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \parallel \left( \frac{r_{\pi 2} + R_S}{1 + \beta_2} \right)$$

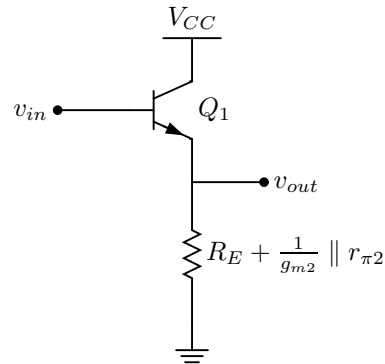- (d) Looking down from the emitter of  $Q_1$  we see an equivalent resistance of  $R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit:




$$A_v = \frac{R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( R_E + \frac{1}{g_{m2}} \right)$$


$$R_{out} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \parallel \left( R_E + \frac{1}{g_{m2}} \right)$$

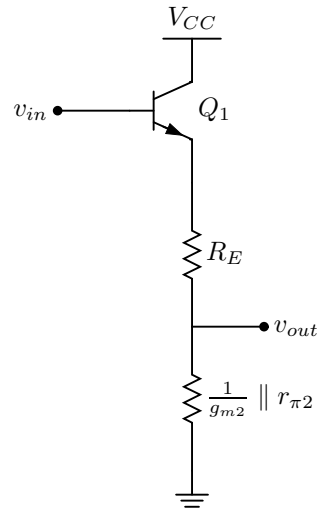- (e) Looking into the emitter of  $Q_2$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit:




$$\begin{aligned}
 A_v &= \frac{R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}} \cdot \frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}} \\
 &= \boxed{\frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}}} \\
 R_{in} &= \boxed{r_{\pi 1} + (1 + \beta_1) \left( R_E + \frac{1}{g_{m2} \parallel r_{\pi 2}} \right)} \\
 R_{out} &= \boxed{\left( \frac{1}{g_{m1}} \parallel r_{\pi 1} + R_E \right) \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}
 \end{aligned}$$

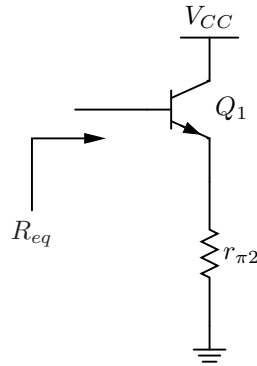- 5.69 (a) Looking into the base of  $Q_2$  we see an equivalent resistance of  $r_{\pi 2}$  (assuming the emitter of  $Q_2$  is grounded), so we can draw the following equivalent circuit for finding the impedance at the base of  $Q_1$ :



$$R_{eq} = r_{\pi 1} + (1 + \beta_1)r_{\pi 2}$$

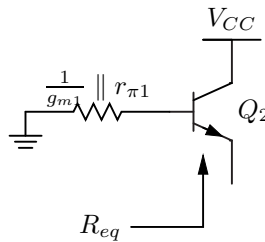- (b) Looking into the emitter of  $Q_1$  we see an equivalent resistance of  $\frac{1}{g_{m1}} \parallel r_{\pi 1}$  (assuming the base of  $Q_1$  is grounded), so we can draw the following equivalent circuit for finding the impedance at the emitter of  $Q_2$ :



$$R_{eq} = \frac{r_{\pi 2} + \frac{1}{g_{m1}} \parallel r_{\pi 1}}{1 + \beta_2}$$

- (c)

$$\begin{aligned} \frac{I_{C1} + I_{C2}}{I_{B1}} &= \frac{\beta_1 I_{B1} + \beta_2 (1 + \beta_1) I_{B1}}{I_{B1}} \\ &= \beta_1 + \beta_2 (1 + \beta_1) \end{aligned}$$

If we assume that  $\beta_1, \beta_2 \gg 1$ , then this simplifies to  $\beta_1 \beta_2$ , meaning a Darlington pair has a current gain approximately equal to the product of the current gains of the individual transistors.

5.70 (a)


$$R_{CS} = \boxed{r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)}$$

(b)

$$A_v = \frac{\boxed{r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)}}{\boxed{\frac{1}{g_{m1}} + r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)}}$$

$$R_{in} = \boxed{r_{\pi1} + (1 + \beta_1)[r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)]}$$
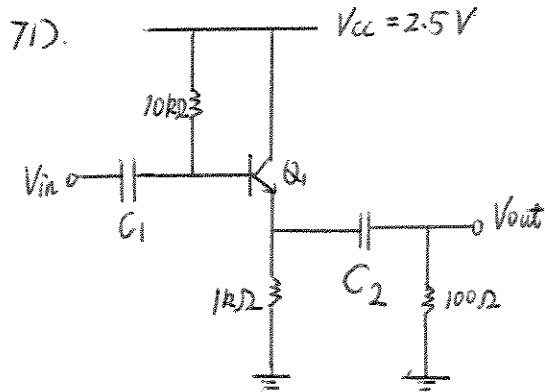
$$R_{out} = \boxed{\frac{1}{g_{m1}} \parallel r_{\pi1} \parallel [r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)]}$$




$$I_s = 7 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = 5 \text{ V}$$

DC Analysis: (Ignore  $V_o$ 's effect).

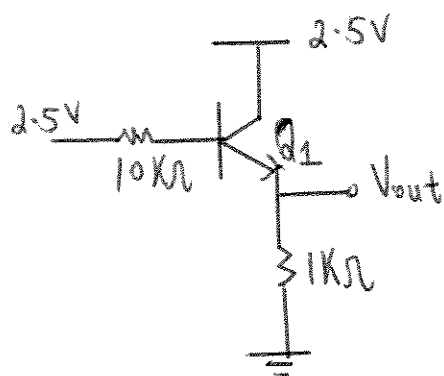

$$I_c = \beta \left( \frac{2.5 - (V_{BE} + \frac{I_c}{\alpha} 1 \text{ k}\Omega)}{10 \text{ k}\Omega} \right)$$

rearrange

$$I_c = \frac{2.5 - V_{BE}}{\frac{10 \text{ k}\Omega}{\beta} + \frac{1 \text{ k}\Omega}{\alpha}}$$

Guess:  $V_{BE} = 0.7 \text{ V}$ ,  $I_c = 1.621 \text{ mA}$

check for  $V_{BE}$ :  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.740 \text{ V}$ , not 0.7, reiterate


$V_{BE} = 0.740 \text{ V}$ ,  $I_c = 1.59 \text{ mA}$

check for  $V_{BE}$ :  $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.740 \text{ V}$ , converged.

So  $I_c = 1.59 \text{ mA}$ ,  $g_m = 0.0612 \left(\frac{1}{\Omega}\right) \text{ S}$ ,  $\frac{1}{g_m} = 16.34 \Omega$ ,  
 $V_o = 3.14 \text{ k}\Omega$


71)

AC Analysis: (Include  $V_o$ )

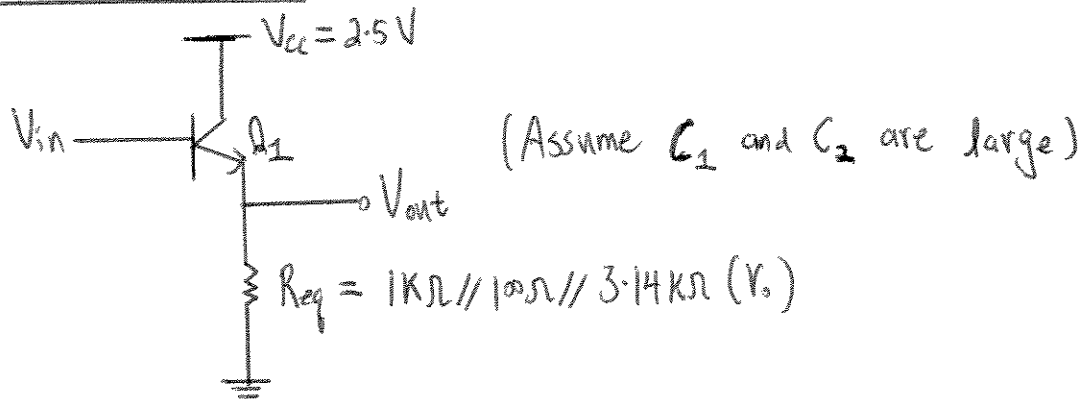

$$A_v = \frac{(1\text{k}\Omega // 100\Omega // 3.14\text{k}\Omega)}{16.34\Omega + (1\text{k}\Omega // 100\Omega // 3.14\text{k}\Omega)} = 0.84$$

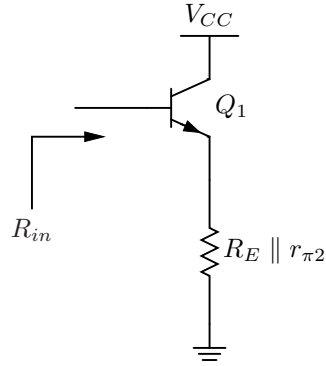- 5.72 (a) Looking into the base of  $Q_2$  we see an equivalent resistance of  $r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = r_{\pi 1} + (1 + \beta_1)(R_E \parallel r_{o1})$$

Looking into the collector of  $Q_2$  we see an equivalent resistance of  $r_{o2}$ . Thus,

$$R_{out} = R_C \parallel r_{o2}$$

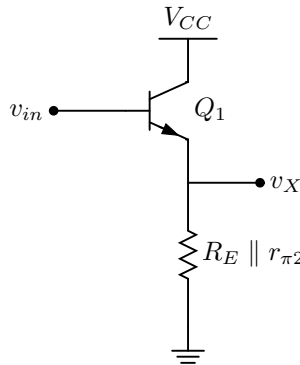- (b) Looking into the base of  $Q_2$  we see an equivalent resistance of  $r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $v_X/v_{in}$ :



$$\frac{v_X}{v_{in}} = \frac{R_E \parallel r_{\pi 2} \parallel r_{o1}}{\frac{1}{g_{m1}} + R_E \parallel r_{\pi 2} \parallel r_{o1}}$$


We can find  $v_{out}/v_X$  by inspection.

$$\frac{v_{out}}{v_X} = -g_{m2}(R_C \parallel r_{o2})$$

$$A_v = \frac{v_X}{v_{in}} \cdot \frac{v_{out}}{v_X}$$

$$= -g_{m2}(R_C \parallel r_{o2}) \frac{R_E \parallel r_{\pi 2} \parallel r_{o1}}{\frac{1}{g_{m1}} + R_E \parallel r_{\pi 2} \parallel r_{o1}}$$

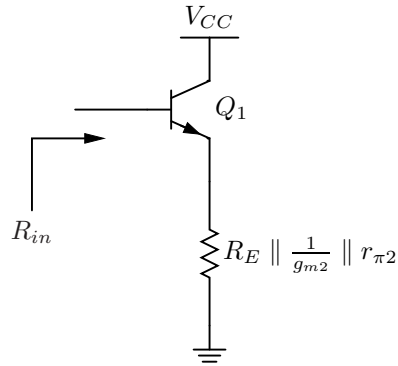- 5.73 (a) Looking into the emitter of  $Q_2$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $R_{in}$ :




$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left( R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

Looking into the collector of  $Q_2$ , we see an equivalent resistance of  $\infty$  (because  $V_A = \infty$ ), so we have

$$R_{out} = R_C$$

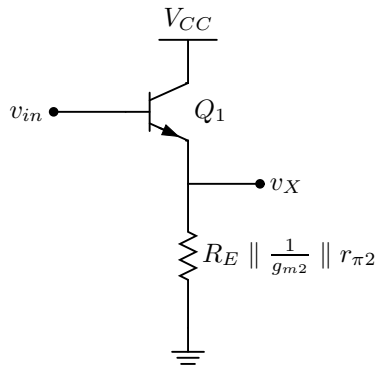- (b) Looking into the emitter of  $Q_2$  we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{\pi 2}$ , so we can draw the following equivalent circuit for finding  $v_X/v_{in}$ :



$$\frac{v_X}{v_{in}} = \frac{R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

We can find  $v_{out}/v_X$  by inspection.

$$\begin{aligned} \frac{v_{out}}{v_X} &= g_{m2} R_C \\ A_v &= \frac{v_X}{v_{in}} \cdot \frac{v_{out}}{v_X} \\ &= g_{m2} R_C \frac{R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}} \end{aligned}$$



$$\begin{aligned}
R_{out} &= R_C = \boxed{1 \text{ k}\Omega} \\
A_v &= -g_m R_C = -10 \\
g_m &= 10 \text{ mS} \\
I_C &= g_m V_T = 260 \text{ }\mu\text{A} \\
\frac{V_{CC} - V_{BE}}{R_B} &= I_B = \frac{I_C}{\beta} \\
R_B &= \beta \frac{V_{CC} - V_T \ln(I_C/I_S)}{I_C} \\
&= \boxed{694 \text{ k}\Omega} \\
R_{in} &= R_B \parallel r_\pi = 9.86 \text{ k}\Omega > 5 \text{ k}\Omega
\end{aligned}$$

In sizing  $C_B$ , we must consider the effect a finite impedance in series with the input will have on the circuit parameters. Any series impedance will cause  $R_{in}$  to increase and will not impact  $R_{out}$ . However, a series impedance can cause gain degradation. Thus, we must ensure that  $|Z_B| = \left| \frac{1}{j\omega C_B} \right|$  does not degrade the gain significantly.

If we include  $|Z_B|$  in the gain expression, we get:

$$A_v = -\frac{R_C}{\frac{1}{g_m} + \frac{(|Z_B|) \parallel R_B}{1+\beta}}$$

Thus, we want  $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$  to ensure the gain is not significantly degraded.

$$\begin{aligned}
\frac{1}{1+\beta} \left| \frac{1}{j\omega C_B} \right| &\ll \frac{1}{g_m} \\
\frac{1}{1+\beta} \frac{1}{2\pi f C_B} &= \frac{1}{10} \frac{1}{g_m} \\
C_B &= \boxed{788 \text{ nF}}
\end{aligned}$$

5.75

$$R_{out} = R_C \leq 500 \Omega$$

To maximize gain, we should maximize  $R_C$ .

$$\begin{aligned} R_C &= \boxed{500 \Omega} \\ V_{CC} - I_C R_C &\geq V_{BE} - 400 \text{ mV} = V_T \ln(I_C/I_S) - 400 \text{ mV} \\ I_C &\leq 4.261 \text{ mA} \end{aligned}$$

To maximize gain, we should maximize  $I_C$ .

$$\begin{aligned} I_C &= \boxed{4.261 \text{ mA}} \\ I_B &= \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE}}{R_B} \\ &= \frac{I_C}{\beta} = \frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} \\ R_B &= \boxed{40.613 \text{ k}\Omega} \end{aligned}$$

5.76

$$\begin{aligned}R_{out} &= R_C = \boxed{1 \text{ k}\Omega} \\|A_v| &= g_m R_C \\&= \frac{I_C R_C}{V_T} \\&\geq 20 \\I_C &\geq 520 \text{ }\mu\text{A}\end{aligned}$$

In order to maximize  $R_{in} = R_B \parallel r_\pi$ , we need to maximize  $r_\pi$ , meaning we should minimize  $I_C$  (since  $r_\pi = \frac{\beta V_T}{I_C}$ ).

$$\begin{aligned}I_C &= 520 \text{ }\mu\text{A} \\I_B &= \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE}}{R_B} \\&= \frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} \\R_B &= \boxed{343 \text{ k}\Omega}\end{aligned}$$

5.77

$$\begin{aligned}R_{out} &= R_C = \boxed{2 \text{ k}\Omega} \\A_v &= -g_m R_C \\&= -\frac{I_C R_C}{V_T} \\&= -15 \\I_C &= 195 \text{ }\mu\text{A} \\V_{BE} &= V_T \ln(I_C/I_S) = 689.2 \text{ mV} \\V_{CE} &\geq V_{BE} - 400 \text{ mV} = 289.2 \text{ mV}\end{aligned}$$

To minimize the supply voltage, we should minimize  $V_{CE}$ .

$$\begin{aligned}V_{CE} &= 289.2 \text{ mV} \\ \frac{V_{CC} - V_{CE}}{R_C} &= I_C \\ V_{CC} &= 679.2 \text{ mV}\end{aligned}$$

Note that this value of  $V_{CC}$  is less than the required  $V_{BE}$ . This means that the value of  $V_{CC}$  is constrained by  $V_{BE}$ , not  $V_{CE}$ . In theory, we could pick  $V_{CC} = V_{BE}$ , but in this case, we'd have to set  $R_B = 0 \text{ }\Omega$ , which would short the input to  $V_{CC}$ . Thus, let's pick a reasonable value for  $R_B$ ,  $R_B = \boxed{100 \text{ }\Omega}$ .

$$\begin{aligned}\frac{V_{CC} - V_{BE}}{R_B} &= I_B = \frac{I_C}{\beta} \\ V_{CC} &= \boxed{689.4 \text{ mV}}\end{aligned}$$

$$\begin{aligned} |A_v| &= g_m R_C \\ &= \frac{I_C R_C}{V_T} \\ &= A_0 \\ R_{out} &= R_C \\ A_0 &= \frac{I_C R_{out}}{V_T} \\ I_C &= \frac{A_0 V_T}{R_{out}} \\ P &= I_C V_{CC} \\ &= \boxed{\frac{A_0 V_T}{R_{out}} V_{CC}} \end{aligned}$$

Thus, we must trade off a small output resistance with low power consumption (i.e., as we decrease  $R_{out}$ , power consumption increases and vice-versa).

5.79

$$P = (I_B + I_C)V_{CC}$$

$$= \frac{1 + \beta}{\beta} I_C V_{CC}$$

$$= 1 \text{ mW}$$

$$I_C = 396 \text{ } \mu\text{A}$$

$$\frac{V_{CC} - V_{BE}}{R_B} = I_B = \frac{I_C}{\beta}$$

$$R_B = \beta \frac{V_{CC} - V_T \ln(I_C/I_S)}{I_C}$$


$$= \boxed{453 \text{ k}\Omega}$$

$$A_v = -g_m R_C$$

$$= -\frac{I_C R_C}{V_T}$$

$$= -20$$

$$R_C = \boxed{1.31 \text{ k}\Omega}$$

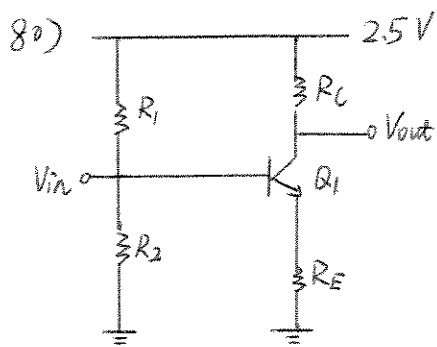

$$A_V = 5$$

$$R_{out} = R_c = 500\Omega$$

$$R_E I_c \approx 300\text{mV}$$

$$A_V = \frac{R_c I_c}{R_E I_c + V_T} = \frac{R_c I_c}{300 + 26} \Rightarrow R_c I_c = 1.63\text{V} \Rightarrow I_c = 3.26\text{mA}$$

$$R_E I_c \approx 300\text{mV} \Rightarrow R_E = 92\Omega$$

$$R_1 = \frac{2.5 - (V_{BE} + 0.3)}{10 I_B}, \quad V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.7624$$

$$10 I_B = 0.326\text{mA}$$

$$R_1 = \frac{2.5 - (0.7624 + 0.3)}{0.326} = 4.41\text{k}$$

$$R_2 = \frac{(0.7624 + 0.3)}{(9 \times 0.0326)} = 3.62\text{k}$$

$$V_{CE} = 2.5 - 1.63 - 0.3 = 0.57, \quad V_{BE} = 0.7624.$$

$Q_1$  is in soft saturation region, so active region characteristics

still apply.

$$R_c = 500\Omega$$

$$R_1 = 4.41\text{k}\Omega$$

$$R_2 = 3.62\text{k}\Omega$$

$$R_E = 92\Omega$$

$$\Rightarrow A_V = 5$$

$$R_{out} = 500\Omega$$

5.81

$$R_{out} = R_C \geq 1 \text{ k}\Omega$$

To maximize gain, we should maximize  $R_{out}$ .

$$\begin{aligned} R_C &= \boxed{1 \text{ k}\Omega} \\ V_{CC} - I_C R_C - I_E R_E &= V_{CE} \geq V_{BE} - 400 \text{ mV} \\ V_{CC} - I_C R_C - 200 \text{ mV} &\geq V_T \ln(I_C/I_S) - 400 \text{ mV} \\ I_C &\leq 1.95 \text{ mA} \end{aligned}$$

To maximize gain, we should maximize  $I_C$ .

$$\begin{aligned} I_C &= 1.95 \text{ mA} \\ I_E R_E &= \frac{1 + \beta}{\beta} I_C R_E = 200 \text{ mV} \\ R_E &= \boxed{101.5 \Omega} \\ V_{CC} - 10I_B R_1 - I_E R_E &= V_{BE} = V_T \ln(I_C/I_S) \\ R_1 &= \boxed{7.950 \text{ k}\Omega} \\ 9I_B R_2 - I_E R_E &= V_{BE} = V_T \ln(I_C/I_S) \\ R_2 &= \boxed{5.405 \text{ k}\Omega} \end{aligned}$$



$$\begin{aligned}
 P &= (10I_B + I_C)V_{CC} \\
 &= \left(10\frac{I_C}{\beta} + I_C\right)V_{CC} \\
 &= 5 \text{ mW}
 \end{aligned}$$

$$I_C = 1.82 \text{ mA}$$

$$I_E R_E = \frac{1 + \beta}{\beta} I_C R_E = 200 \text{ mV}$$

$$R_E = \boxed{109 \ \Omega}$$

$$\begin{aligned}
 A_v &= -\frac{R_C}{\frac{1}{g_m} + R_E} \\
 &= -\frac{R_C}{\frac{V_T}{I_C} + R_E} \\
 &= -5
 \end{aligned}$$

$$R_C = \boxed{616 \ \Omega}$$

$$V_{CC} - 10I_B R_1 - 200 \text{ mV} = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{8.54 \text{ k}\Omega}$$

$$9I_B R_2 - 200 \text{ mV} = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_2 = \boxed{5.79 \text{ k}\Omega}$$

$$R_{in} = \frac{1}{g_m} = 50 \, \Omega \text{ (since } R_E \text{ doesn't affect } R_{in}\text{)}$$

$$g_m = 20 \text{ mS}$$

$$I_C = g_m V_T = 520 \, \mu\text{A}$$

$$I_E R_E = \frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV}$$

$$R_E = \boxed{495 \, \Omega}$$

$$A_v = g_m R_C = 20$$

$$R_C = \boxed{1 \text{ k}\Omega}$$

$$V_{CC} - 10I_B R_1 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{29.33 \text{ k}\Omega}$$

$$9I_B R_2 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_2 = \boxed{20.83 \text{ k}\Omega}$$

To pick  $C_B$ , we must consider its effect on  $A_v$ . If we assume the capacitor has an impedance  $Z_B$  and  $|Z_B| \ll R_1, R_2$ , then we have:

$$A_v = \frac{R_C}{\frac{1}{g_m} + \frac{|Z_B|}{1+\beta}}$$

Thus, we should choose  $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$ .

$$\frac{1}{1+\beta} |Z_B| = \frac{1}{1+\beta} \frac{1}{2\pi f C_B} = \frac{1}{10} \frac{1}{g_m}$$

$$C_B = \boxed{1.58 \, \mu\text{F}}$$

$$R_{out} = R_C = \boxed{500 \Omega}$$

$$A_v = g_m R_C = 8$$

$$g_m = 16 \text{ mS}$$

$$I_C = g_m V_T = 416 \mu\text{A}$$

$$I_E R_E = \frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV}$$

$$R_E = \boxed{619 \Omega}$$

$$V_{CC} - 10I_B R_1 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{36.806 \text{ k}\Omega}$$

$$9I_B R_2 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_2 = \boxed{25.878 \text{ k}\Omega}$$

To pick  $C_B$ , we must consider its effect on  $A_v$ . If we assume the capacitor has an impedance  $Z_B$  and  $|Z_B| \ll R_1, R_2$ , then we have:

$$A_v = \frac{R_C}{\frac{1}{g_m} + \frac{|Z_B|}{1+\beta}}$$

Thus, we should choose  $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$ .

$$\frac{1}{1+\beta} |Z_B| = \frac{1}{1+\beta} \frac{1}{2\pi f C_B} = \frac{1}{10} \frac{1}{g_m}$$

$$C_B = \boxed{1.26 \mu\text{F}}$$

5.85

$$R_{out} = R_C = \boxed{200 \Omega}$$

$$A_v = g_m R_C = \frac{I_C R_C}{V_T} = 20$$

$$I_C = 2.6 \text{ mA}$$

$$P = V_{CC} (10I_B + I_C)$$

$$= V_{CC} \left( 10 \frac{I_C}{\beta} + I_C \right)$$

$$= \boxed{7.15 \text{ mW}}$$

$$\begin{aligned}
 P &= (I_C + 10I_B) V_{CC} \\
 &= \left( I_C + 10 \frac{I_C}{\beta} \right) V_{CC} \\
 &= 5 \text{ mW}
 \end{aligned}$$

$$I_C = 1.82 \text{ mA}$$

$$A_v = g_m R_C$$

$$= \frac{I_C R_C}{V_T}$$

$$= 10$$

$$R_C = \boxed{143 \Omega}$$

$$I_E R_E = \frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV}$$

$$R_E = \boxed{141.6 \Omega}$$

$$V_{CC} - 10I_B R_1 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{8.210 \text{ k}\Omega}$$

$$9I_B R_2 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_2 = \boxed{6.155 \text{ k}\Omega}$$

To pick  $C_B$ , we must consider its effect on  $A_v$ . If we assume the capacitor has an impedance  $Z_B$  and  $|Z_B| \ll R_1, R_2$ , then we have:

$$A_v = \frac{R_C}{\frac{1}{g_m} + \frac{|Z_B|}{1+\beta}}$$

Thus, we should choose  $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$ .

$$\frac{1}{1+\beta} |Z_B| = \frac{1}{1+\beta} \frac{1}{2\pi f C_B} = \frac{1}{10} \frac{1}{g_m}$$

$$C_B = \boxed{5.52 \mu\text{F}}$$

$$\begin{aligned}
R_{in} &= \frac{1}{g_m} = 50 \, \Omega \text{ (since } R_E \text{ doesn't affect } R_{in}\text{)} \\
g_m &= 20 \text{ mS} \\
I_C &= g_m V_T = 520 \, \mu\text{A} \\
A_v &= g_m R_C = 20 \\
R_C &= \boxed{1 \text{ k}\Omega} \\
I_E R_E &= \frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV} \\
R_E &= \boxed{495 \, \Omega}
\end{aligned}$$

To minimize the supply voltage, we should allow  $Q_1$  to operate in soft saturation, i.e.,  $V_{BC} = 400 \text{ mV}$ .

$$\begin{aligned}
V_{BE} &= V_T \ln(I_C/I_S) = 715 \text{ mV} \\
V_{CE} &= V_{BE} - 400 \text{ mV} = 315 \text{ mV} \\
V_{CC} - I_C R_C - I_E R_E &= V_{CE} \\
V_{CC} &= \boxed{1.095 \text{ V}} \\
V_{CC} - 10I_B R_1 - I_E R_E &= V_{BE} \\
R_1 &= \boxed{2.308 \text{ k}\Omega} \\
9I_B R_2 - I_E R_E &= V_{BE} \\
R_2 &= \boxed{20.827 \text{ k}\Omega}
\end{aligned}$$


To pick  $C_B$ , we must consider its effect on  $A_v$ . If we assume the capacitor has an impedance  $Z_B$  and  $|Z_B| \ll R_1, R_2$ , then we have:

$$A_v = \frac{R_C}{\frac{1}{g_m} + \frac{|Z_B|}{1+\beta}}$$

Thus, we should choose  $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$ .

$$\begin{aligned}
\frac{1}{1+\beta} |Z_B| &= \frac{1}{1+\beta} \frac{1}{2\pi f C_B} = \frac{1}{10} \frac{1}{g_m} \\
C_B &= \boxed{1.58 \, \mu\text{F}}
\end{aligned}$$

88)

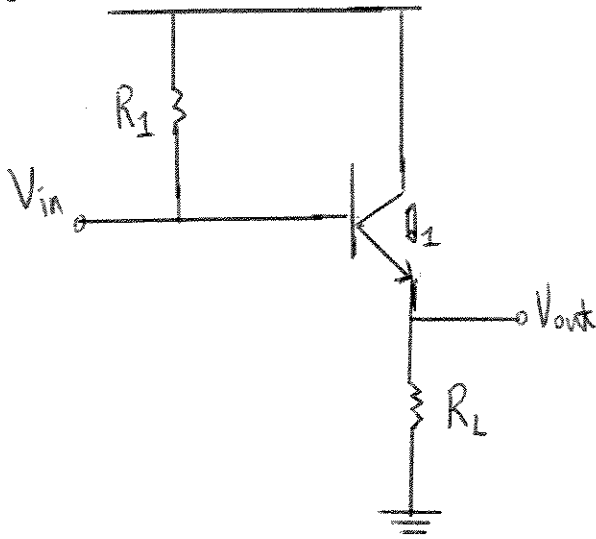

$$A_v = 0.85$$

$$R_{in} > 10\text{K}\Omega$$

$$R_L = 200\Omega$$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.85 \Rightarrow \frac{200}{200 + \frac{1}{g_m}} = 0.85$$

$$\Rightarrow 200 = 0.85 \left( 200 + \frac{1}{g_m} \right) \Rightarrow \frac{1}{g_m} = 35.294\Omega$$

$$\Rightarrow I_c = \frac{26\text{mV}}{35.294\Omega} = 0.737\text{mA}, \quad V_{BE} = V_T \ln\left(\frac{0.737}{6 \times 10^{-8}}\right) = 0.724\text{V}$$

$$R_{in} = R_1 \parallel (r_{\pi} + (1 + \beta)(200\Omega))$$

$$R_{in} = R_1 \parallel 23.73\text{K}$$

$$R_{in} = \frac{R_1 \cdot 23.73\text{K}}{R_1 + 23.73\text{K}} > 10\text{K} \Rightarrow R_1 > 17.28\text{K} \text{ (Input Impedance Requirement)}$$

To support an  $I_c$  of 0.737,  $R_1$  must be determined.

88)

$$R_1 = \frac{2.5 - (0.724 + (0.737)(0.2)/0.99)}{0.737 / 100}$$


$$R_1 = 220.77 \text{ k}\Omega$$

$$R_1 = 220.77 \text{ k}\Omega \Rightarrow R_{in} = 220.77 \text{ k}\Omega // 23.73 \text{ k}\Omega$$
$$R_{in} = 21.43 \text{ k}\Omega > 10 \text{ k}\Omega$$

$$\begin{array}{l} R_1 = 220.77 \text{ k}\Omega \\ R_L = 200 \Omega \end{array} \Rightarrow \begin{array}{l} A_v = 0.85 \\ R_{in} = 21.43 \text{ k}\Omega \end{array}$$



89)

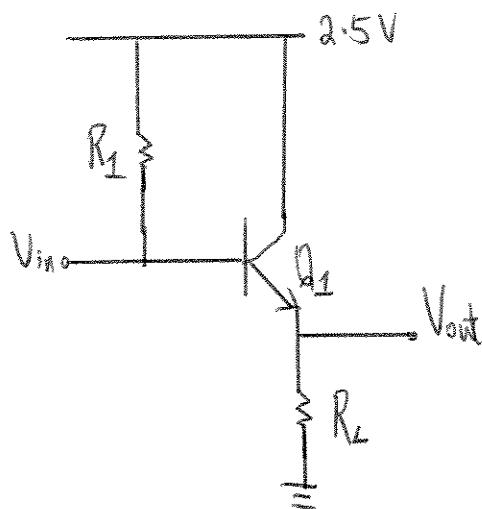

$$\text{Power} = 5 \text{ mW}$$

$$A_v = 0.9$$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.9 \Rightarrow R_L = 0.9 \left( R_L + \frac{1}{g_m} \right)$$

$$R_L = 9 \frac{1}{g_m}$$

$$\text{Power} = 2.5 \left( I_c + \frac{I_c}{\beta} \right) \Rightarrow I_c = 1.98 \text{ mA}$$

$$\frac{1}{g_m} = \frac{V_T}{I_c} = \frac{26 \text{ mV}}{1.98 \text{ mA}} = 13.13 \Omega$$

$$R_L = (9)(13.13) = 118.17 \Omega$$

This is the minimum load resistance, since anything lower will lower the voltage gain.

5.90 As stated in the hint, let's assume that  $I_E R_E \gg V_T$ . Given this assumption, we can assume that  $R_E$  does not affect the gain.

$$I_E R_E = 10V_T = 260 \text{ mV}$$

$$A_v = \frac{R_L}{\frac{1}{g_m} + R_L} = 0.8$$

$$g_m = 80 \text{ mS}$$

$$I_C = g_m V_T = 2.08 \text{ mA}$$

$$\frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV}$$

$$R_E = \boxed{124 \Omega}$$

$$V_{CC} - I_B R_1 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{71.6 \text{ k}\Omega}$$

To pick  $C_1$ , we must consider its effect on  $A_v$ . If we assume the capacitor has an impedance  $Z_1$  and  $|Z_1| \ll R_1$ , then we have:

$$A_v = \frac{R_E}{\frac{1}{g_m} + R_E + \frac{|Z_1|}{1 + \beta}}$$

Thus, we should choose  $\frac{1}{1 + \beta} |Z_1| \ll \frac{1}{g_m}$ .

$$\frac{1}{1 + \beta} |Z_1| = \frac{1}{1 + \beta} \frac{1}{2\pi f C_1} = \frac{1}{10} \frac{1}{g_m}$$


$$C_1 = \boxed{12.6 \text{ pF}}$$

To pick  $C_2$ , we must also consider its effect on  $A_v$ . Since the capacitor appears in series with  $R_L$ , we need to ensure that  $|Z_2| \ll R_L$ , assuming the capacitor has impedance  $Z_2$ .


$$|Z_2| = \frac{1}{2\pi f C_2} = \frac{1}{10} R_L$$

$$C_2 = \boxed{318 \text{ pF}}$$


1.

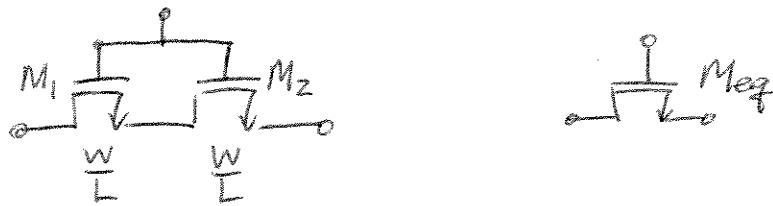

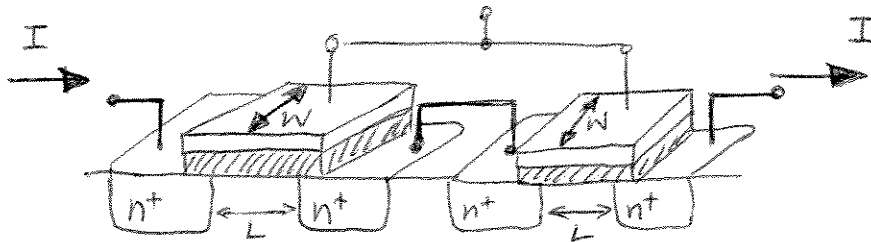Intuitively, this is similar to having twice of the original channel length:



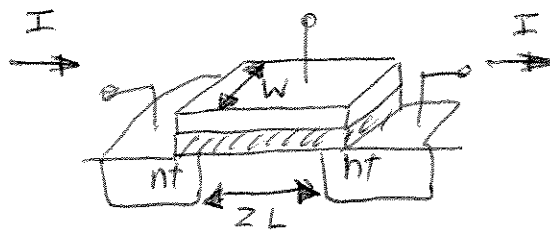
Since current flowing into either non-gate terminals must come out at the other terminal (KCL) and the intermediate node is equipotential, this is as if we have a  $M_{eq}$  with width  $W$  & length  $2L$ :



This approximation can simplify a lot of calculations.

2. A key point to remember: the charge density APPROACHES zero (not EQUALS) at pinch-off. In other words,  $Q$  is never exactly equal to zero (albeit very close.) Another way to view this phenomenon is by observing  $I = Q \cdot v$ : recognize that  $v$  is finite. Since we get some finite value of  $I$  at pinch-off, we expect  $Q \neq 0$ .

Consider the following:

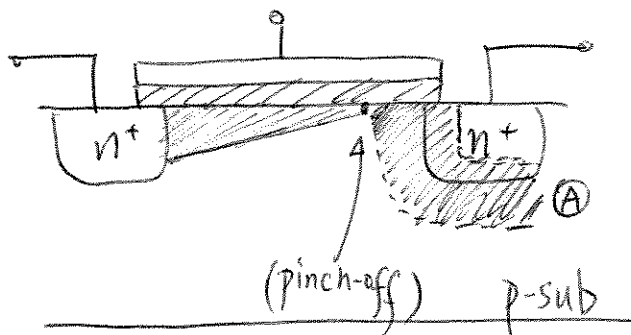

The shaded region,  $\textcircled{A}$ , represents a reverse-biased pn junction. Just as a diode, there exist minority

profiles on p & n sides, which  $\neq 0$ .

Pinch-off implies that the depletion region created no longer has free carriers. The depletion still sweeps all electrons from inversion channel to drain.

3. Given :  $C_{ox} = 10 \text{ fF}/\mu\text{m}^2$      $W = 5 \mu\text{m}$      $L = 0.1 \mu\text{m}$   
 $V_{GS} - V_{TH} = 1 \text{ V}$      $V_{DS} = 0$


Find : total charge stored in channel,  $Q_{tot}$

$$Q_{tot} = W C_{ox} (V_{GS} - V_{TH}) L$$

$$= (5 \mu\text{m})(10 \text{ fF}/\mu\text{m}^2)(1 \text{ V})(0.1 \mu\text{m}) = 5 \text{ fC}$$

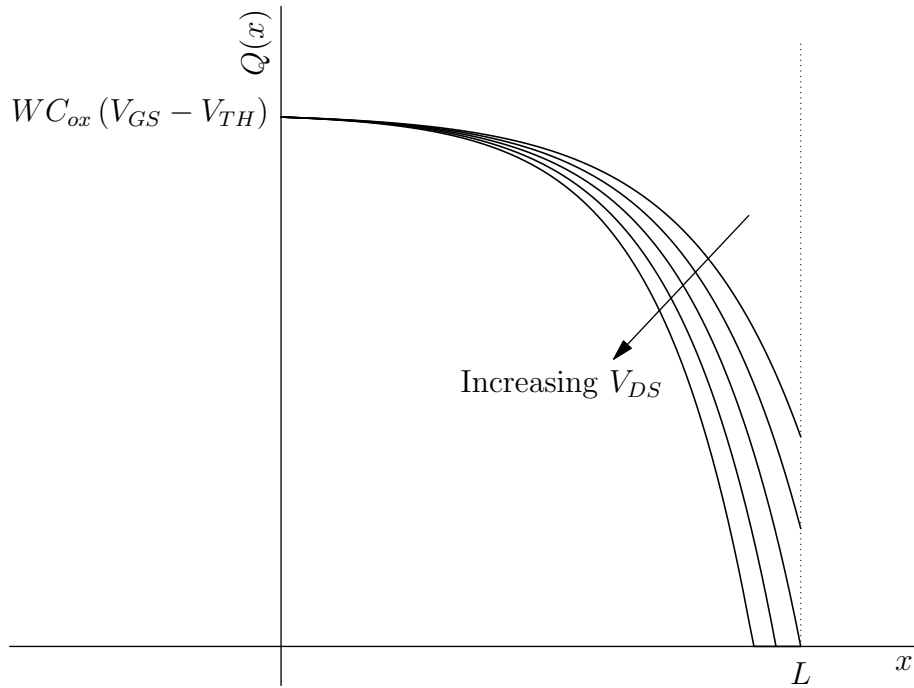6.4 (a)


$$\begin{aligned}
 Q(x) &= WC_{ox}(V_{GS} - V(x) - V_{TH}) \\
 &= WC_{ox}(V_{GS} - V_{TH}) - WC_{ox}V(x)
 \end{aligned}$$



The curve that intersects the axis at  $x = L$  (i.e., the curve for which the channel begins to pinch off) corresponds to  $V_{DS} = V_{GS} - V_{TH}$ .

(b)
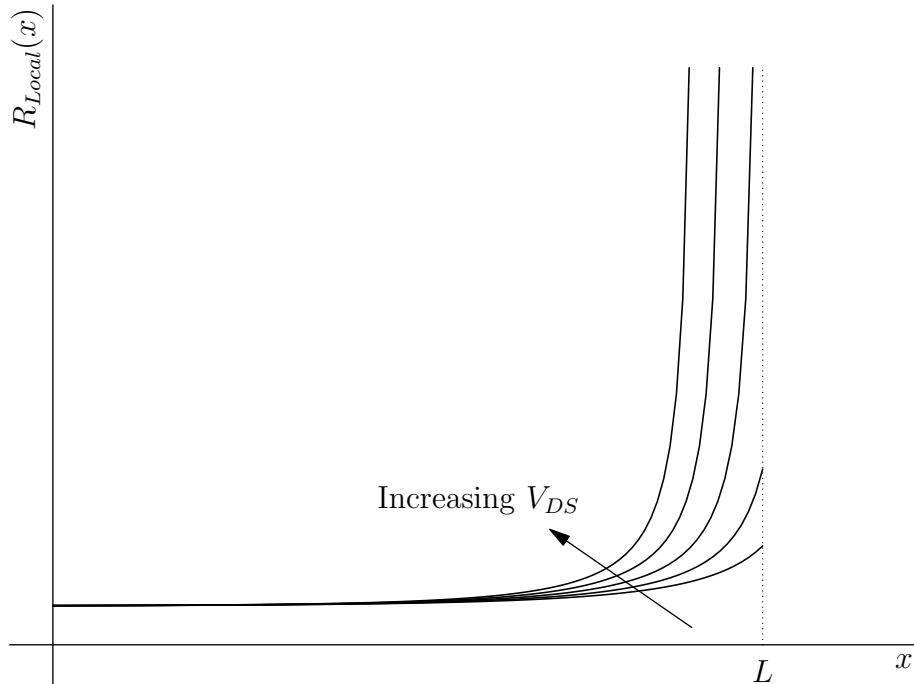
$$R_{Local}(x) \propto \frac{1}{\mu Q(x)}$$



Note that  $R_{Local}$  diverges at  $x = L$  when  $V_{DS} = V_{GS} - V_{TH}$ .

$$5. \quad I_D = W C_{ox} [V_{GS} - V(x) - V_{TH}] \mu_n \frac{dV(x)}{dx}$$

$$\text{Define: } A = \frac{I_D}{W C_{ox} \mu_n}, \quad B = V_{GS} - V_{TH}$$

$$\Rightarrow A = (B - V) \frac{dV}{dx} = \frac{d}{dx} \left( BV - \frac{V^2}{2} \right)$$

Integrating  $A = \frac{d}{dx} (BV - V^2/2)$  gives:

$$Ax = BV - V^2/2 \Rightarrow V^2 - 2BV + 2Ax = 0$$

Using quadratic formula:


$$\begin{aligned} V_{+,-} &= \frac{2B \pm \sqrt{4B^2 - 4 \cdot 2A \cdot x}}{2} = B \pm \sqrt{B^2 - 2Ax} \\ &= B \left( 1 \pm \sqrt{1 - 2 \left( \frac{A}{B^2} \right) x} \right) \end{aligned}$$

$$= (V_{GS} - V_{TH}) \left\{ 1 \pm \sqrt{1 - \left[ 2 \cdot \frac{I_D}{W C_{ox} \mu_n (V_{GS} - V_{TH})^2} \right] x} \right\}$$

We know that  $0 \leq V(x) \leq V_{GS} - V_{TH}$  (pinch-off), and the term inside the square root is  $> 0$ . Therefore, we take  $V_-$  as the solution.



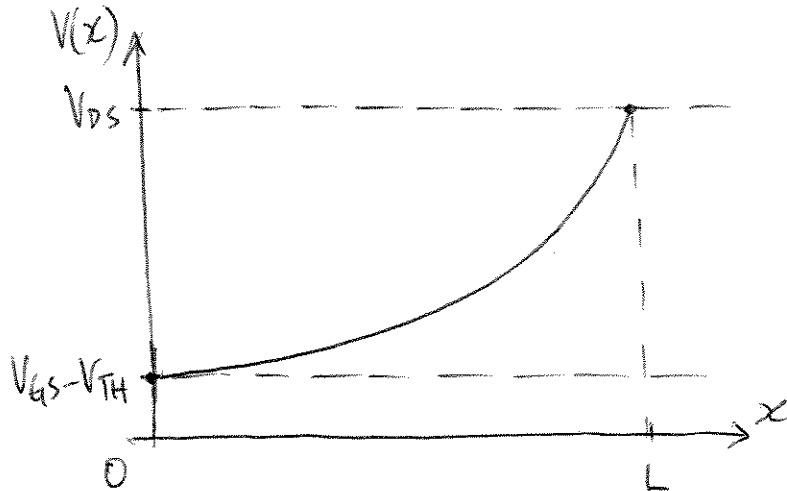
$$\text{i.e. } V(x) = (V_{GS} - V_{TH}) \left\{ 1 - \sqrt{1 - \left[ \frac{2I_D}{WCoxLn(V_{GS} - V_{TH})^2} \right] x} \right\}$$



$\because I_D \propto W$   
 $\Rightarrow V(x)$  is independent of  $W$ .
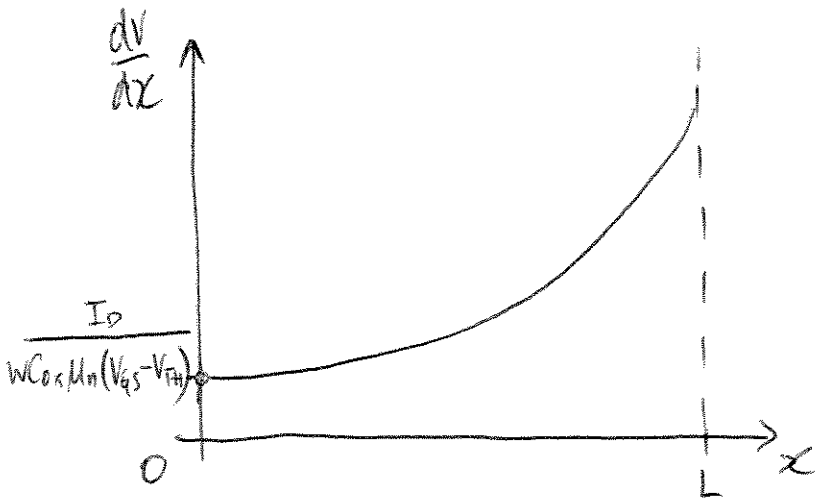
$$\frac{dV}{dx} = \frac{I_D}{WCoxLn(V_{GS} - V_{TH})} \cdot \left[ 1 - \frac{2I_D \cdot x}{WCoxLn(V_{GS} - V_{TH})^2} \right]^{-\frac{1}{2}}$$



6. No.

By varying  $V_{GS} - V_{TH}$  &  $V_{DS}$ , we can only obtain  $\mu_n C_{ox} \frac{W}{L}$ , but not  $\mu_n C_{ox}$  &  $\frac{W}{L}$

individually.

7. Given : NMOS  $I_D = 1 \text{ mA}$   $V_{GS} - V_{TH} = 0.6 \text{ V}$   
 $I_D = 1.6 \text{ mA}$   $V_{GS} - V_{TH} = 0.8 \text{ V}$   
(triode region)  $\mu_n C_{ox} = 200 \frac{\text{mA}}{\text{V}^2}$

Find  $V_{DS}$  &  $W/L$ .

$$1 \text{ mA} = \mu_n C_{ox} \frac{W}{L} \left[ (0.6) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{--- ①}$$

$$1.6 \text{ mA} = \mu_n C_{ox} \frac{W}{L} \left[ (0.8) V_{DS} - \frac{V_{DS}^2}{2} \right] \quad \text{--- ②}$$

$$\text{②} \div \text{①} : 1.6 = \frac{0.8 V_{DS} - \frac{V_{DS}^2}{2}}{0.6 V_{DS} - \frac{V_{DS}^2}{2}} = \frac{1.6 - V_{DS}}{1.2 - V_{DS}}$$

$$\Rightarrow V_{DS} = \frac{1.6(0.2)}{0.6} \approx 0.533 \text{ V}$$

$$\begin{aligned} \Rightarrow \frac{W}{L} &= \frac{I_D}{\mu_n C_{ox} \left[ (V_{GS} - V_{TH}) V_{DS} - \frac{V_{DS}^2}{2} \right]} \\ &= \frac{1 \text{ mA}}{200 \frac{\text{mA}}{\text{V}^2} \left[ (0.6 \text{ V})(0.533 \text{ V}) - \frac{(0.533 \text{ V})^2}{2} \right]} \\ &\approx 28. \end{aligned}$$

$$8. \quad I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH}) V_{DS} - V_{DS}^2]$$

$$g_m \triangleq \frac{\partial I_D}{\partial V_{GS}} = \frac{1}{2} \mu C_{ox} \frac{W}{L} \cdot 2 V_{DS} = \mu C_{ox} \frac{W}{L} V_{DS}$$

$$g_m |_{V_{DS}=0} = 0.$$

Intuitively, when  $V_{GS} > V_{TH}$ , mobile charges (channel) become available. This determines the on-resistance. But since there is no  $I_D$  ( $\because V_{DS}=0$ ), it does not matter if there is an incremental change in  $V_{GS}$  (i.e.  $\partial V_{GS}$ ). Since varying  $V_{GS}$  gives no change in  $I_D$ ,  $g_m |_{V_{DS}=0} = 0$ .

9. Given:  $V_{DD} = 1.8 \text{ V}$       $\frac{W}{L} = 20$       $\mu_n C_{ox} = 200 \frac{\mu\text{A}}{\text{V}^2}$   
 $V_{TH} = 0.4 \text{ V}$

Find minimum-on resistance.

$$R_{on} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})}$$
$$= \frac{1}{\left(200 \frac{\mu\text{A}}{\text{V}^2}\right) (20) (1.8 - 0.4) \text{ V}} = 179. \Omega$$

$$10. \quad 500 = \frac{1}{\mu_n C_{ox} \frac{W}{L} (1 - V_{TH})}$$

$$400 = \frac{1}{\mu_n C_{ox} \frac{W}{L} (1.5 - V_{TH})}$$

For the same NMOS,  $\mu_n C_{ox}$  &  $\frac{W}{L}$  are fixed

$$\Rightarrow 500(1 - V_{TH}) \stackrel{?}{=} 400(1.5 - V_{TH})$$
$$500(0.6) \neq 400(1.1)$$

$\therefore$  This is not possible.

$$11. \quad I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2]$$

$$r_{DS, tri} \triangleq \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \left[ \frac{\partial}{\partial V_{DS}} \left\{ \frac{1}{2} \mu C_{ox} \frac{W}{L} [2(V_{GS} - V_{TH})V_{DS} - V_{DS}^2] \right\} \right]^{-1}$$

$$= \left[ \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) - \mu C_{ox} \frac{W}{L} V_{DS} \right]^{-1}$$

$$= \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH} - V_{DS})}$$

12. When MOS operates as a resistor,

$$R_{on} = \frac{1}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$


$$\Rightarrow \tau = R_{on} C_{GS} = \frac{WL C_{ox}}{\mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})} = \frac{L^2}{\mu (V_{GS} - V_{TH})}$$

To minimize the time constant,

- 1) use minimum channel length, and
- 2) maximize overdrive voltage.




13.

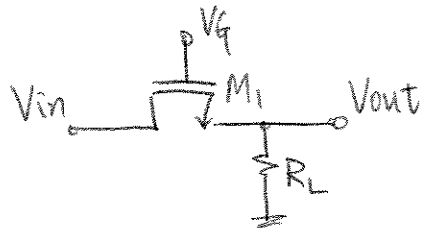

Given  $V_{in} \approx 0$   
 $V_g = 1.8 \text{ V}$   
 $R_L = 100 \Omega$

Find  $\frac{W}{L}$  such that signal output attenuates by only 5%.

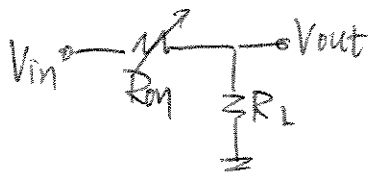$V_{in} \approx 0$  implies that we can approximate  $M_1$  as a linear resistance controlled by  $V_g$ . Therefore, the equivalent circuit becomes a resistive divider:



$$V_{out} = 0.95 V_{in}$$


$$= \frac{R_L}{R_{on} + R_L} V_{in}$$

$$\Rightarrow R_{on} \approx 5.3 \Omega$$

$$\therefore \frac{W}{L} = \frac{1}{\mu C_{ox} (V_{gs} - V_{th}) R_{on}} \approx \frac{1}{200 \frac{\mu\text{A}}{\text{V}^2} (1.8 - 0.4)(5.352)}$$

$$= 674.$$

14.

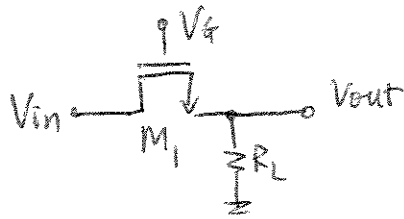

$V_0 \sim \text{few mV.}$

(a)  $V_{in} = V_0 \cos \omega t$        $V_{out} = 0.95 (V_0 \cos \omega t)$

$$V_{out} = \frac{R_L}{R_{on} + R_L} V_{in} \quad \Rightarrow \quad \frac{R_L}{R_{on} + R_L} = 0.95 V_0$$

$$R_{on} = \frac{R_L}{0.95 V_0} = \frac{1}{\left(\frac{0.95 V_0}{1 - 0.95 V_0}\right) \mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})}$$


$$\therefore \frac{W}{L} = \frac{0.95 V_0 / (1 - 0.95 V_0)}{\mu_n C_{ox} R_L (V_G - V_{TH})}$$

(b)  $V_{out} = 0.95 V_{in} = 0.95 (V_0 \cos \omega t + 0.5)$   
 $\approx 0.95 \times 0.5 = 0.475$   
 ( $\because V_0$  is relatively small)

$$\therefore R_{on} = \frac{R_L}{0.9} = \frac{1}{\mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})}$$

$$\Rightarrow \frac{W}{L} = \frac{0.9}{\mu_n C_{ox} R_L (V_G - V_{TH})}$$

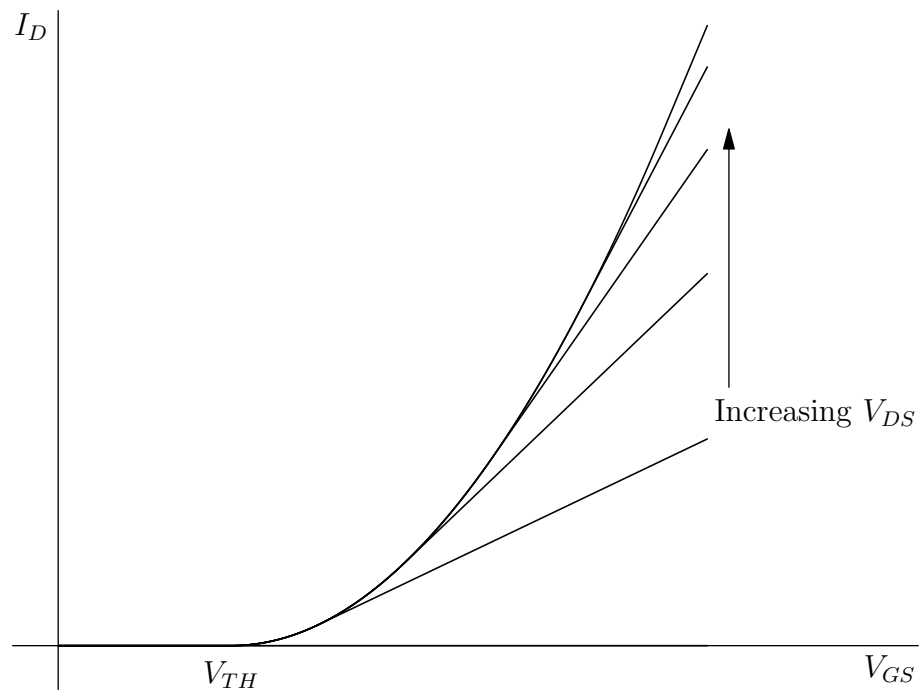Results show that if there is no DC voltage as input, the  $R_{on}$  varies with changing sinewave. With a DC bias voltage,  $R_{on}$  becomes more stable (independent of  $V_o$ ).



Initially, when  $V_{GS}$  is small, the transistor is in cutoff and no current flows. Once  $V_{GS}$  increases beyond  $V_{TH}$ , the curves start following the square-law characteristic as the transistor enters saturation. However, once  $V_{GS}$  increases past  $V_{DS} + V_{TH}$  (i.e., when  $V_{DS} < V_{GS} - V_{TH}$ ), the transistor goes into triode and the curves become linear. As we increase  $V_{DS}$ , the transistor stays in saturation up to larger values of  $V_{GS}$ , as expected.

16. The peak of the parabola signifies pinch-off (i.e.  $V_{DS} = V_{GS} - V_{TH}$ ). This means that (with  $\lambda = 0$ )  $I_D$  cannot be increased further by increasing  $V_{DS}$ . Since this curve must be continuous, the peak  $I_D$  must originate from the peak of the parabola.

6.17

$$\begin{aligned} I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^\alpha, \quad \alpha < 2 \\ g_m &\triangleq \frac{\partial I_D}{\partial V_{GS}} \\ &= \frac{\alpha}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^{\alpha-1} \\ &= \boxed{\frac{\alpha I_D}{V_{GS} - V_{TH}}} \end{aligned}$$

$$18. \quad I_D = W C_{ox} (V_{GS} - V_{TH}) v_{SAT}$$

$$g_m \triangleq \frac{\partial I_D}{\partial V_{GS}} = W C_{ox} v_{SAT}$$

19. (a) OFF  $\because V_{GS} = 0$

(b) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(c) TRIODE (LINEAR)  $\because V_{GS} > V_{TH}$  &  
 $V_{DS} \ll 2(V_{GS} - V_{TH})$

(d) TRIODE  $\because V_{GS} > V_{TH}$  &  $V_{DS} < V_{GS} - V_{TH}$   
(REMEMBER: MOSFET IS SYMMETRIC)

(e) TRIODE  $\because V_{GS} > V_{TH}$  &  $V_{DS} < V_{GS} - V_{TH}$

(f) OFF  $\because V_{GS} = 0$

(g) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(h) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

(i) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$



20. (a) OFF  $\because V_{GS} = 0$  ( $V_{GS} < V_{TH}$ )

(b) OFF  $\because V_{GS} = 0$  ( $V_{GS} < V_{TH}$ )


(c) TRIODE (LINEAR)  $\because V_{GS} > V_{TH}$  &  
 $V_{DS} \ll 2(V_{GS} - V_{TH})$

(d) SATURATION  $\because V_{GS} > V_{TH}$  &  $V_{DS} > V_{GS} - V_{TH}$

6.21 Since they're being used as current sources, assume  $M_1$  and  $M_2$  are in saturation for this problem. To find the maximum allowable value of  $\lambda$ , we should evaluate  $\lambda$  when  $0.99I_{D2} = I_{D1}$  and  $1.01I_{D2} = I_{D1}$ , i.e., at the limits of the allowable values for the currents. However, note that for any valid  $\lambda$  (remember,  $\lambda$  should be non-negative), we know that  $I_{D2} > I_{D1}$  (since  $V_{DS2} > V_{DS1}$ ), so the case where  $1.01I_{D2} = I_{D1}$  (which implies  $I_{D2} < I_{D1}$ ) will produce an invalid value for  $\lambda$  (you can check this yourself). Thus, we need only consider the case when  $0.99I_{D2} = I_{D1}$ .

$$\begin{aligned}
 0.99I_{D2} &= 0.99 \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda V_{DS2}) \\
 &= I_{D1} \\
 &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda V_{DS1}) \\
 0.99(1 + \lambda V_{DS2}) &= 1 + \lambda V_{DS1} \\
 \lambda &= \boxed{0.02 \text{ V}^{-1}}
 \end{aligned}$$

22.

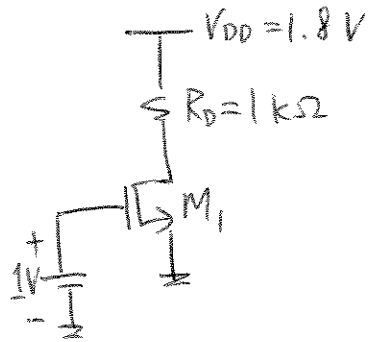

$$\lambda = 0, V_{TH} = 0.4 \text{ V}$$

$$\mu_n C_{ox} = 200 \frac{\mu\text{A}}{\text{V}^2}$$

$M_1$  sits at the edge of saturation when  $V_{DS} = V_{GS} - V_{TH}$ .

$$\Rightarrow V_{DS, \text{edge}} = (1 - 0.4) \text{ V} = 0.6 \text{ V}$$

$$\text{By KCL, } I_{D1} = I_{R_D} = \frac{V_{DD} - V_{DS}}{R_D} = \frac{1.2 \text{ V}}{1 \text{ k}\Omega} = 1.2 \text{ mA}$$

$$\therefore I_{D1} = 1.2 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$\Rightarrow \frac{W}{L} = \frac{2 I_{D1}}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} = \frac{2 (1.2 \text{ mA})}{\left(200 \frac{\mu\text{A}}{\text{V}^2}\right) (1 - 0.4)^2 \text{ V}^2}$$

$$\approx 33.$$

23. If gate oxide thickness,  $t_{ox}$ , doubles, the corresponding capacitance,  $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$ , is halved.

$\Rightarrow \mu_n C_{ox}$  is also halved


$\Rightarrow I_{D_1}$  is halved  $\Rightarrow V_{DS}$  increases

$\Rightarrow M_1$  stays in saturation ( $V_{DS} > V_{GS} - V_{TH}$ )

$$I_{D_1} = \frac{1.2 \text{ mA}}{2} = 0.6 \text{ mA}$$

$$\Rightarrow V_{DS} = (1.8 \text{ V}) - (0.6 \text{ mA})(1 \text{ k}\Omega) = 1.2 \text{ V}$$

24.

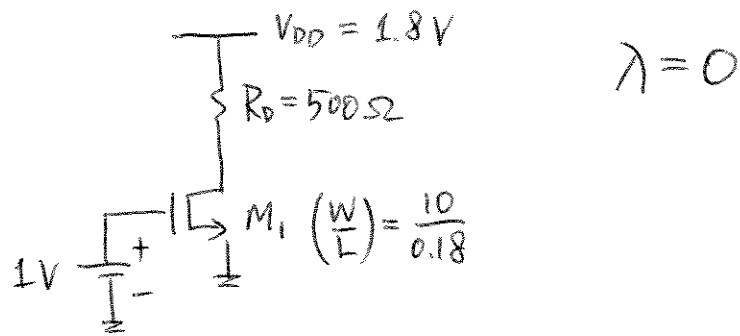

To avoid triode region,  $V_{DS} \geq V_{GS} - V_{TH}$ .

$$\Rightarrow V_{DS} \geq 1 - 0.4 = 0.6 \text{ V}$$


$$\begin{aligned} \Rightarrow I_{D1} &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ &= \frac{1}{2} \left( 200 \frac{\mu\text{A}}{\text{V}^2} \right) \left( \frac{10}{0.18} \right) (0.6)^2 = 2 \text{ mA} \end{aligned}$$

By KCL,  $\frac{V_{DD} - V_{DS}}{R_D} = 2 \text{ mA}$

$$\therefore V_{DD} = (2 \text{ mA})(500 \Omega) + 0.6 \text{ V} = 1.6 \text{ V}$$

Minimum  $V_{DD} = 1.6 \text{ V}$

25.

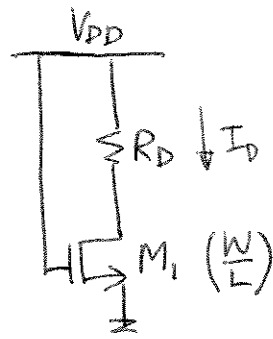


$$\lambda = 0$$

When  $M_1$  operates at the edge of saturation,  $V_{DS} = V_{GS} - V_{TH}$ . Also, by KCL:

$$I_{R_D} = I_{D_1} \Rightarrow \frac{V_{DD} - (V_{DD} - V_{TH})}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})^2$$

$$\therefore V_{TH} = R_D \cdot \underbrace{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})^2}_{I_D}$$

26.

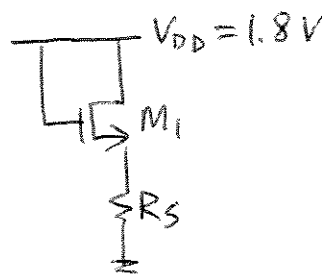

$$\lambda = 0$$

Find  $\left(\frac{W}{L}\right)$  with bias current =  $I_1$ .

Since  $V_{DS} = V_{GS}$  for  $M_1$ , this device always operates in saturation region (given  $V_{GS} > V_{TH}$ ).

By KCL,  $I_1 = I_{RS}$ ; by Ohm's law,  $V_S = I_1 R_S$

$$\Rightarrow \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - I_1 R_S - V_{TH})^2 = I_1$$

$$\therefore \frac{W}{L} = \frac{2 I_1}{\mu_n C_{ox} (V_{DD} - I_1 R_S - V_{TH})^2}$$

$$\begin{aligned}
V_{DD} - I_D R_D &= V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \\
\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}} &= (V_{DD} - V_{TH} - I_D R_D)^2 \\
I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[ (V_{DD} - V_{TH})^2 - 2I_D R_D (V_{DD} - V_{TH}) + I_D^2 R_D^2 \right]
\end{aligned}$$

We can rearrange this to the standard quadratic form as follows:

$$\left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D^2 \right) I_D^2 - \left( \mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1 \right) I_D + \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - V_{TH})^2 = 0$$



Applying the quadratic formula, we have:

$$\begin{aligned}
I_D &= \frac{(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1) \pm \sqrt{(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1)^2 - 4 \left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) \right)^2}}{2 \left( \frac{1}{2} \mu_n C_{ox} \frac{W}{L} R_D^2 \right)} \\
&= \frac{\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1 \pm \sqrt{(\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1)^2 - (\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}))^2}}{\mu_n C_{ox} \frac{W}{L} R_D^2} \\
&= \boxed{\frac{\mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH}) + 1 \pm \sqrt{1 + 2 \mu_n C_{ox} \frac{W}{L} R_D (V_{DD} - V_{TH})}}{\mu_n C_{ox} \frac{W}{L} R_D^2}}
\end{aligned}$$



Note that mathematically, there are two possible solutions for  $I_D$ . However, since  $M_1$  is diode-connected, we know it will either be in saturation or cutoff. Thus, we must reject the value of  $I_D$  that does not match these conditions (for example, a negative value of  $I_D$  would not match cutoff or saturation, so it would be rejected in favor of a positive value).





28. (a)

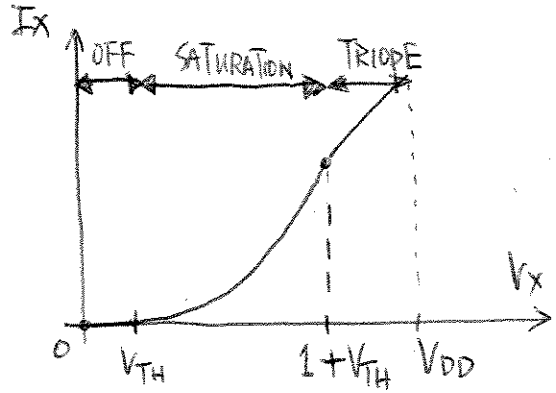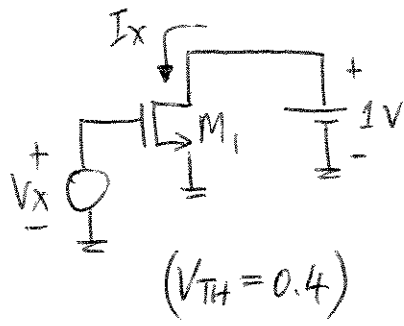



(b)

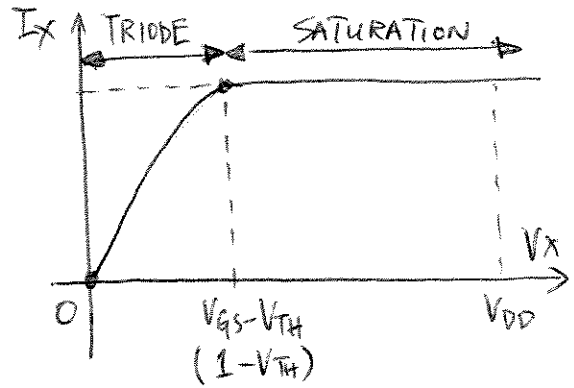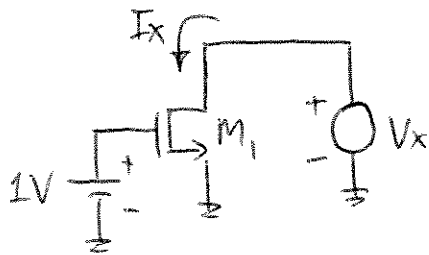


(c)

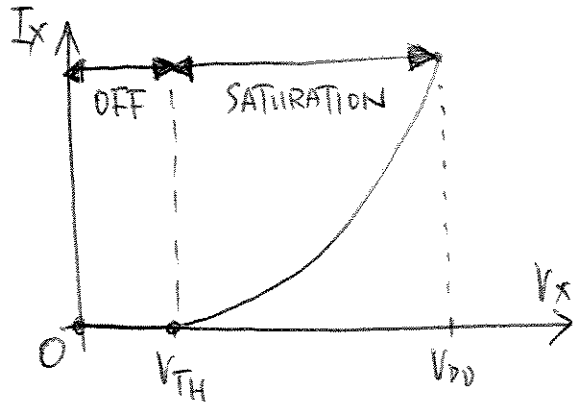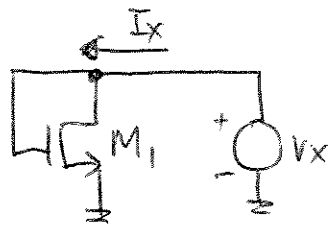

(d)

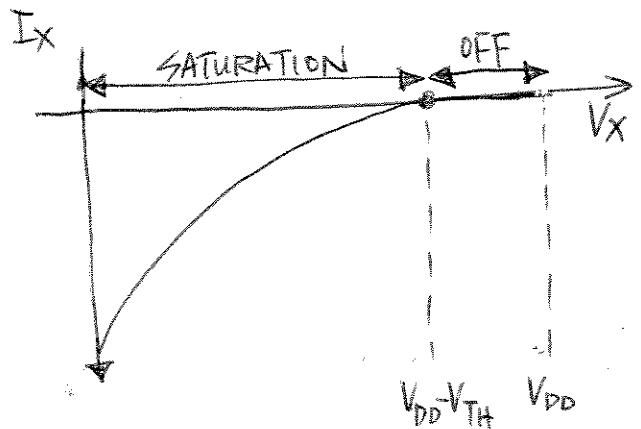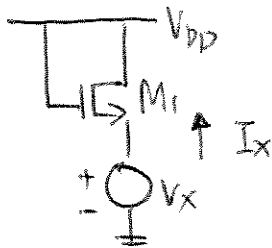

29.

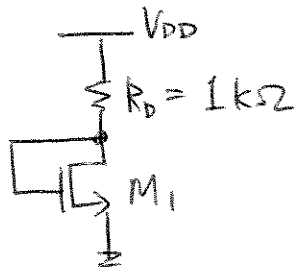

$$\left(\frac{W}{L}\right) = \frac{10}{0.18}, \quad \lambda = 0.1 \text{ V}^{-1}$$

Find  $I_{D1}$ 

Since  $M_1$  is diode-connected, it operates in saturation.


$$\text{By KCL, } \frac{V_{DD} - V_G}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_G - V_{TH})^2 (1 + \lambda V_G)$$

One can solve this by (1) using a graphing calculator, (2) trial-and-error, (3) or iteratively finding  $V_G$ .

Using any method gives  $V_G \approx 0.807 \text{ V}$

$$\Rightarrow I_D = \frac{V_{DD} - V_G}{R_D} \approx 1 \text{ mA}$$

30.

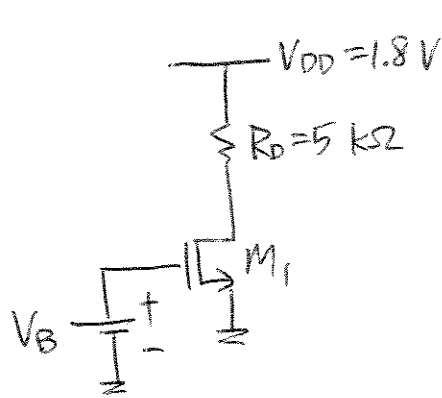

$$\frac{W}{L} = \frac{20}{0.18}, \quad \lambda = 0.1 \text{ V}^{-1}$$

At the edge of saturation,

$$I_{D1} = \frac{V_{DD} - (V_B - V_{TH})}{R_D} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_B - V_{TH})^2 (1 + \lambda(V_B - V_{TH}))$$

This equation can be solved by using a graphing calculator, special programs, or iteratively.

Using any method gives  $V_B \approx 0.57 \text{ V}$   
 $(I_D \approx 0.33 \text{ mA})$

31. An NMOS device with  $\lambda = 0$  must provide a transconductance of  $\frac{1}{50} \frac{1}{\Omega}$ .

(a) Given  $I_D = 0.5 \text{ mA}$ , find  $W/L$ .

$$g_m = \frac{1}{50} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\Rightarrow \frac{W}{L} = \frac{g_m^2}{2 \mu_n C_{ox} I_D} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right)^2}{2 \left(\frac{200 \mu\text{A}}{\text{V}^2}\right) (0.5 \text{ mA})} \approx 2000$$

(b) Given  $V_{GS} - V_{TH} = 0.5 \text{ V}$ , find  $W/L$ .

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$\Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{GS} - V_{TH})} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right)}{\left(\frac{200 \mu\text{A}}{\text{V}^2}\right) (0.5 \text{ V})} \approx 200$$

(c) Given  $V_{GS} - V_{TH} = 0.5 \text{ V}$ , find  $I_D$ .

$$\Rightarrow I_D = \frac{g_m (V_{GS} - V_{TH})}{2} = \frac{\left(\frac{1}{50} \frac{1}{\Omega}\right) (0.5 \text{ V})}{2} \approx 5 \text{ mA}$$

$$32. (a) \quad g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \quad (I_D \text{ constant})$$

Doubling  $(W/L)$  implies a  $\sqrt{2}$  times increase in  $g_m$ :  $g_{m_{NEW}} = \sqrt{2 \mu_n C_{ox} (2 \frac{W}{L}) I_D} = \sqrt{2} g_m$ .

$$(b) \quad g_m = \frac{2 I_D}{V_{GS} - V_{TH}} \quad (I_D \text{ constant})$$

Doubling  $(V_{GS} - V_{TH})$  decreases  $g_m$  by half:

$$g_{m_{NEW}} = \frac{2 I_D}{2(V_{GS} - V_{TH})} = \frac{1}{2} g_m$$

$$(c) \quad g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \quad (W/L \text{ constant})$$

Doubling  $I_D$  increases  $g_m$  by  $\sqrt{2}$  times.

$$(d) \quad g_m = \frac{2 I_D}{V_{GS} - V_{TH}} \quad (V_{GS} - V_{TH} \text{ constant})$$

Doubling  $I_D$  increases  $g_m$  by 2 times.

6.33 (a) Assume  $M_1$  is operating in saturation.

$$V_{GS} = 1 \text{ V}$$


$$V_{DS} = V_{DD} - I_D R_D = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS}) R_D$$

$$V_{DS} = 1.35 \text{ V} > V_{GS} - V_{TH}, \text{ which verifies our assumption}$$

$$I_D = 4.54 \text{ mA}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \boxed{13.333 \text{ mS}}$$
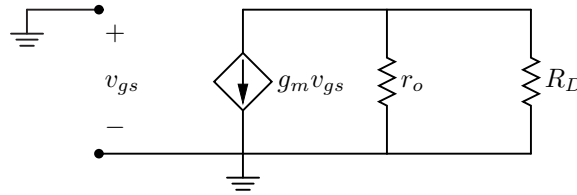
$$r_o = \frac{1}{\lambda I_D} = \boxed{2.203 \text{ k}\Omega}$$



(b) Since  $M_1$  is diode-connected, we know it is operating in saturation.


$$V_{GS} = V_{DS} = V_{DD} - I_D R_D = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS}) R_D$$

$$V_{GS} = V_{DS} = 0.546 \text{ V}$$

$$I_D = 251 \text{ }\mu\text{A}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \boxed{3.251 \text{ mS}}$$
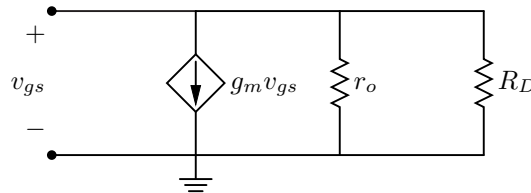
$$r_o = \frac{1}{\lambda I_D} = \boxed{39.881 \text{ k}\Omega}$$




(c) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$I_D = 1 \text{ mA}$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \boxed{6.667 \text{ mS}}$$
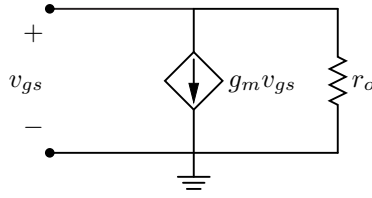
$$r_o = \frac{1}{\lambda I_D} = \boxed{10 \text{ k}\Omega}$$



(d) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$V_{GS} = V_{DS}$$


$$V_{DD} - V_{GS} = I_D(2 \text{ k}\Omega) = \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS}) (2 \text{ k}\Omega)$$

$$V_{GS} = V_{DS} = 0.623 \text{ V}$$

$$I_D = 588 \text{ }\mu\text{A}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) = \boxed{4.961 \text{ mS}}$$
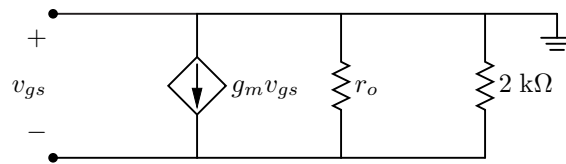
$$r_o = \frac{1}{\lambda I_D} = \boxed{16.996 \text{ k}\Omega}$$




(e) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$I_D = 0.5 \text{ mA}$$


$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \boxed{4.714 \text{ mS}}$$
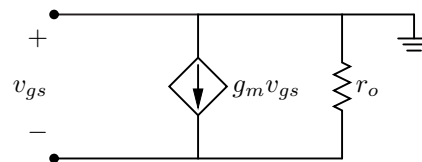
$$r_o = \frac{1}{\lambda I_D} = \boxed{20 \text{ k}\Omega}$$



$$34. \quad g_m = \sqrt{2\mu C_{ox} \frac{W}{L} I_D} \quad r_o = \left( \frac{\partial I_D}{\partial V_{DS}} \right)^{-1} = \frac{1}{\lambda I_D}$$
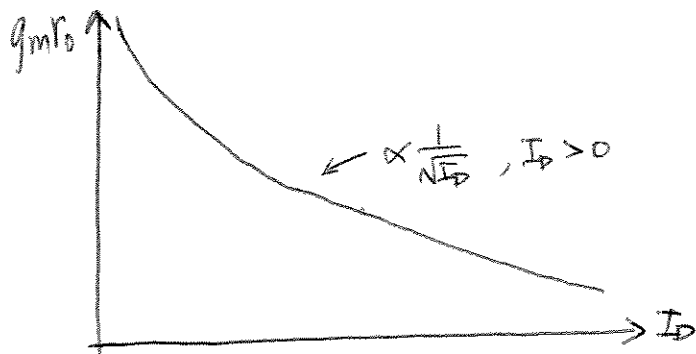
$$g_m r_o = \frac{\sqrt{2\mu C_{ox} \left( \frac{W}{L} \right) I_D}}{\lambda I_D} = \frac{1}{\lambda} \sqrt{\frac{2\mu C_{ox} \left( \frac{W}{L} \right)}{I_D}}$$







$$35 \quad (a) \quad g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$

$$r_o = \frac{1}{\lambda I_D}$$
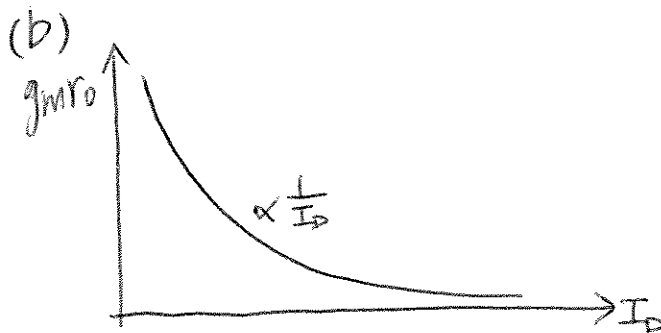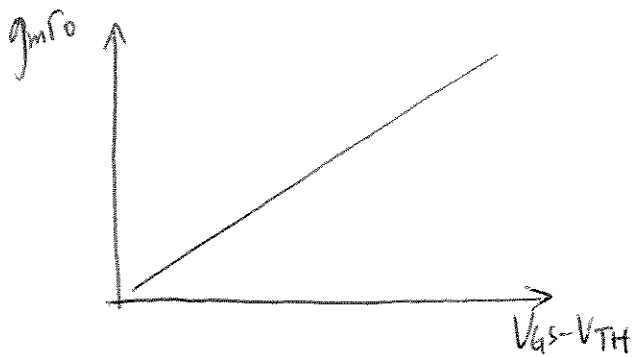
$$g_m r_o = \frac{\mu C_{ox} (W/L) (V_{GS} - V_{TH})}{\lambda I_D}$$




3b. Given NMOS with  $\lambda = 0.1 \text{ V}^{-1}$   $g_m r_o = 20$   
 $V_{DS} = 1.5 \text{ V}$   
 determine  $W/L$  if  $I_D = 0.5 \text{ mA}$ .

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.1 \text{ V}^{-1})(0.5 \text{ mA})} = 20 \text{ k}\Omega$$

$$\Rightarrow g_m = \frac{20}{20 \text{ k}\Omega} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\begin{aligned} \therefore \frac{W}{L} &= \left( \frac{20}{20 \text{ k}\Omega} \right)^2 \frac{1}{2 \mu_n C_{ox} I_D} \\ &= \left( \frac{1}{1 \text{ k}\Omega} \right)^2 \frac{1}{2 \left( \frac{200 \mu\text{A}}{\text{V}^2} \right) (0.5 \text{ mA})} \approx 5. \end{aligned}$$

37.

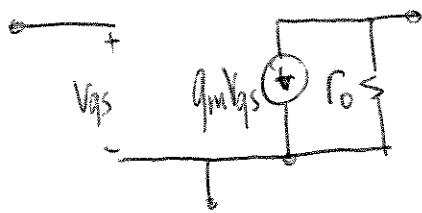Given  $\lambda = 0.2 \text{ V}^{-1}$ 

$$g_m r_o = 20$$

$$V_{DS} = 1.5 \text{ V}$$

$$I_D = 0.5 \text{ mA}$$


Calculate  $\frac{W}{L}$ .

$$g_m = \frac{20}{r_o} = 20 \cdot \lambda I_D = 20 (0.2 \text{ V}^{-1}) (0.5 \text{ mA}) = 0.002 \text{ V}^{-1} \Omega$$


$$\Rightarrow g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$

$$\therefore \frac{W}{L} = \frac{g_m^2}{2 \mu_n C_{ox} I_D} = \frac{(0.0002 \text{ V}^{-1} \Omega)^2}{2 \left( \frac{200 \mu\text{A}}{\text{V}^2} \right) (0.5 \text{ mA})} = 20$$


6.38 (a)

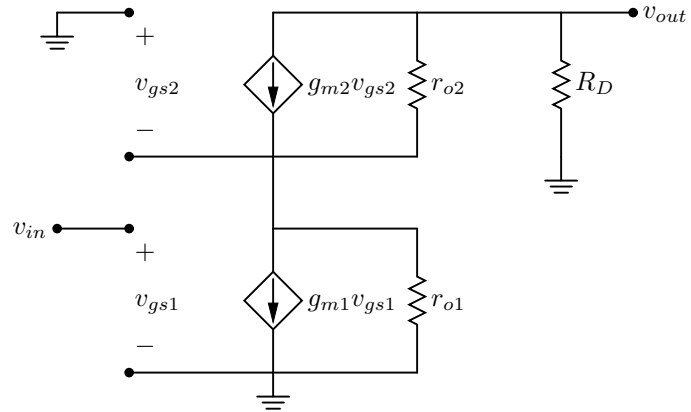


(b)

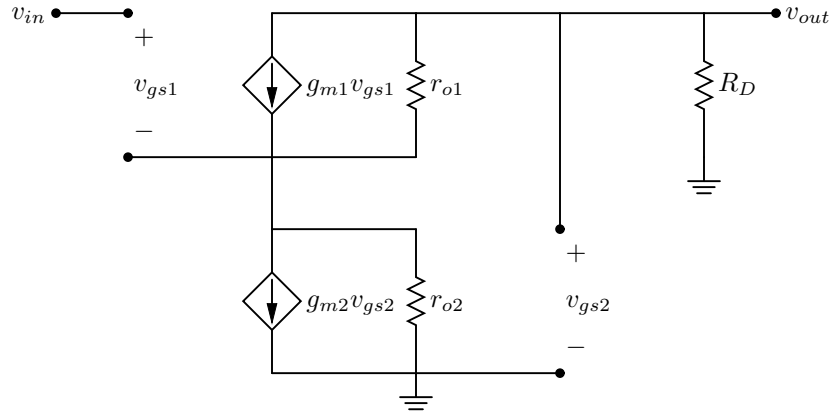


(c)

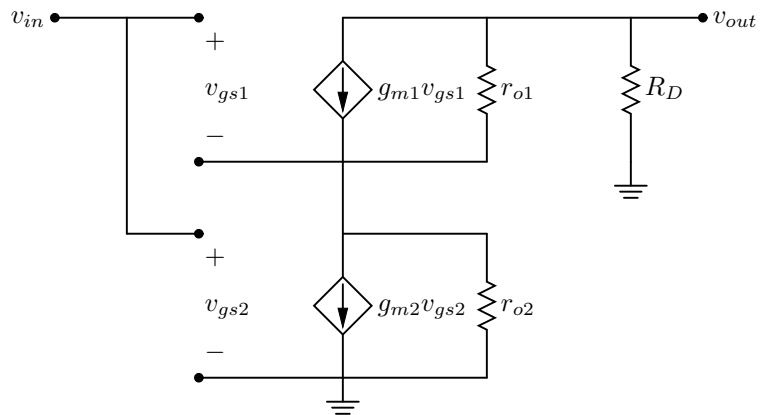

(d)

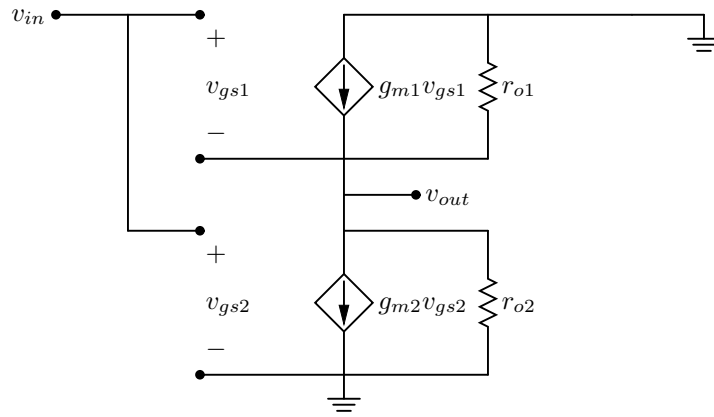

(e)

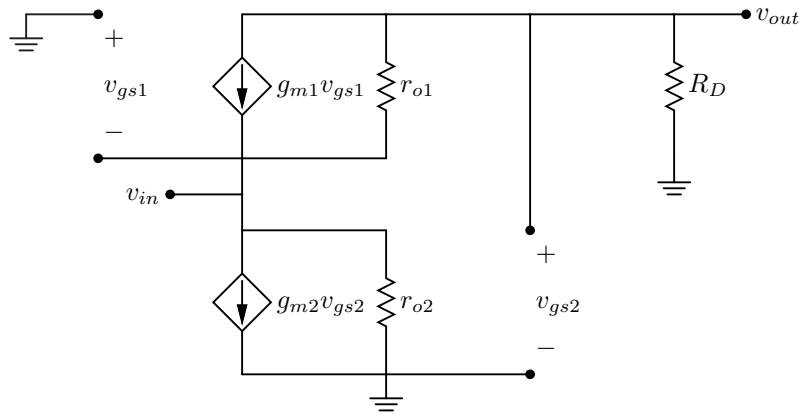

39. (a) OFF  $\because |V_{SG}| = 0$

(b) OFF  $\because |V_{SG}| < |V_{TH}| = 0.4V$

(c) SATURATION  $\because |V_{SD}| > |V_{SG}| - |V_{TH}|$

(d) OFF  $\because V_{SG} < |V_{TH}|$


40. (a) SATURATION  $\because V_{SD} > V_{SG} - |V_{TH}|$

(b) LINEAR (RESISTIVE)  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} \ll 2(V_{SG} - |V_{TH}|)$

(c) (EDGE OF) SATURATION  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} = V_{SG} - |V_{TH}|$

(d) TRIODE  $\because V_{SG} > |V_{TH}|$   
 $V_{SD} < V_{SG} - |V_{TH}|$

41.

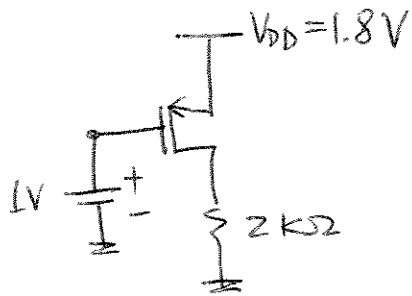

$$\lambda = 0$$

At the edge of saturation,  $V_{SD} = V_{SG} - |V_{TH}|$   
 $\Rightarrow V_D = 1.4V$ .

By KCL,  $I_{D1} = I_R$


$$\Rightarrow \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TH}|)^2 = \frac{V_D}{2k\Omega}$$

$$\therefore \frac{W}{L} = \frac{V_D}{2k\Omega} \cdot \frac{2}{\mu_p C_{ox} (V_{SG} - |V_{TH}|)^2}$$

$$= \frac{1.4V}{2k\Omega} \cdot \frac{2}{100 \frac{\mu A}{V^2} (0.8V - 0.4V)^2} \approx 87.5$$



42.

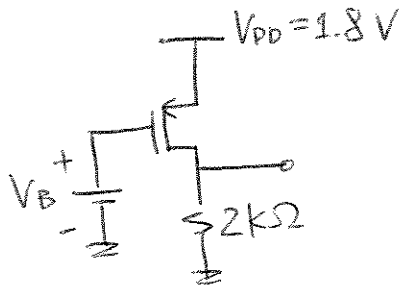

$$\lambda = 0$$

When  $V_B = 1V$ ,  $W/L = 87.5$

When  $V_B = 0.8V$ ,

$$\begin{aligned} I_D &= \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{SG} - |V_{TH}|)^2 \\ &= \frac{1}{2} \left( \frac{100 \mu A}{V^2} \right) (87.5) (1 - 0.4)^2 V^2 \approx 16 \text{ mA} \end{aligned}$$

$\Rightarrow V_D = I_D (2k\Omega) \approx 3.2V$ , which exceeds the supply voltage!

$\therefore$  PMOS goes into triode:  
( $\because I_D$  is too large)

By KCL,

$$\frac{1}{2} \mu_p C_{ox} \frac{W}{L} [(V_{SG} - |V_{TH}|) \cdot 2V_{SD} - V_{SD}^2] = (V_{DD} - V_{SD}) / 2k\Omega$$

Solving this equation numerically (or trial-and-error) gives  $V_{SD} \approx 0.18 \text{ V}$

$$\Rightarrow I_D = \frac{V_{DD} - V_{SD}}{2 \text{ k}\Omega} = \frac{(1.8 - 0.18) \text{ V}}{2 \text{ k}\Omega} \approx 0.81 \text{ mA}$$

6.43 (a) Assume  $M_1$  is operating in triode (since  $|V_{GS}| = 1.8 \text{ V}$  is large).

$$\begin{aligned}
 |V_{GS}| &= \boxed{1.8 \text{ V}} \\
 V_{DD} - |V_{DS}| &= |I_D| (500 \Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} \left[ 2(|V_{GS}| - |V_{TH}|) |V_{DS}| - |V_{DS}|^2 \right] (500 \Omega) \\
 |V_{DS}| &= \boxed{0.418 \text{ V}} < |V_{GS}| - |V_{TH}|, \text{ which verifies our assumption} \\
 |I_D| &= \boxed{2.764 \text{ mA}}
 \end{aligned}$$


(b) Since  $M_1$  is diode-connected, we know it is operating in saturation.

$$\begin{aligned}
 |V_{GS}| &= |V_{DS}| \\
 V_{DD} - |V_{GS}| &= |I_D| (1 \text{ k}\Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 \text{ k}\Omega) \\
 |V_{GS}| = |V_{DS}| &= \boxed{0.952 \text{ V}} \\
 |I_D| &= \boxed{848 \mu\text{A}}
 \end{aligned}$$

(c) Since  $M_1$  is diode-connected, we know it is operating in saturation.


$$\begin{aligned}
 |V_{GS}| &= |V_{DS}| \\
 |V_{GS}| = V_{DD} - |I_D| (1 \text{ k}\Omega) &= V_{DD} - |I_D| (1 \text{ k}\Omega) = \frac{1}{2} \mu_p C_{ox} \frac{W}{L} (|V_{GS}| - |V_{TH}|)^2 (1 \text{ k}\Omega) \\
 |V_{GS}| = |V_{GS}| &= \boxed{0.952 \text{ V}} \\
 |I_D| &= \boxed{848 \mu\text{A}}
 \end{aligned}$$

6.44 (a)

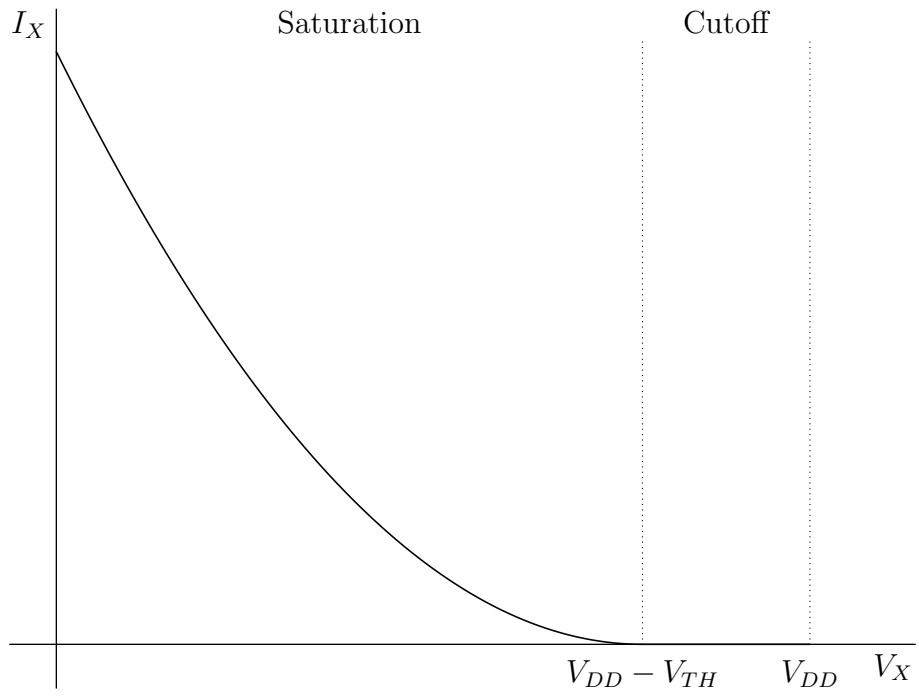


$M_1$  goes from saturation to cutoff when  $V_X = V_{DD} - V_{TH} = 1.4$  V.

(b)

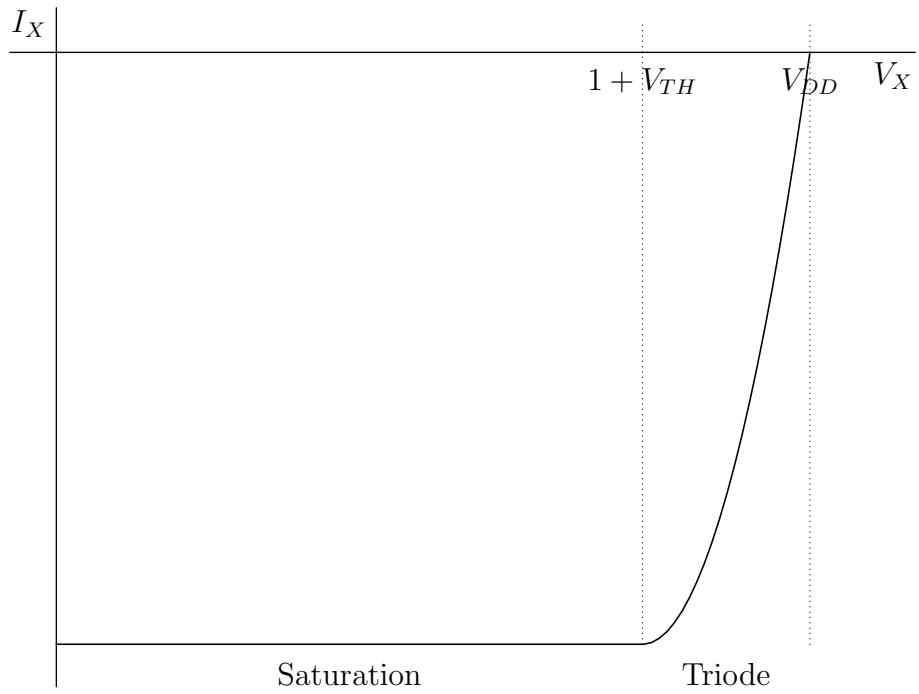


$M_1$  goes from saturation to triode when  $V_X = 1 + V_{TH} = 1.4$  V.

(c)

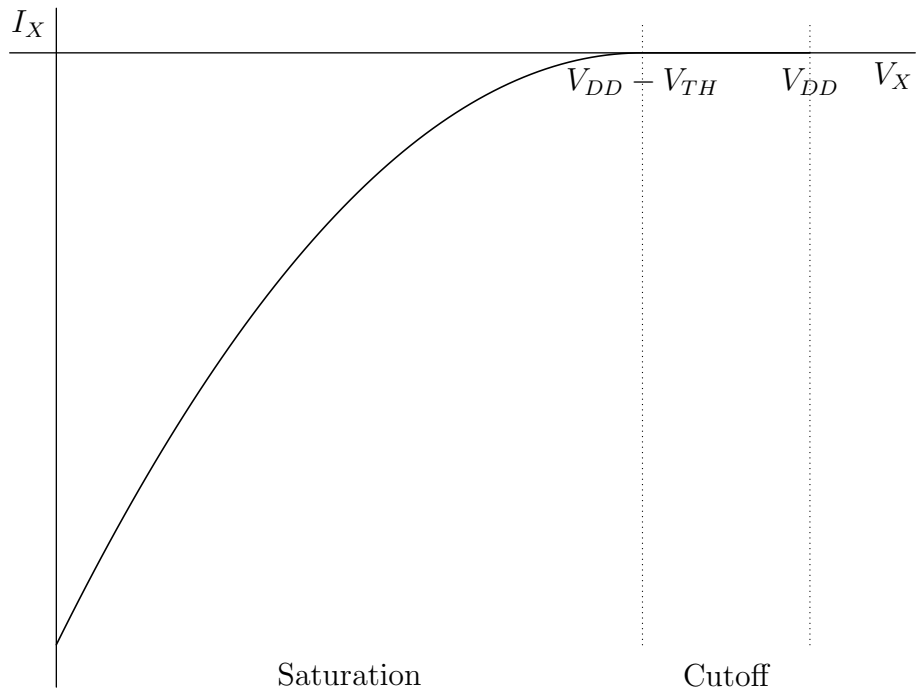



$M_1$  goes from saturation to cutoff when  $V_X = V_{DD} - V_{TH} = 1.4$  V.

(d)


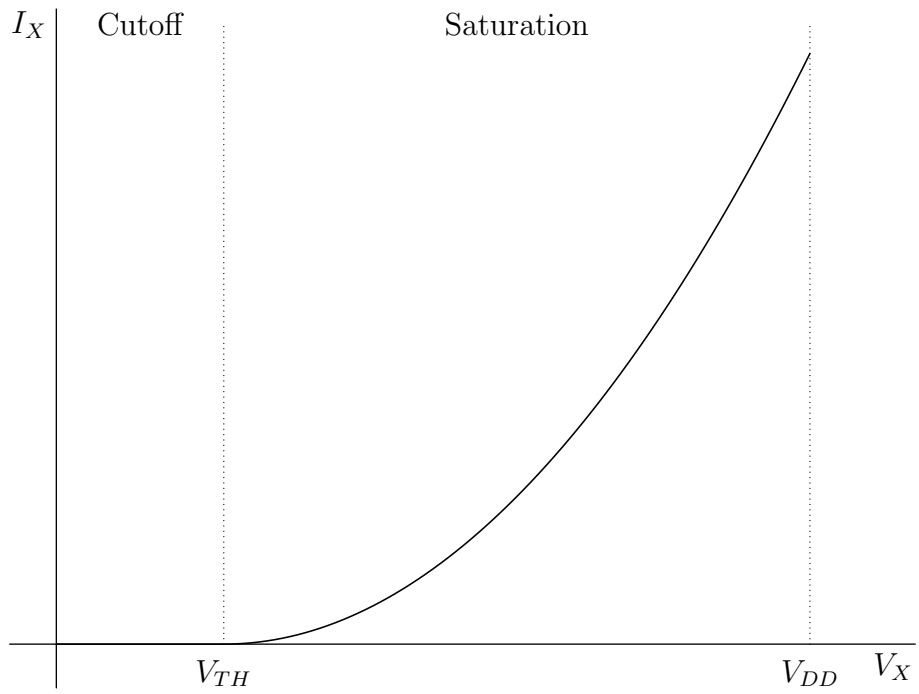


$M_1$  goes from cutoff to saturation when  $V_X = V_{TH} = 0.4$  V.



45. (a)

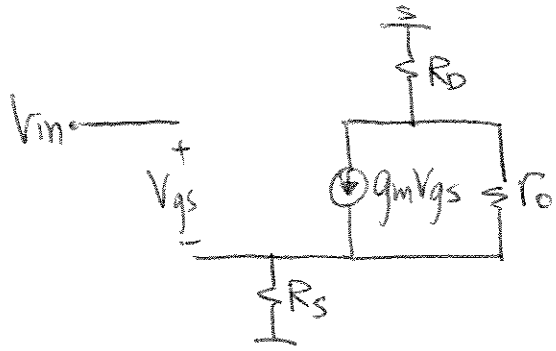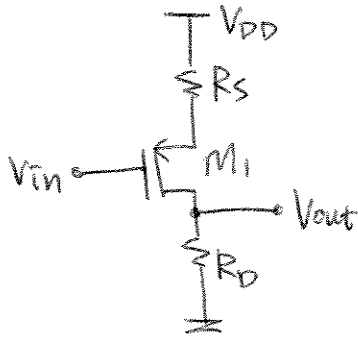



(b)

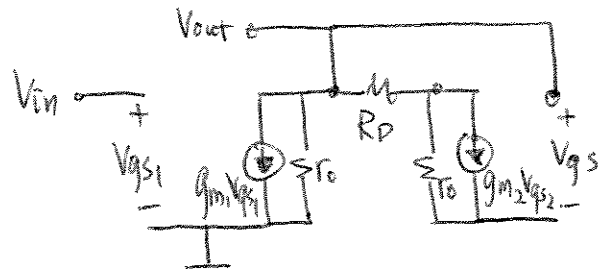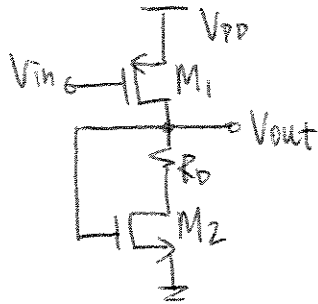



(c)

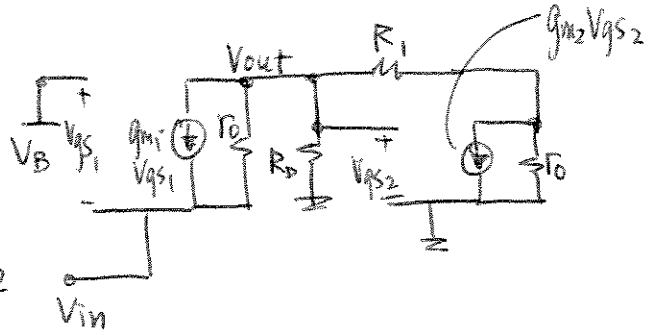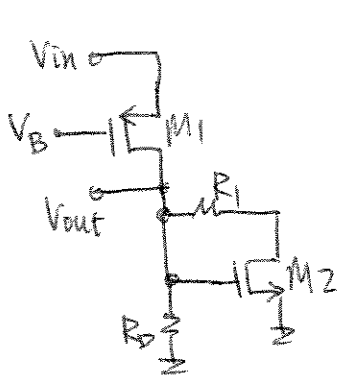


(d)

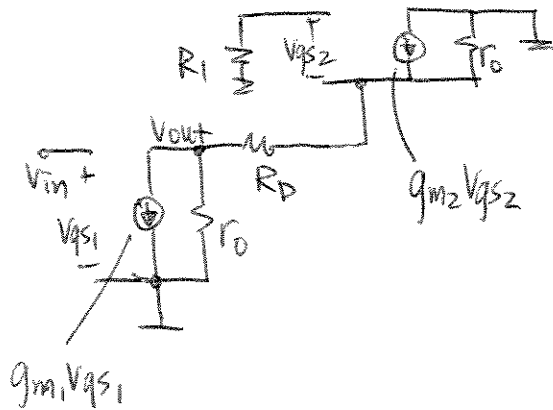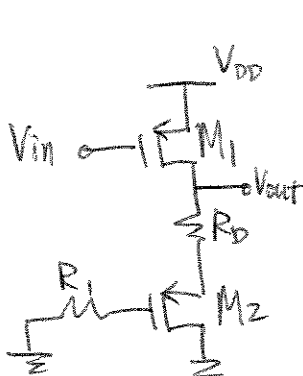

(e)

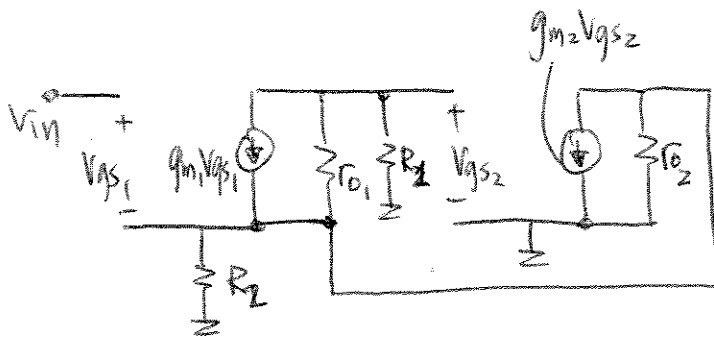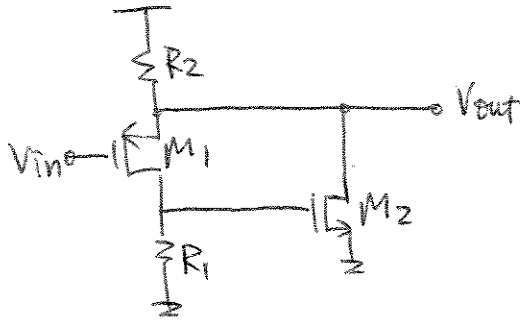


4b.

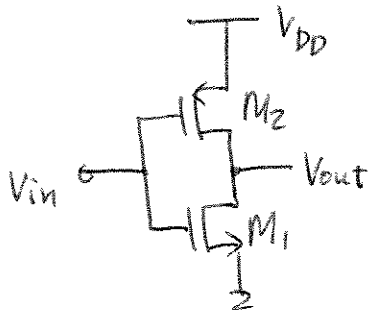

Assume  $\lambda_n$  &  $\lambda_p$ .


(a)

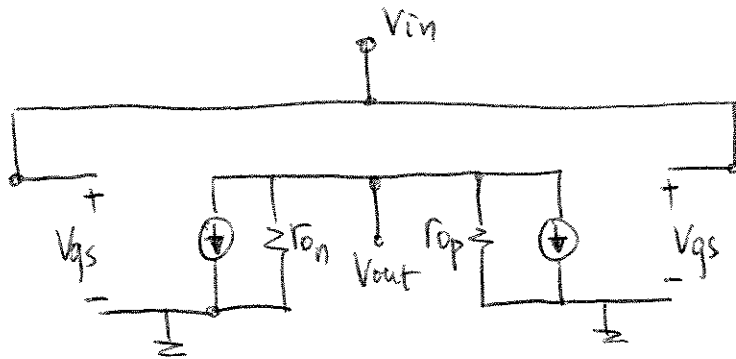

They are in "parallel" because from the small-signal model, both their respective SOURCE and DRAIN nodes are the same.

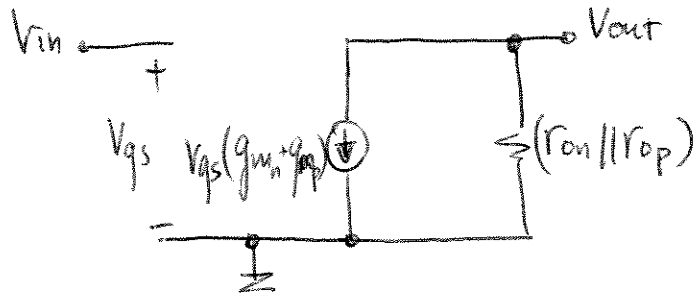(b) Assuming both  $M_1$  &  $M_2$  are in saturation, we can combine  $r_o$ 's &  $g_m$ 's :





$$\therefore \frac{V_{out}}{V_{in}} = -(g_{m_n} + g_{m_p})(r_{on} \parallel r_{op})$$

7.1

$$V_{GS} = V_{DD} = 1.8 \text{ V}$$

$V_{DS} > V_{GS} - V_{TH}$  (in order for  $M_1$  to operate in saturation)

$$V_{DS} = V_{DD} - I_D(1 \text{ k}\Omega)$$

$$= V_{DD} - \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 \text{ k}\Omega)$$

$$> V_{GS} - V_{TH}$$

$$\frac{W}{L} < \boxed{2.04}$$

② To get  $I_{DS} = 1 \text{ mA}$ ,

$$\frac{1}{2} \mu C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH})^2 = 1 \times 10^{-3} \text{ A.}$$

$$\frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18}\right)_1 (V_{GS} - V_{TH})^2 = 10^{-3}$$

$$(V_{GS} - V_{TH})^2 = 0.09$$

$$V_{GS} - V_{TH} = 0.3,$$

$$\text{i.e. } V_{GS} = 0.7.$$

Since  $V_{GS} = \frac{R_2}{R_1 + R_2} \times 1.8$

$$0.7 = \frac{R_2}{R_1 + R_2} \times 1.8$$

$$0.7 R_1 = R_2,$$

$$\therefore \frac{R_1}{R_2} = \frac{11}{7} \quad \text{————— ①}$$

To get input impedance  $\geq 20 \text{ k}$ .

$$R_1 \parallel R_2 \geq 20 \text{ k}\Omega. \quad \text{————— ②}$$

By inspection, setting  $R_1 = 55 \text{ k}\Omega$  and  $R_2 = 35 \text{ k}\Omega$  will satisfy both ① and ②.

$$\begin{aligned}
V_{GS} &= V_{DD} - I_D(100 \Omega) \\
V_{DS} &= V_{DD} - I_D(1 \text{ k}\Omega + 100 \Omega) \\
&> V_{GS} - V_{TH} \text{ (in order for } M_1 \text{ to operate in saturation)} \\
V_{DD} - I_D(1 \text{ k}\Omega + 100 \Omega) &> V_{DD} - I_D(100 \Omega) - V_{TH} \\
I_D(1 \text{ k}\Omega + 100 \Omega) &< I_D(100 \Omega) + V_{TH} \\
I_D(1 \text{ k}\Omega) &< V_{TH} \\
I_D &< 400 \mu\text{A}
\end{aligned}$$

Since  $g_m$  increases with  $I_D$ , we should pick the maximum  $I_D$  to determine the maximum transconductance that  $M_1$  can provide.

$$\begin{aligned}
I_{D,max} &= 400 \mu\text{A} \\
g_{m,max} &= \frac{2I_{D,max}}{V_{GS} - V_{TH}} \\
&= \frac{2I_{D,max}}{V_{DD} - I_{D,max}(100 \Omega) - V_{TH}} \\
&= \boxed{0.588 \text{ mS}}
\end{aligned}$$

$$\textcircled{4} \text{ a) } \therefore V_{RS} = 200 \text{ mV,}$$

$$\therefore I_{DS} R_S = 200 \text{ mV}$$

$$I_{DS} = \frac{0.2}{100}$$

$$I_{DS} = 2 \text{ mA.}$$

For  $M_1$  to stay in saturation,

$$V_{DS} \geq V_{GS} - V_{TH}$$

$$\begin{aligned} \therefore V_{DS} &= V_D - V_S \\ &= [1.8 - (2 \times 10^{-3}) \times 500] - 0.2 \\ &= 0.6, \end{aligned}$$

$$\therefore V_{GS} - V_{TH} \leq 0.6,$$

Since  $I_{DS} = \frac{1}{2} (M_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2,$

$\left(\frac{W}{L}\right)$  is min. when  $(V_{GS} - V_{TH})$  is max,

$$\therefore \text{min. } \left(\frac{W}{L}\right), \text{ is when } (V_{GS} - V_{TH}) = 0.6 \text{ V,}$$

$$2 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right), (0.6)^2$$

$$\therefore \text{min. } \left(\frac{W}{L}\right), = 56$$

b) With  $(V_{GS} - V_{TH}) = 0.6$ ,

$$V_{GS} = 1,$$

$$\therefore V_G = 1 + V_S$$

$$V_G = 1.2V,$$

$$\text{i.e. } 1.8x \frac{R_2}{R_1 + R_2} = 1.2V,$$

$$\frac{R_2}{R_1} = 2 \quad \text{--- ①}$$

$$\text{Input impedance} = R_2 // R_1,$$

$$\text{i.e. } R_2 // R_1 \geq 30k\Omega \quad \text{--- ②}$$

Set  $R_1 = 50k\Omega$  and  $R_2 = 100k\Omega$

will satisfy both ① & ②.

7.5

$$I_{D1} = 0.5 \text{ mA}$$

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}}$$
$$= 0.612 \text{ V}$$

$$V_{GS} = \frac{1}{10} I_{D1} R_2$$

$$R_2 = \boxed{12.243 \text{ k}\Omega}$$

$$V_{GS} = V_{DD} - \frac{1}{10} I_{D1} R_1 - \frac{11}{10} I_{D1} R_S$$

$$R_1 = \boxed{21.557 \text{ k}\Omega}$$

7.6

$$I_D = 1 \text{ mA}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{1}{100}$$

$$V_{GS} = 0.6 \text{ V}$$

$$V_{GS} = V_{DD} - I_D R_D$$

$$R_D = \boxed{1.2 \text{ k}\Omega}$$



(7)

$$I_{D_S} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2$$

$$0.5 \times 10^{-3} = (100 \times 10^{-6}) \left(\frac{50}{0.18}\right) (V_{GS} - V_{TH})^2$$

$$\therefore V_{GS} = 0.534 \text{ V}$$

$$\therefore R_2 = \frac{0.534}{0.05 \times 10^{-3}}$$

$$R_2 = \underline{\underline{10.68 \text{ k}\Omega}}$$

$$\therefore V_{D1} = 1.8 - (1.1 \times I_{D_S} \times 2 \text{ k}\Omega) = 0.1 I_{D_S} (R_1 + R_2),$$

$$\therefore 14 \text{ k}\Omega = R_1 + 10.68 \text{ k}\Omega.$$

$$\therefore R_1 = \underline{\underline{3320 \Omega}}$$

7.8 First, let's analyze the circuit excluding  $R_P$ .

$$V_G = \frac{20 \text{ k}\Omega}{10 \text{ k}\Omega + 20 \text{ k}\Omega} V_{DD} = 1.2 \text{ V}$$


$$V_{GS} = V_G - I_D R_S = V_{DS} = V_{DD} - I_D (1 \text{ k}\Omega + 200 \Omega)$$

$$I_D = 600 \mu\text{A}$$

$$V_{GS} = 1.08 \text{ V}$$

$$\frac{W}{L} = \frac{2I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} = 12.9758 \approx \boxed{13}$$

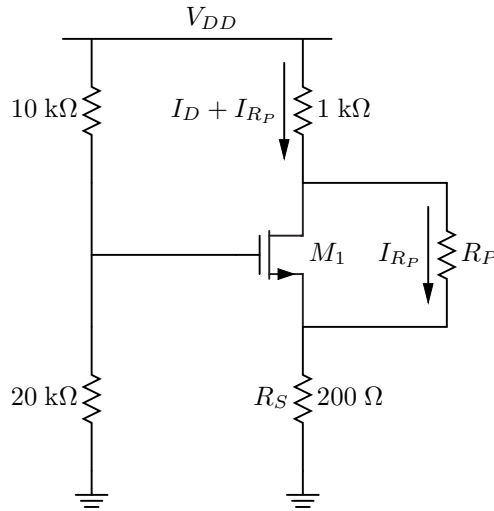Now, let's analyze the circuit with  $R_P$ .



$$V_G = 1.2 \text{ V}$$

$$I_D + I_{R_P} = \frac{V_{DD} - V_{DS}}{1 \text{ k}\Omega + 200 \Omega}$$

$$V_{GS} = V_G - (I_D + I_{R_P}) R_S = V_{DS} + V_{TH}$$

$$V_G - \frac{V_{DD} - V_{DS}}{1 \text{ k}\Omega + 200 \Omega} R_S = V_{DS} + V_{TH}$$

$$V_{DS} = 0.6 \text{ V}$$

$$V_{GS} = 1 \text{ V}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$= 467 \mu\text{A}$$

$$I_D + I_{R_P} = I_D + \frac{V_{DS}}{R_P} = \frac{V_{DD} - V_{DS}}{1 \text{ k}\Omega + 200 \Omega}$$

$$R_P = \boxed{1.126 \text{ k}\Omega}$$

7.9 First, let's analyze the circuit excluding  $R_P$ .


$$V_{GS} = V_{DD} = 1.8 \text{ V}$$

$$V_{DS} = V_{DD} - I_D(2 \text{ k}\Omega) = V_{GS} - 100 \text{ mV}$$

$$V_{DD} - \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (2 \text{ k}\Omega) = V_{GS} - 100 \text{ mV}$$

$$\frac{W}{L} = \boxed{0.255}$$

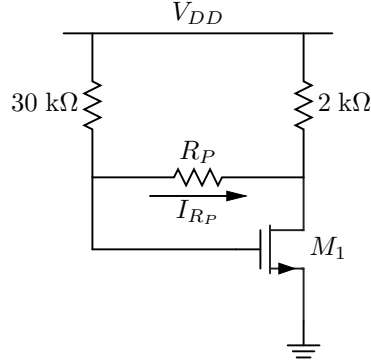Now, let's analyze the circuit with  $R_P$ .



$$V_{GS} = V_{DD} - I_{R_P}(30 \text{ k}\Omega)$$

$$I_{R_P} = \frac{V_{GS} - V_{DS}}{R_P} = \frac{50 \text{ mV}}{R_P}$$

$$V_{GS} = V_{DD} - (I_D - I_{R_P})(2 \text{ k}\Omega) + 50 \text{ mV}$$

$$V_{DD} - I_{R_P}(30 \text{ k}\Omega) = V_{DD} - \left( \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 - I_{R_P} \right) (2 \text{ k}\Omega) + 50 \text{ mV}$$

$$V_{DD} - I_{R_P}(30 \text{ k}\Omega) = V_{DD} - \left( \frac{1}{2}\mu_n C_{ox} \frac{W}{L} (V_{DD} - I_{R_P}(30 \text{ k}\Omega) - V_{TH})^2 - I_{R_P} \right) (2 \text{ k}\Omega) + 50 \text{ mV}$$

$$I_{R_P} = 1.380 \text{ }\mu\text{A}$$

$$R_P = \frac{50 \text{ mV}}{I_{R_P}} = \boxed{36.222 \text{ k}\Omega}$$

(10) For  $M_1$ ,

$$I_x = \frac{1}{2} (200 \times 100^{-6}) \left( \frac{W_1}{0.25} \right) (0.8 - 0.4)^2 \times (1 + 0.1(0.8))$$

$$10^{-3} = 0.16 \times 10^{-4} \left( \frac{W_1}{0.25} \right) (1.08)$$

$$\therefore W_1 = 14.5 \mu \text{m} //$$

For  $M_2$ ,

$$0.5 \times 10^{-3} = 0.16 \times 10^{-4} \left( \frac{W_2}{0.25} \right) (1.08)$$

$$\therefore W_2 = 7.25 \mu \text{m} //$$

Output resistance =  $r_o$

$$= \frac{1}{\lambda} \times \frac{1}{I_D}$$

$$\therefore r_{o1} = \left( \frac{1}{0.1} \right) \left( \frac{1}{10^{-3}} \right)$$

$$= 10 \text{ k}\Omega //$$

$$r_{o2} = \left( \frac{1}{0.1} \right) \left( \frac{1}{0.5 \times 10^{-3}} \right)$$

$$= 20 \text{ k}\Omega //$$

(11)

$$R_{out} = \frac{1}{\eta} \left( \frac{1}{I_D} \right)$$
$$= \frac{1}{0.5 \times 10^{-3} \eta} = 20 \text{ k}\Omega$$

$$\therefore \eta = 0.1 \text{ V}^{-1}$$

7.12 Since we're not given  $V_{DS}$  for the transistors, let's assume  $\lambda = 0$  for large-signal calculations. Let's also assume the transistors operate in saturation, since they're being used as current sources.

$$I_X = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} (V_{B1} - V_{TH})^2 = 0.5 \text{ mA}$$

$$W_1 = \boxed{3.47 \text{ } \mu\text{m}}$$

$$I_Y = \frac{1}{2} \mu_n C_{ox} \frac{W_2}{L_2} (V_{B2} - V_{TH})^2 = 0.5 \text{ mA}$$

$$W_2 = \boxed{1.95 \text{ } \mu\text{m}}$$

$$R_{out1} = r_{o1} = \frac{1}{\lambda I_X} = 20 \text{ k}\Omega$$

$$R_{out2} = r_{o2} = \frac{1}{\lambda I_Y} = 20 \text{ k}\Omega$$

Since  $I_X = I_Y$  and  $\lambda$  is the same for each current source, the output resistances of the current sources are the same.

7.13 Looking into the source of  $M_1$  we see a resistance of  $\frac{1}{g_m}$ . Including  $\lambda$  in our analysis, we have

$$\begin{aligned}\frac{1}{g_m} &= \frac{1}{\mu_p C_{ox} \frac{W}{L} (V_X - V_{B1} - |V_{TH}|) (1 + \lambda V_X)} \\ &= \boxed{372 \Omega}\end{aligned}$$

14

$$I_x = \frac{1}{2} (100 \times 10^{-6}) \left( \frac{20}{0.25} \right) (1 - 1.8 + 0.4)^2$$

$$= 0.64 \text{ mA} //$$

$$I_y = \frac{1}{2} (100 \times 10^{-6}) \left( 2 \times \frac{20}{0.25} \right) (1 - 1.8 + 0.4)^2$$

$$= 1.28 \text{ mA} //$$

$$\therefore r_o \propto \frac{1}{I}$$

and  $I_y = 2 I_x$

$$\therefore r_{out, m_1} = 2 r_{out, m_2} //$$



$$\textcircled{15} \quad |I_{D S 1}| = |I_{D S 2}|,$$

$$\begin{aligned} \frac{1}{2} (200 \times 10^{-6}) \left( \frac{10}{0.18} \right) (V_B - 0.4)^2 (1 + 0.1 \times 0.9) \\ = \frac{1}{2} (100 \times 10^{-6}) (1.8 - V_B - 0.4)^2 (1 + 0.1 \times 0.9) \\ \times \left( \frac{30}{0.18} \right) \end{aligned}$$

$$2 (V_B - 0.4)^2 = 3 (1.4 - V_B)^2$$

$$\sqrt{\frac{2}{3}} (V_B - 0.4) = (1.4 - V_B)$$

$$1.816 V_B = 1.7264$$

$$V_B = 0.95 //$$

⑩ a) For  $M_1$ ,

$$I_{D1} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{5}{0.18} \right) (V_B - 0.4)^2$$

$$(1 + 0.1 \times 0.9)$$

$$\therefore V_B \approx 0.806 \text{ V}$$

b) There are 3 regions of operation:


For  $V_x < V_B - V_{TH1}$ ,  $M_1$  is in triode.  
and  $|I_{DS2}| > |I_{DS1}|$

For  $|V_x - V_{DD}| > |V_B - V_{DD} - V_{TH2}|$ ,  $M_2$  is in triode  
and  $I_{DS1} > |I_{DS2}|$

For  $V_B - V_{TH1} < V_x$  and  $|V_x - V_{DD}| < |V_B - V_{DD} - V_{TH2}|$   
 $M_1$  and  $M_2$  are in saturation.

and  $I_{DS1} = |I_{DS2}| = 0.5 \text{ mA}$  at  $V_x = 0.9 \text{ V}$

In all cases,  $I_x = I_{DS1} - |I_{DS2}|$

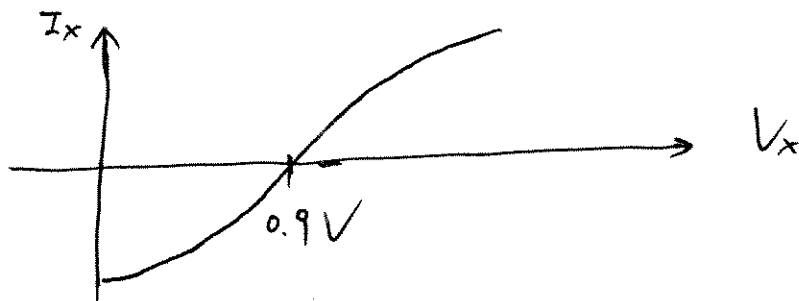

7.17 (a) Assume  $M_1$  is operating in saturation.

$$\begin{aligned} I_D &= 0.5 \text{ mA} \\ V_{GS} &= V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \\ &= \boxed{0.573 \text{ V}} \\ V_{DS} &= V_{DD} - I_D R_D = 0.8 \text{ volt} > V_{GS} - V_{TH}, \text{ verifying that } M_1 \text{ is in saturation} \end{aligned}$$

(b)

$$\begin{aligned} A_v &= -g_m R_D \\ &= -\frac{2I_D}{V_{GS} - V_{TH}} R_D \\ &= \boxed{-11.55} \end{aligned}$$

7.18 (a) Assume  $M_1$  is operating in saturation.

$$\begin{aligned}
 I_D &= 0.25 \text{ mA} \\
 V_{GS} &= V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \\
 &= \boxed{0.55 \text{ V}} \\
 V_{DS} &= V_{DD} - I_D R_D = 1.3 \text{ V} > V_{GS} - V_{TH}, \text{ verifying that } M_1 \text{ is in saturation}
 \end{aligned}$$

(b)

$$\begin{aligned}
 V_{GS} &= 0.55 \text{ V} \\
 V_{DS} &> V_{GS} - V_{TH} \text{ (to ensure } M_1 \text{ remains in saturation)} \\
 V_{DD} - I_D R_D &> V_{GS} - V_{TH} \\
 V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 R_D &> V_{GS} - V_{TH} \\
 \frac{W}{L} &< \frac{2(V_{DD} - V_{GS} + V_{TH})}{\mu_n C_{ox} (V_{GS} - V_{TH})^2 R_D} \\
 &= 366.67 \\
 &= 3.3 \frac{20}{0.18}
 \end{aligned}$$

Thus,  $W/L$  can increase by a factor of  $\boxed{3.3}$  while  $M_1$  remains in saturation.

$$\begin{aligned}
 A_v &= -g_m R_D \\
 &= -\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) R_D \\
 A_{v,max} &= -\mu_n C_{ox} \left( \frac{W}{L} \right)_{max} (V_{GS} - V_{TH}) R_D \\
 &= \boxed{-22}
 \end{aligned}$$

7.19

$$P = V_{DD}I_D < 1 \text{ mW}$$

$$I_D < 556 \text{ } \mu\text{A}$$

$$A_v = -g_m R_D$$

$$= -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} R_D$$

$$= -5$$

$$\frac{W}{L} < \frac{20}{0.18}$$

$$R_D > \boxed{1.006 \text{ k}\Omega}$$

7.20 (a)

$$\begin{aligned}I_{D1} &= I_{D2} = 0.5 \text{ mA} \\A_v &= -g_{m1} (r_{o1} \parallel r_{o2}) \\&= -\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} \left(\frac{1}{\lambda_1 I_{D1}} \parallel \frac{1}{\lambda_2 I_{D2}}\right) \\&= -10 \\ \left(\frac{W}{L}\right)_1 &= \boxed{7.8125}\end{aligned}$$

(b)

$$\begin{aligned}V_{DD} - V_B &= V_{TH} + \sqrt{\frac{2|I_{D2}|}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}} \\V_B &= \boxed{1.1 \text{ V}}\end{aligned}$$

(21)

$$|A_v| = g_{m1} (r_{o1} \parallel r_{o2})$$

$$g_{m1} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{20}{0.18}\right) \times (0.001)}$$

(Since  $V_{ds1}$  is not given, assume  
(if  $\lambda \cdot V_{ds1}$ ) has minimal effect on  $g_{m1}$ )

$$= 6.67 \text{ mS.} \quad (S = \Omega^{-1})$$

$$\begin{aligned} r_{o1} &= \frac{1}{\lambda_1 \times I_{D1}} \\ &= \frac{1}{0.1 \times 1 \text{ mA}} \\ &= 10 \text{ k}\Omega. \end{aligned}$$

$$r_{o2} = \infty$$

$$(\because \lambda_2 \ll \lambda_1)$$

$$\therefore |A_v| = 6.67 \times 10^{-3} \times 10^3 \times 10$$

$$= 66.7 //$$

- 7.22 (a) If  $I_{D1}$  and  $I_{D2}$  remain constant while  $W$  and  $L$  double, then  $g_{m1} \propto \sqrt{(W/L)_1 I_{D1}}$  will not change (since it depends only on the ratio  $W/L$ ),  $r_{o1} \propto \frac{1}{I_{D1}}$  will not change, and  $r_{o2} \propto \frac{1}{I_{D2}}$  will not change. Thus,  $A_v = -g_{m1} (r_{o1} \parallel r_{o2})$  will not change.
- (b) If  $I_{D1}$ ,  $I_{D2}$ ,  $W$ , and  $L$  double, then  $g_{m1} \propto \sqrt{(W/L)_1 I_{D1}}$  will increase by a factor of  $\sqrt{2}$ ,  $r_{o1} \propto \frac{1}{I_{D1}}$  will halve, and  $r_{o2} \propto \frac{1}{I_{D2}}$  will halve. This means that  $r_{o1} \parallel r_{o2}$  will halve as well, meaning  $A_v = -g_{m1} (r_{o1} \parallel r_{o2})$  will decrease by a factor of  $\sqrt{2}$ .



(23). To get higher voltage gain,

(a) is preferred.

For the same dimensions of transistors  
and same bias current,

(a) has a high " $g_m$ " than (b).

$$\therefore g_{m1} > g_{m2}$$

(since  $\mu_n C_{ox} > \mu_p C_{ox}$ )

while  $(R_{o1} \parallel R_{o2})$  is the same  
for both cases.

(24)

$$A_v = f_{m_2} (r_{o1} // r_{o2})$$

$$r_{o1} = \frac{1}{0.15 \times 0.5 \text{ mA}}$$

$$= 13.3 \text{ k}\Omega.$$

$$r_{o2} = \frac{1}{0.05 \times 0.5 \text{ mA}}$$

$$= 40 \text{ k}\Omega.$$

$$\therefore r_{o1} // r_{o2} = 10 \text{ k}\Omega.$$

$$\therefore 15 = \left[ \sqrt{2 \times (100 \times 10^{-6}) \left( \frac{W}{L} \right)_2 \cdot 0.5 \text{ mA}} \right] \cdot (10 \text{ k}\Omega)$$

$$\left( \frac{W}{L} \right)_2 = 22.5 //$$

25 From Eq (7.57),

$$3 = \sqrt{\frac{20/0.18}{(w/L)_2}}$$

$$\therefore (w/L)_2 \approx 12.3 //$$

7.26 (a)

$$\begin{aligned}
 I_{D1} &= I_{D2} = 0.5 \text{ mA} \\
 V_{GS1} &= V_{TH} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} \\
 &= 0.7 \text{ V} \\
 V_{DS1} &= V_{GS1} - V_{TH} \text{ (in order of } M_1 \text{ to operate at the edge of saturation)} \\
 &= V_{DD} - V_{GS2} \\
 V_{GS2} &= V_{DD} - V_{GS1} + V_{TH} = V_{TH} + \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} \\
 \left(\frac{W}{L}\right)_2 &= \boxed{4.13}
 \end{aligned}$$

(b)

$$\begin{aligned}
 A_v &= -\frac{g_{m1}}{g_{m2}} \\
 &= -\frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}}} \\
 &= -\sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}} \\
 &= \boxed{-3.667}
 \end{aligned}$$

- (c) Since  $(W/L)_1$  is fixed, we must minimize  $(W/L)_2$  in order to maximize the magnitude of the gain (based on the expression derived in part (b)). If we pick the size of  $M_2$  so that  $M_1$  operates at the edge of saturation, then if  $M_2$  were to be any smaller,  $V_{GS2}$  would have to be larger (given the same  $I_{D2}$ ), driving  $M_1$  into triode. Thus,  $(W/L)_2$  is its smallest possible value (without driving  $M_1$  into saturation) when  $M_1$  is at the edge of saturation, meaning the gain is largest in magnitude with this choice of  $(W/L)_2$ .

7.27 (a)

$$\begin{aligned}A_v &= -\frac{g_{m1}}{g_{m2}} \\&= -\frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}}} \\&= -\sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}} \\&= -5 \\ \left(\frac{W}{L}\right)_1 &= \boxed{277.78}\end{aligned}$$

(b)

$$\begin{aligned}V_{DS1} &> V_{GS1} - V_{TH} \text{ (to ensure } M_1 \text{ is in saturation)} \\V_{DD} - V_{GS2} &> V_{GS1} - V_{TH} \\V_{DD} - V_{TH} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} &> \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} \\I_{D1} = I_{D2} &< \boxed{1.512 \text{ mA}}\end{aligned}$$

7.28 For this problem, recall that looking into the drain of a transistor with a grounded gate and source we see a resistance of  $r_o$ , and looking into either terminal of a diode-connected transistor we see a resistance of  $\frac{1}{g_m} \parallel r_o$ .

(a)

$$A_v = \boxed{-g_{m1} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

(b)

$$A_v = \boxed{-g_{m1} \left( r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$

(c)

$$A_v = \boxed{-g_{m1} \left( r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$


(d)

$$A_v = \boxed{-g_{m2} \left( r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$

(e)

$$A_v = \boxed{-g_{m2} \left( r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$

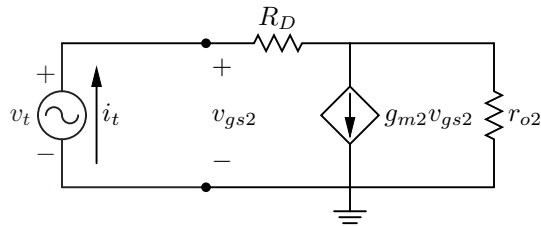(f) Let's draw a small-signal model to find the equivalent resistance seen looking up from the output.



$$i_t = g_{m2} v_{gs2} + \frac{v_t - i_t R_D}{r_{o2}}$$

$$v_{gs2} = v_t$$

$$i_t = g_{m2} v_t + \frac{v_t - i_t R_D}{r_{o2}}$$

$$i_t \left( 1 + \frac{R_D}{r_{o2}} \right) = v_t \left( g_{m2} + \frac{1}{r_{o2}} \right)$$

$$\frac{v_t}{i_t} = \frac{1 + \frac{R_D}{r_{o2}}}{g_{m2} + \frac{1}{r_{o2}}} = \frac{r_{o2} + R_D}{1 + g_{m2} r_{o2}}$$

$$A_v = \boxed{-g_{m1} \left( r_{o1} \parallel \frac{r_{o2} + R_D}{1 + g_{m2} r_{o2}} \right)}$$

7.30 (a) Assume  $M_1$  is operating in saturation.

$$\begin{aligned}
 I_D &= 1 \text{ mA} \\
 I_D R_S &= 200 \text{ mV} \\
 R_S &= 200 \Omega \\
 A_v &= -\frac{R_D}{\frac{1}{g_m} + R_S} \\
 &= -\frac{R_D}{\frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} + R_S} \\
 &= -4 \\
 \frac{W}{L} &= \boxed{1000} \\
 V_{GS} &= V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \\
 &= 0.5 \text{ V} \\
 V_{DS} &= V_{DD} - I_D R_D - I_D R_S \\
 &= 0.6 \text{ V} > V_{GS} - V_{TH}, \text{ verifying that } M_1 \text{ is in saturation}
 \end{aligned}$$

$\boxed{\text{Yes}}$ , the transistor operates in saturation.


(b) Assume  $M_1$  is operating in saturation.

$$\begin{aligned}
 \frac{W}{L} &= \frac{50}{0.18} \\
 R_S &= 200 \Omega \\
 A_v &= -\frac{R_D}{\frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} + R_S} \\
 &= -4 \\
 R_D &= \boxed{1.179 \text{ k}\Omega} \\
 V_{GS} &= V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \\
 &= 0.590 \text{ V} \\
 V_{DS} &= V_{DD} - I_D R_D - I_D R_S \\
 &= 0.421 \text{ V} > V_{GS} - V_{TH}, \text{ verifying that } M_1 \text{ is in saturation}
 \end{aligned}$$

$\boxed{\text{Yes}}$ , the transistor operates in saturation.

(31)

The small signal model is:

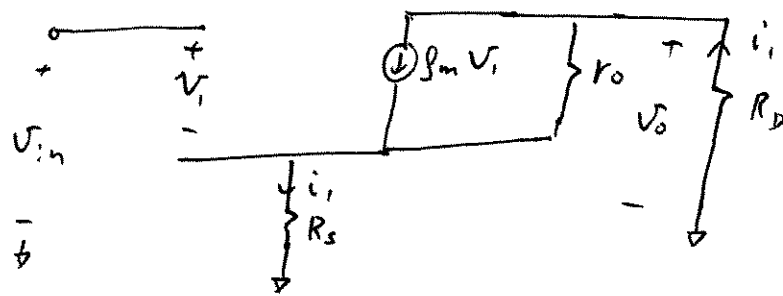

$$v_o = -i_i R_D \quad \text{--- (1)}$$

$$\begin{aligned} i_i &= g_m v_i + \frac{v_o - v_i}{r_o} \\ &= \frac{(g_m r_o - 1) v_i + v_o}{r_o} \end{aligned}$$

$$i_i \approx g_m v_i + \frac{v_o}{r_o}$$

$$-\frac{v_o}{R_D} = g_m v_i + \frac{v_o}{r_o} \quad \text{--- (2)}$$

$$v_{in} = v_i + i_i R_s$$

$$\therefore v_i = v_{in} + \frac{v_o}{R_D} R_s \quad \text{--- (3)}$$

(2) combined with (3):

$$-\frac{v_o}{R_D} = g_m v_{in} + g_m v_o \frac{R_s}{R_D} + \frac{v_o}{r_o}$$


$$-v_o \left[ \frac{1}{R_D} + g_m \frac{R_s}{R_D} + \frac{1}{r_o} \right] = g_m v_{in}$$

$$\therefore \text{Volt. gain} = \frac{v_o}{v_{in}} = - \left[ \frac{g_m}{r_o + g_m R_s + \frac{1}{R_D}} \right] (r_o R_D) //$$



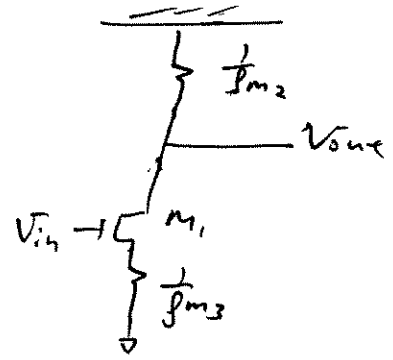32. a) Equivalent circuit is:

$$\therefore A_v = - \frac{\frac{1}{\beta m_2}}{\frac{1}{\beta m_1} + \frac{1}{\beta m_3}}$$




b) Similar to Prob. 28 (f),

Equivalent circuit is:

From Prob. 28 (f),


$$Z_L = \frac{1}{\beta m_2} \quad (\text{as } r_{o2} \rightarrow \infty)$$
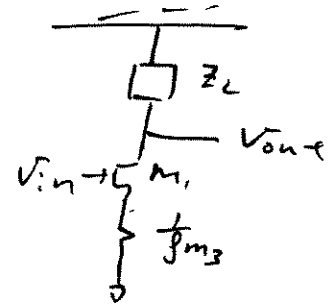
$$\therefore A_v = - \frac{\frac{1}{\beta m_2}}{\frac{1}{\beta m_1} + \frac{1}{\beta m_3}}$$



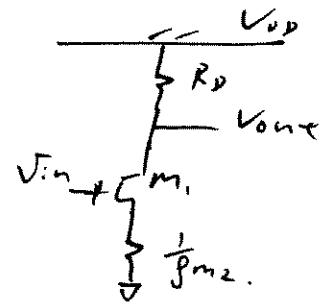
c) Equivalent circuit is:

$$\therefore A_v = - \frac{R_D}{\frac{1}{\beta m_1} + \frac{1}{\beta m_2}}$$



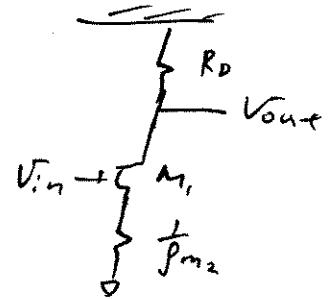
(d) Equivalent circuit is

$$A_V = - \frac{R_D}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m2}}}$$



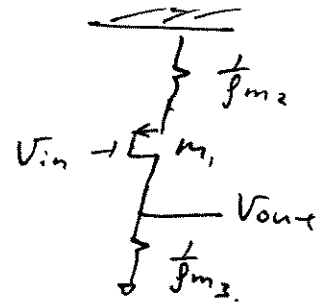(e) Equivalent circuit is

$$A_V = \frac{\frac{1}{\beta_{m3}}}{\frac{1}{\beta_{m1}} + \frac{1}{\beta_{m2}}}$$



33

a) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) \left( \frac{1}{\beta_{m2}} + r_{o1} \right) //$$

b) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) \left( \frac{1}{\beta_{m2}} + r_{o1} \right) //$$

c) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m2} r_{o2}) \left( r_{o1} // \frac{1}{\beta_{m3}} \right) + r_{o2} //$$

d) From Eq. (7.71),

$$R_{out} = (1 + \beta_{m1} r_{o1}) \left( r_{o2} // \frac{1}{\beta_{m3}} \right) + r_{o1} //$$

34. To find  $\left(\frac{w}{L}\right)$

$$10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{w}{L}\right) (1 - 0.4)^2 \times (1 + 0.1 V_{DS})$$

$$\text{Where } V_{DS} = 1.8 - 1 \text{ k}\Omega \times 1 \text{ mA} \\ = 0.8 \text{ V}$$

$$\therefore \left(\frac{w}{L}\right) \approx 25.7 //$$

$$\text{Voltage gain, } (A_v) = -f_{m_i} (r_{o_i} // R_D)$$

$$f_{m_i} = \sqrt{2(200 \times 10^{-6}) / (25.7) \times 10^{-3} \times (1 + 0.1 \times 0.8)} \\ = 3.33 \text{ mS}$$

$$r_{o_i} = \frac{1}{0.1 \times 10^{-3}} \\ = 10 \text{ k}\Omega$$

$$\therefore A_v = (-3.33 \times 10^{-3}) / (10 \text{ k}\Omega // 1 \text{ k}\Omega) \\ = -3.03 //$$

(35) With  $\lambda = 0$ ,

$$10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left( \frac{V}{L} \right) (1 - 0.4)^2$$

$$\therefore \left( \frac{V}{L} \right) \approx 27.8 //$$


$$A_V = -g_m R_D$$

$$= -\sqrt{2(200 \times 10^{-6})(27.8) \times 10^{-3}} \times 1000$$

$$= -3.33 //$$

Without  $r_o$ , gain increases due mainly to increase in load resistance.

36 The small-signal circuit is:

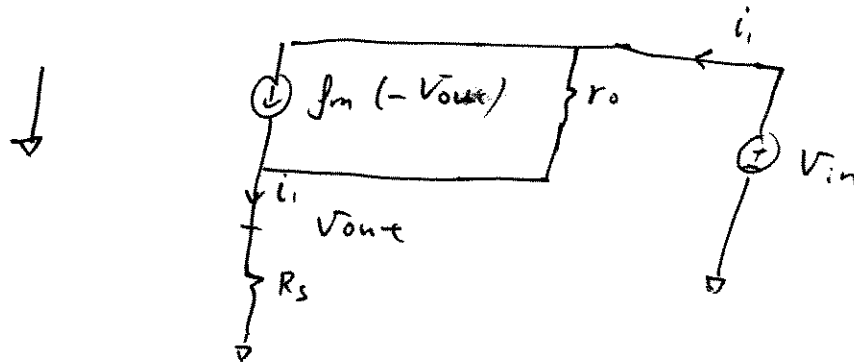

$$i_i = \frac{V_{out}}{R_s} \quad \text{--- (1)}$$

$$i_i = g_m(-V_{out}) + \frac{V_{in} - V_{out}}{r_o} \quad \text{--- (2)}$$

$$\therefore \frac{V_{out}}{R_s} = -g_m V_{out} + \frac{V_{in}}{r_o} - \frac{V_{out}}{r_o}$$

$$V_{out} \left( \frac{1}{R_s} + g_m + \frac{1}{r_o} \right) = \frac{V_{in}}{r_o}$$

$$\frac{V_{out}}{V_{in}} = \frac{1}{r_o} \left( \frac{R_s r_o}{r_o + g_m r_o R_s + R_s} \right)$$

$$= \frac{R_s}{g_m r_o R_s + r_o + R_s}$$

Since  $(g_m r_o R_s + r_o) > 0$ , the voltage gain  $< 1$ .

This is expected: Any variation in  $V_{in}$  causes minimal change in the bias current.  
 $\therefore V_{out}$  is determined largely by the amount of bias current ( $\therefore V_{out}$  is set by  $V_{BS1}$ )  
 $\therefore$  There is almost no variation in  $V_{out}$ . (ie.  $\frac{V_{out}}{V_{in}} \ll 1$ )

$$\textcircled{37} \quad a) \quad |Voltage \ gain| = \beta_m R_D$$

$$= 5$$

$$\therefore \beta_m = \frac{5}{500}$$

$$= 10 \text{ mS}$$

$$= \sqrt{2(200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \frac{W}{L} = 250 //$$

$$b) \quad V_D = 1.8 - 500 \times 10^{-3}$$

$$= 1.3 \text{ V}$$

$$\text{To obtain } V_{DS} \geq V_{GS} - V_{TH} + 0.2,$$

$$V_D \geq V_G - 0.2$$

$$\therefore V_G \leq 1.5$$

$$\text{Also, } I_{R_1+R_2} = 0.1 \times 10^{-3} \text{ A}$$

$$\therefore R_1 + R_2 = \frac{1.8}{0.1 \times 10^{-3}} \\ = 18 \text{ k}\Omega$$

$$\text{choose } R_2 = 15 \text{ k}\Omega \quad \& \quad R_1 = 3 \text{ k}\Omega$$

c) With twice of  $(W/L)$ ,  $M_1$  will go further away from triode. As  $(W/L)$  doubles, &  $I_{bias}$  is fixed by the current source,  $V_{GS}$  is forced to decrease (so  $M_1$  will have same  $I_{DS}$ ). Thus,  $(V_{GS} - V_{TH})$  decreases, and  $V_{OS}$  can be allowed to drop more before  $M_1$  goes into triode.

Gain will be increased by  $\sqrt{2}$ , because gain  $\propto g_m$ , and  $g_m \propto \sqrt{W/L}$ .



$$\textcircled{38} \text{ a) } V_G = 1.8 \text{ V.}$$

$$\therefore V_{D, \min} = 1.8 - 0.4 \quad (\text{for } M_1 \text{ stays in saturation})$$
$$= 1.4 \text{ V}$$

$$\therefore R_{D, \max} = \frac{1.4 \text{ V}}{1 \text{ mA}}$$
$$= 1.4 \text{ k}\Omega //$$

$$\text{b) } |\text{Voltage gain}| = g_m R_D$$

$$= 5.$$

$$\therefore g_m = \frac{5}{R_D}$$

$$= 3.57 \text{ mS.}$$

$$= \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \left(\frac{W}{L}\right) = 31.9 //$$

$$\textcircled{39} \quad \text{To get } R_{in} = 50 \Omega,$$

$$\frac{1}{f_m} = 50 \Omega$$

$$\therefore f_m = 20 \text{ mS.}$$

$$\text{voltage gain (Av)} = f_m R_D$$

$$= 4,$$

$$\therefore R_D = \frac{4}{0.02}$$

$$R_D = 200 \Omega //$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 0.5 \times 10^3}$$

$$\therefore \left(\frac{W}{L}\right) = 2000 //$$

7.42 (a)

$$\begin{aligned}R_{out} &= R_D = 500 \Omega \\V_G &= V_{DD} \\V_D &> V_G - V_{TH} \text{ (in order for } M_1 \text{ to operate in saturation)} \\V_{DD} - I_D R_D &> V_{DD} - V_{TH} \\I_D &< \boxed{0.8 \text{ mA}}\end{aligned}$$

(b)

$$\begin{aligned}I_D &= 0.8 \text{ mA} \\R_{in} &= \frac{1}{g_m} \\&= \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} \\&= 50 \Omega \\ \frac{W}{L} &= \boxed{1250}\end{aligned}$$

(c)

$$\begin{aligned}A_v &= g_m R_D \\g_m &= \frac{1}{50} \text{ S} \\R_D &= 500 \Omega \\A_v &= \boxed{10}\end{aligned}$$

7.43 (a)

$$\begin{aligned}I_D &= I_1 = 1 \text{ mA} \\V_G &= V_{DD} \\V_D &= V_G - V_{TH} + 100 \text{ mV} \\V_{DD} - I_D R_D &= V_G - V_{TH} + 100 \text{ mV} \\R_D &= \boxed{300 \Omega}\end{aligned}$$

(b)


$$\begin{aligned}R_D &= 300 \Omega \\A_v &= g_m R_D \\&= \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D} \\&= 5 \\\frac{W}{L} &= \boxed{694.4}\end{aligned}$$

7.44 For this problem, recall that looking into the drain of a transistor with a grounded gate and source we see a resistance of  $r_o$ , and looking into either terminal of a diode-connected transistor we see a resistance of  $\frac{1}{g_m} \parallel r_o$ .

(a) Referring to Eq. (7.109) with  $R_D = \frac{1}{g_{m2}}$  and  $g_m = g_{m1}$ , we have

$$A_v = \boxed{\frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_S}}$$

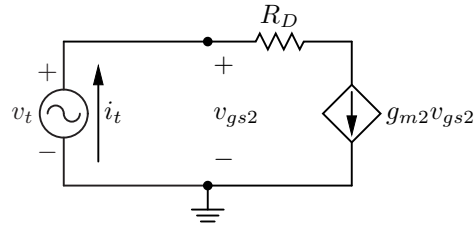(b) Let's draw a small-signal model to find the equivalent resistance seen looking up from the output.



$$i_t = g_{m2} v_{gs2}$$

$$v_{gs2} = v_t$$

$$i_t = g_{m2} v_t$$

$$\frac{v_t}{i_t} = \frac{1}{g_{m2}}$$

$$A_v = \boxed{\frac{g_{m1}}{g_{m2}}}$$

(c) Referring to Eq. (7.119) with  $R_D = \frac{1}{g_{m2}}$ ,  $R_3 = R_1$ , and  $g_m = g_{m1}$ , we have

$$A_v = \boxed{\frac{R_1 \parallel \frac{1}{g_{m1}}}{R_S + R_1 \parallel \frac{1}{g_{m1}}} \frac{g_{m1}}{g_{m2}}}$$

(d)

$$A_v = \boxed{g_{m1} \left( R_D + \frac{1}{g_{m2}} \parallel r_{o3} \right)}$$

(e)

$$A_v = \boxed{g_{m1} \left( R_D + \frac{1}{g_{m2}} \right)}$$

7.45 (a)

$$\begin{aligned}\frac{v_X}{v_{in}} &= -g_{m1} \left( R_{D1} \parallel \frac{1}{g_{m2}} \right) \\ \frac{v_{out}}{v_X} &= g_{m2} R_{D2} \\ \frac{v_{out}}{v_{in}} &= \frac{v_X}{v_{in}} \frac{v_{out}}{v_X} \\ &= \boxed{-g_{m1} g_{m2} R_{D2} \left( R_{D1} \parallel \frac{1}{g_{m2}} \right)}\end{aligned}$$

(b)

$$\lim_{R_{D1} \rightarrow \infty} -g_{m1} g_{m2} R_{D2} \left( R_{D1} \parallel \frac{1}{g_{m2}} \right) = \boxed{-g_{m1} R_{D2}}$$

This makes sense because the common-source stage acts as a transconductance amplifier with a transconductance of  $g_{m1}$ . The common-gate stage acts as a current buffer with a current gain of 1. Thus, the current  $g_{m1}v_{in}$  flows through  $R_{D2}$ , meaning  $v_{out} = -g_{m1}v_{in}R_{D2}$ , so that  $\frac{v_{out}}{v_{in}} = -g_{m1}R_{D2}$ .

This type of amplifier (with  $R_{D1} = \infty$ ) is known as a cascode and will be studied in detail in Chapter 9.

7.40

$$I_D = 0.5 \text{ mA}$$

$$\begin{aligned} R_{in} &= \frac{1}{g_m} \\ &= \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} \\ &= 50 \Omega \end{aligned}$$

$$\frac{W}{L} = \boxed{2000}$$

$$V_D > V_G - V_{TH} \text{ (in order for } M_1 \text{ to operate in saturation)}$$


$$V_{DD} - I_D R_D > V_b - V_{TH}$$

$$R_D < 2.4 \text{ k}\Omega$$

Since  $|A_v| \propto R_D$ , we need to maximize  $R_D$  in order to maximize the gain. Thus, we should pick  $R_D = \boxed{2.4 \text{ k}\Omega}$ . This corresponds to a voltage gain of  $A_v = -g_m R_D = -48$ .

(4) Voltage gain ( $A_v$ ) =  $G_m R_{out}$ ,  
 where  $G_m$  and  $R_{out}$  are the transconductance  
 and output resistance of the circuit respectively.


To find  $G_m$ :

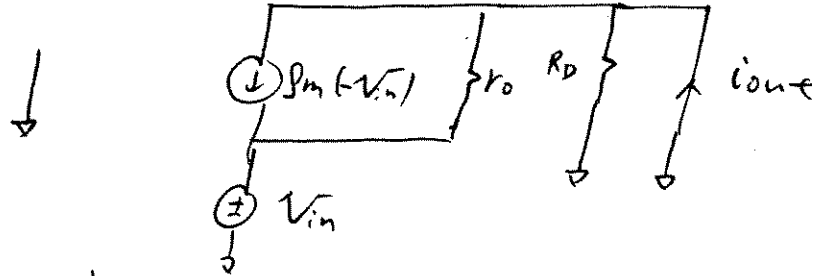

$$G_m = \frac{i_{out}}{V_{in}} = g_m + \frac{1}{r_o}$$

$$\approx g_m \quad (\because g_m r_o \gg 1)$$

To find  $R_{out}$ :

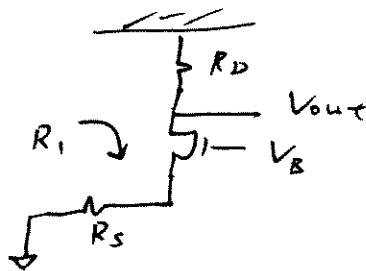

$$R_{out} = R_D \parallel R_i$$

$$= R_D \parallel [(1 + g_m r_o) R_s + r_o]$$

(from Eq. (7.110))

$$\approx R_D \parallel (g_m r_o R_s + r_o) \quad (\because g_m r_o \gg 1)$$

$$= \frac{g_m r_o R_s R_D + r_o R_D}{R_D + g_m r_o R_s + r_o}$$



$$\therefore \text{Voltage gain} = \beta_m \left[ \frac{\beta_m r_o R_D R_S + r_o R_D}{R_D + \beta_m r_o R_S + r_o} \right]$$

7.42 (a)

$$\begin{aligned}R_{out} &= R_D = 500 \Omega \\V_G &= V_{DD} \\V_D &> V_G - V_{TH} \text{ (in order for } M_1 \text{ to operate in saturation)} \\V_{DD} - I_D R_D &> V_{DD} - V_{TH} \\I_D &< \boxed{0.8 \text{ mA}}\end{aligned}$$

(b)

$$\begin{aligned}I_D &= 0.8 \text{ mA} \\R_{in} &= \frac{1}{g_m} \\&= \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} \\&= 50 \Omega \\ \frac{W}{L} &= \boxed{1250}\end{aligned}$$

(c)

$$\begin{aligned}A_v &= g_m R_D \\g_m &= \frac{1}{50} \text{ S} \\R_D &= 500 \Omega \\A_v &= \boxed{10}\end{aligned}$$

7.43 (a)

$$\begin{aligned}I_D &= I_1 = 1 \text{ mA} \\V_G &= V_{DD} \\V_D &= V_G - V_{TH} + 100 \text{ mV} \\V_{DD} - I_D R_D &= V_G - V_{TH} + 100 \text{ mV} \\R_D &= \boxed{300 \Omega}\end{aligned}$$

(b)


$$\begin{aligned}R_D &= 300 \Omega \\A_v &= g_m R_D \\&= \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D} \\&= 5 \\ \frac{W}{L} &= \boxed{694.4}\end{aligned}$$

7.44 For this problem, recall that looking into the drain of a transistor with a grounded gate and source we see a resistance of  $r_o$ , and looking into either terminal of a diode-connected transistor we see a resistance of  $\frac{1}{g_m} \parallel r_o$ .

(a) Referring to Eq. (7.109) with  $R_D = \frac{1}{g_{m2}}$  and  $g_m = g_{m1}$ , we have

$$A_v = \boxed{\frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_S}}$$

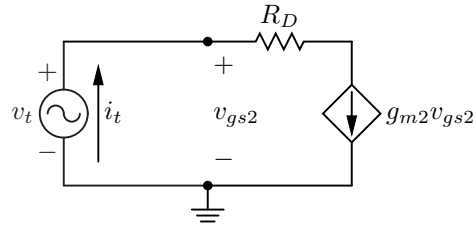(b) Let's draw a small-signal model to find the equivalent resistance seen looking up from the output.



$$i_t = g_{m2} v_{gs2}$$

$$v_{gs2} = v_t$$

$$i_t = g_{m2} v_t$$

$$\frac{v_t}{i_t} = \frac{1}{g_{m2}}$$

$$A_v = \boxed{\frac{g_{m1}}{g_{m2}}}$$

(c) Referring to Eq. (7.119) with  $R_D = \frac{1}{g_{m2}}$ ,  $R_3 = R_1$ , and  $g_m = g_{m1}$ , we have

$$A_v = \boxed{\frac{R_1 \parallel \frac{1}{g_{m1}}}{R_S + R_1 \parallel \frac{1}{g_{m1}}} \frac{g_{m1}}{g_{m2}}}$$

(d)

$$A_v = \boxed{g_{m1} \left( R_D + \frac{1}{g_{m2}} \parallel r_{o3} \right)}$$

(e)

$$A_v = \boxed{g_{m1} \left( R_D + \frac{1}{g_{m2}} \right)}$$

7.45 (a)

$$\begin{aligned}\frac{v_X}{v_{in}} &= -g_{m1} \left( R_{D1} \parallel \frac{1}{g_{m2}} \right) \\ \frac{v_{out}}{v_X} &= g_{m2} R_{D2} \\ \frac{v_{out}}{v_{in}} &= \frac{v_X}{v_{in}} \frac{v_{out}}{v_X} \\ &= \boxed{-g_{m1} g_{m2} R_{D2} \left( R_{D1} \parallel \frac{1}{g_{m2}} \right)}\end{aligned}$$

(b)

$$\lim_{R_{D1} \rightarrow \infty} -g_{m1} g_{m2} R_{D2} \left( R_{D1} \parallel \frac{1}{g_{m2}} \right) = \boxed{-g_{m1} R_{D2}}$$

This makes sense because the common-source stage acts as a transconductance amplifier with a transconductance of  $g_{m1}$ . The common-gate stage acts as a current buffer with a current gain of 1. Thus, the current  $g_{m1}v_{in}$  flows through  $R_{D2}$ , meaning  $v_{out} = -g_{m1}v_{in}R_{D2}$ , so that  $\frac{v_{out}}{v_{in}} = -g_{m1}R_{D2}$ .

This type of amplifier (with  $R_{D1} = \infty$ ) is known as a cascode and will be studied in detail in Chapter 9.

$$(46) \quad \frac{V_x}{V_{in}} = (R_{D1} \parallel \frac{1}{g_{m2}}) g_{m1}$$

$$\frac{V_{out}}{V_x} = g_{m2} R_{D2}$$


$$\therefore \frac{V_{out}}{V_{in}} = g_{m1} g_{m2} R_{D2} (R_{D1} \parallel \frac{1}{g_{m2}})$$

Similar to prob. (45), voltage gain approaches that of cascode stage as  $R_{D1}$  approaches infinity. The gain is  $g_{m1} R_{D2}$ .

47

With  $\lambda = 0$ ,  $M_1$  appears as a diode-connected device.


∴ the circuit becomes :

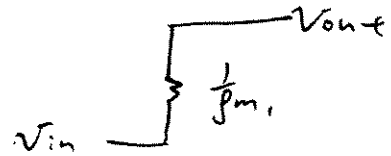

ie.  $\frac{v_{out}}{v_{in}} = 1 //$

This is not a common-gate amplifier, (CG) because the gate is not fixed. (ie. gate is not at an "a.c. ground").

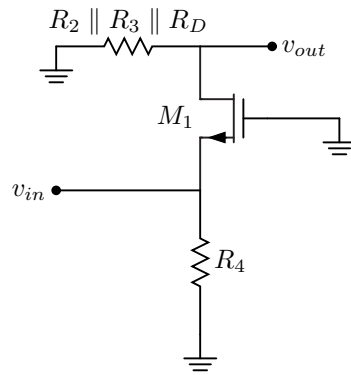7.48 For small-signal analysis, we can short the capacitors, producing the following equivalent circuit.



$$A_v = \boxed{g_m (R_2 \parallel R_3 \parallel R_D)}$$



7.49

$$V_{GS} = V_{DS}$$

$$V_{GS} = V_{DD} - I_D R_S = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS}) R_S$$

$$V_{GS} = V_{DS} = 0.7036 \text{ V}$$

$$I_D = 1.096 \text{ mA}$$

$$A_v = \frac{r_o \parallel R_S}{\frac{1}{g_m} + r_o \parallel R_S}$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = 6.981 \text{ mS}$$

$$r_o = \frac{1}{\lambda I_D} = 9.121 \text{ k}\Omega$$

$$A_v = \boxed{0.8628}$$

7.50

$$\begin{aligned}A_v &= \frac{R_S}{\frac{1}{g_m} + R_S} \\&= \frac{R_S}{\frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})} + R_S} \\&= 0.8\end{aligned}$$

$$V_{GS} = 0.64 \text{ V}$$

$$\begin{aligned}I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\&= 960 \text{ } \mu\text{A}\end{aligned}$$

$$\begin{aligned}V_G &= V_{GS} + V_S = V_{GS} + I_D R_S \\&= \boxed{1.12 \text{ V}}\end{aligned}$$

(51)

$$A_v = \frac{R_s}{\frac{1}{\beta_m} + R_s}$$
$$= 0.8$$

$$0.8 = \frac{500}{\frac{1}{\beta_m} + 500}$$

$$\therefore \beta_m = 8 \text{ mS.}$$

$$I_{ds} = \frac{1}{2} \beta (V_{gs} - V_t)^2,$$

$$\text{where } \beta = \left(\frac{w}{L}\right) \mu_n C_{ox}$$

$$\text{and } \beta_m = \beta (V_{gs} - V_t).$$

$$\therefore I_{ds} = \frac{1}{2} \beta_m (V_{gs} - V_t)$$

$$= \frac{1}{2} \beta_m (1.8 - I_{ds}(500) - 0.4)$$

$$I_{ds} = 4 \times 10^{-3} (1.4 - 500 I_{ds})$$

$$\therefore I_{ds} = 1.87 \text{ mA.}$$

$$\therefore \beta_m = \sqrt{2(200 \times 10^{-6}) \frac{w}{L} \times 1.87 \times 10^{-3}}$$

$$\therefore \frac{w}{L} \approx 85.7 //$$

52. To get  $R_{out} = 100 \Omega$ ,

$$\frac{1}{g_m} = 100$$

$$\therefore g_m = 10 \text{ mS.}$$

$$\therefore I_{ds} = \frac{1}{2} \beta (V_{gs} - V_{TH})^2$$

$$\text{where } \beta = \mu_n C_{ox} \frac{W}{L}$$

$$\text{and } g_m = \beta (V_{gs} - V_{TH})$$

$$\begin{aligned} \therefore I_{ds} &= \frac{1}{2} g_m (V_{gs} - V_{TH}) \\ &= \frac{1}{2} (10 \times 10^{-3}) (0.8 - 0.4) \end{aligned}$$

$$\therefore I_{ds} = 2.5 \text{ mA.}$$

$$\therefore g_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) (2.5 \times 10^{-3})}$$

$$\therefore \left(\frac{W}{L}\right) = 100 //$$

(53)

To get  $R_{out} = 50 \Omega$ ,

$$\frac{1}{f_m} = 50 \Omega$$

$$\therefore f_m = 20 \text{ mS}$$

$$\begin{aligned} \text{Power (P)} &= 1.8 \times I_{Ds} \\ &= 2 \times 10^{-3} \text{ W} \end{aligned}$$

$$\therefore I_{Ds} = 1.11 \text{ mA}$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) / \left(\frac{W}{L}\right) / (1.11 \text{ mA})}$$

$$\therefore \frac{W}{L} = 900 //$$

(54)

$$A_v = \frac{R_L}{\frac{1}{\beta_m} + R_L}$$

$$\therefore 0.8 = \frac{50}{\frac{1}{\beta_m} + 50}$$

$$\beta_m = 80 \text{ mS}$$

$$\begin{aligned} \text{Power (P)} &= 1.8 \times I_{DS} \\ &= 3 \text{ mW} \end{aligned}$$

$$\therefore I_{DS} = 1.67 \text{ mA}$$

$$\beta_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) (1.67 \times 10^{-3})}$$

$$\therefore \left(\frac{W}{L}\right) = \underline{\underline{9600}}$$

7.55 For this problem, recall that looking into the drain of a transistor with a grounded gate and source we see a resistance of  $r_o$ , and looking into either terminal of a diode-connected transistor we see a resistance of  $\frac{1}{g_m} \parallel r_o$ .

(a)

$$A_v = \frac{r_{o1} \parallel (R_S + r_{o2})}{\frac{1}{g_{m1}} + r_{o1} \parallel (R_S + r_{o2})}$$


(b) Looking down from the output we see an equivalent resistance of  $r_{o2} + (1 + g_{m2}r_{o2})R_S$  by Eq. (7.110).

$$A_v = \frac{r_{o1} \parallel [r_{o2} + (1 + g_{m2}r_{o2})R_S]}{\frac{1}{g_{m1}} + r_{o1} \parallel [r_{o2} + (1 + g_{m2}r_{o2})R_S]}$$

(c)

$$A_v = \frac{r_{o1} \parallel \frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + r_{o1} \parallel \frac{1}{g_{m2}}}$$

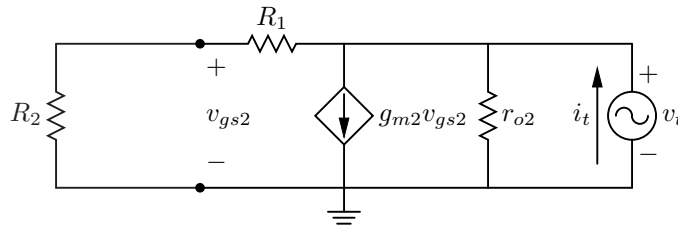(d) Let's draw a small-signal model to find the equivalent resistance seen looking down from the output.



$$i_t = \frac{v_t}{R_1 + R_2} + g_{m2}v_{gs2} + \frac{v_t}{r_{o2}}$$

$$v_{gs2} = \frac{R_2}{R_1 + R_2}v_t$$

$$i_t = \frac{v_t}{R_1 + R_2} + g_{m2}\frac{R_2}{R_1 + R_2}v_t + \frac{v_t}{r_{o2}}$$

$$i_t = v_t \left( \frac{1}{R_1 + R_2} + \frac{g_{m2}R_2}{R_1 + R_2} + \frac{1}{r_{o2}} \right)$$

$$\frac{v_t}{i_t} = (R_1 + R_2) \parallel \left( \frac{R_1 + R_2}{g_{m2}R_2} \right) \parallel r_{o2}$$

$$A_v = \frac{r_{o1} \parallel (R_1 + R_2) \parallel \left( \frac{R_1 + R_2}{g_{m2}R_2} \right) \parallel r_{o2}}{\frac{1}{g_{m1}} + r_{o1} \parallel (R_1 + R_2) \parallel \left( \frac{R_1 + R_2}{g_{m2}R_2} \right) \parallel r_{o2}}$$

(e)

$$A_v = \frac{r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m1}}}{\frac{1}{g_{m2}} + r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m1}}}$$

(f) Looking up from the output we see an equivalent resistance of  $r_{o2} + (1 + g_{m2}r_{o2})r_{o3}$  by Eq. (7.110).

$$A_v = \frac{r_{o1} \parallel [r_{o2} + (1 + g_{m2}r_{o2})r_{o3}]}{\frac{1}{g_{m1}} + r_{o1} \parallel [r_{o2} + (1 + g_{m2}r_{o2})r_{o3}]}$$



$$(56) \quad \frac{v_x}{v_{in}} = \frac{g_{m2}}{\frac{1}{g_{m1}} + g_{m2}}$$

$$\frac{v_{out}}{v_x} = g_{m2} R_D$$

$$\therefore \frac{v_{out}}{v_{in}} = \frac{R_D}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

b) if  $g_{m1} = g_{m2}$ ,

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1} R_D}{2}$$

(57)

$$\therefore R_{out} = 1k\Omega$$

$$\therefore R_D = 1k\Omega$$

$$\begin{aligned}\therefore A_v &= 5 \\ &= g_{m1} R_D\end{aligned}$$

$$\therefore g_{m1} (1000) = 5$$

$$g_{m1} = 5\text{mS}$$

$\therefore M_1$  is 00 mV away from triode,

$$V_D = (V_G - V_{TH}) + 0.1$$

$$V_D = (1.8 - 0.4) + 0.1$$

$$V_D = 1.5\text{V}$$

$$\therefore I_{D1} = \frac{1.8 - 1.5}{R_D} = \frac{0.3}{R_D}$$

$$= 0.3\text{mA}$$

$$\therefore g_{m1} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) I_{D1}}$$

$$\therefore \left(\frac{W}{L}\right) \approx 208$$

$$\therefore R_D = 1k\Omega, R_G = 10k\Omega, \left(\frac{W}{L}\right) = 208$$

7.58

$$P = V_{DD}I_D = 2 \text{ mW}$$

$$I_D = 1.11 \text{ mA}$$

$$R_D I_D = 1 \text{ V}$$

$$R_D = 900 \ \Omega$$

$$A_v = -g_m R_D$$

$$= -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D}$$

$$= -5$$

$$\frac{W}{L} = \boxed{69.44}$$

$$(59) \quad |A_v| = g_m R_L.$$

∴ To achieve maximum gain, use maximum  $R_L$ .

$$\text{i.e. set } R_D = 500 \Omega.$$

For maximum  $g_m$ , use maximum  $I_{D_s}$ .

(... while keeping  $M_1$  in saturation),

$$\text{i.e. } V_D \geq V_G - V_{TH}$$

$$1.8 - (I_{D_s})(500) \geq 1.8 - 0.4,$$

$$\therefore I_{D_s} \leq \frac{0.4}{500}$$

$$I_{D_s, \max} = 0.8 \text{ mA}.$$

Note: Setting a large  $R_D$  in this case would force  $I_{D_s, \max}$  to be lower (in order to keep  $M_1$  in saturation).

But since  $A_v \propto R_D$ , while  $A_v \propto \sqrt{I_{D_s}}$ , sacrificing  $I_{D_s}$  to get higher  $R_D$  would yield a higher gain.

7.60 Let's let  $R_1$  and  $R_2$  consume exactly 5 % of the power budget (which means the branch containing  $R_D$ ,  $M_1$ , and  $R_S$  will consume 95 % of the power budget). Let's also assume  $V_{ov} = V_{GS} - V_{TH} = 300$  mV exactly.

$$\begin{aligned}
 I_D V_{DD} &= 0.95(2 \text{ mW}) \\
 I_D &= 1.056 \text{ mA} \\
 I_D R_S &= 200 \text{ mV} \\
 R_S &= \boxed{189.5 \ \Omega} \\
 V_{ov} &= V_{GS} - V_{TH} = 300 \text{ mV} \\
 I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2 \\
 \frac{W}{L} &= \boxed{117.3} \\
 A_v &= -\frac{R_D}{\frac{1}{g_m} + R_S} \\
 &= -\frac{R_D}{\frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} + R_S} \\
 &= -4 \\
 R_D &= \boxed{1.326 \text{ k}\Omega} \\
 \frac{V_{DD}^2}{R_1 + R_2} &= 0.05(2 \text{ mW}) \\
 R_1 + R_2 &= \frac{V_{DD}^2}{0.1 \text{ mW}} \\
 V_G &= V_{GS} + I_D R_S = V_{ov} + V_{TH} + I_D R_S = 0.9 \text{ V} \\
 V_G &= \frac{R_2}{R_1 + R_2} V_{DD} \\
 &= \frac{R_2}{\frac{V_{DD}^2}{0.1 \text{ mW}}} = 0.9 \text{ V} \\
 R_2 &= \boxed{29.16 \text{ k}\Omega} \\
 R_1 &= \boxed{3.24 \text{ k}\Omega}
 \end{aligned}$$

7.61 Let's let  $R_1$  and  $R_2$  consume exactly 5 % of the power budget (which means the branch containing  $R_D$ ,  $M_1$ , and  $R_S$  will consume 95 % of the power budget).

$$R_D = 200 \Omega$$

$$I_D V_{DD} = 0.95(6 \text{ mW})$$

$$I_D = 3.167 \text{ mA}$$

$$I_D R_S = V_{ov} = V_{GS} - V_{TH}$$

$$R_S = \frac{V_{ov}}{I_D}$$

$$g_m = \frac{2I_D}{V_{ov}}$$

$$\begin{aligned} A_v &= -\frac{R_D}{\frac{1}{g_m} + R_S} \\ &= -\frac{R_D}{\frac{V_{ov}}{2I_D} + \frac{V_{ov}}{I_D}} \\ &= -5 \end{aligned}$$

$$V_{ov} = 84.44 \text{ mV}$$

$$R_S = \boxed{26.67 \Omega}$$

$$\frac{W}{L} = \frac{2I_D}{\mu_n C_{ox} V_{ov}^2} = \boxed{4441}$$

$$\frac{V_{DD}^2}{R_1 + R_2} = 0.05(6 \text{ mW})$$

$$R_1 + R_2 = \frac{V_{DD}^2}{0.3 \text{ mW}}$$

$$V_G = V_{GS} + I_D R_S = V_{ov} + V_{TH} + I_D R_S = 0.5689 \text{ V}$$

$$\begin{aligned} V_G &= \frac{R_2}{R_1 + R_2} V_{DD} \\ &= \frac{R_2}{\frac{V_{DD}^2}{0.3 \text{ mW}}} = 0.5689 \text{ V} \end{aligned}$$

$$R_2 = \boxed{6.144 \text{ k}\Omega}$$

$$R_1 = \boxed{4.656 \text{ k}\Omega}$$

$$R_{in} = R_1 = \boxed{20 \text{ k}\Omega}$$

$$P = V_{DD}I_D = 2 \text{ mW}$$

$$I_D = 1.11 \text{ mA}$$

$$V_{DS} = V_{GS} - V_{TH} + 200 \text{ mV}$$

$$V_{DD} - I_D R_D = V_{DD} - V_{TH} + 200 \text{ mV}$$

$$R_D = 180 \Omega$$

$$A_v = -g_m R_D$$

$$= -\sqrt{2\mu_n C_{ox} \frac{W}{L}} I_D R_D$$

$$= -6$$

$$\frac{W}{L} = \boxed{2500}$$

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}}$$

$$= 0.467 \text{ V}$$

$$V_{GS} = V_{DD} - I_D R_S$$

$$R_S = \boxed{1.2 \text{ k}\Omega}$$

$$\frac{1}{2\pi f C_1} \ll R_1$$

$$\frac{1}{2\pi f C_1} = \frac{1}{10} R_1$$

$$f = 1 \text{ MHz}$$

$$C_1 = \boxed{79.6 \text{ pF}}$$

$$\frac{1}{2\pi f C_S} \parallel R_S \ll \frac{1}{g_m}$$

$$\frac{1}{2\pi f C_S} = \frac{1}{10} \frac{1}{g_m}$$

$$g_m = \sqrt{2\mu_n C_{ox} \frac{W}{L}} I_D = 33.33 \text{ mS}$$

$$C_S = \boxed{52.9 \text{ nF}}$$

63. Power  $(P) = 2 \text{ mW}$ ,

$$\therefore I_{DS1} = |I_{DS2}| = \frac{2 \text{ mW}}{1.8 \text{ V}} = 1.11 \text{ mA}$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda I_{DS}}$$
$$= \frac{1}{0.1 \times 1.11 \times 10^{-3}}$$
$$= 9000 \Omega$$

$$f_{\text{ain}} (A_v) = f_{m1} (r_{o1} \parallel r_{o2}) = 20,$$

$$f_{m1} \left( \frac{9000}{2} \right) = 20$$

$$\therefore f_{m1} = 4.44 \text{ mS}$$

$$\text{Set } V_{DS1} \text{ (ie. } V_{out}) = 1.2 \text{ V}$$

$$\text{(which is } < 1.5 \text{ V)}$$

$$\therefore V_{IN} = V_{GS1} \leq 1.2 + V_{TH}$$

(for  $M_1$  to stay in saturation)

$$\text{Set } V_{GS1} = 1.2 \text{ V}$$

$$\therefore f_{m1} = \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS1} - V_{TH})$$

$$\left( \frac{W}{L} \right)_1 = 27.75$$

For  $M_2$ ,  $\therefore M_2$  must be in saturation

for  $V_{out} \leq 1.5 \text{ V}$ .

$$\therefore V_{DD} - V_B \leq V_{DD} - 1.5 \text{ V} + V_{TH}$$

$$\therefore V_B \geq 1.1 \text{ V}$$



$$\text{Set } V_B = 1.2V$$

$$|I_{DS2}| = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (|V_{GS2}| - V_{TH})^2 \\ (1 + \lambda |V_{DS2}|)$$

$$1.11 \times 10^{-3} = \frac{1}{2} \times 100 \times 10^{-6} \left( \frac{W}{L} \right)_2 (0.6 - 0.2)^2 \\ (1 + 0.1 \times (1.8 - 1.5))$$

$$(\text{assuming } V_{out} = 1.5V)$$

$$\therefore \left( \frac{W}{L} \right)_2 \approx 135$$

$$\therefore \left( \frac{W}{L} \right)_1 = 27.75 \quad \left( \frac{W}{L} \right)_2 = 135$$

$$V_{ZN} = 1.2 \quad V_b = 1.1$$

$$I_{DS1} = I_{DS2} = 1.11 \text{ mA}$$

7.64 (a)

$$A_v = \boxed{-g_{m1} (r_{o1} \parallel R_G \parallel r_{o2})}$$

(b)

$$P = V_{DD} I_{D1} = 3 \text{ mW}$$

$$I_{D1} = |I_{D2}| = 1.67 \text{ mA}$$

$$|V_{GS2}| = |V_{DS2}| = V_{DS} = \frac{V_{DD}}{2}$$

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (|V_{GS2}| - |V_{TH}|)^2 (1 + \lambda_p |V_{DS2}|)$$

$$\left( \frac{W}{L} \right)_2 = \boxed{113}$$

$$A_v = -g_{m1} (r_{o1} \parallel R_G \parallel r_{o2})$$

$$R_G = 10 (r_{o1} \parallel r_{o2})$$

$$r_{o1} = \frac{1}{\lambda_n I_{D1}} = 6 \text{ k}\Omega$$

$$r_{o2} = \frac{1}{\lambda_p |I_{D2}|} = 3 \text{ k}\Omega$$

$$R_G = 10 (r_{o1} \parallel r_{o2}) = \boxed{20 \text{ k}\Omega}$$

$$A_v = -\sqrt{2\mu_n C_{ox} \left( \frac{W}{L} \right)_1} I_{D1} (r_{o1} \parallel R_G \parallel r_{o2})$$

$$= -15$$

$$\left( \frac{W}{L} \right)_1 = \boxed{102.1}$$

$$V_{IN} = V_{GS1} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \left( \frac{W}{L} \right)_1 (1 + \lambda_n V_{DS1})}}$$

$$= \boxed{0.787 \text{ V}}$$

65) Impedance looking into drain of  $M_2$

$$= (1 + g_{m2} r_{o2}) R_s + r_{o2}$$

$$= 10 r_{o1}$$

Assume  $g_{m2} r_{o2} \gg 1$ ,

$$\therefore g_{m2} r_{o2} R_s + r_{o2} \approx 10 r_{o1}$$

$$\therefore r_{o1} = r_{o2} \quad (\lambda_1 = \lambda_2 \text{ and } I_{D1} = |I_{D2}|)$$

$$\therefore g_{m2} R_s + 1 = 10$$

$$g_{m2} R_s = 9 \quad \text{--- (1)}$$

Given  $V_B = 1V$ ,

$$\text{Set } |V_{GS2}| = 0.6V, \quad (\text{ie. } V_{GS2} - V_{TH} = 0.2V)$$

$$\therefore V_{S2} = 1.6V$$

$$\therefore V_{RS} = 1.8V - 1.6V = 0.2V$$

$$\therefore \text{Power} = 2mW$$

$$I_{D1} = |I_{D2}| = \frac{2mW}{1.8V} = 1.11mA$$

$$\therefore R_s = \frac{V_{RS}}{1.11 \times 10^{-3}} \approx 180 \Omega //$$

$$\text{From (1), } g_{m2} = \frac{9}{180} = 50 \text{ mS}$$

$$\therefore g_{m2} = \left(\frac{W}{L}\right)_2 (100 \times 10^{-6}) (V_{GS2} - V_{TH})$$

$$\therefore \left(\frac{W}{L}\right)_2 = 2500 //$$

$$b). \text{Gain } (A_v) = f_{m_1} (r_{o1} // 10r_{o1})$$

$$30 = f_{m_1} (0.909 r_{o1})$$

$$r_{o1} = \frac{1}{0.1 \times 1.1 \times 10^{-3}}$$

$$= 9009 \Omega$$

$$\therefore f_{m_1} = 3.66 \text{ mS.}$$

$$\therefore f_{m_1} = \sqrt{2} (M_n C_{ox}) \left( \frac{W}{L} \right)_1 \times I_{DS1}$$

$$\therefore \left( \frac{W}{L} \right)_1 \approx 30.2 //$$

$$P = V_{DD}I_{D1} = 1 \text{ mW}$$

$$I_{D1} = |I_{D2}| = 556 \text{ } \mu\text{A}$$

$$V_{ov1} = V_{GS1} - V_{TH} = \sqrt{2I_D\mu_n C_{ox}} \left(\frac{W}{L}\right)_1 = 200 \text{ mV}$$

$$\left(\frac{W}{L}\right)_1 = \boxed{138.9}$$

$$A_v = -\frac{g_{m1}}{g_{m2}}$$

$$= -\frac{\sqrt{2\mu_n C_{ox}} \left(\frac{W}{L}\right)_1 I_{D1}}{\sqrt{2\mu_n C_{ox}} \left(\frac{W}{L}\right)_2 |I_{D2}|}$$

$$= -\sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}}$$

$$= -4$$

$$\left(\frac{W}{L}\right)_2 = \boxed{8.68}$$

$$V_{IN} = V_{GS1} = V_{ov1} + V_{TH} = \boxed{0.6 \text{ V}}$$

7.67

$$P = V_{DD}I_D = 3 \text{ mW}$$

$$I_D = I_1 = \boxed{1.67 \text{ mA}}$$

$$R_{in} = \frac{1}{g_m} = \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} = 50 \Omega$$

$$\frac{W}{L} = \boxed{600}$$

$$A_v = g_m R_D = \frac{1}{50 \Omega} R_D = 5$$

$$R_D = \boxed{250 \Omega}$$

$$P = V_{DD}I_D = 2 \text{ mW}$$

$$I_D = 1.11 \text{ mA}$$

$$V_D = V_G - V_{TH} + 100 \text{ mV}$$

$$V_{DD} - I_D R_D = V_G - V_{TH} + 100 \text{ mV}$$

$$V_G = V_{DD}$$

$$A_v = g_m R_D = \frac{2I_D}{V_{GS} - V_{TH}} R_D = 4$$

$$R_D = A_v \frac{V_{GS} - V_{TH}}{2I_D}$$

$$V_{DD} - I_D A_v \frac{V_{GS} - V_{TH}}{2I_D} = V_{DD} - V_{TH} + 100 \text{ mV}$$

$$V_{GS} = 0.55 \text{ V}$$

$$R_D = \boxed{270 \Omega}$$

$$V_S = V_{DD} - V_{GS} = I_D R_S$$

$$R_S = \boxed{1.125 \text{ k}\Omega}$$

$$\frac{W}{L} = \frac{2I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} = \boxed{493.8}$$

69

$$\text{Power} = 5 \text{ mW}$$

$$\therefore I_{DS1} = \frac{5 \times 10^{-3}}{1.8} = 2.78 \text{ mA}$$

$$\text{Gain } (A_v) = \beta_m R_D = 5$$

$$V_{GS1} = V_{OUT} = 1.8 - I R_D$$

$$V_{S1} = I R_S$$

$$\text{Let } R_S = \frac{10}{\beta_m}$$

$$\therefore V_{S1} = \frac{10 I}{\beta_m}$$

$$\therefore V_{GS1} = 1.8 - I R_D - \frac{10 I}{\beta_m}$$

$$\therefore I_{DS1} = \frac{1}{2} \beta_m (V_{GS1} - V_{T4})$$

$$\begin{aligned} 2.78 \times 10^{-3} &= \frac{\beta_m}{2} \left( 1.8 - 2.78 \times 10^{-3} R_D - \frac{2.78 \times 10^{-2}}{\beta_m} \right) \\ &= 0.9 \beta_m - 1.39 \times 10^{-3} \beta_m R_D - 1.39 \times 10^{-2} \end{aligned}$$

$$\therefore \beta_m R_D = A_v = 5$$

$$2.78 \times 10^{-3} = 0.9 \beta_m - 6.95 \times 10^{-3} - 1.39 \times 10^{-2}$$

$$\therefore \beta_m \approx 26.3 \text{ mS}$$

$$\text{and } R_D = \frac{5}{26.3 \times 10^{-3}} \approx 190 \Omega //$$

$$R_S = \frac{10}{26.3 \times 10^{-3}} = 380 \Omega //$$

$$\therefore \beta_m = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_{DS1}} \Rightarrow \left(\frac{W}{L}\right) \approx 622 //$$



(70)

$$\therefore R_s \approx \frac{10}{\beta_m}$$

$$\therefore R_{in} \approx \frac{1}{\beta_m} = 50 \Omega$$

$$\text{i.e. } \beta_m = 20 \text{ mS} //$$

$$| \text{gain (AV)} | = \frac{\beta_m R_D}{1 + \beta_m R_s} = 4$$

$$\beta_m R_D = 4 + 4 \beta_m R_s$$

$$R_D = \frac{4 + 0.08 R_s}{0.02} = 200 + 4 R_s \quad \text{--- (1)}$$

$$\therefore R_s I_D + V_{GS} - V_{TH} + 0.25 = 1.8 - I_D R_D \quad (\text{given})$$

$$\text{and } I_D = \frac{1}{2} \beta_m (V_{GS} - V_{TH})$$

$$\text{i.e. } V_{GS} - V_{TH} = 100 I_D$$

$$\therefore R_s I_D + 100 I_D + 0.25 = 1.8 - I_D R_D$$

From (1):

$$R_s I_D + 100 I_D + 0.25 = 1.8 - 200 I_D - 4 I_D R_s$$

$$5 R_s I_D + 300 I_D = 1.55$$

$$\text{See } R_s = \frac{10}{\beta_m} = 500 \Omega$$

$$\therefore 2500 I_D + 300 I_D = 1.55$$

$$\therefore I_D = 0.554 \text{ mA} //$$

$$\therefore I_D = \frac{1}{2} \beta_m (V_{GS} - V_{TH})$$

$$0.554 \times 10^{-3} = \frac{1}{2} \times 20 \times 10^{-3} (V_{GS} - 0.4)$$

$$\therefore V_{GS} = 0.455 \text{ V}$$

To find  $(\frac{W}{L})$ :

$$f_m = \sqrt{2 \left( \frac{W}{L} \right) \mu_n C_{ox} I_{D1}}$$

$$\therefore \left( \frac{W}{L} \right) \approx 1805$$

To find  $R_D$ :

$$\therefore R_D = 200 + 4R_S \quad (\text{from (1)})$$

$$R_D = 2200$$

To find  $R_1$  and  $R_2$ ,

$$\therefore R_1 + R_2 = 20 \text{ k}\Omega$$

$$\text{and } V_{GS} = V_G - I_D R_S = 0.455 \text{ V}$$

$$\text{i.e. } V_G = 0.732 \text{ V}$$

$$V_G = \frac{R_2}{R_1 + R_2} \times V_{DD}$$

$$\therefore R_1 = 8133 \Omega$$

$$R_2 \approx 11.9 \text{ k}\Omega$$

$$\therefore R_1 = 8133 \Omega, R_2 = 11.9 \text{ k}\Omega, R_D = 2200 \Omega, R_S = 500 \Omega$$

$$\left( \frac{W}{L} \right) = 1805 \quad I_{D1} = 0.554 \text{ mA}$$

(71)

$$R_{in} = R_g = 10 \text{ k}\Omega //$$

$$\text{Power} = 2 \text{ mW}$$

$$\therefore I_{DS} = \frac{2 \text{ mW}}{1.8 \text{ V}} = 1.11 \text{ mA} //$$

$$A_v = \frac{R_s}{\frac{1}{\beta_m} + R_s} = 0.8$$

$$\therefore R_s = \frac{4}{\beta_m} \quad \text{--- (1)}$$

$$\therefore V_{out} = \frac{V_{DD}}{2} = I_{DS} R_s$$

$$I_{DS} R_s = 0.9 \quad \text{--- (2)}$$

$$\therefore V_G = 1.8 \text{ V and } V_S = 0.9$$

$$\therefore V_{GS} = 0.9 \text{ V}$$

$$\text{From (2), } \therefore I_{DS} = 1.11 \text{ mA}$$

$$R_s = \frac{0.9 \text{ V}}{1.11 \text{ mA}} \approx 810 \Omega //$$

$$\text{From (1), } \beta_m = \frac{4}{810 \Omega} \approx 4.94 \text{ mS}$$

$$\therefore \beta_m = \left(\frac{W}{L}\right) (\mu_n C_{ox}) (V_{GS} - V_{TH})$$

$$\frac{W}{L} \approx 49.4 //$$

72

$$R_{in} = R_g = 20k\Omega$$

$$\therefore \text{Power} = 3\text{mW}$$

$$\therefore I_{DS} = \frac{3\text{mW}}{1.8\text{V}} = 1.67\text{mA}$$


$$V_{x,ac\&dc} = I_{DS} R_s = 0.9\text{V}$$

$$\therefore R_s = 540\Omega$$

$$\text{Load impedance, } Z_L = R_s \parallel \left( \frac{1}{sC_1} + R_L \right)$$

(at 100 MHz)
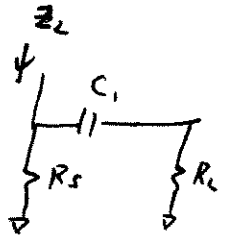
$$= 540 \parallel \left( \frac{1}{2\pi \times 10^8 C_1} + 50 \right)$$



$$\text{Voltage gain } (A_v) = \frac{Z_L}{f_m + Z_L}$$

$$f_m = \frac{2I_{DS}}{V_{GS} - V_{TH}}$$

$$= \frac{2 \times 1.67 \times 10^{-3}}{(1.8 - 0.9) - 0.4}$$

$$= 6.67\text{ms}^{-1}$$

$$\therefore A_v = \frac{Z_L}{f_m + Z_L} = 0.8$$

$$Z_L = 120 + Z_L (0.8)$$

$$\therefore Z_L = 150$$

$$\therefore 150 = 540 \parallel \left( \frac{1}{2\pi \times 10^8 C_1} + 50 \right)$$

$$= 540 \parallel \left[ \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1} \right]$$

$$= \frac{540 \times \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1}}{540 + \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1}}$$

$$\therefore \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1} \approx 208$$

$$\therefore C_1 \approx 10.1 \text{ pF} //$$

To find  $\left(\frac{W}{L}\right)$ :

$$\therefore f_m = \left(\frac{W}{L}\right) \mu_n C_{ox} (V_{GS} - V_{TH})$$

$$\frac{W}{L} = 66.7 //$$


$$\therefore \frac{W}{L} = 66.7, C_1 = 10.1 \text{ pF}, R_S = 540 \Omega.$$

$$\begin{aligned}
P &= V_{DD}I_{D1} = 3 \text{ mW} \\
I_{D1} &= I_{D2} = 1.67 \text{ mA} \\
A_v &= \frac{r_{o1} \parallel r_{o2}}{\frac{1}{g_{m1}} + r_{o1} \parallel r_{o2}} \\
&= \frac{r_{o1} \parallel r_{o2}}{\frac{1}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}} + r_{o1} \parallel r_{o2}} \\
&= 0.9 \\
r_{o1} &= r_{o2} = \frac{1}{\lambda I_{D1}} = 6 \text{ k}\Omega \\
\left(\frac{W}{L}\right)_1 &= \boxed{13.5}
\end{aligned}$$


Let  $V_{ov2} = V_{GS2} - V_{TH} = 0.3 \text{ V}$ . Let's assume that  $V_{OUT} = V_{DS2} = V_{ov2}$ .

$$\begin{aligned}
V_{GS2} &= V_b = V_{ov2} + V_{TH} = \boxed{0.7 \text{ V}} \\
\left(\frac{W}{L}\right)_2 &= \frac{2I_{D2}}{\mu_n C_{ox} (V_{GS2} - V_{TH})^2 (1 + \lambda V_{DS2})} \\
&= \boxed{161} \\
V_{GS1} &= V_{TH} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (1 + \lambda V_{DS1})}} \\
V_{DS1} &= V_{DD} - V_{DS2} = 1.5 \text{ V} \\
V_{GS1} &= 1.44 \text{ V} \\
V_{IN} &= V_{GS1} + V_{DS2} = \boxed{1.74 \text{ V}}
\end{aligned}$$

8.1

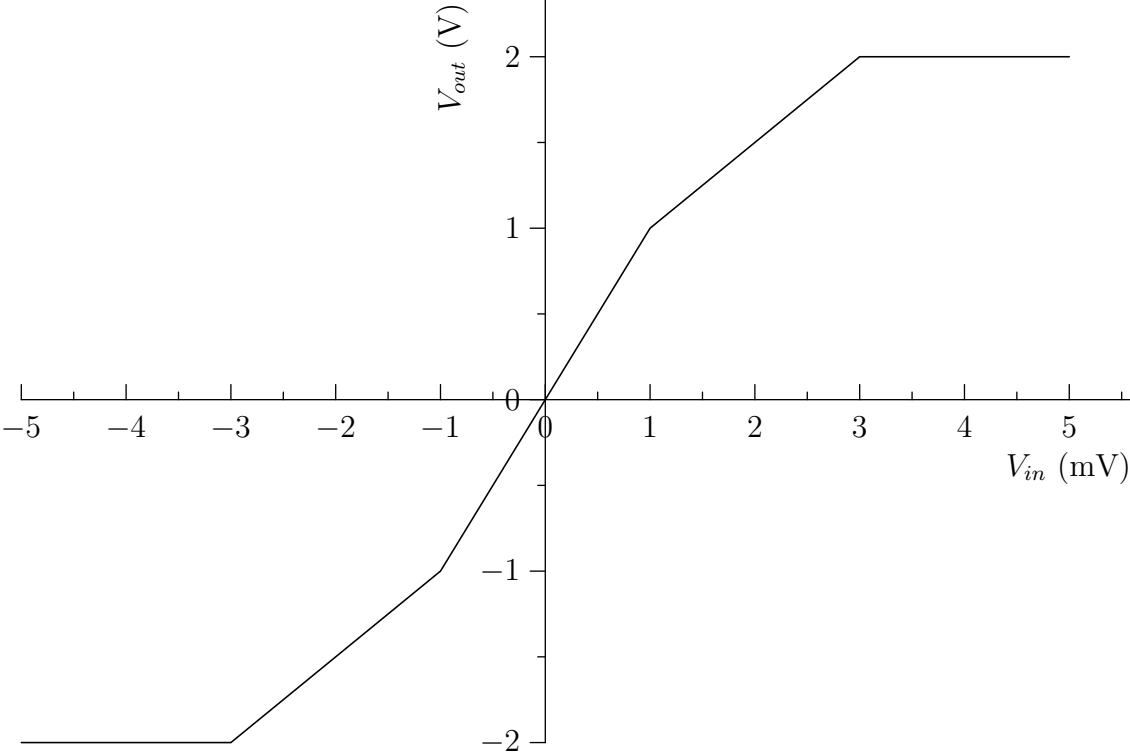
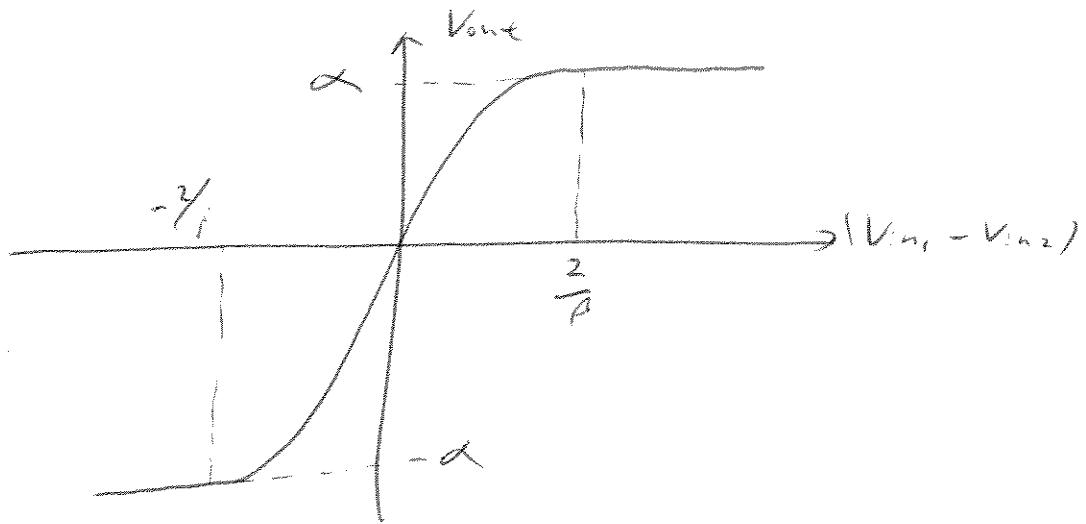
$$(2) \quad V_{out} = \alpha \tanh \left[ \beta (V_{in1} - V_{in2}) \right]$$



To find small-signal gain,

$$\therefore \tanh z = z - \frac{1}{3} z^3 + \frac{2}{15} z^5 + \dots$$

$\therefore$  for  $\beta (V_{in1} - V_{in2}) \approx 0$ ,

$$\frac{d V_{out}}{d (V_{in1} - V_{in2})} \approx \frac{d}{d (V_{in1} - V_{in2})} \alpha \beta (V_{in1} - V_{in2})$$

$$= \underline{\underline{\alpha \beta}}$$



$$\textcircled{3} \quad \text{closed-loop gain} = \left(1 + \frac{R_1}{R_2}\right)$$

$$= 8$$

$$\text{Gain error} = \left(1 + \frac{R_1}{R_2}\right) (A_0)^{-1}$$

$$= \frac{8}{2000}$$

$$= \underline{\underline{0.4\%}}$$

$$\textcircled{4} \quad \text{closed loop gain} = \left(1 + \frac{R_1}{R_2}\right)$$

$$= 4$$

$$\text{Gain error} = \left(1 + \frac{R_1}{R_2}\right) \left(\frac{1}{A_0}\right)$$

$$= 0.1\%$$

$$\therefore 4/A_0 = 0.1\%$$

$$A_0 = \underline{\underline{4000}}$$

$$\textcircled{5} \quad \text{Let } G_0 = \left(1 + \frac{R_1}{R_2}\right)$$

$$\text{Desired gain} = \alpha_1$$

$$= \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0}$$

$$\therefore \alpha_1 = \frac{A_0}{1 + \frac{A_0}{G_0}}$$

$$1 + \frac{A_0}{G_0} = \frac{A_0}{\alpha_1}$$

$$\frac{1}{G_0} = \frac{1}{\alpha_1} - \frac{1}{A_0}$$

$$G_0 = \frac{A_0 \alpha_1}{A_0 - \alpha_1}$$

$$\therefore \frac{R_2}{R_1 + R_2} = \frac{1}{G_0} = \frac{1}{\alpha_1} - \frac{1}{A_0} //$$

b) if  $A_0$  drops to  $0.6 A_0$ ,

$$\text{Actual gain} = \frac{0.6 A_0}{1 + \left(\frac{1}{\alpha_1} - \frac{1}{A_0}\right) 0.6 A_0}$$

$$= \frac{0.6 A_0}{0.4 + \frac{0.6 A_0}{\alpha_1}}$$

⑤ b) (cont'd)


$$\text{Actual gain} = \frac{\alpha_1}{1 + \frac{0.4}{0.6} \frac{\alpha_1}{A_0}}$$

$$\approx \alpha_1 \left( 1 - \frac{0.4}{0.6} \frac{\alpha_1}{A_0} \right)$$

$$\therefore \text{the gain error} = \frac{0.4}{0.6} \frac{\alpha_1^2}{A_0}$$

$$= \frac{2}{3} \frac{\alpha_1^2}{A_0}$$

⑥ Using the model in Fig. 8.44,

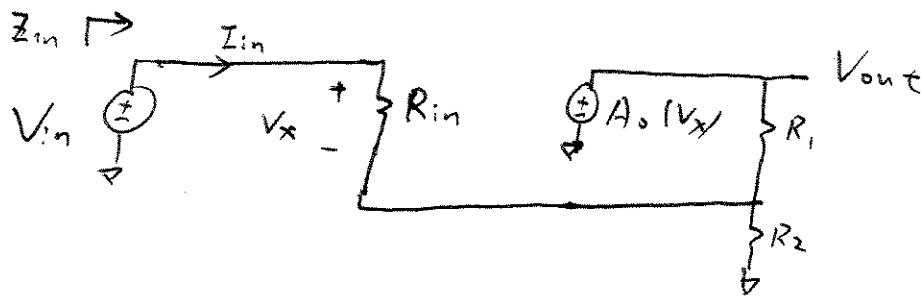

$$V_x = V_{in} - V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = A_0 V_x$$

$$= A_0 \left( V_{in} - V_{out} \frac{R_1}{R_1 + R_2} \right)$$

$$A_0 V_{in} = V_{out} \left( 1 + A_0 \frac{R_1}{R_1 + R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0}{1 + A_0 \frac{R_1}{R_1 + R_2}} \quad \text{--- ①}$$

To find input impedance ( $Z_{in}$ ),

$$I_{in} = \frac{V_x}{R_{in}}$$

$$= \frac{1}{R_{in}} \left( V_{in} - V_{out} \frac{R_1}{R_1 + R_2} \right)$$

$$= \frac{V_{in}}{R_{in}} \left( 1 - \frac{V_{out}}{V_{in}} \frac{R_1}{R_1 + R_2} \right)$$

⑥ (cont'd)

$$\begin{aligned} I_{in} &= \frac{V_{in}}{R_{in}} \left( 1 - \frac{A_o}{1 + A_o \frac{R_1}{R_1 + R_2}} \frac{R_1}{R_1 + R_2} \right) \\ &= \frac{V_{in}}{R_{in}} \left( 1 - \frac{1}{\frac{R_1 + R_2}{A_o R_1} + 1} \right) \\ &= \frac{V_{in}}{R_{in}} \left( \frac{\frac{R_1 + R_2}{A_o R_1}}{\frac{R_1 + R_2}{A_o R_1} + 1} \right) \end{aligned}$$


$$\therefore Z_{in} = \frac{V_{in}}{I_{in}} = R_{in} \left[ \frac{1 + \frac{R_1 + R_2}{A_o R_1}}{\frac{R_1 + R_2}{A_o R_1}} \right] \quad \text{--- (2)}$$

As  $A_o \rightarrow \infty$ ,

$$\begin{aligned} \text{Gain} &= \frac{V_{out}}{V_{in}} \Big|_{A_o \rightarrow \infty} \quad [\text{From (1)}] \\ &= 1 + \frac{R_2}{R_1} // \end{aligned}$$

$$\begin{aligned} Z_{in} &= \frac{V_{in}}{I_{in}} \Big|_{A_o \rightarrow \infty} \quad [\text{From (2)}] \\ &= \infty // \end{aligned}$$

7

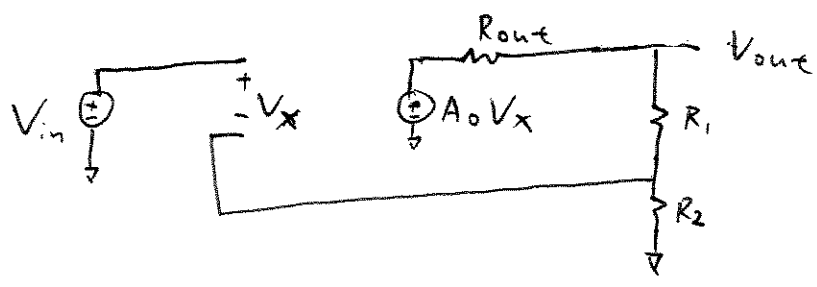

Similar to Prob. (6),

$$\text{gain} = \frac{V_{out}}{V_{in}}$$

$$V_x = V_{in} - V_{out} \frac{R_2}{R_1 + R_2}$$


$$V_{out} = A_0 V_x \frac{R_1 + R_2}{R_{out} + R_1 + R_2}$$

$$= A_0 \left( V_{in} - V_{out} \frac{R_2}{R_1 + R_2} \right) \frac{R_1 + R_2}{R_{out} + R_1 + R_2}$$

$$V_{in} A_0 \frac{R_1 + R_2}{R_{out} + R_1 + R_2} = V_{out} \left( 1 + \frac{A_0 R_2}{R_{out} + R_1 + R_2} \right)$$

$$\frac{V_{out}}{V_{in}} = \frac{A_0 \frac{R_1 + R_2}{R_{out} + R_1 + R_2}}{1 + \frac{A_0 R_2}{R_{out} + R_1 + R_2}}$$

To find output impedance ( $Z_{out}$ )

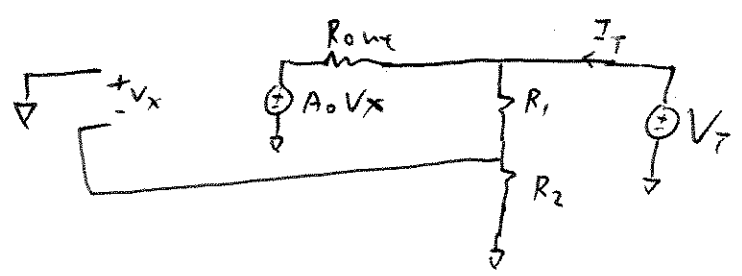

$$(7) \text{ (cont'd)} \quad V_x = \frac{R_2}{R_1 + R_2} V_T$$

$$\begin{aligned} I_T &= \frac{V_T}{R_1 + R_2} + \frac{V_T - A_o V_x}{R_{out}} \\ &= V_T \left[ \frac{R_{out} + R_1 + R_2 - A_o R_2}{(R_{out})(R_1 + R_2)} \right] \end{aligned}$$

$$Z_{out} = \frac{V_T}{I_T} = \frac{(R_{out})(R_1 + R_2)}{R_{out} + R_1 + R_2 - A_o R_2}$$


As  $A_o \rightarrow \infty$ ,

$$\text{gain} = 1 + \frac{R_1}{R_2} //$$

$$Z_{out} = 0 //$$



8

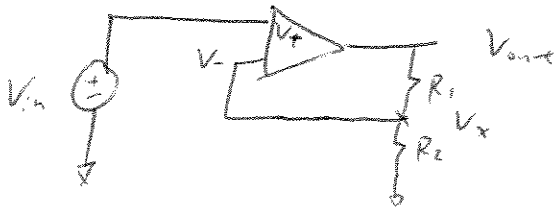

$\Delta R$  for now.

$$V_{out} = A_o (V_x)$$

$$V_x = V_{in} - \frac{R_2}{R_1 + R_2} V_{out}$$

$$\therefore \frac{-V_{out}}{A_o} = V_{in} - \frac{R_1}{R_1 + R_2} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{A_o (R_1 + R_2)}{A_o R_1 - 1} = \text{nominal gain}$$

$$\text{if } R_2' = \Delta R + R_2$$

$$\left( \frac{V_{out}}{V_{in}} \right)' = \frac{A_o (R_1 + \Delta R + R_2)}{A_o R_1 - 1}$$

$$\therefore \text{gain error} = \frac{\left( \frac{V_{out}}{V_{in}} \right)' - \left( \frac{V_{out}}{V_{in}} \right)}{\frac{V_{out}}{V_{in}}}$$

$$= \frac{\Delta R}{A_o R_1 - 1} \times \frac{A_o R_1 - 1}{A_o (R_1 + R_2)}$$

$$= \frac{\Delta R}{A_o (R_1 + R_2)} //$$

$$\textcircled{9} \quad \text{Closed-loop gain} \approx \left(1 + \frac{R_1}{R_2}\right) \left[1 - \left(1 + \frac{R_1}{R_2}\right) \frac{1}{A_0}\right]$$

$$= 5 \left[1 - \frac{5}{A_0}\right]$$

∴ As  $A_0$  decreases to  $0.8A_0$ , closed-loop gain decreases along. (deviating more from the nominal)

$A_0$  drops to  $0.8A_0$  when  $|V_{in1} - V_{in2}| = 2\text{mV}$ .

$$\therefore V_{in2} = V_{out} \left(\frac{R_2}{R_1 + R_2}\right)$$


$$\text{and } V_{out} = 5 \left(1 - \frac{5}{A_0}\right) V_{in1}$$

$$\therefore V_{in2} = 5 \left(1 - \frac{5}{A_0}\right) \left(\frac{1}{5}\right) V_{in1}$$

$$V_{in1} - V_{in2} = \frac{5}{A_0} V_{in1}$$

$$\text{At } V_{in1} - V_{in2} = 2\text{mV},$$

$$V_{in1} = \frac{A_0}{5} (2\text{mV})$$

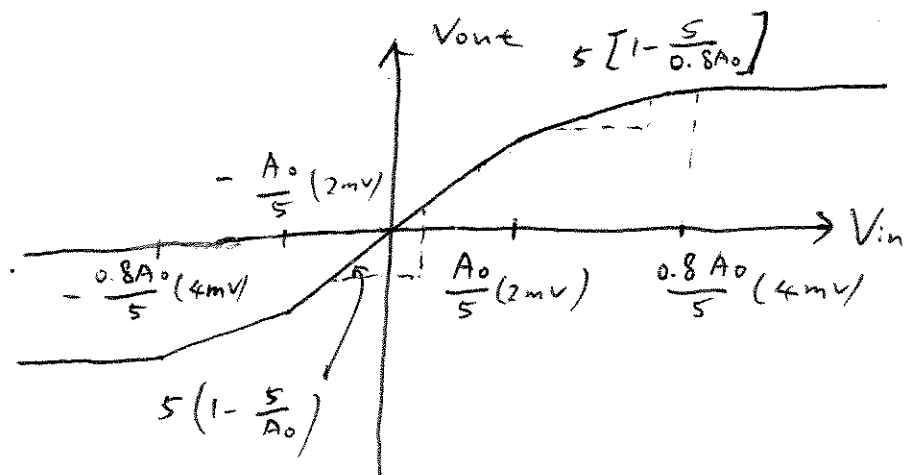

(10)

$$\frac{V_{out}}{V_{in}} = 1 + \frac{R_1}{R_2}$$

$$\therefore V_{in} = 1V, \quad V_{out} = 1 + \frac{R_1}{R_0 + \Delta W}$$

$$\frac{dV_{out}}{dW} = -R_1 \Delta (R_0 + \Delta W)^{-2}$$

$$= \frac{-R_1 \Delta}{(R_0 + \Delta W)^2}$$

$$\begin{aligned}
V_- &= V_+ = V_{in} \\
V_- &= \frac{R_4 \parallel (R_2 + R_3)}{R_1 + R_4 \parallel (R_2 + R_3)} \frac{R_2}{R_2 + R_3} V_{out} = V_{in} \\
\frac{V_{out}}{V_{in}} &= \left[ \frac{R_4 \parallel (R_2 + R_3)}{R_1 + R_4 \parallel (R_2 + R_3)} \frac{R_2}{R_2 + R_3} \right]^{-1} \\
&= \boxed{\frac{(R_2 + R_3) [R_1 + R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]}}
\end{aligned}$$

If  $R_1 \rightarrow 0$ , we expect the result to be:

$$\begin{aligned}
V_{in} &= \frac{R_2}{R_2 + R_3} V_{out} \\
\left. \frac{V_{out}}{V_{in}} \right|_{R_1=0} &= \frac{R_2 + R_3}{R_2} = 1 + \frac{R_3}{R_2}
\end{aligned}$$

Taking limit of the original expression as  $R_1 \rightarrow 0$ , we have:

$$\begin{aligned}
\lim_{R_1 \rightarrow 0} \frac{(R_2 + R_3) [R_1 + R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]} &= \frac{(R_2 + R_3) [R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]} \\
&= 1 + \frac{R_3}{R_2}
\end{aligned}$$

This agrees with the expected result. Likewise, if  $R_3 \rightarrow 0$ , we expect the result to be:

$$\begin{aligned}
V_{in} &= \frac{R_2 \parallel R_4}{R_1 + R_2 \parallel R_4} V_{out} \\
\left. \frac{V_{out}}{V_{in}} \right|_{R_3=0} &= \frac{R_1 + R_2 \parallel R_4}{R_2 \parallel R_4} \\
&= 1 + \frac{R_1}{R_2 \parallel R_4}
\end{aligned}$$

Taking the limit of the original expression as  $R_3 \rightarrow 0$ , we have:

$$\begin{aligned}
\lim_{R_3 \rightarrow 0} \frac{(R_2 + R_3) [R_1 + R_4 \parallel (R_2 + R_3)]}{R_2 [R_4 \parallel (R_2 + R_3)]} &= \frac{R_2 (R_1 + R_2 \parallel R_4)}{R_2 (R_2 \parallel R_4)} \\
&= \frac{R_1 + R_2 \parallel R_4}{R_2 \parallel R_4} \\
&= 1 + \frac{R_1}{R_2 \parallel R_4}
\end{aligned}$$


This agrees with the expected result.

$$\begin{aligned} \textcircled{12} \quad \text{Gain Error} &= \frac{1}{A_0} \left( 1 + \frac{R_1}{R_2} \right) \\ &= \frac{1}{A_0} (1 + 8) \\ &= 0.2 \% \end{aligned}$$

$$\therefore \frac{1}{A_0} (9) = 0.2 \%$$

$$A_0 = 4500 //$$

(13)

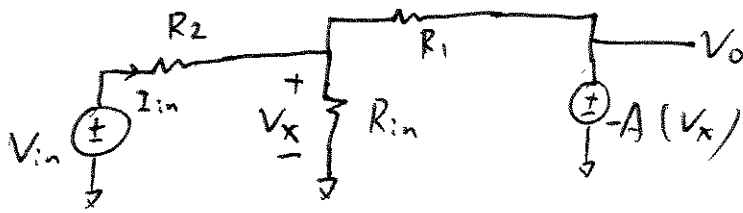

$$V_o = -A V_x \quad \text{--- (1)}$$

$$\frac{V_{in} - V_x}{R_2} + \frac{V_o - V_x}{R_1} = \frac{V_x}{R_{in}} \quad \text{--- (2)}$$

Combining (1) and (2),

$$\frac{V_{in}}{R_2} = -\frac{V_o}{R_1} + \frac{V_o}{(-A)} \left( \frac{1}{R_{in}} + \frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{V_{in}}{R_2} = V_o \left[ \frac{A R_{in} R_2 + R_1 R_2 + R_{in} R_2 + R_{in} R_1}{(-A) R_{in} R_1 R_2} \right]$$

$$\frac{V_o}{V_{in}} = - \frac{A R_{in} R_1}{R_1 R_2 + R_{in} R_2 + R_{in} R_1 + A R_{in} R_2}$$

$$\text{Input impedance } (Z_{in}) = \frac{V_{in}}{I_{in}}$$

$$I_{in} - \frac{V_x}{R_{in}} + \frac{(-A)V_x - V_x}{R_1} = 0$$

$$I_{in} = V_x \left[ \frac{1}{R_{in}} + \frac{A+1}{R_1} \right]$$


$$\therefore V_x = V_{in} - I_{in} R_2$$

$$I_{in} = [V_{in} - I_{in} R_2] \left[ \frac{1}{R_{in}} + \frac{A+1}{R_1} \right]$$

$$I_{in} \left[ 1 + \frac{R_2}{R_{in}} + \frac{R_2}{R_1} (A+1) \right] = V_{in} \left( \frac{1}{R_{in}} + \frac{A+1}{R_1} \right)$$

$$I_{in} = \frac{V_{in}}{I_{in}} = \frac{1 + \frac{R_2}{R_{in}} + \frac{R_2}{R_1} (A+1)}{\frac{1}{R_{in}} + \frac{A+1}{R_1}} //$$

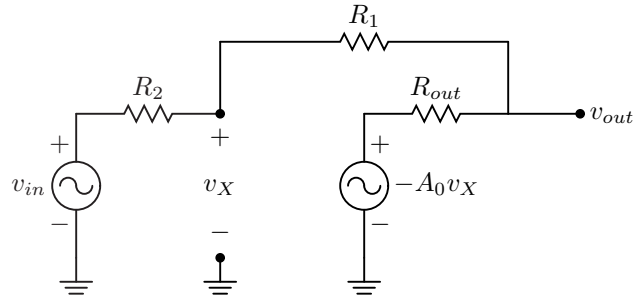8.14 We need to derive the closed-loop gain of the following circuit:



$$v_X = (v_{out} - v_{in}) \frac{R_2}{R_1 + R_2} + v_{in}$$

$$v_{out} = (-A_0 v_X - v_{in}) \frac{R_1 + R_2}{R_{out} + R_1 + R_2} + v_{in}$$

$$= \left\{ -A_0 \left[ (v_{out} - v_{in}) \frac{R_2}{R_1 + R_2} + v_{in} \right] - v_{in} \right\} \frac{R_1 + R_2}{R_{out} + R_1 + R_2} + v_{in}$$

Grouping terms, we have:

$$v_{out} \left[ 1 + A_0 \frac{R_2}{R_1 + R_2} \frac{R_1 + R_2}{R_{out} + R_1 + R_2} \right] = v_{in} \left( \frac{R_1 + R_2}{R_{out} + R_1 + R_2} \right) \left[ A_0 \frac{R_2}{R_1 + R_2} - A_0 - 1 + \frac{R_{out} + R_1 + R_2}{R_1 + R_2} \right]$$

$$= v_{in} \left( \frac{R_1 + R_2}{R_{out} + R_1 + R_2} \right) \left[ \frac{R_{out} + R_1 + R_2}{R_1 + R_2} - A_0 \frac{R_1}{R_1 + R_2} - 1 \right]$$

$$= v_{in} \frac{1}{R_{out} + R_1 + R_2} [R_{out} + R_1 + R_2 - A_0 R_1 - R_1 - R_2]$$


$$= v_{in} \left[ 1 - \frac{A_0 R_1 + R_1 + R_2}{R_{out} + R_1 + R_2} \right]$$

$$\frac{v_{out}}{v_{in}} = \frac{1 - \frac{A_0 R_1 + R_1 + R_2}{R_{out} + R_1 + R_2}}{1 + \frac{A_0 R_2}{R_{out} + R_1 + R_2}}$$

$$= \frac{R_{out} + R_1 + R_2 - A_0 R_1 - R_1 - R_2}{R_{out} + R_1 + R_2 + A_0 R_2}$$

$$= \boxed{\frac{R_{out} - A_0 R_1}{R_{out} + R_1 + (1 + A_0) R_2}}$$

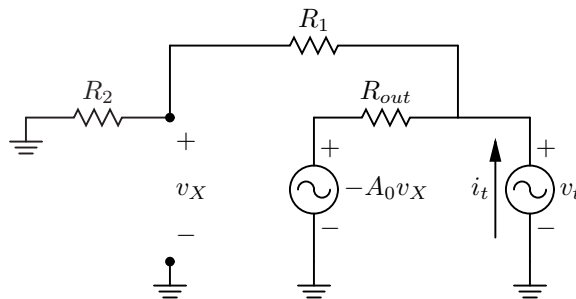To find the output impedance, we must find  $Z_{out} = \frac{v_t}{i_t}$  for the following circuit:





$$\begin{aligned}
i_t &= \frac{v_t + A_0 v_X}{R_{out}} + \frac{v_t}{R_1 + R_2} \\
v_X &= \frac{R_2}{R_1 + R_2} v_t \\
i_t &= \frac{v_t + A_0 \frac{R_2}{R_1 + R_2} v_t}{R_{out}} + \frac{v_t}{R_1 + R_2} \\
&= v_t \left( \frac{1}{R_{out}} + \frac{A_0 R_2}{R_{out} (R_1 + R_2)} + \frac{1}{R_1 + R_2} \right) \\
&= v_t \frac{R_1 + (1 + A_0) R_2 + R_{out}}{R_{out} (R_1 + R_2)} \\
Z_{out} &= \frac{v_t}{i_t} = \boxed{\frac{R_{out} (R_1 + R_2)}{R_1 + (1 + A_0) R_2 + R_{out}}}
\end{aligned}$$

8.15 Refer to the analysis for Fig. 8.42.

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{R_1}{R_2} = 4$$
$$R_{in} \approx R_2 = 10 \text{ k}\Omega$$
$$R_1 = 4R_2 = 40 \text{ k}\Omega$$

From Eq. (8.99), we have


$$\mathcal{E} = 1 - \frac{A_0 - \frac{R_{out}}{R_1}}{1 + \frac{R_{out}}{R_2} + A_0 + \frac{R_1}{R_2}}$$

$$A_0 = 1000$$

$$R_{out} = 1 \text{ k}\Omega$$

$$\mathcal{E} = \boxed{0.51 \%}$$

(16)

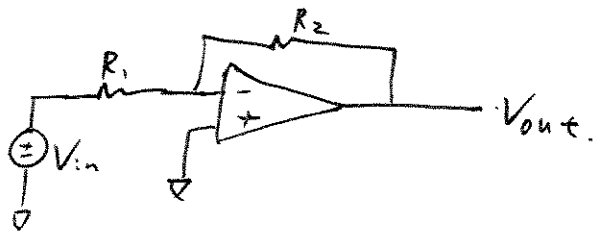

$$\text{Nominal gain} = \frac{R_2}{R_1} = 8 \quad \text{--- (1)}$$

$$R_2 = 8R_1$$

$$\text{Input impedance} \approx R_1 = 1000 \Omega \quad \text{--- (2)}$$

$$\therefore R_2 = 8000 \Omega.$$

$$\text{Gain error} = 0.1\% \quad \text{--- (3)}$$

$$\therefore \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right) = 0.1\%$$

$$\frac{1}{A_0} (9) = \frac{0.1}{100}$$

$$\therefore A_0 = 9000 //$$

8.17

$$\begin{aligned}V_+ &= V_- \text{ (since } A_0 = \infty\text{)} \\ \frac{V_{in}}{R_2} &= -\frac{V_{out}}{R_3} \frac{R_3 \parallel R_4}{R_1 + R_3 \parallel R_4} \\ \frac{V_{out}}{V_{in}} &= \boxed{-\frac{R_3}{R_2} \frac{R_1 + R_3 \parallel R_4}{R_3 \parallel R_4}}\end{aligned}$$

If  $R_1 \rightarrow 0$  or  $R_3 \rightarrow 0$ , we expect the amplifier to reduce to the standard inverting amplifier.

$$\begin{aligned}\left. \frac{V_{out}}{V_{in}} \right|_{R_1 \rightarrow 0} &= -\frac{R_3}{R_2} \\ \left. \frac{V_{out}}{V_{in}} \right|_{R_3 \rightarrow 0} &= -\frac{R_1}{R_2}\end{aligned}$$

The gain reduces to the expected expressions.

$$\begin{aligned}V_+ &= V_- \text{ (since } A_0 = \infty\text{)} \\V_X &= \frac{R_3}{R_3 + R_4} V_{out} = \frac{R_2}{R_1 + R_2} (V_{out} - V_{in}) + V_{in} \\V_{out} \left( \frac{R_3}{R_3 + R_4} - \frac{R_2}{R_1 + R_2} \right) &= V_{in} \left( 1 - \frac{R_2}{R_1 + R_2} \right) \\V_{out} \left[ \frac{R_3 (R_1 + R_2) - R_2 (R_3 + R_4)}{(R_1 + R_2) (R_3 + R_4)} \right] &= V_{in} \left( \frac{R_1}{R_1 + R_2} \right) \\ \frac{V_{out}}{V_{in}} &= \boxed{\frac{R_1 (R_3 + R_4)}{R_3 (R_1 + R_2) - R_2 (R_3 + R_4)}}\end{aligned}$$

(19)

From eq (8.31),

$$\begin{aligned}V_{out} &= -\frac{1}{R_1 C_1} \int V_{in} dt \\&= -\frac{1}{R_1 C_1} \int V_0 \sin \omega t dt \\&= \frac{V_0}{R_1 C_1 \omega} \cos \omega t\end{aligned}$$

$$\therefore \text{Amplitude of output} = \frac{V_0}{R_1 C_1 \omega} //$$

(20) From prob. (19)

Amplification of the integrator =  $\frac{1}{R_1 C_1 \omega}$

$$\therefore \frac{1}{R_1 C_1 \omega} = 10$$

$$\frac{1}{\omega} = 10 \times 10^{-6} \text{ s}$$

$$\therefore \omega = 10 \text{ MHz}$$

$\therefore$  The frequency of the sinusoid is 10 MHz.

(21)

From Eq. (8.37)


$$S_p = \frac{-1}{2\pi (A_0 + 1) R. C.} \quad \leq -1 \text{ Hz.}$$

$$\therefore 2\pi (A_0 + 1) / (10 \text{ k}\Omega) / (1 \text{ nF}) \geq 1$$

$$A_0 \geq \underline{\underline{15915}}$$



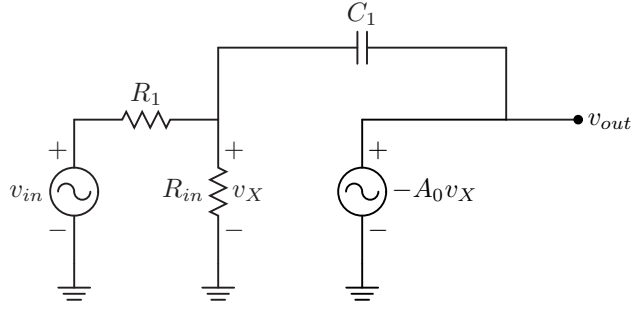8.22 We must find the transfer function of the following circuit:



$$\begin{aligned}
 v_{out} &= -A_0 v_X \\
 v_X &= v_{out} - \frac{1}{sC_1} \left( \frac{v_X}{R_{in}} + \frac{v_X - v_{in}}{R_1} \right) \\
 v_X \left( 1 + \frac{1}{sR_{in}C_1} + \frac{1}{sR_1C_1} \right) &= v_{out} + \frac{v_{in}}{sR_1C_1} \\
 v_X &= \frac{sR_1R_{in}C_1 v_{out} + R_{in}v_{in}}{sR_1R_{in}C_1 + R_1 + R_{in}} \\
 v_{out} &= -A_0 \frac{sR_1R_{in}C_1 v_{out} + R_{in}v_{in}}{sR_1R_{in}C_1 + R_1 + R_{in}} \\
 v_{out} \left( 1 + A_0 \frac{sR_1R_{in}C_1}{sR_1R_{in}C_1 + R_1 + R_{in}} \right) &= -A_0 v_{in} \frac{R_{in}}{sR_1R_{in}C_1 + R_1 + R_{in}} \\
 \frac{v_{out}}{v_{in}} &= \frac{-A_0 R_{in}}{sR_1R_{in}C_1 + R_1 + R_{in}} \cdot \frac{sR_1R_{in}C_1 + R_1 + R_{in}}{sR_1R_{in}C_1 + R_1 + R_{in} + sR_1R_{in}C_1 A_0} \\
 &= \frac{-A_0 R_{in}}{sR_1R_{in}C_1 + R_1 + R_{in} + sR_1R_{in}C_1 A_0} \\
 &= \frac{-A_0 R_{in}}{sR_1R_{in}C_1 (1 + A_0) + R_1 + R_{in}} \\
 &= \frac{-A_0 R_{in}}{1 + s \frac{R_1 R_{in} C_1 (1 + A_0)}{R_1 + R_{in}}} \\
 &= \frac{-A_0 R_{in} / (R_1 + R_{in})}{1 + s (R_1 \parallel R_{in}) C_1 (1 + A_0)} \\
 s_p &= -\frac{1}{(R_1 \parallel R_{in}) C_1 (1 + A_0)}
 \end{aligned}$$


Comparing this to the result in Eq. (8.37), we can see that we can simply replace  $R_1$  with  $R_1 \parallel R_{in}$ , effectively increasing the pole frequency (since  $R_1 \parallel R_{in} < R_1$  for finite  $R_{in}$ ).

We can also write the result as

$$s_p = -\frac{1}{R_1 C_1 (1 + A_0)} \left( 1 + \frac{R_1}{R_{in}} \right)$$

In this form, it's clear that the pole frequency increases by  $1 + R_1/R_{in}$ .

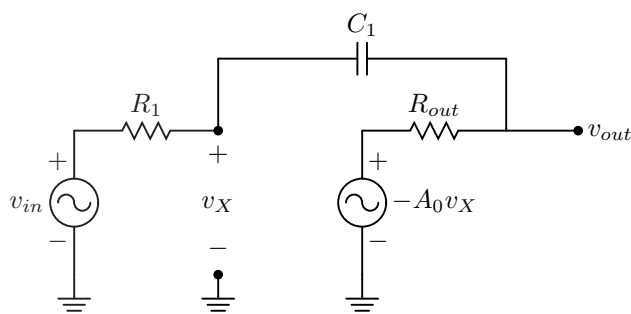8.23 We must find the transfer function of the following circuit:



$$v_{out} = -A_0 v_X + \frac{v_{in} - v_{out}}{R_1 + \frac{1}{sC_1}} R_{out}$$

$$v_X = v_{in} + \frac{R_1}{R_1 + \frac{1}{sC_1}} (v_{out} - v_{in})$$

$$v_{out} = -A_0 \left[ v_{in} + \frac{R_1}{R_1 + \frac{1}{sC_1}} (v_{out} - v_{in}) \right] + \frac{v_{in} - v_{out}}{R_1 + \frac{1}{sC_1}} R_{out}$$

$$v_{out} \left[ 1 + \frac{A_0 R_1 + R_{out}}{R_1 + \frac{1}{sC_1}} \right] = v_{in} \left[ -A_0 + \frac{A_0 R_1 + R_{out}}{R_1 + \frac{1}{sC_1}} \right]$$

$$v_{out} \frac{R_1 + \frac{1}{sC_1} + A_0 R_1 + R_{out}}{R_1 + \frac{1}{sC_1}} = v_{in} \frac{-A_0 R_1 - A_0 \frac{1}{sC_1} + A_0 R_1 + R_{out}}{R_1 + \frac{1}{sC_1}}$$

$$v_{out} \{1 + sC_1 [(1 + A_0) R_1 + R_{out}]\} = -v_{in} \{A_0 - sC_1 R_{out}\}$$

$$\frac{v_{out}}{v_{in}} = \frac{A_0 - sC_1 R_{out}}{1 + sC_1 [(1 + A_0) R_1 + R_{out}]}$$

$$s_p = \frac{1}{C_1 [(1 + A_0) R_1 + R_{out}]}$$

Comparing this to the result in Eq. (8.37), we can see that the pole gets reduced in magnitude due to  $R_{out}$ .

$$\textcircled{24} \quad \therefore A_o = \infty$$

$$|A_v| = \frac{R_i}{\frac{1}{\omega C_i}}$$

$$= \omega R_i C_i$$

$$= 5$$

$$\therefore R_i C_i = \frac{5}{\omega}$$

$$= \frac{5}{2\pi \times 10^6}$$

$$= 7.958 \times 10^{-7}$$

(25)

From eq: (8.55)


$$S_p = - \frac{A_0 + 1}{R_1 C_1}$$

$$2\pi \times 100 \times 10^6 = \frac{A_0 + 1}{1000 \times 10^{-9}}$$

(ie.  $R_1$  and  $C_1$  are chosen at minimum)

$$A_0 \approx 627$$

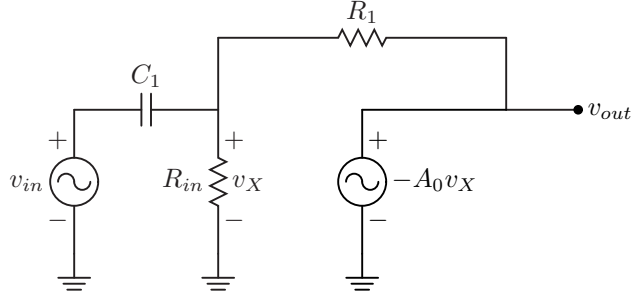
8.26 We must find the transfer function of the following circuit:



$$\begin{aligned}
 v_{out} &= -A_0 v_X \\
 v_X &= \left[ (v_{in} - v_X) sC_1 - \frac{v_X - v_{out}}{R_1} \right] R_{in} \\
 v_X \left[ 1 + sR_{in}C_1 + \frac{R_{in}}{R_1} \right] &= v_{in}sR_{in}C_1 + v_{out} \frac{R_{in}}{R_1} \\
 v_X &= \frac{v_{in}sR_{in}C_1 + v_{out} \frac{R_{in}}{R_1}}{1 + sR_{in}C_1 + \frac{R_{in}}{R_1}} \\
 v_{out} &= -A_0 \frac{v_{in}sR_{in}C_1 + v_{out} \frac{R_{in}}{R_1}}{1 + sR_{in}C_1 + \frac{R_{in}}{R_1}} \\
 v_{out} \left[ 1 + \frac{A_0 \frac{R_{in}}{R_1}}{1 + sR_{in}C_1 + \frac{R_{in}}{R_1}} \right] &= -v_{in} \frac{sR_{in}C_1 A_0}{1 + sR_{in}C_1 + \frac{R_{in}}{R_1}} \\
 v_{out} \left[ \frac{1 + sR_{in}C_1 + (1 + A_0) \frac{R_{in}}{R_1}}{1 + sR_{in}C_1 + \frac{R_{in}}{R_1}} \right] &= -v_{in} \frac{sR_{in}C_1 A_0}{1 + sR_{in}C_1 + \frac{R_{in}}{R_1}} \\
 v_{out} \left[ 1 + sR_{in}C_1 + (1 + A_0) \frac{R_{in}}{R_1} \right] &= -v_{in} sR_{in}C_1 A_0 \\
 \frac{v_{out}}{v_{in}} &= \boxed{-\frac{sR_1 R_{in} C_1 A_0}{R_1 + sR_1 R_{in} C_1 + (1 + A_0) R_{in}}} \\
 \lim_{A_0 \rightarrow \infty} \frac{v_{out}}{v_{in}} &= -sR_1 C_1
 \end{aligned}$$

Comparing this to Eq. (8.42), we can see that if we let  $A_0 \rightarrow \infty$ , the result actually reduces to Eq. (8.42).

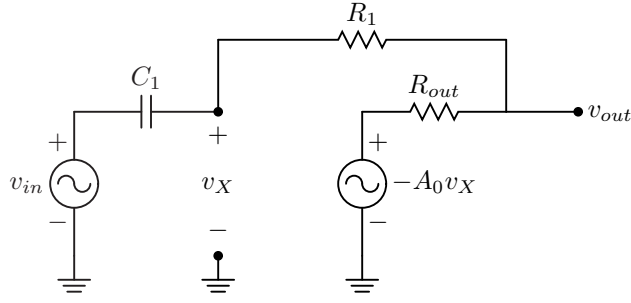8.27 We must find the transfer function of the following circuit:



$$\begin{aligned}
 v_{out} &= -A_0 v_X + \frac{v_{in} - v_{out}}{R_1 + \frac{1}{sC_1}} R_{out} \\
 v_X &= v_{in} + \frac{\frac{1}{sC_1}}{R_1 + \frac{1}{sC_1}} (v_{out} - v_{in}) \\
 v_{out} &= -A_0 \left[ v_{in} + \frac{\frac{1}{sC_1}}{R_1 + \frac{1}{sC_1}} (v_{out} - v_{in}) \right] + \frac{v_{in} - v_{out}}{R_1 + \frac{1}{sC_1}} R_{out} \\
 v_{out} \left[ 1 + \frac{A_0 \frac{1}{sC_1} + R_{out}}{R_1 + \frac{1}{sC_1}} \right] &= v_{in} \left[ -A_0 + \frac{A_0 \frac{1}{sC_1} + R_{out}}{R_1 + \frac{1}{sC_1}} \right] \\
 v_{out} \frac{R_1 + \frac{1}{sC_1} + A_0 \frac{1}{sC_1} + R_{out}}{R_1 + \frac{1}{sC_1}} &= v_{in} \frac{-A_0 R_1 - A_0 \frac{1}{sC_1} + A_0 \frac{1}{sC_1} + R_{out}}{R_1 + \frac{1}{sC_1}} \\
 v_{out} \{1 + A_0 + sC_1 (R_1 + R_{out})\} &= -v_{in} \{sC_1 (A_0 R_1 - R_{out})\} \\
 \frac{v_{out}}{v_{in}} &= \boxed{-\frac{sC_1 (A_0 R_1 - R_{out})}{1 + A_0 + sC_1 (R_1 + R_{out})}} \\
 \lim_{A_0 \rightarrow \infty} \frac{v_{out}}{v_{in}} &= -sR_1 C_1
 \end{aligned}$$

Comparing this to Eq. (8.42), we can see that if we let  $A_0 \rightarrow \infty$ , the result actually reduces to Eq. (8.42).

$$\begin{aligned}
v_{out} &= -A_0 v_- \\
v_- &= v_{in} + (v_{out} - v_{in}) \frac{\frac{1}{sC_1} \parallel R_1}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \\
v_{out} &= -A_0 \left[ v_{in} + (v_{out} - v_{in}) \frac{\frac{1}{sC_1} \parallel R_1}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \right] \\
v_{out} \left[ 1 + A_0 \frac{\frac{1}{sC_1} \parallel R_1}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \right] &= -v_{in} A_0 \left[ 1 - \frac{\frac{1}{sC_1} \parallel R_1}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \right] \\
v_{out} \frac{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right) + A_0 \left(\frac{1}{sC_1} \parallel R_1\right)}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} &= -v_{in} A_0 \frac{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right) - \left(\frac{1}{sC_1} \parallel R_1\right)}{\left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)} \\
v_{out} \left\{ (1 + A_0) \left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right) \right\} &= -v_{in} A_0 \left(\frac{1}{sC_2} \parallel R_2\right) \\
\frac{v_{out}}{v_{in}} &= \boxed{-A_0 \frac{\frac{1}{sC_2} \parallel R_2}{(1 + A_0) \left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right)}}
\end{aligned}$$

Unity gain occurs when the numerator and denominator are the same (note that we can drop the negative sign since we only care about the magnitude of the gain):

$$\begin{aligned}
A_0 \left(\frac{1}{sC_2} \parallel R_2\right) &= (1 + A_0) \left(\frac{1}{sC_1} \parallel R_1\right) + \left(\frac{1}{sC_2} \parallel R_2\right) \\
(A_0 - 1) \left(\frac{1}{sC_2} \parallel R_2\right) &= (1 + A_0) \left(\frac{1}{sC_1} \parallel R_1\right) \\
\frac{\left(\frac{1}{sC_2} \parallel R_2\right)}{\left(\frac{1}{sC_1} \parallel R_1\right)} &= \frac{A_0 + 1}{A_0 - 1}
\end{aligned}$$

It is possible to obtain unity gain by choosing the resistors and capacitors according to the above formula.

(29)

if  $A_0 < \infty$ ,

Let  $V_-$  be the voltage at the negative input terminal of the opamp.

By KCL,

$$\frac{V_{in} - V_-}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out} - V_-}{R_2 \parallel \frac{1}{sC_2}}$$

$$V_{out} = -A_0 V_-$$

$$\frac{V_{in} + \frac{V_{out}}{A_0}}{R_1 \parallel \frac{1}{sC_1}} = - \frac{V_{out} + \frac{V_{out}}{A_0}}{R_2 \parallel \frac{1}{sC_2}}$$

$$V_{in} = - \left[ R_1 \parallel \frac{1}{sC_1} \right] \left[ \frac{\left( R_2 \parallel \frac{1}{sC_2} \right) \frac{V_{out}}{A_0} + V_{out} + \frac{V_{out}}{A_0}}{R_2 \parallel \frac{1}{sC_2}} \right]$$

$$\therefore \frac{V_{out}}{V_{in}} = - \frac{R_2 \parallel \frac{1}{sC_2}}{R_1 \parallel \frac{1}{sC_1}} \left[ \frac{A_0}{(A_0 + 1) + \left( R_2 \parallel \frac{1}{sC_2} \right)} \right]$$

To see  $\left| \frac{V_{out}}{V_{in}} \right| = 1$ ,

Let  $x = R_1 \parallel \frac{1}{sC_1}$  and  $y = R_2 \parallel \frac{1}{sC_2}$ .

$$\therefore \text{For } \left| \frac{V_{out}}{V_{in}} \right| = 1, \quad y A_0 = x \left[ (A_0 + 1) + y \right]$$

$$y (A_0 - 1) = x (A_0 + 1)$$



(29) Cont'd

$$\therefore \frac{x}{y} = \frac{A_0 + 1}{A_0 - 1},$$

ie. we need to set  $\frac{R_1 // \frac{1}{sC_1}}{R_2 // \frac{1}{sC_2}} = \frac{A_0 + 1}{A_0 - 1}$ .

Since  $A_0$  is generally rather large,

$\frac{A_0 + 1}{A_0 - 1}$  is a rational fraction,  
in which the numerator and the  
denominator are large, and differ  
by a small amount.

(e.g. if  $A_0 = 1000$ ,  $\frac{A_0 + 1}{A_0 - 1} = \frac{1001}{999}$ )

Hence, setting  $\left| \frac{V_{out}}{V_{in}} \right|$  to unity is possible  
in principle, although it would be rather  
difficult to precisely control  $A_0$ .


30

From eq = (8.63),

$$V_{out} = -R_F \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right)$$

$$\therefore R_1 = R_2,$$
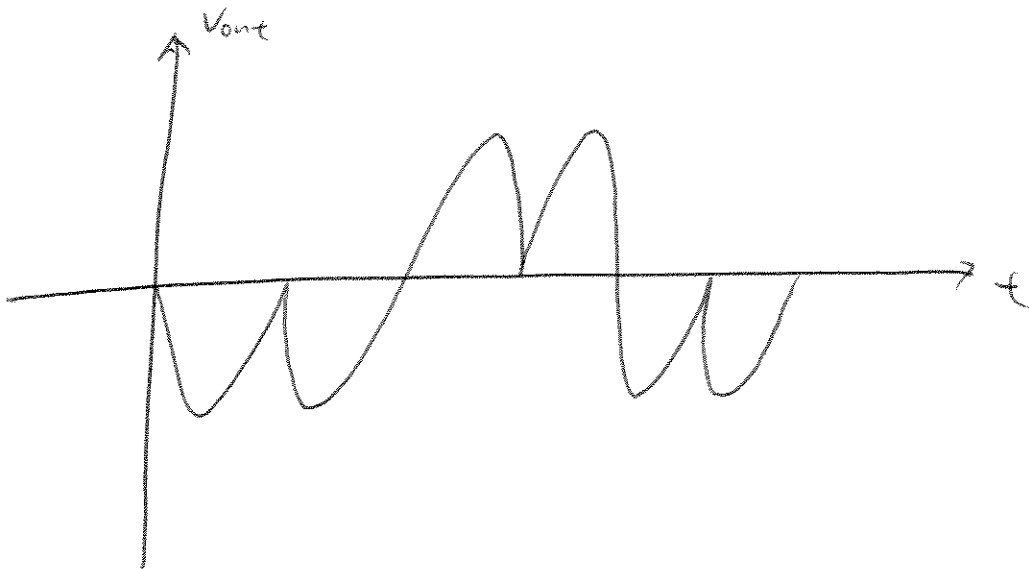
$$V_{out} = -\frac{R_F}{R_1} (V_1 + V_2)$$



$$\begin{aligned}
v_{out} &= -A_0 v_X \\
\frac{v_1 - v_X}{R_2} + \frac{v_2 - v_X}{R_1} &= \frac{v_X - v_{out}}{R_F} \\
\frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} &= \frac{v_X}{R_1 \parallel R_2 \parallel R_F} \\
v_{out} &= -A_0 (R_1 \parallel R_2 \parallel R_F) \left( \frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \\
v_{out} \left[ 1 + A_0 \frac{(R_1 \parallel R_2 \parallel R_F)}{R_F} \right] &= -A_0 (R_1 \parallel R_2 \parallel R_F) \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \\
v_{out} &= -A_0 (R_1 \parallel R_2 \parallel R_F) \frac{\frac{v_1}{R_2} + \frac{v_2}{R_1}}{1 + A_0 \frac{(R_1 \parallel R_2 \parallel R_F)}{R_F}} \\
&= -A_0 R_F (R_1 \parallel R_2 \parallel R_F) \frac{\frac{v_1}{R_2} + \frac{v_2}{R_1}}{R_F + A_0 (R_1 \parallel R_2 \parallel R_F)} \\
&= \boxed{- \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) [R_F \parallel A_0 (R_1 \parallel R_2 \parallel R_F)]}
\end{aligned}$$


8.32 For  $A_0 = \infty$ , we know that  $v_+ = v_-$ , meaning that no current flows through  $R_P$ . Thus,  $R_P$  will have no effect on  $v_{out}$ .

$$v_{out} = \boxed{-R_F \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right), A_0 = \infty}$$

For  $A_0 < \infty$ , we have to include the effects of  $R_P$ .

$$\begin{aligned}
v_{out} &= -A_0 v_X \\
v_X &= \left( \frac{v_1 - v_X}{R_2} + \frac{v_2 - v_X}{R_1} + \frac{v_{out} - v_X}{R_F} \right) R_P \\
v_X \left( \frac{1}{R_P} + \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_F} \right) &= \frac{v_1}{R_2} + \frac{v_2}{R_1} + \frac{v_{out}}{R_F} \\
v_X &= \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} + \frac{v_{out}}{R_F} \right) (R_1 \parallel R_2 \parallel R_F \parallel R_P) \\
v_{out} &= -A_0 \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} + \frac{v_{out}}{R_F} \right) (R_1 \parallel R_2 \parallel R_F \parallel R_P) \\
v_{out} \left[ 1 + \frac{A_0}{R_F} (R_1 \parallel R_2 \parallel R_F \parallel R_P) \right] &= -A_0 \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) (R_1 \parallel R_2 \parallel R_F \parallel R_P) \\
v_{out} &= -A_0 \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \frac{(R_1 \parallel R_2 \parallel R_F \parallel R_P)}{1 + \frac{A_0}{R_F} (R_1 \parallel R_2 \parallel R_F \parallel R_P)} \\
&= - \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \frac{R_F A_0 (R_1 \parallel R_2 \parallel R_F \parallel R_P)}{R_F + A_0 (R_1 \parallel R_2 \parallel R_F \parallel R_P)} \\
&= \boxed{- \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) [R_F \parallel A_0 (R_1 \parallel R_2 \parallel R_F \parallel R_P)], A_0 < \infty}
\end{aligned}$$

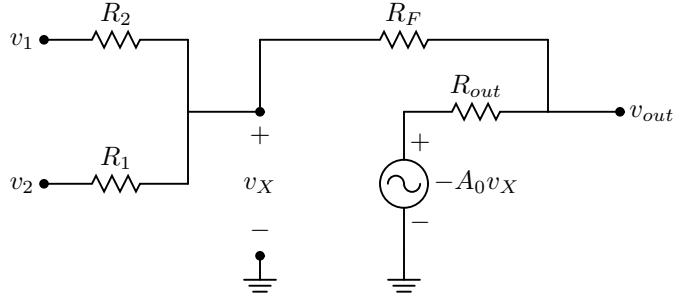8.33 We must find  $v_{out}$  for the following circuit:




$$\begin{aligned}
 v_{out} &= -A_0 v_X + \left( \frac{v_1 - v_X}{R_2} + \frac{v_2 - v_X}{R_1} \right) R_{out} \\
 &= -v_X \left( A_0 + \frac{R_{out}}{R_1} + \frac{R_{out}}{R_2} \right) + R_{out} \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \\
 v_X &= v_{out} + \left( \frac{v_1 - v_X}{R_2} + \frac{v_2 - v_X}{R_1} \right) R_F \\
 v_X \left( \frac{1}{R_F} + \frac{1}{R_1} + \frac{1}{R_2} \right) &= \frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} \\
 v_X &= \left( \frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) (R_1 \parallel R_2 \parallel R_F) \\
 v_{out} &= - \left( \frac{v_{out}}{R_F} + \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) (R_1 \parallel R_2 \parallel R_F) \left( A_0 + \frac{R_{out}}{R_1} + \frac{R_{out}}{R_2} \right) + R_{out} \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right)
 \end{aligned}$$

Grouping terms, we have:

$$\begin{aligned}
 v_{out} \left[ 1 + \frac{(R_1 \parallel R_2 \parallel R_F) \left( A_0 + \frac{R_{out}}{R_1 \parallel R_2} \right)}{R_F} \right] &= - \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) (R_1 \parallel R_2 \parallel R_F) \left( A_0 + \frac{R_{out}}{R_1 \parallel R_2} \right) + R_{out} \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \\
 &= - \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \left[ (R_1 \parallel R_2 \parallel R_F) \left( A_0 + \frac{R_{out}}{R_1 \parallel R_2} \right) + R_{out} \right] \\
 v_{out} &= \boxed{ -R_F \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \frac{R_{out} + (R_1 \parallel R_2 \parallel R_F) \left( A_0 + \frac{R_{out}}{R_1 \parallel R_2} \right)}{R_F + (R_1 \parallel R_2 \parallel R_F) \left( A_0 + \frac{R_{out}}{R_1 \parallel R_2} \right)} }
 \end{aligned}$$

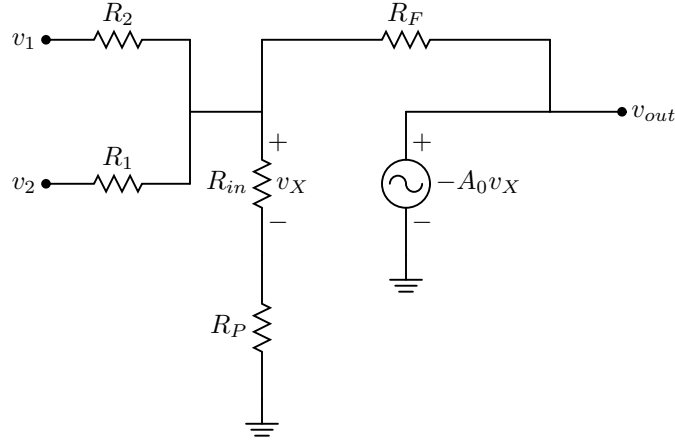8.34 We must find  $v_{out}$  for the following circuit:



$$v_{out} = -A_0 v_X$$

$$v_X = \left[ \frac{v_1 - v_X \left(1 + \frac{R_P}{R_{in}}\right)}{R_1} + \frac{v_2 - v_X \left(1 + \frac{R_P}{R_{in}}\right)}{R_2} + \frac{v_{out} - v_X \left(1 + \frac{R_P}{R_{in}}\right)}{R_F} \right] R_{in}$$

Grouping terms, we have:

$$v_X \left[ \frac{1}{R_{in}} + \left(1 + \frac{R_P}{R_{in}}\right) \frac{1}{R_1 \parallel R_2 \parallel R_F} \right] = \frac{v_1}{R_2} + \frac{v_2}{R_1} + \frac{v_{out}}{R_F}$$

$$v_X \left[ \frac{(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}}{R_{in} (R_1 \parallel R_2 \parallel R_F)} \right] = \frac{v_1}{R_2} + \frac{v_2}{R_1} + \frac{v_{out}}{R_F}$$

$$v_X = \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} + \frac{v_{out}}{R_F} \right) \frac{R_{in} (R_1 \parallel R_2 \parallel R_F)}{(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}}$$

$$v_{out} = -A_0 \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} + \frac{v_{out}}{R_F} \right) \frac{R_{in} (R_1 \parallel R_2 \parallel R_F)}{(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}}$$

Grouping terms, we have:

$$v_{out} \left[ 1 + \frac{A_0}{R_F} \frac{R_{in} (R_1 \parallel R_2 \parallel R_F)}{(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}} \right] = - \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \frac{A_0 R_{in} (R_1 \parallel R_2 \parallel R_F)}{(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}}$$


$$v_{out} \left[ \frac{R_F [(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}] + A_0 R_{in} (R_1 \parallel R_2 \parallel R_F)}{R_F [(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}]} \right] = - \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \frac{A_0 R_{in} (R_1 \parallel R_2 \parallel R_F)}{(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}}$$

Simplifying, we have:

$$v_{out} = - \left( \frac{v_1}{R_2} + \frac{v_2}{R_1} \right) \frac{A_0 R_F R_{in} (R_1 \parallel R_2 \parallel R_F)}{R_F [(R_1 \parallel R_2 \parallel R_F) + R_P + R_{in}] + A_0 R_{in} (R_1 \parallel R_2 \parallel R_F)}$$


$$I_{D1} = \begin{cases} \frac{V_{in}}{R_1} & V_{in} > 0 \\ 0 & V_{in} < 0 \end{cases}$$

Plotting  $I_{D1}(t)$ , we have

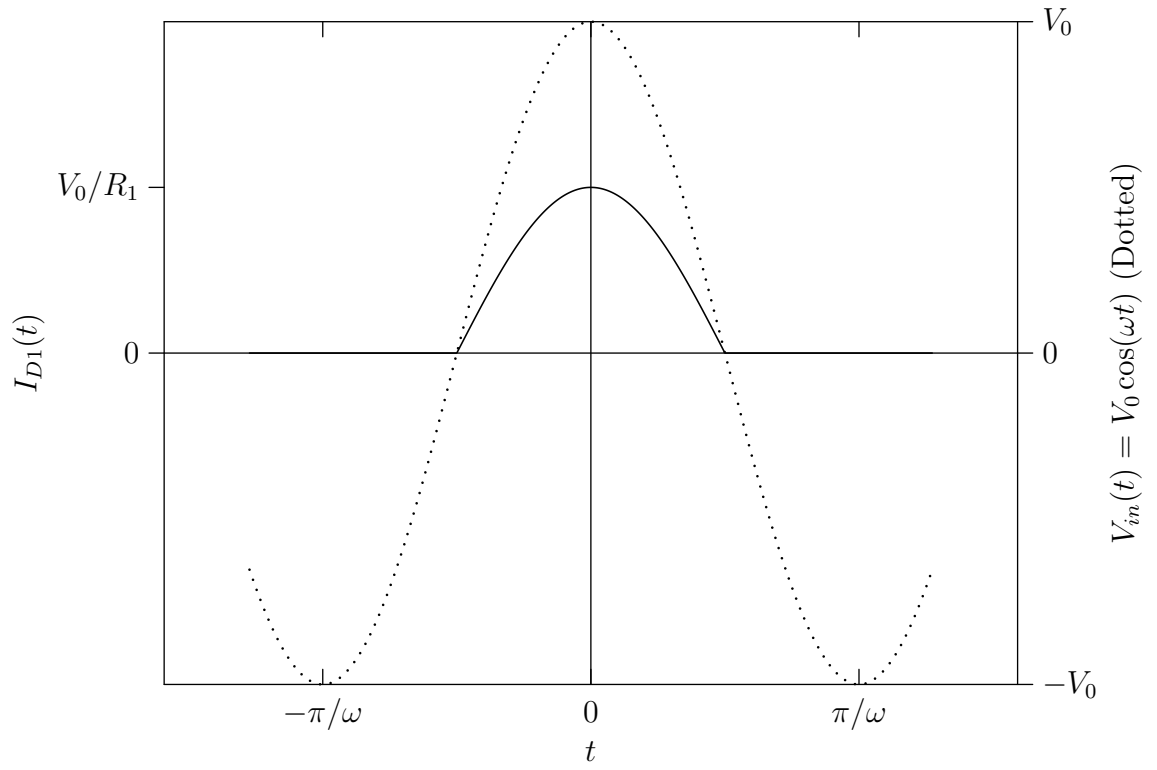

$$I_{D1} = \begin{cases} \frac{V_{in}}{R_1} & V_{in} > 0 \\ 0 & V_{in} < 0 \end{cases}$$

Plotting  $I_{D1}(t)$ , we have

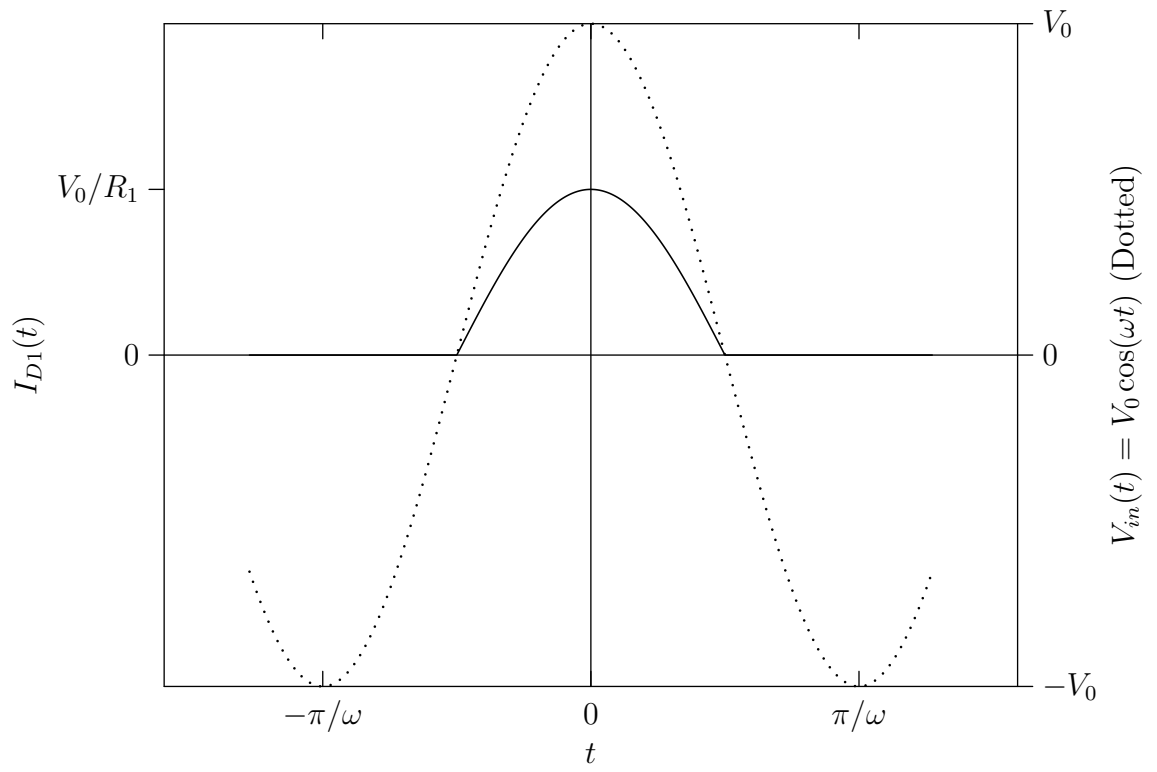




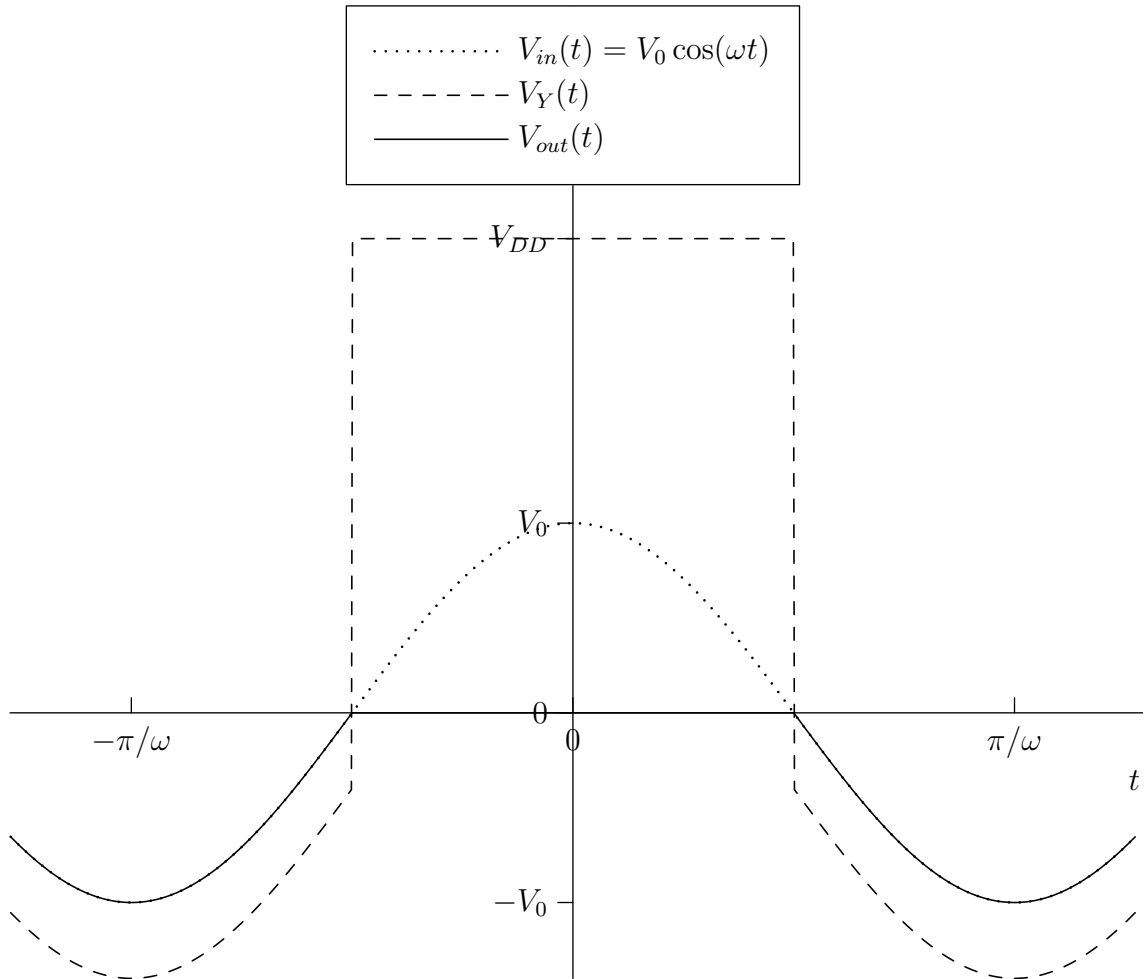
8.37

$$V_Y = \begin{cases} V_{in} - V_{D,on} & V_{in} < 0 \\ V_{DD} & V_{in} > 0 \end{cases} V_{out} = \begin{cases} V_{in} & V_{in} < 0 \\ 0 & V_{in} > 0 \end{cases} I_{D1} = \begin{cases} \frac{V_{in}}{R_1} & V_{in} < 0 \\ 0 & V_{in} > 0 \end{cases}$$

Plotting  $V_Y(t)$  and  $V_{out}(t)$ , we have



Plotting  $I_{D1}(t)$ , we have:

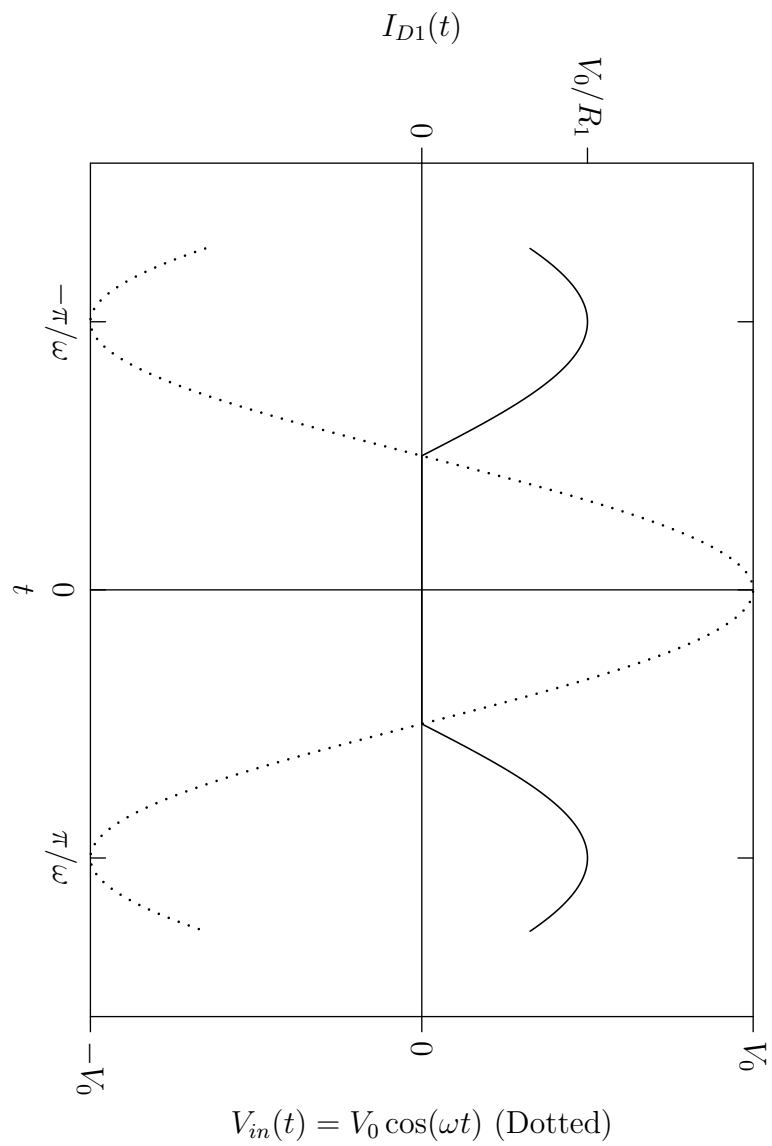

8.38 Since the negative feedback loop is never broken (even when the diode is off,  $R_P$  provides negative feedback),  $V_+ = V_-$  will always hold, meaning  $V_X = V_{in}$ .

We must determine when  $D_1$  turns on/off to determine  $V_Y$ . We know that for  $V_{in} < 0$ , the diode will be off, and  $V_X$  will follow  $V_{in}$ . As  $V_{in}$  begins to go positive, the diode will remain off until


$$V_{in} \frac{R_P}{R_1} > V_{D,on}$$

Once the diode turns on,  $V_Y$  will be fixed at  $V_{in} + V_{D,on}$ . Thus, we can write:

$$V_X = V_{in}$$


$$V_Y = \begin{cases} V_{in} \left(1 + \frac{R_P}{R_1}\right) & V_{in} < V_{D,on} \frac{R_1}{R_P} \\ V_{in} + V_{D,on} & V_{in} > V_{D,on} \frac{R_1}{R_P} \end{cases}$$

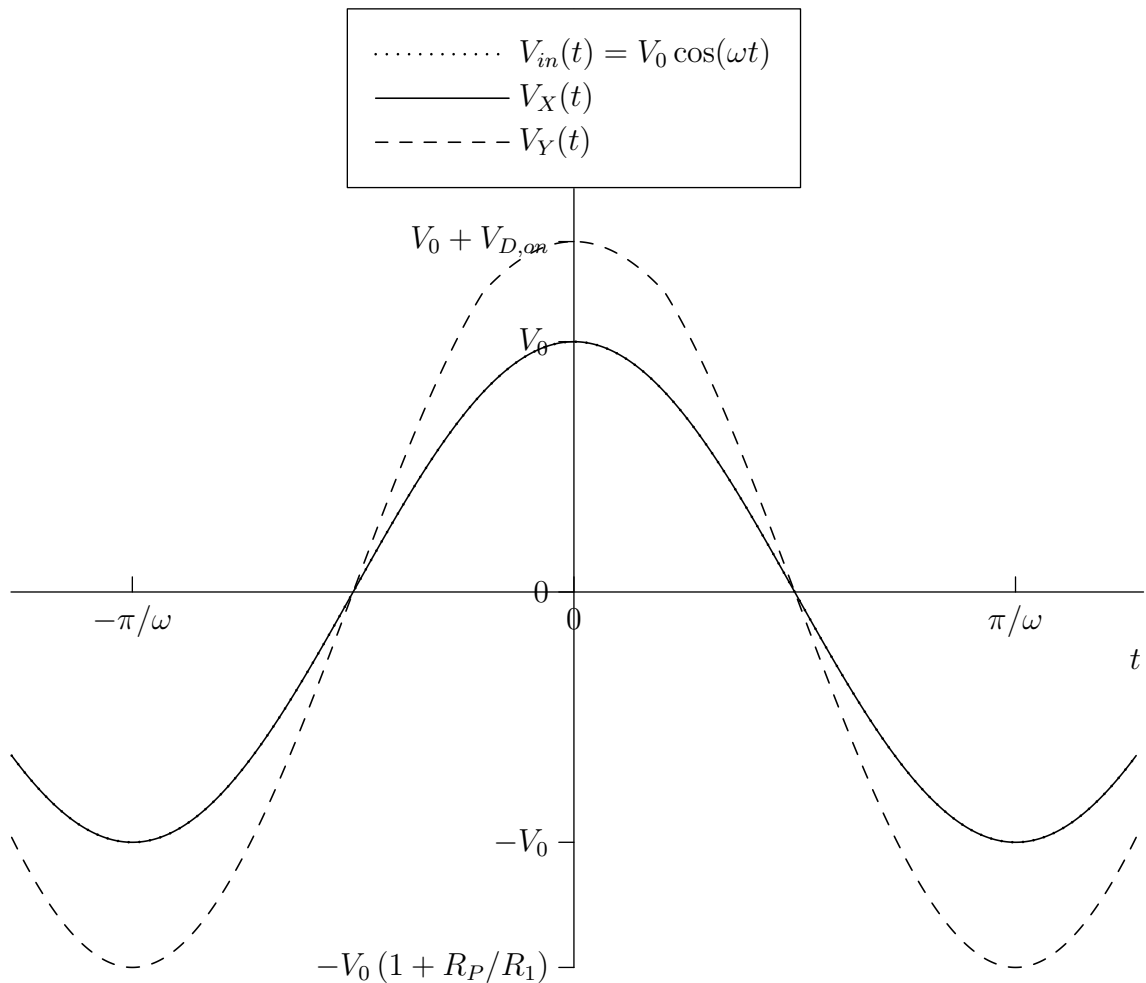Plotting  $V_Y(t)$  and  $V_{out}(t)$ , we have




39

Connecting a diode as below:

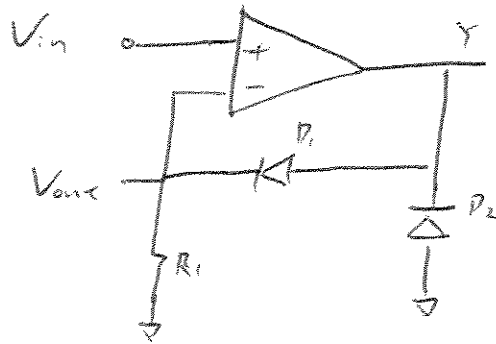


$D_2$  allows the parasitic capacitance to charge up faster, right before  $D_1$  conducts.

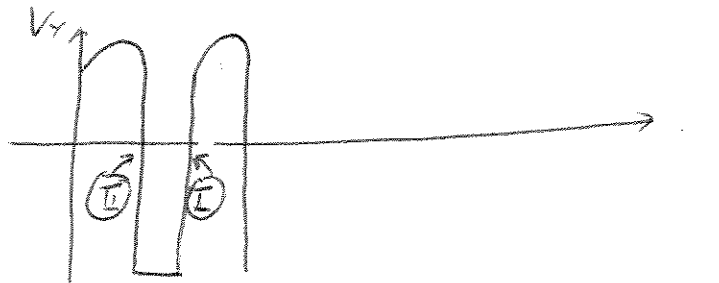This corresponds to sharpening the transition (I) of  $V_Y$ , as shown below



But it will not speed up transition (II).  
(which is not critical)

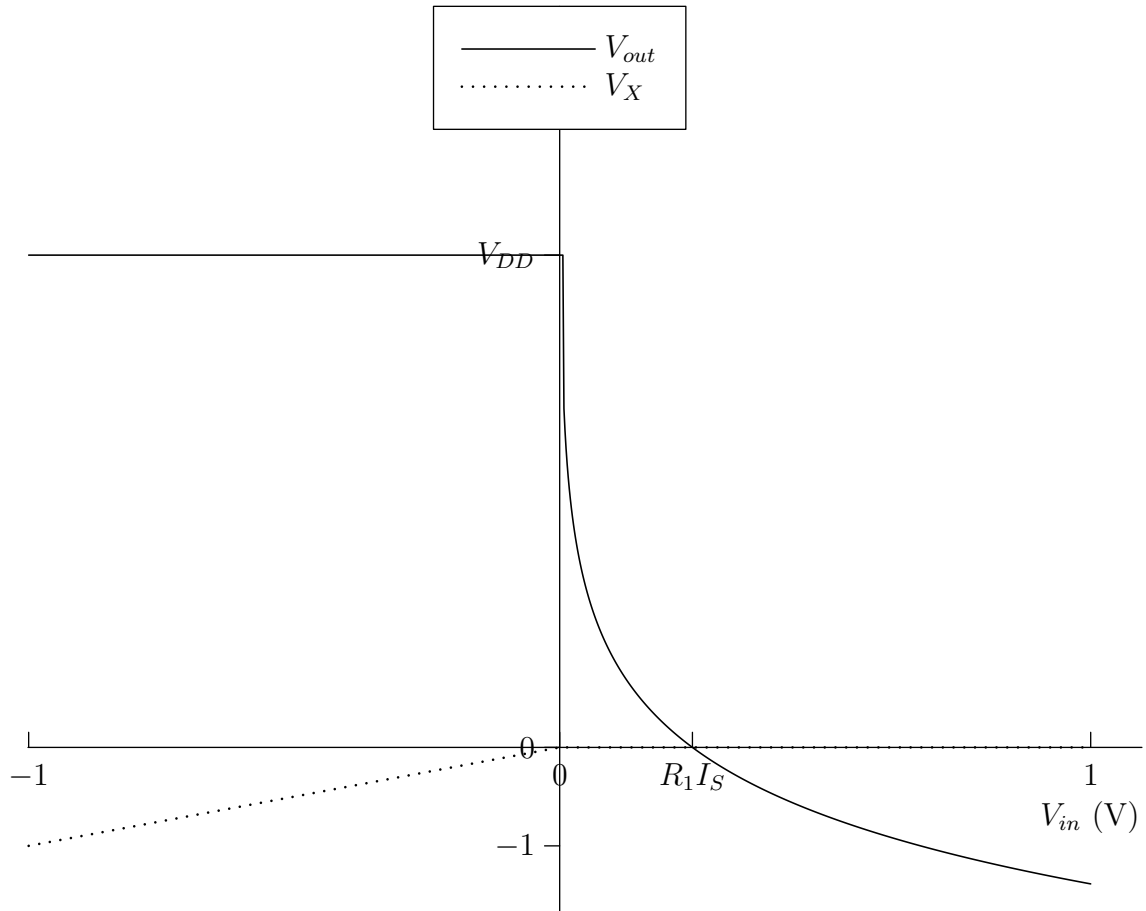8.40 Note that although in theory the output is unbounded (i.e., by Eq. (8.66), we can take the logarithm of an arbitrarily small positive number), in reality the output will be limited by the positive supply rail, as shown in the following plot.



④ By KCL,

$$\frac{V_{in} - V_x}{R_1} = I_{R_1}$$

$$\therefore V_{BE} = V_T \ln \frac{V_{in} - V_x}{R_1 I_s}$$

$$= -V_{out}$$

$$\therefore -A_o V_x = V_{out}$$

$$V_x = -\frac{V_{out}}{A_o}$$

$$\therefore V_{out} = -V_T \ln \frac{V_{in} + \frac{V_{out}}{A_o}}{R_1 I_s}$$




8.42 When  $V_{in} > 0$ , the feedback loop will be broken, and the output will go to the positive rail.

When  $V_{in} < 0$ , we have:

$$I_C = -\frac{V_{in}}{R_1} = I_S e^{V_{BE}/V_T} = I_S e^{-V_{out}/V_T}$$

$$V_{out} = \boxed{-V_T \ln\left(-\frac{V_{in}}{R_1 I_S}\right)}$$

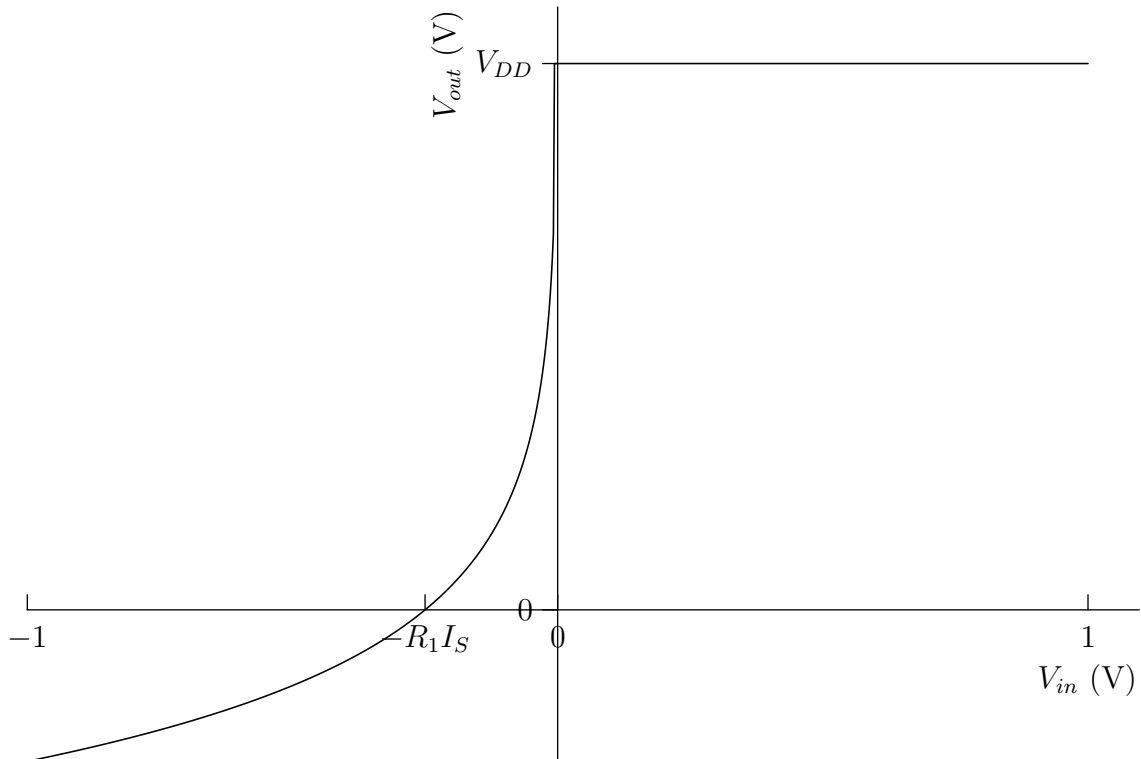This gives us the following plot of  $V_{out}$  vs.  $V_{in}$ :




Note that this circuit fails to behave as a non-inverting logarithmic amplifier.

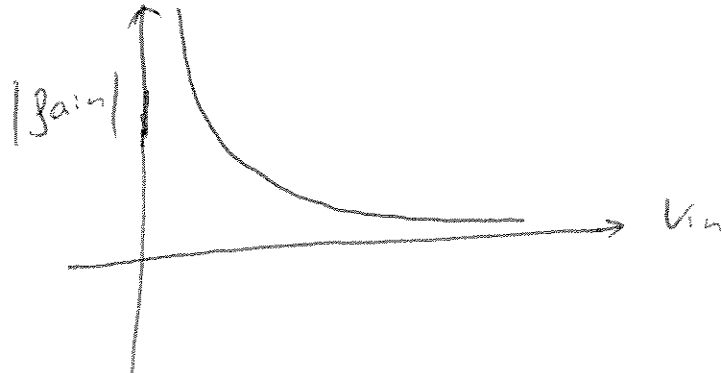(43)

$$V_{out} = -V_T / n \frac{V_{in}}{R_i I_s}$$

$$\frac{dV_{out}}{dV_{in}} = -\frac{V_T}{V_{in}}$$



The gain is compressive, because as  $V_{in}$  increases, the magnitude of the gain decreases.



8.44 (a)

$$\begin{aligned}V_{out} &= -V_T \ln \left( \frac{V_{in}}{R_1 I_S} \right) \\-0.2 \text{ V} &= -V_T \ln \left( \frac{1 \text{ V}}{R_1 I_S} \right) \\R_1 I_S &= \boxed{456 \text{ } \mu\text{V}}\end{aligned}$$

(b)

$$\begin{aligned}A_v &= \left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=1 \text{ V}} \\&= - \left. \frac{V_T}{V_{in}} \right|_{V_{in}=1 \text{ V}} \\&= \boxed{-0.026}\end{aligned}$$

8.45 When  $V_{in} < V_{TH}$ , the output goes to the positive rail. When  $V_{in} > V_{TH}$ , we have:

$$I_D = \frac{V_{in} - V_{TH}}{R_1}$$

$$V_{GS} = -V_{out} = V_{TH} + \sqrt{\frac{2I_D}{\frac{W}{L}\mu_n C_{ox}}}$$

$$V_{out} = \boxed{-V_{TH} - \sqrt{\frac{2(V_{in} - V_{TH})}{R_1 \frac{W}{L}\mu_n C_{ox}}}}$$

$$\frac{dV_{out}}{dV_{in}} = -\frac{1}{2} \sqrt{\frac{R_1 \frac{W}{L}\mu_n C_{ox}}{2(V_{in} - V_{TH})}} \frac{2}{R_1 \frac{W}{L}\mu_n C_{ox}}$$

$$= \boxed{-\sqrt{\frac{1}{2R_1 \frac{W}{L}\mu_n C_{ox} (V_{in} - V_{TH})}}, V_{in} > V_{TH}}$$

8.46 When  $V_{in} > 0$ , the output goes to the negative rail. When  $V_{in} < 0$ , we have:

$$I_D = -\frac{V_{in}}{R_1}$$

$$V_{SG} = V_{out} = |V_{TH}| + \sqrt{\frac{2|I_D|}{\frac{W}{L}\mu_p C_{ox}}}$$

$$V_{out} = \boxed{V_{TH} + \sqrt{-\frac{2V_{in}}{R_1 \frac{W}{L} \mu_p C_{ox}}}, V_{in} < 0}$$

(47)

Assume  $A_o = \infty$ ,

$$\therefore V_+ = V_- = V_{in}$$

Using voltage divider:

$$V_{in} + V_{os} = V_{out} \frac{R_1}{R_1 + R_2}$$

$$V_{out} = \left( 1 + \frac{R_2}{R_1} \right) (V_{in} + V_{os}) //$$

(48)

In Fig (8.25),


Assuming input is zero,

$$\begin{aligned}V_x &= 10 \times V_{os, A_1} \\ &= 30 \text{ mV}\end{aligned}$$

$$\begin{aligned}\therefore V_{out} &= 10 \times (V_{os, A_2} + V_x) \\ &= 330 \text{ mV}\end{aligned}$$

Thus, the maximum offset error is 330 mV.

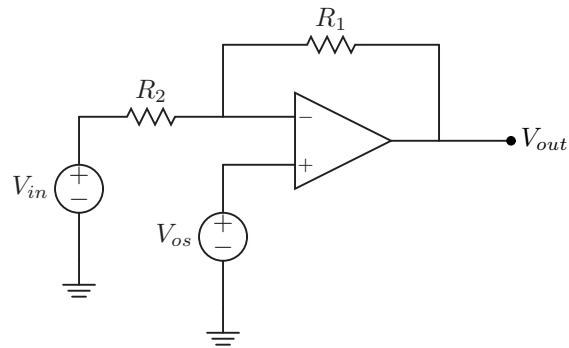8.49 We model an input offset with a series voltage source at one of the inputs.



$$\begin{aligned}
 V_{out} &= V_{in} - \frac{V_{in} - V_{os}}{R_2} (R_1 + R_2) \\
 &= V_{in} \left( 1 - \frac{R_1 + R_2}{R_2} \right) + V_{os} \frac{R_1 + R_2}{R_2} \\
 &= \boxed{-\frac{R_1}{R_2} V_{in} + \left( 1 + \frac{R_1}{R_2} \right) V_{os}}
 \end{aligned}$$

Note that even when  $V_{in} = 0$ ,  $V_{out} = (1 + R_1/R_2) V_{os}$ .

(50) By eqn (8.72)

$$V_{out} = V_{os} \left( 1 + \frac{R_2}{R_1} \right)$$

$$\therefore 20 \text{ mV} = 3 \text{ mV} \left( 1 + \frac{R_2}{R_1} \right)$$

$$\frac{17}{3} = \frac{R_2}{R_1} \quad \text{--- (1)}$$

$$\therefore \frac{1}{R_2 C_1} \ll 2\pi (1000)$$

and setting  $C_1 = 100 \text{ pF}$ ,

$$\frac{1}{R_2 \times 100 \times 10^{-12}} \ll 2\pi (1000)$$

$$\frac{1}{R_2} \ll 6.283 \times 10^{-7}$$

$$\therefore R_2 \gg 1.59 \text{ M}\Omega$$

choose  $R_2 = 17 \text{ M}\Omega //$

$R_1 = 3 \text{ M}\Omega //$  (From (1))

(51) From eqn (8.44),

$$V_{out} \propto \frac{dV_{in}}{dt}$$

(proportional)

Since offset is static (invariant with time)

$$\text{i.e. } \frac{dV_{os}}{dt} = 0.$$

$\therefore$  offset has no effect to  $V_{out}$ .



(52) From eqn (8.60),

with the presence of offset ( $V_{os}$ ),

$$V_{out} = -V_T \ln \frac{V_{in} + V_{os}}{R \cdot I_s}$$

The effect of offset to  $V_{out}$  is very small, because  $V_{out}$  is proportional to the log. of  $(V_{in} + V_{os})$ .

Thus,  $V_{out}$  is very insensitive to the magnitude of the offset.

(53). From eqn (8.76),

$$V_{out} = R_1 I_{B2}$$

∴  $V_{out}$  is independent of  $I_{B1}$

Also  $I_{B1}$  will not affect  $\frac{V_{out}}{V_{in}}$ .

Thus, the small offset ( $\Delta I$ ) in the input bias currents has no effect on  $V_{out}$ .

8.54 Let  $V_{in} = 0$ .

$$\begin{aligned}V_+ &= -I_{B1} (R_1 \parallel R_2) = -(I_{B2} + \Delta I) (R_1 \parallel R_2) = V_- \\V_{out} &= V_- + \left( I_{B2} + \frac{V_-}{R_2} \right) R_1 \\&= -(I_{B2} + \Delta I) (R_1 \parallel R_2) + \left( I_{B2} - \frac{(I_{B2} + \Delta I) (R_1 \parallel R_2)}{R_2} \right) R_1 \\&= -(I_{B2} + \Delta I) (R_1 \parallel R_2) \left( 1 + \frac{R_1}{R_2} \right) + I_{B2} R_1 \\&= \boxed{-\Delta I R_1}\end{aligned}$$

If the magnitude of the error must be less than  $\Delta V$ , we have:

$$\begin{aligned}\Delta I R_1 &< \Delta V \\R_1 &< \boxed{\frac{\Delta V}{\Delta I}}\end{aligned}$$

Note that this does not depend on  $R_2$ .

(55) Using eqn. (8.84)

$$\text{Gain} = \frac{A_0}{1 + \frac{s}{\omega_c}}$$

For opamp (a); At 100 MHz:

$$\text{Gain}_{(a)} = \frac{1000}{1 + \frac{2\pi \times 100 \times 10^6}{2\pi \times 50}}$$

$$\approx 5 \times 10^{-4}$$


For opamp (b) at 100 MHz,

$$\text{Gain}_{(b)} = \frac{500}{1 + \frac{2\pi \times 100 \times 10^6}{2\pi \times 10}}$$

$$\approx 4.95 > 4$$

$\therefore$  opamp (b) is a possible candidate

(56)

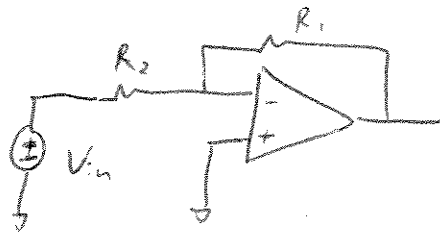

Using eq<sup>n</sup> (8.20),

$$\frac{V_{out}}{V_{in}} = - \frac{R_2}{R_1} + \frac{1}{A_0} \left( 1 + \frac{R_2}{R_1} \right)$$

Here,  $A_0$  becomes  $\frac{A_0}{1 + \frac{s}{\omega_1}}$ ,

$$\begin{aligned} \therefore \frac{V_{out}}{V_{in}} &= \frac{-1}{\frac{R_2}{R_1} + \frac{A_0}{1 + \frac{s}{\omega_1}} \left( 1 + \frac{R_2}{R_1} \right)} \\ &= \frac{- \left( 1 + \frac{s}{\omega_1} \right)}{\left( 1 + \frac{s}{\omega_1} \right) \frac{R_2}{R_1} + A_0 \left( 1 + \frac{R_2}{R_1} \right)} \end{aligned}$$

To find the pole, equate denominator to 0.

$$\text{i.e. } \left( 1 + \frac{s}{\omega_1} \right) \frac{R_2}{R_1} + A_0 \left( 1 + \frac{R_2}{R_1} \right) = 0$$

$$\left( 1 + \frac{s}{\omega_1} \right) = - \frac{R_1}{R_2} A_0 \left( 1 + \frac{R_2}{R_1} \right)$$


$$\therefore |W_{p, closed}| = \left( 1 + \frac{R_1}{R_2} A_0 \left( 1 + \frac{R_2}{R_1} \right) \right) \omega_1$$

$$\begin{aligned}
V_{out} &= -\frac{A_0}{1 + \frac{s}{\omega_0}} V_- \\
V_- &= V_{in} + \frac{V_{out} - V_{in}}{R_1 + \frac{1}{sC_1}} R_1 \\
V_{out} &= -\frac{A_0}{1 + \frac{s}{\omega_0}} \left( V_{in} + \frac{V_{out} - V_{in}}{R_1 + \frac{1}{sC_1}} R_1 \right) \\
V_{out} \left[ 1 + \frac{A_0}{1 + \frac{s}{\omega_0}} \frac{R_1}{R_1 + \frac{1}{sC_1}} \right] &= \frac{A_0}{1 + \frac{s}{\omega_0}} V_{in} \left[ \frac{R_1}{R_1 + \frac{1}{sC_1}} - 1 \right] \\
V_{out} \frac{\left( 1 + \frac{s}{\omega_0} \right) \left( R_1 + \frac{1}{sC_1} \right) + A_0 R_1}{\left( 1 + \frac{s}{\omega_0} \right) \left( R_1 + \frac{1}{sC_1} \right)} &= -V_{in} \frac{A_0 \frac{1}{sC_1}}{\left( 1 + \frac{s}{\omega_0} \right) \left( R_1 + \frac{1}{sC_1} \right)} \\
\frac{V_{out}}{V_{in}} &= -\frac{A_0 \frac{1}{sC_1}}{\left( 1 + \frac{s}{\omega_0} \right) \left( R_1 + \frac{1}{sC_1} \right) + A_0 R_1} \\
&= -\frac{A_0}{\left( 1 + \frac{s}{\omega_0} \right) (1 + sR_1C_1) + sA_0R_1C_1} \\
&= -\frac{A_0}{1 + s \left( R_1C_1 + \frac{1}{\omega_0} + A_0R_1C_1 \right) + s^2 \frac{R_1C_1}{\omega_0}} \\
&= \boxed{-\frac{A_0}{1 + s \left[ (1 + A_0) R_1C_1 + \frac{1}{\omega_0} \right] + s^2 \frac{R_1C_1}{\omega_0}}}
\end{aligned}$$

If  $\omega_0 \gg \frac{1}{R_1C_1}$ , we have:

$$\begin{aligned}
\frac{V_{out}}{V_{in}} &= -\frac{1}{\frac{1}{A_0} + s \left[ \left( 1 + \frac{1}{A_0} \right) R_1C_1 + \frac{1}{\omega_0} \right] + s^2 \frac{R_1C_1}{A_0\omega_0}} \\
&= -\frac{1}{\frac{1}{A_0} + s \left( 1 + \frac{1}{A_0} \right) R_1C_1 + s^2 \frac{R_1C_1}{A_0\omega_0}} \\
&\approx -\frac{1}{sR_1C_1 + s^2 \frac{R_1C_1}{A_0\omega_0}} \quad (\text{assuming } A_0 \gg 1) \\
&= \boxed{-\frac{1}{sR_1C_1 \left( 1 + \frac{s}{A_0\omega_0} \right)}}
\end{aligned}$$

58.

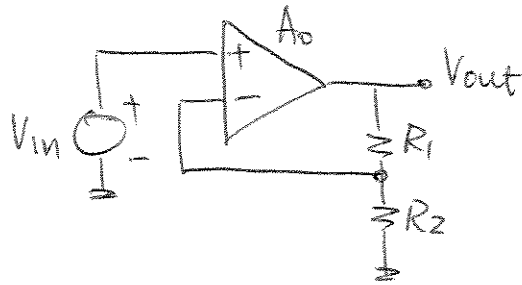

Nominal gain = 4  
 Slew Rate = 1V/ns  
 $V_p = 0.5V$

$$V_{in}(t) = 0.5 \sin \omega t \Rightarrow V_{out} = 0.5 \times \overbrace{\left(1 + \frac{R_1}{R_2}\right)}^{=4} \sin \omega t.$$

$$\frac{dV_{out}}{dt} = 0.5 \left(1 + \frac{R_1}{R_2}\right) \omega \cdot \cos \omega t.$$


$$= \text{Maximum when } \cos \omega t = 1$$

$$\Rightarrow \left. \frac{dV_{out}}{dt} \right|_{\max} = 0.5 \omega \left(1 + \frac{R_1}{R_2}\right) = 2\omega$$

$$\therefore \text{Highest frequency} \Rightarrow 2\omega = 1V/ns$$


$$\Rightarrow \omega = 0.5 \text{ rad/ns} \Rightarrow f_{\max} \approx 79.6 \text{ MHz}$$

59.

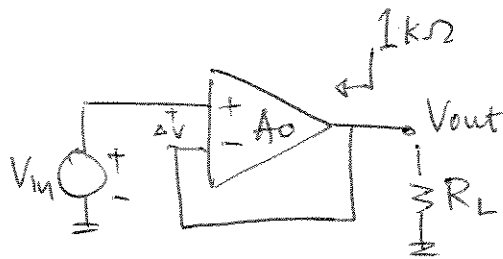

$R_L = 100 \Omega$   
Gain Error = 0.5%
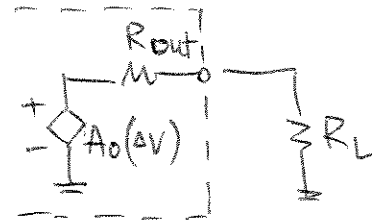
$$(V_{in} - V_{out}) A_0 \times \frac{R_L}{R_{out} + R_L} = V_{out}$$



$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{1}{1 + \frac{R_{out} + R_L}{A_0 R_L}} \approx 1 - \underbrace{\frac{R_{out} + R_L}{A_0 R_L}}_{= \epsilon}$$

$$\therefore \epsilon = \frac{R_{out} + R_L}{A_0 R_L} \Rightarrow A_0 = \frac{R_{out} + R_L}{\epsilon R_L} = \frac{1000 + 100}{0.5\% \times 100} \approx 2200$$




60.

Nominal Gain = 4

Gain Error = 0.2%

$$R_1 + R_2 = 20 \text{ k}\Omega$$

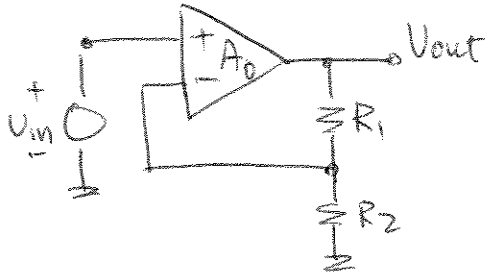

$$\left[ V_{in} - \frac{R_2}{R_1 + R_2} \times V_{out} \right] A_0 = V_{out}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0} \approx \left( 1 + \frac{R_1}{R_2} \right) \left[ 1 - \left( 1 + \frac{R_1}{R_2} \right) \frac{1}{A_0} \right]$$

$$\left( 1 + \frac{R_1}{R_2} \right) = 4 \quad \& \quad (R_1 + R_2) = 20 \text{ k}\Omega$$

$$\Rightarrow R_1 = 15 \text{ k}\Omega, \quad R_2 = 5 \text{ k}\Omega.$$


$$0.2\% = \left( 1 + \frac{R_1}{R_2} \right) \frac{1}{A_0} \Rightarrow A_0 = \left( 1 + \frac{R_1}{R_2} \right) \times \frac{1}{0.2\%}$$
$$= 2000$$

8.61 Let  $\mathcal{E}$  refer to the gain error.

$$\begin{aligned}\frac{R_1}{R_2} &= 8 \\ R_1 &= \boxed{8 \text{ k}\Omega} \\ R_2 &= \boxed{1 \text{ k}\Omega} \\ \frac{v_{out}}{v_{in}} &= -\frac{R_1}{R_2} \frac{A_0 - \frac{R_{out}}{R_1}}{1 + \frac{R_{out}}{R_2} + A_0 + \frac{R_1}{R_2}} \quad (\text{Eq. 8.99}) \\ &= -\frac{R_1}{R_2} (1 - \mathcal{E}) \\ \mathcal{E} &= 1 - \frac{A_0 - \frac{R_{out}}{R_1}}{1 + \frac{R_{out}}{R_2} + A_0 + \frac{R_1}{R_2}} \\ &= 0.1 \% \\ A_0 &= \boxed{9103}\end{aligned}$$

Note that we can pick any  $R_1, R_2$  such that their ratio is 8 (i.e., this solution is not unique). However,  $A_0$  will change depending on the values chosen.

62.

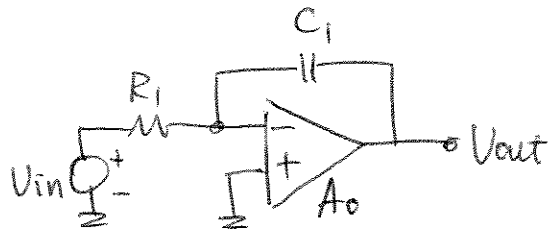

$$\begin{aligned} &= 100 \text{ kHz} \\ \text{pole} &= 100 \text{ Hz} \\ C_{\text{MAX}} &= 50 \text{ pF}. \end{aligned}$$

$$\frac{V_{in} - V_{(-)}}{R_1} = (V_{(-)} - V_{out}) \leq C_1 \quad \text{--- (1)}$$

$$V_{(-)} \cdot (-A_0) = V_{out} \quad \text{--- (2)}$$

Substitute (2) into (1):

$$\frac{V_{out}}{V_{in}} = \frac{-1}{\frac{1}{A_0} + (1 + \frac{1}{A_0}) R_1 C_1 s}$$

$$\Rightarrow s_p = \frac{-1}{(A_0 + 1) R_1 C_1} = -100 \text{ Hz} \quad \text{--- (1)}$$


Attenuation above 100 kHz  $\Rightarrow \left| \frac{V_{out}}{V_{in}} \right|_{100 \text{ kHz}} = 1$

$$\Rightarrow \frac{A_0}{\sqrt{1 + [(A_0 + 1) R_1 C_1 \omega] ^2}} \Big|_{100 \text{ kHz}} = 1 \quad \text{--- (2)}$$

Substitute (1) into (2):

$$\Rightarrow A_0 \approx 1000. \quad \text{Choose } C = 50 \text{ pF} \Rightarrow R \approx 200 \text{ k}\Omega.$$

63.

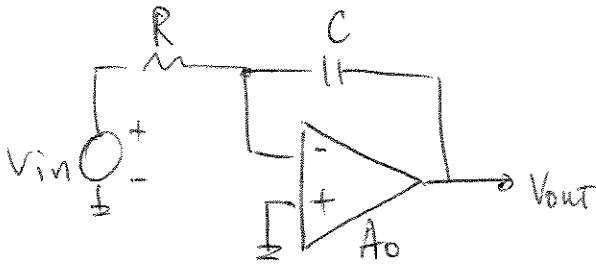

$$V(t) = \alpha t$$


$$0 < V(t) < V_0$$

$$\text{where } \alpha = 10 \text{ V}/\mu\text{s}$$

$$V_0 = 1 \text{ V}$$

$$C_{\text{max}} = 20 \text{ pF}$$

$$\text{Error} < 0.1\%$$

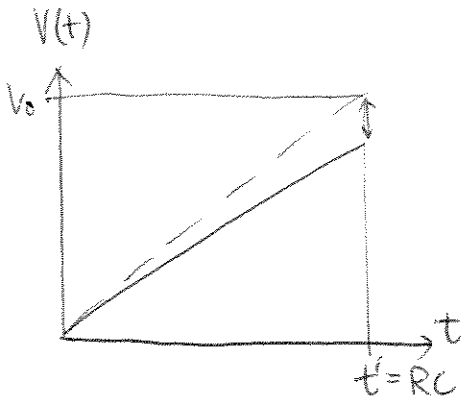

$$V_{\text{out}}(t) = -\frac{V_0}{RC} t, \quad t \in [0, RC]$$

$$V(t) = -\alpha t$$

$$\text{At } t = RC, \quad \frac{\Delta V}{V_0} = \frac{V_{\text{out}}(t) - V(t)}{V_0} \Bigg|_{t=RC} < 0.1\%$$


$$\Rightarrow \Delta V = V_0 \times 0.1\% = 0.001 \text{ V}$$

$$\Rightarrow -\frac{V_0}{RC} \times t + \alpha t \Bigg|_{t=RC} = 0.001 \text{ V } (= \Delta V)$$

Choose  $C = 20 \text{ pF}$

$$\therefore R = \frac{V_0 - \Delta V}{\alpha C} = \frac{1 \text{ V} - 0.001 \text{ V}}{10 \text{ V}/\mu\text{s} \times 20 \text{ pF}} = 499552$$

64.

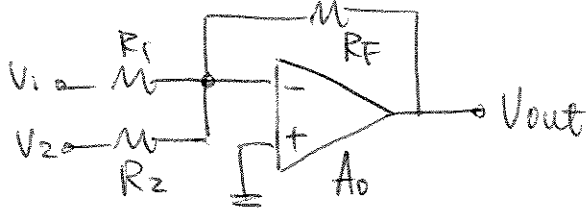

$$V_{out} = \alpha_1 V_1 + \alpha_2 V_2$$

$\uparrow$                        $\uparrow$   
 0.5                      1.5

Error of  $\alpha \leq 0.5\%$   
 $r_{in} \geq 10 \text{ k}\Omega$ .

$$\frac{V_1 - V(-)}{R_1} + \frac{V_2 - V(-)}{R_2} = \frac{V(-) - V_{out}}{R_F} \quad \text{--- ①}$$

$$V(-) \cdot (-A_0) = V_{out} \quad \text{--- ②}$$

Substitute ② into ① & solve for  $V_{out}$ :

$$V_{out} = - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right) \cdot \left[ \frac{1}{A_0} \left( \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right) + 1 \right]^{-1}$$


$$\approx - \left( \frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right) \cdot \left[ 1 - \frac{1}{A_0} \left( \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right) \right]$$

Choose  $r_{in, v_2} (\approx R_2) = 10 \text{ k}\Omega \Rightarrow R_F = \alpha_2 \times R_2 = 15 \text{ k}\Omega$   
 $\Rightarrow R_1 = R_F / \alpha_1 = 30 \text{ k}\Omega$   
 $\approx r_{in, v_1}$

$$\Rightarrow \epsilon = 0.5\% = \frac{1}{A_0} \left( \frac{R_F}{R_1} + \frac{R_F}{R_2} + 1 \right)$$

$$\Rightarrow A_0 = \frac{1}{0.5\%} (0.5 + 1.5 + 1) = 600 \quad (\text{or larger})$$

65.

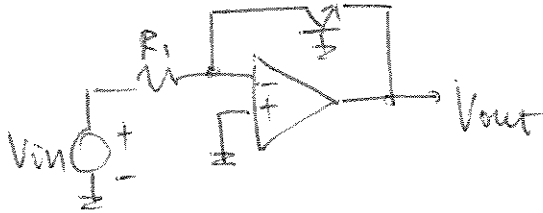

$$[0.1, 2] \text{ V} \mapsto [-0.5, -1] \text{ V}$$

$$V_{out} = -V_T \ln \frac{V_{in}}{I_s R_i}$$

$$-0.5 \text{ V} = -V_T \ln \left[ \frac{(0.1)}{I_s R_i} \right] \Rightarrow I_s R_i = 4.45 \cdot 10^{-10} \text{ V} \quad \text{--- (1)}$$

$$\Rightarrow -V_T \ln \left( \frac{2}{I_s R_i} \right) = -0.026 \text{ V} \ln \left( \frac{2}{4.45 \cdot 10^{-10}} \right) \approx -0.58 \text{ V}$$


∴ input range of  $0.1 \leftrightarrow 2 \text{ V}$  corresponds to output range of  $-0.5 \leftrightarrow -0.58 \text{ V}$

$$\text{Choose } I_s = 1 \times 10^{-16} \text{ A} \Rightarrow R_i = 4.45 \text{ M}\Omega.$$

$$\begin{aligned}V_{out} &= -V_T \ln \left( \frac{V_{in}}{R_1 I_S} \right) \\ \frac{dV_{out}}{dV_{in}} &= -V_T \frac{R_1 I_S}{V_{in}} \frac{1}{R_1 I_S} \\ &= -\frac{V_T}{V_{in}}\end{aligned}$$

No, it is not possible to satisfy both requirements. As shown above,  $\left| \frac{dV_{out}}{dV_{in}} \right| = \frac{V_T}{V_{in}}$ , meaning for a specified temperature and input, the gain is fixed. Assuming we could fix the temperature as part of the design, we could still only meet one of the two constraints, since the temperatures at which the constraints are met are not equal.

1.

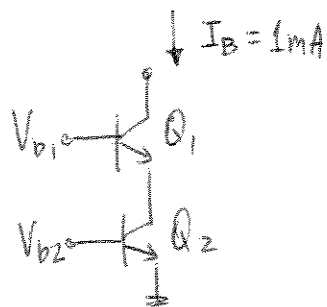

$$I_S = 6 \cdot 10^{-17} \text{ A}$$

$$\beta = 100$$

$$V_A \rightarrow \infty$$

$$V_T = \frac{kT}{q}$$

$$\alpha = \frac{\beta}{\beta + 1}$$

$$(a) \quad V_{b2} = V_T \ln\left(\frac{I_B / \alpha^2}{I_S}\right) = (0.026 \text{ V}) \ln\left(\frac{1.02 \text{ mA}}{6 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 0.792 \text{ V}$$

(b) From the configuration,

$$V_{b1} = V_{CE2} + V_{BE1} = (V_{BE2} - 300 \text{ mV}) + V_{BE1}$$


$$V_{BE1} = V_T \ln\left(\frac{I_B}{I_S}\right) = (0.026 \text{ V}) \ln\left(\frac{1 \text{ mA}}{6 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 0.792 \text{ V}$$

$$\therefore V_{b1} = (0.792 - 0.3) + 0.79 = 1.28 \text{ V}$$



2.

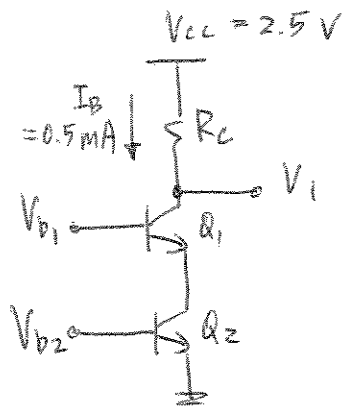

$$(a) \quad V_{b2} = V_{BE2} = V_T \ln\left(\frac{I_B/\alpha^2}{I_s}\right) = (0.026\text{V}) \ln\left(\frac{0.51\text{mA}}{6 \cdot 10^{-17}\text{A}}\right) \\ \approx 0.774\text{V}$$

$$V_{BE1} = V_{b1} - V_{c2} = V_{b1} - (V_{b2} - 300\text{mV})$$


$$\Rightarrow V_{b1} = V_{BE1} + V_{b2} - 0.3\text{V} \\ = (0.026\text{V}) \ln\left(\frac{0.5\text{mA}}{6 \cdot 10^{-17}\text{A}}\right) + (0.774\text{V}) - (0.3\text{V}) \\ \approx 1.25\text{V}$$

$$(b) \quad V_1 = V_{b1} - 0.3\text{V} = 0.95\text{V}$$

$$\therefore R_c = \frac{V_{cc} - V_1}{I_B} = \frac{(2.5 - 0.95)\text{V}}{0.5\text{mA}} \approx 3.1\text{K}\Omega$$

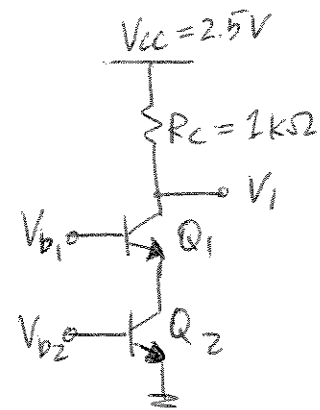3. From previous experience,  
 assume both  $V_{BE1}$  &  
 $V_{BE2} = 0.8 \text{ V}$

$$\begin{aligned} \Rightarrow V_1 &= V_{CE1} + V_{CE2} \\ &= (V_{BE1} - 200\text{mV}) + (V_{BE2} - 200\text{mV}) \\ &= 1.2 \text{ V} \end{aligned}$$




\* By KCL, maximum bias current

$$\approx \frac{V_{CC} - V_1}{R_c} = \frac{(2.5 - 1.2) \text{ V}}{1 \text{ k}\Omega} = 1.3 \text{ mA.}$$

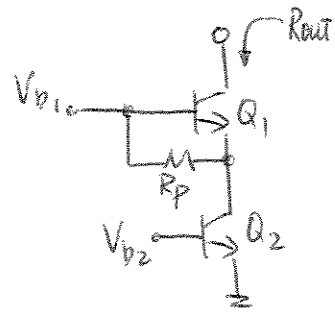
4. (a)  $R_p$  appears in parallel with  $r_{\pi_1}$

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1} \parallel R_p)]r_{o_1} + (r_{o_2} \parallel r_{\pi_1} \parallel R_p)$$



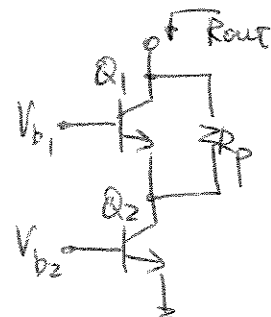
(b)  $R_p$  appears in parallel with  $r_{o_1}$

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1})](r_{o_1} \parallel R_p) + (r_{o_2} \parallel r_{\pi_1})$$



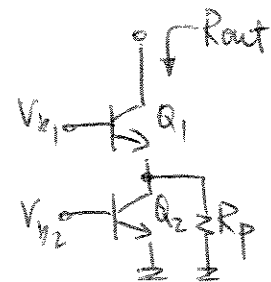
(c)  $R_p$  appears in parallel with  $r_{o_2}$

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1} \parallel R_p)]r_{o_1} + (r_{o_2} \parallel r_{\pi_1} \parallel R_p)$$




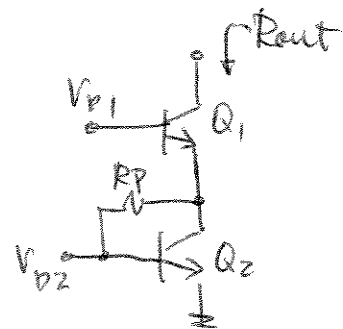(d)  $R_p$  appears in parallel with  $r_{o_2}$  (in small-signal)  $\therefore V_{b_2}$  is AC GND.

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1} \parallel R_p)]r_{o_1} + (r_{o_2} \parallel r_{\pi_1} \parallel R_p)$$



5.

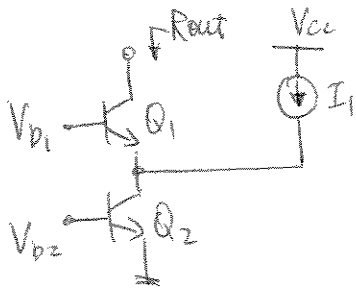

$$I_1 = 0.5 \text{ mA}$$

$$I_{C1} = 0.5 \text{ mA}$$

$$I_{C2} = 1 \text{ mA}$$

$$= 2 I_{C1}$$

$$\beta = 100 \quad V_A = 5 \text{ V}$$

$$R_{out} = g_{m1} r_{o1} (r_{o2} \parallel r_{\pi1})$$


$$= \frac{I_{C1}}{V_T} \cdot \frac{V_A}{I_{C1}} \cdot \frac{V_{A2}/I_{C2} \cdot \beta V_T / I_{C1}}{V_{A2}/I_{C2} + \beta V_T / I_{C1}}$$

$$= \frac{V_A}{V_T} \cdot \frac{V_{A2}/2}{I_{C1}} \cdot \frac{\beta V_T / I_{C1}}{\frac{V_{A2}/2}{I_{C1}} + \beta V_T / I_{C1}} \approx \frac{1}{I_{C1}} \cdot \frac{V_A}{V_T} \cdot \frac{\beta V_A V_T}{V_A + 2\beta V_T}$$

$$= \frac{1}{0.5 \text{ mA}} \cdot \frac{5 \text{ V}}{0.026 \text{ V}} \cdot \frac{100(5 \text{ V})(0.026 \text{ V})}{(5 \text{ V}) + 2(100)(0.026 \text{ V})}$$


$$\therefore R_{out} \approx 490 \text{ k}\Omega$$

6.

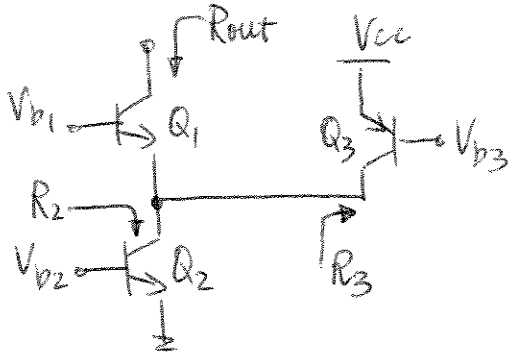

$$R_3 = r_{o3} \quad (V_{cc} \text{ \& } V_{b3} \text{ are AC GND})$$
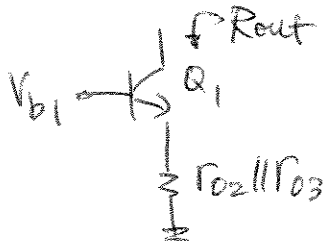
$$R_2 = r_{o2} \quad (V_{b2} \text{ is AC GND})$$



$$\therefore R_{out} = [1 + g_{m1} (r_{o2} \parallel r_{o3} \parallel r_{\pi 1})] r_{o1} + (r_{o2} \parallel r_{o3} \parallel r_{\pi 1})$$

$$\approx g_{m1} r_{o1} (r_{o2} \parallel r_{o3} \parallel r_{\pi 1})$$

9.7 Let  $R_2$  be the resistance seen looking into the collector of  $Q_2$ .

$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi1} \parallel R_2)$$


Note that this expression is maximized as  $R_2 \rightarrow \infty$ . This gives us

$$R_{out,max} = \boxed{r_{o1} + (1 + g_{m1}r_{o1})r_{\pi1}}$$

$$8. (a) R_2 = (r_{\pi_2} \parallel r_{\pi_1})$$

$$\therefore R_{out} = [1 + g_{m_1} R_2] r_{o_1} + R_2$$
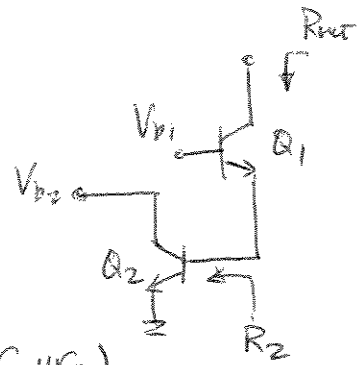
$$= [1 + g_{m_1} (r_{\pi_1} \parallel r_{\pi_2})] r_{o_1} + (r_{\pi_1} \parallel r_{\pi_2})$$



$$(b) \text{ In part (a), } I_{c_2} = \beta I_{c_1} (= I_{B_2})$$

$$\therefore R_{out(a)} = \left[ 1 + g_{m_1} \left( \frac{\beta V_T}{I_{c_1}} \parallel \frac{V_T}{I_{c_1}} \right) \right] r_{o_1} + (r_{\pi_1} \parallel r_{\pi_2})$$

$$\approx \left( 1 + g_{m_1} \frac{V_T}{I_{c_1}} \right) r_{o_1} + \frac{V_T}{I_{c_1}}$$

$$= 2r_{o_1} + V_T/I_{c_1}$$

$$\begin{aligned} R_{out, \text{cascode}} &= [1 + g_{m_1} (r_{o_2} \parallel r_{\pi_1})] r_{o_1} + (r_{o_2} \parallel r_{\pi_1}) \\ &\approx [1 + g_{m_1} r_{\pi_1}] r_{o_1} + r_{\pi_1} \\ &\approx \beta r_{o_1} + r_{\pi_1} = \beta r_{o_1} + V_A/I_{c_1} \end{aligned}$$

Compare term-by-term:

$$\left. \begin{array}{l} 2r_{o_1} \ll \beta r_{o_1} \\ V_T \ll V_A \end{array} \right\} \Rightarrow R_{out(a)} \ll R_{out, \text{cascode}}$$

i.e. using (a) reduces the effect of having a cascode configuration.

9.9

$$\begin{aligned} R_{out} &\approx \frac{1}{I_{C1}} \frac{V_A}{V_T} \frac{\beta V_A V_T}{V_A + \beta V_T} \quad (\text{Eq. 9.9}) \\ &= \frac{1}{I_{C1}} \frac{V_A}{V_T} \beta V_T \\ &= \frac{\beta V_A}{I_{C1}} \\ &= \boxed{\beta r_o} \end{aligned}$$

This resembles Eq. (9.12) because the assumption that


$$V_A \gg \beta V_T$$

can be equivalently expressed as

$$\begin{aligned} \frac{V_A}{I_C} &\gg \beta \frac{V_T}{I_C} \\ r_o &\gg r_\pi \end{aligned}$$

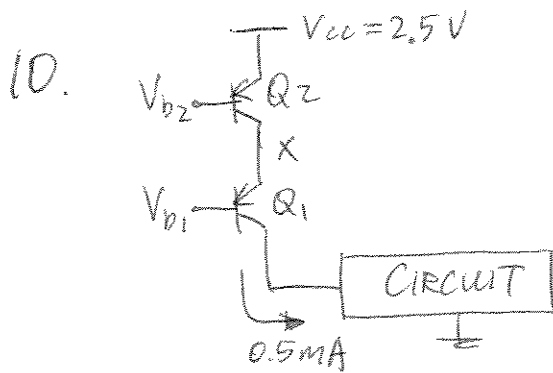This is the same assumption used in arriving at Eq. (9.12).





$$I_S = 10^{-16} \text{ A} \quad \beta = 100$$

$$I_{BIAS} = 0.5 \text{ mA}$$

(a)  $I_{BIAS} \approx I_{C2} = 0.5 \text{ mA}$


$$\begin{aligned} \therefore V_{b2} &= V_{CC} - |V_{BE2}| \\ &= V_{CC} - V_T \ln \left( \frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \\ &= (2.5 \text{ V}) - (0.026 \text{ V}) \ln \left( \frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \approx 1.74 \text{ V} \end{aligned}$$

(b)  $|V_{CB2}| = V_X - V_{b2} = 200 \text{ mV}$   
 $\Rightarrow V_{C2} = V_{b2} + |V_{CB2}| = 1.94 \text{ V}$


$$\begin{aligned} \therefore V_{b1} &= V_{C2} - |V_{BE1}| = V_{C2} - V_T \ln \left( \frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \\ &= (1.94 \text{ V}) - (0.026 \text{ V}) \ln \left( \frac{0.5 \text{ mA}}{10^{-16} \text{ A}} \right) \approx 1.18 \text{ V} \end{aligned}$$

$\Rightarrow$  Maximum allowable  $V_{b1} = 1.18 \text{ V}$

11. (a)

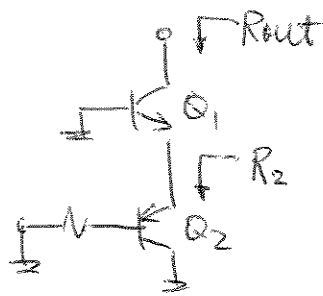

(Ac-small signal)

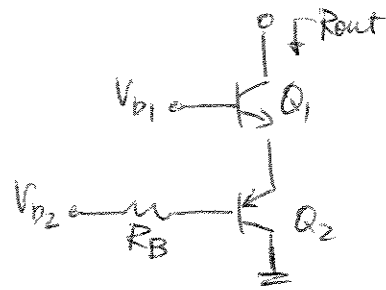


Looking into emitter of  $Q_2$ ,

$$R_2 = \frac{1}{\left( \frac{\beta+1}{R_B + r_{\pi_2}} + \frac{1}{r_{o_2}} \right)}$$

$$\Rightarrow R_{out} = [1 + g_{m_1}(R_2 \parallel r_{\pi_1})] r_{o_1} + (R_2 \parallel r_{\pi_1})$$

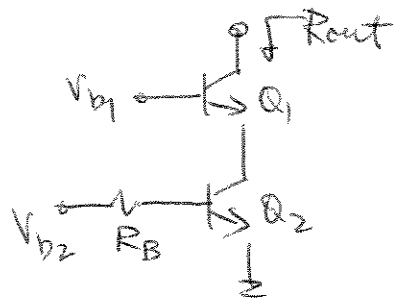(b)  $R_B$  does not affect  $Q_2$  in small-signal  $R_{out}$ :

$$\therefore R_{out} = [1 + g_{m_1}(r_{o_2} \parallel r_{\pi_1})] r_{o_1} + (r_{o_2} \parallel r_{\pi_1})$$




This is a cascode stage.

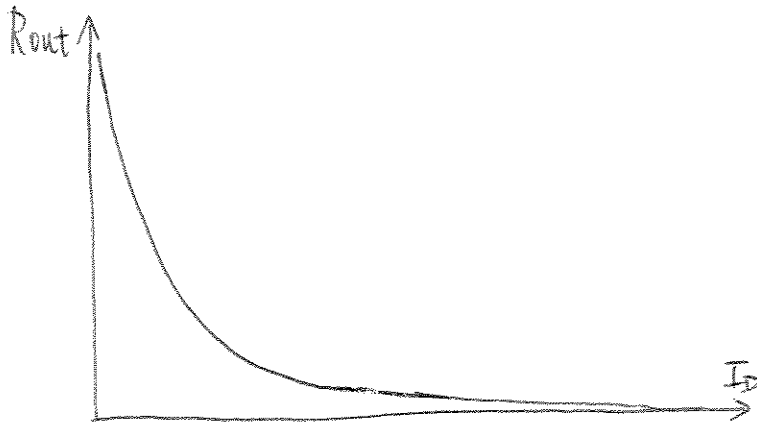9.12

$$\begin{aligned}I_D &= 0.5 \text{ mA} \\R_{out} &= r_{o1} + (1 + g_{m1}r_{o1})r_{o2} \\&= \frac{1}{\lambda I_D} + \left(1 + \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D} \frac{1}{\lambda I_D}\right) \frac{1}{\lambda I_D} \\&\geq 50 \text{ k}\Omega \\ \lambda &\leq \boxed{0.558 \text{ V}^{-1}}\end{aligned}$$


$$\begin{aligned}
 13. (a) \quad R_{out} &= g_{m2} r_{o1} r_{o2} = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} \cdot \frac{1}{\lambda I_D} \cdot \frac{1}{\lambda I_D} \\
 &= 2 \mu_n C_{ox} \left(\frac{W}{L}\right) \cdot (I_D)^{-3/2}
 \end{aligned}$$



$$\begin{aligned}
 (b) \quad R_{out} \text{ (BJT)} &\propto I_B^{-1} \\
 R_{out} \text{ (MOS)} &\propto I_B^{-3/2}
 \end{aligned}$$

$\therefore$  MOS cascode is a stronger function of  $I$  in terms of  $R_{out}$ .

14.

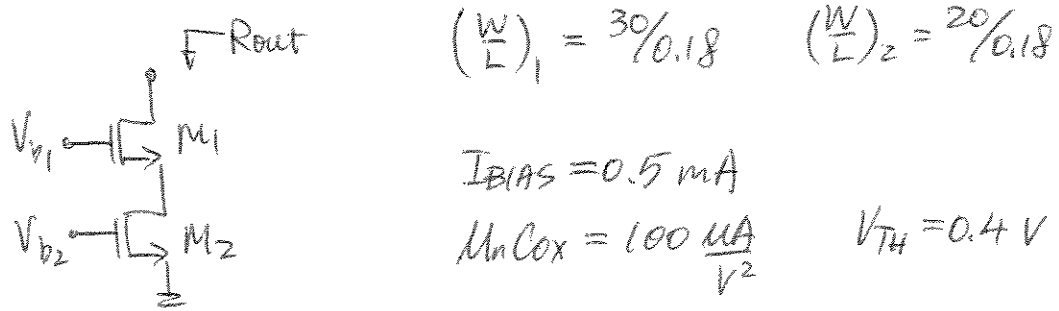

$$(a) \quad I_{D2} = I_{BIAS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{b2} - V_{TH})^2$$

$$\begin{aligned} \Rightarrow V_{b2} &= \sqrt{\frac{2 I_{BIAS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} + V_{TH} \\ &= \sqrt{\frac{2 (0.5 \text{ mA})}{(100 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{20}{0.18}\right)}} + 0.4 \text{ V} \approx 0.7 \text{ V} \end{aligned}$$

$M_2$  operates in saturation as long as

$$V_{GS2} - V_{TH} \leq V_{DS2} \Rightarrow V_{DS2} \geq 0.3 \text{ V.}$$

Observe that  $V_{GS1} = V_{b1} - V_{DS2}$

$$I_{D1} = I_{BIAS} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{b1} - V_{DS2} - V_{TH})^2$$

$$\begin{aligned} \Rightarrow V_{b1} &\geq \sqrt{\frac{2 I_{BIAS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} + 0.4 \text{ V} + 0.3 \text{ V} \\ &= \sqrt{\frac{2 (0.5 \text{ mA})}{(100 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{30}{0.18}\right)}} + 0.7 \text{ V} \approx 0.95 \text{ V.} \end{aligned}$$

$\therefore$  Minimum  $V_{b1} = 0.95 \text{ V.}$

$$(b) R_{out} = (1 + g_{m1} r_{o2}) r_{o1} + r_{o2}$$

$$= \left( 1 + \sqrt{2 \mu_n C_{ox} \left( \frac{W}{L} \right)_1 I_{BIAS}} \cdot \frac{1}{\lambda I_{BIAS}} \right) \cdot \frac{1}{\lambda I_{BIAS}} + \frac{1}{\lambda I_{BIAS}}$$
$$= \left[ 1 + \sqrt{2 \left( \frac{100 \mu A}{V^2} \right) \left( \frac{30}{0.18} \right) (0.5 \text{ mA})} \cdot \frac{1}{(0.1)(0.5 \text{ m})} \right] \cdot \frac{1}{(0.1)(0.5 \text{ m})}$$
$$+ \frac{1}{(0.1)(0.5 \text{ mA})}$$
$$\approx 1.67 \text{ M}\Omega$$

9.15 (a)

$$V_{D1} = V_{DD} - I_D R_D = 1.3 \text{ V} > V_{G1} - V_{TH} = V_{b1} - V_{TH}$$

$$V_{b1} < \boxed{1.7 \text{ V}}$$

(b)

$$V_{b1} = 1.7 \text{ V}$$

$$V_{GS1} = V_{b1} - V_X$$

$$= V_{TH} + \sqrt{\frac{2I_D}{\left(\frac{W}{L}\right)_1 \mu_n C_{ox}}}$$

$$= 0.824 \text{ V}$$

$$V_X = \boxed{0.876 \text{ V}}$$

9.16 (a) Looking down from the source of  $M_1$ , we see an equivalent resistance of  $\frac{1}{g_{m2}} \parallel r_{o2}$ . Thus, we have

$$R_{out} = \boxed{g_{m1}r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$


(b)

$$R_{out} = \boxed{g_{m1}r_{o1}r_{o2}}$$

(c) Putting two transistors in parallel, their transconductances will add and their output resistances will be in parallel (i.e., we can treat  $M_1$  and  $M_3$  as a single transistor with  $g_m = g_{m1} + g_{m3}$  and  $r_o = r_{o1} \parallel r_{o3}$ ). This can be seen from the small-signal model.

$$R_{out} = \boxed{(g_{m1} + g_{m3})(r_{o1} \parallel r_{o3})r_{o2}}$$

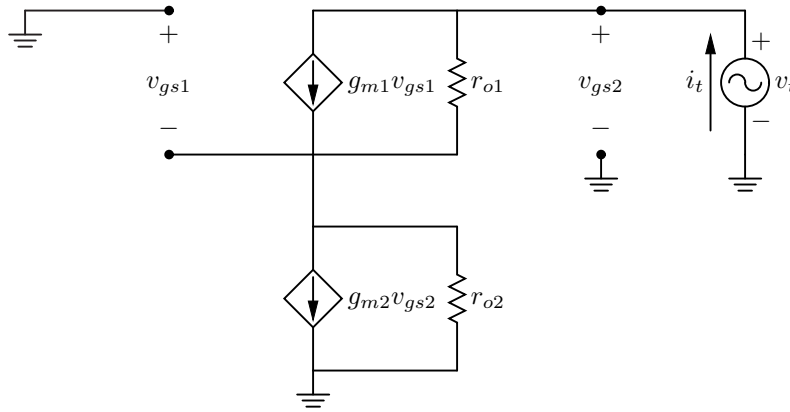(d) Let's draw the small-signal model and apply a test source to find  $R_{out}$ .



$$i_t = g_{m2}v_{gs2} - \frac{v_{gs1}}{r_{o2}} = g_{m1}v_{gs1} + \frac{v_{gs2} + v_{gs1}}{r_{o1}}$$

$$v_{gs1} = g_{m2}r_{o2}v_t - i_t r_{o2}$$

$$i_t = g_{m1}(g_{m2}r_{o2}v_t - i_t r_{o2}) + \frac{v_t + g_{m2}r_{o2}v_t - i_t r_{o2}}{r_{o1}}$$

$$i_t \left( 1 + g_{m1}r_{o2} + \frac{r_{o2}}{r_{o1}} \right) = v_t \left( g_{m1}g_{m2}r_{o2} + \frac{1 + g_{m2}r_{o2}}{r_{o1}} \right)$$

$$i_t (g_{m1}r_{o1}r_{o2}) = v_t (g_{m1}g_{m2}r_{o1}r_{o2})$$


$$R_{out} = \frac{v_t}{i_t} = \boxed{\frac{1}{g_{m2}}}$$



9.17

$$\begin{aligned} I_D &= 0.5 \text{ mA} \\ R_{out} &= r_{o1} + (1 + g_{m1}r_{o1})r_{o2} \\ &= \frac{1}{\lambda I_D} + \left( 1 + \sqrt{2 \left( \frac{W}{L} \right)_1 \mu_p C_{ox} I_D \frac{1}{\lambda I_D}} \right) \frac{1}{\lambda I_D} \\ &= 40 \text{ k}\Omega \\ \left( \frac{W}{L} \right)_1 &= \left( \frac{W}{L} \right)_2 = \boxed{8} \end{aligned}$$

18.

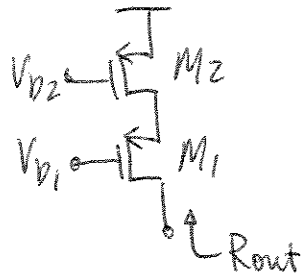


$$R_{out} = g_{m1} r_{o1} r_{o2} = \sqrt{2 \mu_p C_{ox} \left(\frac{W}{L}\right)_1 I_D} \cdot \frac{1}{\lambda I_D} \cdot \frac{1}{\lambda I_D}$$

If  $W_1$  &  $W_2$  increase by  $N$  times and  $L_1, L_2$ , and  $I_D$  remain unchanged:


$$\begin{aligned} R_{out}(\text{new}) &= \sqrt{2 \mu_p C_{ox} \left(\frac{NW}{L}\right) I_D} \cdot \left(\frac{1}{\lambda I_D}\right)^2 \\ &= \sqrt{N} \sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D} \cdot \left(\frac{1}{\lambda I_D}\right)^2 = \sqrt{N} R_{out} \end{aligned}$$

$\therefore R_{out}$  is increased by  $\sqrt{N}$  times.

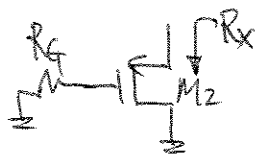19. (a)  $R_x$  is the input impedance of a common-gate configuration:



"Looking into" the source of  $M_2$ ,

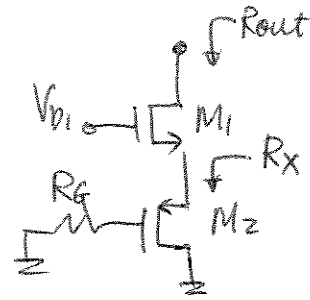


$$R_x = \frac{1}{g_{m2}} \parallel r_{o2}$$

$$\therefore R_{out} = g_{m1} r_{o1} R_x = g_{m1} r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)$$

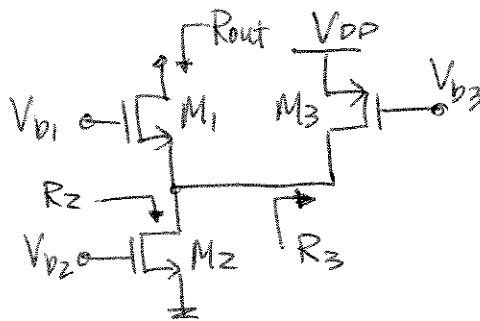(b) From observation,

$$\rightarrow R_3 = r_{o3} \quad (\because V_{sg} = 0 \text{ in AC})$$

$$\rightarrow R_2 = r_{o2} \quad (\because V_{sg} = 0 \text{ in AC})$$




$$\therefore R_{out} = g_{m1} r_{o1} (R_2 \parallel R_3) = g_{m1} r_{o1} (r_{o2} \parallel r_{o3})$$

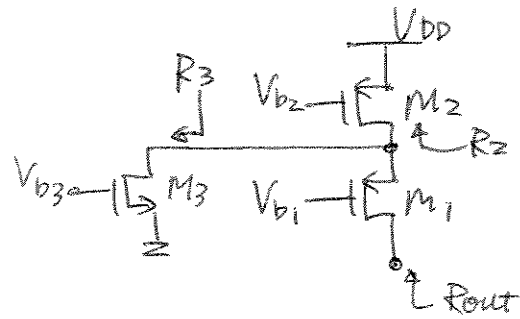(c) By observation,

$$R_2 = r_{o2} \quad (V_s = V_G = AC \text{ GND})$$

$$R_3 = r_{o3} \quad (V_s = V_G = AC \text{ GND})$$




$$\therefore R_{out} = g_{m1} r_{o1} (R_2 \parallel R_3) = g_{m1} r_{o1} (r_{o2} \parallel r_{o3})$$

(d)  $R_x = g_{m2} r_{o2} r_{o3}$

$$\Rightarrow R_{out} = g_{m1} r_{o1} R_x$$

$$= g_{m1} g_{m2} r_{o1} r_{o2} r_{o3}$$

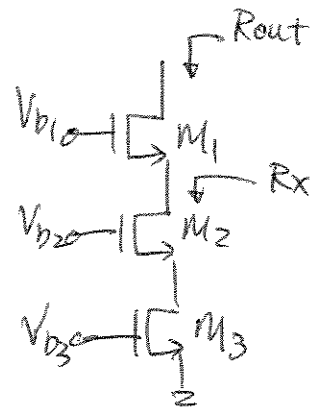

9.20 (a)

$$G_m = \boxed{g_{m1}}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{o1}$$

$$A_v = \boxed{-g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{o1} \right)}$$


(b)

$$G_m = \boxed{-g_{m2}}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{o1}$$

$$A_v = \boxed{g_{m2} \left( \frac{1}{g_{m2}} \parallel r_{o2} \parallel r_{o1} \right)}$$

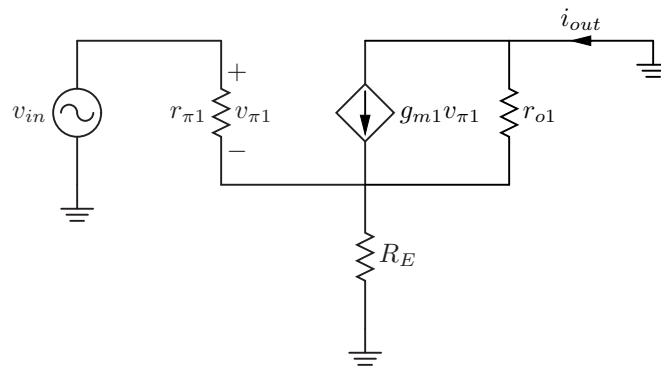(c) Let's draw the small-signal model to find  $G_m$ .




$$\begin{aligned}
i_{out} &= -\frac{v_{\pi 1}}{r_{\pi 1}} + \frac{v_{in} - v_{\pi 1}}{R_E} \\
v_{\pi 1} &= v_{in} + (i_{out} - g_{m1}v_{\pi 1})r_{o1} \\
v_{\pi 1}(1 + g_{m1}r_{o1}) &= v_{in} + i_{out}r_{o1} \\
v_{\pi 1} &= \frac{v_{in} + i_{out}r_{o1}}{1 + g_{m1}r_{o1}} \\
i_{out} &= -\frac{v_{in} + i_{out}r_{o1}}{r_{\pi 1}(1 + g_{m1}r_{o1})} + \frac{v_{in}}{R_E} - \frac{v_{in} + i_{out}r_{o1}}{R_E(1 + g_{m1}r_{o1})} \\
i_{out} \left[ 1 + \frac{r_{o1}}{r_{\pi 1}(1 + g_{m1}r_{o1})} + \frac{r_{o1}}{R_E(1 + g_{m1}r_{o1})} \right] &= v_{in} \left[ \frac{1}{R_E} - \frac{1}{r_{\pi 1}(1 + g_{m1}r_{o1})} - \frac{1}{R_E(1 + g_{m1}r_{o1})} \right] \\
i_{out} \frac{r_{\pi 1}R_E(1 + g_{m1}r_{o1}) + r_{o1}R_E + r_{o1}r_{\pi 1}}{r_{\pi 1}R_E(1 + g_{m1}r_{o1})} &= v_{in} \frac{r_{\pi 1}(1 + g_{m1}r_{o1}) - R_E - r_{\pi 1}}{r_{\pi 1}R_E(1 + g_{m1}r_{o1})} \\
i_{out} [r_{\pi 1}R_E(1 + g_{m1}r_{o1}) + r_{o1}R_E + r_{o1}r_{\pi 1}] &= v_{in} [r_{\pi 1}(1 + g_{m1}r_{o1}) - R_E - r_{\pi 1}] \\
G_m &= \frac{i_{out}}{v_{in}} \\
&= \frac{r_{\pi 1}(1 + g_{m1}r_{o1}) - R_E - r_{\pi 1}}{r_{\pi 1}R_E(1 + g_{m1}r_{o1}) + r_{o1}R_E + r_{o1}r_{\pi 1}} \\
&\approx \frac{g_{m1}}{1 + g_{m1}R_E} \quad (\text{if } r_{\pi 1}, r_{o1} \text{ are large}) \\
R_{out} &= r_{o2} \parallel [r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi 1} \parallel R_E)]
\end{aligned}$$

$$A_v = -\frac{r_{\pi 1}R_E(1 + g_{m1}r_{o1}) - R_E - r_{\pi 1}}{r_{\pi 1}R_E(1 + g_{m1}r_{o1}) + r_{o1}R_E + r_{o1}r_{\pi 1}} \{r_{o2} \parallel [r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi 1} \parallel R_E)]\}$$

(d)

$$\begin{aligned}
G_m &= g_{m2} \\
R_{out} &= r_{o2} \parallel [r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi 1} \parallel R_E)] \\
A_v &= -g_{m2} \{r_{o2} \parallel [r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi 1} \parallel R_E)]\}
\end{aligned}$$

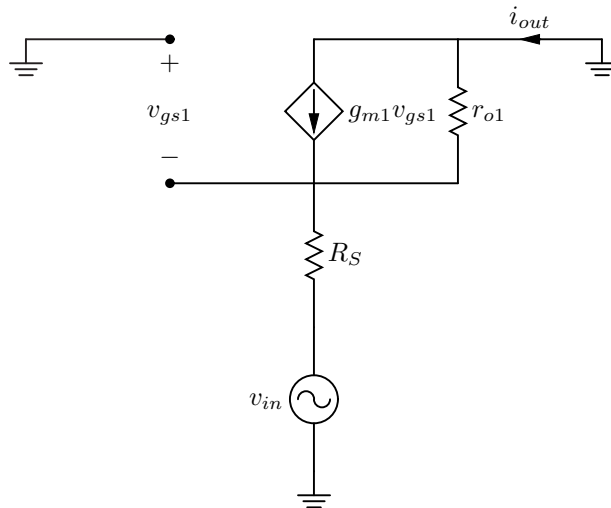(e) Let's draw the small-signal model to find  $G_m$ .



Since the gate and drain are both at AC ground, the dependent current source looks like a resistor with value  $1/g_{m1}$ . Thus, we have:

$$\begin{aligned}
G_m &= \frac{i_{out}}{v_{in}} = -\frac{1}{R_S + \frac{1}{g_{m1}} \parallel r_{o1}} \\
&= -\frac{1}{R_S + \frac{r_{o1}}{1+g_{m1}r_{o1}}} \\
&= \boxed{-\frac{1+g_{m1}r_{o1}}{r_{o1} + R_S + g_{m1}r_{o1}R_S}} \\
&\approx -\frac{g_{m1}}{1+g_{m1}R_S} \text{ (if } r_{o1} \text{ is large)} \\
R_{out} &= [r_{o2} + (1+g_{m2}r_{o2})R_E] \parallel [r_{o1} + (1+g_{m1}r_{o1})R_S] \\
A_v &= \boxed{-\frac{1+g_{m1}r_{o1}}{r_{o1} + R_S + g_{m1}r_{o1}R_S} \{[r_{o2} + (1+g_{m2}r_{o2})R_E] \parallel [r_{o1} + (1+g_{m1}r_{o1})R_S]\}}
\end{aligned}$$

- (f) We can use the result from part (c) to find  $G_m$  here. If we simply let  $r_{\pi} \rightarrow \infty$  (and obviously we replace the subscripts as appropriate) in the expression for  $G_m$  from part (c), we'll get the result we need here.

$$\begin{aligned}
G_m &= \lim_{r_{\pi 2} \rightarrow \infty} \frac{r_{\pi 2}R_E(2+g_{m2}r_{o2}) - R_E - r_{\pi 2}}{r_{\pi 2}R_E(2+g_{m2}r_{o2}) + r_{o2}R_E + r_{o2}r_{\pi 2}} \\
&= \boxed{\frac{g_{m2}r_{o2}}{r_{o2} + R_E + g_{m2}r_{o2}R_E}} \\
&\approx \frac{g_{m2}}{1+g_{m2}R_E} \text{ (if } r_{o2} \text{ is large)} \\
R_{out} &= [r_{o2} + (1+g_{m2}r_{o2})R_E] \parallel [r_{o1} + (1+g_{m1}r_{o1})R_S] \\
A_v &= \boxed{-\frac{g_{m2}r_{o2}}{r_{o2} + R_E + g_{m2}r_{o2}R_E} \{[r_{o2} + (1+g_{m2}r_{o2})R_E] \parallel [r_{o1} + (1+g_{m1}r_{o1})R_S]\}}
\end{aligned}$$

- (g) Once again, we can use the result from part (c) to find  $G_m$  here (replacing subscripts as appropriate).

$$\begin{aligned}
G_m &= \boxed{\frac{r_{\pi 2}R_E(1+g_{m2}r_{o2}) - R_E - r_{\pi 2}}{r_{\pi 2}R_E(1+g_{m2}r_{o2}) + r_{o2}R_E + r_{o2}r_{\pi 2}}} \\
&\approx \frac{g_{m2}}{1+g_{m2}R_E} \text{ (if } r_{\pi 2}, r_{o2} \text{ are large)} \\
R_{out} &= R_C \parallel [r_{o2} + (1+g_{m2}r_{o2})(r_{\pi 2} \parallel R_E)] \\
A_v &= \boxed{-\frac{r_{\pi 2}R_E(1+g_{m2}r_{o2}) - R_E - r_{\pi 2}}{r_{\pi 2}R_E(1+g_{m2}r_{o2}) + r_{o2}R_E + r_{o2}r_{\pi 2}} \{R_C \parallel [r_{o2} + (1+g_{m2}r_{o2})(r_{\pi 2} \parallel R_E)]\}}
\end{aligned}$$

$$\begin{aligned}
 21. \quad A_v &= -g_{m1} r_{o1} g_{m1} (r_{o1} \parallel r_{\pi 2}) \\
 &= -\frac{I_{c1}}{V_T} \cdot \frac{V_{A1}}{I_{c1}} \cdot \frac{I_{c1}}{V_T} \cdot \frac{1}{\frac{I_{c1}}{V_{A1}} + \frac{I_{c2}}{\beta V_T}}
 \end{aligned}$$

Since  $I_{c1} \approx I_{c2}$ ,

$$A_v \approx -\frac{V_{A1}/V_T^2}{\frac{1}{V_{A1}} + \frac{1}{\beta V_T}} = -\frac{\beta V_A^2}{V_T(V_A + \beta V_T)}$$



9.22

$$A_v = -g_{m1} [r_{o2} + (1 + g_{m2}r_{o2}) (r_{\pi2} \parallel r_{o1})]$$

$$I_{C1} \approx I_{C2} = I_1$$

$$V_{A1} = V_{A2} = V_A$$

$$A_v \approx -\frac{I_1}{V_T} \left[ \frac{V_A}{I_1} + \left( 1 + \frac{V_A}{V_T} \right) \left( \frac{\beta V_T}{I_1} \parallel \frac{V_A}{I_1} \right) \right]$$
$$= -500$$

$$V_{A1} = V_{A2} = \boxed{0.618 \text{ V}^{-1}}$$

9.23 (a) Although the output resistance of this stage is the same as that of a cascode, the transconductance of this stage is lower than that of a cascode stage. A cascode has  $G_m = g_m$ , where as this stage has  $G_m = \frac{g_{m2}}{1+g_{m2}r_{o1}}$ .

(b)

$$\begin{aligned} G_m &= \boxed{\frac{g_{m2}}{1+g_{m2}r_{o1}}} \\ R_{out} &= r_{o2} + (1+g_{m2}r_{o2})(r_{\pi2} \parallel r_{o1}) \\ A_v &= -G_m R_{out} \\ &= \boxed{-\frac{g_{m2}}{1+g_{m2}r_{o1}} [r_{o2} + (1+g_{m2}r_{o2})(r_{\pi2} \parallel r_{o1})]} \end{aligned}$$

9.24

$$G_m = \boxed{-g_{m1}}$$

$$R_{out} = r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi 2} \parallel r_{o1})$$

$$A_v = \boxed{g_{m1} [r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi 2} \parallel r_{o1})]}$$

9.25 (a)

$$\begin{aligned}
 G_m &= g_{m2} \frac{R_P \parallel r_{\pi 1}}{\frac{1}{g_{m1}} + R_P \parallel r_{\pi 1}} \\
 R_{out} &= r_{o1} + (1 + g_{m1} r_{o1}) (r_{\pi 1} \parallel r_{o2} \parallel R_P) \\
 A_v &= \boxed{-g_{m2} \frac{R_P \parallel r_{\pi 1}}{\frac{1}{g_{m1}} + R_P \parallel r_{\pi 1}} [r_{o1} + (1 + g_{m1} r_{o1}) (r_{\pi 1} \parallel r_{o2} \parallel R_P)]}
 \end{aligned}$$

(b)

$$\begin{aligned}
 G_m &= g_{m2} \\
 R_{out} &= r_{o1} \parallel R_P + [1 + g_{m1} (r_{o1} \parallel R_P)] (r_{\pi 1} \parallel r_{o2}) \\
 A_v &= \boxed{-g_{m2} \{r_{o1} \parallel R_P + [1 + g_{m1} (r_{o1} \parallel R_P)] (r_{\pi 1} \parallel r_{o2})\}}
 \end{aligned}$$

(c)

$$\begin{aligned}
 G_m &= \frac{g_{m2}}{1 + g_{m2} R_E} \\
 R_{out} &= r_{o1} + (1 + g_{m1} r_{o1}) [r_{\pi 1} \parallel (r_{o2} + (1 + g_{m2} r_{o2}) (r_{\pi 2} \parallel R_E))] \\
 A_v &= \boxed{-\frac{g_{m2}}{1 + g_{m2} R_E} \{r_{o1} + (1 + g_{m1} r_{o1}) [r_{\pi 1} \parallel (r_{o2} + (1 + g_{m2} r_{o2}) (r_{\pi 2} \parallel R_E))]\}}
 \end{aligned}$$



(d)

$$\begin{aligned}
 G_m &= g_{m2} \\
 R_{out} &= r_{o1} + (1 + g_{m1} r_{o1}) (r_{\pi 1} \parallel r_{o2} \parallel r_{o3}) \\
 A_v &= \boxed{-g_{m2} [r_{o1} + (1 + g_{m1} r_{o1}) (r_{\pi 1} \parallel r_{o2} \parallel r_{o3})]}
 \end{aligned}$$

$$\begin{aligned}
A_v &= -g_{m1} \{ [r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel r_{o1})] \parallel [r_{o3} + (1 + g_{m3}r_{o3})(r_{\pi3} \parallel r_{o4})] \} \\
&= -\frac{I_C}{V_T} \left\{ \left[ \frac{V_{A,N}}{I_C} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \left( \frac{\beta_N V_T}{I_C} \parallel \frac{V_{A,N}}{I_C} \right) \right] \parallel \left[ \frac{V_{A,P}}{I_C} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \left( \frac{\beta_P V_T}{I_C} \parallel \frac{V_{A,P}}{I_C} \right) \right] \right\} \\
&= -\frac{I_C}{V_T} \frac{\left[ \frac{V_{A,N}}{I_C} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \left( \frac{\beta_N V_T}{I_C} \parallel \frac{V_{A,N}}{I_C} \right) \right] \left[ \frac{V_{A,P}}{I_C} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \left( \frac{\beta_P V_T}{I_C} \parallel \frac{V_{A,P}}{I_C} \right) \right]}{\left[ \frac{V_{A,N}}{I_C} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \left( \frac{\beta_N V_T}{I_C} \parallel \frac{V_{A,N}}{I_C} \right) \right] + \left[ \frac{V_{A,P}}{I_C} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \left( \frac{\beta_P V_T}{I_C} \parallel \frac{V_{A,P}}{I_C} \right) \right]} \\
&= -\frac{I_C}{V_T} \frac{\left[ \frac{V_{A,N}}{I_C} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \frac{\beta_N V_T V_{A,N}}{I_C^2 \left( \frac{\beta_N V_T}{I_C} + \frac{V_{A,N}}{I_C} \right)} \right] \left[ \frac{V_{A,P}}{I_C} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \frac{\beta_P V_T V_{A,P}}{I_C^2 \left( \frac{\beta_P V_T}{I_C} + \frac{V_{A,P}}{I_C} \right)} \right]}{\left[ \frac{V_{A,N}}{I_C} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \frac{\beta_N V_T V_{A,N}}{I_C^2 \left( \frac{\beta_N V_T}{I_C} + \frac{V_{A,N}}{I_C} \right)} \right] + \left[ \frac{V_{A,P}}{I_C} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \frac{\beta_P V_T V_{A,P}}{I_C^2 \left( \frac{\beta_P V_T}{I_C} + \frac{V_{A,P}}{I_C} \right)} \right]} \\
&= -\frac{I_C}{V_T} \frac{\frac{1}{I_C^2} \left[ V_{A,N} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \frac{\beta_N V_T V_{A,N}}{\beta_N V_T + V_{A,N}} \right] \left[ V_{A,P} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \frac{\beta_P V_T V_{A,P}}{\beta_P V_T + V_{A,P}} \right]}{\frac{1}{I_C} \left[ V_{A,N} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \frac{\beta_N V_T V_{A,N}}{\beta_N V_T + V_{A,N}} \right] + \frac{1}{I_C} \left[ V_{A,P} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \frac{\beta_P V_T V_{A,P}}{\beta_P V_T + V_{A,P}} \right]} \\
&= -\frac{1}{V_T} \frac{\left[ V_{A,N} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \frac{\beta_N V_T V_{A,N}}{\beta_N V_T + V_{A,N}} \right] \left[ V_{A,P} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \frac{\beta_P V_T V_{A,P}}{\beta_P V_T + V_{A,P}} \right]}{\left[ V_{A,N} + \left( 1 + \frac{V_{A,N}}{V_T} \right) \frac{\beta_N V_T V_{A,N}}{\beta_N V_T + V_{A,N}} \right] + \left[ V_{A,P} + \left( 1 + \frac{V_{A,P}}{V_T} \right) \frac{\beta_P V_T V_{A,P}}{\beta_P V_T + V_{A,P}} \right]}
\end{aligned}$$

The result does not depend on the bias current.

27. Equivalent circuit.

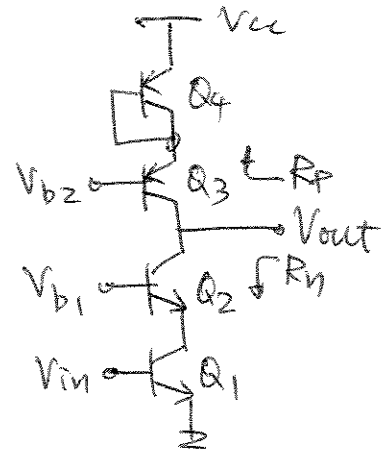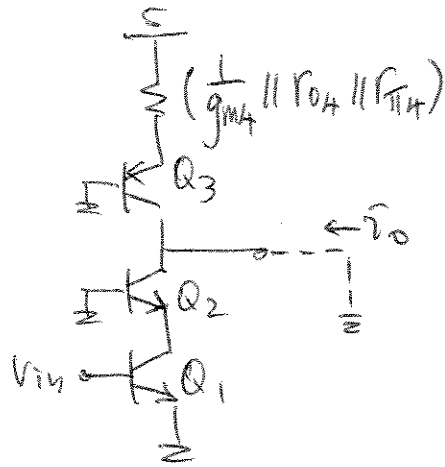

$$G_m = g_{m1} = \frac{\bar{i}_o}{V_{in}} = \frac{\bar{i}_{e1}}{V_{in}}$$


$$R_{out} = R_p \parallel R_n$$

$$R_p = \left[ 1 + g_{m3} \left( \frac{1}{g_{m4}} \parallel r_{o4} \parallel r_{\pi4} \parallel r_{\pi3} \right) \right] r_{o3} + \left[ \frac{1}{g_{m4}} \parallel r_{o4} \parallel r_{\pi4} \parallel r_{\pi3} \right]$$

$$R_n = \left[ 1 + g_{m2} (r_{o1} \parallel r_{\pi2}) \right] r_{o2} + (r_{o1} \parallel r_{\pi2})$$

$$\therefore A_v = -G_m R_{out} = -g_{m1} (R_p \parallel R_n)$$


$$\begin{aligned}
A_v &\approx -g_{m1}g_{m2}r_{o1}r_{o2} \text{ (Eq. 9.69)} \\
&= -\sqrt{2\left(\frac{W}{L}\right)_1 \mu_n C_{ox} I_D} \sqrt{2\left(\frac{W}{L}\right)_2 \mu_n C_{ox} I_D} \left(\frac{1}{\lambda I_D}\right)^2 \\
&= -2\mu_n C_{ox} I_D \sqrt{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2} \left(\frac{1}{\lambda I_D}\right)^2 \\
&= \boxed{-2\mu_n C_{ox} \frac{1}{I_D} \frac{1}{\lambda^2} \sqrt{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2}}
\end{aligned}$$

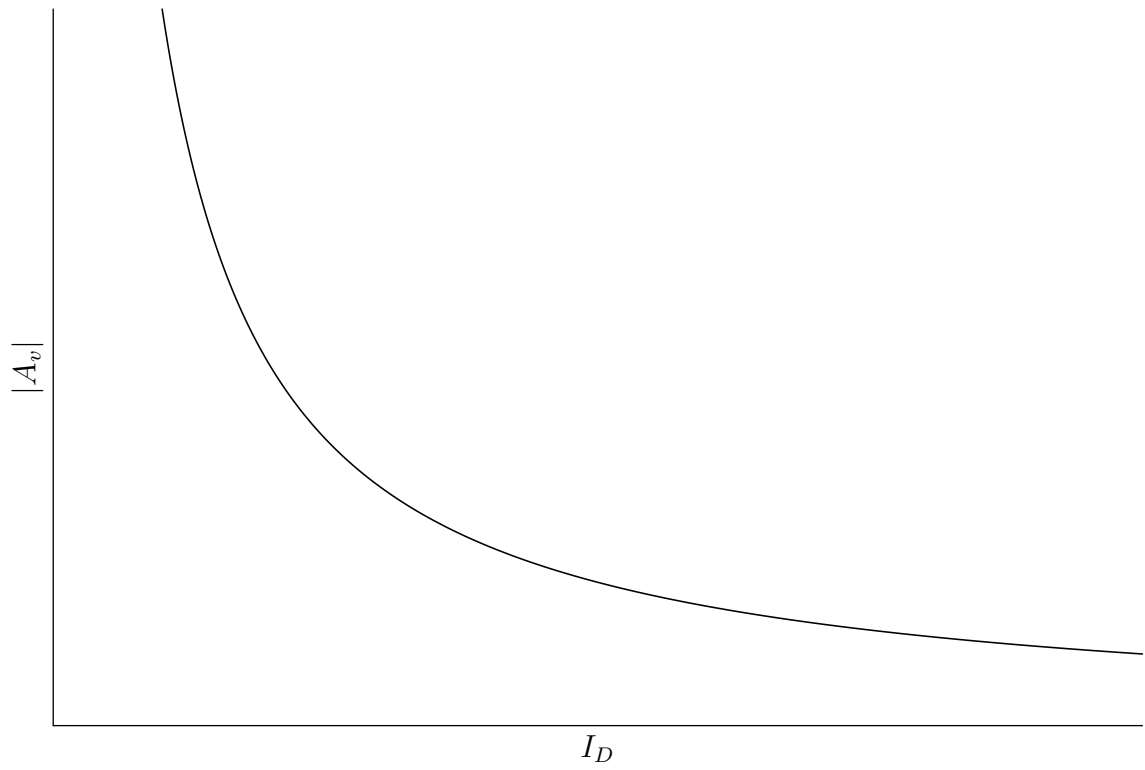

29.  $|A_v| = 200$


$\mu_n C_{ox} = 100 \frac{\mu A}{V^2}$        $\lambda = 0.1 \text{ V}^{-1}$

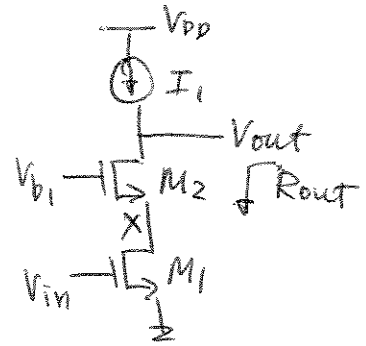Determine  $(\frac{W}{L})_1 = (\frac{W}{L})_2$



$R_{out} = (1 + g_{m2} r_{o1}) r_{o2} + r_{o1}$

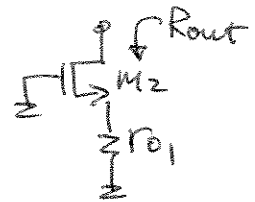$G_m \cong g_{m1}$  (short-circuit current flows through both  $M_1$  &  $M_2$ )



$|A_v| = G_m R_{out} = g_{m1} [(1 + g_{m2} r_{o1}) r_{o2} + r_{o1}]$

$\approx g_{m1} g_{m2} r_{o1} r_{o2} = (g_m r_o)^2 = 200$

( $\because (\frac{W}{L})_1 = (\frac{W}{L})_2$  and  $I_{D1} = I_{D2}$ )

$(g_m r_o)^2 = \left( \frac{2 I_D}{V_{GS} - V_{TH}} \cdot \frac{1}{\lambda I_D} \right)^2 = 200$

$\Rightarrow V_{GS} - V_{TH} = \left( \sqrt{200} \cdot \lambda / 2 \right)^{-1} = \left[ \sqrt{200} \cdot (0.05 \text{ V}^{-1}) \right]^{-1}$   
 $\approx 1.41 \text{ V}$



$$\Rightarrow I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2$$

$$\begin{aligned} \therefore \left(\frac{W}{L}\right) &= \frac{2 I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} \\ &= \frac{2(1 \text{ mA})}{100 \frac{\mu\text{A}}{\text{V}^2} (1.4 \text{ V})^2} \approx 10 \end{aligned}$$

9.30 From Problem 28, we have

$$A_v = -2\mu_n C_{ox} \frac{1}{I_D} \frac{1}{\lambda^2} \sqrt{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2}$$

If we increase the transistor widths by a factor of  $N$ , we will get a new voltage gain  $A'_v$ :

$$\begin{aligned} A'_v &= -2\mu_n C_{ox} \frac{1}{I_D} \frac{1}{\lambda^2} \sqrt{N^2 \left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2} \\ &= -2N\mu_n C_{ox} \frac{1}{I_D} \frac{1}{\lambda^2} \sqrt{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2} \\ &= NA_v \end{aligned}$$

Thus, the gain increases by a factor of  $N$ .

9.31 From Problem 28, we have

$$A_v = -2\mu_n C_{ox} \frac{1}{I_D} \frac{1}{\lambda^2} \sqrt{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2}$$

If we decrease the transistor widths by a factor of  $N$ , we will get a new voltage gain  $A'_v$ :

$$\begin{aligned} A'_v &= -2\mu_n C_{ox} \frac{1}{I_D} \frac{1}{\lambda^2} \sqrt{\frac{1}{N^2} \left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2} \\ &= -2\frac{1}{N}\mu_n C_{ox} \frac{1}{I_D} \frac{1}{\lambda^2} \sqrt{\left(\frac{W}{L}\right)_1 \left(\frac{W}{L}\right)_2} \\ &= \frac{1}{N} A_v \end{aligned}$$

Thus, the gain decreases by a factor of  $N$ .

9.32

$$\begin{aligned}G_m &= -g_{m2} \\R_{out} &= r_{o2} \parallel [r_{o3} + (1 + g_{m3}r_{o3})r_{o4}] \\A_v &= \boxed{g_{m2} \{r_{o2} \parallel [r_{o3} + (1 + g_{m3}r_{o3})r_{o4}]\}}\end{aligned}$$

$$A_v = -g_{m1} \{ [r_{o2} + (1 + g_{m2}r_{o3}) r_{o1}] \parallel [r_{o3} + (1 + g_{m3}r_{o3}) r_{o4}] \}$$

$$= -500$$

$$g_{m1} = g_{m2} = \sqrt{2 \left( \frac{W}{L} \right) \mu_n C_{ox} I_D}$$

$$g_{m3} = g_{m4} = \sqrt{2 \left( \frac{W}{L} \right) \mu_p C_{ox} I_D}$$

$$r_{o1} = r_{o1} = \frac{1}{\lambda_n I_D}$$

$$r_{o3} = r_{o4} = \frac{1}{\lambda_p I_D}$$

$$I_D = \boxed{1.15 \text{ mA}}$$

9.34 (a)

$$\begin{aligned}
 G_m &= g_{m1} \\
 R_{out} &= [(r_{o2} \parallel R_P) + (1 + g_{m2}(r_{o2} \parallel R_P))r_{o1}] \parallel [r_{o3} + (1 + g_{m3}r_{o3})r_{o4}] \\
 A_v &= \boxed{-g_{m1} \{[(r_{o2} \parallel R_P) + (1 + g_{m2}(r_{o2} \parallel R_P))r_{o1}] \parallel [r_{o3} + (1 + g_{m3}r_{o3})r_{o4}]\}}
 \end{aligned}$$

(b)

$$\begin{aligned}
 G_m &= g_{m1} \frac{r_{o1} \parallel R_P}{\frac{1}{g_{m2}} + r_{o1} \parallel R_P} \\
 R_{out} &= [r_{o2} + (1 + g_{m2}r_{o2})(r_{o1} \parallel R_P)] \parallel [r_{o3} + (1 + g_{m3}r_{o3})r_{o4}] \\
 A_v &= \boxed{-g_{m1} \frac{r_{o1} \parallel R_P}{\frac{1}{g_{m2}} + r_{o1} \parallel R_P} \{[r_{o2} + (1 + g_{m2}r_{o2})(r_{o1} \parallel R_P)] \parallel [r_{o3} + (1 + g_{m3}r_{o3})r_{o4}]\}}
 \end{aligned}$$

(c)

$$\begin{aligned}
 G_m &= g_{m5} \\
 R_{out} &= [r_{o2} + (1 + g_{m2}r_{o2})(r_{o1} \parallel r_{o5})] \parallel [r_{o3} + (1 + g_{m3}r_{o3})r_{o4}] \\
 A_v &= \boxed{-g_{m5} \{[r_{o2} + (1 + g_{m2}r_{o2})(r_{o1} \parallel r_{o5})] \parallel [r_{o3} + (1 + g_{m3}r_{o3})r_{o4}]\}}
 \end{aligned}$$

(d)

$$\begin{aligned}
 G_m &= g_{m5} \\
 R_{out} &= [r_{o2} + (1 + g_{m2}r_{o2})r_{o1}] \parallel [r_{o3} + (1 + g_{m3}r_{o3})(r_{o4} \parallel r_{o5})] \\
 A_v &= \boxed{-g_{m5} \{[r_{o2} + (1 + g_{m2}r_{o2})r_{o1}] \parallel [r_{o3} + (1 + g_{m3}r_{o3})(r_{o4} \parallel r_{o5})]\}}
 \end{aligned}$$

$$35. \quad \frac{R_2}{R_1 + R_2} V_{CC} = V_T \ln \left( \frac{I_1}{I_S} \right)$$

$$\Rightarrow I_1 = I_S \cdot \exp \left[ \frac{V_{CC}}{V_T} \cdot \frac{R_2}{R_1 + R_2} \right]$$

$$\begin{aligned} \frac{\partial I_1}{\partial V_{CC}} &= \frac{I_S}{V_T} \cdot \frac{R_2}{R_1 + R_2} \cdot \exp \left[ \frac{V_{CC}}{V_T} \cdot \frac{R_2}{R_1 + R_2} \right] \\ &= \frac{I_1}{V_T} \cdot \frac{R_2}{R_1 + R_2} = g_m \left( \frac{R_2}{R_1 + R_2} \right) \end{aligned}$$

Intuitively, we know that an exponential relationship exists between  $I_C$  &  $V_{BE}$ . Its transconductance is also a function (linear) of  $I_C$ . Since  $V_{BE}$  comes from a voltage divider (which is also linear), we expect a linear relationship between  $I_C$  &  $V_{CC}$ .

$$\begin{aligned}
 I_1 &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2 \quad (\text{Eq. 9.85}) \\
 \frac{\partial I_1}{\partial V_{DD}} &= \frac{W}{L} \mu_n C_{ox} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right) \frac{R_2}{R_1 + R_2} \\
 &= \boxed{\frac{R_2}{R_1 + R_2} g_m}
 \end{aligned}$$

Intuitively, we know that  $g_m$  is the derivative of  $I_1$  with respect to  $V_{GS}$ , or  $g_m = \frac{\partial I_1}{\partial V_{GS}}$ . Since  $V_{GS}$  is linearly dependent on  $V_{DD}$  by the relationship established by the voltage divider (meaning  $\frac{\partial V_{GS}}{\partial V_{DD}}$  is a constant), we'd expect  $\frac{\partial I_1}{\partial V_{DD}}$  to also be proportional to  $g_m$ , since  $\frac{\partial I_1}{\partial V_{DD}} = \frac{\partial V_{GS}}{\partial V_{DD}} \cdot \frac{\partial I_1}{\partial V_{GS}} = \frac{\partial V_{GS}}{\partial V_{DD}} g_m$ .



$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)^2 \quad (\text{Eq. 9.85})$$

$$\frac{\partial I_1}{\partial V_{TH}} = \boxed{-\mu_n C_{ox} \frac{W}{L} \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_{TH} \right)}$$

The sensitivity of  $I_1$  to  $V_{TH}$  becomes a more serious issue at low supply voltages because as  $V_{DD}$  becomes smaller with respect to  $V_{TH}$ ,  $V_{TH}$  has more control over the sensitivity. When  $V_{DD}$  is large enough, it dominates the last term of the expression, reducing the control of  $V_{TH}$  over the sensitivity.

9.38 As long as  $V_{REF} > 0$ , the circuit operates in negative feedback, so that  $V_+ = V_- = 0$  V.

$$I_{C1} = I_{S1}e^{-V_1/V_T} = \frac{V_{REF}}{R_1}$$
$$V_1 = -V_T \ln\left(\frac{V_{REF}}{R_1 I_{S1}}\right) = V_{BE2}$$

If  $V_{REF} > R_1 I_{S1}$ , then we have  $V_{BE2} < 0$ , and  $I_X = 0$ . If  $V_{REF} < R_1 I_{S1}$ , then we have:

$$I_X = I_{S2}e^{-V_T \ln\left(\frac{V_{REF}}{R_1 I_{S1}}\right)/V_T}$$
$$= I_{S2}e^{-\ln\left(\frac{V_{REF}}{R_1 I_{S1}}\right)}$$
$$= I_{S2} \frac{R_1 I_{S1}}{V_{REF}}$$

Thus, if  $V_{REF} > R_1 I_{S1}$  (which will typically be true, since  $I_{S1}$  is typically very small), then we get no output, i.e.,  $I_X = 0$ . When  $V_{REF} < R_1 I_{S1}$ , we get an inverse relationship between  $I_X$  and  $V_{REF}$ .

9.39 As long as  $V_{REF} > 0$ , the circuit operates in negative feedback, so that  $V_+ = V_- = 0$  V.

$$I_{C1} = I_{S1} e^{-V_1/V_T} = \frac{V_{REF}}{R_1}$$

$$V_1 = -V_T \ln \left( \frac{V_{REF}}{R_1 I_{S1}} \right) = -V_{BE2}$$

If  $V_{REF} < R_1 I_{S1}$ , then we have  $V_{BE2} < 0$ , and  $I_X = 0$ . If  $V_{REF} > R_1 I_{S1}$ , then we have:

$$I_X = I_{S2} e^{V_T \ln \left( \frac{V_{REF}}{R_1 I_{S1}} \right) / V_T}$$


$$= I_{S2} \frac{V_{REF}}{R_1 I_{S1}}$$

$$= \frac{I_{S2}}{I_{S1}} \frac{V_{REF}}{R_1}$$

$$= \frac{I_{S2}}{I_{S1}} I_{C1}$$

Thus, if  $V_{REF} < R_1 I_{S1}$ , then we get no output, i.e.,  $I_X = 0$ . When  $V_{REF} > R_1 I_{S1}$  (which will typically be true, since  $I_{S1}$  is typically very small), we get a current mirror relationship between  $Q_1$  and  $Q_2$  (with  $I_X$  copying  $I_{C1}$ ), where the reference current for  $Q_1$  is  $\frac{V_{REF}}{R_1}$  (ensured by the op-amp).

40.

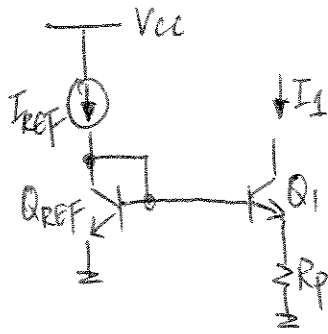

$$Q_{REF} = Q_1$$

$$\beta \rightarrow \infty$$

$$I_1 = \frac{I_{REF}}{2}$$


By KVL,  $V_{BE,REF} = V_{BE_1} + I_1 R_p$

$$\Rightarrow V_T \ln\left(\frac{I_{REF}}{I_{S,REF}}\right) = V_T \ln\left(\frac{I_{REF}/2}{I_{S,1}}\right) + \frac{I_{REF} R_p}{2}$$

$$V_T \ln(2) = \frac{I_{REF} R_p}{2}$$

$$R_p = 2 \cdot \ln(2) \cdot (V_T / I_{REF})$$

41.

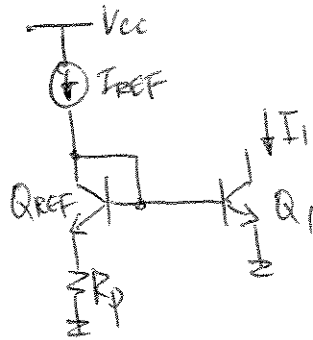

$$Q_{REF} = Q_1$$

$$\beta \rightarrow \infty$$


By KVL,  $V_{BE,REF} + I_{REF} R_P = V_{BE,1}$

$$\Rightarrow V_T \ln \left( \frac{I_{REF}}{I_{S,REF}} \right) + I_{REF} R_P = V_T \ln \left( \frac{2 I_{REF}}{I_{S,1}} \right)$$

$$I_{REF} R_P = V_T \ln(2)$$

$$R_P = \frac{V_T \ln(2)}{I_{REF}}$$


42.

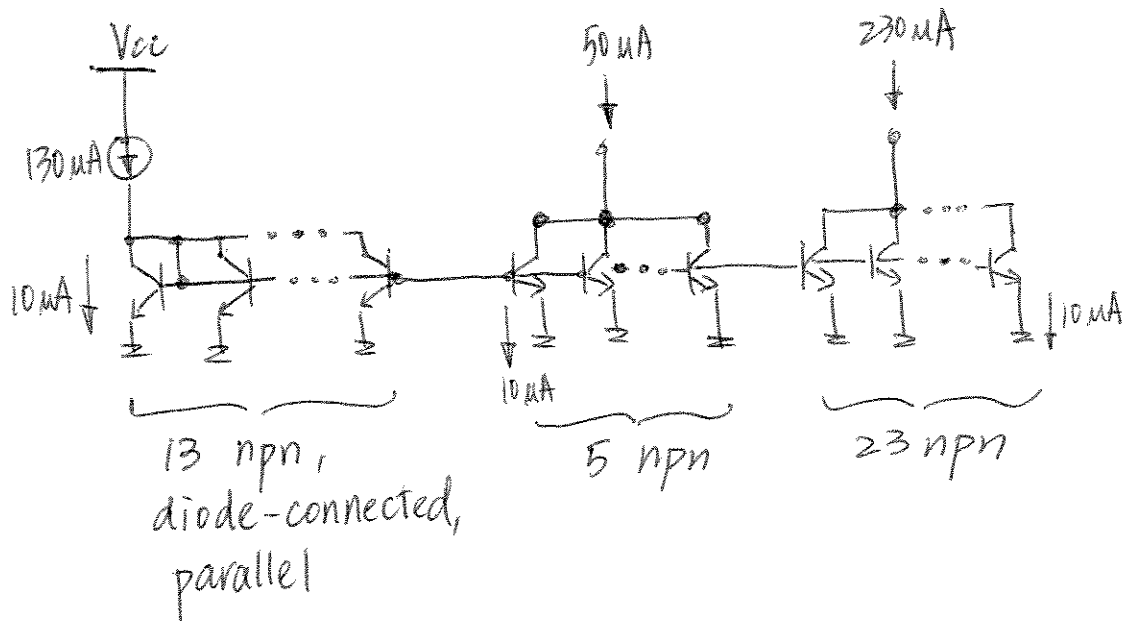


All the bases are the same node.

If the area of BJT is flexible, the 5-npn group can be replaced by one BJT that is 5 times as big in area. Similar concept applies to 23-npn grouping.

43.

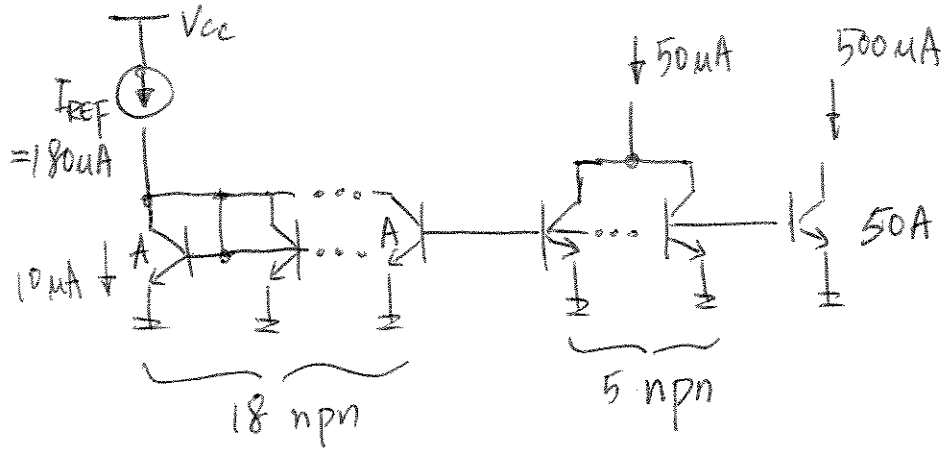

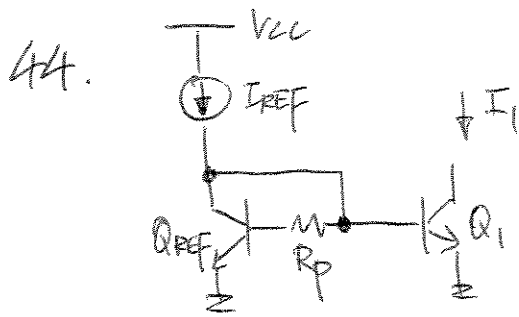

$$Q_{REF} = Q_1$$

$I_1$  10% larger. ( $I_1 = 1.1 I_{C,REF}$ )  
Solve for  $R_P$ .

By KVL,

$$V_{BE,REF} + \frac{I_{C,REF} \cdot R_P}{\beta} = V_{BE,1}$$

$$\Rightarrow V_T \ln\left(\frac{I_1}{I_S}\right) - V_T \ln\left(\frac{I_{C,REF}}{I_S}\right) = \frac{I_{C,REF}}{\beta} \cdot R_P$$

$$V_T \ln\left(\frac{I_1}{I_{C,REF}}\right) = \frac{I_{C,REF}}{\beta} \cdot R_P$$

$$\Rightarrow V_T \ln(1.1) = \frac{I_{C,REF}}{\beta} R_P \quad \Rightarrow \quad I_{C,REF} = \frac{\beta V_T \ln(1.1)}{R_P}$$


By KCL,  $I_{REF} = I_{C,REF} + I_{C,REF}/\beta + I_1/\beta$

$$= \frac{\beta V_T \ln(1.1)}{R_P} \cdot \left(1 + \frac{1}{\beta}\right) + \frac{I_1}{\beta}$$

$$\therefore R_P = \frac{(\beta + 1) V_T \ln(1.1)}{I_{REF} - I_1/\beta}$$



45.

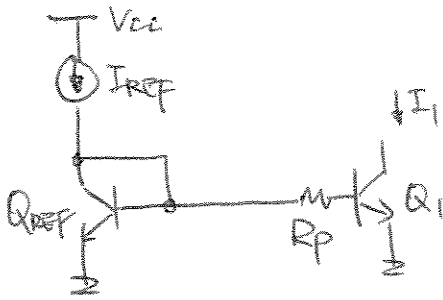

$$I_1 = 0.9 I_{C,REF}$$

By KVL,  $V_{BE,REF} = \frac{I_1}{\beta} R_P + V_{BE,1}$

$$\Rightarrow V_T \ln\left(\frac{I_{B,REF}}{I_1}\right) = \frac{I_1}{\beta} R_P$$

$$V_T \ln\left(\frac{1}{0.9}\right) = 0.9 I_{C,REF} \frac{R_P}{\beta}$$

$$\Rightarrow I_{C,REF} = \frac{\beta}{0.9 R_P} V_T \ln\left(\frac{1}{0.9}\right)$$

By KCL,

$$I_{REF} = I_{C,REF} + I_{C,REF}/\beta + I_1/\beta$$

$$\therefore I_{REF} - \frac{I_1}{\beta} = \frac{\beta}{0.9 R_P} V_T \ln\left(\frac{1}{0.9}\right) \left(1 + \frac{1}{\beta}\right)$$

$$\Rightarrow R_P = \frac{(\beta + 1) V_T \ln(10/9)}{0.9 (I_{REF} - I_1/\beta)}$$

9.46 (a)

$$\begin{aligned}I_{copy} &= 5I_{C,REF} \\I_{REF} &= I_{C,REF} + I_{B,REF} + I_{B1} \\&= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{copy}}{\beta} \\&= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{5I_{C,REF}}{\beta} \\&= I_{C,REF} \left( 1 + \frac{1}{\beta} + \frac{5}{\beta} \right) \\&= \frac{I_{copy}}{5} \left( \frac{6 + \beta}{\beta} \right) \\I_{copy} &= \boxed{\left( \frac{\beta}{6 + \beta} \right) 5I_{REF}}\end{aligned}$$

(b)

$$\begin{aligned}I_{copy} &= \frac{I_{C,REF}}{5} \\I_{REF} &= I_{C,REF} + I_{B,REF} + I_{B1} \\&= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{copy}}{\beta} \\&= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{C,REF}}{5\beta} \\&= I_{C,REF} \left( 1 + \frac{1}{\beta} + \frac{1}{5\beta} \right) \\&= 5I_{copy} \left( \frac{6 + 5\beta}{5\beta} \right) \\I_{copy} &= \boxed{\left( \frac{5\beta}{6 + 5\beta} \right) \frac{I_{REF}}{5}}\end{aligned}$$

(c)

$$I_{copy} = \frac{3}{2}I_{C,REF}$$

$$I_2 = \frac{5}{2}I_{C,REF}$$

$$I_{REF} = I_{C,REF} + I_{B,REF} + I_{B1} + I_{B2}$$

$$= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{copy}}{\beta} + \frac{I_2}{\beta}$$


$$= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{3I_{C,REF}}{2\beta} + \frac{5I_{C,REF}}{2\beta}$$

$$= I_{C,REF} \left( 1 + \frac{1}{\beta} + \frac{3}{2\beta} + \frac{5}{2\beta} \right)$$

$$= \frac{2}{3}I_{copy} \left( \frac{10 + 2\beta}{2\beta} \right)$$

$$I_{copy} = \boxed{\left( \frac{2\beta}{10 + 2\beta} \right) \frac{3}{2}I_{REF}}$$

47.

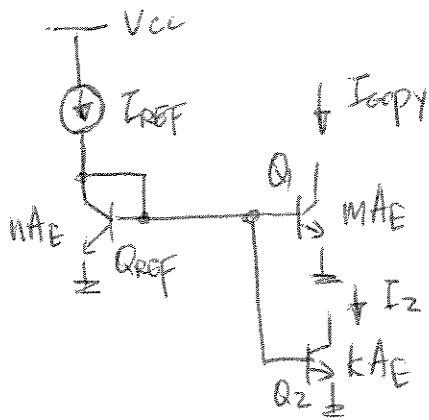


By observing the areas of the BJTs,

$$I_{C,REF} = \left(\frac{n}{m}\right) I_{COPY} = \left(\frac{n}{k}\right) I_2$$

By KCL, 
$$I_{C,REF} = I_{REF} - \frac{I_{C,REF}}{\beta} - \frac{I_{COPY}}{\beta} - \frac{I_2}{\beta}$$

$$\Rightarrow \frac{n}{m} I_{COPY} = I_{REF} - \frac{\left(\frac{n}{m}\right) I_{COPY}}{\beta} - \frac{I_{COPY}}{\beta} - \frac{\left(\frac{k}{m}\right) I_{COPY}}{\beta}$$
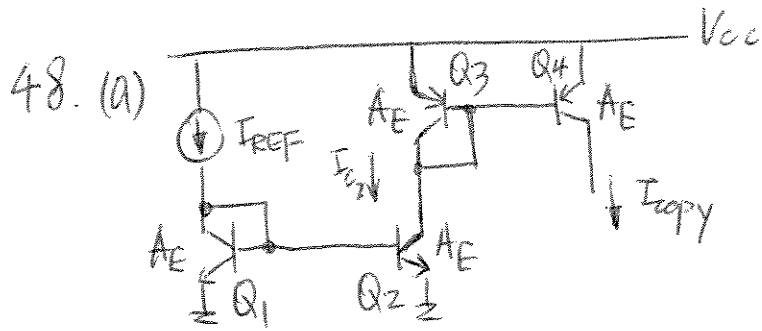
$$\therefore I_{COPY} = I_{REF} \left[ \frac{\beta m}{(\beta+1)n + k + m} \right]$$



$$V_{BE1} = V_{BE2}$$

$$\Rightarrow I_{C1} = I_{C2}$$

$$V_{BE3} = V_{BE4}$$

$$\Rightarrow I_{C3} = I_{C4}$$

First compute  $I_{C1,2}$ :

$$I_{C1} = I_{REF} - \frac{I_{C1}}{\beta} - \frac{I_{C2}}{\beta} \Rightarrow I_{C2} = \frac{\beta}{\beta+2} \cdot I_{REF}$$


View  $I_{C2}$  as the "I<sub>REF</sub>" for the Q<sub>3</sub>-Q<sub>4</sub> current mirror and apply the equation derived.

$$\Rightarrow I_{copy} = \frac{\beta}{\beta+2} \left[ \frac{\beta}{\beta+2} \cdot I_{REF} \right] = I_{REF} \left( \frac{\beta}{\beta+2} \right)^2$$

$$\begin{aligned}
V_{GS,REF} &= V_{TH} + \sqrt{\frac{2I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} \\
V_{GS1} &= V_{GS,REF} - I_1 R_P \\
&= V_{TH} + \sqrt{\frac{2I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} - I_1 R_P \\
&= V_{TH} + \sqrt{\frac{2I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} - \frac{I_{REF}}{2} R_P \\
I_1 &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left( \sqrt{\frac{2I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} - \frac{I_{REF}}{2} R_P \right)^2 \\
&= \frac{I_{REF}}{2} \\
\sqrt{\frac{2I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} - \frac{I_{REF}}{2} R_P &= \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} \\
\frac{I_{REF}}{2} R_P &= \sqrt{\frac{2I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} - \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} \\
&= (\sqrt{2} - 1) \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \frac{W}{L}}} \\
R_P &= \boxed{\frac{2(\sqrt{2} - 1)}{\sqrt{I_{REF} \mu_n C_{ox} \frac{W}{L}}}}
\end{aligned}$$

Given this choice of  $R_P$ ,  $I_1$  does not change if the threshold voltages of the transistors change by the same amount  $\Delta V$ . Looking at the expression for  $I_1$  in the derivation above, we can see that it has no dependence on  $V_{TH}$  (note that  $R_P$  does not depend on  $V_{TH}$  either).

50.

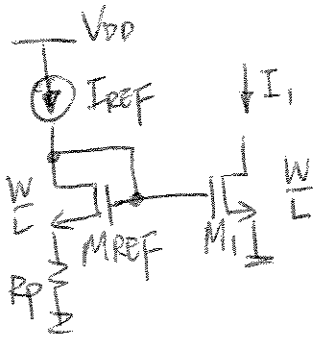

Determine  $R_p$  such that  $I_1 = 2I_{REF}$ .

First calculate  $V_{GS1}$ :

$$V_{GS1} = \sqrt{\frac{2I_1}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{TH} = 2 \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} + V_{TH} \quad \text{--- (1)}$$

Assuming  $I_1$  is in saturation:

$$\begin{aligned} I_{REF} &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS, REF} - V_{TH})^2 \\ &= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) [V_{GS1} - I_{REF} R_p - V_{TH}]^2 \end{aligned}$$


Substitute (1) into  $I_{REF}$ :

$$I_{REF} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[ 2 \sqrt{\frac{I_{REF}}{\mu_n C_{ox} \left(\frac{W}{L}\right)}} - I_{REF} R_p \right]^2 \quad \text{--- (2)}$$

$$\text{Solve for } R_p: \quad R_p = \frac{(2 - \sqrt{2})}{\sqrt{I_{REF}} \cdot \mu_n C_{ox} \left(\frac{W}{L}\right)}$$

From (2), we find that  $R_p$  is independent of any change in  $V_{TH}, \Delta V$  !!

51.

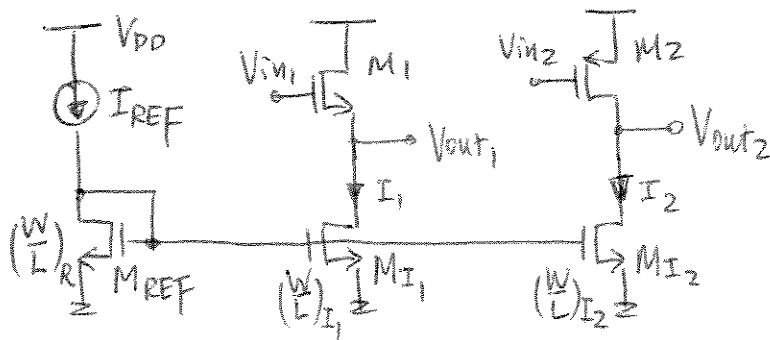

This figure implies that  $V_{GS, REF} = V_{GS, I_1} = V_{GS, I_2}$ .  
 Assuming all devices operate in saturation, with  $(V_{GS} - V_{TH})$  fixed,  $I_D \propto (\frac{W}{L})$


$$\Rightarrow \text{we have } (\frac{W}{L})_R = 7 (\frac{W}{L})$$

$$(\frac{W}{L})_{I_1} = 4 (\frac{W}{L})$$

$$(\frac{W}{L})_{I_2} = 10 (\frac{W}{L})$$



52. (a)

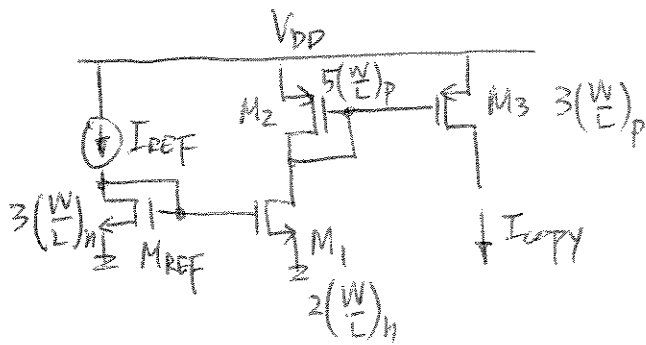


$$V_{GS, REF} = V_{GS, 1} \quad \Rightarrow \quad I_{D, 1} = \frac{2}{3} I_{REF}$$

$$V_{GS, 2} = V_{GS, 3} \quad \Rightarrow \quad I_{COPY} = \frac{3}{5} I_{D, 2} = \frac{3}{5} I_{D, 1}$$

$$= \frac{3}{5} \cdot \left( \frac{2}{3} I_{REF} \right) = \frac{2}{5} I_{REF}$$

(b)

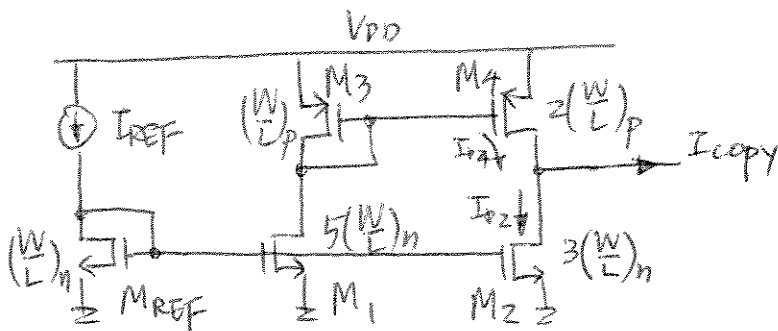


$$V_{GS, REF} = V_{GS, 1} \quad \Rightarrow \quad I_{D, 1} = 5 I_{REF}$$

$$V_{GS, 3} = V_{GS, 4} \quad \Rightarrow \quad I_{D, 4} = 2 I_{D, 3} = 2 I_{D, 1} = 10 I_{REF}$$

$$V_{GS, REF} = V_{GS, 2} \quad \Rightarrow \quad I_{D, 2} = 3 I_{REF}$$

$$\therefore I_{COPY} = I_{D, 4} - I_{D, 2} = 7 I_{REF}$$

53.

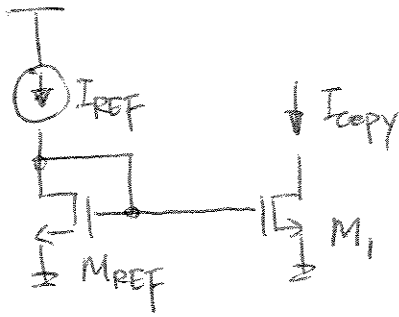

$$V_{GS, REF} = V_{GS, 1} = V_{GS}$$

$$\lambda \neq 0$$

$$(a) \quad I_{REF} = \frac{1}{2} \mu_n C_{OX} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS})$$

$$I_{COPY} = \frac{1}{2} \mu_n C_{OX} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS, 1})$$

$$\text{For } I_{REF} = I_{COPY} \Rightarrow V_{DS, 1} = V_{GS}$$


$$(b) \quad \frac{I_{REF}}{I_{COPY}} = \frac{1 + \lambda V_{GS}}{1 + \lambda (V_{GS} - V_{TH})}$$

$$\Rightarrow I_{COPY} = I_{REF} \left( 1 - \frac{\lambda V_{TH}}{1 + \lambda V_{GS}} \right)$$

$$\begin{aligned}I_{C1} &= 1 \text{ mA} \\I_{E1}R_E &= \frac{1 + \beta_n}{\beta_n} I_{C1}R_E = 0.5 \text{ V} \\R_E &= 0.5 \text{ V} \\R_E &= \boxed{495.05 \Omega} \\R_{out,a} &= r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi1} \parallel R_E) \\&= 85.49 \text{ k}\Omega \\R_{out,b} &= r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi1} \parallel r_{o2}) \\&= 334.53 \text{ k}\Omega\end{aligned}$$

The output impedance of the circuit in Fig. 9.72(b) is significantly larger than the output impedance of the circuit in Fig. 9.72(a) (by a factor of about 4).

55.

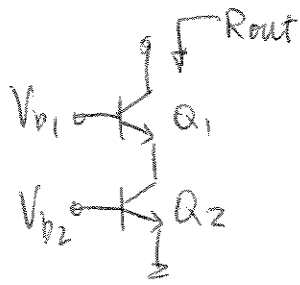

$$I_{BIAS} = 1 \text{ mA}$$

$$\beta = 100$$

Given  $R_{out} = 50 \text{ k}\Omega$ ,  $V_{BC2} = 100 \text{ mV}$ ,  
determine  $V_{b1}$ .

$$R_{out} = [1 + g_{m1} (r_{o2} \parallel r_{\pi 1})] r_{o1} + (r_{o2} \parallel r_{\pi 1})$$

$$\approx g_{m1} (r_{o2} \parallel r_{\pi 1}) r_{o1}$$

$$= \frac{\beta V_A^2}{(V_A + \beta V_T) I_{BIAS}}$$

$$\Rightarrow I_{BIAS} = \left[ \frac{R_{out} (V_A + \beta V_T)}{\beta V_A^2} \right]^{-1} = \left[ \frac{(50 \text{ k}\Omega) (5 \text{ V} + 100 \cdot 0.026 \text{ V})}{100 (5 \text{ V})^2} \right]^{-1}$$

$$\approx 6.6 \text{ mA}$$

$$V_{b2} = V_{BE2} = V_T \ln \left( \frac{I_{BIAS}}{I_S} \right) = (0.026 \text{ V}) \ln \left( \frac{6.6 \text{ mA}}{6 \cdot 10^{-16} \text{ A}} \right)$$

$$\approx 0.78 \text{ V}$$

$$\Rightarrow V_{C2} = V_{BE2} - 100 \text{ mV} = 0.68 \text{ V}$$

$$\therefore V_{b1} = V_{C2} + V_{BE1} = V_{C2} + V_T \ln \left( \frac{I_{BIAS}}{I_S} \right)$$

$$= 0.68 \text{ V} + (0.026 \text{ V}) \ln \left( \frac{6.6 \text{ mA}}{6 \cdot 10^{-16} \text{ A}} \right) \approx 1.46 \text{ V}$$

9.56 (a)

$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1})r_{o2} = 200 \text{ k}\Omega$$

$$r_{o1} = r_{o2} = \frac{1}{\lambda I_D}$$

$$g_{m1} = g_{m2} = \sqrt{2 \frac{W}{L} \mu_n C_{ox} I_D}$$

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = \boxed{1.6}$$

(b)

$$\begin{aligned} V_{b2} = V_{GS2} &= V_{TH} + \sqrt{\frac{2I_D}{\frac{W}{L} \mu_n C_{ox}}} \\ &= \boxed{2.9 \text{ V}} \end{aligned}$$

9.57 (a) Assume  $I_{C1} \approx I_{C2}$ , since  $\beta \gg 1$ .

$$\begin{aligned}
 A_v &= -g_{m1} [r_{o2} + (1 + g_{m2}r_{o2}) (r_{\pi2} \parallel r_{o1})] \\
 g_{m1} = g_{m2} &= \frac{I_1}{V_T} \\
 r_{o1} = r_{o2} &= \frac{V_A}{I_1} \\
 r_{\pi1} = r_{\pi2} &= \beta \frac{V_T}{I_1} \\
 A_v &= -\frac{I_1}{V_T} \left[ \frac{V_A}{I_1} + \left( 1 + \frac{V_A}{V_T} \right) \frac{\beta \frac{V_T}{I_1} \frac{V_A}{I_1}}{\beta \frac{V_T}{I_1} + \frac{V_A}{I_1}} \right] \\
 &= -\frac{1}{V_T} \left[ V_A + \left( 1 + \frac{V_A}{V_T} \right) \frac{\beta V_T V_A}{\beta V_T + V_A} \right] \\
 &= -500 \\
 V_A &= \boxed{0.618 \text{ V}}
 \end{aligned}$$

(b)

$$\begin{aligned}
 V_{in} = V_{BE1} &= V_T \ln \left( \frac{I_1}{I_{S1}} \right) \\
 &= \boxed{714 \text{ mV}}
 \end{aligned}$$

(c)

$$\begin{aligned}
 V_{b1} &= V_{BE2} + V_{CE1} \\
 &= V_{BE2} + 500 \text{ mV} \\
 &= V_T \ln \left( \frac{I_1}{I_{S2}} \right) + 500 \text{ mV} \\
 &= \boxed{1.214 \text{ V}}
 \end{aligned}$$

9.58 Assume all of the collector currents are the same, since  $\beta \gg 1$ .

$$P = I_C V_{CC} = 2 \text{ mW}$$

$$I_C = 0.8 \text{ mA}$$

$$V_{in} = V_T \ln \left( \frac{I_C}{I_S} \right) = \boxed{726 \text{ mV}}$$


$$\begin{aligned} V_{b1} &= V_{BE2} + V_{CE1} \\ &= V_T \ln \left( \frac{I_C}{I_S} \right) + V_{BE1} - V_{BC1} \\ &= \boxed{1.252 \text{ V}} \end{aligned}$$

$$V_{b3} = V_{CC} - V_T \ln \left( \frac{I_C}{I_S} \right) = \boxed{1.774 \text{ V}}$$

$$\begin{aligned} V_{b2} &= V_{CC} - V_{EC4} - V_{EB3} \\ &= V_{CC} - (V_{EB4} - V_{CB4}) - V_T \ln \left( \frac{I_C}{I_S} \right) \\ &= \boxed{1.248 \text{ V}} \end{aligned}$$

$$\begin{aligned} A_v &= -g_{m1} \{ [r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel r_{o1})] \parallel [r_{o3} + (1 + g_{m3}r_{o3})(r_{\pi3} \parallel r_{o4})] \} \\ &= \boxed{4887} \end{aligned}$$

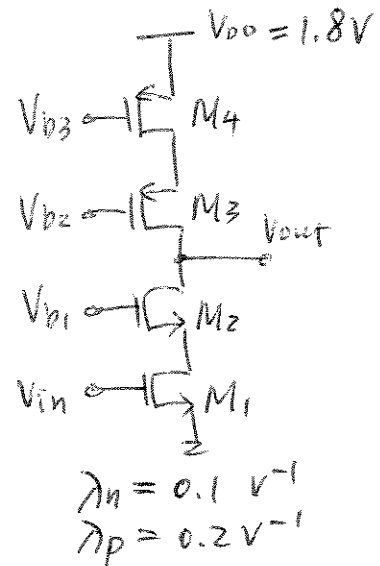59. Given  $A_v = 200$   
 power budget = 2mW  
 all  $(\frac{W}{L}) = \frac{20}{0.18}$   
 $V_{b1} = V_{b2} = 0.9V$



calculate  $V_{in}$  &  $V_{b3}$

$$A_v \approx -g_{m1} (g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4}) = 200$$

$$\text{power} = V_{DD} \times I_{BIAS} \Rightarrow I_{BIAS} = \frac{\text{power}}{V_{DD}} = \frac{2\text{mW}}{1.8V} \approx 1.11\text{mA}$$

$$g_{m2} r_{o1} r_{o2} = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right) I_{BIAS} \left(\frac{1}{\lambda_n I_{BIAS}}\right)^2}$$

$$= \sqrt{2 \cdot 100\text{MA} \cdot \frac{20}{0.18} \cdot 1.11\text{mA} \cdot \left[\frac{1}{(0.1\text{V}^{-1})(1.11\text{mA})}\right]^2}$$

$$\approx 403\text{K}\Omega$$

$$g_{m3} r_{o3} r_{o4} \approx 71\text{K}\Omega$$

We know that  $\frac{|A_v|}{(g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4})} = g_{m1} = \frac{2I_D}{V_{GS1} - V_{TH}}$

$$\therefore V_{in} = V_{GS1} = V_{TH} + \frac{2I_D \cdot (g_{m2} r_{o1} r_{o2} \parallel g_{m3} r_{o3} r_{o4})}{A_v}$$



$$= (0.4 \text{ V}) + 2(1.11 \text{ mA}) \frac{(403 \text{ k}\Omega \parallel 71. \text{ k}\Omega)}{200}$$

$$\approx 1.07 \text{ V}$$


$$g_{m4} = \frac{2I_D}{V_{DD} - V_{D3} - |V_{THP}|} = \sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D}$$

$$\therefore V_{D3} = V_{DD} - |V_{THP}| - \frac{2I_D}{\sqrt{2 \mu_p C_{ox} \frac{W}{L} I_D}}$$

$$= (1.8 \text{ V}) - (0.5 \text{ V}) - \frac{2(1.11 \text{ mA})}{\sqrt{2 \cdot (50 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{20}{0.18}\right) (1.11 \text{ mA})}}$$

$$\approx 0.67 \text{ V}$$

60.

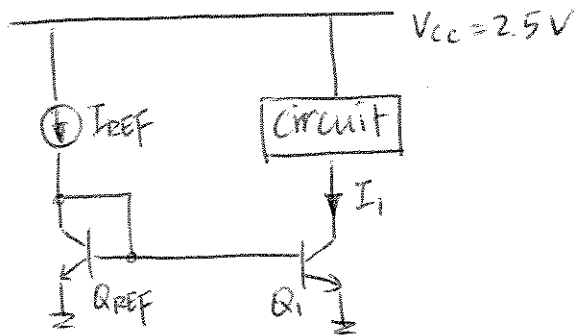

$$I_1 = 0.5 \text{ mA}$$

$$\text{power} = 2 \text{ mW}$$


$$\text{Power} = V_{CC} (I_{REF} + I_1)$$

$$\Rightarrow I_{REF} = \frac{\text{Power}}{V_{CC}} - I_1 = \frac{2 \text{ mW}}{2.5 \text{ V}} - 0.5 \text{ mA} = 0.3 \text{ mA}$$

Therefore, if  $Q_{REF}$  has area  $A_E$ , then  $Q_1$  has area  $\frac{5}{3} A_E$  for the currents specified.

$$\text{i.e. } \frac{A_{REF}}{A_1} = \frac{3}{5}$$

61.

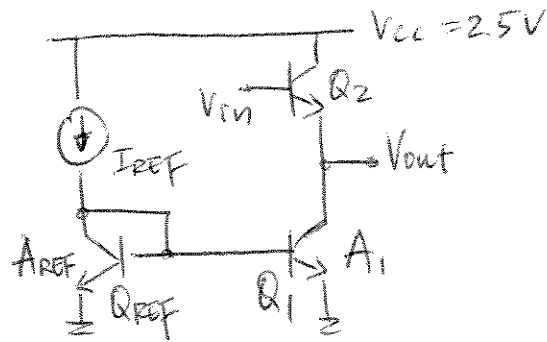

$$\text{power} = 3\text{mW}$$

$$R_{out} = 50\Omega$$

For an emitter follower,  $R_{out} = r_{\pi 2} \parallel \frac{1}{g_{m2}}$

$$\Rightarrow R_{out} = 50\Omega = \frac{1}{\frac{I_{c2}}{V_T} \left(1 + \frac{1}{\beta}\right)}$$

$$\therefore I_{c2} = \frac{V_T}{R_{out}} \cdot \frac{1}{1 + 1/\beta} = \frac{0.026}{50} \cdot \frac{1}{1 + 0.01} \approx 0.51\text{mA}$$

Realize that  $V_{cc}$  is providing current through  $I_{REF}$  &  $I_{c2}$ , and we are given

$$\text{power} = V_{cc} (I_{REF} + I_{c2}) = 3\text{mW}$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{cc}} - I_{c2} = \frac{3\text{mW}}{2.5\text{V}} - 0.51\text{mA} \approx 0.69\text{mA}$$

$$\Rightarrow \frac{I_{c2}}{I_{REF}} = \frac{A_1}{A_{REF}} = \frac{0.51}{0.69} \approx \frac{5}{7}$$

9.62

$$R_{out} = R_C = \boxed{500 \Omega}$$

$$A_v = g_{m2} R_C = \frac{I_C R_C}{V_T} = 20$$

$$I_C = 1.04 \text{ mA}$$

$$P = (I_C + I_{REF}) V_{CC} = 3 \text{ mW}$$

$$I_{REF} = \boxed{0.16 \text{ mA}}$$

$$I_C = \frac{A_{E1}}{A_{E,REF}} I_{REF}$$

$$\frac{A_{E1}}{A_{E,REF}} = 6.5$$

$$A_{E,REF} = \boxed{A_E}$$

$$A_{E1} = \boxed{6.5 A_E}$$

$$\begin{aligned}
I_{copy} &= nI_{C,REF} \\
I_{REF} &= I_{C,REF} + I_{B,REF} + I_{B1} \\
&= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{I_{copy}}{\beta} \\
&= I_{C,REF} + \frac{I_{C,REF}}{\beta} + \frac{nI_{C,REF}}{\beta} \\
&= I_{C,REF} \left( 1 + \frac{1}{\beta} + \frac{n}{\beta} \right) \\
&= \frac{I_{copy}}{n} \left( \frac{n+1+\beta}{\beta} \right) \\
I_{copy} &= \left( \frac{\beta}{n+1+\beta} \right) nI_{REF}
\end{aligned}$$

Since  $nI_{REF}$  is the nominal value of  $I_{copy}$ , the error term,  $\frac{\beta}{n+1+\beta}$ , must be between 0.99 and 1.01 so that the actual value of  $I_{copy}$  is within 1% of the nominal value. Since the upper constraint (that the error term must be less than 1.01) results in a negative value of  $n$  (meaning that we can only get less than the nominal current if we include the error term), we only care about the lower error bound.

$$\begin{aligned}
\frac{\beta}{n+1+\beta} &\geq 0.99 \\
n &\leq 0.0101 \\
I_{REF} &\geq \boxed{50 \text{ mA}}
\end{aligned}$$

We can see that in order to decrease the error term, we must use a smaller value for  $n$  (in the ideal case, we have  $n$  approaching zero and the error term approaching  $\frac{\beta}{1+\beta}$ ). However, the smaller value of  $n$  we use, the larger value we must use for  $I_{REF}$ , meaning the more power we must consume. Thus, we have a direct trade-off between accuracy and power consumption.

$$\begin{aligned}
I_{C,M} &= \frac{A_{E,M}}{A_{E,REF1}} I_{C,REF1} \\
I_{REF1} &= I_{C,REF1} + I_{B,REF1} + I_{B,M} \\
&= I_{C,REF1} + \frac{I_{C,REF1}}{\beta_n} + \frac{I_{C,M}}{\beta_n} \\
&= I_{C,REF1} + \frac{I_{C,REF1}}{\beta_n} + \frac{A_{E,M} I_{C,REF1}}{A_{E,REF1} \beta_n} \\
&= I_{C,REF1} \left( 1 + \frac{1}{\beta_n} + \frac{A_{E,M}}{A_{E,REF1} \beta_n} \right) \\
&= \frac{A_{E,REF1}}{A_{E,M}} I_{C,M} \left( \frac{A_{E,REF1} \beta_n + A_{E,REF1} + A_{E,M}}{A_{E,REF1} \beta_n} \right) \\
I_{C,M} &= \left( \frac{A_{E,REF1} \beta_n}{A_{E,REF1} \beta_n + A_{E,REF1} + A_{E,M}} \right) \frac{A_{E,M}}{A_{E,REF1}} I_{REF}
\end{aligned}$$

Using a similar derivation to find  $I_{C2}$ , we have:

$$\begin{aligned}
I_{C1} = I_{C2} &= \left( \frac{A_{E,REF2} \beta_p}{A_{E,REF2} \beta_p + A_{E,REF2} + A_{E2}} \right) \frac{A_{E2}}{A_{E,REF2}} I_{C,M} \\
&= \left( \frac{A_{E,REF1} \beta_p}{A_{E,REF1} \beta_p + A_{E,REF1} + A_{E,M}} \right) \left( \frac{A_{E,REF2} \beta_p}{A_{E,REF2} \beta_p + A_{E,REF2} + A_{E2}} \right) \frac{A_{E,M}}{A_{E,REF1}} \cdot \frac{A_{E2}}{A_{E,REF2}} I_{REF}
\end{aligned}$$

We want the error term to be between 0.90 and 1.10 so that  $I_{C2}$  is within 10 % of its nominal value. Since the error term cannot exceed 1 (since we only lose current through the base), we only have to worry about the lower bound.


$$\left( \frac{A_{E,REF1} \beta_n}{A_{E,REF1} \beta_n + A_{E,REF1} + A_{E,M}} \right) \left( \frac{A_{E,REF2} \beta_p}{A_{E,REF2} \beta_p + A_{E,REF2} + A_{E2}} \right) \geq 0.90$$

Let's let the reference transistors  $Q_{REF1}$  and  $Q_{REF2}$  have unit size  $A_E$ . Then we have:

$$\left( \frac{\beta_n}{\beta_n + 1 + \frac{A_{E,M}}{A_E}} \right) \left( \frac{\beta_p}{\beta_p + 1 + \frac{A_{E2}}{A_E}} \right) > 0.90$$

We can pick any  $A_{E,M}$  and  $A_{E2}$  such that this constraint is satisfied. One valid solution is  $A_{E,M} = A_E$ ,  $A_{E2} = 3.466 A_E$ , and  $I_{REF} = 0.2885$  mA. This gives a nominal value for  $I_{C2}$  of 1 mA with an error of 10 %. This solution is not unique (for example, another solution would be  $A_{E,M} = A_{E2} = A_E$  and  $I_{REF} = 1$  mA, which gives a nominal current of 1 mA and an error of 5.73 %).

65.

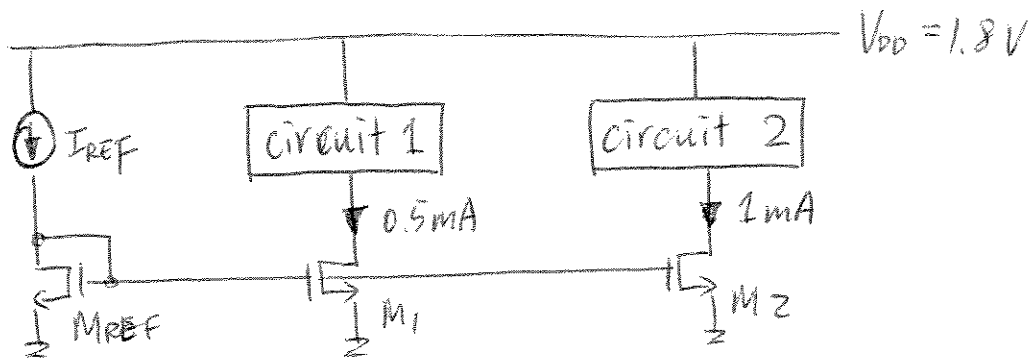

power budget = 3 mW.

$$\text{power} = V_{DD} (I_{REF} + 0.5mA + 1mA)$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{DD}} - 0.5mA - 1mA \approx 0.17mA$$


Assuming  $M_1$  &  $M_2$  operate in saturation,

If  $M_{REF}$  has  $(\frac{W}{L})_{REF}$ , then

$$\frac{(W/L)_1}{(W/L)_{REF}} = \frac{I_1}{I_{REF}} = \frac{50}{17}$$

$$\frac{(W/L)_2}{(W/L)_{REF}} = \frac{I_2}{I_{REF}} = \frac{100}{17}$$

66.

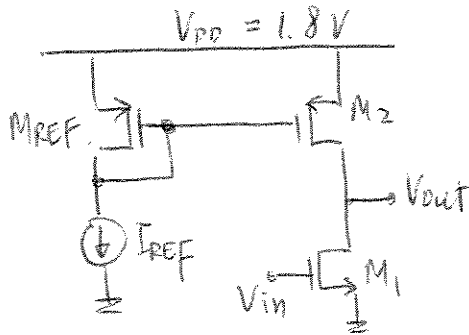

$$A_v = -20$$

$$\text{power} = 2 \text{ mW}$$

$$\left(\frac{W}{L}\right)_1 = \frac{20}{0.18}$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$\lambda_p = 0.2 \text{ V}^{-1}$$

$$R_{out} = r_{o2} \parallel r_{o1} = \frac{1}{\lambda_n I_{D1} + \lambda_p I_{D1}}$$

$$\Rightarrow A_v = -g_{m1} R_{out} = \frac{-g_{m1}}{\lambda_n I_{D1} + \lambda_p I_{D1}} = -\frac{2 I_{D1} / (V_{GS1} - V_{TH})}{I_{D1} (\lambda_n + \lambda_p)}$$

$$\Rightarrow -20 = -\frac{2}{(V_{GS1} - V_{TH}) (\lambda_n + \lambda_p)}$$

$$\Rightarrow V_{GS1} = \frac{1}{10 (\lambda_n + \lambda_p)} + V_{THn}$$

$$= \frac{1}{10 (0.1 + 0.2) \text{ V}^{-1}} + 0.4 \text{ V} \approx 0.73 \text{ V}$$

$$\Rightarrow I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS1} - V_{THn})^2$$

$$= \frac{1}{2} (100 \frac{\mu\text{A}}{\text{V}^2}) \left(\frac{20}{0.18}\right) (0.33 \text{ V})^2 \approx 0.61 \text{ mA}$$

$$\therefore \text{power} = V_{DD} (I_{REF} + I_{D1})$$

$$\Rightarrow I_{REF} = \frac{\text{power}}{V_{DD}} - I_{D1} = \frac{2 \text{ mW}}{1.8 \text{ V}} - 0.61 \text{ mA}$$


$$\approx 0.5 \text{ mA}$$



$\therefore$  if  $M_{REF}$  has  $(\frac{W}{L})_{REF}$ , then

$$\frac{(\frac{W}{L})_2}{(\frac{W}{L})_{REF}} = \frac{I_{D2}}{I_{REF}} = \frac{61}{50} \approx 1.2$$

67.

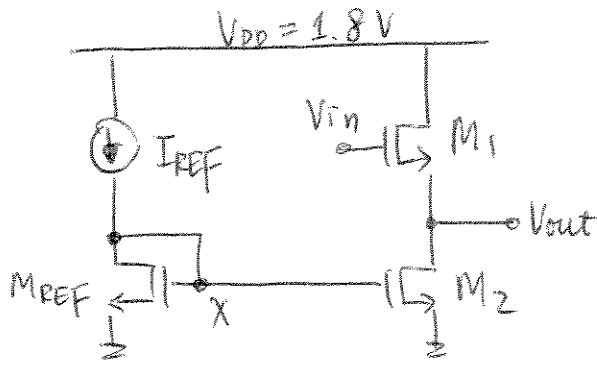

Given:

$$A_v = 0.85$$

$$R_{out} = 100 \Omega$$

$$(W/L)_2 = 10/0.18$$

$$\lambda_n = 0.1 \text{V}^{-1}, \lambda_p = 0.2 \text{V}^{-1}$$

$$R_{out} = r_{o2} \parallel \left( \frac{1}{g_{m1}} \parallel r_{o1} \right) = \frac{1}{g_{m1} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}}} = 100$$

For source follower,

$$A_v = \frac{g_{m1}}{g_{m1} + \frac{1}{r_{o2}} + \frac{1}{r_{o1}}} = 0.85$$

$$\Rightarrow g_{m1} = \frac{0.85}{100} = 8.5 \cdot 10^{-3} \text{S}$$

$$R_{out} = \frac{1}{g_{m1} + \frac{2}{r_o}} = 100$$

$$\Rightarrow r_o = \frac{200}{1 - 100g_{m1}} = \frac{200}{1 - 100(8.5 \cdot 10^{-3})} \approx 1333 \Omega$$

$$\Rightarrow I_{D1} = \frac{1}{\lambda_p r_{o1}} = 7.5 \text{mA}$$

Assume  $V_x \approx 1 \text{V}$ 

$$\left( \frac{W}{L} \right)_2 = \frac{2I_{D1}}{\mu_n C_{ox} (V_x - V_{TH})^2} \approx 416$$

Set  $I_{REF} \approx 0.75 \text{ mA}$ .

$$\Rightarrow \left(\frac{W}{L}\right)_{REF} = \left(\frac{W}{L}\right)_2 \frac{I_{REF}}{I_{D2}} \approx 42.$$

$$\begin{aligned}
A_v &= g_{m1}r_{o3} = g_{m1} \frac{1}{\lambda_p I_{D1}} = 20 \\
R_{in} &= \frac{1}{g_{m1}} \parallel r_{o2} \\
&= \frac{r_{o2}}{1 + g_{m1}r_{o2}} \\
&= \frac{\frac{1}{\lambda_n I_{D1}}}{1 + g_{m1} \frac{1}{\lambda_n I_{D1}}} \\
&= 50 \, \Omega \\
g_{m1} &= 19.5 \, \text{mS} \\
I_{D1} &= 4.88 \, \text{mA} \\
g_{m1} &= \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} \\
\left(\frac{W}{L}\right)_1 &= \boxed{390}
\end{aligned}$$


We need to size the rest of the transistors to ensure they provide the correct bias current to the amplifier and to ensure they are all in saturation.  $V_{G3}$  will be important in determining how we should bias  $V_{G5}$ , since in order for  $M_5$  to be in saturation, we require  $V_{G3} > V_{G5} - V_{THn}$ , and  $V_{G3}$  is fixed by the previously calculated value of  $I_{D1}$ .

$$\begin{aligned}
V_{G3} &= V_{DD} - V_{SG3} = V_{DD} - \left( |V_{THp}| + \sqrt{\frac{2I_{D1}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_3}} \right) \\
&= 0.363 \, \text{V}
\end{aligned}$$


Let's let  $I_{REF} = I_{D5} = 1 \, \text{mA}$  (which ensures we meet our power constraint, since  $P = (I_{REF} + I_{D5} + I_{D1})V_{DD} = 12.4 \, \text{mW}$ ) and  $V_{GS,REF} = V_{GS5} = 0.5 \, \text{V}$  (which ensures  $M_5$  operates in saturation). Then we have

$$\begin{aligned}
I_{REF} &= \frac{1}{2}\mu_n C_{ox} \left(\frac{W}{L}\right)_{REF} (V_{GS,REF} - V_{TH})^2 \\
\left(\frac{W}{L}\right)_{REF} &= \left(\frac{W}{L}\right)_5 = \boxed{\frac{360}{0.18}} \\
\frac{(W/L)_3}{(W/L)_4} &= \frac{I_{D3}}{I_{D4}} \\
\left(\frac{W}{L}\right)_4 &= \boxed{\frac{8.2}{0.18}} \\
\frac{(W/L)_2}{(W/L)_{REF}} &= \frac{I_{D2}}{I_{REF}} \\
\left(\frac{W}{L}\right)_2 &= \boxed{\frac{1756}{0.18}}
\end{aligned}$$

(1)

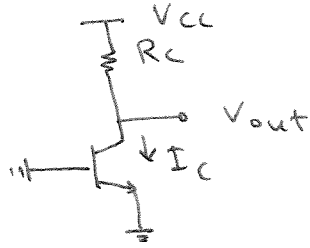


the small signal model is as follows:

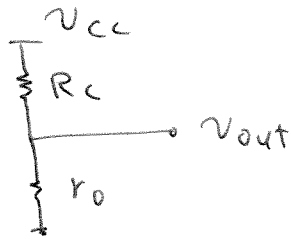


$$\frac{v_{out}}{V_{cc}} = \frac{r_o}{r_o + R_c} = \frac{\frac{V_A}{I_c}}{\frac{V_A}{I_c} + R_c} = \frac{V_A}{V_A + R_c I_c}$$

(2)

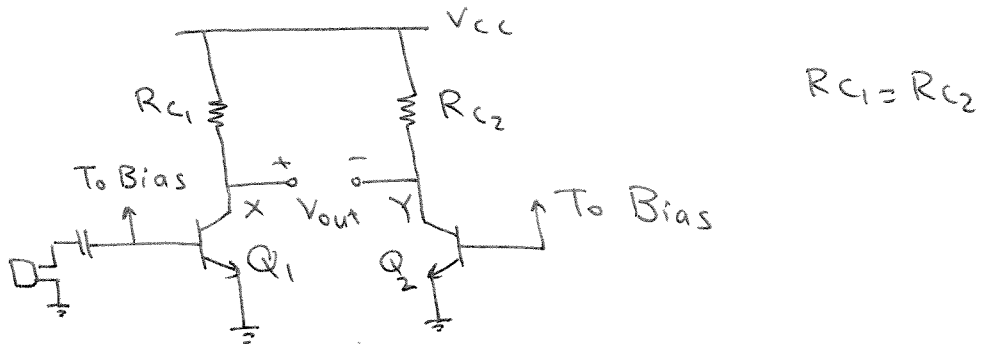

The small signal model is:

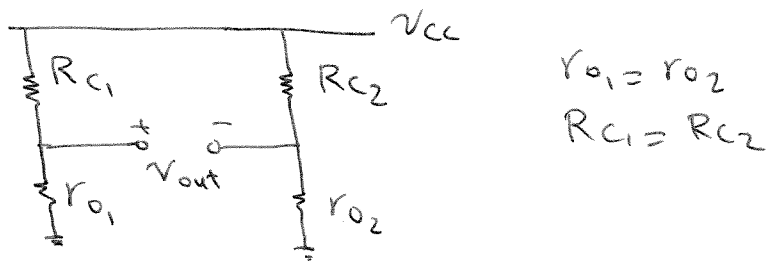


$$\frac{V_{out}}{V_{cc}} = \frac{1}{V_{cc}} \left( \frac{r_{o1}}{R_{C1} + r_{o1}} - \frac{r_{o2}}{R_{C2} + r_{o2}} \right) V_{cc} = 0$$

- 10.3 (a) Looking into the collector of  $Q_1$ , we see an infinite impedance (assuming  $I_{EE}$  is an ideal source). Thus, the gain from  $V_{CC}$  to  $V_{out}$  is  $\boxed{1}$ .
- (b) Looking into the drain of  $M_1$ , we see an impedance of  $r_{o1} + (1 + g_{m1}r_{o1}) R_S$ . Thus, the gain from  $V_{CC}$  to  $V_{out}$  is


$$\boxed{\frac{r_{o1} + (1 + g_{m1}r_{o1}) R_S}{R_D + r_{o1} + (1 + g_{m1}r_{o1}) R_S}}$$

- (c) Let's draw the small-signal model.

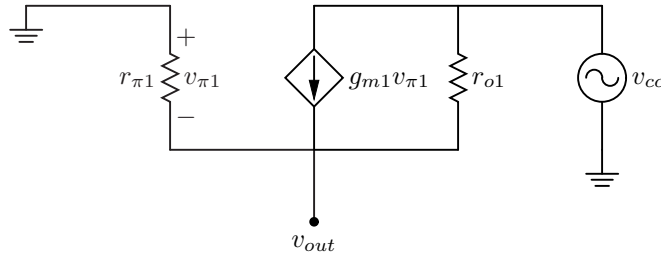

$$\begin{aligned} v_{out} &= -v_{\pi 1} \\ v_{out} &= \left( g_{m1}v_{\pi 1} + \frac{v_{cc} - v_{out}}{r_{o1}} \right) r_{\pi 1} \\ &= \left( -g_{m1}v_{out} + \frac{v_{cc} - v_{out}}{r_{o1}} \right) r_{\pi 1} \\ v_{out} \left( 1 + g_{m1}r_{\pi 1} + \frac{r_{\pi 1}}{r_{o1}} \right) &= v_{cc} \frac{r_{\pi 1}}{r_{o1}} \\ \frac{v_{out}}{v_{cc}} &= \frac{r_{\pi 1}}{r_{o1} \left( 1 + \beta + \frac{r_{\pi 1}}{r_{o1}} \right)} \\ &= \boxed{\frac{r_{\pi 1}}{r_{o1} (1 + \beta) + r_{\pi 1}}} \end{aligned}$$

- (d) Let's draw the small-signal model.

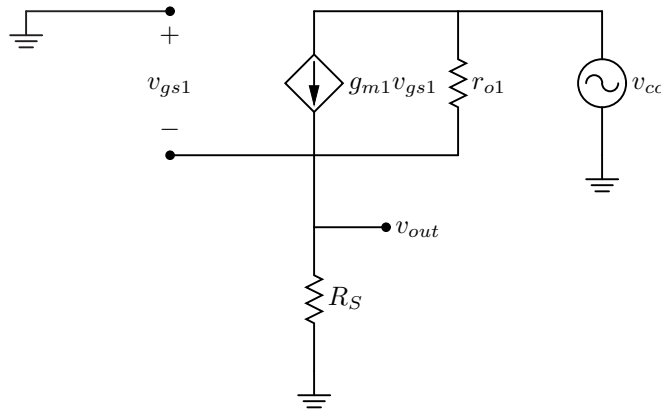

$$v_{out} = -v_{gs1}$$

$$v_{out} = \left( g_{m1}v_{gs1} + \frac{v_{cc} - v_{out}}{r_{o1}} \right) R_S$$
$$= \left( -g_{m1}v_{out} + \frac{v_{cc} - v_{out}}{r_{o1}} \right) R_S$$


$$v_{out} \left( 1 + g_{m1}R_S + \frac{R_S}{r_{o1}} \right) = v_{cc} \frac{R_S}{r_{o1}}$$

$$\frac{v_{out}}{v_{cc}} = \frac{R_S}{r_{o1} \left( 1 + g_{m1}R_S + \frac{R_S}{r_{o1}} \right)}$$

$$= \boxed{\frac{R_S}{r_{o1} (1 + g_{m1}R_S) + R_S}}$$




④

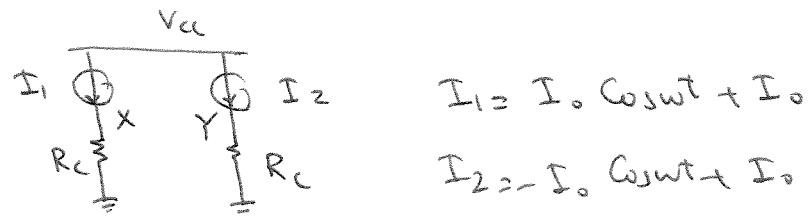

$$V_X = R_C I_1 = R_C I_0 (1 + \cos \omega t)$$

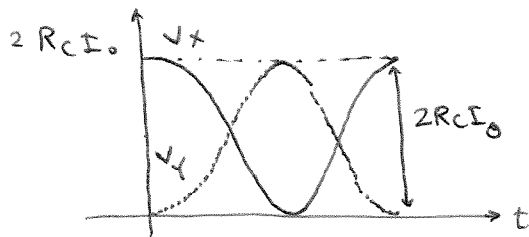
$$V_Y = R_C I_2 = R_C I_0 (1 - \cos \omega t)$$



$$V_{X,P-P} = V_{Y,P-P} = 2R_C I_0$$

$$V_{X,CM} = V_{Y,CM} = R_C I_0$$

⑤

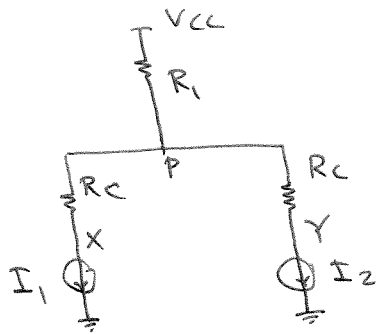

$$I_1 = I_0 \cos \omega t + I_0$$


$$I_2 = -I_0 \cos \omega t + I_0$$

$$V_P = V_{CC} - R_1 (I_1 + I_2) = V_{CC} - 2R_1 I_0$$

$$V_X = V_P - R_C I_1 = V_{CC} - 2R_1 I_0 - R_C I_0 - R_C I_0 \cos \omega t$$

$$\Rightarrow V_X = V_{CC} - (2R_1 + R_C) I_0 - R_C I_0 \cos \omega t$$

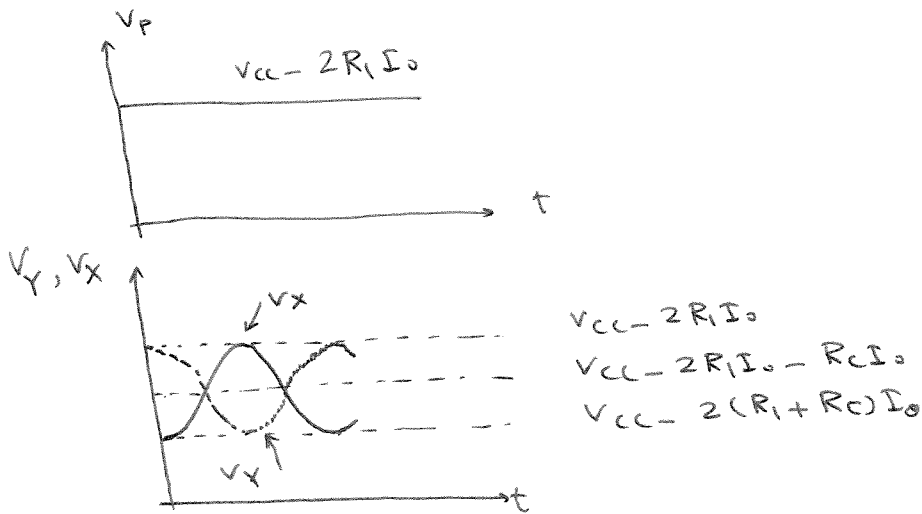
$$V_Y = V_P - R_C I_2 = V_{CC} - (2R_1 + R_C) I_0 + R_C I_0 \cos \omega t$$



$$V_{X,CM} = V_{Y,CM} = V_{CC} - (2R_1 + R_C) I_0$$

$$V_{X,P-P} = V_{Y,P-P} = 2R_C I_0$$

6

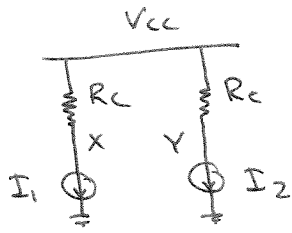


$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + I_0$$

$$V_X = V_{CC} - R_C I_1 = V_{CC} - R_C I_0 (1 + \cos \omega t)$$

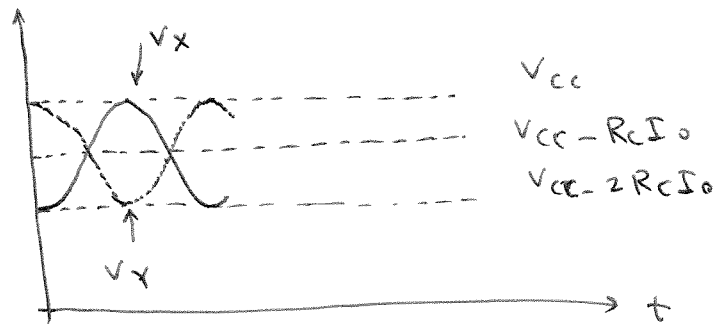
$$V_Y = V_{CC} - R_C I_2 = V_{CC} - R_C I_0 (1 - \cos \omega t)$$



$$V_{X,CM} = V_{Y,CM} = V_{CC} - R_C I_0$$

$$V_{X,P-P} = V_{Y,P-P} = 2 R_C I_0$$

⑦

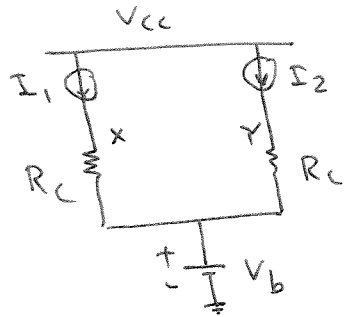


$$I_1 = I_0 \cos \omega t + I_0$$

$$I_2 = -I_0 \cos \omega t + I_0$$


$$V_x = R_C I_1 + V_b = R_C I_0 (1 + \cos \omega t) + V_b$$
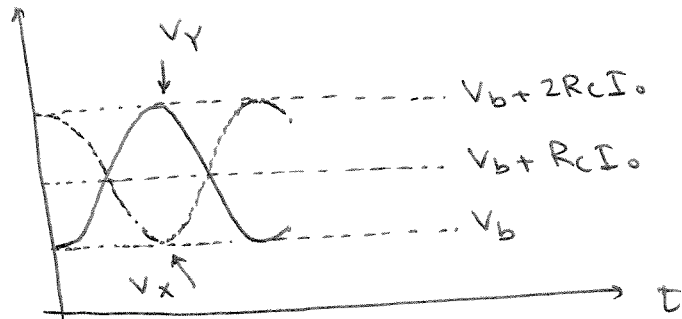
$$V_Y = R_C I_2 + V_b = R_C I_0 (1 - \cos \omega t) + V_b$$



$$V_{x,CM} = V_{Y,CM} = V_b + R_C I_0$$

$$V_{x,P-P} = V_{Y,P-P} = 2R_C I_0$$

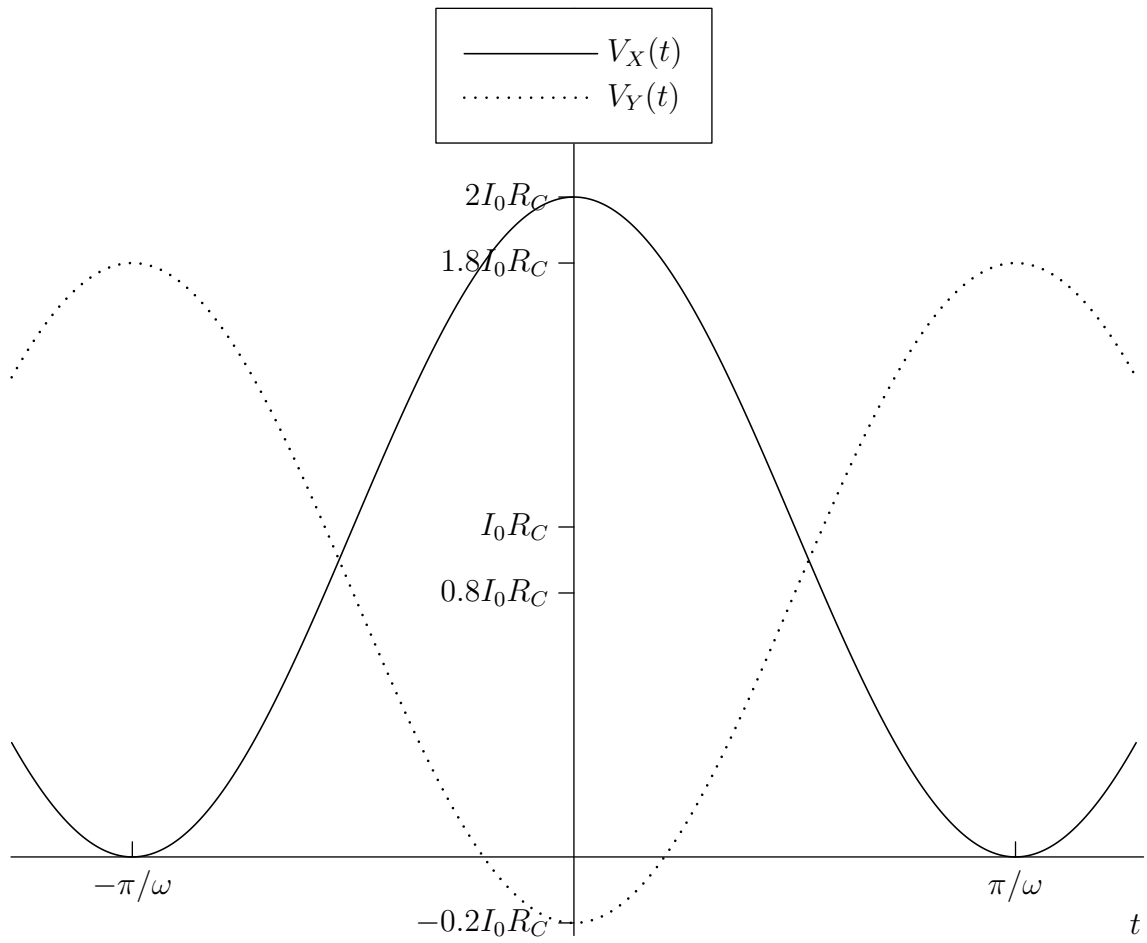


$X$  and  $Y$  are not true differential signals, since their common-mode values differ.

10.9 (a)

$$V_X = V_{CC} - I_1 R_C$$


$$V_Y = V_{CC} - (I_2 + I_T) R_C$$

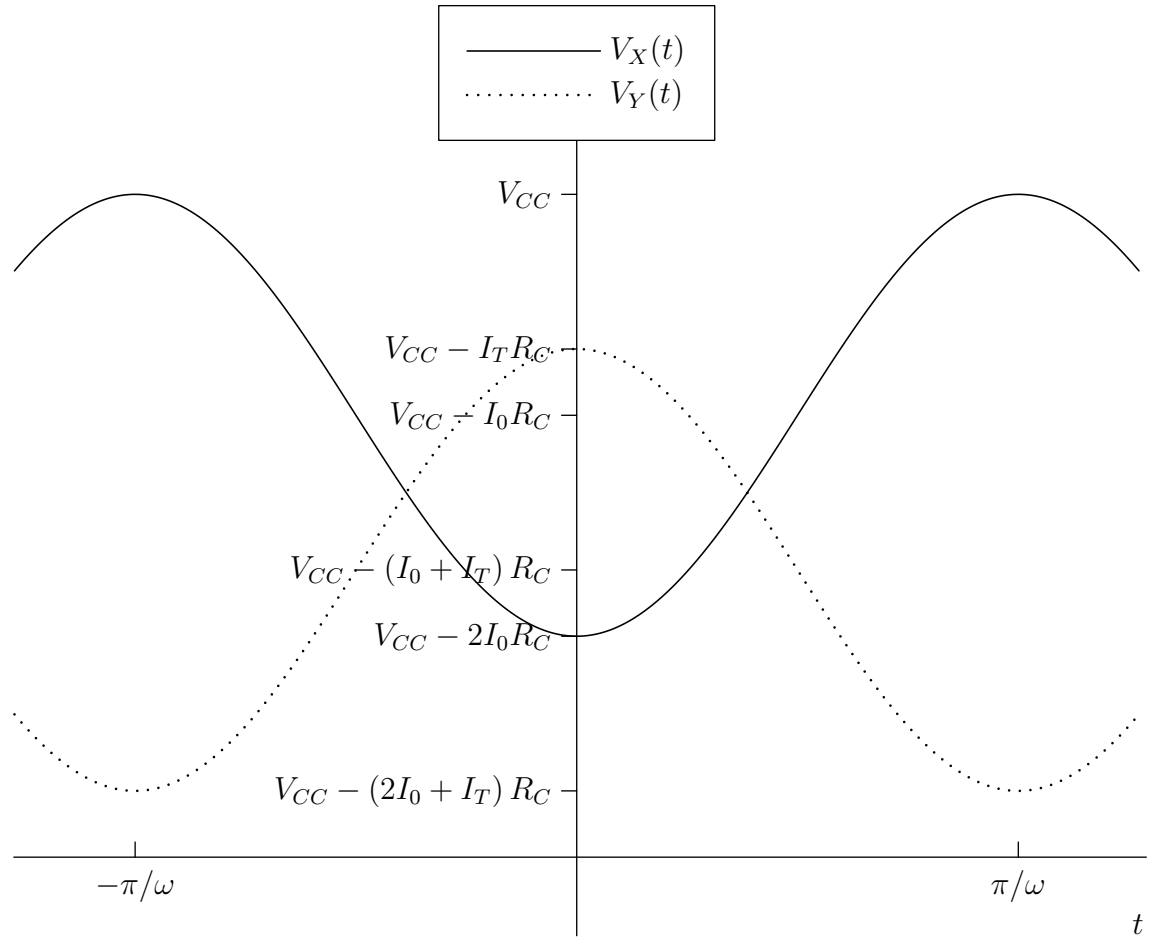

(b)

$$V_X = V_{CC} - (I_1 - I_T) R_C$$

$$V_Y = V_{CC} - (I_2 + I_T) R_C$$

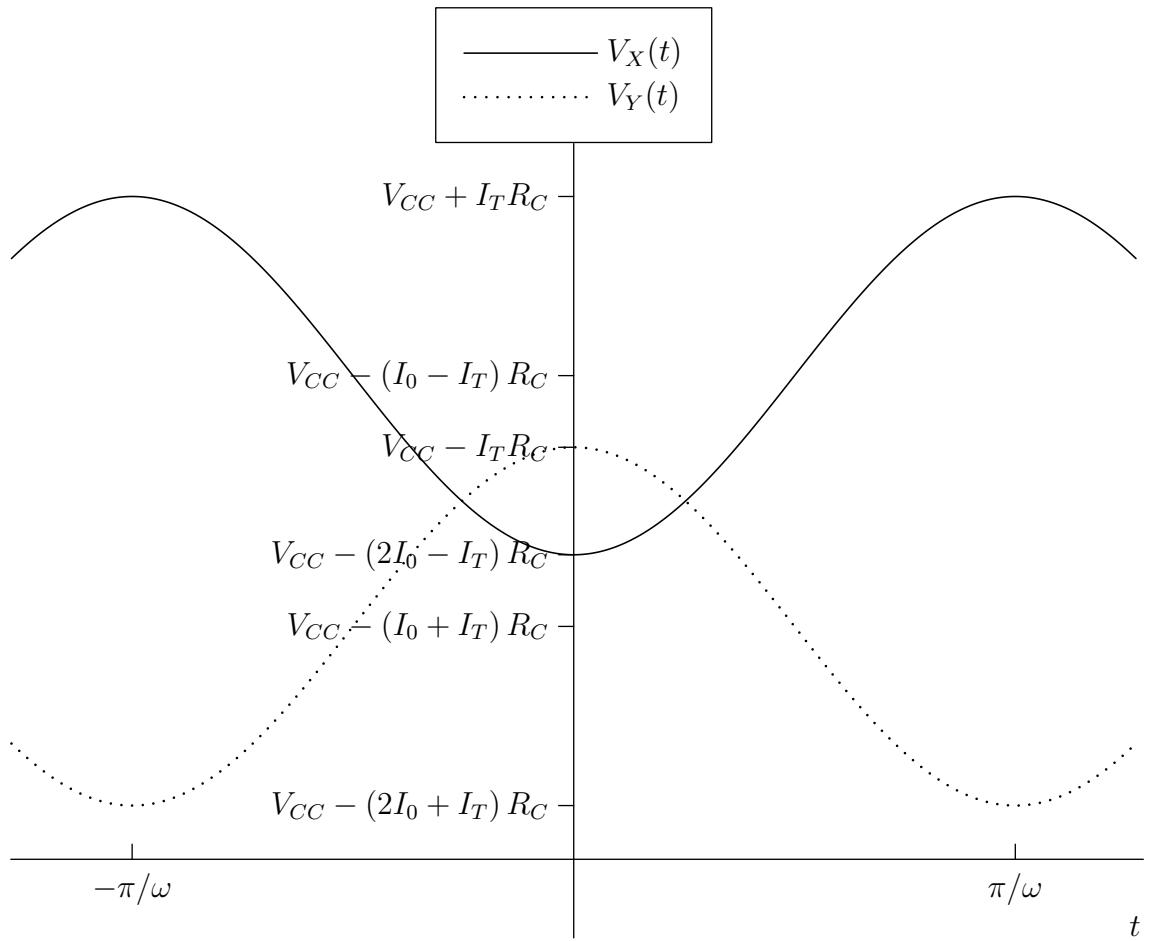

(c)

$$\begin{aligned}
V_X &= V_{CC} - \left( I_1 + \frac{V_X - V_Y}{R_P} \right) R_C \\
V_X \left( 1 + \frac{R_C}{R_P} \right) &= V_{CC} - \left( I_1 - \frac{V_Y}{R_P} \right) R_C \\
V_X &= \frac{V_{CC} - \left( I_1 - \frac{V_Y}{R_P} \right) R_C}{1 + \frac{R_C}{R_P}} \\
&= \frac{V_{CC} R_P - (I_1 R_P - V_Y) R_C}{R_P + R_C} \\
V_Y &= V_{CC} - \left( I_2 + \frac{V_Y - V_X}{R_P} \right) R_C \\
V_Y \left( 1 + \frac{R_C}{R_P} \right) &= V_{CC} - \left( I_2 - \frac{V_X}{R_P} \right) R_C \\
V_Y &= \frac{V_{CC} - \left( I_2 - \frac{V_X}{R_P} \right) R_C}{1 + \frac{R_C}{R_P}} \\
&= \frac{V_{CC} R_P - (I_2 R_P - V_X) R_C}{R_P + R_C} \\
V_X &= \frac{V_{CC} R_P - \left( I_1 R_P - \frac{V_{CC} R_P - (I_2 R_P - V_X) R_C}{R_P + R_C} \right) R_C}{R_P + R_C} \\
&= \frac{V_{CC} R_P - I_1 R_P R_C + \frac{V_{CC} R_P R_C - I_2 R_P R_C^2 + V_X R_C^2}{R_P + R_C}}{R_P + R_C} \\
V_X \left( 1 - \frac{R_C^2}{(R_P + R_C)^2} \right) &= \frac{V_{CC} R_P - I_1 R_P R_C + \frac{V_{CC} R_P R_C - I_2 R_P R_C^2}{R_P + R_C}}{R_P + R_C} \\
V_X \left( \frac{(R_P + R_C)^2 - R_C^2}{R_P + R_C} \right) &= V_{CC} R_P - I_1 R_P R_C + \frac{V_{CC} R_P R_C - I_2 R_P R_C^2}{R_P + R_C} \\
V_X (R_P^2 + 2R_P R_C) &= V_{CC} R_P (R_P + R_C) - I_1 R_P R_C (R_P + R_C) + V_{CC} R_P R_C - I_2 R_P R_C^2 \\
V_X &= \frac{V_{CC} R_P (R_P + R_C) - I_1 R_P R_C (R_P + R_C) + V_{CC} R_P R_C - I_2 R_P R_C^2}{R_P^2 + 2R_P R_C} \\
&= \frac{V_{CC} R_P (2R_C + R_P) - R_P R_C [I_1 (R_P + R_C) + I_2 R_C]}{R_P (2R_C + R_P)}
\end{aligned}$$


Substituting  $I_1$  and  $I_2$ , we have:

$$\begin{aligned}
V_X &= \frac{V_{CC} R_P (2R_C + R_P) - R_P R_C [(I_0 + I_0 \cos(\omega t)) (R_P + R_C) + (I_0 - I_0 \cos(\omega t)) R_C]}{R_P (2R_C + R_P)} \\
&= \frac{V_{CC} R_P (2R_C + R_P) - R_P R_C [I_0 (2R_C + R_P) + I_0 \cos(\omega t) R_P]}{R_P (2R_C + R_P)} \\
&= V_{CC} - I_0 R_C + I_0 \cos(\omega t) \frac{R_C R_P}{2R_C + R_P}
\end{aligned}$$

By symmetry, we can write:

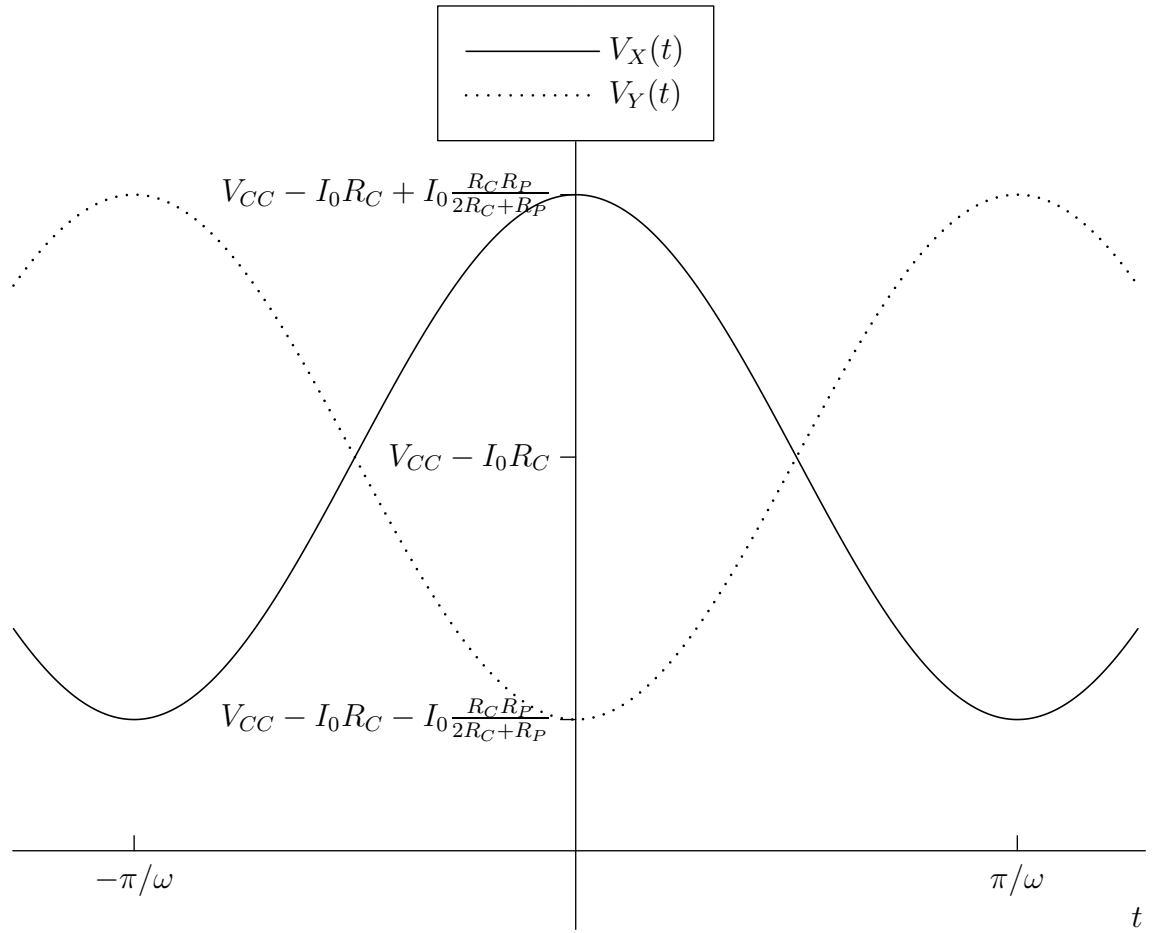
$$V_Y = V_{CC} - I_0 R_C - I_0 \cos(\omega t) \frac{R_C R_P}{2R_C + R_P}$$





(d)
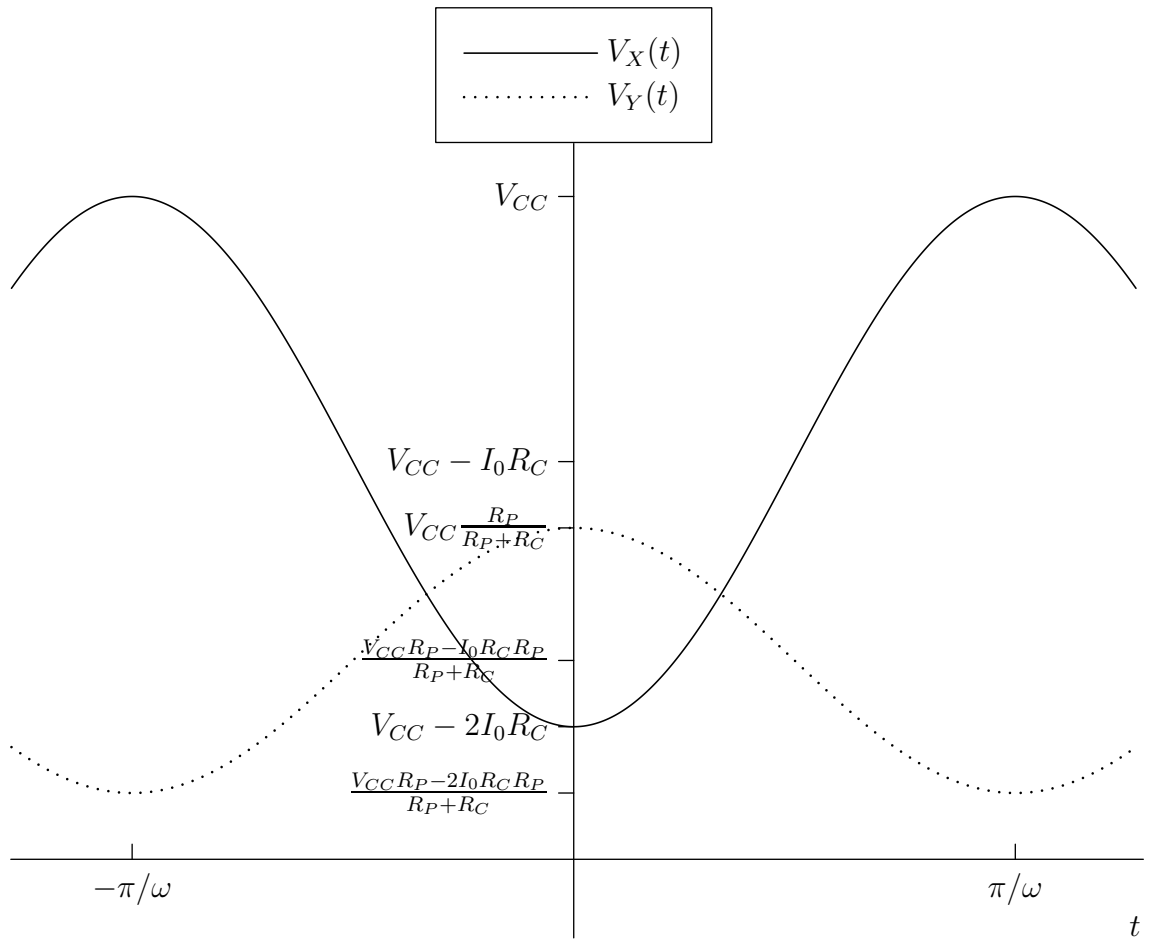
$$\begin{aligned}
 V_X &= V_{CC} - I_1 R_C \\
 V_Y &= V_{CC} - \left( I_2 + \frac{V_Y}{R_P} \right) R_C \\
 V_Y \left( 1 + \frac{R_C}{R_P} \right) &= V_{CC} - I_2 R_C \\
 V_Y &= \frac{V_{CC} - I_2 R_C}{1 + \frac{R_C}{R_P}} \\
 &= \frac{V_{CC} R_P - I_2 R_C R_P}{R_P + R_C}
 \end{aligned}$$




(10)

$$V_1 = V_0 \cos \omega t + V_0$$

$$V_2 = -V_0 \cos \omega t + V_0$$


(a)

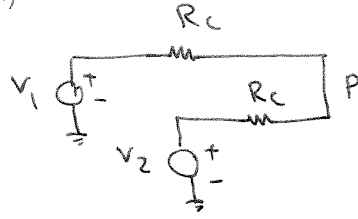

$$V_P = \frac{V_1 + V_2}{2} = V_0$$




(b)

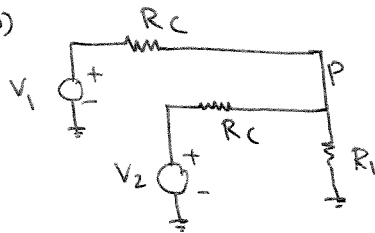


$$\frac{2V_P - V_1 - V_2}{R_c} + \frac{V_P}{R_i} = 0 \Rightarrow$$

$$\frac{2V_P - 2V_0}{R_c} + \frac{V_P}{R_i} = 0 \Rightarrow (2R_i + R_c)V_P = 2V_0 R_i$$
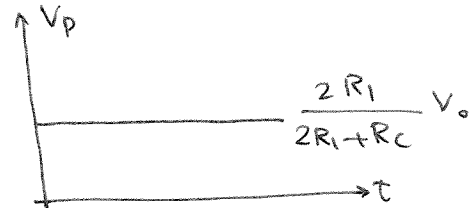
$$\rightarrow V_P = \frac{2R_i}{2R_i + R_c} V_0$$




(c)

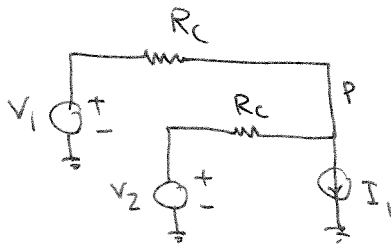

$$\frac{2V_P - V_1 - V_2}{R_c} + I_1 = 0 \Rightarrow$$

$$\frac{2V_P - 2V_0}{R_c} = -I_1 \Rightarrow$$

$$V_P = V_0 - \frac{R_c I_1}{2}$$

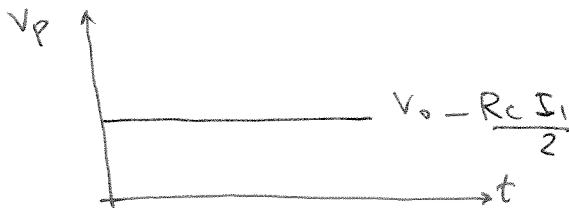

10.11 Note that since the circuit is symmetric and  $I_{EE}$  is an ideal source, no matter what value of  $V_{CC}$  we have, the current through  $Q_1$  and  $Q_2$  must be  $I_{EE}/2$ . That means if the supply voltage increases by some amount  $\Delta V$ ,  $V_X$  and  $V_Y$  must also increase by the same amount to ensure the current remains the same.


$$\Delta V_X = \boxed{\Delta V}$$

$$\Delta V_Y = \boxed{\Delta V}$$

$$\Delta(V_X - V_Y) = \boxed{0}$$

We can say that this circuit rejects supply noise because changes in the supply voltage (i.e., supply noise) do not show up as changes in the differential output voltage  $V_X - V_Y$ .

12

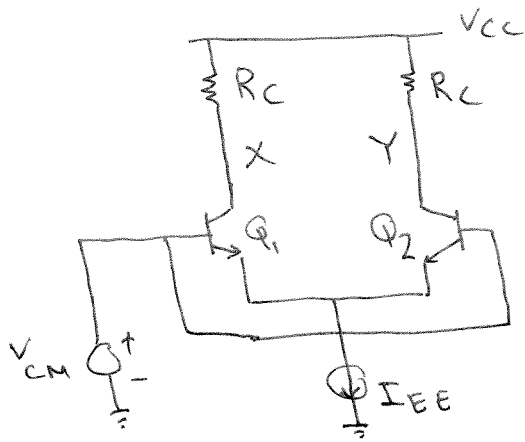


$$\Delta V_X = - \frac{R_C \Delta I_{EE}}{2} = - \frac{R_C \Delta I}{2}$$

$$\Delta V_Y = - \frac{R_C \Delta I_{EE}}{2} = - \frac{R_C \Delta I}{2}$$

$$\Rightarrow \Delta(V_X - V_Y) = 0$$

(13)

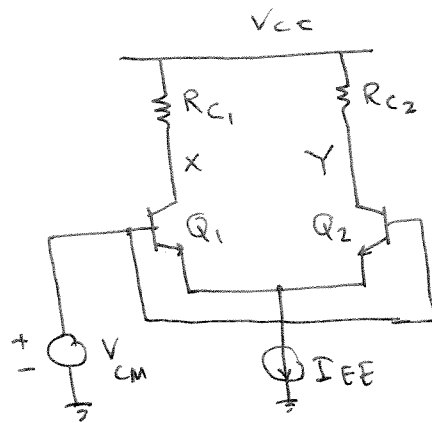


$$R_{C1} = R_{C2} + \Delta R$$

$$\Delta V_X = - \frac{R_{C1} \Delta I}{2} = - \frac{(R_{C2} + \Delta R) \Delta I}{2}$$

$$\Delta V_Y = - \frac{R_{C2} \Delta I}{2} \Rightarrow$$

$$\Delta(V_X - V_Y) = - \frac{\Delta R \Delta I}{2}$$


14

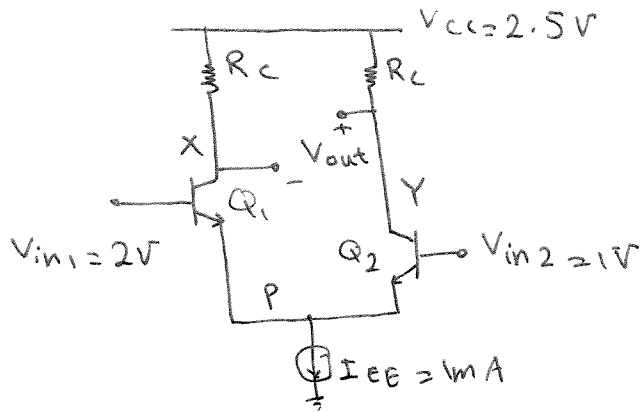

$$V_X \geq V_{in1} \Rightarrow V_X \geq 2 \Rightarrow V_{CC} - R_C I_{EE} \geq 2$$

$$\Rightarrow 2.5 - R_C^{(k\Omega)} \geq 2 \Rightarrow R_C \leq 0.5\text{ k}\Omega$$

15

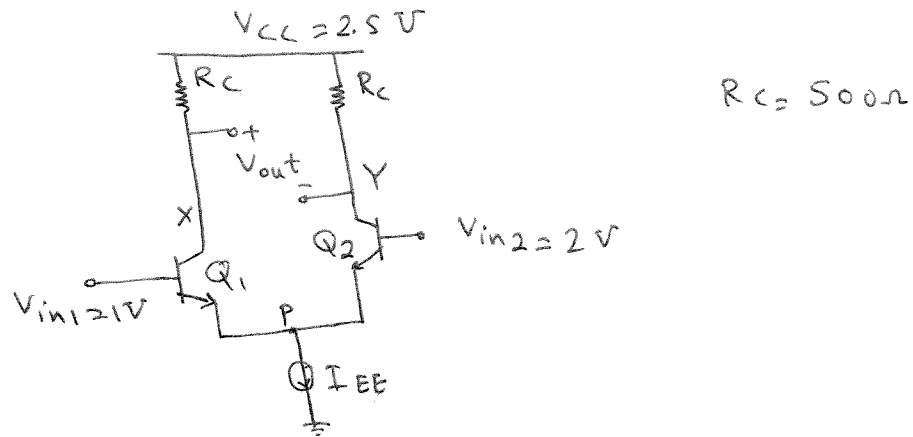


$$V_Y \geq V_{in2} \Rightarrow V_{CC} - R_c I_{EE} \geq 2 \Rightarrow$$

$$2.5 - 500 I_{EE} \geq 2 \Rightarrow I_{EE} \leq 1\text{mA}$$



16

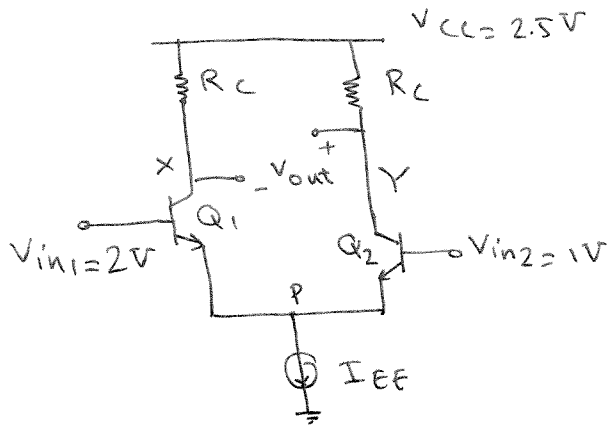

$$I_{EE} = 1\text{mA}$$



$$R_C = 800\ \Omega$$

$$V_X = V_{CC} - R_C \bar{I}_{EE} = 2.5 - 0.8 = 1.7\text{V}$$



$\Rightarrow V_X < V_{in1} \Rightarrow Q_1$  is in saturation region.

(17)



(a)

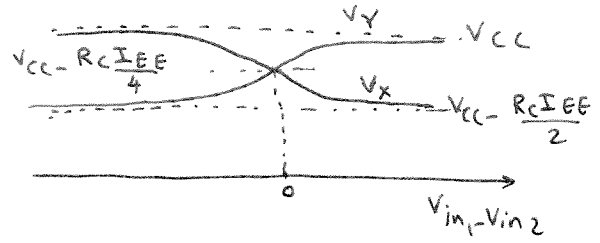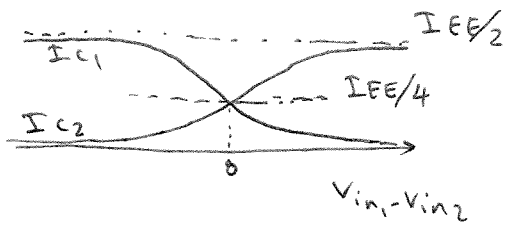


(b)

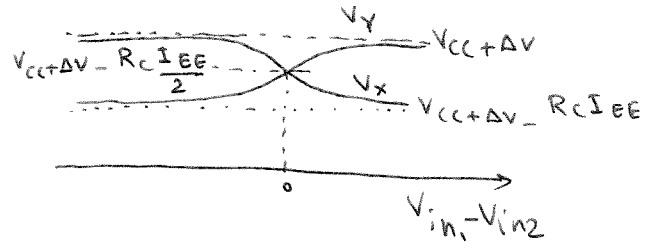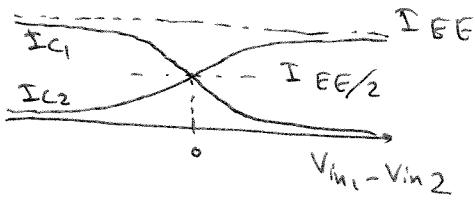

(c)

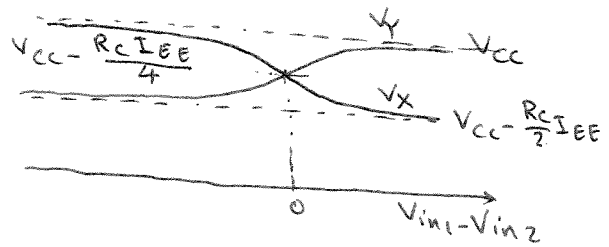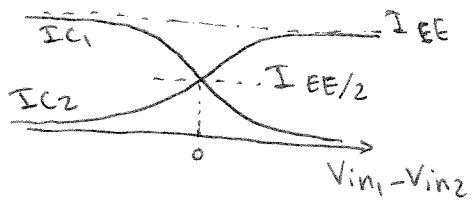

18

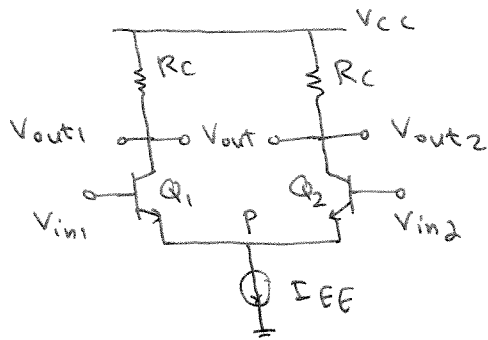

$$\frac{I_{C1}}{I_{C2}} = 5$$

$$V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 0.026 \ln 5 = 41.845 \text{ mV}$$

at  $27^\circ$ ,  $V_T = 26 \text{ mV} \Rightarrow$  at  $100^\circ$ ,

$$V_T = \frac{(273 + 100)}{273 + 27} 26^{\text{mV}} = 32.33 \text{ mV}$$

$$\Rightarrow \frac{41.845 \text{ mV}}{\text{mV}} = \frac{32.33 \text{ mV}}{\text{mV}} \ln \frac{I_{C1}}{I_{C2}} \Rightarrow \frac{I_{C1}}{I_{C2}} = 3.65$$

(19)

$$I_{C2} = I_{C1} = \frac{I_{EE}}{2}$$

if  $I_{C2}$  changes by 10% then


$$1.1 \times I_{C2 \text{ bias}} = \frac{I_{EE}}{1 + \exp \frac{V_{in1} - V_{in2}}{V_T}} \Rightarrow$$

$$1.1 \times \frac{I_{EE}}{2} = \frac{I_{EE}}{1 + \exp \frac{V_{in1} - V_{in2}}{V_T}} \Rightarrow$$

$$V_{in1} - V_{in2} = V_T \ln \frac{0.9}{1.1} = -0.2 V_T = -5.217 \text{ mV}$$

So the input differential voltage should change by no more than 5.2 mV.

(20)

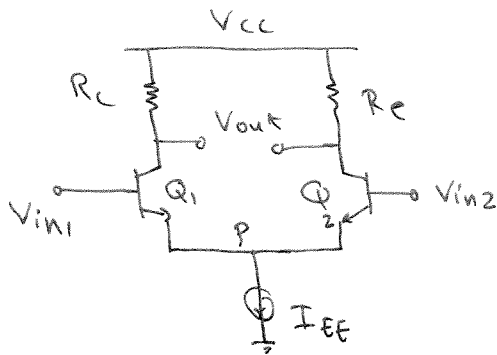

$$I_{C2} = \frac{I_{EE}}{1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)}$$

$$I_{C2 \text{ bias}} = \frac{I_{EE}}{2}$$

if the transconductance of  $Q_2$  drops by a factor of 2, then  $I_{C2} = \frac{I_{EE}}{4}$

$$\Rightarrow \frac{I_{EE}}{4} = \frac{I_{EE}}{1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)} \Rightarrow$$


$$V_{in1} - V_{in2} = V_T \ln 3 = 1.0986 V_T = 28.564 \text{ mV}$$

$$(21) \quad v_{in1} - v_{in2} = \Delta v_{in}$$

$$I_{C1} - I_{C2} = \frac{I_{EE} \exp \frac{\Delta v_{in}}{V_T}}{1 + \exp \frac{\Delta v_{in}}{V_T}} - \frac{I_{EE}}{1 + \exp \frac{\Delta v_{in}}{V_T}}$$

$$\Rightarrow \frac{\partial (I_{C1} - I_{C2})}{\partial (\Delta v_{in})} = I_{EE} \left[ \frac{\frac{1}{V_T} \exp \left( \frac{\Delta v_{in}}{V_T} \right) (1 + \exp \frac{\Delta v_{in}}{V_T}) - \frac{(\exp \frac{\Delta v_{in}}{V_T})^2}{V_T}}{(1 + \exp \frac{\Delta v_{in}}{V_T})^2} + \frac{\frac{1}{V_T} \exp \frac{\Delta v_{in}}{V_T}}{(1 + \exp \frac{\Delta v_{in}}{V_T})^2} \right]$$
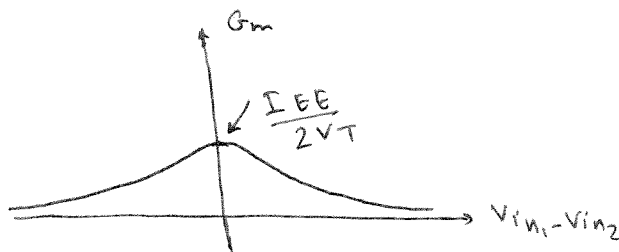
$$= \frac{2 I_{EE}}{V_T} \frac{\exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right)}{\left( 1 + \exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right) \right)^2}$$



$$\begin{cases} \max G_m = \frac{I_{EE}}{2V_T} \\ \text{At } v_{in1} - v_{in2} = 0 \end{cases}$$

$$\text{if } G_m = \frac{1}{2} G_{m_{\max}} = \frac{I_{EE}}{4V_T} \Rightarrow$$

$$\frac{\exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right)}{\left( 1 + \exp \left( \frac{v_{in1} - v_{in2}}{V_T} \right) \right)^2} = \frac{1}{8} \Rightarrow v_{in1} - v_{in2} = \pm 1.763 V_T = \pm 45.838 \text{ mV}$$

Q2)


$$V_{out1} - V_{out2} = -R_C I_{EE} \tanh \frac{V_{in1} - V_{in2}}{2V_T}$$

$$A_V = \frac{\partial (V_{out1} - V_{out2})}{\partial (V_{in1} - V_{in2})} = -\frac{2R_C I_{EE}}{V_T} \frac{\exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)}{\left[1 + \exp\left(\frac{V_{in1} - V_{in2}}{V_T}\right)\right]^2}$$



if  $V_{in1} - V_{in2} = 30 \text{ mV} \Rightarrow$

$$A_V = -14.02 R_C I_{EE}$$

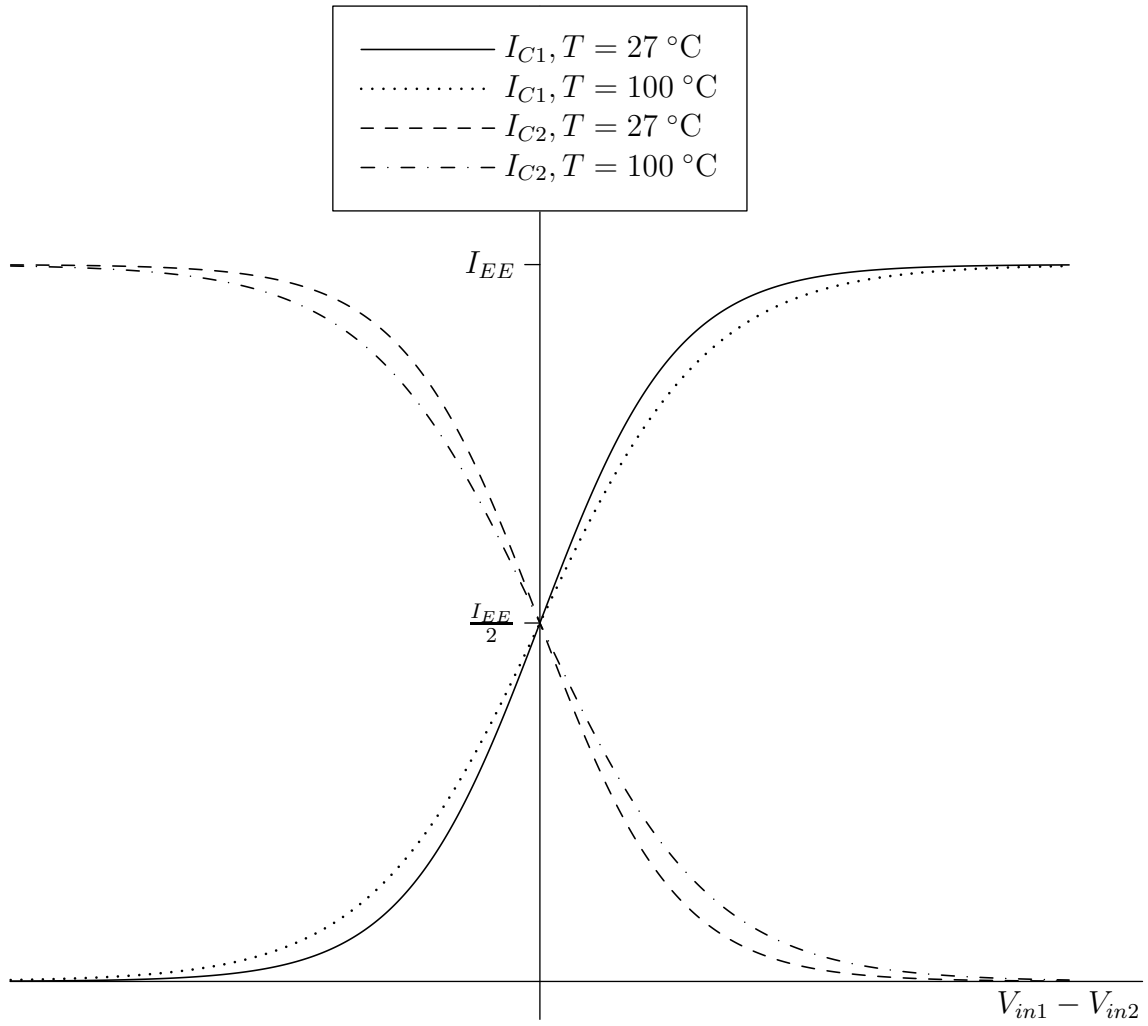
10.23 If the temperature increases from 27 °C to 100 °C, then  $V_T$  will increase from 25.87 mV to 32.16 mV. This will cause the curves to stretch horizontally, since the differential input will have to be larger in magnitude in order to drive the current to one side of the differential pair. This stretching is shown in the following plots.






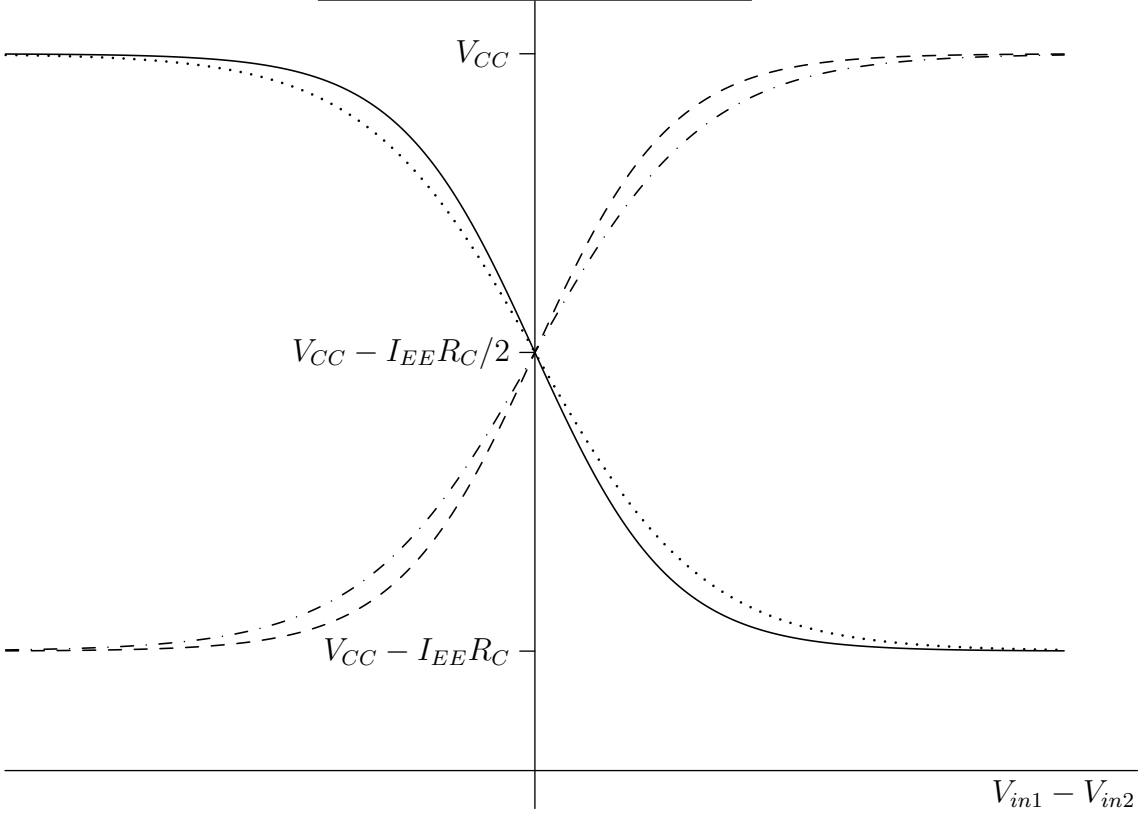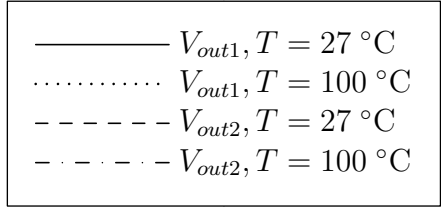

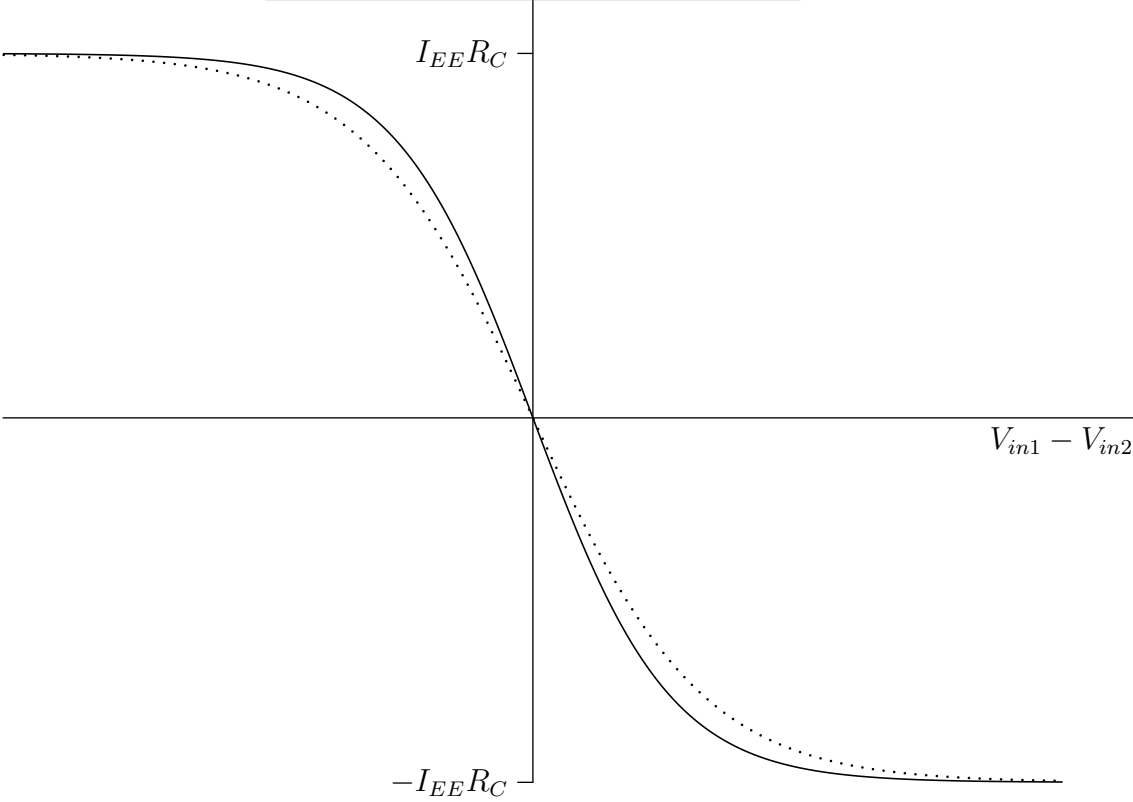—  $V_{out1} - V_{out2}, T = 27\text{ }^\circ\text{C}$   
.....  $V_{out1} - V_{out2}, T = 100\text{ }^\circ\text{C}$



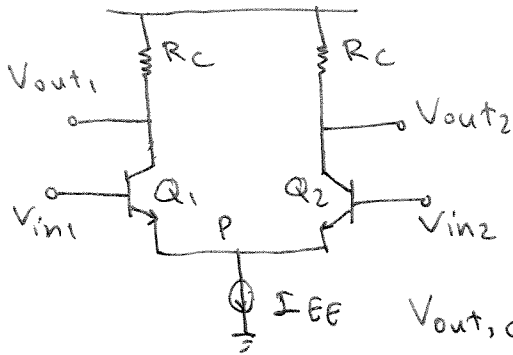(24)  $R_C = 500 \Omega$ ,  $I_{EE} = 1 \text{ mA}$ ,  $V_{CC} = 2.5 \text{ V}$   
 $V_{in1} = V_0 \sin \omega t + V_{CM}$   $V_{in2} = -V_0 \sin \omega t + V_{CM}$ ,  $V_{CM} = 1 \text{ V}$   
 $V_{CC}$




$$A_v = -g_m R_C = -\frac{I_{EE}}{2V_T} R_C =$$

$$= -\frac{10^{-3} \times 500}{2 \times 0.026} = -9.615$$

$$V_{out, CM} = V_{CC} - R_C \frac{I_{EE}}{2} = 2.5 - 0.5 \times 0.5 \Rightarrow$$

$$V_{out, CM} = 2.25$$

(a)  $|V_{out}| = |A_v V_{in}| = 9.615 \times 2 \text{ m} = 19.23 \text{ mV}$

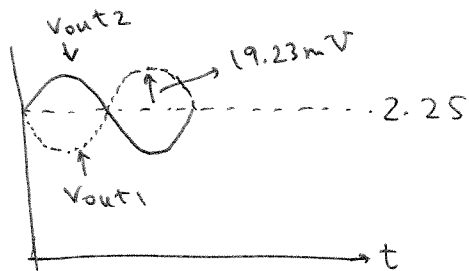


(b)  $I_{C1} = 0.95 I_{EE}$ ,  $I_{C2} = 0.05 I_{EE}$ ,  $\frac{I_{C1}}{I_{C2}} = 19$


$$V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 76.555 \text{ mV}$$

$$\frac{V_{in1} - V_{in2}}{2} = \frac{50 \text{ mV}}{2} \sin \omega t_1 \Rightarrow 38.278 = \frac{50 \text{ mV}}{2} \sin \omega t_1 \Rightarrow$$

$$t_1 = \frac{0.872}{\omega}$$

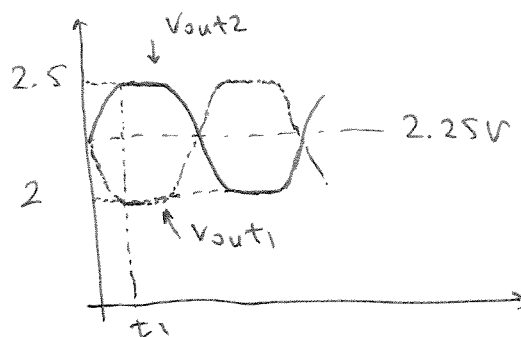

(25)

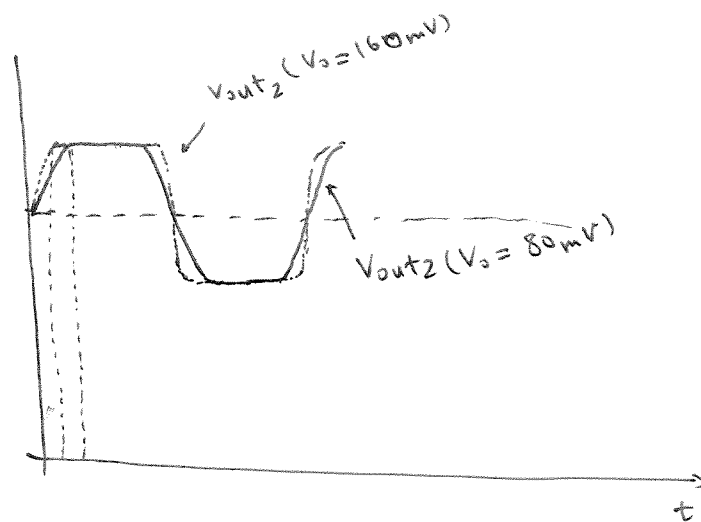

The time at which one transistor takes 95% of the tail current source is achievable through:

$$\frac{I_{C1}}{I_{C2}} = 19 \Rightarrow V_{in1} - V_{in2} = V_T \ln \frac{I_{C1}}{I_{C2}} = 76.555 \text{ mV}$$

$$\frac{V_{in1} - V_{in2}}{2} = V_0 \sin \omega t_1 \Rightarrow t_1 = \frac{\text{Arc Sin } \frac{38.278}{V_0}}{\omega}$$

evidently as  $V_0$  increases,  $t_1$  decreases and the output waveform becomes sharper.

$$t_1 (V_0 = 80 \text{ mV}) = \frac{0.499}{\omega}$$

$$t_1 (V_0 = 160 \text{ mV}) = \frac{0.242}{\omega}$$


$$(26) \quad \omega = 2\pi \times (100 \text{ MHz})$$

$$\text{Slope} \approx \frac{V_{CC} - V_{CM}}{t_1} = \frac{0.25 \text{ V}}{\text{Arc Sin}\left(\frac{38.278}{V_o \text{ (mV)}}\right)}$$


$$\Rightarrow \text{if } V_o = 80 \text{ mV} \Rightarrow \text{slope} = 3.148 \times 10^8 \text{ V/s}$$

$$\text{if } V_o = 160 \text{ mV} \Rightarrow \text{slope} = 6.491 \times 10^8 \text{ V/s}$$

(27)

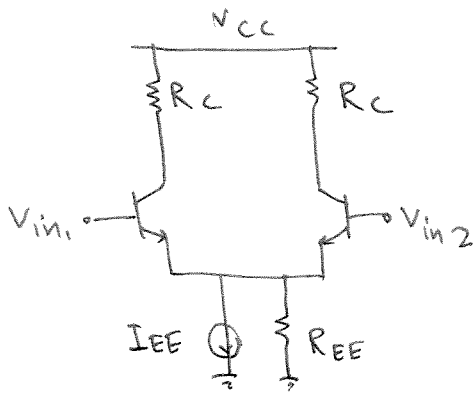

The small signal model is,

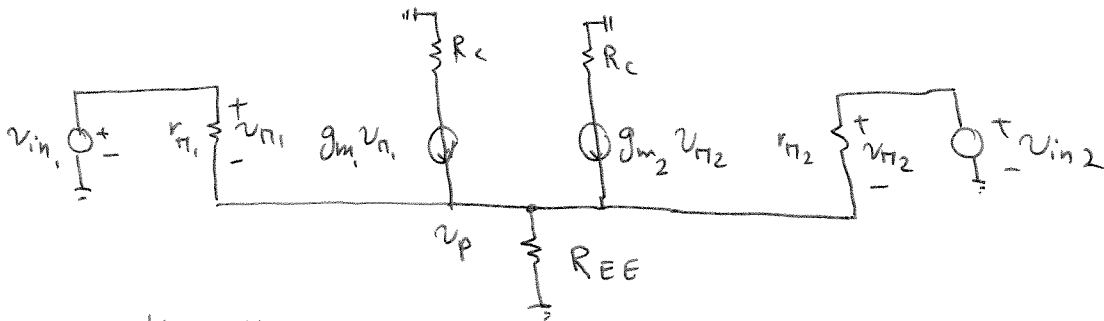


writing the node equation at P we have:

$$\frac{v_p}{R_{EE}} + \frac{v_p - v_{in1}}{r_{\pi 1}} + g_{m1}(v_p - v_{in1}) + \frac{v_p - v_{in2}}{r_{\pi 2}} + g_{m2}(v_p - v_{in2}) = 0$$


Since  $v_{in1} = -v_{in2}$  and  $\begin{cases} r_{\pi 1} = r_{\pi 2} \\ g_{m1} = g_{m2} \end{cases}$ , the above equation simplifies to:
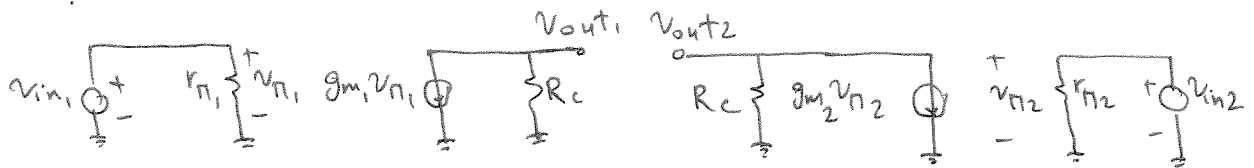
$$\frac{v_p}{R_{EE}} + \frac{2v_p}{r_{\pi 1}} + 2g_{m1}v_p = 0 \Rightarrow v_p = 0 \Rightarrow \text{the small signal model is:}$$



$$A_v = \frac{v_{out1} - v_{out2}}{v_{in1} - v_{in2}} = \frac{-g_{m1}v_{in1}R_C + g_{m2}v_{in2}R_C}{v_{in1} - v_{in2}} = -g_{m1}R_C$$

(28)

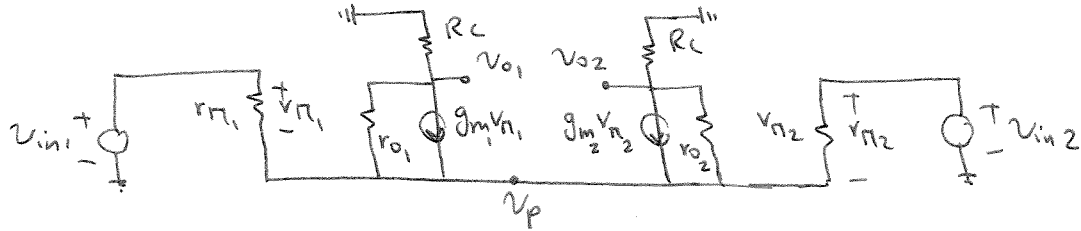

$$V_{in1} = -V_{in2} \rightarrow V_{in1} + V_{in2} = 0$$
$$g_{m1} = g_{m2}, r_{\pi1} = r_{\pi2}, r_{o1} = r_{o2}$$

Writing the node equation at  $V_p$ :

$$\frac{V_p - V_{in1}}{r_{\pi1}} + \frac{V_p - V_{o1}}{r_{o1}} + g_{m1}(V_p - V_{in1}) + g_{m2}(V_p - V_{in2}) +$$
$$\frac{V_p - V_{in2}}{r_{\pi2}} + \frac{V_p - V_{o2}}{r_{o2}} = 0 \Rightarrow 2g_{m1} V_p + \frac{2V_p - V_{o1} - V_{o2}}{r_{o1}} + \frac{2V_p \times 2}{r_{\pi1}} = 0 \quad (1)$$

Now the node equations at nodes  $V_{o1}$  and  $V_{o2}$  leads to:


$$\begin{cases} \frac{V_{o1}}{R_c} + \frac{V_{o1} - V_p}{r_{o1}} + g_{m1}(V_{in1} - V_p) = 0 & (2) \\ \frac{V_{o2}}{R_c} + \frac{V_{o2} - V_p}{r_{o2}} + g_{m2}(V_{in2} - V_p) = 0 & (3) \end{cases} \Rightarrow (2) + (3) =$$

$$(V_{o1} + V_{o2}) \left( \frac{1}{R_c} + \frac{1}{r_{o1}} \right) = \frac{2V_p}{r_{o1}} + 2g_{m1} V_p \quad (4)$$

placing 4 in (1)  $\Rightarrow$

$$2g_{m1} V_p + \frac{1}{r_{o1}} \left( 2V_p - \frac{1}{\frac{1}{R_c} + \frac{1}{r_{o1}}} \left( \frac{2V_p}{r_{o1}} + 2g_{m1} V_p \right) \right) + \frac{2V_p \times 2}{r_{\pi1}} = 0$$
$$\Rightarrow \underline{V_p = 0}$$

(29)

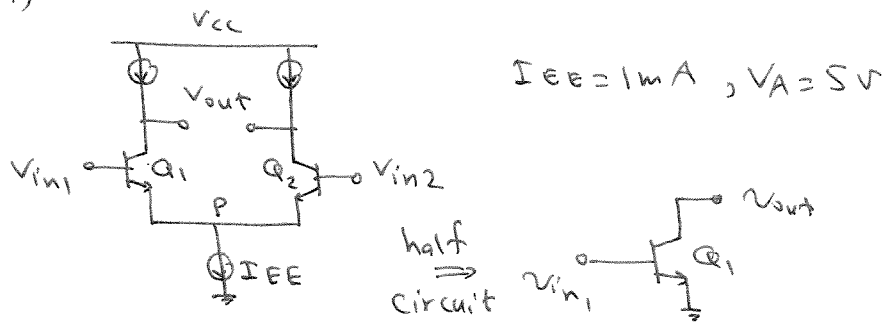


$$A_v = -g_{m1} \cdot r_{o1} = -\frac{I_{EE}}{2V_T} \frac{V_A}{\frac{I_{EE}}{2}} = -\frac{V_A}{V_T} = \frac{-5}{0.026}$$


$$\rightarrow A_v = -192.31$$



(30)

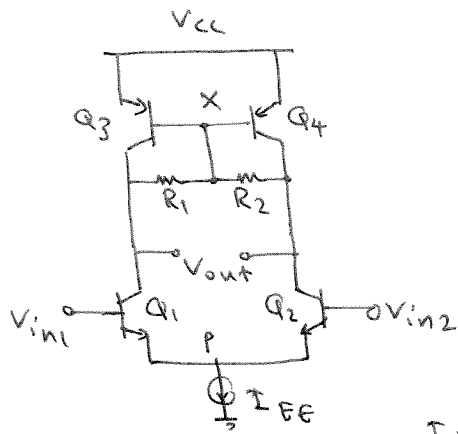

half  
=>  
circuit

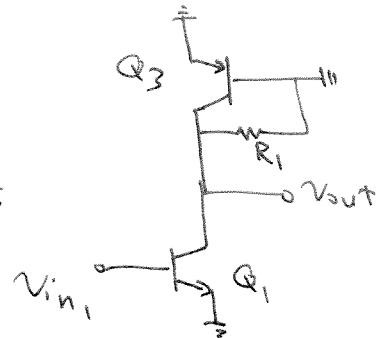

$I_{EE} = 2\text{mA}$  ,  $V_{A,n} = 5\text{V}$  ,  $V_{A,p} = 4\text{V}$

$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$

$$\Rightarrow 50 = \frac{I_{EE}}{2V_T} \left( \frac{V_{A,n}}{\frac{I_{EE}}{2}} \parallel \frac{V_{A,p}}{\frac{I_{EE}}{2}} \parallel R_1 \right) \Rightarrow$$

$$50 = \frac{2}{2 \times 26} \left( \frac{5}{10^{-3}} \parallel \frac{4}{10^{-3}} \parallel R_1 \right) \rightarrow$$

$$R_1 = 3132.53 \Omega$$

(31)

The half circuit is:

$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$


$\Rightarrow$

$$S_0 = \frac{I_{EE}}{2 \times 0.026} \left( \frac{5}{\frac{I_{EE}}{2}} \parallel \frac{4}{\frac{I_{EE}}{2}} \parallel 5K \right) \Rightarrow$$


$$S_0 = \frac{1}{0.052} \left( 10 \parallel 8 \parallel 5 I_{EE} \right) \Rightarrow$$

$\downarrow$        $\downarrow$   
10K      5mA


$$I_{EE} = 1.253 \text{ mA}$$

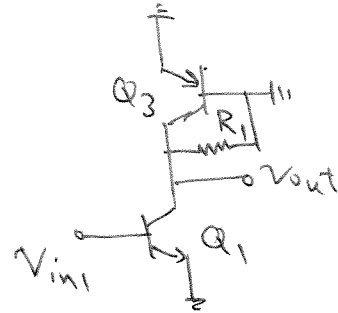


32

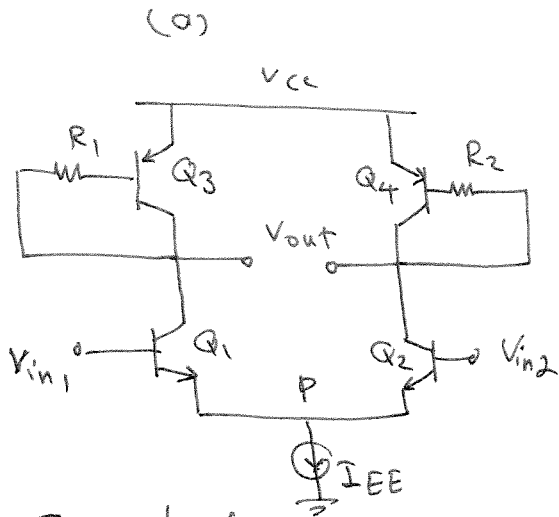

From half circuit concept we have:  $A_v = -g_{m1}(r_{o1} || R_{op})$

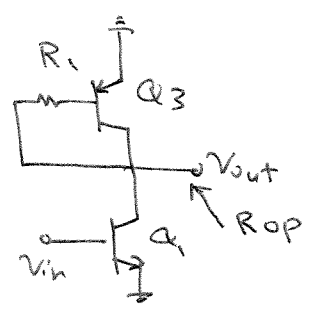

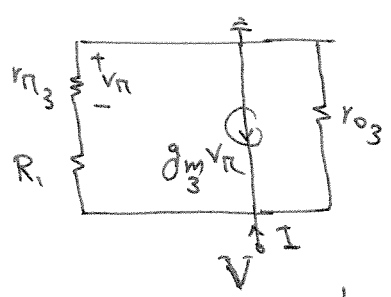To calculate  $R_{op}$ , from small signal model we have:




$$I = \frac{V}{r_{o3}} - g_{m3}V_{\pi} + \frac{V}{R_1 + r_{\pi 3}} = V \left[ \frac{1}{r_{o3}} + \frac{1}{R_1 + r_{\pi 3}} \right] + g_{m3} \frac{r_{\pi 3}}{R_1 + r_{\pi 3}} V$$

$$\rightarrow R_{op} = \frac{V}{I} = r_{o3} || (R_1 + r_{\pi 3}) || \left( \left( 1 + \frac{R_1}{r_{\pi 3}} \right) \frac{1}{g_{m3}} \right)$$


$$\rightarrow A_v = -g_{m1} \left[ r_{o1} || r_{o3} || (R_1 + r_{\pi 3}) || \left( \left( 1 + \frac{R_1}{r_{\pi 3}} \right) \frac{1}{g_{m3}} \right) \right]$$

32


b)

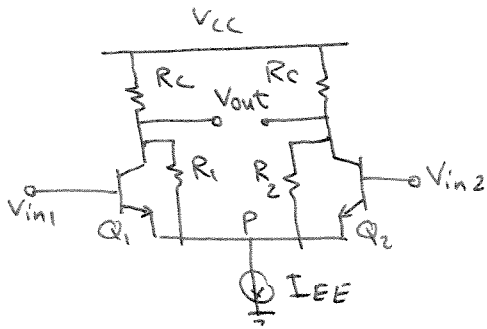


From half circuit concept:

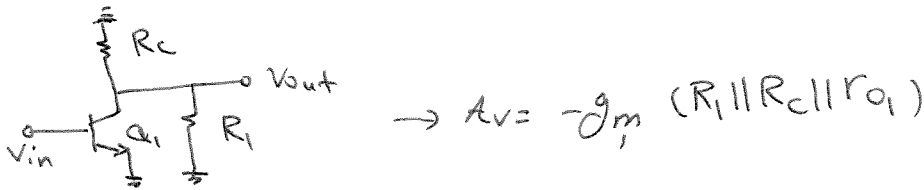

(c)

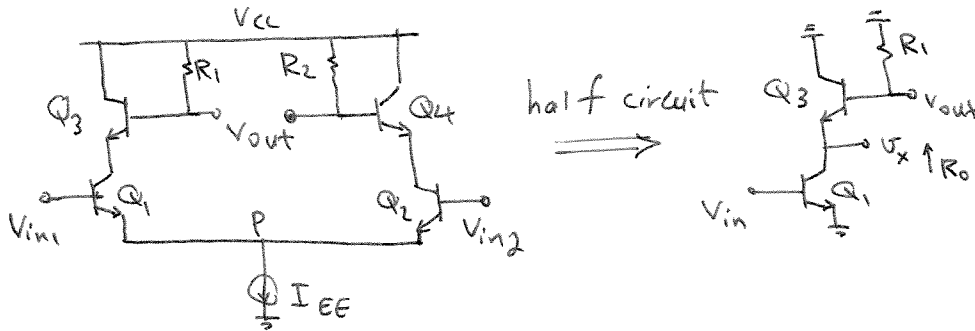

To calculate  $R_o$  we have:

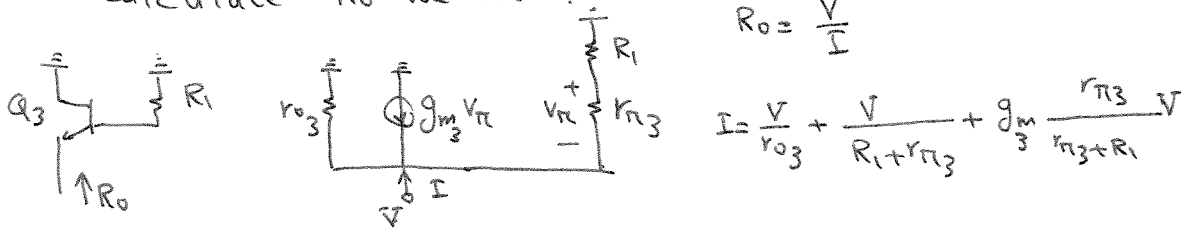

$$R_o = \frac{V}{I}$$


$$I = \frac{V}{r_{o3}} + \frac{V}{R_1 + r_{\pi 3}} + g_{m3} \frac{r_{\pi 3}}{r_{\pi 3} + R_1} V$$

$$\Rightarrow R_o = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left(1 + \frac{R_1}{r_{\pi 3}}\right) \frac{1}{g_{m3}}$$


$$A_v = \frac{v_{out}}{v_{in}} = \frac{v_x}{v_{in}} \frac{v_{out}}{v_x} = -g_{m1} (r_{o1} \parallel R_o) \frac{R_1}{R_1 + r_{\pi 3}}$$

32

(d)

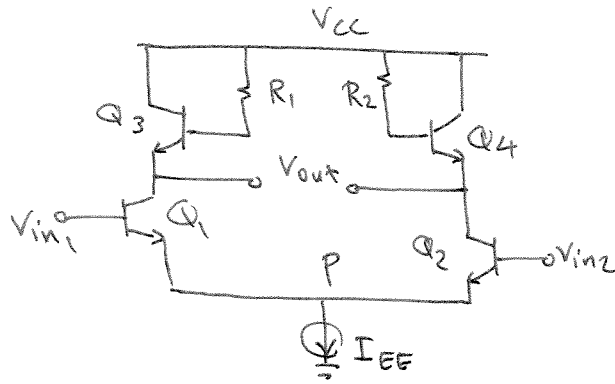

From half circuit concept :

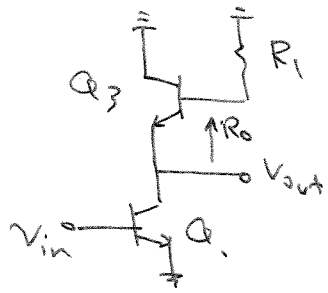


we already proved in part (c) that

$$R_o = r_{o3} \parallel (R_1 + r_{\pi 3}) \parallel \left(1 + \frac{R_1}{r_{\pi 3}}\right) \frac{1}{g_{m3}}$$

$$\rightarrow A_v = \frac{v_{out}}{v_{in}} = -g_{m1} (r_{o1} \parallel R_o)$$

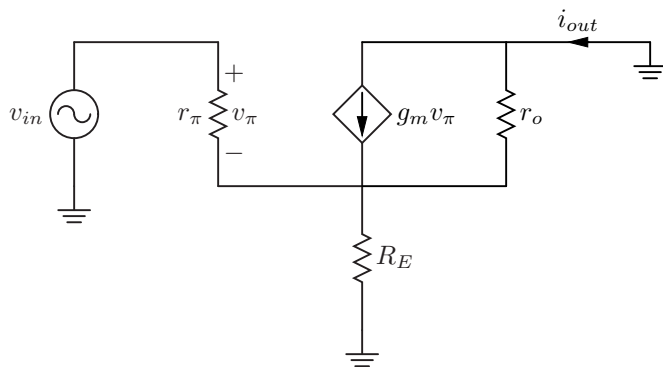10.33 (a) Treating node  $P$  as a virtual ground, we can draw the small-signal model to find  $G_m$ .




$$\begin{aligned}
 i_{out} &= -\frac{v_{\pi}}{r_{\pi}} + \frac{v_{in} - v_{\pi}}{R_E} \\
 v_{\pi} &= v_{in} - (-i_{out} + g_m v_{\pi}) r_o \\
 v_{\pi} (1 + g_m r_o) &= v_{in} + i_{out} r_o \\
 v_{\pi} &= \frac{v_{in} + i_{out} r_o}{1 + g_m r_o} \\
 i_{out} &= -\frac{v_{in} + i_{out} r_o}{r_{\pi} (1 + g_m r_o)} + \frac{v_{in}}{R_E} - \frac{v_{in} + i_{out} r_o}{R_E (1 + g_m r_o)} \\
 i_{out} \left( 1 + \frac{r_o}{r_{\pi} (1 + g_m r_o)} + \frac{r_o}{R_E (1 + g_m r_o)} \right) &= v_{in} \left( \frac{1}{R_E} - \frac{1}{r_{\pi} (1 + g_m r_o)} - \frac{1}{R_E (1 + g_m r_o)} \right) \\
 i_{out} \left( \frac{r_{\pi} R_E (1 + g_m r_o) + r_o (r_{\pi} + R_E)}{r_{\pi} R_E (1 + g_m r_o)} \right) &= v_{in} \left( \frac{r_{\pi} (1 + g_m r_o) - R_E - r_{\pi}}{r_{\pi} R_E (1 + g_m r_o)} \right) \\
 G_m = \frac{i_{out}}{v_{in}} &= \frac{r_{\pi} (1 + g_m r_o) - R_E - r_{\pi}}{r_{\pi} R_E (1 + g_m r_o) + r_o (r_{\pi} + R_E)} \\
 R_{out} &= R_C \parallel [r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)]
 \end{aligned}$$

$$A_v = \boxed{-\frac{r_{\pi} (1 + g_m r_o) - R_E - r_{\pi}}{r_{\pi} R_E (1 + g_m r_o) + r_o (r_{\pi} + R_E)} \{R_C \parallel [r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)]\}}$$


(b) The result is identical to the result from part (a), except  $R_1$  appears in parallel with  $r_o$ .

$$A_v = \boxed{-\frac{r_{\pi} (1 + g_m (r_o \parallel R_1)) - R_E - r_{\pi}}{r_{\pi} R_E (1 + g_m (r_o \parallel R_1)) + (r_o \parallel R_1) (r_{\pi} + R_E)} \{R_C \parallel [(r_o \parallel R_1) + (1 + g_m (r_o \parallel R_1)) (r_{\pi} \parallel R_E)]\}}$$

34

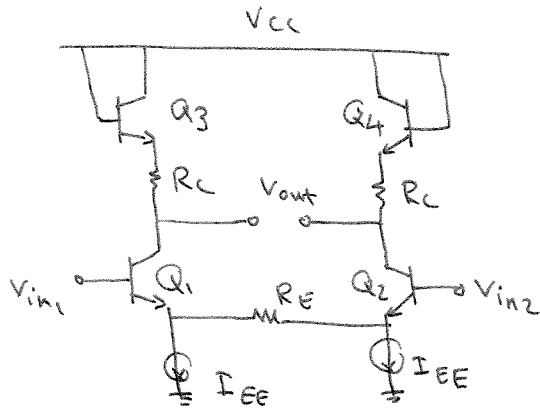

The half circuit is shown as:

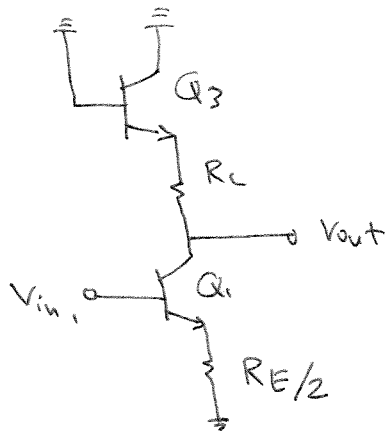


$$a) \quad A_v = \frac{v_{out}}{v_{in1}} = - \frac{R_C + 1/g_{m3}}{R_E/2 + 1/g_{m1}}$$

$$b) \quad \text{if } \frac{R_C}{R_E/2} = A, \text{ then if } \frac{1/g_{m3}}{1/g_{m1}} = A$$

we conclude  $A_v = -A$ . So the circuit is very linear.

35

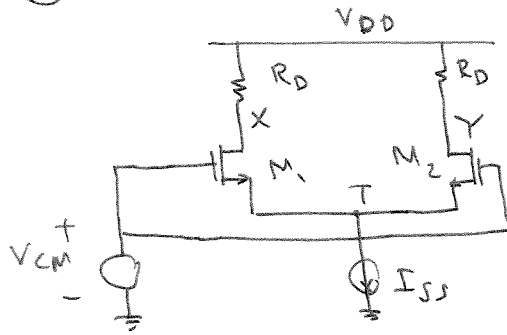

$$V_T = V_{CM} - V_{GS1} = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

(a)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{2W}{L}}}$

The tail voltage increases

(b)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$

The tail voltage decreases

(c)  $V_T = V_{CM} - V_{TH} - \sqrt{\frac{I_{SS}}{\mu_n \frac{C_{ox}}{2} \frac{W}{L}}}$


The tail voltage decreases



10.36

$$\begin{aligned}V_{DD} - \frac{I_{SS}R_D}{2} &> V_{CM} - V_{TH,n} \\V_{DD} &> V_{CM} - V_{TH,n} + \frac{I_{SS}R_D}{2} \\V_{DD} &> \boxed{1\text{ V}}\end{aligned}$$

37

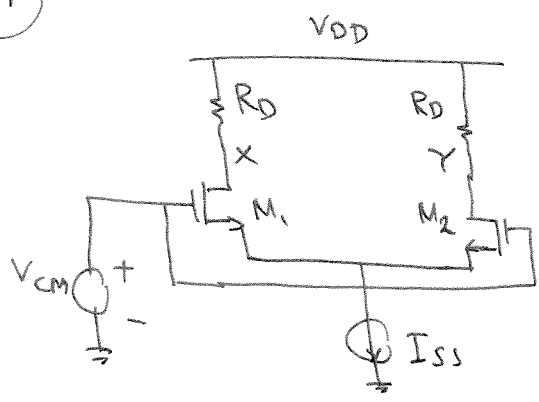

$$V_{GS} - V_{TH} = 200 \text{ mV}$$
$$\mu_n C_{ox} = 100 \text{ } \mu\text{A/V}^2$$
$$\frac{W}{L} = 20/0.18$$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \rightarrow$$

$$0.2 = \sqrt{\frac{I_{SS}}{10^{-4} \times \frac{20}{0.18}}} \rightarrow I_{SS} = 0.44 \text{ mA}$$

10.38 Let  $J_D$  be the current density of a MOSFET, as defined in the problem statement.

$$\begin{aligned} J_D &= \frac{I_D}{W} = \frac{1}{2} \frac{1}{L} \mu_n C_{ox} (V_{GS} - V_{TH})^2 \\ (V_{GS} - V_{TH})_{equil} &= \sqrt{\frac{2I_D}{\frac{W}{L} \mu_n C_{ox}}} \\ &= \sqrt{\frac{2J_D}{\frac{1}{L} \mu_n C_{ox}}} \end{aligned}$$


The equilibrium overdrive voltage increases as the square root of the current density.

10.39 Let  $i_{d1}$ ,  $i_{d2}$ , and  $v_P$  denote the changes in their respective values given a small differential input of  $v_{in}$  ( $+v_{in}$  to  $V_{in1}$  and  $-v_{in}$  to  $V_{in2}$ ).

$$\begin{aligned}i_{d1} &= g_m (v_{in} - v_P) \\i_{d2} &= g_m (-v_{in} - v_P) \\v_P &= (i_{d1} + i_{d2}) R_{SS} \\&= -2g_m v_P R_{SS} \\&\Rightarrow v_P = 0\end{aligned}$$

Note that we can justify the last step by noting that if  $v_P \neq 0$ , then we'd have  $2g_m R_{SS} = -1$ , which makes no sense, since all the values on the left side must be positive. Thus, since the voltage at  $P$  does not change with a small differential input, node  $P$  acts as a virtual ground.

40

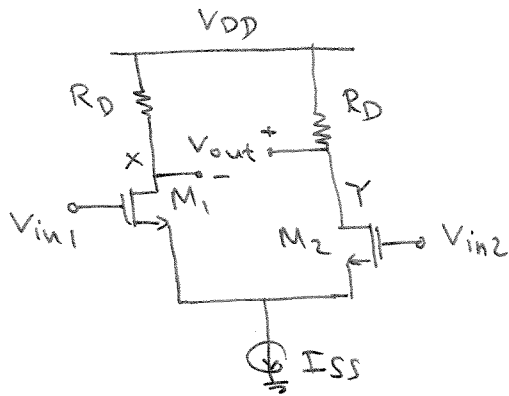

$$V_{in1} = 1.5$$
$$V_{in2} = 0.3$$

$$V_x - V_{TH} > V_{in1} \rightarrow V_{DD} - R_D I_{SS} - V_{TH} > 1.5$$


$$\begin{aligned}
P &= I_{SS}V_{DD} = 2 \text{ mW} \\
I_{SS} &= \boxed{1 \text{ mA}} \\
V_{CM,out} &= V_{DD} - \frac{I_{SS}R_D}{2} = 1.6 \text{ V} \\
R_D &= \boxed{800 \ \Omega} \\
|A_v| &= g_m R_D \\
&= \sqrt{2 \left(\frac{W}{L}\right)_1 \mu_n C_{ox} I_D R_D} \\
&= 5 \\
\left(\frac{W}{L}\right)_1 &= \left(\frac{W}{L}\right)_2 = \boxed{390.625}
\end{aligned}$$

Let's formulate the trade-off between  $V_{DD}$  and  $W/L$ , let's assume we're trying to meet an output common-mode level of  $V_{CM,out}$ . Then we have:

$$\begin{aligned}
I_{SS} &= \frac{P}{V_{DD}} \\
V_{CM,out} &= V_{DD} - \frac{I_{SS}R_D}{2} \\
&= V_{DD} - \frac{PR_D}{2V_{DD}} \\
R_D &= 2V_{DD} \left( \frac{V_{DD} - V_{CM,out}}{P} \right) \\
|A_v| &= g_m R_D \\
&= \sqrt{\frac{W}{L} \mu_n C_{ox} I_{SS} R_D} \\
&= \sqrt{\frac{W}{L} \mu_n C_{ox} \frac{P}{V_{DD}}} \left[ 2V_{DD} \left( \frac{V_{DD} - V_{CM,out}}{P} \right) \right]
\end{aligned}$$

To meet a certain gain,  $W/L$  and  $V_{DD}$  must be adjusted according to the above equation. We can see that if we decrease  $V_{DD}$ , we'd have to increase  $W/L$  in order to meet the same gain.

(42)

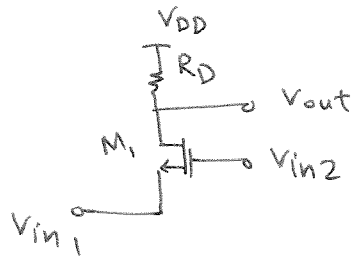

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{in2} - V_{in1} - V_{TH})^2$$

- (1) The current is not an odd function of  $(V_{in2} - V_{in1})$ . Therefore it is not symmetric around  $V_{in1} = V_{in2} [(V_{in1} - V_{in2}) = 0]$ .
- (2) The input impedance seen at  $V_{in1}$  and  $V_{in2}$  are different
- (3) The circuit cannot suppress the supply noise, because there is no differential output available.

(43)

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - 2\sqrt{I_{D1}I_{D2}})$$

(a)

$$I_{D1} = 0 \Rightarrow$$

$$(V_{in1} - V_{in2})^2 = \frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}} \rightarrow V_{in1} - V_{in2} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

This is the minimum differential input voltage to turn  $M_1$  off.

$$(b) I_{D1} = \frac{I_{SS}}{2} \Rightarrow I_{D2} = \frac{I_{SS}}{2}$$

$$(V_{in1} - V_{in2})^2 = \frac{2}{\mu_n C_{ox} \frac{W}{L}} (I_{SS} - I_{SS}) = 0 \rightarrow V_{in1} - V_{in2} = 0$$

This is the equilibrium input case.

$$(c) I_{D1} = I_{SS} \rightarrow I_{D2} = 0$$

$$(V_{in1} - V_{in2})^2 = \frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}} \rightarrow V_{in1} - V_{in2} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

This is the minimum input differential

voltage to turn  $M_2$  off.



(44)

$$I_{D1} = \frac{I_{SS}}{2} - \frac{1}{4} \sqrt{4I_{SS}^2 - \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right]}$$

The analyses which led to the above equation assume that the transistors work in saturation region.

So,

$$-(V_{in1} - V_{in2})_{\max} \leq V_{in1} - V_{in2} \leq (V_{in1} - V_{in2})_{\max}$$

$$(V_{in1} - V_{in2})_{\max} = \sqrt{\frac{2I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$\mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 \leq 2I_{SS} \Rightarrow$$


$$- \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right] \geq 0 \Rightarrow$$

$$\frac{1}{4} \sqrt{4I_{SS}^2 - \left[ \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2})^2 - 2I_{SS} \right]} \geq \frac{1}{2} I_{SS}$$

$$\Rightarrow I_{D1} < 0$$

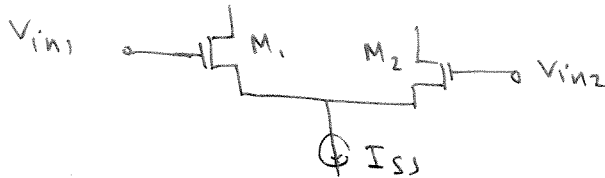(45)

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$



The equilibrium overdrive voltage is:

$$(V_{GS1} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} = V_{OV} \Rightarrow$$

$$\mu_n C_{ox} \frac{W}{L} = \frac{I_{SS}}{V_{OV}^2} \quad \text{therefore}$$

$$I_{D1} - I_{D2} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{OV}^2} \sqrt{\frac{4I_{SS}}{\frac{I_{SS}}{V_{OV}^2}} - (V_{in1} - V_{in2})^2} \Rightarrow$$

$$I_{D1} - I_{D2} = I_{SS} \Rightarrow$$

$$I_{SS} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{OV}^2} \sqrt{4V_{OV}^2 - (V_{in1} - V_{in2})^2}$$

$$\Rightarrow (V_{in1} - V_{in2})^4 - 4V_{OV}^2 (V_{in1} - V_{in2})^2 + 4V_{OV}^4 = 0$$

$$\Rightarrow ((V_{in1} - V_{in2})^2 - 2V_{OV}^2)^2 = 0 \Rightarrow$$

$$V_{in1} - V_{in2} = \sqrt{2} V_{OV} = \sqrt{2} \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$$

(46)

$$I_{D1} - I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in1} - V_{in2}) \sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}$$

$$V_{ov} = (V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow \mu_n C_{ox} \frac{W}{L} = \frac{I_{SS}}{V_{ov}^2}$$

$$\Rightarrow I_{D1} - I_{D2} = \frac{I_{SS}}{2} \frac{(V_{in1} - V_{in2})}{V_{ov}^2} \sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}$$

$$\Rightarrow G_m = \frac{\partial(I_{D1} - I_{D2})}{\partial(V_{in1} - V_{in2})} =$$


$$\frac{I_{SS}}{2V_{ov}^2} \left[ \frac{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} - \frac{(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \right] =$$

$$\frac{I_{SS}}{2V_{ov}^2} \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} =$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} \frac{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - 2(V_{in1} - V_{in2})^2}{\sqrt{\frac{4I_{SS}}{\mu_n C_{ox} \frac{W}{L}} - (V_{in1} - V_{in2})^2}}$$

$$V_{in1} - V_{in2} = 0 \Rightarrow$$
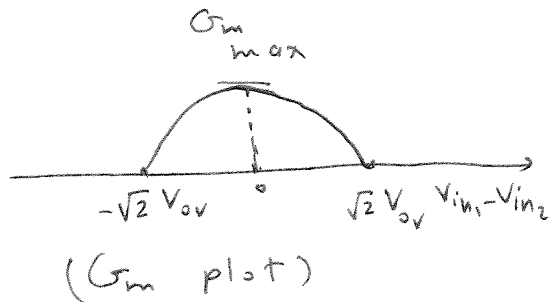
$$G_{m \max} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}}$$



47

From problem 46:

$$G_{m \max} = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} = \sqrt{\frac{I_{SS}}{V_{ov}^2} I_{SS}} = \frac{I_{SS}}{V_{ov}}$$

$$\Rightarrow \text{if } G_m = \frac{1}{2} \frac{I_{SS}}{V_{ov}} \text{ we have}$$

$$\frac{1}{2} \frac{I_{SS}}{V_{ov}} = \frac{I_{SS}}{2 V_{ov}^2} \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \Rightarrow$$

$$V_{ov} = \frac{4V_{ov}^2 - 2(V_{in1} - V_{in2})^2}{\sqrt{4V_{ov}^2 - (V_{in1} - V_{in2})^2}} \Rightarrow$$

$$(4V_{ov}^2 - (V_{in1} - V_{in2})^2) V_{ov}^2 = 16V_{ov}^4 + 4(V_{in1} - V_{in2})^4 - 16V_{ov}^2 (V_{in1} - V_{in2})^2$$

$$\Rightarrow 4(V_{in1} - V_{in2})^4 - 15V_{ov}^2 (V_{in1} - V_{in2})^2 + 12V_{ov}^4 = 0$$

$$\Rightarrow (V_{in1} - V_{in2})^2 = \frac{15V_{ov}^2 \pm \sqrt{225V_{ov}^4 - 192V_{ov}^4}}{8} =$$

$$\frac{15V_{ov}^2 \pm \sqrt{33} V_{ov}^2}{8}$$


positive sign is not accepted

$$\text{because } (V_{in1} - V_{in2})^2 \leq 2V_{ov}^2 \Rightarrow$$


$$V_{in1} - V_{in2} = \pm \sqrt{\frac{15 - \sqrt{33}}{8}} V_{ov} = \pm 1.0756 V_{ov}$$

48-

$$I_D = \gamma (V_{GS} - V_{TH})^3$$

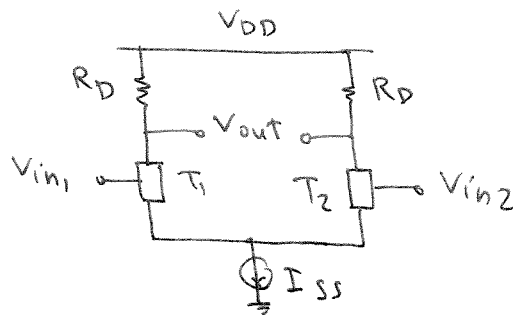

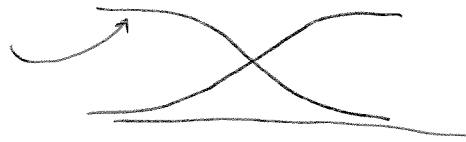(a) The characteristic of  $I_{D1} - I_{D2}$  vs.  $V_{in1} - V_{in2}$  is similar to the standard CMOS differential pair, because it has saturation part.



(b)  $I_D = \frac{I_{SS}}{2} = \gamma (V_{GS} - V_{TH})^3 \Rightarrow$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt[3]{\frac{I_{SS}}{2\gamma}}$$

(c)  $I_{D1} = I_{SS} = \gamma (V_{GS1} - V_{TH})^3 \Rightarrow V_{GS1} - V_{TH} = \sqrt[3]{\frac{I_{SS}}{\gamma}}$

$I_{D2} = 0 = \gamma (V_{GS2} - V_{TH})^3 \Rightarrow V_{GS2} - V_{TH} = 0$


$\Rightarrow V_{GS1} - V_{GS2} = V_{in1} - V_{in2} = \sqrt[3]{\frac{I_{SS}}{\gamma}} =$

$$\sqrt[3]{\frac{I_{SS}}{2\gamma}} (V_{GS} - V_{TH})_{\text{equil}}$$

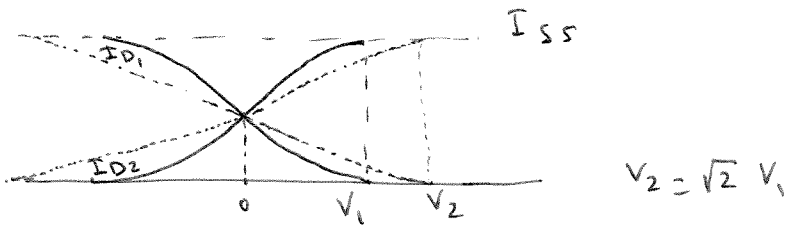(49)

(a)


gate oxide thickness is doubled  $\Rightarrow C_{ox}$  is halved  $\Rightarrow$   
 $(V_{in1} - V_{in2})_{max}$  scales up by  $\sqrt{2}$ .



so all the curves stretch out to the sides by  $\sqrt{2}$  times.

(b) if threshold voltage is halved, nothing will change in the curves. The reason is that the curves depend on  $V_{in1} - V_{in2}$ .

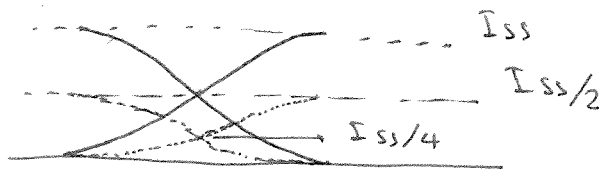
(c) In this case,  $(V_{in1} - V_{in2})_{max}$  does not change so all the curves scale half downward because  $I_{SS}$  is halved.




(50)

if mobility falls then  $(V_{in1} - V_{in2})_{max}$  will increase because  $(V_{in1} - V_{in2})_{max} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}}$


So the curves stretch out to the sides.

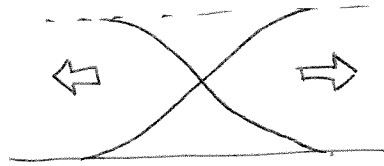

(51)

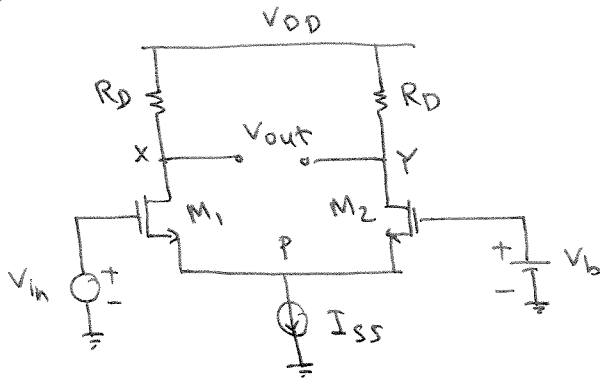


$$g_{m1} = g_{m2} = g_m$$

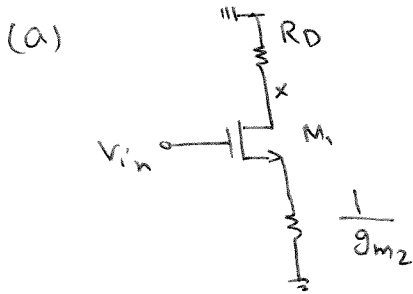

$$v_x = -g_{m1} v_{gs1} R_D =$$

$$-g_{m1} \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in} R_D =$$
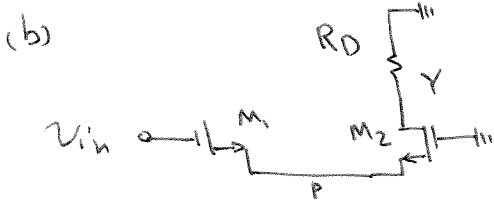
$$-\frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in} = -\frac{g_m}{2} R_D v_{in}$$



$$v_p = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}} v_{in}$$

$$\Rightarrow v_p = \frac{g_{m1}}{g_{m1} + g_{m2}} v_{in} \Rightarrow$$

$$v_y = -g_{m2} v_{gs2} R_D = g_{m2} v_p R_D = \frac{g_{m1} g_{m2}}{g_{m1} + g_{m2}} R_D v_{in}$$


$$\rightarrow v_y = \frac{g_m}{2} R_D v_{in}$$

(c)  $\frac{v_x - v_y}{v_{in}} = -g_m R_D$  This value is equal to the gain of the differential amplifier.




(52)

(a)

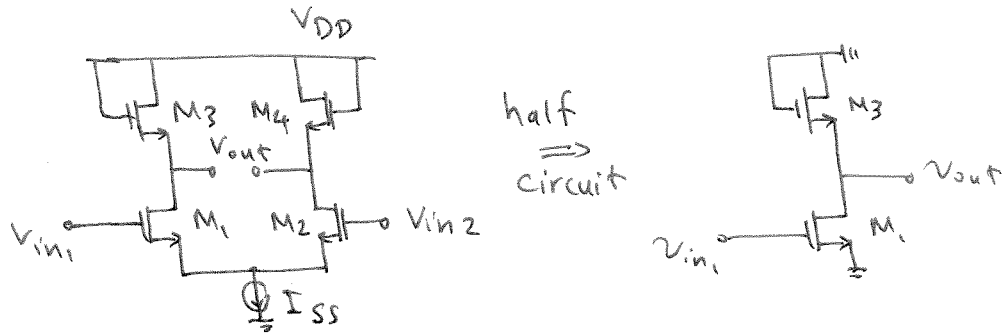


$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel \frac{1}{g_{m3}})$$

(b)

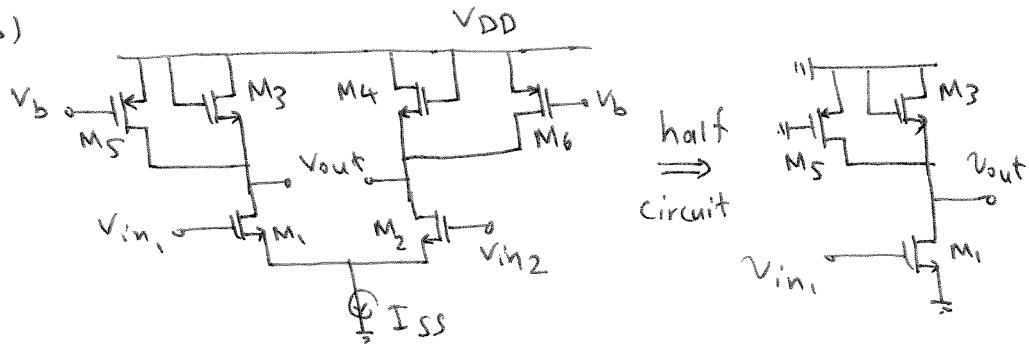


$$A_v = -g_{m1} (r_{o1} \parallel r_{o5} \parallel \frac{1}{g_{m3}} \parallel r_{o3})$$

(c)

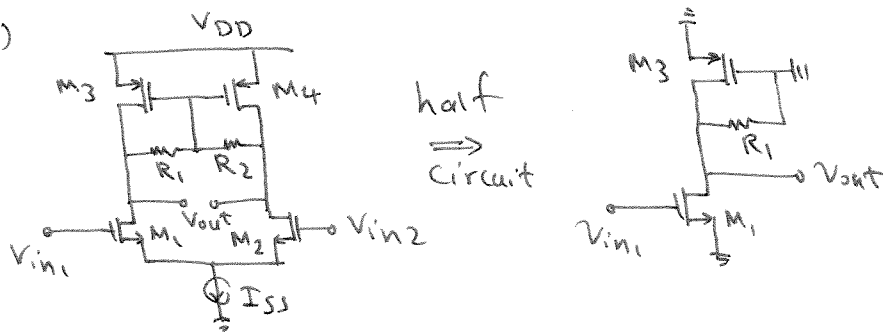


$$A_v = -g_{m1} (r_{o1} \parallel r_{o3} \parallel R_1)$$

(53)

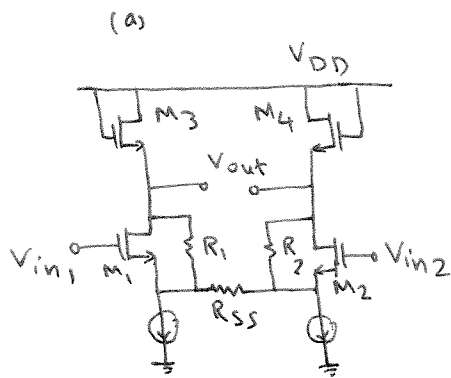


half  
⇒  
circuit

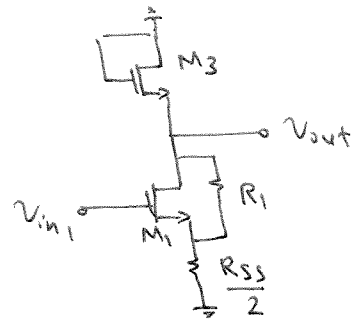

$$R_{out} = \left( r_{o3} \parallel \frac{1}{g_{m3}} \right) \parallel \left( g_{m1} (R_1 \parallel r_{o1}) \frac{R_{SS}}{2} + \frac{R_{SS}}{2} + R_1 \parallel r_{o1} \right)$$

To calculate  $G_m$ :

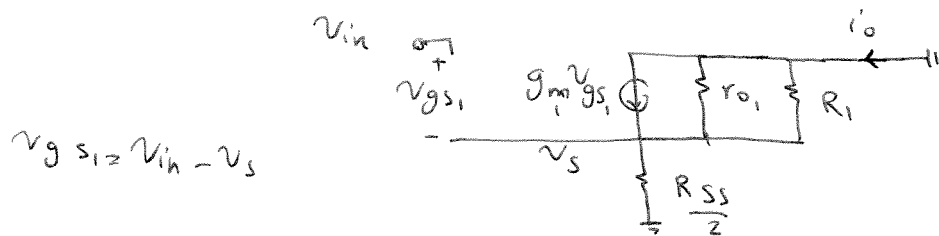

$$v_{gs1} = v_{in} - v_s$$

$$\frac{v_s}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}} + g_{m1} v_s = g_{m1} v_{in} \Rightarrow v_s = \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}}}$$


$$i_o = + \frac{v_s}{\frac{R_{SS}}{2}} = + \frac{1}{\frac{R_{SS}}{2}} \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}} \Rightarrow$$

$$G_m = \frac{i_o}{v_{in}} = + \frac{2 g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel R_1 \parallel r_{o1}}}}$$


$$A_v = -G_m R_{out}$$

53

(b)

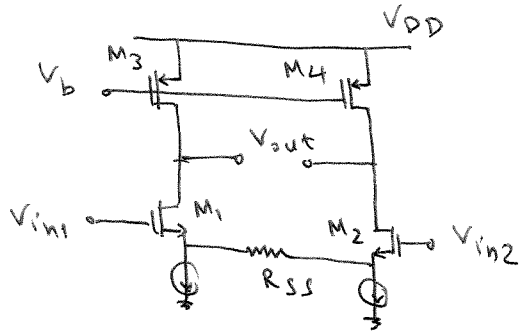


half  
 $\Rightarrow$   
 circuit

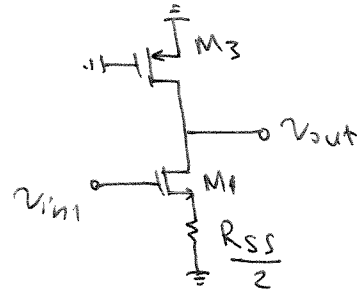

$$R_{out} = r_{o3} \parallel \left( g_{m1} r_{o1} \frac{R_{SS}}{2} + r_{o1} + \frac{R_{SS}}{2} \right)$$


To calculate  $G_m$ :

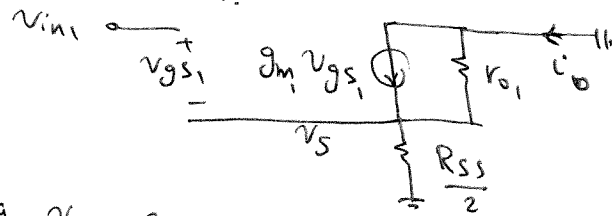


$$\frac{v_s}{r_{o1} \parallel \frac{R_{SS}}{2}} + g_{m1} v_s = g_{m1} v_{in} \Rightarrow v_s = \frac{g_{m1} v_{in}}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}}$$

$$G_m = \frac{i_o}{v_{in}} = + \frac{v_s}{\frac{R_{SS}}{2}} \frac{1}{v_{in}} = + \frac{2g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}}$$

$$\rightarrow A_{v3} = -G_m R_{out}$$

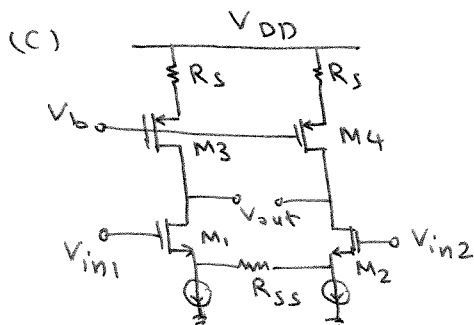

half  
 $\Rightarrow$   
 circuit

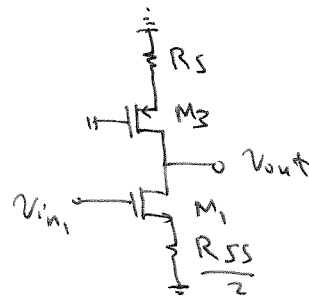


$$R_{out} = (g_{m3} r_{o3} R_s + r_{o3} + R_s) \parallel \left( g_{m1} r_{o1} \frac{R_{SS}}{2} + r_{o1} + \frac{R_{SS}}{2} \right)$$


$G_m$  for this circuit is equal to the one for part (b) so:

$$G_m = + \frac{2g_{m1}}{R_{SS}} \frac{1}{g_{m1} + \frac{1}{\frac{R_{SS}}{2} \parallel r_{o1}}} \Rightarrow A_{v2} = -G_m R_{out}$$

(54)

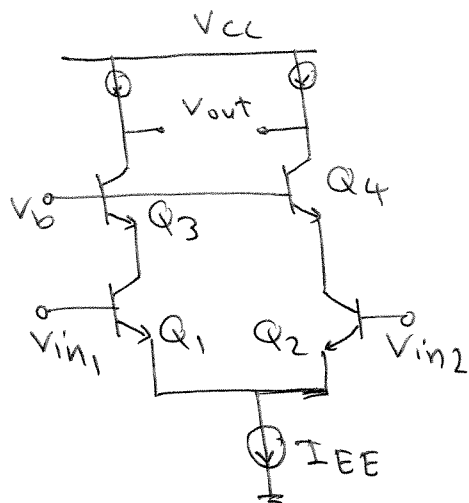

half  
=>  
circuit

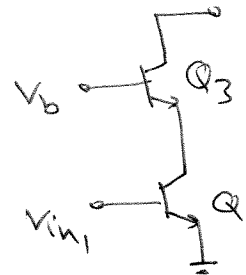

$$A_v = 4000$$
$$\beta = 100$$

$$A_v = -g_{m1} \left[ g_{m3} (r_{o1} \parallel r_{\pi 3}) r_{o3} + r_{o3} + r_{o1} \parallel r_{\pi 3} \right]$$

$$g_{m_{1-4}} = \frac{I_{EE}}{2V_T} \quad r_{o_{1-4}} = \frac{2V_A}{I_{EE}} \quad r_{\pi 3} = \frac{2V_T \beta}{I_{EE}}$$

$$4000 = \frac{I_{EE}}{2V_T} \left[ \frac{I_{EE}}{2V_T} \left( \frac{2V_A}{I_{EE}} \parallel \frac{2V_T \beta}{I_{EE}} \right) \frac{2V_A}{I_{EE}} + \frac{2V_A}{I_{EE}} + \left( \frac{2V_A}{I_{EE}} \parallel \frac{2V_T \beta}{I_{EE}} \right) \right]$$

$$\Rightarrow 4000 = \frac{1}{2V_T} \left[ \frac{V_A}{V_T} (2V_A \parallel 2V_T \beta) + 2V_A + (2V_A \parallel 2V_T \beta) \right] \Rightarrow$$


$$4000 = \frac{1}{V_T} \left[ \frac{V_A}{V_T} (V_A \parallel \beta V_T) + V_A + (V_A \parallel \beta V_T) \right] \Rightarrow$$

$$4000 = \frac{1}{V_T} \left[ \frac{\beta V_A^2}{\beta V_T + V_A} + V_A + \frac{\beta V_A V_T}{\beta V_T + V_A} \right] \Rightarrow$$

$$4000 = \frac{1}{0.026} \left[ \frac{100 V_A^2}{2.6 + V_A} + V_A + \frac{2.6 V_A}{2.6 + V_A} \right] \Rightarrow$$

$$V_A = 2.197$$

10.55 Let's draw the half circuit.

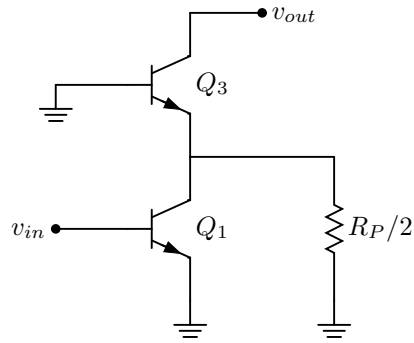


$$G_m = g_{m1} \frac{\frac{R_P}{2} \parallel r_{o1} \parallel r_{\pi 3}}{\frac{R_P}{2} \parallel r_{o1} \parallel r_{\pi 3} + \frac{1}{g_{m3}}}$$

$$= g_{m1} \frac{g_{m3} \left( \frac{R_P}{2} \parallel r_{o1} \parallel r_{\pi 3} \right)}{1 + g_{m3} \left( \frac{R_P}{2} \parallel r_{o1} \parallel r_{\pi 3} \right)}$$

$$R_{out} = r_{o3} + (1 + g_{m3} r_{o3}) \left( r_{\pi 3} \parallel \frac{R_P}{2} \parallel r_{o1} \right)$$


$$A_v = \boxed{-g_{m1} \frac{g_{m3} \left( \frac{R_P}{2} \parallel r_{o1} \parallel r_{\pi 3} \right)}{1 + g_{m3} \left( \frac{R_P}{2} \parallel r_{o1} \parallel r_{\pi 3} \right)} \left\{ r_{o3} + (1 + g_{m3} r_{o3}) \left( r_{\pi 3} \parallel \frac{R_P}{2} \parallel r_{o1} \right) \right\}}$$

(56)

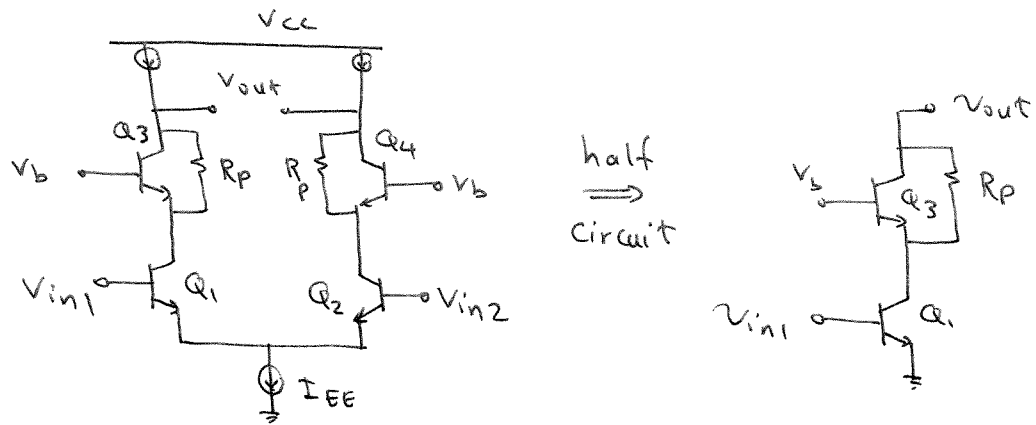


$$A_v = -g_{m_1} (g_{m_3} (r_{o_3} \parallel R_P) (r_{o_1} \parallel r_{\pi_3}) + (r_{o_3} \parallel R_P) + (r_{o_1} \parallel r_{\pi_3}))$$

(57)

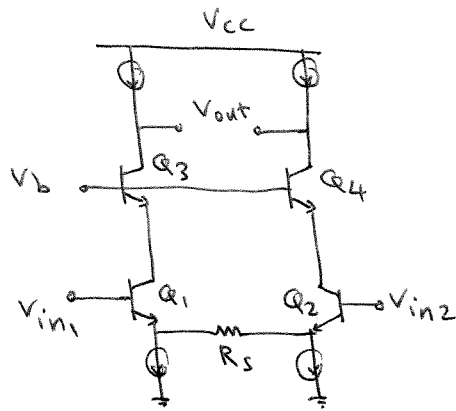

half  
⇒  
circuit

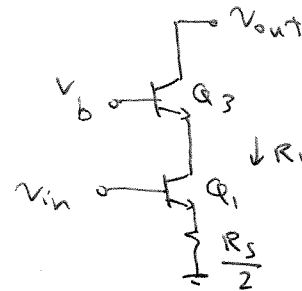


$$R_1 = g_{m1} r_{o1} \left( \frac{R_s}{2} \parallel r_{\pi 1} \right) + r_{o1} + \frac{R_s}{2} \parallel r_{\pi 1}$$

$$R_{out} = g_{m3} r_{o3} (R_1 \parallel r_{\pi 3}) + r_{o3} + (R_1 \parallel r_{\pi 3})$$

To calculate  $G_m$ :

$$v_{\pi 1} \approx \frac{1}{g_{m1}} \frac{1}{\frac{1}{g_{m1}} + \frac{R_s}{2}} v_{in}$$

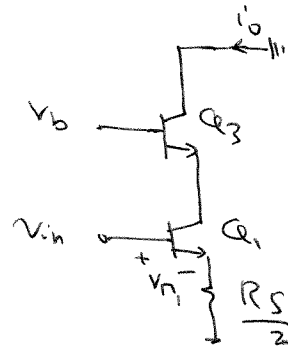
$$= \frac{1}{1 + g_{m1} \frac{R_s}{2}} v_{in}$$




$$G_m = \frac{i_o}{v_{in}} = +g_{m1} \frac{v_{\pi 1}}{v_{in}} = \frac{+g_{m1}}{1 + g_{m1} \frac{R_s}{2}}$$

$$A_v = -G_m R_{out}$$

(58)

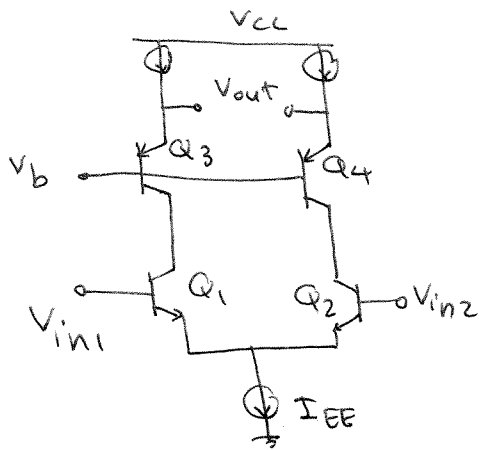


half  
=>  
Circuit

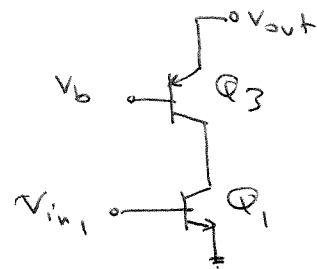

To calculate Rout

$$v_{\pi 3} = v_t$$

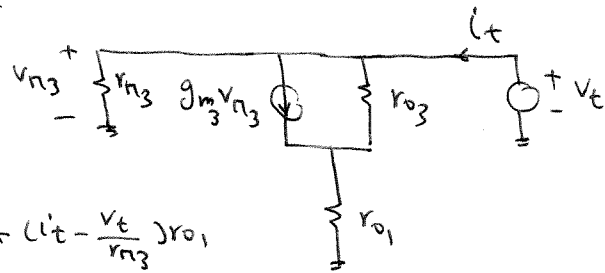

$$v_t = (i_t - g_{m3} v_t - \frac{v_t}{r_{\pi 3}}) r_{o3} + (i_t - \frac{v_t}{r_{\pi 3}}) r_{o1}$$

$$\rightarrow v_t \left( 1 + g_{m3} r_{o3} + \frac{r_{o3}}{r_{\pi 3}} + \frac{r_{o1}}{r_{\pi 3}} \right) = i_t (r_{o1} + r_{o3})$$

$$\rightarrow \frac{v_t}{i_t} = \frac{r_{o1} + r_{o3}}{1 + g_{m3} r_{o3} + \frac{g_{m3} r_{o3}}{\beta_3} + \frac{g_{m3} r_{o1}}{\beta_3}} = R_{out} \rightarrow$$


$$R_{out} \approx \frac{r_{o1} + r_{o3}}{g_{m3} r_{o3}}$$

$$G_m = +g_{m1} \Rightarrow$$


$$A_v \approx -G_m R_{out} \approx -g_{m1} \frac{r_{o1} + r_{o3}}{g_{m3} r_{o3}}$$



(59)

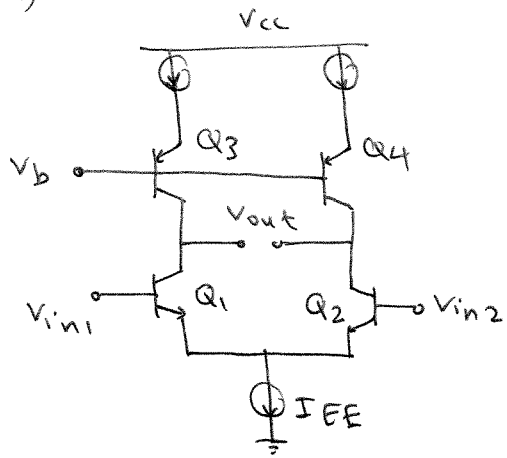

half  
 $\Rightarrow$   
circuit

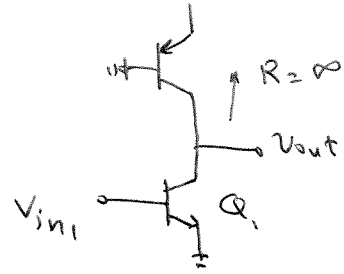

$$A_v = -g_{m1} R_{o1}$$

10.60 Assume  $I_C = \frac{I_{EE}}{2}$  for all of the transistors (since  $\beta \gg 1$ ).



$$\begin{aligned}
 A_v &= -g_{m1} \{ [r_{o3} + (1 + g_{m3}r_{o3})(r_{\pi3} \parallel r_{o1})] \parallel [r_{o5} + (1 + g_{m5}r_{o5})(r_{\pi5} \parallel r_{o7})] \} \\
 &= -\frac{1}{V_T} \frac{ \left[ V_{A,n} + \left( 1 + \frac{V_{A,n}}{V_T} \right) \frac{\beta_n V_T V_{A,n}}{\beta_n V_T + V_{A,n}} \right] \left[ V_{A,p} + \left( 1 + \frac{V_{A,p}}{V_T} \right) \frac{\beta_p V_T V_{A,p}}{\beta_p V_T + V_{A,p}} \right] }{ \left[ V_{A,n} + \left( 1 + \frac{V_{A,n}}{V_T} \right) \frac{\beta_n V_T V_{A,n}}{\beta_n V_T + V_{A,n}} \right] + \left[ V_{A,p} + \left( 1 + \frac{V_{A,p}}{V_T} \right) \frac{\beta_p V_T V_{A,p}}{\beta_p V_T + V_{A,p}} \right] } \\
 &= -800 \\
 V_{A,n} &= \boxed{2.16 \text{ V}} \\
 V_{A,p} &= \boxed{1.08 \text{ V}}
 \end{aligned}$$

10.61

$$A_v = \boxed{-g_{m1} \left\{ [r_{o3} + (1 + g_{m3}r_{o3})(r_{\pi3} \parallel r_{o1})] \parallel \left[ r_{o5} + (1 + g_{m5}r_{o5}) \left( r_{\pi5} \parallel \frac{1}{g_{m7}} \parallel r_{\pi7} \parallel r_{o7} \right) \right] \right\}}$$

This topology is not a telescopic cascode. The use of NPN transistors for  $Q_7$  and  $Q_8$  drops the output resistance of the structure from that of the typical telescopic cascode.

(62)

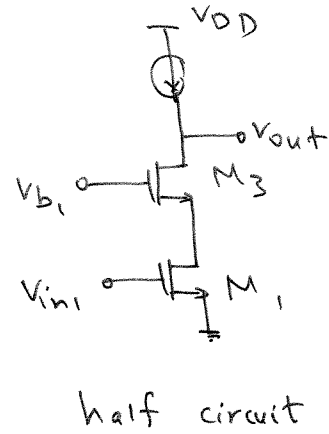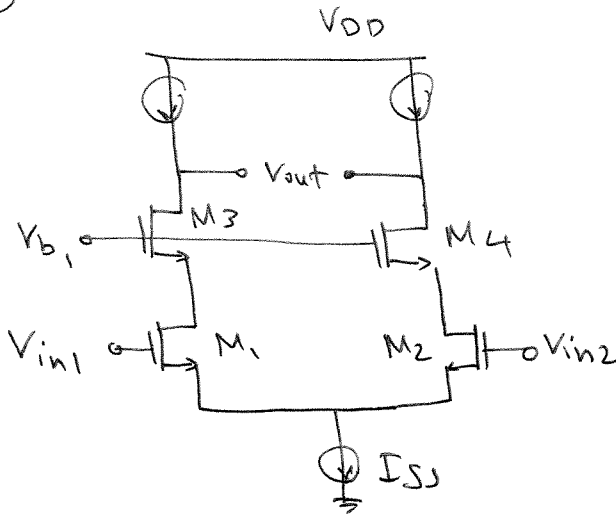

$$A_v = 300, \quad W/L = \frac{20}{0.18}, \quad \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$
$$\lambda = 0.1 \text{ V}^{-1}$$

$$A_v \approx -g_{m3} r_{o3} g_{m1} r_{o1}$$

$$g_{m1} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \frac{I_{SS}}{2}} \quad g_{m3} = \sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_3 \frac{I_{SS}}{2}}$$

$$\rightarrow g_{m1} = g_{m3} = \sqrt{10^{-4} \frac{20}{0.18} I_{SS}}$$



$$r_{o1} = \frac{1}{\lambda \frac{I_{SS}}{2}}, \quad r_{o3} = \frac{1}{\lambda \frac{I_{SS}}{2}} \rightarrow r_{o1} = r_{o3} = \frac{20}{I_{SS}}$$

So:

$$300 = \left(10^{-4} \frac{20}{0.18} I_{SS}\right) \frac{400}{I_{SS}} \Rightarrow$$

$$I_{SS} = 14.815 \text{ mA}$$

63

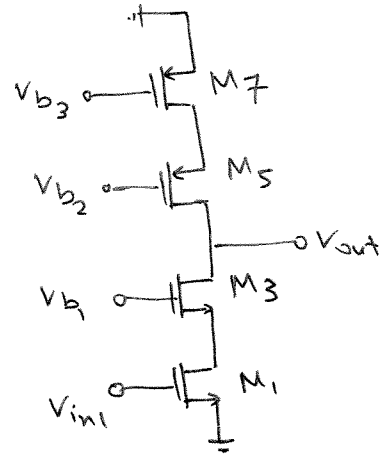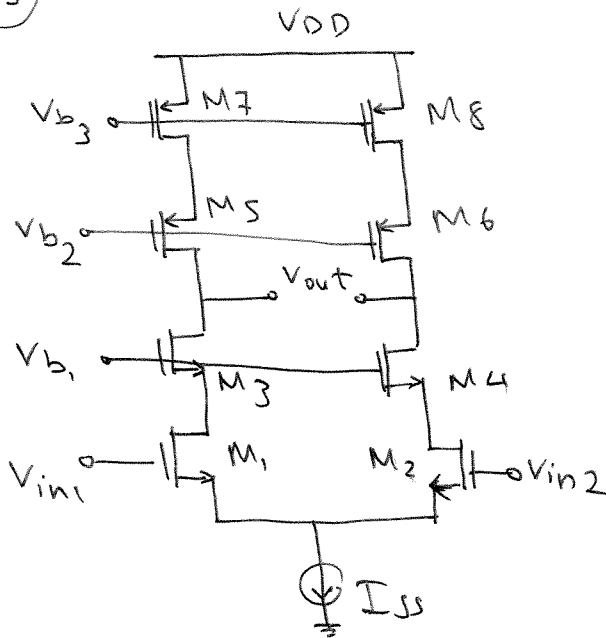

$A_v = 200$ ,  $I_{SS} = 1\text{mA}$ ,  $\mu_n C_{ox} = 100 \mu\text{A/V}^2$   
 $\mu_p C_{ox} = 50 \mu\text{A/V}^2$ ,  $\lambda_n = 0.1\text{V}^{-1}$ ,  $\lambda_p = 0.2\text{V}^{-1}$

$(\frac{W}{L})_1 = \dots = (\frac{W}{L})_8 = ?$



$A_v \approx -g_{m1} \left[ (g_{m3} r_{o3} r_{o1}) \parallel (g_{m5} r_{o5} r_{o7}) \right] \Rightarrow$

$200 = \sqrt{\mu_n C_{ox} (\frac{W}{L})_1 I_{SS}} \left[ \left( \sqrt{\mu_n C_{ox} (\frac{W}{L})_3 I_{SS}} \left( \frac{2}{\lambda_n I_{SS}} \right)^2 \right) \parallel \left( \sqrt{\mu_p C_{ox} (\frac{W}{L})_5 I_{SS}} \left( \frac{2}{\lambda_p I_{SS}} \right)^2 \right) \right]$

$\Rightarrow 200 = \sqrt{10^{-4} (\frac{W}{L})_1 10^{-3}} \left[ \left( \sqrt{10^{-4} (\frac{W}{L})_3 10^{-3}} \left( \frac{20}{10^{-3}} \right)^2 \right) \parallel \left( \sqrt{0.5 \times 10^{-4} (\frac{W}{L})_5 10^{-3}} \left( \frac{10}{10^{-3}} \right)^2 \right) \right]$


$\Rightarrow \frac{W}{L} = 33.28$

(64)

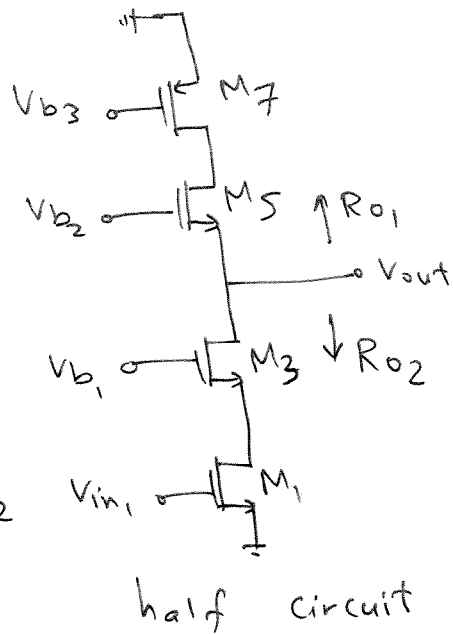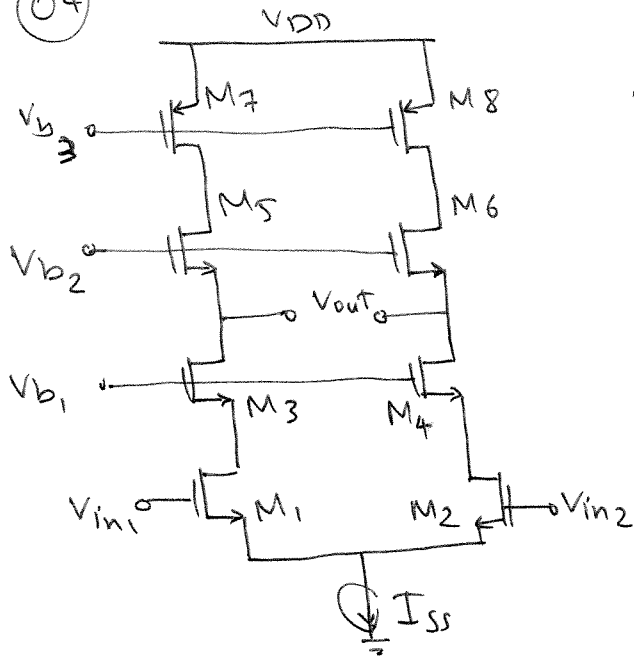

$$R_{o2} = g_{m3} r_{o3} r_{o1} + r_{o1} + r_{o3}$$

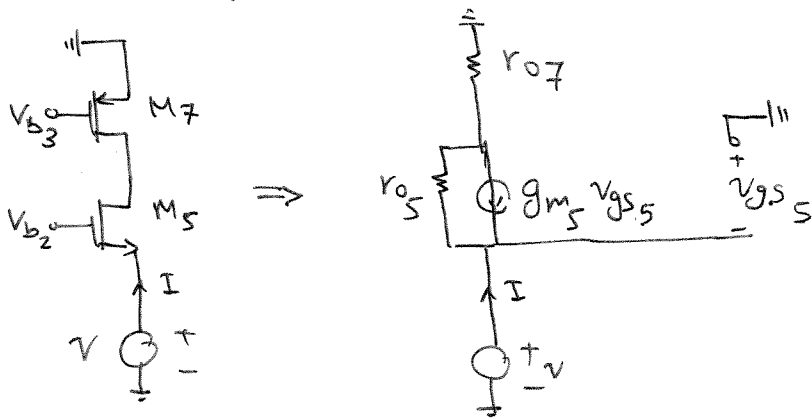To calculate  $R_{o1}$ , using the small signal model we have:






$$v_{gs5} = -v \rightarrow g_{m5} v_{gs5} = -g_{m5} v$$

From KVL: 
$$v = r_{o5} (I - g_{m5} v) + r_{o7} I$$

$$\rightarrow \frac{v}{I} = R_{o1} = \frac{r_{o5} + r_{o7}}{1 + g_{m5} r_{o5}} \Rightarrow A_v = -g_{m1} (R_{o1} \parallel R_{o2})$$


(65)

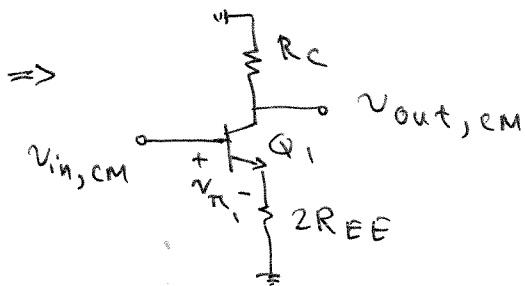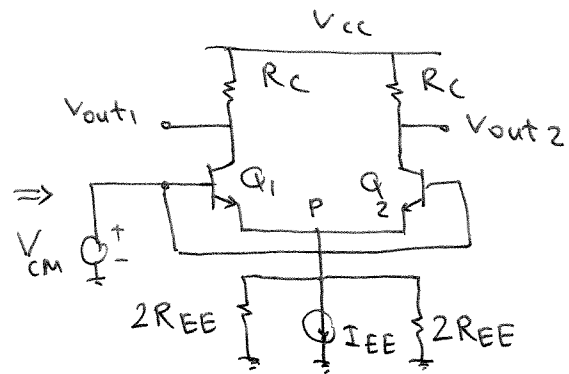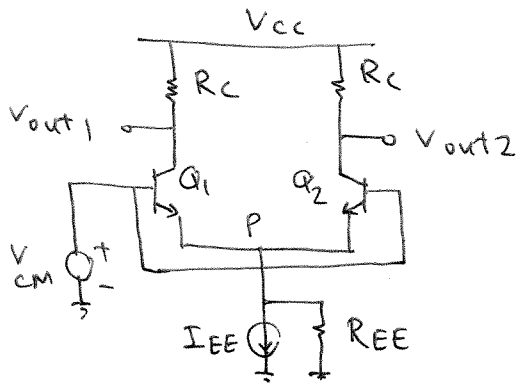

$$v_{out,cm} = -g_{m1} v_{\pi1} R_c = -g_{m1} R_c \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + 2R_{EE}} v_{in,cm}$$

$$\Rightarrow \frac{v_{out,cm}}{v_{in,cm}} = -\frac{g_{m1} R_c}{1 + 2R_{EE} g_{m1}} = -\frac{\frac{R_c}{2}}{R_{EE} + \frac{1}{2g_{m1}}}$$

66

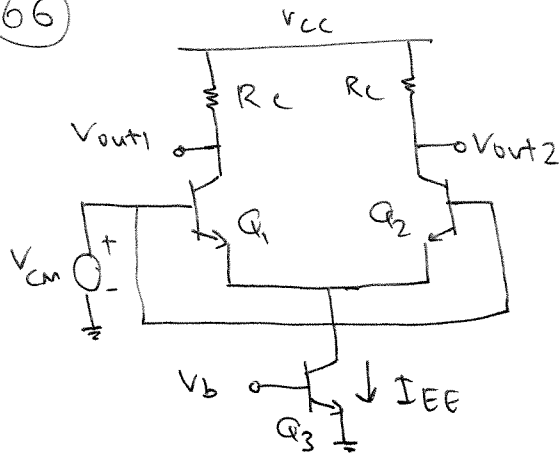


$$A_{cm} = \frac{\Delta V_{out, CM}}{\Delta V_{in, CM}} = \frac{R_c/2}{\frac{1}{2g_m} + r_{o3}} \Rightarrow$$

$$A_{cm} \leq 0.01 \Rightarrow \frac{R_c/2}{\frac{1}{2 \frac{I_{EE}}{2V_T}} + \frac{V_A}{I_{EE}}} < 0.01 \Rightarrow$$


$$\frac{R_c I_{EE}}{2 (V_A + V_T)} < 0.01 \Rightarrow R_c I_{EE} < 0.02 (V_A + V_T)$$



67

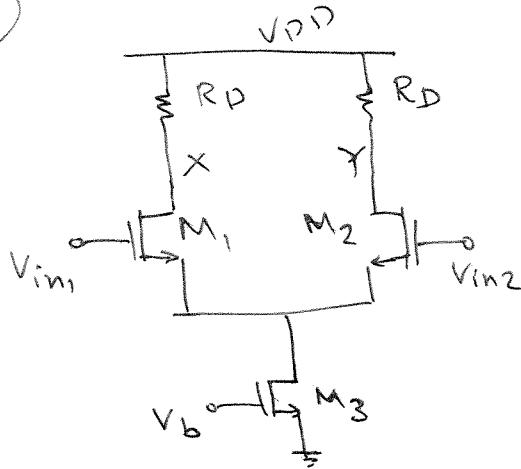

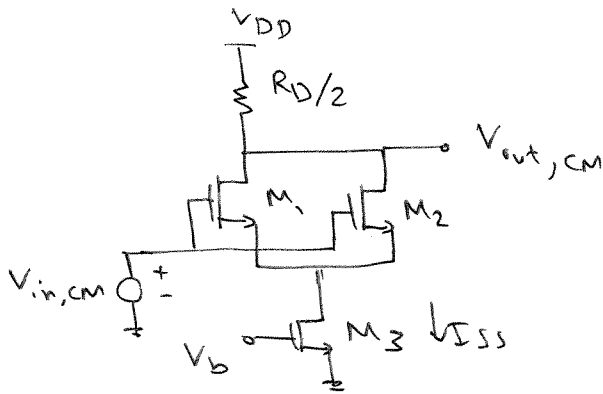The same value for the inputs common-mode leads to the following circuit:



$$g_{m1} = g_{m2} = \frac{2 I_{SS}/2}{(V_{GS} - V_{TH})_{eq}}$$


$$= \frac{I_{SS}}{(V_{GS} - V_{TH})_{eq}}$$

$$\frac{\Delta V_{out, CM}}{\Delta V_{in, CM}} = - \frac{R_D/2}{\frac{1}{2g_{m1}} + r_{o3}}$$

$$= \frac{- R_D}{\frac{1}{g_{m1}} + 2r_{o3}} = \frac{- R_D}{\frac{(V_{GS} - V_{TH})_{eq}}{I_{SS}} + \frac{2}{\lambda I_{SS}}} \Rightarrow$$

$$A_{CM} = - \frac{R_D I_{SS}}{\frac{2}{\lambda} + (V_{GS} - V_{TH})_{eq}}$$

68

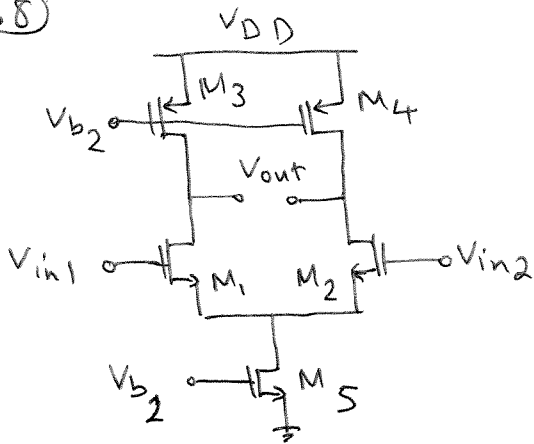


$$\lambda > 0, g_m r_o \gg 1$$

$$r_{o3} = r_{o4}$$

$$r_{o1} = r_{o2}$$

$$g_{m1} = g_{m2}$$

For the common mode input we have:

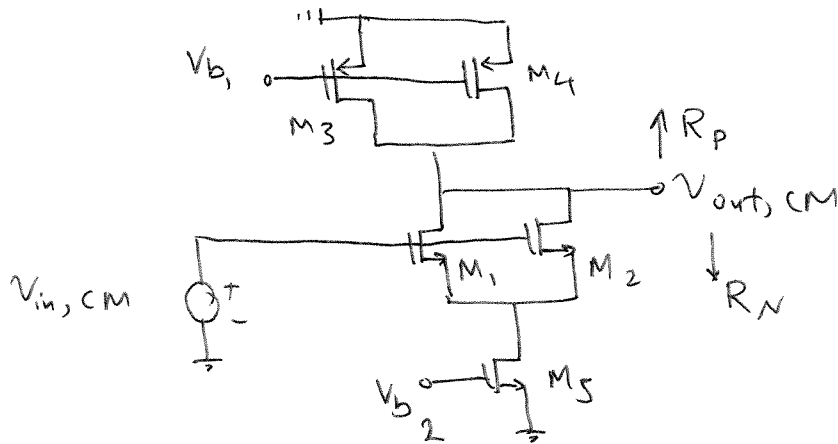


$$R_P = r_{o3} \parallel r_{o4} = \frac{r_{o3}}{2} = \frac{r_{o4}}{2}$$

$$R_N = r_{o5} + \frac{r_{o1}}{2} + 2g_{m1} \frac{r_{o1}}{2} r_{o5} =$$

$$g_{m1} r_{o1} r_{o5} + r_{o5} + \frac{r_{o1}}{2}$$

$$\frac{i_o}{v_{in,CM}} = G_m = \frac{2g_{m1} v_{gs1}}{v_{in,CM}} = 2g_{m1} \frac{\frac{1}{2g_{m1}}}{\frac{1}{2g_{m1}} + r_{o5}}$$
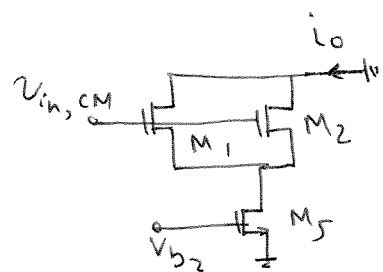
$$\rightarrow G_m = \frac{2g_{m1}}{1 + 2g_{m1} r_{o5}} \approx \frac{1}{r_{o5}}$$



$$\Rightarrow A_{CM} = -G_m R_o$$


$$R_o = R_P \parallel R_N = \frac{r_{o4}}{2} \parallel (g_{m1} r_{o1} r_{o5} + r_{o5} + \frac{r_{o1}}{2})$$

$$\approx \frac{r_{o4}}{2} \parallel g_{m1} r_{o1} r_{o5} \approx \frac{r_{o4}}{2}$$


$$\rightarrow A_{CM} = -\frac{1}{r_{o5}} \frac{r_{o4}}{2} = -\frac{r_{o4}}{2 r_{o5}}$$

(69)

(a)

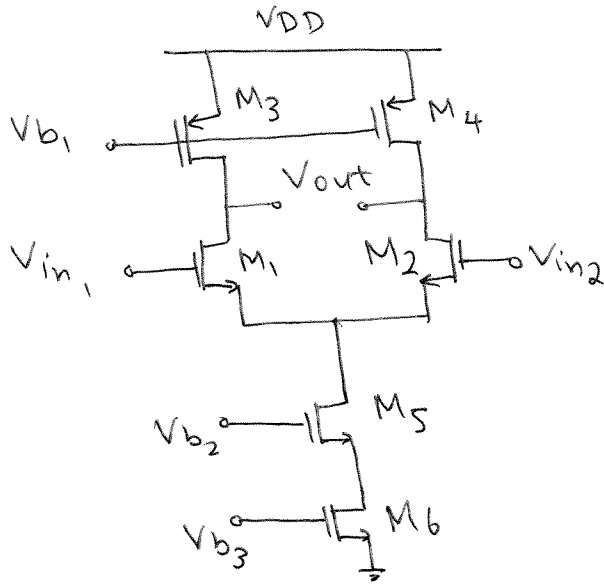

For the common mode input :

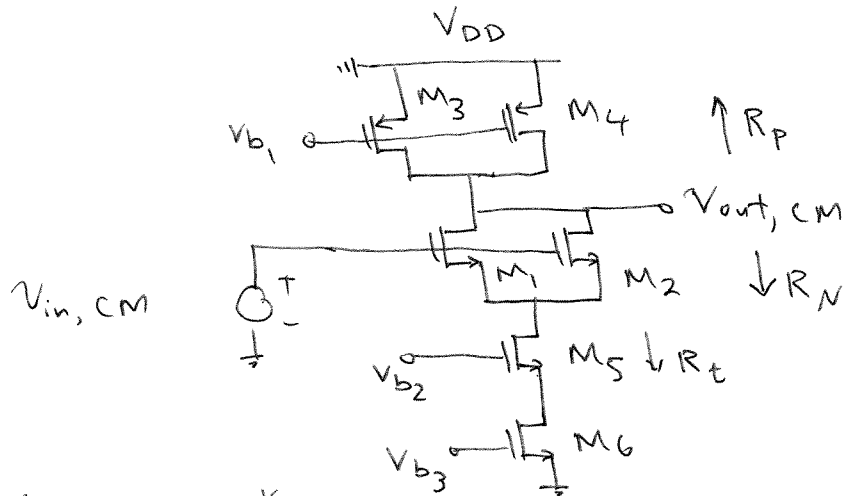

$$R_P = r_{o3} \parallel r_{o4} = \frac{r_{o3}}{2}$$

$$R_N = \frac{r_{o1}}{2} + R_t + 2g_{m1} \frac{r_{o1}}{2} R_t \approx g_{m1} r_{o1} R_t \approx$$


$$g_{m1} r_{o1} g_{m5} r_{o5} r_{o6}$$

$$R_{out} = R_P \parallel R_N = \frac{r_{o3}}{2} \parallel g_{m1} g_{m5} r_{o1} r_{o5} r_{o6} \approx \frac{r_{o3}}{2}$$

To calculate  $G_m$ :

$$G_m = \frac{i_o}{v_{in, CM}} = \frac{2g_{m1} v_{gs1}}{v_{in, CM}}$$
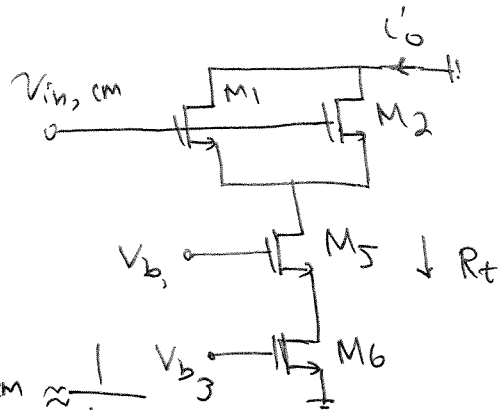
$$= \frac{2g_{m1}}{v_{in, CM}} \frac{\frac{1}{2g_{m1}}}{\frac{1}{2g_{m1}} + R_t} v_{in, CM} \approx \frac{1}{R_t} v_{in, CM}$$




$$\rightarrow A_{CM} = -G_m R_{out} = -\frac{r_{o3}}{2R_t} =$$

$$\frac{r_{o3}}{2g_{m5} r_{o5} r_{o6}}$$

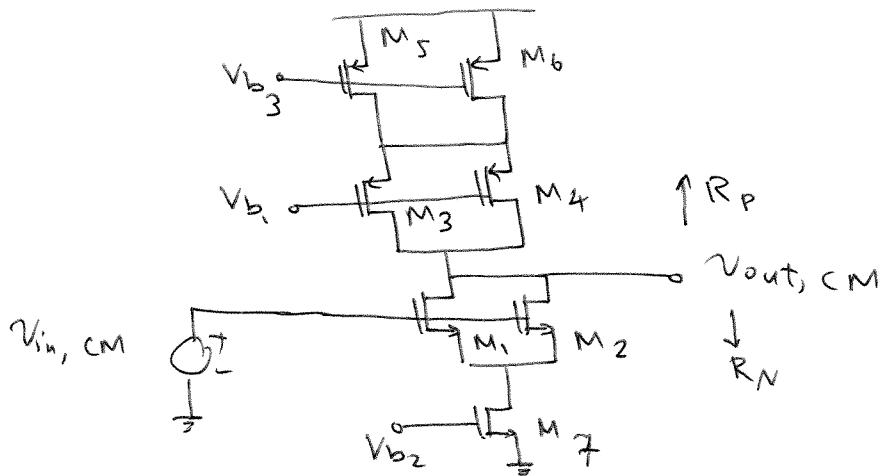(69) (b)

For the common mode input, the circuit is:




$$R_P = 2g_{m3} \frac{r_{o3}}{2} \frac{r_{o5}}{2} + \frac{r_{o3}}{2} + \frac{r_{o5}}{2} \approx \frac{g_{m3} r_{o3} r_{o5}}{2}$$

$$R_N = 2g_{m1} \frac{r_{o1}}{2} r_{o7} + \frac{r_{o1}}{2} + r_{o7} \approx g_{m1} r_{o1} r_{o7}$$

$$R_{out} = R_N \parallel R_P$$

To calculate  $G_m$ :

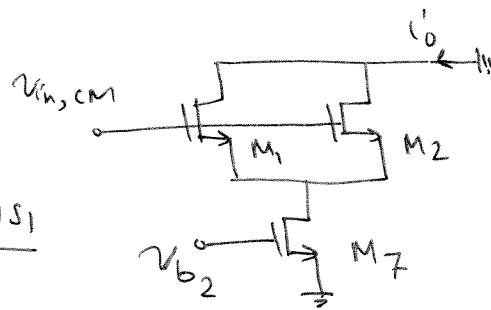


$$G_m = \frac{i'_o}{v_{in,CM}} = \frac{2g_{m1} v_{gs1}}{v_{in,CM}}$$

$$= \frac{2g_{m1}}{v_{in,CM}} \frac{\frac{1}{2g_{m1}} v_{in,CM}}{\frac{1}{2g_{m1}} + r_{o7}} \approx \frac{1}{r_{o7}}$$


$$\rightarrow A_{cm} = -G_m R_{out}$$

(70)


(a)

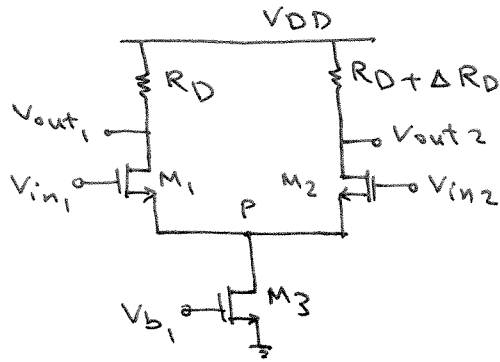

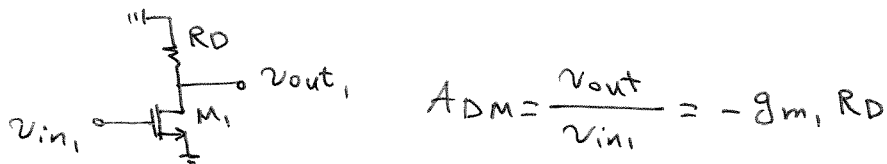To calculate  $A_{DM}$ , using the half circuit:



To calculate  $A_{CM-DM}$  we have:

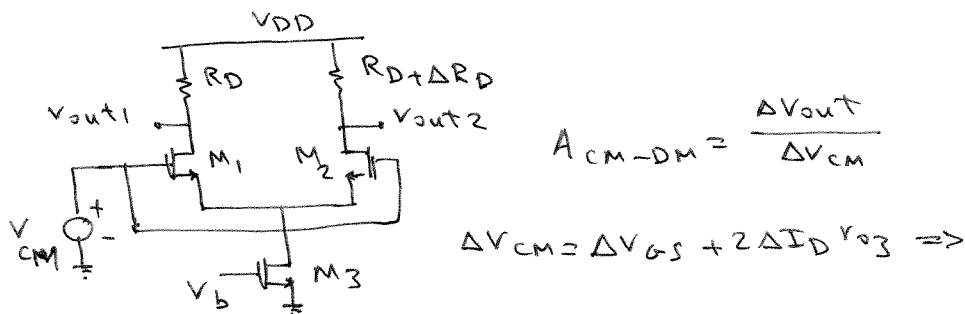


$$\Delta V_{cm} = \Delta I_D \left( \frac{1}{g_{m1}} + 2r_{o3} \right)$$

$$\Delta V_{out} = \Delta V_{out1} - \Delta V_{out2} = -\Delta R_D \Delta I_D \Rightarrow$$

$$A_{CM-DM} = -\frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}} \Rightarrow$$

$$CMRR = \frac{A_{DM}}{A_{CM-DM}} = \frac{g_{m1} R_D}{\frac{\Delta R_D}{\frac{1}{g_{m1}} + 2r_{o3}}} = (1 + 2g_{m1} r_{o3}) \frac{R_D}{\Delta R_D}$$

(70) (b)

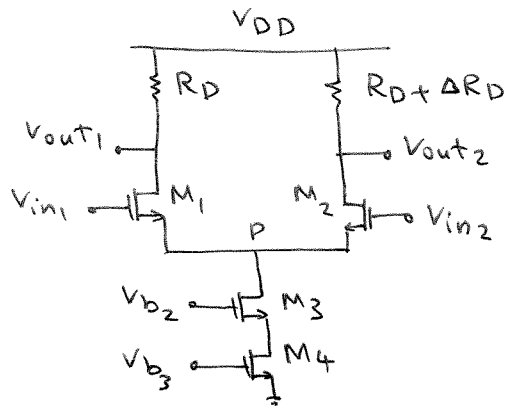

To calculate  $A_{DM}$ , using the half circuit, we have

$$A_{DM} = \frac{V_{out1}}{V_{in1}} = -g_{m1} R_D$$

Similar to part (a) we have:


$$A_{CM-DM} = - \frac{\Delta R_D}{\frac{1}{g_{m1}} + 2 [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]}$$

$$\Rightarrow CMMR = \frac{A_{DM}}{A_{CM-DM}} = (1 + 2g_{m1} [g_{m3} r_{o3} r_{o4} + r_{o3} + r_{o4}]) \frac{R_D}{\Delta R_D}$$

Notice that CMMR of part (b) is much higher than the one for part (a).



(71)

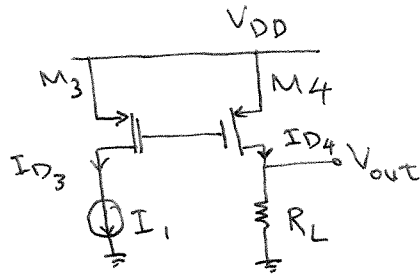


$$\left(\frac{W}{L}\right)_3 = N \left(\frac{W}{L}\right)_4$$

$$\left(\frac{W}{L}\right)_3 = N \left(\frac{W}{L}\right)_4 \Rightarrow I_{D3} = N I_{D4} \Rightarrow \underbrace{i_{d3} = N i_{d4}}_{\text{small signal}}$$

$$\left. \begin{array}{l} i_{d3} = i_i \\ v_{out} = R_L i_{d4} = \frac{R_L}{N} i_{d3} = \frac{R_L}{N} i_i \Rightarrow \end{array} \right\}$$

$$\frac{v_{out}}{i_i} = \frac{R_L}{N}$$

72

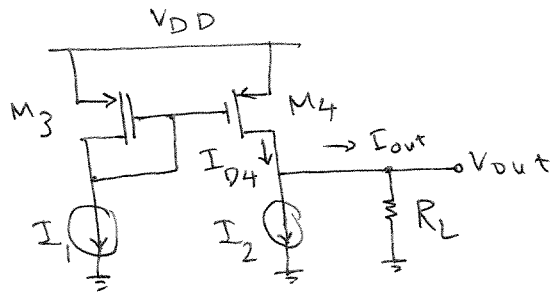

$$(a) \left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4$$

if  $I_1 = I_2 = I_0$   $\Rightarrow \begin{cases} V_{out} = I_{out} \times R_L = 0 & \text{because} \\ I_{out} = I_{D4} - I_2 = I_1 - I_2 = 0 \end{cases}$

$$\text{if } I_1 = I_0 + \Delta I \Rightarrow I_{D4} = I_{D3} = I_1 = I_0 + \Delta I$$

$$I_2 = I_0 - \Delta I \Rightarrow I_{out} = I_{D4} - I_2 = 2\Delta I$$

$$V_{out} = I_{out} R_L = 2 R_L \Delta I$$

$$(b) \left(\frac{W}{L}\right)_3 = 2\left(\frac{W}{L}\right)_4$$

$$\Rightarrow I_{D3} = 2 I_{D4}$$

$$\text{if } I_1 = I_2 = I_0 \text{ then } I_{D3} = I_1 = I_0 \Rightarrow I_{D4} = \frac{I_{D3}}{2}$$

$$\Rightarrow I_{D4} = \frac{I_0}{2} \Rightarrow I_{out} = I_{D4} - I_2 = -\frac{I_0}{2}$$

$$\Rightarrow V_{out} = R_L I_{out} = -\frac{R_L I_0}{2}$$

$$\text{if } I_1 = I_0 + \Delta I \Rightarrow I_{D4} = \frac{I_{D3}}{2} = \frac{I_1}{2} = \frac{I_0 + \Delta I}{2}$$

$$I_2 = I_0 - \Delta I \Rightarrow I_{out} = I_{D4} - I_2 = -\frac{I_0}{2} + \frac{3\Delta I}{2}$$


$$\Rightarrow V_{out} = R_L I_{out} = +R_L \left(-\frac{I_0}{2} + \frac{3\Delta I}{2}\right)$$

10.73 (a)

$$\begin{aligned}V_N &= V_{DD} - V_{SG3} \\ &= V_{DD} - \sqrt{\frac{I_{SS}}{\left(\frac{W}{L}\right)_3 \mu_p C_{ox}}} - |V_{THp}|\end{aligned}$$

- (b) By symmetry, we know that  $I_D$  for  $M_3$  and  $M_4$  is the same, and we also know that their  $V_{SG}$  values are the same. Thus, their  $V_{SD}$  values must also be equal, meaning  $V_Y = V_N$ .
- (c) If  $V_{DD}$  changes by  $\Delta V$ , then both  $V_Y$  and  $V_N$  will change by  $\Delta V$ .

74

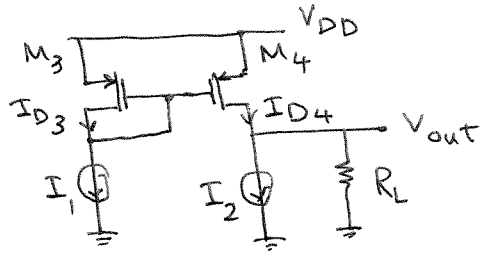


$$I_{D3} = I_{D4} = I_1$$

$$V_{out} = (I_{D4} - I_2) R_L = (I_1 - I_2) R_L$$

small  
=> signal  $\frac{V_{out}}{i_1} = R_L$  ,  $\frac{V_{out}}{i_2} = -R_L$

(75)

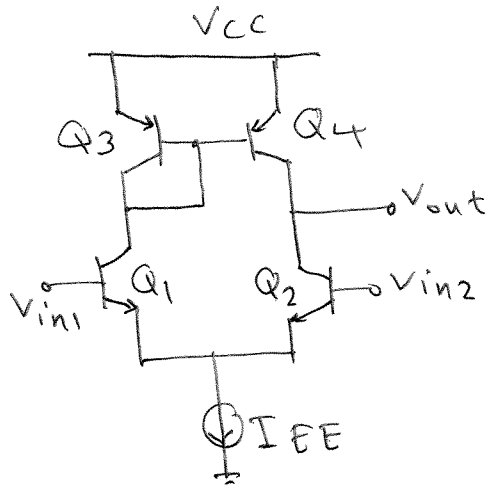

$$V_{A,n} = 5V$$


$$A_v = 100$$

$$\frac{v_{out}}{v_{in1} - v_{in2}} = g_{mN} (r_{oN} || r_{oP}) =$$


$$\frac{I_{EE}/2}{V_T} \left( \frac{V_{A,n}}{I_{EE}/2} || \frac{V_{A,p}}{I_{EE}/2} \right) = \frac{V_{A,n} V_{A,p}}{(V_{A,n} + V_{A,p}) V_T}$$

$$\Rightarrow 100 = \frac{5 V_{A,p}}{(5 + V_{A,p}) 0.026} \Rightarrow V_{A,p} = 5.417V$$

(76)

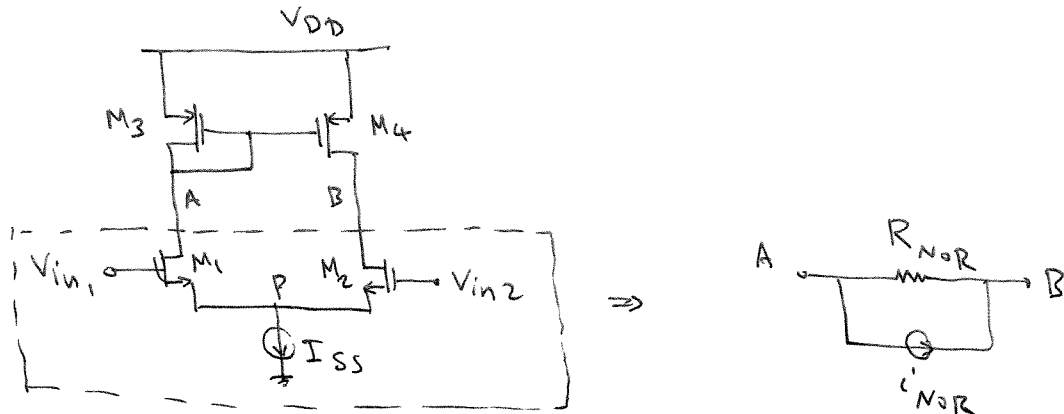

To calculate  $i_{NOR}$  we have:

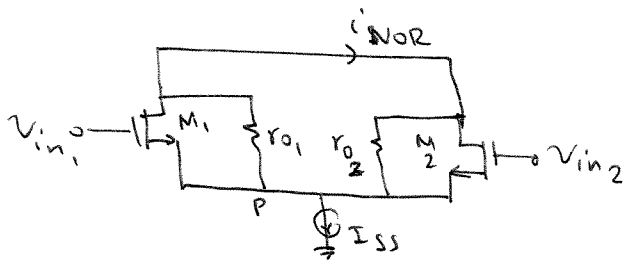


$$r_{o1} (i_{NOR} + g_{m1} v_{in1}) + r_{o2} (i_{NOR} - g_{m2} v_{in2}) = 0$$

$$\rightarrow 2 r_{oN} i_{NOR} = -g_{m1} r_{o1} v_{in1} + g_{m2} r_{o2} v_{in2} \Rightarrow$$

$$i_{NOR} = -\frac{g_{mN}}{2} (v_{in1} - v_{in2})$$

To calculate  $R_{NOR}$ :

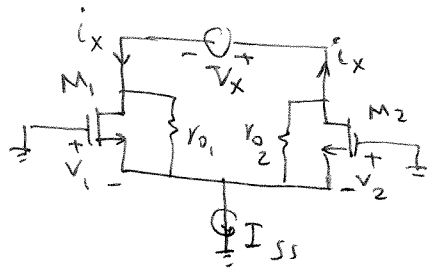


$$v_1 = v_2$$

$$(i_x - g_{m1} v_1) r_{o1} + (i_x + g_{m2} v_2) r_{o2} = v_x$$

$$\Rightarrow R_{NOR} = \frac{v_x}{i_x} = 2 r_{oN}$$

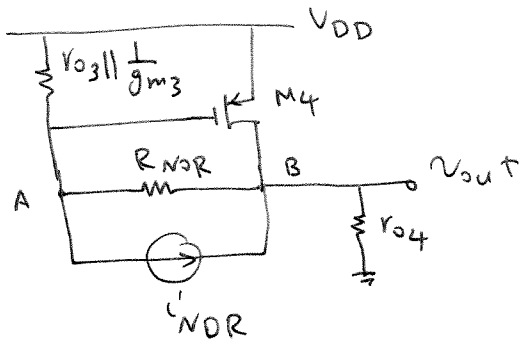Therefore, utilizing the Norton model we have:



$$\begin{cases} \frac{V_A - V_B}{R_{NOR}} + \frac{V_A}{r_{o3} \parallel \frac{1}{g_{m3}}} + i_{NOR} = 0 \Rightarrow V_A = \frac{\frac{V_B}{R_{NOR}} - i_{NOR}}{\frac{1}{R_{NOR}} + \frac{1}{r_{o3} \parallel \frac{1}{g_{m3}}}} \\ \frac{V_B - V_A}{R_{NOR}} + \frac{V_B}{r_{o4}} - i_{NOR} + g_{m4} V_A = 0, V_B = v_{out} \end{cases}$$

$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{o4}} \right) + \left( g_{m4} - \frac{1}{R_{NOR}} \right) \frac{\frac{v_{out}}{R_{NOR}} - i_{NOR}}{\frac{1}{R_{NOR}} + \frac{1}{r_{o3} \parallel \frac{1}{g_{m3}}}} = i_{NOR}$$

$$\frac{1}{g_{m3}} \ll r_{o3}, \frac{1}{g_{m3}} \ll R_{NOR}, g_{m3} = g_{m4} = g_m, r_{o3} = r_{o4} = r_{op}$$


$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{op}} \right) + g_{m4} \frac{\frac{v_{out}}{R_{NOR}} - i_{NOR}}{g_{m3}} = i_{NOR}$$

$$\Rightarrow v_{out} \left( \frac{1}{R_{NOR}} + \frac{1}{r_{op}} \right) + \frac{v_{out}}{R_{NOR}} = 2 i_{NOR} \Rightarrow$$

$$\frac{2 v_{out}}{R_{NOR}} + \frac{v_{out}}{r_{op}} = 2 i_{NOR} \Rightarrow v_{out} \left( \frac{1}{r_{on}} + \frac{1}{r_{op}} \right) = -g_{mN} (v_{in1} - v_{in2})$$

$$\Rightarrow \frac{v_{out}}{v_{in1} - v_{in2}} = -g_{mN} (r_{on} \parallel r_{op})$$


77

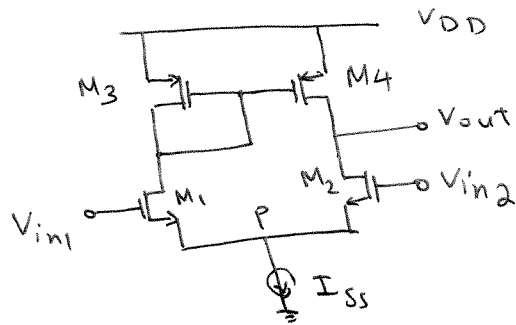

$$g_m r_o \gg 1$$


$$g_{m1} = g_{m2}$$

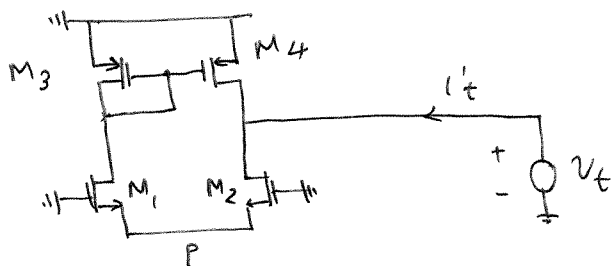To calculate the output impedance we have the following circuit:



$$R_{out} = \frac{v_t}{i_t}$$

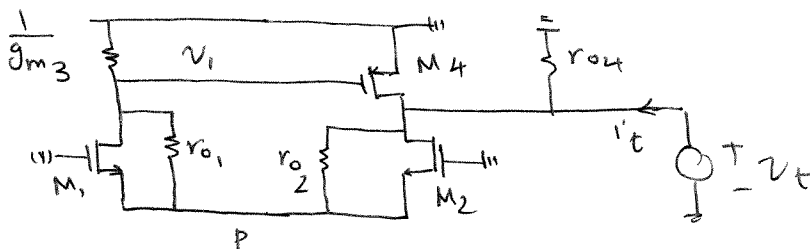↓ neglecting  $r_{o3}$  ( $r_{o3} \gg \frac{1}{g_{m3}}$ )




writing node equations of  $v_i$  and  $v_p$ :

$$\begin{cases} g_{m3} v_i + \frac{v_i - v_p}{r_{o1}} - g_{m1} v_p = 0 \\ 2g_{m1} v_p + \frac{v_p - v_i}{r_{o1}} + \frac{v_p - v_t}{r_{o2}} = 0 \end{cases} \xrightarrow{g_m r_o \gg 1} \begin{cases} g_{m3} v_i \approx g_{m1} v_p \\ 2g_{m1} v_p \approx 0 \end{cases}$$

$$\Rightarrow v_p \approx v_i = 0 \Rightarrow R_{out} = \frac{v_t}{i_t} = r_{o4} \parallel r_{o2} = r_{oN} \parallel r_{oP}$$



78


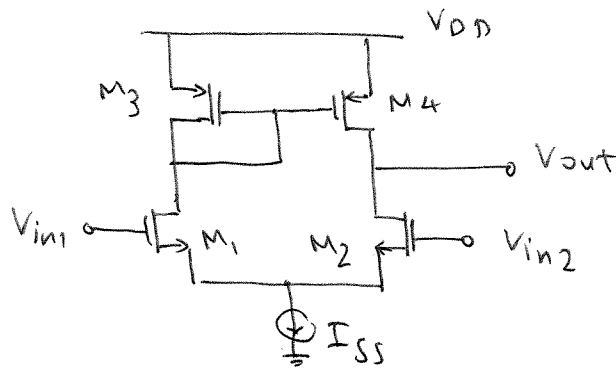


$$g_m r_o \gg 1$$

$$g_{m1} = g_{m2}$$

$$g_{m3} = g_{m4}$$

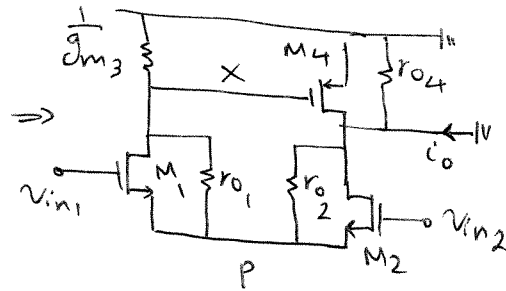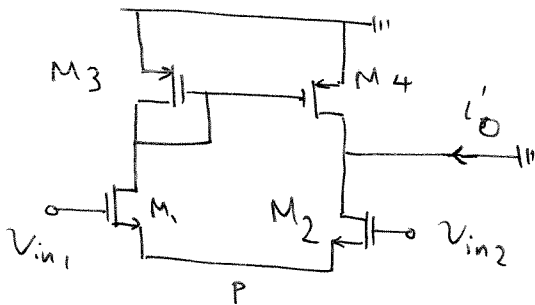To calculate  $G_m$  we have from small signal model:



writing node equations of nodes P and X we have:

$$\begin{cases} g_{m1}(v_p - v_{in1}) + g_{m2}(v_p - v_{in2}) + \frac{v_p - v_x}{r_{o1}} + \frac{v_p}{r_{o2}} = 0 \\ g_{m3} v_x + g_{m1}(v_{in1} - v_p) + \frac{v_x - v_p}{r_{o1}} = 0 \end{cases}$$

Since  $g_m r_o \gg 1$  we have

$$\begin{cases} g_{m1}(v_p - v_{in1}) + g_{m2}(v_p - v_{in2}) = 0 \Rightarrow v_p = \frac{v_{in1} + v_{in2}}{2} \\ v_x = -\frac{g_{m1}}{g_{m3}}(v_{in1} - v_p) = -\frac{g_{m1}}{g_{m3}} \left( \frac{v_{in1} - v_{in2}}{2} \right) \end{cases}$$

$$i_o = -\frac{v_p}{r_{o2}} + g_{m2}(v_{in2} - v_p) - g_{m4}(-v_x)$$

$$\Rightarrow i_o \approx -g_{m4}(-v_x) + g_{m2} \left( v_{in2} - \frac{v_{in1} + v_{in2}}{2} \right)$$


$$= - \left[ g_{m4} \frac{g_{m1}}{g_{m3}} \left( \frac{v_{in1} - v_{in2}}{2} \right) + g_{m2} \left( \frac{v_{in1} - v_{in2}}{2} \right) \right]$$

$$= -g_{m1} (v_{in1} - v_{in2})$$

$$G_m = \frac{i_o}{v_{in1} - v_{in2}} = -g_{m1} = -g_{mN}$$

$$\rightarrow A_v = -G_m R_{out} = g_{mN} (r_{oN} \parallel r_{op})$$

79

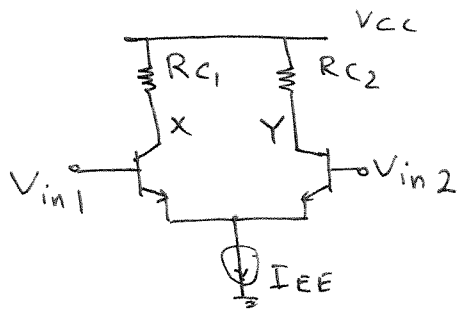


$$\begin{aligned}A_v &= 10, \\ P &= 2 \text{ mW} \\ V_{CC} &= 2.5 \text{ V} \\ V_A &= \infty\end{aligned}$$

$$P = V_{CC} I_{EE} \Rightarrow 2 \times 10^{-3} = 2.5 I_{EE} \Rightarrow I_{EE} = 0.8 \text{ mA}$$

$$A_v = \frac{v_{XY}}{v_{in1} - v_{in2}} = -g_m R_C = -\frac{I_{EE}/2}{V_T} R_C$$

$$\Rightarrow 10 = \frac{0.4 \times 10^{-3}}{0.026} R_C \Rightarrow R_C = 650 \Omega$$

(80)

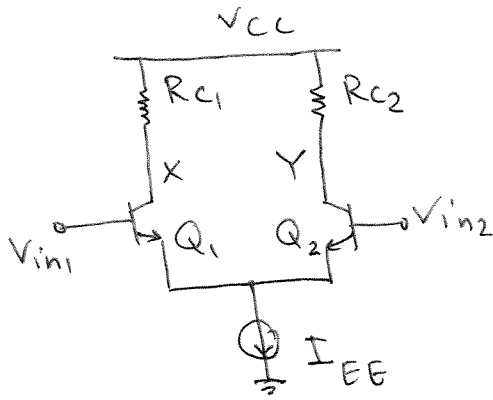

$$V_{in, CM} = 1.2 \text{ V}$$

$$P = 3 \text{ mW}$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = I_{EE} V_{CC} \Rightarrow 3 \times 10^{-3} = 2.5 I_{EE} \Rightarrow I_{EE} = 1.2 \text{ mA}$$

$$A_v = -g_m R_C = -\frac{I_{EE}/2}{V_T} R_C = -\frac{R_C I_{EE}}{2 V_T}$$


To maximize gain,  $R_C I_{EE}$  and therefore  $R_C$  should be maximum. However, the upper bound of  $R_C$  value is limited by the voltage value of  $X$ . because:

$$V_{in, CM} \leq V_X \Rightarrow 1.2 \leq V_{CC} - R_C I_{EE}/2 \Rightarrow$$

$$R_C \leq 2 \frac{V_{CC} - 1.2}{I_{EE}} \Rightarrow R_C \leq 2 \frac{2.5 - 1.2}{1.2 \times 10^{-3}} \Rightarrow$$

$$R_C \leq 2.167 \text{ k}\Omega \Rightarrow R_C = 2.167 \text{ k}\Omega$$

81

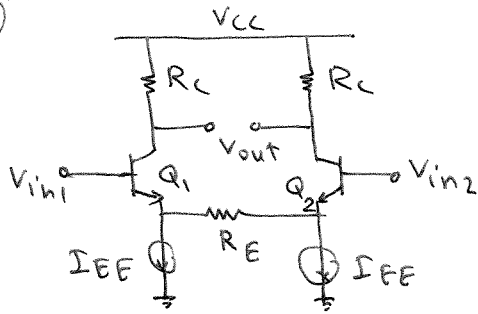


$$A_v = 5$$

$$P = 4 \text{ mW}$$

$$V_{CC} = 2.5 \text{ V}$$

$$V_A = \infty$$

The half circuit is:

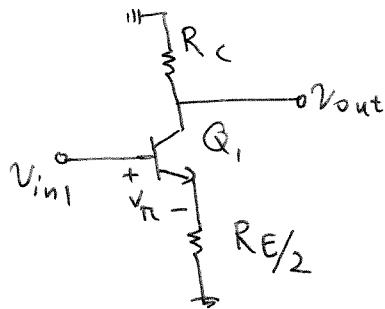

$$A_v = \frac{v_{out}}{v_{in1}} \approx \frac{-g_{m1} v_{\pi} R_C}{v_{in1}} = - \frac{g_{m1} R_C}{\frac{1}{g_{m1}} + \frac{R_E}{2}} v_{in1}$$

$$= - \frac{R_C}{\frac{R_E}{2} + \frac{1}{g_{m1}}}$$

$$P = 4 \text{ mW} = 2 I_{EE} V_{CC} = 5 I_{EE} \Rightarrow I_{EE} = 0.8 \text{ mA}$$

$$g_m = \frac{I_{EE}}{V_T} = 0.03077$$

$$A_v = 5 \Rightarrow \frac{R_C}{\frac{R_E}{2} + 32.5} = 5 \quad (1)$$

if  $I_{EE}$  increases by 10%, the gain will be:

$$A_v = \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{1.1}} \Rightarrow 5 < \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{1.1}} < 5 \times 1.02 \quad (2)$$

if  $I_{EE}$  decreases by 10% then:

$$5 \times 0.98 < \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{0.9}} < 5 \quad (3)$$

The worse case is:

$$\left\{ \begin{array}{l} \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{1.1}} = 5 \times 1.02 \quad (4) \\ \frac{R_C}{\frac{R_E}{2} + \frac{32.5}{0.9}} = 5 \times 0.98 \quad (5) \end{array} \right.$$


dividing (4) and (5) to (1) leads to:

$$\left\{ \begin{array}{l} \frac{\frac{R_E}{2} + 32.5}{\frac{R_E}{2} + \frac{32.5}{1.1}} = 1.02 \Rightarrow R_E = 236.36 \Omega \\ \frac{\frac{R_E}{2} + 32.5}{\frac{R_E}{2} + \frac{32.5}{0.9}} = 0.98 \Rightarrow R_E = 288.89 \Omega \end{array} \right.$$

To ensure less than 2% gain variation for 10% current variation  $R_E = 288.89 \Omega$

$$\text{From (1)} \quad R_C = 5 \left( \frac{R_E}{2} + 32.5 \right) = 884.72 \Omega$$

(82)

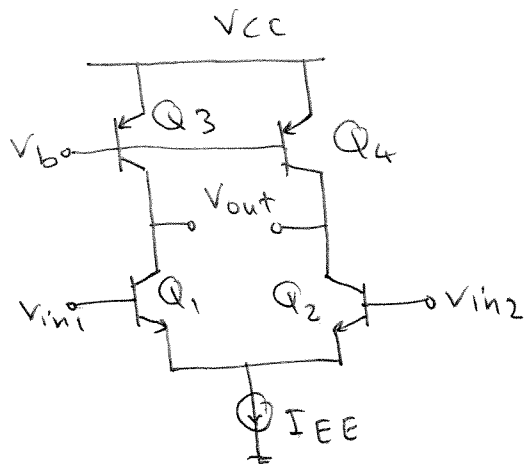

$$A_v = 100$$

$$P = 1 \text{ mW}$$

$$V_{A, n} = 6$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = 1 \text{ mW} = I_{EE} V_{CC} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$

$$r_{oN} = \frac{V_{A, n}}{I_{EE}/2} = \frac{6}{0.2 \times 10^{-3}} = 30 \text{ k}\Omega, \quad g_{mN} = \frac{I_{EE}/2}{V_T} = \frac{0.2}{26} \text{ S}$$

$$A_v = -g_{mN} (r_{oN} \parallel r_{op}) \Rightarrow$$

$$100 = \frac{0.2}{26} (30 \times 10^3 \parallel r_{op}) \Rightarrow r_{op} = 22.94 \text{ k}\Omega$$


$$\Rightarrow V_{A, P} = r_{op} \frac{I_{EE}}{2} = 4.588 \text{ V}$$

10.83

$$\begin{aligned}P &= V_{CC}I_{EE} = 1 \text{ mW} \\I_{EE} &= 0.4 \text{ mA} \\A_v &= -g_{m1}(r_{o1} \parallel r_{o3} \parallel R_1) \\&= -100 \\R_1 = R_2 &= \boxed{59.1 \text{ k}\Omega}\end{aligned}$$



84

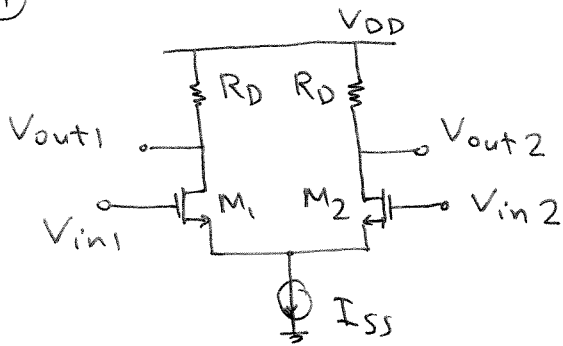

$$\Delta V_{in, \max} = 0.3 \text{ V}$$

$$P = 3 \text{ mW}$$

$$R_D = 500 \Omega$$

$$\lambda = 0, \mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$$

$$V_{DD} = 1.8 \text{ V}$$


$$P = V_{DD} I_{SS} \Rightarrow 3 \times 10^{-3} = 1.8 I_{SS} \Rightarrow$$

$$I_{SS} = 1.67 \text{ mA}$$

$$\Delta V_{in, \max} = \sqrt{\frac{2 I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.3 = \sqrt{\frac{2 \times 1.67 \times 10^{-3}}{10^{-4} \times \frac{W}{L}}} \Rightarrow \frac{W}{L} = 370.37$$

(85)

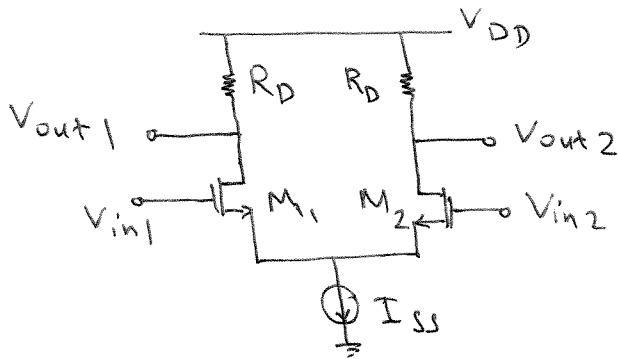

$$\begin{aligned} P &= 2 \text{ mW} \\ \text{overdrive} &= 100 \text{ mV} \\ V_{CM} &= 1 \text{ V} \\ \lambda &= 0, \mu_n C_{ox} = 100 \mu\text{A/V}^2 \\ V_{DD} &= 1.8 \text{ V} \\ V_{TH,n} &= 0.5 \end{aligned}$$

$$P = I_{SS} V_{DD} \Rightarrow 2 \times 10^{-3} = 1.8 I_{SS} \Rightarrow I_{SS} = 1.11 \text{ mA}$$

$$V_{GS1} - V_{TH} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.1^2 = \frac{1.11 \times 10^{-3}}{10^{-4} \times \frac{W}{L}} \Rightarrow \frac{W}{L} = 1111.11$$

$$g_m = \sqrt{\mu_n C_{ox} \frac{W}{L} I_{SS}} = \sqrt{10^{-4} \times 1111.11 \times 1.11 \times 10^{-3}} = 0.011$$

To place the transistor at the edge of triode region:


$$V_{in,CM} = V_{out1} + V_{TH,n}$$

$$1 = V_{DD} - R_D \frac{I_{SS}}{2} + 0.5 \Rightarrow$$

$$1 = 1.8 - R_D \frac{1.11 \times 10^{-3}}{2} + 0.5 \Rightarrow R_D = 2.34 \text{ k}\Omega$$

$$A_V = -g_m R_D = -25.74$$

86

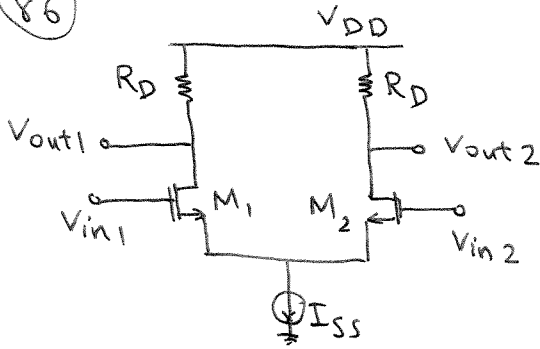

$$A_v = 5$$

$$P = 1 \text{ mW}$$

$$(V_{GS} - V_{TH})_{\text{equil}} = 150 \text{ mV}$$

$$\lambda = 0, \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$V_{DD} = 1.8 \text{ V}$$

$$P = 1 \text{ mW} = V_{DD} I_{SS} = 1.8 I_{SS} \Rightarrow I_{SS} = 0.556 \text{ mA}$$

$$g_{m1} = \frac{2 I_{D1}}{(V_{GS} - V_{TH})_{\text{equil}}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{\text{equil}}} = \frac{0.556 \times 10^{-3}}{0.15}$$


$$= 3.704 \text{ mS}$$

$$A_v = -g_{m1} R_D \Rightarrow 5 = 3.704 \times 10^{-3} \times R_D \Rightarrow R_D = 1.35 \text{ k}\Omega$$

$$(V_{GS} - V_{TH})_{\text{equil}} = \sqrt{\frac{2 I_{D1}}{\mu_n C_{ox} \frac{W}{L}}} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \frac{W}{L}}} \Rightarrow$$

$$0.15 = \sqrt{\frac{0.556 \times 10^{-3}}{10^{-4} \times \frac{W}{L}}} \Rightarrow \left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 = 246.91$$

(87)

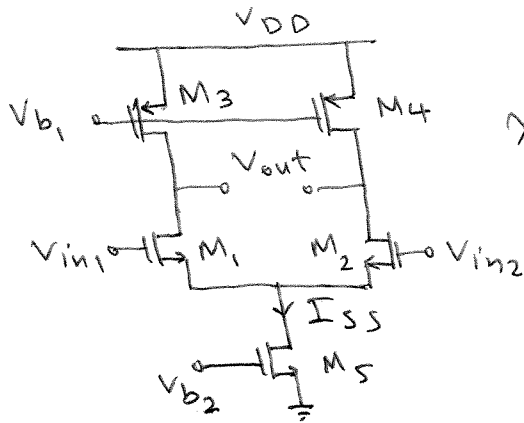

$$A_V = 40$$

$$(V_{GS} - V_{TH})_{\text{equil}} = ?$$

$$\lambda_n = 0.1 \text{ V}^{-1} \quad \lambda_p = 0.2 \text{ V}^{-1}$$

$$\mu_n C_{ox} = 100 \text{ MA/V}^2$$

$$\mu_p C_{ox} = 50 \text{ MA/V}^2$$

$$V_{DD} = 1.8$$

$$P = 2 \text{ mW}$$

$$A_V = -g_{m_N} (r_{op} \parallel r_{on}) = -\frac{I_{SS}}{(V_{GS_1} - V_{TH})_{\text{equil}}} \left( \frac{1}{\frac{I_{SS} \lambda_n}{2}} \parallel \frac{1}{\frac{I_{SS} \lambda_p}{2}} \right)$$

$$= -\frac{2}{(V_{GS_1} - V_{TH})_{\text{equil}}} \left( \frac{1}{\lambda_n} \parallel \frac{1}{\lambda_p} \right) \Rightarrow$$

$$\frac{2}{(V_{GS_1} - V_{TH})_{\text{equil}}} (10 \parallel 5) = 40 \Rightarrow (V_{GS_1} - V_{TH})_{\text{equil}} = 166.67 \text{ mV}$$


$$P = 2 \times 10^{-3} = V_{DD} I_{SS} \Rightarrow I_{SS} = \frac{2 \times 10^{-3}}{1.8} = 1.11 \text{ mA}$$

$$\left( \frac{W}{L} \right)_{1,2} = \frac{I_{SS}}{\mu_n C_{ox} (V_{GS_1} - V_{TH})_{\text{equil}}^2} = \frac{1.11 \times 10^{-3}}{10^{-4} \times (0.16667)^2} = 400$$

$$\left( \frac{W}{L} \right)_{3,4} = \frac{I_{SS}}{\mu_p C_{ox} (V_{GS} - V_{TH})_{\text{equil}}^2} = \frac{1.11 \times 10^{-3}}{0.5 \times 10^{-4} \times (0.16667)^2} = 800$$

$$\left( \frac{W}{L} \right)_5 = \frac{2 I_{SS}}{\mu_n C_{ox} (V_{GS} - V_{TH})_{\text{equil}}^2} = \frac{2 \times 1.11 \times 10^{-3}}{10^{-4} \times (0.16667)^2} = 800$$

(88)

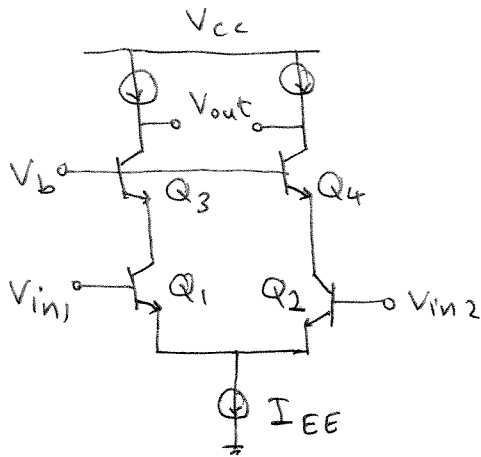

$$A_v = 4000$$

$$\beta = 100$$

$$V_{CC} = 2.5 \text{ V}$$

$$P = 1 \text{ mW}$$

$$P = I_{EE} V_{CC} = 10^{-3} \Rightarrow I_{EE} = \frac{10^{-3}}{2.5} = 0.4 \text{ mA}$$

$$g_{m1-4} = \frac{I_{EE}}{2V_T} = \frac{0.2}{26} = 7.692 \text{ mS}$$

$$r_{\pi1-4} = \frac{\beta}{g_{m1}} = 13 \text{ k}\Omega$$


$$r_{o1-4} = \frac{V_A}{\frac{I_{EE}}{2}} = 5 \times 10^3 \text{ V}_A$$

$$A_v = -g_{m1} \left[ g_{m3} (r_{o1} \parallel r_{\pi3}) r_{o3} + (r_{o1} \parallel r_{\pi3}) + r_{o3} \right] \Rightarrow$$

$$4000 = \frac{0.2}{26} \left[ \frac{0.2}{26} (5 \times 10^3 \text{ V}_A \parallel 13 \times 10^3) 5 \times 10^3 \text{ V}_A + (5 \times 10^3 \text{ V}_A) \parallel 13 \times 10^3 + 5 \times 10^3 \text{ V}_A \right]$$

$$\Rightarrow V_A = 2.197$$

(89)

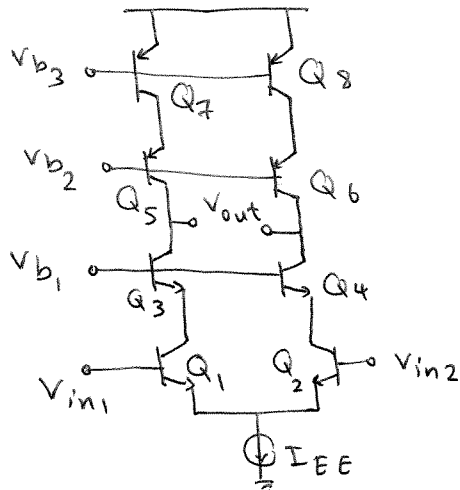

$$A_v = 2000$$

$$\beta_n = 100$$

$$\beta_p = 50$$

$$V_{A,n} = 5V$$

$$V_{CC} = 2.5V$$

$$P = 2mW$$

$$P = I_{EE} V_{CC} = 2 \times 10^{-3} \Rightarrow I_{EE} = \frac{2 \times 10^{-3}}{2.5} = 0.8mA$$

$$g_{m_{1-8}} = \frac{I_{EE}}{2V_T} = \frac{0.4}{26} = 0.0154 \Rightarrow$$

$$r_{\pi_{1-4}} = \frac{\beta_n}{g_{m_1}} = 6.5k\Omega \quad r_{\pi_{5-8}} = \frac{\beta_p}{g_{m_5}} = 3.25k\Omega$$


$$r_{o_{1-4}} = \frac{V_{A,n}}{I_{EE}/2} = 12.5k\Omega \quad r_{o_{5-8}} = \frac{V_{A,p}}{I_{EE}/2}$$

$$A_v \approx -g_{m_1} \left[ g_{m_3} r_{o_3} (r_{o_1} \parallel r_{\pi_3}) \right] \parallel \left[ g_{m_5} r_{o_5} (r_{o_7} \parallel r_{\pi_5}) \right]$$

$$\Rightarrow \frac{0.4}{26} \left[ \frac{0.4}{26} \times 12.5 \times 10^3 (12.5 \times 10^3 \parallel 6.5 \times 10^3) \right] \parallel \left[ \frac{0.4}{26} \frac{V_{A,p}}{I_{EE}/2} \left( \frac{V_{A,p}}{I_{EE}/2} \parallel 3250 \right) \right] = 2000$$

$$\Rightarrow V_{A,p} = 2.027V$$

(90)

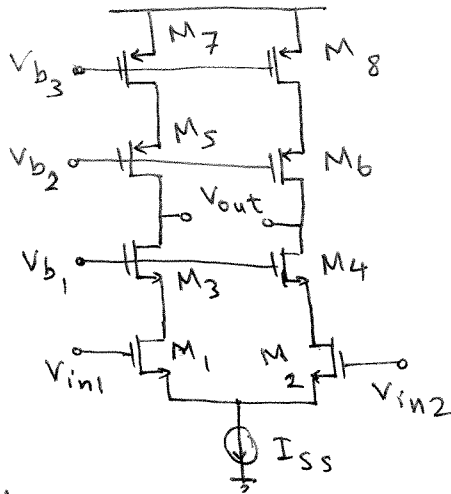

$$A_v = 600$$

$$P = 4 \text{ mW}$$

$$(V_{GS} - V_{TH})_{NMOS} = 100 \text{ mV}$$

$$(V_{GS} - V_{TH})_{PMOS} = 150 \text{ mV}$$

$$\mu_n C_{ox} = 100 \text{ } \mu\text{A/V}^2$$

$$\mu_p C_{ox} = 50 \text{ } \mu\text{A/V}^2$$

$$\lambda_n = 0.1 \text{ V}^{-1}$$

$$A_v \approx -g_{m1} [(g_{m3} r_{o3} r_{o1}) \parallel (g_{m5} r_{o5} r_{o7})] = -600$$

$$P = 4 \text{ mW} = I_{SS} V_{DD} \Rightarrow I_{SS} = \frac{4 \times 10^{-3}}{1.8} = 2.22 \text{ mA}$$

$$g_{m_{1-4}} = \frac{2I_{D1}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{2.22 \times 10^{-3}}{0.1} = 22.22 \text{ mS}$$

$$g_{m_{5-8}} = \frac{2I_{D5}}{(V_{GS} - V_{TH})_{PMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{PMOS}} = \frac{2.22 \times 10^{-3}}{0.15} = 14.815 \text{ mS}$$

$$r_{o_{1-4}} = \frac{1}{\lambda_n \frac{I_{SS}}{2}} = \frac{1}{0.1 \times \frac{2.22}{2} \times 10^{-3}} = 9 \text{ k}\Omega$$

$$r_{o_{5-8}} = \frac{1}{\lambda_p \frac{I_{SS}}{2}} = \frac{1}{\lambda_p \times \frac{2.22 \times 10^{-3}}{2}} = \frac{0.9 \times 10^3}{\lambda_p}$$

in  $A_v$   
 $\Rightarrow$  equation


$$22.22 \times 10^{-3} \left[ (22.22 \times 10^{-3} \times 81 \times 10^6) \parallel (14.815 \times 10^{-3} \times \frac{0.81 \times 10^6}{\lambda_p^2}) \right] = 600 \Rightarrow$$

$$\lambda_p = 0.66 \text{ V}^{-1}$$

$$\left(\frac{W}{L}\right)_{NMOS} = I_{SS} / (\mu_n C_{ox} (V_{GS} - V_{TH})_{NMOS}^2) = 2222.2$$

$$\left(\frac{W}{L}\right)_{PMOS} = I_{SS} / (\mu_p C_{ox} (V_{GS} - V_{TH})_{PMOS}^2) = 1975.31$$

(91)

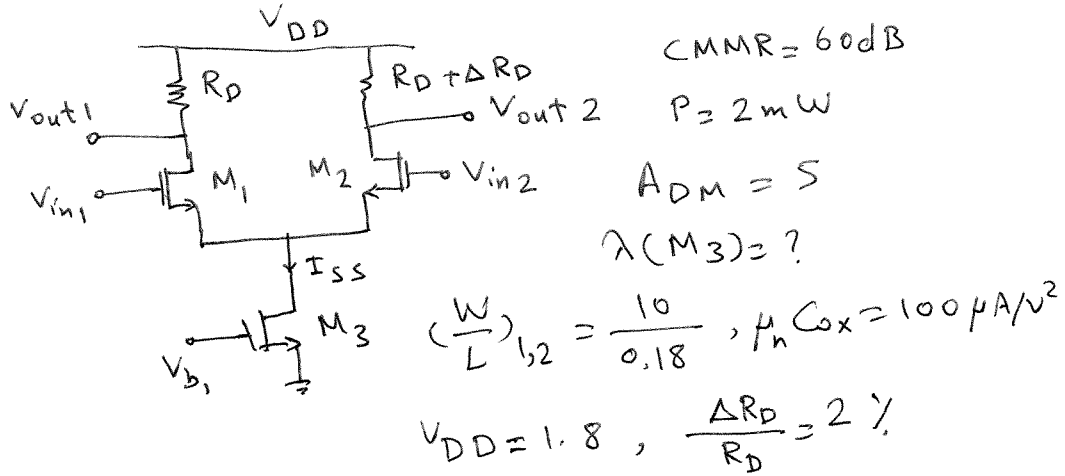


$$P = 2 \text{ mW} = I_{SS} V_{DD} \Rightarrow I_{SS} = \frac{2 \times 10^{-3}}{1.8} = 1.11 \text{ mA}$$

$$A_{DM} = -g_{m1} R_D$$

$$g_{m1} = \sqrt{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{SS}} = \sqrt{10^{-4} \times \frac{10}{0.18} \times 1.11 \times 10^{-3}} = 2.4845 \text{ mS}$$

$$\Rightarrow R_D = \frac{|A_{DM}|}{g_{m1}} = \frac{5}{2.4845 \times 10^{-3}} = 2.012 \text{ k}\Omega$$

To calculate  $A_{CM,DM}$  we have:

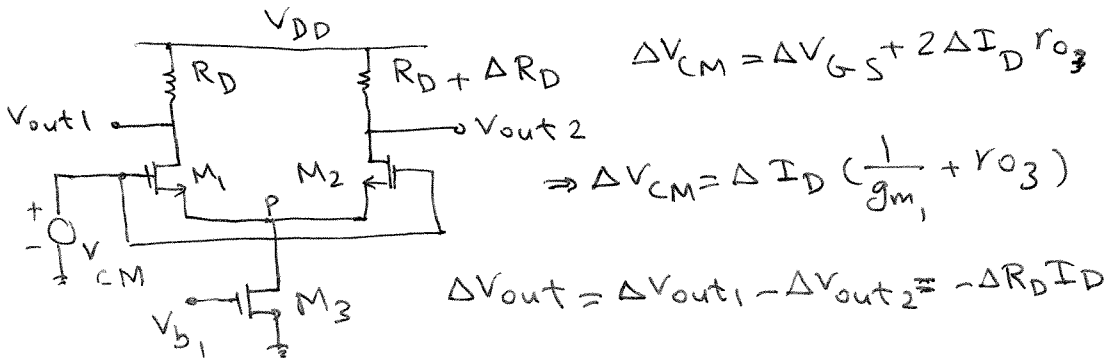

$$\Rightarrow A_{CM,DM} = \frac{\Delta V_{out}}{\Delta V_{CM}} = - \frac{\Delta R_D / 2}{\frac{1}{2g_{m1}} + r_{o3}}$$

$$\Rightarrow \text{CMMR} = \frac{A_{DM}}{A_{CM,DM}} = (1 + 2g_{m1} r_{o3}) \frac{R_D}{\Delta R_D}, \quad r_{o3} = \frac{1}{\lambda_3 I_{SS}}$$



$$\Rightarrow \text{CMRR} = 60\text{dB} = 10^3 = \left(1 + 2 \times 2.4845 \times 10^{-3} \frac{1}{\lambda_3 \times 1.11 \times 10^{-3}}\right) 50$$

$$\Rightarrow \lambda_3 = 0.2354$$

10.92

$$P = V_{CC}I_{EE} = 3 \text{ mW}$$


$$I_{EE} = 1.2 \text{ mA}$$

$$A_v = g_{m,n}(r_{o,n} \parallel r_{o,p}) \\ = 200$$

$$V_{A,n} = \boxed{15.6 \text{ V}}$$

$$V_{A,p} = \boxed{7.8 \text{ V}}$$

93

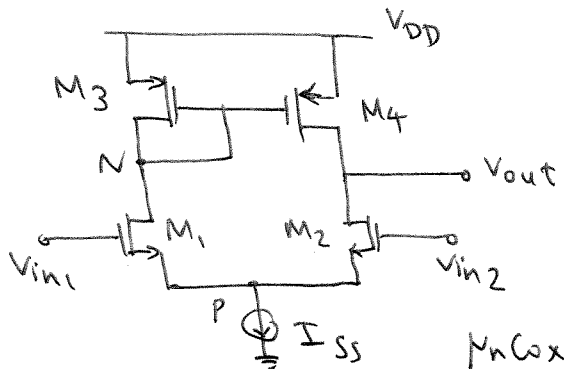

$A_V = 20$   
 $P = 1 \text{ mW}$   
 $V_{DD} = 1.8 \text{ V}$   
 $V_{in, cm} = 1 \text{ V}$

$\mu_n C_{ox} = 2 \mu_p C_{ox} = 100 \mu\text{A/V}^2$   
 $V_{TH, n} = 0.5 \text{ V}, V_{TH, p} = -0.4 \text{ V}$   
 $\lambda_n = \frac{\lambda_p}{2} = 0.1 \text{ V}^{-1}$

$$P = V_{DD} I_{SS} \Rightarrow I_{SS} = \frac{10^{-3}}{1.8} = 0.556 \text{ mA}$$

$$A_V = + g_{m_N} (r_{o_N} \parallel r_{o_P}) = 20$$

$$r_{o_N} = \frac{1}{\lambda_n \frac{I_{SS}}{2}} = \frac{1}{0.1 \frac{0.556 \times 10^{-3}}{2}} = 36 \text{ k}\Omega$$

$$r_{o_P} = \frac{1}{\lambda_p \frac{I_{SS}}{2}} = 18 \text{ k}\Omega$$

$$g_{m_N} (36 \text{ k} \parallel 18 \text{ k}) = 20 \Rightarrow g_{m_N} = 1.667 \text{ mS}$$

$$\Rightarrow g_{m_N} = \frac{2 I_{D_N}}{(V_{GS} - V_{TH})_{NMOS}} = \frac{I_{SS}}{(V_{GS} - V_{TH})_{NMOS}} \Rightarrow$$

$$(V_{GS} - V_{TH})_{NMOS} = 0.333 \text{ V}$$

$$(V_{GS} - V_{TH})_{NMOS} = \sqrt{\frac{I_{SS}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_{NMOS}}} \Rightarrow \left(\frac{W}{L}\right)_{1/2} = 50$$

$$V_N = V_{in,CM} - V_{TH,n} = 1 - 0.5 = 0.5 \text{ V}$$


$$\rightarrow |V_{G_s}| - V_{TH,p} = 1.3 - 0.4 = 0.9 \text{ V}$$

$$\rightarrow 0.9 = \sqrt{\frac{I_{SS}}{\mu_p C_{ox} \left(\frac{W}{L}\right)_{PMOS}}} \Rightarrow$$

$$\left(\frac{W}{L}\right)_{3,4} = 13.717$$

11.1

$$\begin{aligned}\frac{V_{out}}{V_{in}}(j\omega) &= -g_m \left( R_D \parallel \frac{1}{j\omega C_L} \right) \\ &= -\frac{g_m R_D}{1 + j\omega C_L R_D} \\ \left| \frac{V_{out}}{V_{in}}(j\omega) \right| &= \frac{g_m R_D}{\sqrt{1 + (\omega C_L R_D)^2}} \\ \frac{g_m R_D}{\sqrt{1 + (\omega_{-1 \text{ dB}} C_L R_D)^2}} &= 0.9 g_m R_D \\ \omega_{-1 \text{ dB}} &= 4.84 \times 10^8 \text{ rad/s} \\ f_{-1 \text{ dB}} &= \frac{\omega_{-1 \text{ dB}}}{2\pi} = \boxed{77.1 \text{ MHz}}\end{aligned}$$

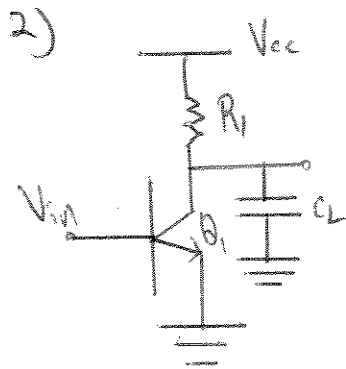

-3dB bandwidth = 1 GHz

$$C_L = 2 \text{ pF}$$

$$\text{Power} = 2 \text{ mW}$$

Low freq gain?

$$\text{Power} = 2.5 \text{ V } I_c, \quad I_c = 0.8 \text{ mA}$$

$$\text{Dominant Pole at the output} = \frac{1}{R_L C_L} = 2\pi (1 \text{ GHz})$$

$$R_L = 79.58 \text{ Ohm}$$

$$\text{Low Freq gain: } -g_m R_L = \frac{-I_c R_L}{V_T} = \frac{(79.58)(0.8)}{26}$$

$$A_v \Big|_{\text{low freq}} = -2.45$$

11.3 (a)

$$\omega_{-3 \text{ dB}} = \frac{1}{\left(\frac{1}{g_{m2}} \parallel r_{\pi2}\right) C_L}$$

(b)

$$\omega_{-3 \text{ dB}} = \frac{1}{\left(\frac{r_{\pi2} + R_B}{1 + \beta}\right) C_L} \approx \frac{1}{\left(\frac{1}{g_{m2}} + \frac{R_B}{1 + \beta}\right) C_L}$$


(c)

$$\omega_{-3 \text{ dB}} = \frac{1}{(r_{o1} \parallel r_{o2}) C_L}$$

(d)

$$\omega_{-3 \text{ dB}} = \frac{1}{\left(r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2}\right) C_L}$$

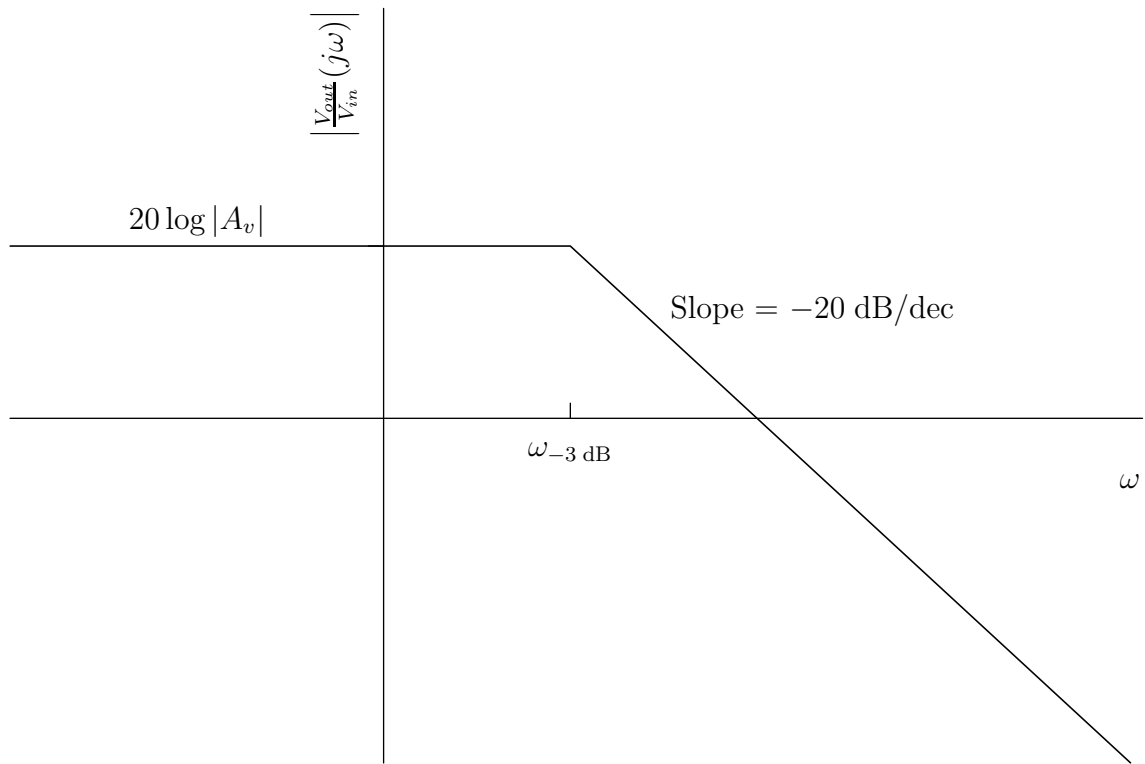11.4 Since all of these circuits have one pole, all of the Bode plots will look qualitatively identical, with some DC gain at low frequencies that rolls off at 20 dB/dec after hitting the pole at  $\omega_{-3\text{ dB}}$ . This is shown in the following plot:



For each circuit, we'll derive  $|A_v|$  and  $\omega_{-3\text{ dB}}$ , from which the Bode plot can be constructed as in the figure.

(a)

$$|A_v| = \boxed{g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)}$$

$$\omega_{-3\text{ dB}} = \boxed{\frac{1}{\left( \frac{1}{g_{m2}} \parallel r_{\pi 2} \right) C_L}}$$

(b)

$$|A_v| = \boxed{g_{m1} \left( \frac{r_{\pi 2} + R_B}{1 + \beta} \right)} \approx g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_B}{1 + \beta} \right)$$

$$\omega_{-3\text{ dB}} = \boxed{\frac{1}{\left( \frac{r_{\pi 2} + R_B}{1 + \beta} \right) C_L}} \approx \frac{1}{\left( \frac{1}{g_{m2}} + \frac{R_B}{1 + \beta} \right) C_L}$$

(c)

$$|A_v| = \boxed{g_{m1} (r_{o1} \parallel r_{o2})}$$

$$\omega_{-3\text{ dB}} = \boxed{\frac{1}{(r_{o1} \parallel r_{o2}) C_L}}$$




(d)

$$|A_v| = \boxed{g_{m1} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$
$$\omega_{-3 \text{ dB}} = \boxed{\frac{1}{\left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right) C_L}}$$


11.5 Assuming the transfer function is of the form

$$\frac{V_{out}(j\omega)}{V_{in}} = \frac{A_v}{\left(1 + j\frac{\omega}{\omega_{p1}}\right)^2}$$


we get the following Bode plot:

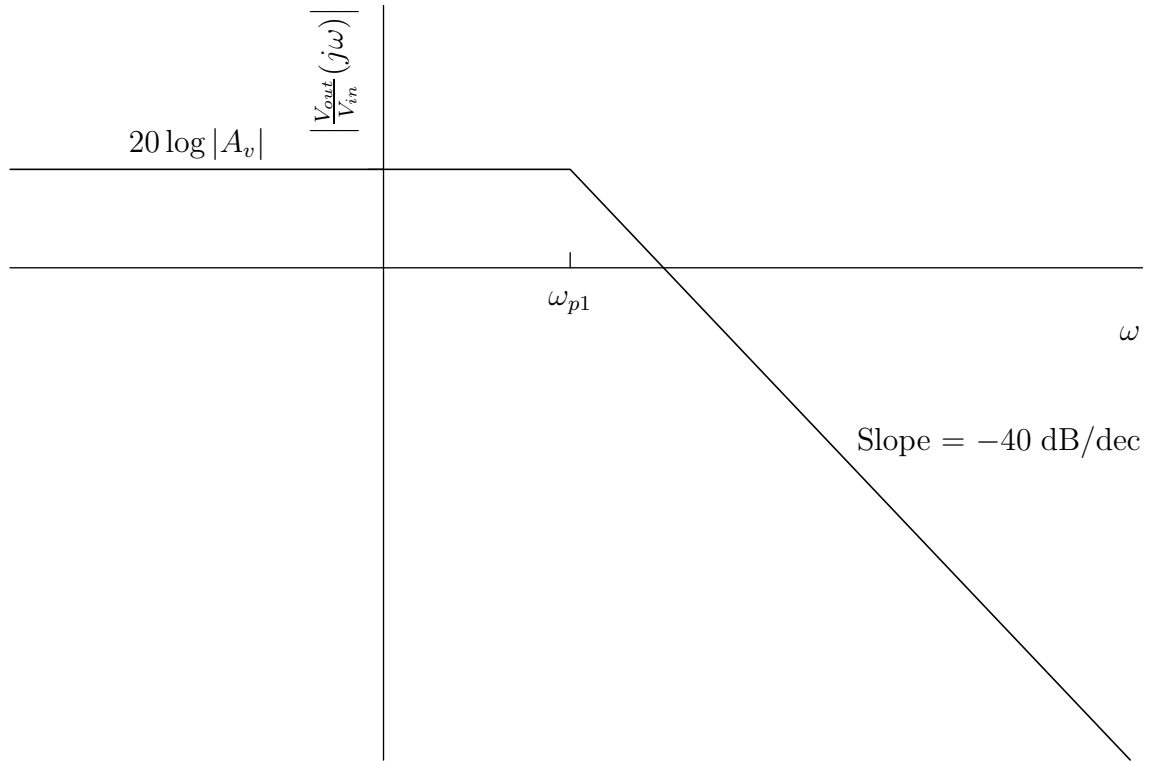


11.6

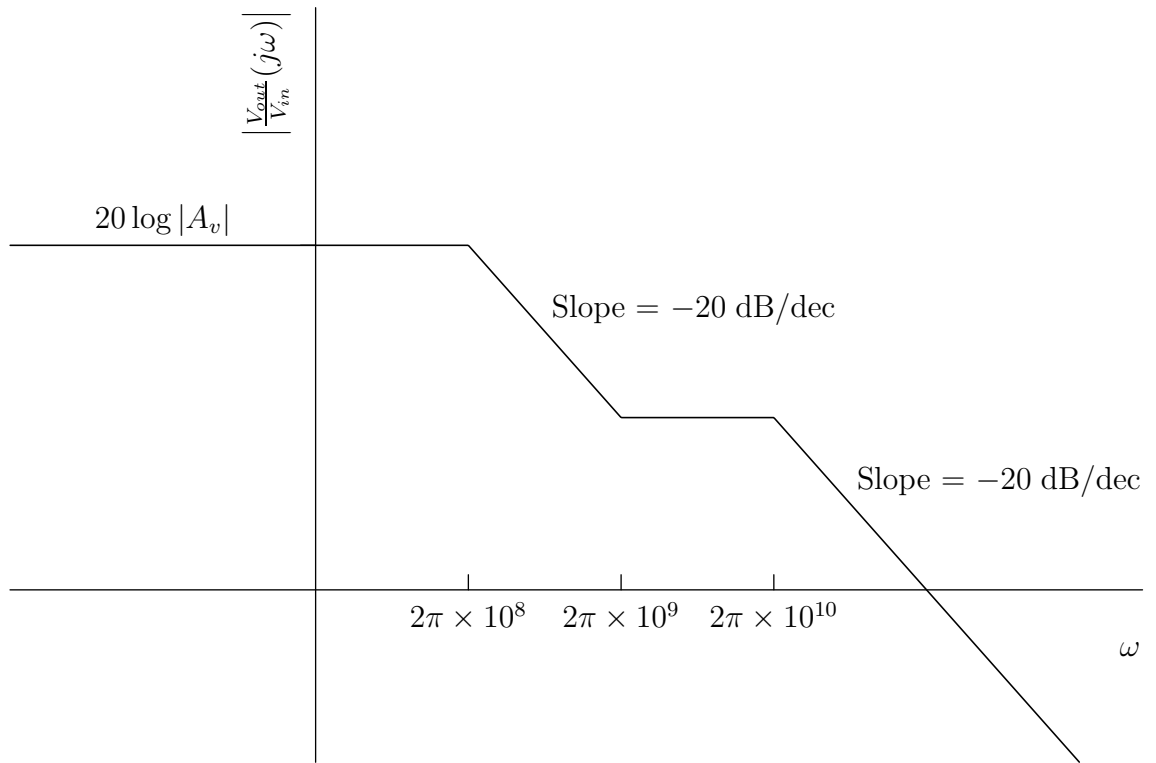


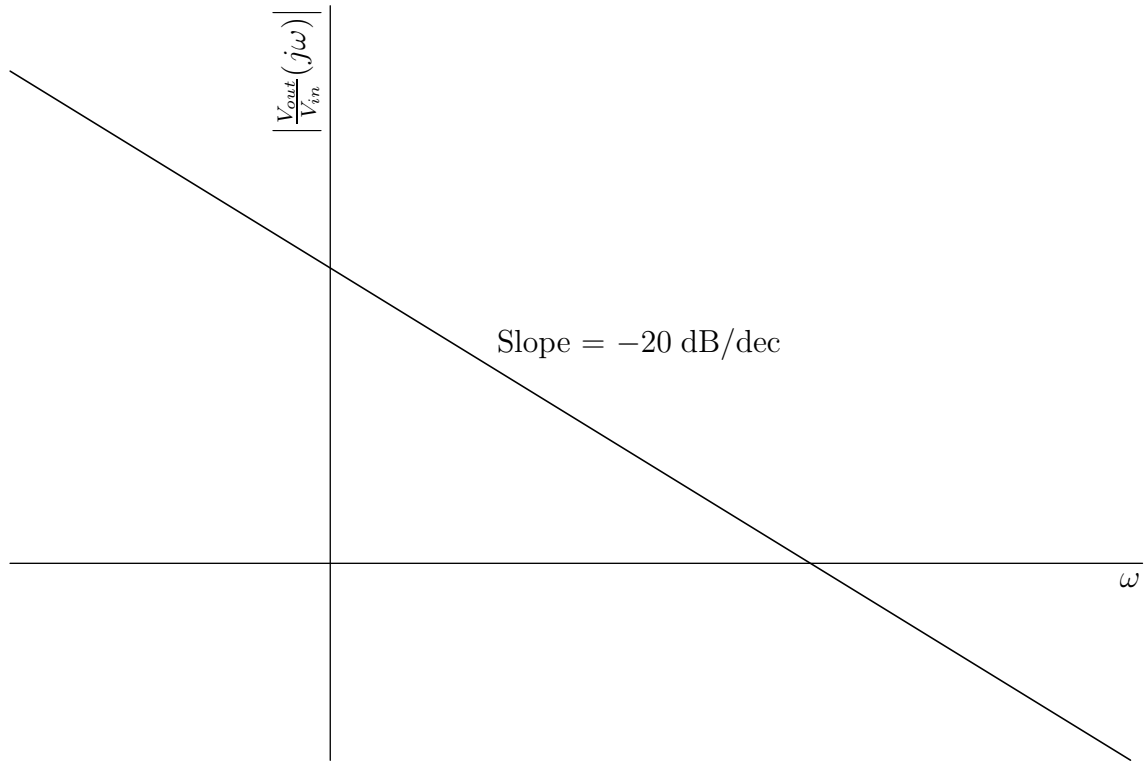11.7 The gain at arbitrarily low frequencies approaches infinity.



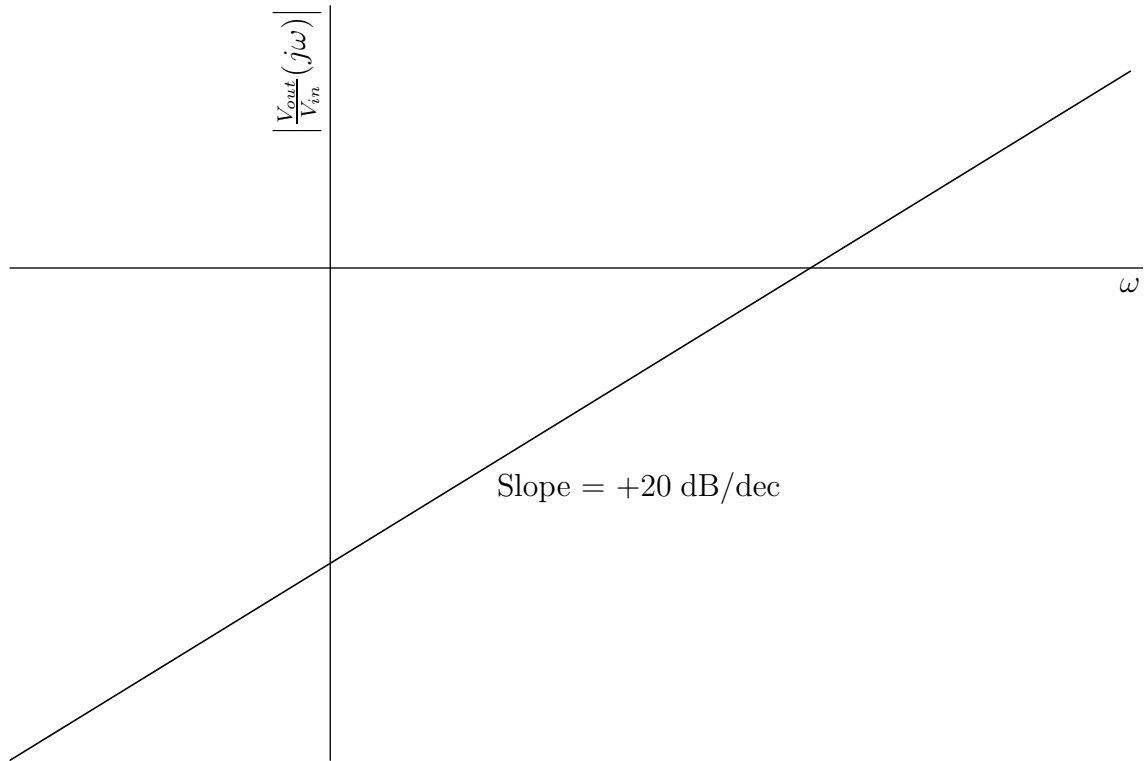11.8 The gain at arbitrarily high frequencies approaches infinity.



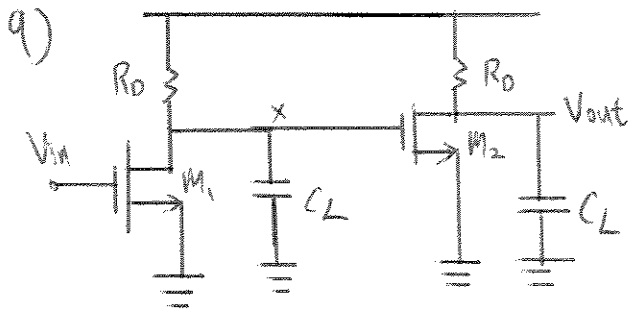



$\lambda = 0$ ,  $\downarrow$  neglect other caps.

DC gain:  $\frac{V_x}{V_{in}} = -g_m R_o$ ,  $\frac{V_{out}}{V_x} = -g_m R_o$

$$\frac{V_{out}}{V_{in}} = (g_m R_o)^2 \quad (\text{At DC})$$

2 poles at  $\frac{1}{R_o C_L}$

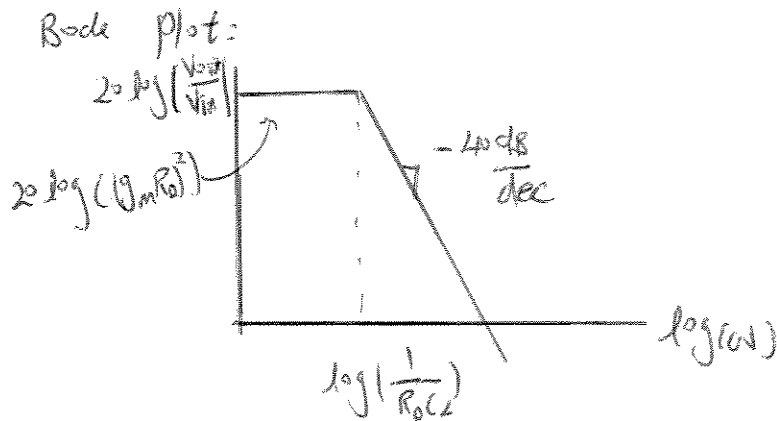

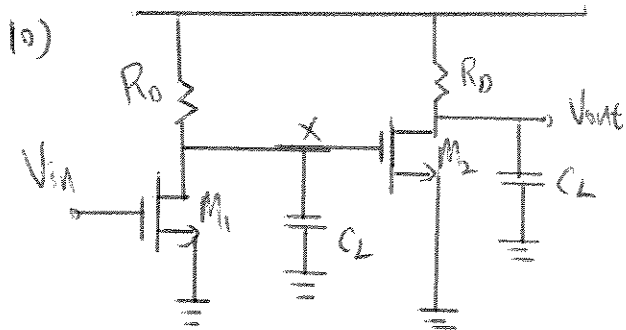

$$\frac{V_x(s)}{V_{in}} = -g_m \left( R_D \parallel \frac{1}{C_L s} \right), \quad \frac{V_{out}(s)}{V_x} = -g_m \left( \frac{R_D}{R_D C_L s + 1} \right)$$

$$= -g_m \left( \frac{R_D}{R_D C_L s + 1} \right)$$

$$H(s) = \frac{V_x(s)}{V_{in}} \frac{V_{out}(s)}{V_x} = \left( \frac{g_m R_D}{R_D C_L s + 1} \right)^2$$

$$s \rightarrow j\omega, \quad H(j\omega) = \left( \frac{g_m R_D}{1 + R_D C_L j\omega} \right)^2$$

$$|H(j\omega)| = \frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2}$$

-3dB Bandwidth:


$$\frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} = \frac{(g_m R_D)^2}{\sqrt{2}}$$

$$\Rightarrow (R_D C_L \omega)^2 + 1 = \sqrt{2}$$

$$\Rightarrow \omega = \frac{\sqrt{\sqrt{2}-1}}{R_D C_L} = \frac{0.6436}{R_D C_L} \text{ (rad/s)}$$

$$2\pi f = \frac{0.6436}{R_D C_L} \Rightarrow f = \frac{0.10243}{R_D C_L} \text{ (Hz)}$$

11)

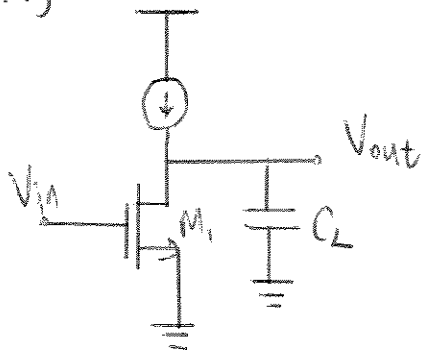

$$\lambda > 0$$

Since  $\lambda > 0$ , and we have an ideal current source, the impedance looking from out to ground is  $r_o \parallel \frac{1}{C_2 s}$

$$\text{So, } V_{out} = -g_m V_{in} \left( r_o \parallel \frac{1}{C_2 s} \right)$$


$$H(s) = -g_m \left( \frac{r_o}{r_o C_2 s + 1} \right), \quad |H(j\omega)| = \frac{g_m r_o}{\sqrt{(r_o C_2 \omega)^2 + 1}}$$

$$\text{For } \lambda \rightarrow 0, r_o \rightarrow \infty \Rightarrow H(s) \rightarrow \frac{-g_m r_o}{r_o C_2 s}$$

$H(s) = \frac{-g_m}{C_2 s}$ , A pole at origin, thus operating as an ideal integrator.



12)

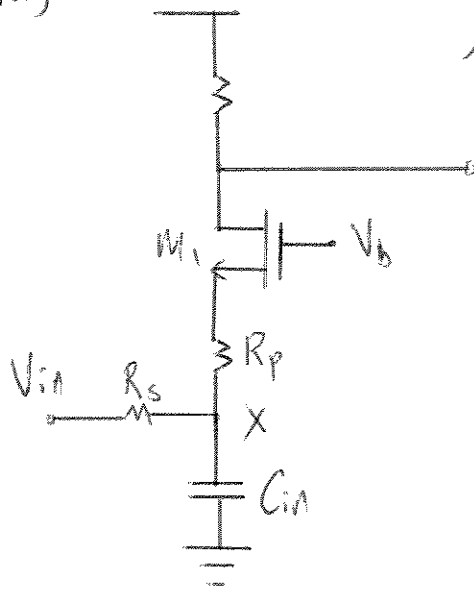


To find input pole,  
let  $V_{in} = 0$  and  
find the equivalent  
resistance and capacitance  
from node X to  
ground.

$$R_x = R_s \parallel \left( R_p + \frac{1}{g_{m1}} \right), \quad C_x = C_{in}$$

$$\omega_{p.in} = \frac{1}{C_{in} \left[ R_s \parallel \left( R_p + \frac{1}{g_m} \right) \right]}$$

$$\omega_{p.out} = \frac{1}{R_D C_L}$$

13)

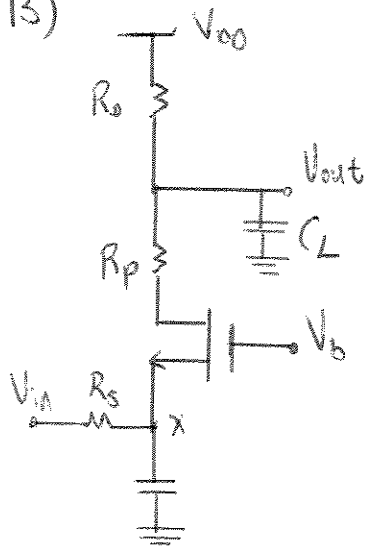

$\lambda=0$ , neglect all other caps.

$$R_x = R_s // \frac{1}{g_m}$$

$$C_x = C_{in}$$


$$R_{out} = R_o \quad (\text{since } V_o = \infty)$$

$$C_{out} = C_L$$

$$\omega_{pin} = \frac{1}{(R_s // \frac{1}{g_m}) C_{in}}$$

$$\omega_{pout} = \frac{1}{R_o C_L}$$


(4)

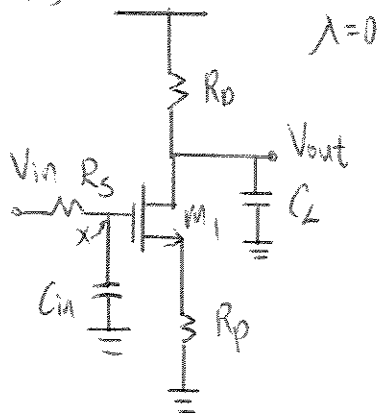

$$R_x = R_s, \quad R_{out} = R_D$$

$$C_x = C_{in}, \quad C_{out} = C_L$$
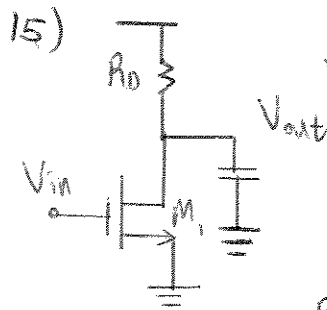
$$\omega_{pin} = \frac{1}{R_s C_{in}}, \quad \omega_{pout} = \frac{1}{R_D C_L}$$



DC Gain:  $g_m R_D = \frac{2I_D R_D}{V_{eff}}$

where  $V_{eff} = V_{GS} - V_{th}$

Band Width:  $\frac{1}{R_D C_L}$

Power Consumption:  $V_{DD} I_D$


F.O.M. (11.5) =  $\frac{\text{Gain} \times \text{Band Width}}{\text{Power Consumption}}$

$$= \frac{\left( \frac{2I_D R_D}{V_{eff}} \right) \left( \frac{1}{R_D C_L} \right)}{V_{DD} I_D}$$

$$= \frac{2}{V_{eff} V_{DD} C_L}$$


For practical design,  $V_{eff} > V_t$ , thus bipolar has a larger F.O.M. than MOS.

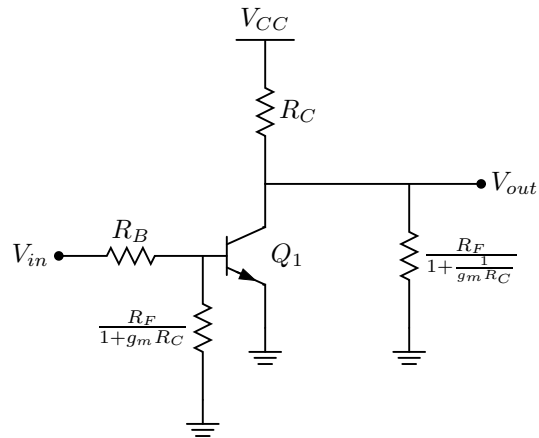11.16 Using Miller's theorem, we can split the resistor  $R_F$  as follows:




$$A_v = \boxed{-g_m \left( \frac{r_\pi \parallel \frac{R_F}{1+g_m R_C}}{R_B + r_\pi \parallel \frac{R_F}{1+g_m R_C}} \right) \left( R_C \parallel \frac{R_F}{1 + \frac{1}{g_m R_C}} \right)}$$

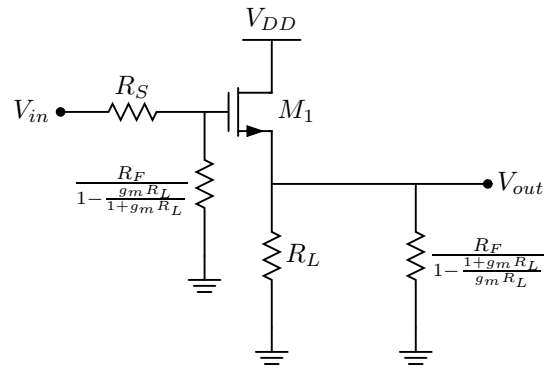11.17 Using Miller's theorem, we can split the resistor  $R_F$  as follows:




$$A_v = \left( \frac{\frac{R_F}{1 - \frac{g_m R_L}{1 + g_m R_L}}}{R_S + \frac{R_F}{1 - \frac{g_m R_L}{1 + g_m R_L}}} \right) \left( \frac{g_m \left( R_L \parallel \frac{R_F}{1 - \frac{g_m R_L}{1 + g_m R_L}} \right)}{1 + g_m \left( R_L \parallel \frac{R_F}{1 - \frac{g_m R_L}{1 + g_m R_L}} \right)} \right)$$

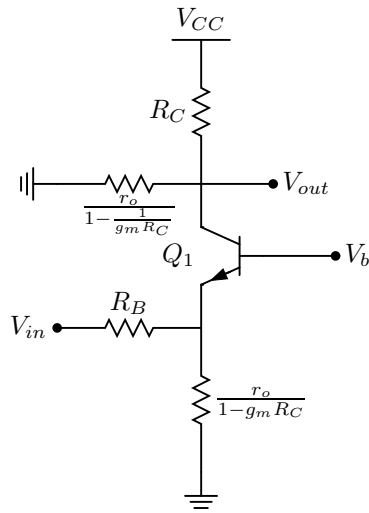11.18 Using Miller's theorem, we can split the resistor  $r_o$  as follows:


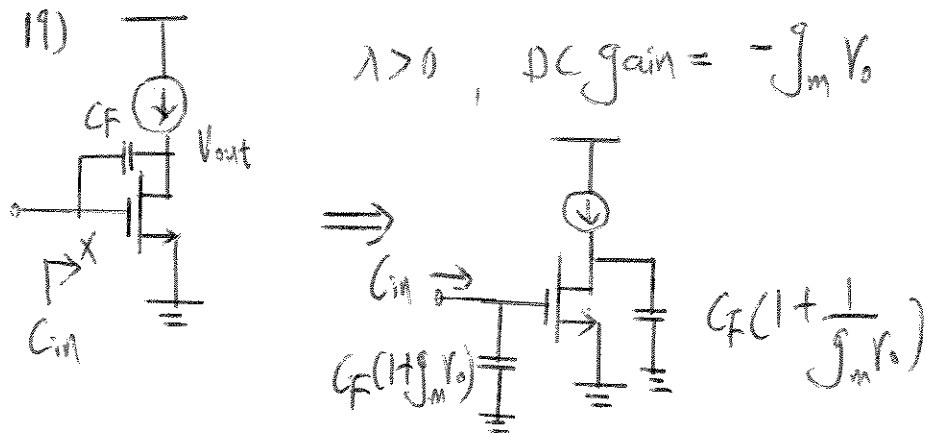
$$A_v = \boxed{g_m \left( \frac{\frac{1}{g_m} \parallel r_\pi \parallel \frac{r_o}{1-g_m R_C}}{R_B + \frac{1}{g_m} \parallel r_\pi \parallel \frac{r_o}{1-g_m R_C}} \right) \left( R_C \parallel \frac{r_o}{1 - \frac{1}{g_m R_C}} \right)}$$




$$C_{in} = C_F(1 + g_m R_o), \text{ neglecting other caps.}$$

$$\text{As } \lambda \rightarrow 0, R_o \rightarrow \infty, \text{ DC gain} \rightarrow \infty,$$

$$C_{in} \rightarrow \infty, \text{ this bandwidth will } \rightarrow 0.$$



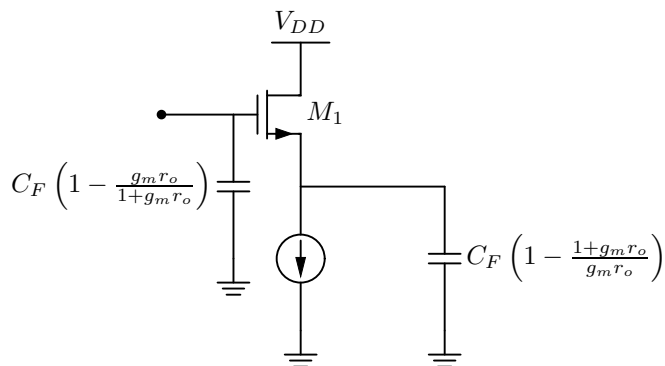
11.20 Using Miller's theorem, we can split the capacitor  $C_F$  as follows (note that the DC gain is  $A_v = \frac{g_m r_o}{1 + g_m r_o}$ ):




Thus, we have

$$C_{in} = \boxed{C_F \left(1 - \frac{g_m r_o}{1 + g_m r_o}\right)}$$

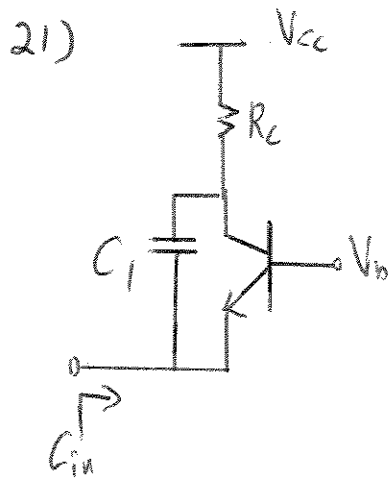As  $\lambda \rightarrow 0$ ,  $r_o \rightarrow \infty$ , meaning the gain approaches 1. When this happens, the input capacitance goes to zero.




DC gain:  $g_m R_c$

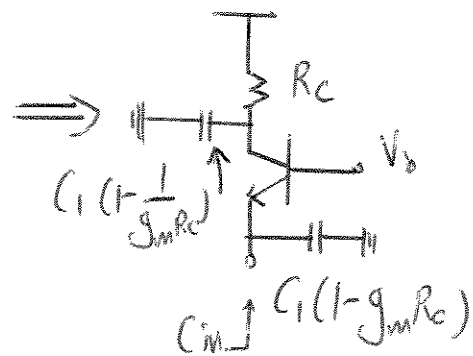


$$C_{in} = C_1 (1 - g_m R_c)$$

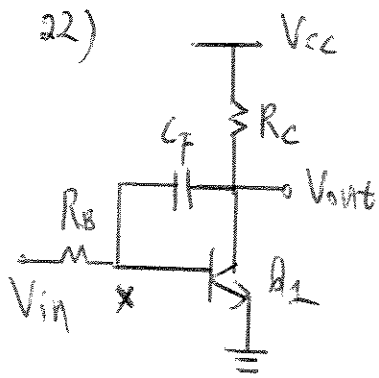If  $g_m R_c$  is designed to be larger than 1, as it normally would, we will have inductive action.



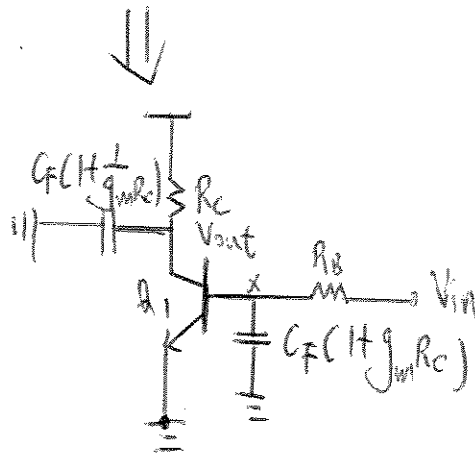DC gain (from  $x$  to out):  
 $-g_m R_c$



$$C_{in} = C_F (1 + g_m R_c)$$

$$R_{in} = R_B \parallel Y_{\pi}$$

$$C_{out} = C_F (1 + \frac{1}{g_m R_c})$$


$$R_{out} = R_c$$

$$\omega_{p1} = \frac{1}{R_B \parallel Y_{\pi} [C_F (1 + g_m R_c)]}$$


$$\omega_{pout} = \frac{1}{R_c C_F (1 + \frac{1}{g_m R_c})} \approx \frac{1}{R_c C_F}$$

(If  $g_m R_c \gg 1$ )

23)

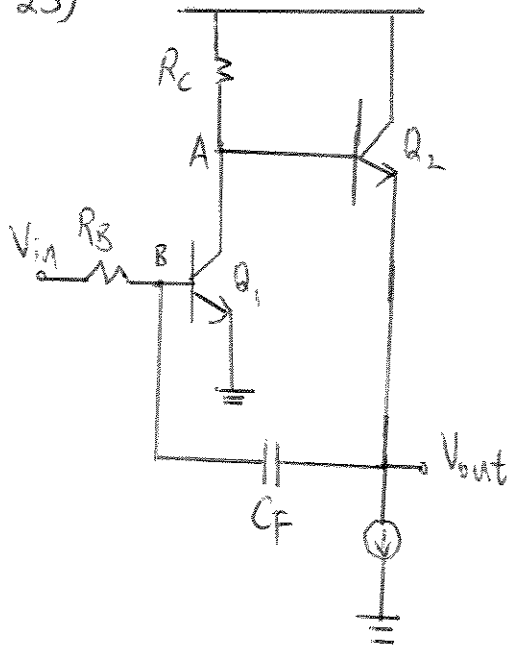

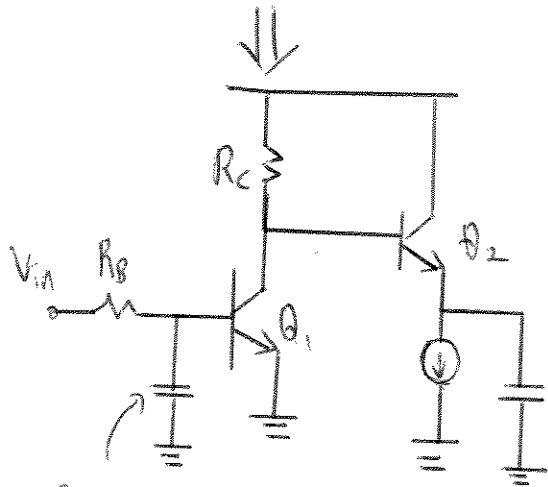The gain from B to A is  $-g_m R_C$ , from A to out is 1 (since we have an ideal current source). So the gain from B to out is  $-g_m R_C$ .



$$R_{in} = R_B \parallel r_{\pi}$$

$$C_{in} = C_F (1 + g_m R_C)$$

$$R_{out} = \frac{1}{g_m} + \frac{R_C}{\beta + 1}$$


$$C_F \left(1 + \frac{1}{g_m R_C}\right)$$

$$C_F (1 + g_m R_C)$$

$$C_{out} = C_F \left(1 + \frac{1}{g_m R_C}\right)$$

$$\omega_{p_{in}} = \frac{1}{R_B \parallel r_{\pi} [C_F (1 + g_m R_C)]}$$

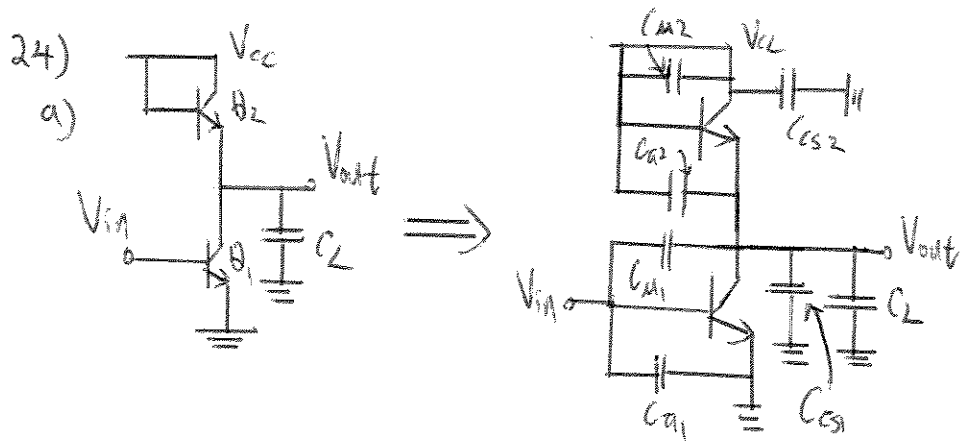
$$\omega_{p_{out}} = \frac{1}{\left(\frac{1}{g_m} + \frac{R_C}{\beta + 1}\right) C_F \left(1 + \frac{1}{g_m R_C}\right)} \approx \frac{1}{\left(\frac{1}{g_m} + \frac{R_C}{\beta + 1}\right) C_F}, \quad (g_m R_C \gg 1)$$



$C_{\mu 2}, C_{cs1}, C_L$  are in parallel

$C_{\mu 2}, C_{cs2}$  are grounded on both ends.



(and technically in parallel as well)

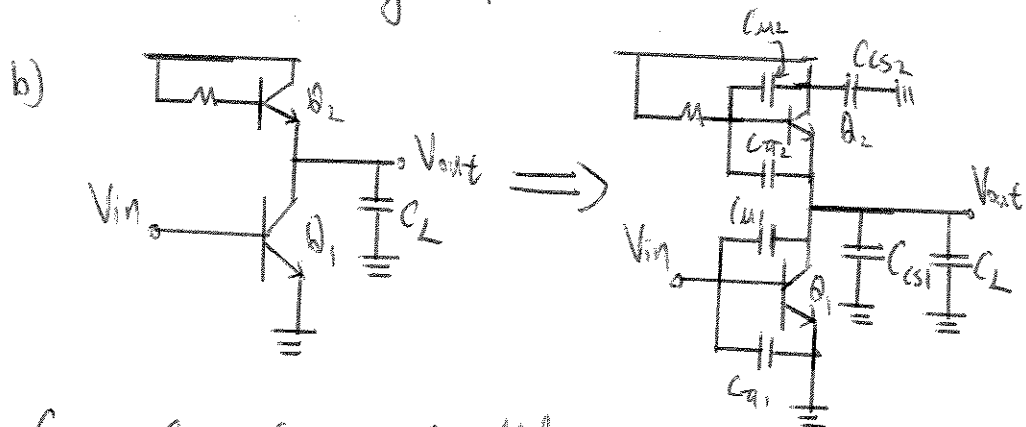


$C_{cs1}, C_L$  are in parallel

$C_{cs2}$  is grounded on both ends


24)

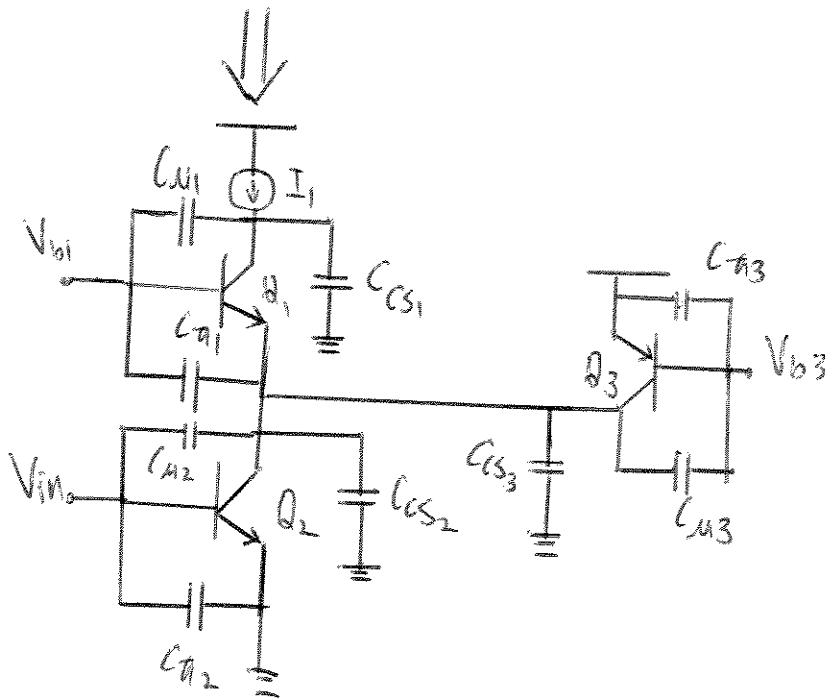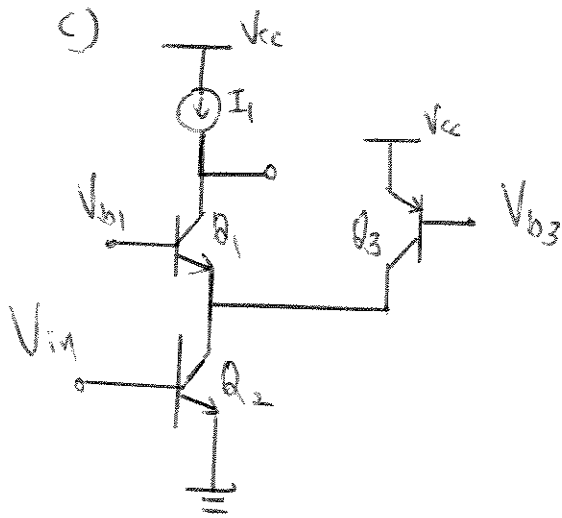

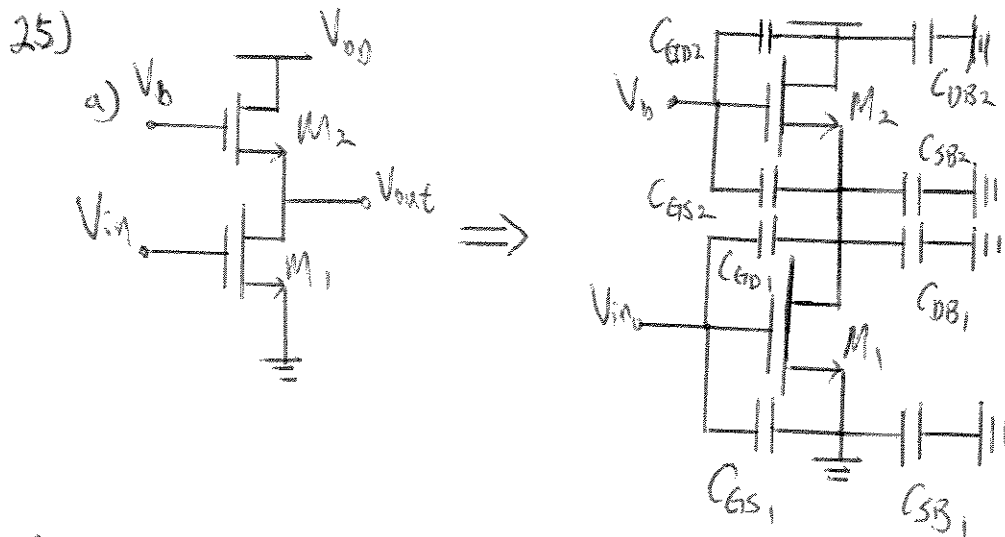$C_{\mu 1}, C_{CS 2}, C_{CS 3}, C_{\mu 3}$  are in parallel  
 $C_{\mu 1}, C_{CS 1}$  are also in parallel  
 $C_{\mu 3}$  is grounded on both ends



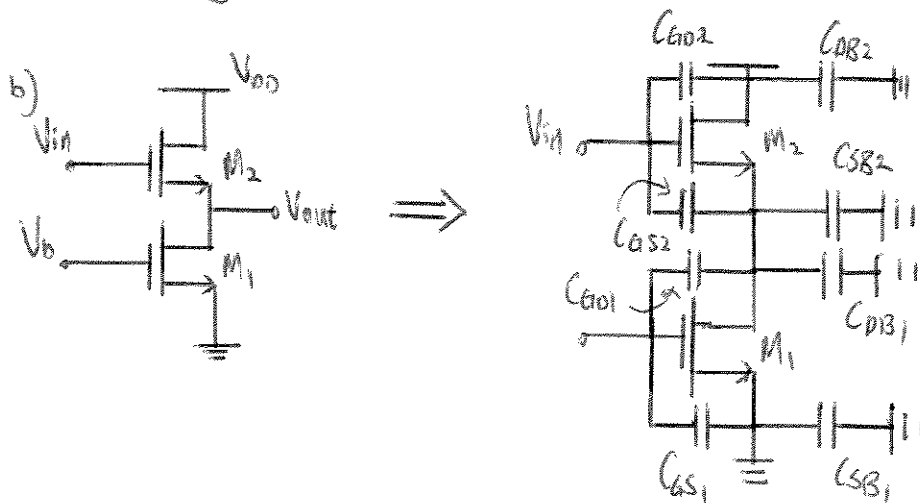$C_{GS2}$ ,  $C_{SB2}$ ,  $C_{DB1}$  are in parallel  
 $C_{GD2}$ ,  $C_{DB2}$  are in parallel and grounded on both ends  
 $C_{SB1}$  is grounded on both ends.




$C_{GD1}$ ,  $C_{DB1}$ ,  $C_{SB2}$  are in parallel

$C_{GS1}$ ,  $C_{SB1}$  are in parallel and grounded on both ends

$C_{DB2}$  is grounded on both ends.

25)

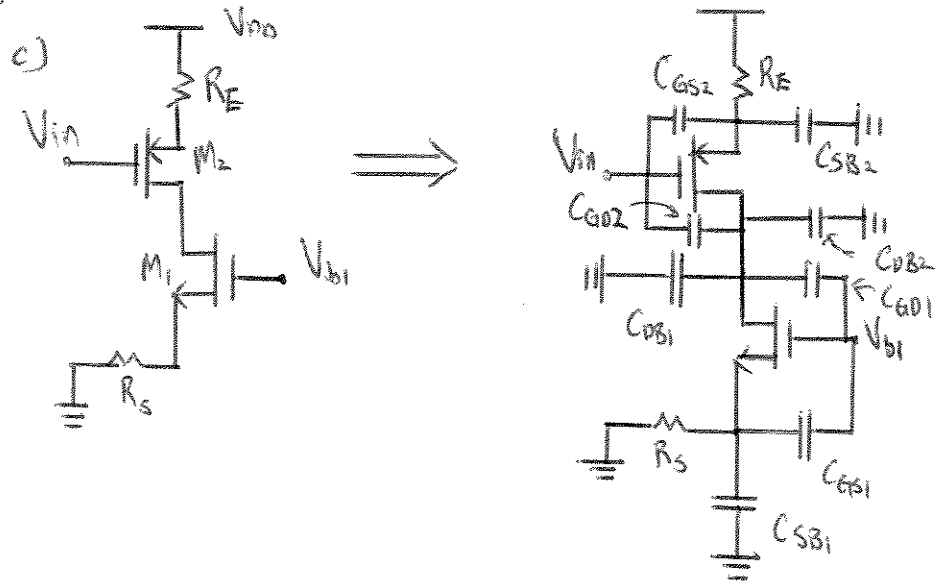


$C_{DB2}$ ,  $C_{GO1}$ ,  $C_{DB1}$ , are in parallel

$C_{SB1}$ ,  $C_{GS1}$  are also in parallel.



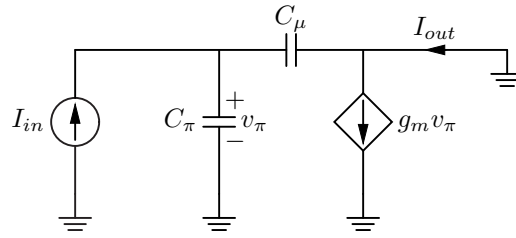11.26 At high frequencies (such as  $f_T$ ), we can neglect the effects of  $r_\pi$  and  $r_o$ , since the low impedances of the capacitors will dominate at high frequencies. Thus, we can draw the following small-signal model to find  $f_T$  (for BJTs):



$$\begin{aligned}
 I_{in} &= j\omega v_\pi (C_\pi + C_\mu) \\
 I_\pi &= \frac{I_{in}}{j\omega (C_\pi + C_\mu)} \\
 I_{out} &= g_m v_\pi - j\omega C_\mu v_\pi \\
 &= v_\pi (g_m - j\omega C_\mu) \\
 &= \frac{I_{in}}{j\omega (C_\pi + C_\mu)} (g_m - j\omega C_\mu) \\
 \frac{I_{out}}{I_{in}} &= \frac{g_m - j\omega C_\mu}{j\omega (C_\pi + C_\mu)} \\
 \left| \frac{I_{out}}{I_{in}} \right| &= \frac{\sqrt{g_m^2 + (\omega C_\mu)^2}}{\omega (C_\pi + C_\mu)} \\
 \frac{\sqrt{g_m^2 + (\omega_T C_\mu)^2}}{\omega_T (C_\pi + C_\mu)} &= 1 \\
 g_m^2 + \omega_T^2 C_\mu^2 &= \omega_T^2 (C_\pi^2 + 2C_\pi C_\mu + C_\mu^2) \\
 g_m^2 &= \omega_T^2 (C_\pi^2 + 2C_\pi C_\mu) \\
 \omega_T &= \frac{g_m}{\sqrt{C_\pi^2 + 2C_\pi C_\mu}} \\
 f_T &= \boxed{\frac{g_m}{2\pi \sqrt{C_\pi^2 + 2C_\pi C_\mu}}}
 \end{aligned}$$

The derivation of  $f_T$  for a MOSFET is identical to the derivation of  $f_T$  for a BJT, except we have  $C_{GS}$  instead of  $C_\pi$  and  $C_{GD}$  instead of  $C_\mu$ . Thus, we have:

$$f_T = \boxed{\frac{g_m}{2\pi \sqrt{C_{GS}^2 + 2C_{GS}C_{GD}}}}$$


27)

$$C_{\pi} = g_m \tau_F + C_{je}$$

$$2\pi f_T = \frac{g_m}{C_{\pi}} = \frac{g_m}{g_m \tau_F + C_{je}}$$

Assume  $C_{je}$  to be independent  
of  $I_c$ .
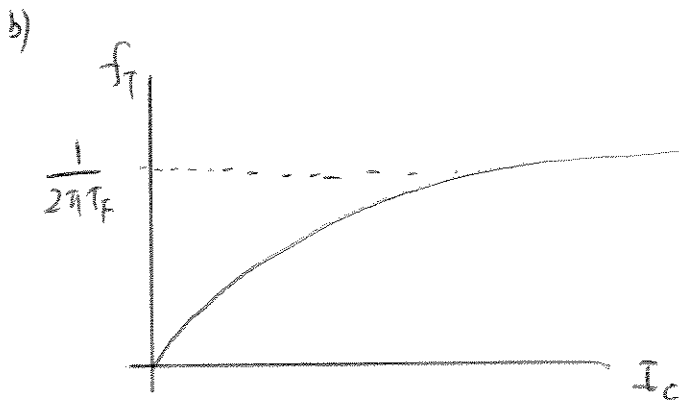
$$a) \quad 2\pi f_T = \frac{\frac{I_c}{V_T}}{\frac{I_c}{V_T} \tau_F + C_{je}} \Rightarrow f_T = \frac{I_c}{2\pi (I_c \tau_F + V_T C_{je})}$$



As  $I_c \rightarrow \infty$ ,  $f_T \rightarrow \frac{1}{2\pi \tau_F}$

28)

$$C_{GS} \approx \left(\frac{2}{3}\right) WL C_{ox}$$

$$2\pi f_T = \frac{g_m}{C_{GS}} = \frac{\frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})}{\frac{2}{3} WL C_{ox}}$$

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

29)

$$2\pi f_T = \frac{3}{2} \frac{2I_D}{WLC_{ox}} \frac{1}{(V_{GS} - V_{TH})}$$

Apparently,  $f_T$  decreases with the overdrive.

However, when we look closely,  $I_D$  is

actually proportional to  $(V_{GS} - V_{TH})^2$  (in

saturation), so  $f_T$  is proportional to

$(V_{GS} - V_{TH})$ .


30)

a) As  $W \uparrow$ ,  $(V_{GS} - V_{TH})$  has to  $\downarrow$  by

$\frac{1}{\sqrt{W}}$  in order to maintain  $I_D$  constant

Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \frac{1}{\sqrt{W}}$$

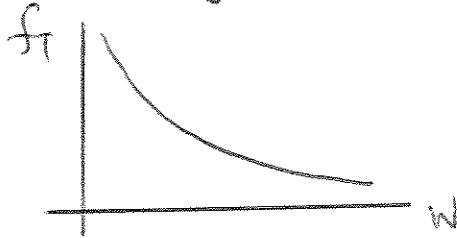

b)  $I_D \uparrow$ ,  $W$  constant it means  $V_{GS} - V_{TH} \uparrow$

With  $\sqrt{I_D}$ . Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$


$$2\pi f_T \propto \sqrt{I_D}$$

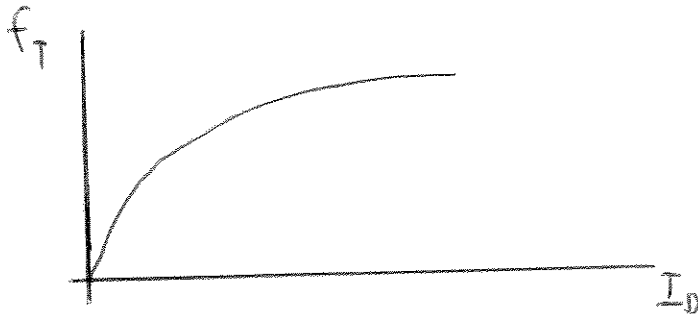

31)


Using equation  $2\pi f_T = \frac{3\mu_n}{2L^2} (V_{GS} - V_{TH})$

a)  $2\pi f_T \propto (V_{GS} - V_{TH})$

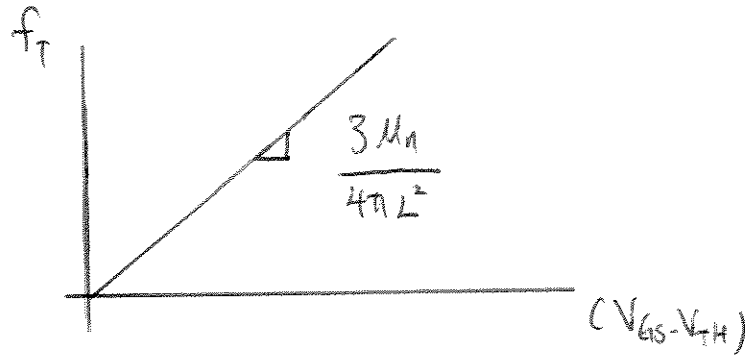

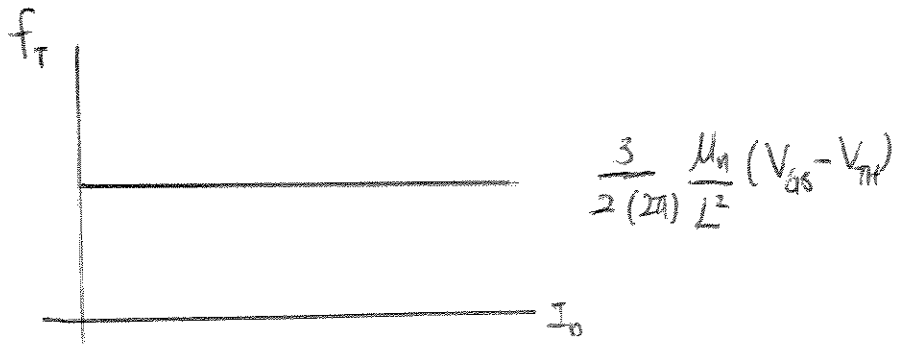b) Using equation  $2\pi f_T = \frac{3\mu_n}{2L^2} (V_{GS} - V_{TH})$


$2\pi f_T = \text{constant for all } I_D$



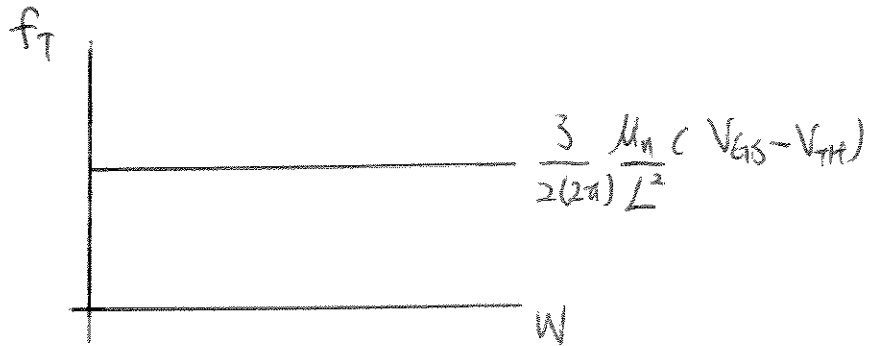32) a)


Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$

We know that  $2\pi f_T$  is constant for all  $W$ .



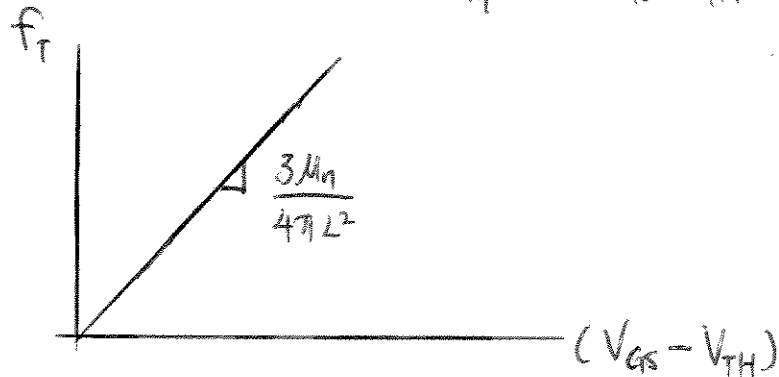b) Using equation  $2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$ ,

we know that  $2\pi f_T \propto (V_{GS} - V_{TH})$ .



33)

$$a) I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{GS} - V_{TH})^2$$

As  $L \uparrow$ , to maintain the same current and overdrive voltage,  $W \uparrow$  as well.

So  $W$  also  $2X$ .

$$b) \text{ Since } 2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH}), \text{ and}$$

$L$   $2X$  while  $(V_{GS} - V_{TH})$  is constant,

$$f_T \downarrow \text{ by } \frac{3}{4} \text{ or } f_{T_{\text{new}}} = \frac{1}{4} f_{T_{\text{old}}}.$$



34)

$$a) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$

constant  $I_D$  and  $W \uparrow$  ( $L$  constant)

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T, \text{new}} = \frac{f_{T, \text{old}}}{2}$$

$$b) V_{GS} - V_{TH} \rightarrow \frac{1}{2} (V_{GS} - V_{TH})$$


constant  $W$  and  $I_D \downarrow$  ( $L$  constant)

$$2\pi f_T = \frac{3}{2} \frac{\mu_n}{L^2} (V_{GS} - V_{TH})$$

$$f_{T, \text{new}} = \frac{f_{T, \text{old}}}{2}$$

35)


Bipolar CE Stage

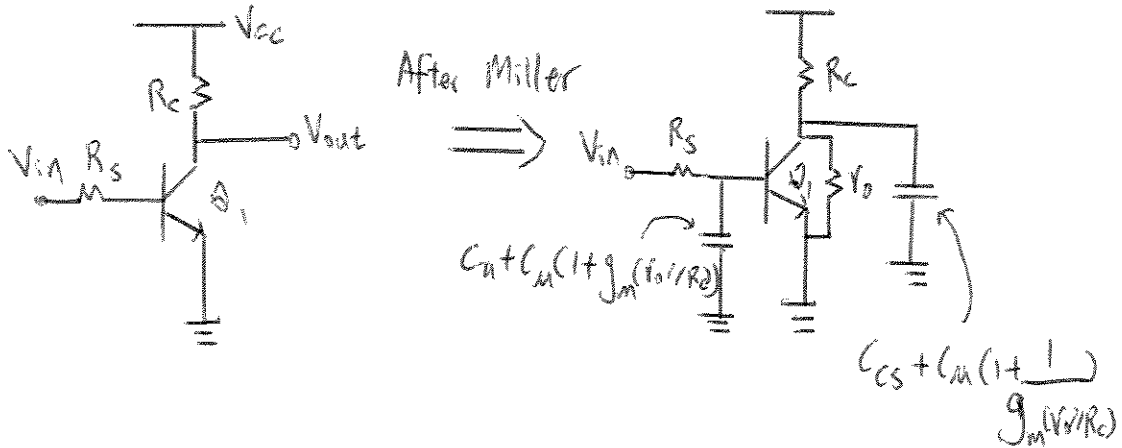

$$\omega_{p_{in}} = \frac{1}{(R_S // R_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m(R_L/R_C))]}$$

$$\omega_{p_{out}} = \frac{1}{(R_C // R_L) [C_{CS} + C_{\mu}(1 + 1/g_m(R_L/R_C))]}$$


MOS CS Stage

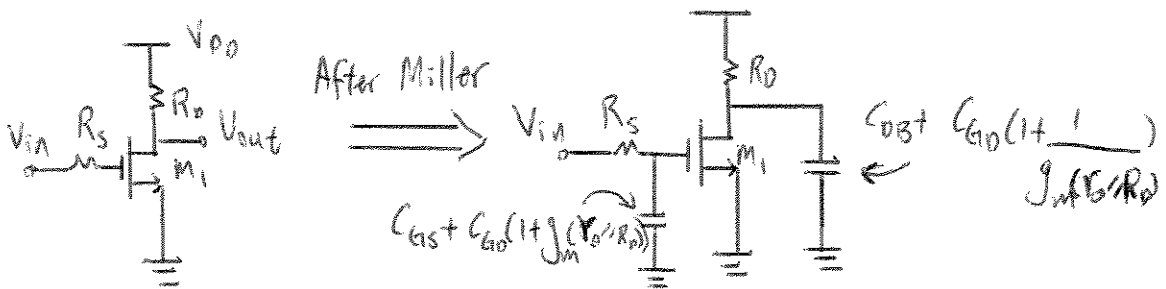

$$\omega_{p_{in}} = \frac{1}{R_S [C_{GS} + C_{GD}(1 + g_m(R_L/R_D))]}$$

$$\omega_{p_{out}} = \frac{1}{(R_D // R_L) [C_{DB} + C_{GD}(1 + 1/g_m(R_L/R_D))]}$$

36)

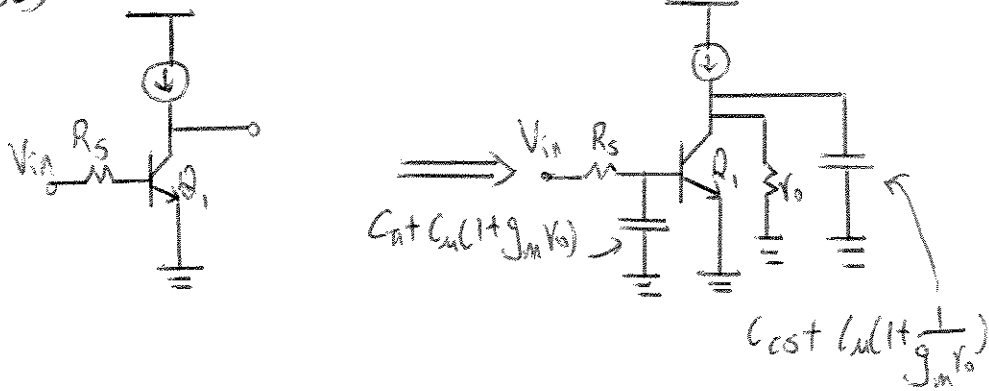

$$\omega_{p1} = \frac{1}{(R_s \parallel r_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m r_o)]}$$

$$\omega_{pout} = \frac{1}{r_o [C_{cs} + C_{\mu}(1 + 1/(g_m r_o))]}$$

$$H(s) = \frac{DC \text{ gain}}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{pout}}\right)}$$

$$H(s) = \frac{g_m r_o (r_{\pi} / (r_{\pi} + R_s))}{\left(1 + \frac{s}{1 / (R_s \parallel r_{\pi}) [C_{\pi} + C_{\mu}(1 + g_m r_o)]}\right) \left(1 + \frac{s}{1 / (r_o [C_{cs} + C_{\mu}(1 + 1/(g_m r_o))])}\right)}$$

11.37 Using Miller's theorem to split  $C_{\mu 1}$ , we have:



$$\omega_{p,in} = \frac{1}{(R_S \parallel r_{\pi 1}) \{C_{\pi 1} + C_{\mu 1} [1 + g_{m1} (r_{o1} \parallel r_{o2})]\}}$$

$$\omega_{p,out} = \frac{1}{(r_{o1} \parallel r_{o2}) \left\{ C_{\mu 2} + C_{CS1} + C_{CS2} + C_{\mu 1} \left[ 1 + \frac{1}{g_{m1} (r_{o1} \parallel r_{o2})} \right] \right\}}$$

$$\frac{V_{out}}{V_{in}}(s) = - \frac{g_{m1} \left( \frac{r_{\pi 1}}{r_{\pi 1} + R_S} \right) (r_{o1} \parallel r_{o2})}{\left( 1 + \frac{s}{\omega_{p,in}} \right) \left( 1 + \frac{s}{\omega_{p,out}} \right)}$$

3B)

a)

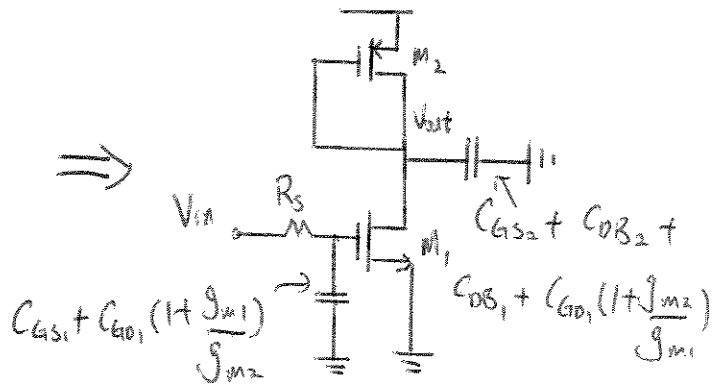
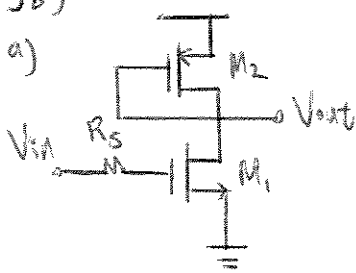


$$\text{DC gain} = -g_{m1} (V_{o1} // V_{o2} // \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{p_{in}} = \frac{1}{R_s (C_{gs1} + C_{gd1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{p_{out}} = \frac{g_{m2}}{C_{gs2} + C_{db2} + C_{db1} + C_{gd1} (1 + \frac{g_{m2}}{g_{m1}})}$$

b)

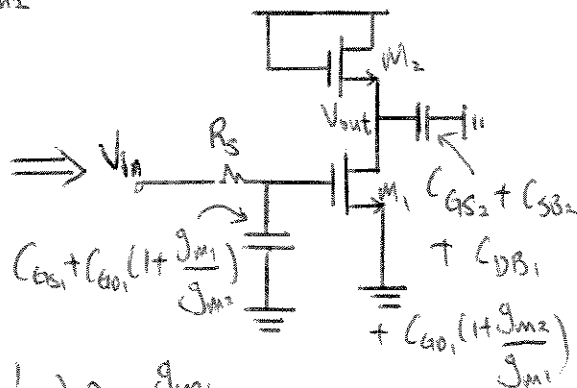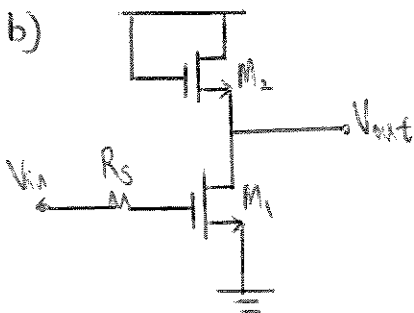


$$\text{DC gain} = -g_{m1} (V_{o1} // V_{o2} // \frac{1}{g_{m2}}) \approx -\frac{g_{m1}}{g_{m2}}$$

$$\omega_{p_{in}} = \frac{1}{R_s (C_{gs1} + C_{gd1} (1 + \frac{g_{m1}}{g_{m2}}))}$$

$$\omega_{p_{out}} = \frac{g_{m2}}{C_{sb2} + C_{gs2} + C_{db1} + C_{gd1} (1 + \frac{g_{m2}}{g_{m1}})}$$

38)

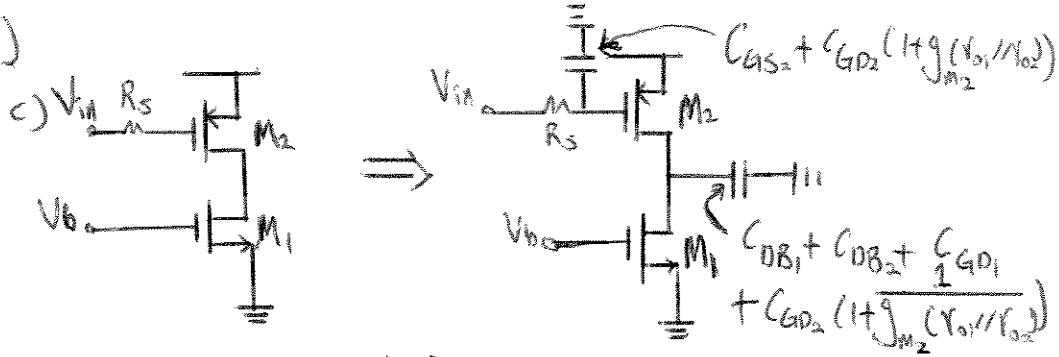

DC gain:  $-g_{m2} (r_{o1} // r_{o2})$

$$\omega_{pin} = \frac{1}{R_s (C_{gs2} + C_{GD2} (1 + g_{m2} (r_{o1} // r_{o2})))}$$

$$\omega_{pout} = \frac{1}{(r_{o1} // r_{o2}) [C_{DB1} + C_{DB2} + C_{GD1} + C_{GD2} (1 + \frac{1}{g_{m2} (r_{o1} // r_{o2})})]}$$

$$\omega_{pout} \approx \frac{1}{(r_{o1} // r_{o2}) [C_{DB1} + C_{DB2} + C_{GD1} + C_{GD2}]}$$

Since  $g_{m2} (r_{o1} // r_{o2}) \gg 1$

11.39 (a)

$$\omega_{p,in} = \frac{1}{R_S [C_{GS} + C_{GD} (1 + g_m R_D)]} = \boxed{3.125 \times 10^{10} \text{ rad/s}}$$

$$\omega_{p,out} = \frac{1}{R_D \left[ C_{DB} + C_{GD} \left( 1 + \frac{1}{g_m R_D} \right) \right]} = \boxed{3.846 \times 10^{10} \text{ rad/s}}$$

(b)

$$\frac{V_{out}}{V_{Thev}}(s) = \frac{(C_{GD}s - g_m) R_D}{as^2 + bs + 1}$$

$$a = R_S R_D (C_{GS} C_{GD} + C_{DB} C_{GD} + C_{GS} C_{DB}) = 2.8 \times 10^{-22}$$

$$b = (1 + g_m R_D) C_{GD} R_S + R_S C_{GS} + R_D (C_{GD} + C_{DB}) = 5.7 \times 10^{-11}$$

Setting the denominator equal to zero and solving for  $s$ , we have:

$$s = \frac{-b \pm \sqrt{b^2 - 4a}}{2a}$$

$$|\omega_{p1}| = \boxed{1.939 \times 10^{10} \text{ rad/s}}$$

$$|\omega_{p2}| = \boxed{1.842 \times 10^{11} \text{ rad/s}}$$

We can see substantial differences between the poles calculated with Miller's approximation and the poles calculated from the transfer function directly. We can see that Miller's approximation does a reasonably good job of approximating the input pole (which corresponds to  $|\omega_{p1}|$ ). However, the output pole calculated with Miller's approximation is off by nearly an order of magnitude when compared to  $\omega_{p2}$ .

11.40 (a) Note that the DC gain is  $A_v = -\infty$  if we assume  $V_A = \infty$ .

$$\omega_{p,in} = \frac{1}{(R_S \parallel r_\pi) [C_\pi + C_\mu (1 - A_v)]} = \boxed{0}$$

$$\omega_{p,out} = \boxed{0}$$

(b)

$$\frac{V_{out}}{V_{Thev}}(s) = \lim_{R_L \rightarrow \infty} \frac{(C_\mu s - g_m) R_L}{as^2 + bs + 1}$$

$$a = (R_S \parallel r_\pi) R_L (C_\pi C_\mu + C_{CS} C_\mu + C_\pi C_{CS})$$

$$b = (1 + g_m R_L) C_\mu (R_S \parallel r_\pi) + (R_S \parallel r_\pi) C_\pi + R_L (C_\mu + C_{CS})$$

$$\lim_{R_L \rightarrow \infty} \frac{(C_\mu s - g_m) R_L}{as^2 + bs + 1} = \frac{C_\mu s - g_m}{[(R_S \parallel r_\pi) (C_\pi C_\mu + C_{CS} C_\mu + C_\pi C_{CS})] s^2 + [g_m C_\mu (R_S \parallel r_\pi) + C_\mu + C_{CS}] s}$$

$$= \frac{C_\mu s - g_m}{s \{ (R_S \parallel r_\pi) (C_\pi C_\mu + C_{CS} C_\mu + C_\pi C_{CS}) s + [g_m C_\mu (R_S \parallel r_\pi) + C_\mu + C_{CS}] \}}$$

$$|\omega_{p1}| = \boxed{0}$$

$$|\omega_{p2}| = \boxed{\frac{g_m C_\mu (R_S \parallel r_\pi) + C_\mu + C_{CS}}{(R_S \parallel r_\pi) (C_\pi C_\mu + C_{CS} C_\mu + C_\pi C_{CS})}}$$

We can see that the Miller approximation correctly predicts the input pole to be at DC. However, it incorrectly estimates the output pole to be at DC as well, when in fact it is not, as we can see from the direct analysis.




11.41

$$\begin{aligned}
 |\omega_{p1}| &= \lim_{R_L \rightarrow \infty} \frac{1}{(1 + g_m R_L) C_\mu (R_S \parallel r_\pi) + (R_S \parallel r_\pi) C_\pi + R_L (C_\mu + C_{CS})} = \boxed{0} \\
 |\omega_{p2}| &= \lim_{R_L \rightarrow \infty} \frac{(R_S \parallel r_\pi) R_L (C_\pi C_\mu + C_{CS} C_\mu + C_\pi C_{CS})}{(1 + g_m R_L) C_\mu (R_S \parallel r_\pi) + (R_S \parallel r_\pi) C_\pi + R_L (C_\mu + C_{CS})} \\
 &= \boxed{\frac{(R_S \parallel r_\pi) (C_\pi C_\mu + C_{CS} C_\mu + C_\pi C_{CS})}{g_m C_\mu (R_S \parallel r_\pi) + C_\mu + C_{CS}}}
 \end{aligned}$$

The dominant-pole approximation gives the same results as analyzing the transfer function directly, as in Problem 40(b).

42)

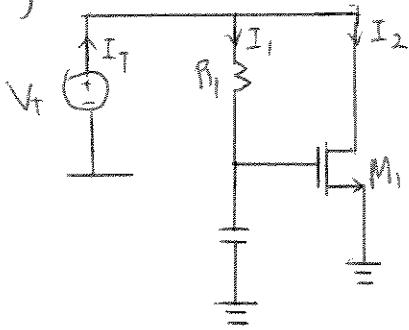

$\lambda=0$ , and neglect other capacitances.

$$I_T = I_1 + I_2$$


$$I_1 = \frac{V_T}{(R_1 + \frac{1}{C_1 s})}, \quad I_2 = \frac{g_m V_T}{C_1 R_1 s + 1}$$

$$I_T = \frac{C_1 s V_T}{C_1 R_1 s + 1} + \frac{g_m V_T}{C_1 R_1 s + 1} \Rightarrow \frac{V_T}{I_T} = \frac{C_1 R_1 s + 1}{C_1 s + g_m}$$

$$s \rightarrow j\omega \Rightarrow \frac{C_1 R_1 (j\omega) + 1}{C_1 j\omega + g_m} = Z_T(j\omega)$$


$$|Z_T| = |Z_{in}| = \frac{\sqrt{(C_1 R_1 \omega)^2 + 1}}{\sqrt{C_1^2 \omega^2 + g_m^2}} = \frac{\sqrt{C_1 R_1 \omega^2 + 1}}{g_m \sqrt{\left(\frac{C_1 \omega}{g_m}\right)^2 + 1}}$$

At  $\omega = \frac{1}{C_1 R_1}$ , we have a zero, at  $\omega = \frac{g_m}{C_1}$ , we have a pole. If  $R_1 > \frac{1}{g_m}$ , the zero  $C_1$  is at a lower frequency than the pole, and the bode-plot for magnitude would look like the following.

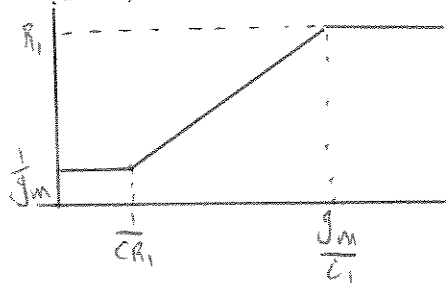 $20 \log(Z_{in})$ 


The bode-plot shows an impedance that increases with frequency, an inductive behavior.

43)

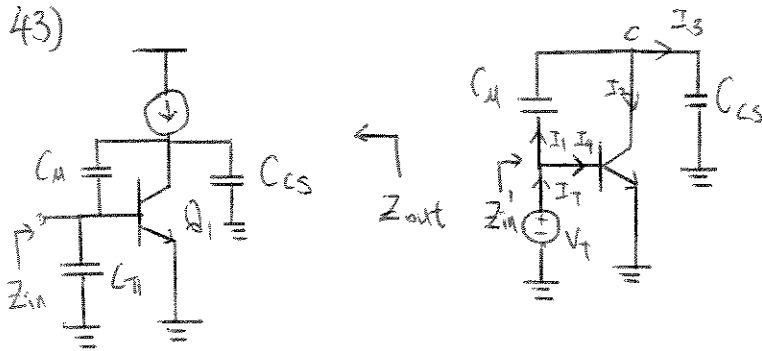

$$Z_{in} = Z_{in}' \parallel \frac{1}{C_{in} s}, \quad I_T = I_1 + I_4 = C_{\mu} s V_{bc} + \frac{g_m V_T}{\beta}$$

$$V_{bc} = V_T - V_c, \quad V_c = (I_1 - g_m V_T) \frac{1}{C_{CS} s}$$

$$I_1 = \left[ V_T - (I_1 - g_m V_T) \frac{1}{C_{CS} s} \right] C_{\mu} s$$

$$I_1 = V_T \left[ C_{\mu} s + \frac{g_m C_{\mu}}{C_{CS}} \right] / \left( 1 + \frac{C_{\mu}}{C_{CS}} \right)$$


$$I_T = V_T \left[ C_{\mu} s + \frac{g_m C_{\mu}}{C_{CS}} \right] / \left( 1 + \frac{C_{\mu}}{C_{CS}} \right) + \frac{g_m V_T}{\beta}$$

$$Z_{in}' = \frac{V_T}{I_T} = \frac{1}{\frac{g_m}{\beta} + \frac{C_{\mu} s}{\left( 1 + \frac{C_{\mu}}{C_{CS}} \right)} + \frac{g_m C_{\mu}}{\left( 1 + \frac{C_{\mu}}{C_{CS}} \right) C_{CS}}}$$

$$Z_{in} = Z_{in}' \parallel \frac{1}{C_{in} s} = r_{\pi} \parallel \frac{1}{\frac{C_{CS} C_{\mu} s}{C_{CS} + C_{\mu}}} \parallel \frac{1}{C_{in} s} \parallel \frac{C_{CS} + C_{\mu}}{g_m C_{\mu}}$$

$$Z_{out} = \frac{1}{(C_{out} + C_{CS}) s}$$

44)

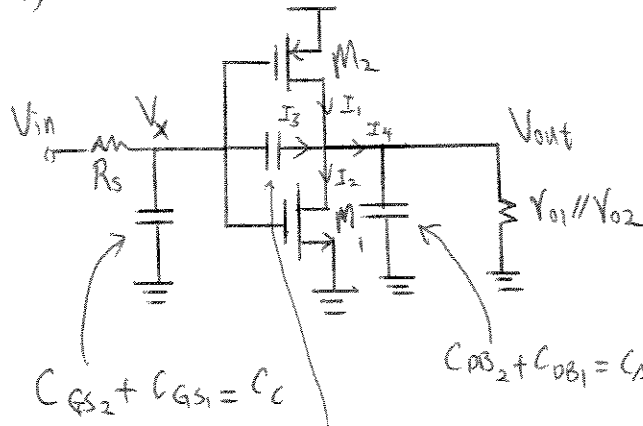 $\lambda > 0$ 

$$C_{GS2} + C_{GS1} = C_C$$

$$C_{GD1} + C_{GD2} = C_B$$

$$C_{DB2} + C_{DB1} = C_A$$

$$V_{out} = I_4 \left( Y_{01} // Y_{02} // \frac{1}{[C_{DB2} + C_{DB1}]s} \right) \xrightarrow{Z_{out}}$$

$$I_4 = I_1 + I_3 - I_2$$

$$I_1 = (0 - V_x) g_{m2}$$

$$I_2 = V_x g_{m1}$$

$$I_3 = (V_x - V_{out}) (C_{GD1} + C_{GD2}) s$$

$$I_4 = -V_x g_{m2} + (V_x - V_{out}) C_B s - V_x g_{m1}$$

$$V_{out} = Z_{out} [-V_x (g_{m2} + g_{m1}) + (V_x - V_{out}) C_B s]$$

Writing a node equation at X.

$$\frac{V_x - V_{in}}{R_s} + V_x C_C s + (V_x - V_{out}) C_B s = 0$$

$$V_x = \frac{V_{out} C_B s + V_{in}/R_s}{(1/R_s + C_C s + C_B s)}$$

$$(1/R_s + C_C s + C_B s)$$

44)

Substitute everything and we get

$$V_{out} = Z_{out} \left[ -(g_{m1} + g_{m2}) \left( \frac{V_{out} C_B s + V_{in}/R_s}{1/R_s + C_c s + C_B s} \right) + \left( \frac{V_{out} C_B s + V_{in}/R_s}{1/R_s + C_c s + C_B s} - V_{out} \right) C_B s \right]$$

Collect all the  $V_{out}$ 's on one-side and likewise for  $V_{in}$ 's,  
we will get

$$\frac{V_{out}}{V_{in}} = \frac{Z_{out} (C_B s - (g_{m1} + g_{m2}))}{R_s}$$


$$\frac{1}{R_s + (C_c + C_B)s + Z_{out} C_B s (g_{m1} + g_{m2}) + Z_{out} C_B s \left( \frac{1}{R_s} + (C_c + C_B)s \right) - Z_{out} C_B^2 s^2}$$

$$\text{where } Z_{out} = Y_{o1} // Y_{o2} // \frac{1}{[C_{DB1} + C_{DB2}]s}$$

$$C_B = C_{GD1} + C_{GD2}$$

$$C_c = C_{CS1} + C_{CS2}$$

45)

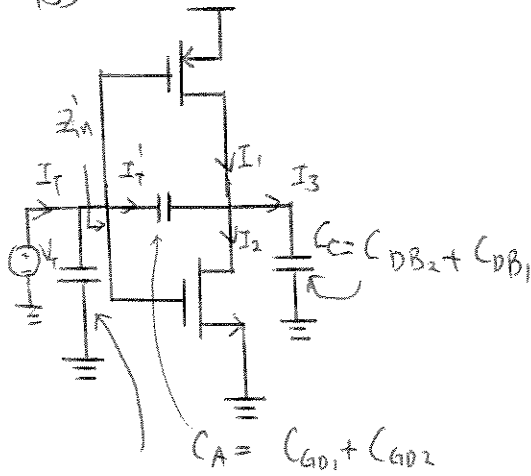

$$Z_{in} = \frac{V_T}{I_T} = \frac{1}{C_B} \parallel Z_{in}'$$

$$Z_{in}' = \frac{V_T}{I_T'}$$

$$C_B = C_{GS1} + C_{GS2}$$

$$I_T' = \left[ V_T - \left( I_3 \frac{1}{C_{CS}} \right) \right] C_{AS}$$

$$I_3 = I_T' - V_T g_{m2} - g_{m1} V_T$$


$$\text{We get } \Rightarrow I_T' \left( 1 + \frac{C_A}{C_C} \right) = V_T \left[ C_{AS} + (g_{m1} + g_{m2}) \frac{C_A}{C_C} \right]$$

$$Z_{in}' = \frac{V_T}{I_T'} = \frac{\left( 1 + \frac{C_A}{C_C} \right)}{\left[ C_{AS} + (g_{m1} + g_{m2}) \frac{C_A}{C_C} \right]}$$

$$Z_{in} = \frac{1}{[C_{GS1} + C_{GS2}]s} \parallel \frac{\left( 1 + \frac{C_{GD1} + C_{GD2}}{C_{DB1} + C_{DB2}} \right)}{\left[ (C_{GD1} + C_{GD2})s + (g_{m1} + g_{m2}) \frac{C_{GD1} + C_{GD2}}{C_{DB2} + C_{DB1}} \right]}$$

46)

a)

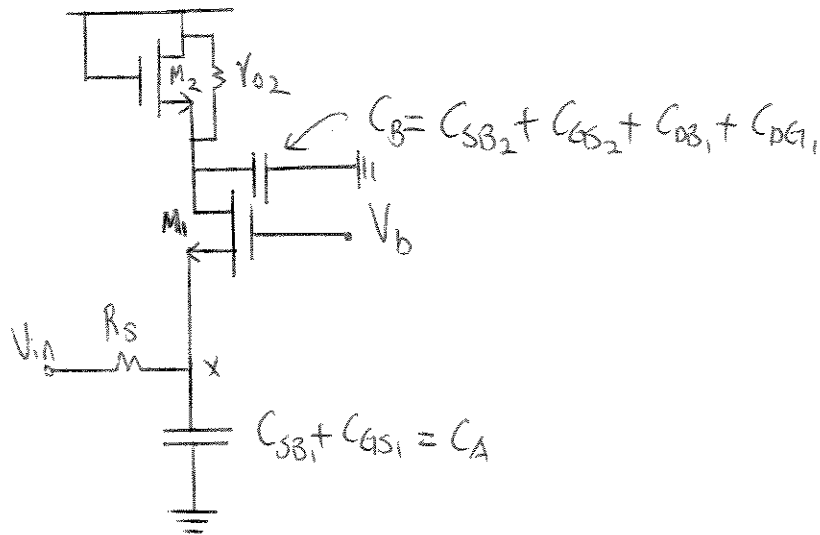

$$V_{out} = -(0 - V_x) g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_{BS}} \right] = V_x g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_{BS}} \right]$$

Node equation at X,  $\frac{V_x - V_{in}}{R_s} + V_x C_A s - g_m (0 - V_x) = 0$

$$V_x \left( \frac{1}{R_s} + C_A s + g_m \right) = \frac{V_{in}}{R_s} \Rightarrow V_x = \frac{V_{in}}{(1 + R_s C_A s + R_s g_m)}$$

substitute in  $V_x$  and solving for  $V_{out}/V_{in} \Rightarrow$


$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} \left[ \frac{1}{g_{m2}} \parallel \frac{1}{C_{BS}} \right]}{(1 + R_s C_A s + R_s g_m)}$$

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (1/g_{m2}) s + 1) (1 + R_s C_A s + R_s g_m)}$$

Where  $C_B = C_{SB2} + C_{AS2} + C_{OB1} + C_{OG1}$

$$C_A = C_{SB1} + C_{AS1}$$

46)

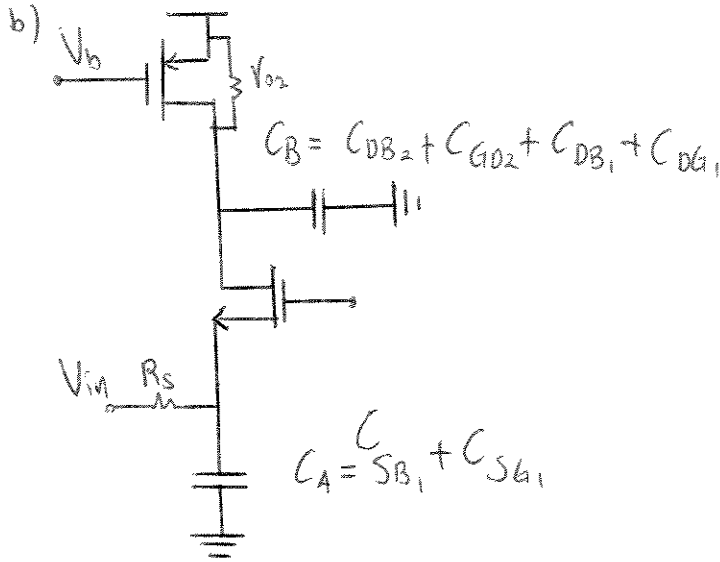

Similar to part a), with  $\frac{1}{g_{m2}}$  replaced by  $V_{o2}$ ,  
and different  $C_B$

$$\text{So } \frac{V_{out}}{V_{in}} = \frac{g_{m1} V_{o2}}{(C_B V_{o2} s + 1)(1 + R_S C_A s + R_S g_{m1})}$$


Where  $C_B = C_{DB2} + C_{GO2} + C_{DB1} + C_{DG1}$

$$C_A = C_{SB1} + C_{SE1}$$



46)

c)

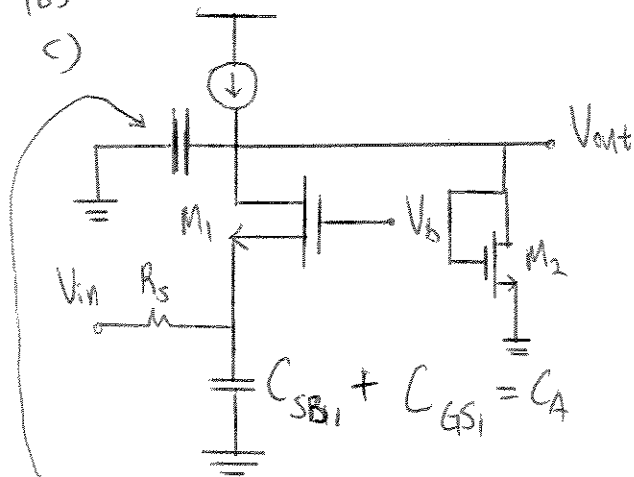

$$C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$$


AC-wise, this circuit is very similar to part a), Its transfer function is the same as part a), except for  $C_B$ .

$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} (1/g_{m2})}{(C_B (V_{g_{m2}})^2 s + 1) (1 + R_S C_A s + R_S g_{m1})}$$

Where  $C_B = C_{DB1} + C_{GD1} + C_{DB2} + C_{GS2}$

$$C_A = C_{SB1} + C_{GS1}$$

47)

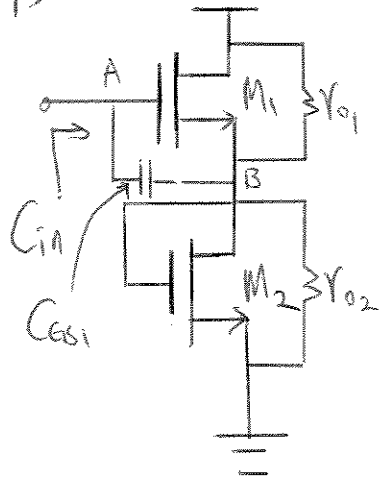

DC gain from A to B:

$$A_V = \frac{\frac{1}{g_{m2}} \parallel R_{O1} \parallel R_{O2}}{\frac{1}{g_{m2}} \parallel R_{O1} \parallel R_{O2} + \frac{1}{g_{m1}}}$$

$$A_V \approx \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m2}} + \frac{1}{g_{m1}}} = \frac{g_{m1}}{g_{m1} + g_{m2}}$$


since  $g_{m1} r_{O1} \gg 1$

Using Miller's Capacitance:

$$C_{in} = C_{GS1} (1 - A_V) = C_{GS1} \left( 1 - \frac{g_{m1}}{g_{m1} + g_{m2}} \right)$$

$$C_{in} = C_{GS1} \left( \frac{g_{m2}}{g_{m2} + g_{m1}} \right)$$

48)

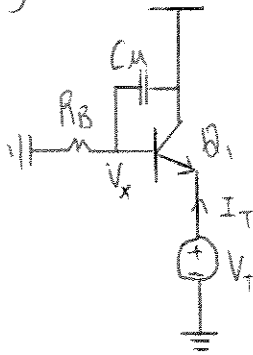

$V_A = \infty$ ,

$\frac{\beta}{\beta+1} \approx 1$ , if  $\beta \gg 1$

$$I_T = -(V_x - V_T) g_m \approx -(V_x - V_T) g_m$$

$$V_x = \frac{I_T}{\beta} \left( R_B \parallel \frac{1}{C_{\mu} s} \right)$$

$$I_T = \left( V_T - \frac{I_T}{\beta} \left( R_B \parallel \frac{1}{C_{\mu} s} \right) \right) g_m$$

$$I_T = g_m V_T - \frac{g_m}{\beta} \left( R_B \parallel \frac{1}{C_{\mu} s} \right) I_T$$


$$I_T \left( 1 + \frac{g_m}{\beta} \left( R_B \parallel \frac{1}{C_{\mu} s} \right) \right) = g_m V_T$$

$$\frac{V_T}{I_T} = \frac{1}{g_m} + \frac{R_B \parallel \frac{1}{C_{\mu} s}}{\beta} = \frac{\beta C_{\mu} R_B (s + \frac{\beta + R_B g_m}{\beta C_{\mu} R_B})}{g_m \beta (1 + C_{\mu} R_B s)}$$

Zero:  $\frac{\beta + R_B g_m}{\beta C_{\mu} R_B}$ , Pole:  $\frac{1}{C_{\mu} R_B}$

At DC,  $|Z_{out}| = \frac{1}{g_m} + \frac{R_B}{\beta}$


At very high freq:  $|Z_{out}| = \frac{1}{g_m}$

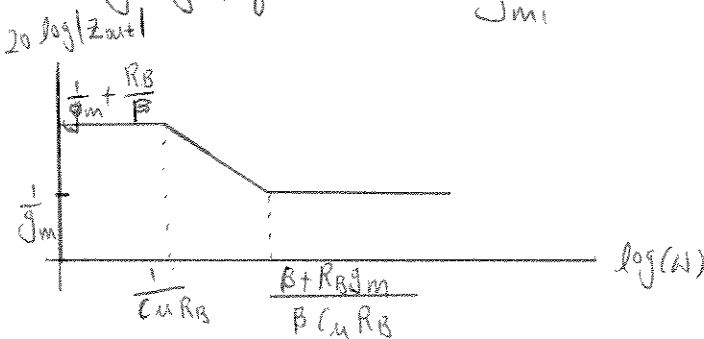

$$\begin{aligned}
\omega_{p1} &= \frac{1}{(R_B \parallel r_{\pi1}) \left\{ C_{\pi1} + C_{\mu1} \left[ 1 + g_{m1} \left( \frac{1}{g_{m2}} \parallel r_{\pi2} \right) \right] \right\}} \\
&\approx \frac{1}{(R_B \parallel r_{\pi1}) \left\{ C_{\pi1} + C_{\mu1} \left[ 1 + \frac{g_{m1}}{g_{m2}} \right] \right\}} \\
I_{C1} &= 4I_{C2} \Rightarrow g_{m1} = 4g_{m2} \\
\omega_{p1} &= \frac{1}{(R_B \parallel r_{\pi1}) (C_{\pi1} + 5C_{\mu1})} \\
\omega_{p2} &\approx \frac{1}{\frac{1}{g_{m2}} \left[ C_{CS1} + C_{CS3} + C_{\mu3} + C_{\pi2} + C_{\mu1} \left( 1 + \frac{g_{m2}}{g_{m1}} \right) \right]} \\
&= \frac{g_{m2}}{C_{CS1} + C_{CS3} + C_{\mu3} + C_{\pi2} + \frac{5}{4}C_{\mu1}} \\
\omega_{p3} &= \frac{1}{R_C (C_{CS2} + C_{\mu2})}
\end{aligned}$$

Miller's effect is more significant here than in a standard cascode. This is because the gain in the common-emitter stage is increased to four in this topology, where it is about one in a standard cascode. This means that the capacitor  $C_{\mu1}$  will be multiplied by a larger factor when using Miller's theorem.

50)

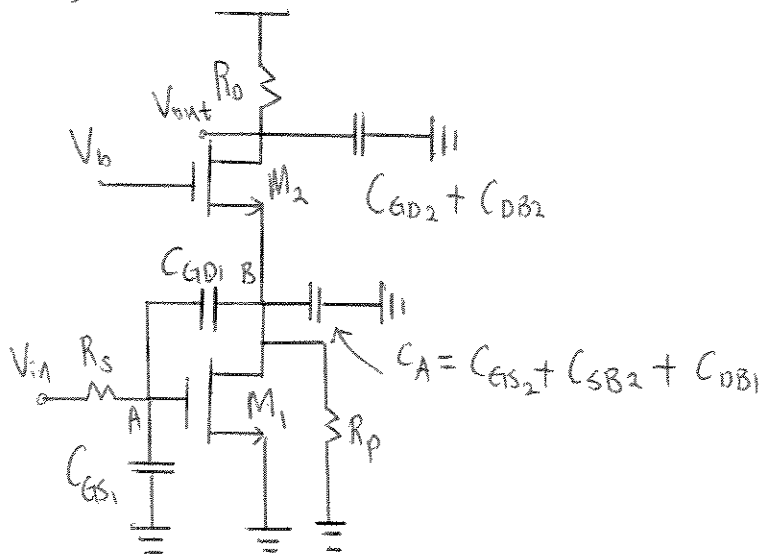

DC gain from A to B is  $-g_{m1} (R_p \parallel \frac{1}{g_{m2}})$


Applying Miller's Theorem:

$$\omega_{pin} (\omega_{pA}) = \frac{1}{R_s (C_{GS1} + C_{GD1} (1 + g_{m1} (R_p \parallel \frac{1}{g_{m2}})))}$$

$$\omega_{pB} = \frac{1}{R_p \parallel \frac{1}{g_{m2}} [C_{GS2} + C_{SB2} + C_{DB1} + C_{GD1} (1 + 1/g_{m1} (R_p \parallel \frac{1}{g_{m2}}))]}$$

$$\omega_{pout} = \frac{1}{R_o (C_{GD2} + C_{DB2})}$$

51)

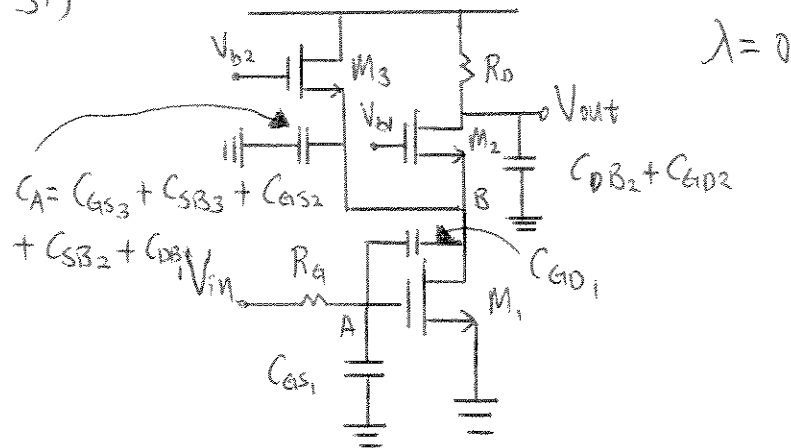

DC gain from A to B:  $-g_{m1} \left( \frac{1}{g_{m3}} \parallel \frac{1}{g_{m2}} \right) = -g_{m1} \left( \frac{1}{g_{m2} + g_{m3}} \right)$

Applying Miller's Theorem:


$$\omega_{p1} (\omega_{pa}) = \frac{1}{R_A (C_{as1} + C_{d1} \left( \frac{g_{m1} + g_{m2} + g_{m3}}{g_{m2} + g_{m3}} \right))}$$

$$\omega_{pB} = \frac{g_{m3} + g_{m2}}{\left( C_A + C_{d1} \left( \frac{g_{m1} + g_{m2} + g_{m3}}{g_{m1}} \right) \right)}$$

$$\omega_{pout} = \frac{1}{R_D (C_{DB2} + C_{d2})}$$

Where  $C_A = C_{as3} + C_{sb3} + C_{as2} + C_{sb2} + C_{DB1}$

52)

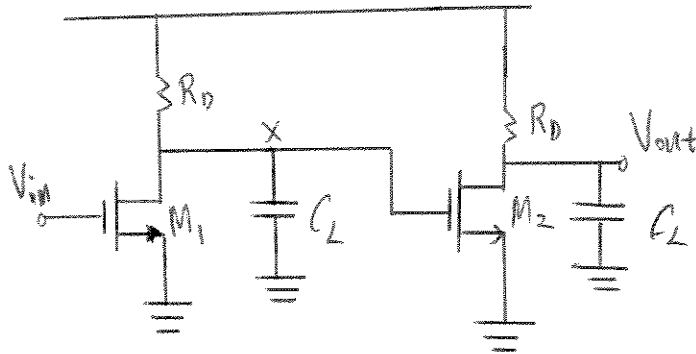

Bias Current = 1mA (each stage)

$$C_L = 50 \text{ fF}$$

$$\mu_n C_{ox} = 100 \mu\text{A/V}^2, A_V = 20, -3\text{dB}: 1 \text{ GHz}$$

$$\text{DC gain: } (g_m R_D)^2 = 20$$

$$\text{-3dB bandwidth: } 0.10243 / (R_D C_L) = 1 \text{ GHz}$$

$$\text{Since } C_L = 50 \text{ fF}, R_D = 2048.6 \Omega$$

$$(g_m R_D)^2 = 20 \Rightarrow g_m = 0.002183 = \frac{2I_D}{V_{eff}} \Rightarrow V_{eff} = 0.916 \text{ V}$$


$$V_{eff} = V_{GS} - V_{th} = 0.916 \text{ V}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{eff}) \Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{eff})} = 23.83$$

$$\text{So } R_D = 2.05 \text{ K}, C_L = 50 \text{ fF}$$

$$V_{GS} - V_{th} = 0.916 \text{ V}, W/L = 23.83$$

53)

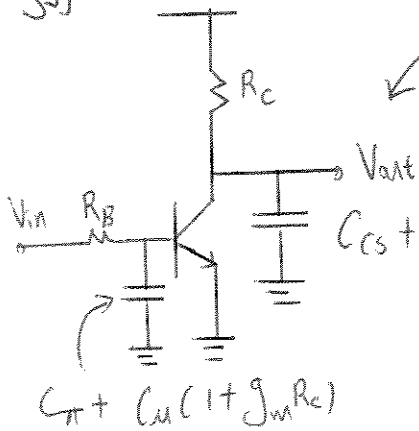

After apply Miller's theorem

$$\omega_{pin} = (2\pi)(500\text{MHz})$$

$$\omega_{pout} = (2\pi)(2\text{G})$$

$$I_c = 1\text{mA}, C_{\pi} = 2\text{pF},$$

$$C_u = 5\text{fF}, C_{cs} = 1\text{pF}$$

$$V_A = \infty$$

Low frequency Voltage gain: 
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{\frac{1}{g_m} + \frac{R_B}{\beta + 1}}$$

$$\omega_{pin} = \frac{1}{(R_B // r_{\pi})(C_{\pi} + C_u(1 + g_m R_c))} = (2\pi)(500\text{MHz})$$

$$\omega_{pout} = \frac{1}{R_c [C_{cs} + (1 + \beta(g_m R_c))C_u]} = (2\pi)(2\text{G})$$

$$\Rightarrow g_m = 2\pi(2\text{G}) [g_m R_c C_{cs} + g_m R_c C_u + C_u]$$

$$\Rightarrow R_c = \left( \frac{g_m}{(2\pi)(2\text{G})} - C_u \right) / (g_m (C_{cs} + C_u))$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}, R_c = 5296.53 \Omega$$



53)

In order to maximize low frequency gain  $V_{out}/V_{in}$ ,  $R_B$  should be as small as possible (restricted by the input pole location). So  $R_B \approx R_{\pi} \approx R_B$ .

$$\omega_{pin} \approx \frac{1}{R_B (C_{\pi} + C_{\mu} (1 + g_m R_c))} = (2\pi \times 500 \times 10^6)$$

$$g_m R_c = 204.446$$


$$R_B = \frac{1}{\omega_{pin} (C_{\pi} + C_{\mu} (1 + g_m R_c))} \approx 303.95 \Omega$$

So

$$R_B = 303.95 \Omega$$

$$R_c = 5296.53 \Omega$$

54)

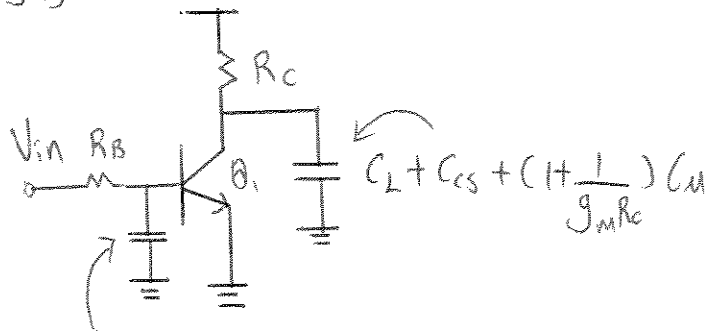

$$C_{\pi} + (1 + g_m R_c) C_{\mu}$$

Low freq Voltage gain: 
$$\frac{V_{out}}{V_{in}} = \frac{-R_c}{\frac{1}{g_m} + \frac{R_B}{\beta + 1}}$$

$$\omega_{pout} = \frac{1}{R_c [C_L + C_{CS} + (1 + \frac{1}{g_m R_c}) C_{\mu}]} = (2\pi)(2 \text{ GHz})$$

$$g_m = \frac{I_c}{V_T} = 0.0386 \frac{1}{\Omega}$$

$$g_m = (2\pi)(2 \text{ GHz}) [g_m R_c [C_L + C_{CS}] + g_m R_c (C_{\mu} + C_{\pi})]$$

$$R_c = \left[ \frac{g_m}{(2\pi)(2 \text{ GHz})} - C_{\mu} \right] / (g_m [C_L + C_{CS} + C_{\mu}])$$

$$R_c = 2269.94 \Omega \approx 2.27 \text{ K}\Omega$$


Again, to maximize low freq gain,  $R_B$  should be as small as possible, so  $R_B / (\beta + 1) \approx R_B$

$$\omega_{pin} \approx \frac{1}{R_B (C_{\pi} + C_{\mu} (1 + g_m R_c))} = (2\pi)(500 \times 10^6), g_m R_c = 87.62$$

$$R_B = 687.35 \Omega$$

So,  $R_c = 2.27 \text{ K}\Omega, R_B = 687.35 \Omega$

55)

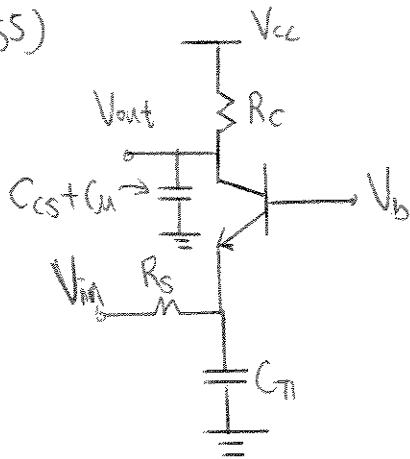

$$V_A = \infty, I_C = 1 \text{ mA}, R_S = 50 \Omega,$$

$$C_{\pi} = 20 \text{ fF}, C_{cs} = 20 \text{ fF}, C_u = 5 \text{ fF}$$

$$-3 \text{ dB bandwidth} = 10 \text{ GHz}$$

Since the output node sees a larger capacitance and resistance than the input, ( $R_C$  usually large for large gain), dominant pole and thus  $-3 \text{ dB}$  bandwidth occurs at the output.


$$\omega_{\text{pout}} = \frac{1}{R_C [C_u + C_{cs}]} = (2\pi)(10 \text{ GHz})$$

$$R_C = 636.62 \Omega, \quad \frac{1}{g_m} = \frac{25.9 \text{ mV}}{1 \text{ mA}}$$

$$\text{Maximum achievable gain} = \frac{R_C}{R_S + \frac{1}{g_m}} = 8.4$$

Here we have a tradeoff between gain and bandwidth.

36)

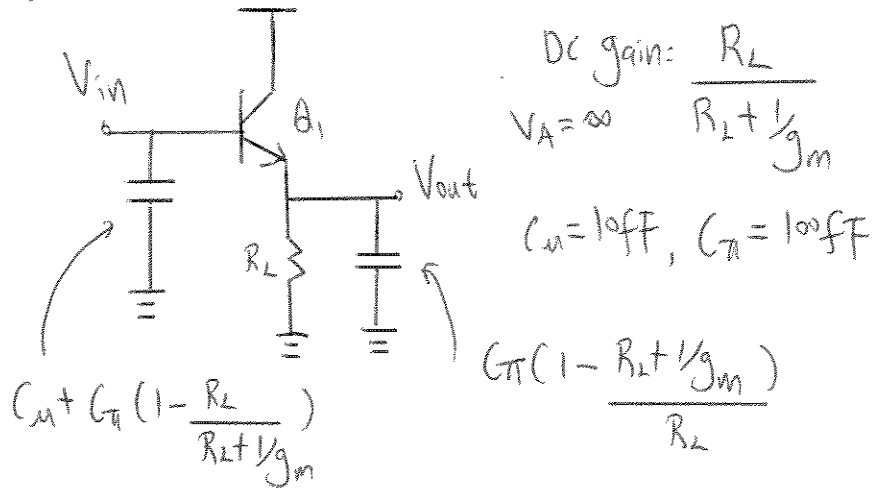

$$C_{in} < 50\text{fF} \Rightarrow C_u + C_{\pi} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 50\text{fF}$$


$$10\text{fF} + 100\text{fF} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 50\text{fF}$$

$$100\text{fF} \left(1 - \frac{R_L}{R_L + 1/g_m}\right) < 40\text{fF}$$

$$\left(\frac{1/g_m}{R_L + 1/g_m}\right) < 0.4$$

$$R_L > \frac{3}{2g_m} = 38.85\Omega$$

57)

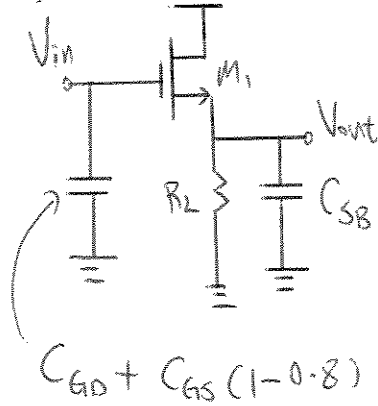

$$R_L = 100\Omega, \quad I_D = 1\text{mA}$$

$$A_V = \frac{V_{out}}{V_{in}} = 0.8 \quad \mu_n C_{ox} = 100 \mu\text{A/V}^2$$

$$L = 0.18 \mu\text{m}, \quad \lambda = 0, \quad C_{GD} \approx 0,$$

$$C_{SB} \approx 0, \quad C_{GS} = \left(\frac{2}{3}\right) WL C_{ox}$$

$$C_{ox} = 12 \text{ fF}/\mu\text{m}^2$$

$$C_{in} = C_{GD} + C_{GS}(0.2), \quad C_{in} = C_{GS}(0.2) = C_{in, \min}$$

$$A_V = \frac{R_L}{R_L + 1/g_m} = 0.8, \quad \frac{1}{g_m} = 25 = \frac{V_{eff}}{2I_D}$$

$$V_{eff} = 50 \text{ mV}, \quad I_D = \frac{1}{2} \frac{W}{L} \mu_n C_{ox} (V_{eff})^2 \Rightarrow W = 1440$$

$$C_{in, \min} = 0.2 C_{GS} = 0.2 \left(\frac{2}{3}\right) WL C_{ox} = 414.72 \text{ fF}$$

$$\text{or } C_{in, \min} = 0.415 \text{ pF}$$

$$I_D = \frac{1}{2} \left( \frac{W}{L} \right)_1 \mu_n C_{ox} V_{ov}^2 = 0.5 \text{ mA}$$

$$(W/L)_1 = (W/L)_2 = \boxed{250}$$

$$W_1 = W_2 = 45 \text{ } \mu\text{m}$$

$$g_{m1} = g_{m2} = \frac{W}{L} \mu_n C_{ox} V_{ov} = 5 \text{ mS}$$

$$C_{GD1} = C_{GD2} = C_0 W = 9 \text{ fF}$$

$$C_{GS1} = C_{GS2} = \frac{2}{3} W L C_{ox} = 64.8 \text{ fF}$$

$$\omega_{p,in} = \frac{1}{R_G \left\{ C_{GS1} + C_{GD1} \left( 1 + \frac{g_{m1}}{g_{m2}} \right) \right\}} = 2\pi \times 5 \text{ GHz}$$

$$R_G = \boxed{384 \text{ } \Omega}$$

$$\omega_{p,out} = \frac{1}{R_D C_{GD2}} = 2\pi \times 10 \text{ GHz}$$

$$R_D = \boxed{1.768 \text{ k}\Omega}$$

$$A_v = -g_{m1} R_D = \boxed{-8.84}$$

59)

$$W_2 = 4W_1, \quad V_{eff2} = \frac{V_{eff1}}{2} \quad (\text{To maintain the current constant})$$

$$V_{eff1} = 200 \text{ mV}, \quad V_{eff2} = 100 \text{ mV} \quad (\text{Assume } V_{eff1} \text{ is not changed})$$

$$\text{DC gain: } -\frac{g_{m1}}{g_{m2}} = -\frac{g_{m1}}{2g_{m1}} = -\frac{1}{2}$$

$$\omega_{pin} = \frac{1}{R_G \left[ \frac{2}{3} W L (C_x + (0.2) W \left( \frac{1}{2} \right) \right]} = (5 \times 10^9) (2\pi)$$

$$W = 45 \mu\text{m}$$

$$\Rightarrow R_G = 459.32 \Omega$$

$$R_0 = \frac{1}{(10 \times 10^9) (2\pi) (0.2) (4) (45)} = 442.097 \Omega$$

$$\text{DC gain: } |g_{m1} R_0| = \frac{2I_D R_0}{V_{eff1}} = 2.2105$$

12.1 (a)

$$\begin{aligned} Y &= A_1 (X - K A_2 Y) \\ Y (1 + K A_1 A_2) &= A_1 X \\ \frac{Y}{X} &= \boxed{\frac{A_1}{1 + K A_1 A_2}} \end{aligned}$$

(b)

$$\begin{aligned} Y &= X - KY - A_1 (X - KY) \\ Y (1 + K - A_1 K) &= X (1 - A_1) \\ \frac{Y}{X} &= \boxed{\frac{1 - A_1}{1 + K (1 - A_1)}} \end{aligned}$$

(c)

$$\begin{aligned} Y &= A_2 X - A_1 (X - KY) \\ Y (1 - A_1 K) &= X (A_2 - A_1) \\ \frac{Y}{X} &= \boxed{\frac{A_2 - A_1}{1 - A_1 K}} \end{aligned}$$

(d)

$$\begin{aligned} Y &= X - (KY - Y) - A_1 [X - (KY - Y)] \\ Y &= X - KY + Y - A_1 X + K A_1 Y - A_1 Y \\ Y [A_1 (1 - K) + K] &= X (1 - A_1) \\ \frac{Y}{X} &= \boxed{\frac{1 - A_1}{A_1 (1 - K) + K}} \end{aligned}$$



$$2. \quad (a) \quad W = A_2 Y = A_2 [(X - KW)A_1]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1 A_2}{1 + A_1 A_2 K}$$

$$(b) \quad W = A_1 X E = A_1 [X - K(\frac{W}{A_1} - W)]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1}{1 + K(1 - A_1)}$$

$$(c) \quad W = A_1 E = A_1 [X - (A_2 X - W)K]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1 (1 - A_2 K)}{(1 - A_1 K)}$$

$$(d) \quad W = A_1 E = A_1 [X - \left\{ \left( \frac{W}{A_1} - W \right) K - \left( \frac{W}{A_1} - W \right) \right\}]$$

$$\Rightarrow \frac{W}{X} = \frac{A_1}{1 + (K-1)(1-A_1)}$$

$$3. (a) E = X - KA_2A_1E$$
$$\Rightarrow \frac{E}{X} = \frac{1}{1 + KA_2A_1}$$

$$(b) E = X - K[E - A_1E]$$

$$\Rightarrow \frac{E}{X} = \frac{1}{1 + K(1 - A_1)}$$

$$(c) E = X - K[A_2X - A_1E]$$


$$\Rightarrow \frac{E}{X} = \frac{1 - A_2K}{1 - A_1K}$$

$$(d) E = X - \{K[E - A_1E] - [E - A_1E]\}$$

$$\Rightarrow \frac{E}{X} = \frac{1}{1 + (K-1)(1-A_1)}$$

4.

(a)

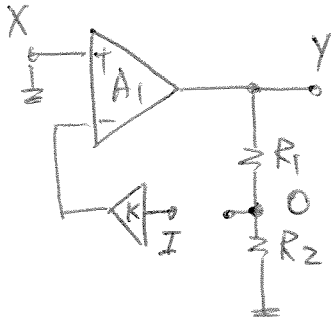


(X is grounded  
in loop-gain calculation)

$$0 = Y \frac{R_2}{R_1 + R_2} = (-IK)A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +KA_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

(b)

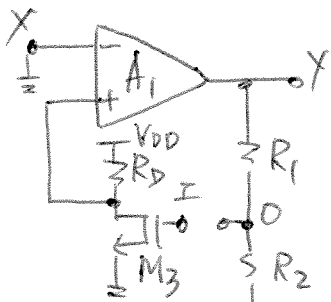


(X is grounded)

$$0 = Y \left( \frac{R_2}{R_1 + R_2} \right) = -I g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +g_{m3} R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)$$

(c)

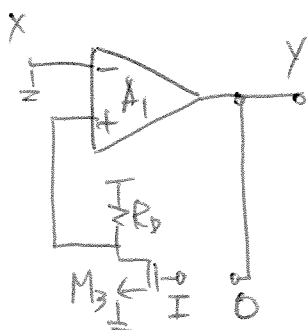


(X is grounded)

$$0 = Y = -I g_{m3} R_D A_1$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain} = +g_{m3} R_D A_1$$

(d)

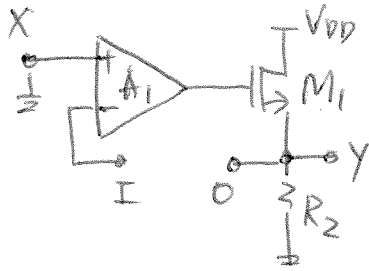

(X is grounded)

$$0 = Y = -I \times \frac{g_{m1} R_2}{1 + g_{m1} R_2} \times A_1$$

$$\Rightarrow -\frac{0}{I} = \text{Loop Gain}$$
$$= + A_1 \frac{g_{m1} R_2}{1 + g_{m1} R_2}$$

12.5 The loop gains calculated in Problem 4 are used.

(a)

$$\begin{aligned}A_{OL} &= A_1 \\A_{loop} &= KA_1 \left( \frac{R_2}{R_1 + R_2} \right) \\ \frac{Y}{X} &= \boxed{\frac{A_1}{1 + KA_1 \left( \frac{R_2}{R_1 + R_2} \right)}}\end{aligned}$$

(b)

$$\begin{aligned}A_{OL} &= -A_1 \\A_{loop} &= g_{m3}R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right) \\ \frac{Y}{X} &= \boxed{-\frac{A_1}{1 + g_{m3}R_D A_1 \left( \frac{R_2}{R_1 + R_2} \right)}}\end{aligned}$$

(c)

$$\begin{aligned}A_{OL} &= -A_1 \\A_{loop} &= g_{m3}R_D A_1 \\ \frac{Y}{X} &= \boxed{-\frac{A_1}{1 + g_{m3}R_D A_1}}\end{aligned}$$

(d)

$$\begin{aligned}A_{OL} &= A_1 \left( \frac{g_{m1}R_2}{1 + g_{m1}R_2} \right) \\A_{loop} &= A_1 \left( \frac{g_{m1}R_2}{1 + g_{m1}R_2} \right) \\ \frac{Y}{X} &= \boxed{\frac{A_1 \left( \frac{g_{m1}R_2}{1 + g_{m1}R_2} \right)}{1 + A_1 \left( \frac{g_{m1}R_2}{1 + g_{m1}R_2} \right)}}\end{aligned}$$

b.  $A_1 = 500$   
 $R_1/R_2 = 7$


$$\frac{Y}{X} \approx 1 + \frac{R_1}{R_2} = 8$$

$$\Rightarrow \frac{R_2}{R_1 + R_2} = \frac{1}{8} = K$$

$$E = \frac{X}{1 + KA_1} = \frac{2 \text{ mV}}{1 + 500/8} \approx 0.031 \text{ mV}$$

$\therefore$  Amplitude of feedback waveform  
 $= X - E \approx 1.969 \text{ mV}$

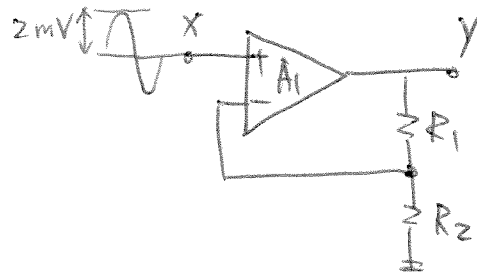Amplitude of output waveform  
 $= X \frac{A_1}{1 + KA_1} \approx 15.75 \text{ mV}$



$$1. \quad A_{CL} = \frac{A_1}{1+A_1K}$$

$$\frac{dA_{CL}}{dA_1} = \frac{1}{(1+A_1K)^2} \Rightarrow dA_{CL} = \frac{dA_1}{(1+A_1K)^2}$$

$$\begin{aligned} \Rightarrow \frac{dA_{CL}}{A_{CL}} &= \frac{dA_{CL}}{\left(\frac{A_1}{1+A_1K}\right)} = dA_1 \left(\frac{1+A_1K}{A_1}\right) \left(\frac{1}{(1+A_1K)^2}\right) \\ &= \frac{(dA_1/A_1)}{(1+A_1K)} \end{aligned}$$

This equation implies that for a fractional change in  $A_{CL}$ , it is reduced by  $(1+A_1K)$  compared to a fractional change in  $A_1$ .

$$\Rightarrow 0.01 > \frac{0.2}{1+A_1K} \Rightarrow A_1K > 19$$

$$\begin{aligned}
A_{OL} &= -g_m r_o \\
&= -\sqrt{2\frac{W}{L}\mu_n C_{ox} I_D} \frac{1}{\lambda I_D} \\
&= -\frac{1}{\lambda\sqrt{I_D}} \sqrt{2\frac{W}{L}\mu_n C_{ox}} \\
\frac{V_{out}}{V_{in}} &= \frac{A_{OL}}{1 + K A_{OL}}
\end{aligned}$$

We want to look at the maximum and minimum deviations that  $\frac{V_{out}}{V_{in}}$  will have from the base value given the variations in  $\lambda$  and  $\mu_n C_{ox}$ . First, let's consider what happens when  $\lambda$  decreases by 20 % and  $\mu_n C_{ox}$  increases by 10 %. This causes  $A_{OL}$  to increase in magnitude by a factor of  $\frac{\sqrt{1.1}}{0.8} = 1.311$ . We want  $\frac{V_{out}}{V_{in}}$  to change by less than 5 % given this deviation in  $A_{OL}$ .

$$\begin{aligned}
\frac{1.311A_{OL}}{1 + 1.311KA_{OL}} &< 1.05 \frac{A_{OL}}{1 + KA_{OL}} \\
KA_{OL} &> 3.982
\end{aligned}$$

Next, let's consider what happens when  $\lambda$  increases by 20 % and  $\mu_n C_{ox}$  decreases by 10 %. This causes  $A_{OL}$  to decrease in magnitude by a factor of  $\frac{\sqrt{0.9}}{1.2} = 0.7906$ . We want  $\frac{V_{out}}{V_{in}}$  to change by less than 5 % given this deviation in  $A_{OL}$ .

$$\begin{aligned}
\frac{0.7906A_{OL}}{1 + 0.7906KA_{OL}} &< 0.95 \frac{A_{OL}}{1 + KA_{OL}} \\
KA_{OL} &> 4.033
\end{aligned}$$

Thus, to satisfy the constraints on both the maximum and minimum deviations, we require  $KA_{OL} > \boxed{4.033}$ .



9. From the question,

$$(1-10\%)A_0 = |A(j\omega')| \quad \text{where } \omega' = \text{-1-dB bandwidth frequency}$$

$$0.9A_0 = \frac{A_0}{|1+j\frac{\omega'}{\omega_0}|} = \frac{A_0}{\sqrt{1+(\frac{\omega'}{\omega_0})^2}}$$

$$\Rightarrow \omega' \cong 0.48\omega_0$$

$\Rightarrow$  This is the open-loop -1dB bandwidth.

Similarly,

$$0.9 \frac{A_0}{1+L.G.} = \left| \frac{Y}{X}(j\omega'') \right| \quad \text{where } \omega'' = \text{-1dB bandwidth frequency}$$

$$0.9 \frac{A_0}{1+L.G.} = \frac{\frac{A_0}{1+L.G.}}{\left| 1 + j \frac{\omega''}{\omega_0(1+L.G.)} \right|}$$
$$= \frac{\frac{A_0}{1+L.G.}}{\sqrt{1 + \left[ \frac{\omega''}{\omega_0(1+L.G.)} \right]^2}}$$

L.G. = Loop Gain

$$\Rightarrow \omega'' \cong 0.48\omega_0(1+L.G.)$$

$\therefore$  -1dB bandwidth is boosted (expected) by  $(1+L.G.)$  in closed-loop measurement.

12.10

$$\begin{aligned}A_{OL} &= -g_m \left( r_o \parallel \frac{1}{sC_L} \right) \\ &= -\frac{g_m r_o}{1 + sr_o C_L} \\ \frac{V_{out}}{V_{in}} &= \frac{A_{OL}}{1 + KA_{OL}} \\ &= \frac{-\frac{g_m r_o}{1 + sr_o C_L}}{1 - K \frac{g_m r_o}{1 + sr_o C_L}} \\ &= -\frac{g_m r_o}{1 + sr_o C_L - Kg_m r_o}\end{aligned}$$

Setting the denominator equal to zero and solving for  $s$  gives us the bandwidth  $B$ .

$$\begin{aligned}B &= \frac{Kg_m r_o - 1}{r_o C_L} \\ K &= \boxed{\frac{1 + Br_o C_L}{g_m r_o}}\end{aligned}$$

- 12.11 (a)
- Feedforward system:  $M_1$  and  $R_D$  (which act as a common-gate amplifier)
  - Sense mechanism:  $C_1$  and  $C_2$  (which act as a capacitive divider)
  - Feedback network:  $C_1$  and  $C_2$
  - Comparison mechanism:  $M_1$  (which amplifies the difference between the fed back signal and the input)

(b)

$$A_{OL} = g_m R_D$$

$$A_{loop} = g_m R_D \left( \frac{C_1}{C_1 + C_2} \right)$$

$$\frac{v_{out}}{v_{in}} = \frac{g_m R_D}{1 + g_m R_D \left( \frac{C_1}{C_1 + C_2} \right)}$$

(c)

$$R_{in,open} = \frac{1}{g_m}$$


$$R_{in,closed} = \frac{1 + g_m R_D \left( \frac{C_1}{C_1 + C_2} \right)}{g_m}$$

$$R_{out,open} = R_D$$

$$R_{out,closed} = \frac{R_D}{1 + g_m R_D \left( \frac{C_1}{C_1 + C_2} \right)}$$

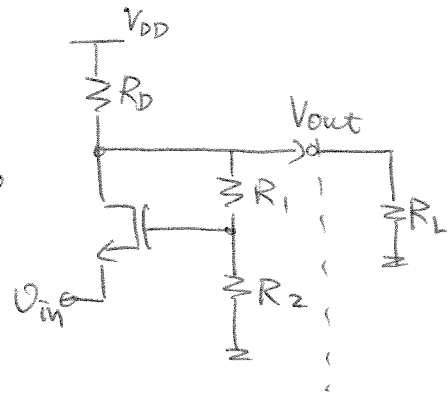12.

Given:  $\frac{\text{Gain}_{\text{unloaded}} - \text{Gain}_{\text{loaded}}}{\text{Gain}_{\text{unloaded}}} = 10\%$   
 $= 0.1$



$$\text{Gain}_{\text{unloaded}} \cong \frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D} \quad (\text{assume } R_1 + R_2 \gg R_D)$$

$$\text{Gain}_{\text{loaded}} = \frac{g_m (R_D \parallel R_L)}{1 + \frac{R_2}{R_1 + R_2} g_m (R_D \parallel R_L)}$$

$$\therefore 0.1 = \frac{\frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D} - \frac{g_m (R_D \parallel R_L)}{1 + \frac{R_2}{R_1 + R_2} g_m (R_D \parallel R_L)}}{\frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}}$$

After solving for  $R_L$ :

$$R_L = \frac{g_m R_D}{1 + \left(\frac{R_2}{R_1 + R_2}\right) g_m R_D}$$

$$13. \text{ Gain at } x_1 = \frac{500}{1+500K}$$

$$\text{Gain at } x_2 = \frac{420}{1+420K}$$

$$\Rightarrow \frac{\frac{500}{1+500K} - \frac{420}{1+420K}}{\frac{500}{1+500K}} < 0.05$$

$$\Rightarrow K > \frac{11}{2100}$$

$$A_{x_1} = \frac{500}{1+500(K)} = \frac{2625}{19} \approx 138.16$$

$$A_{x_2} = \frac{420}{1+420(K)} = \frac{525}{4} \approx 131.25$$

$$14. \quad y = \alpha_1 x - \alpha_3 x^3$$

$$(a) \quad \frac{\partial y}{\partial x} = \alpha_1 - 3\alpha_3 x^2$$


$$\left. \frac{\partial y}{\partial x} \right|_{x=0} = \alpha_1$$

$$\left. \frac{\partial y}{\partial x} \right|_{x=\Delta x} = \alpha_1 \quad (\text{around } x=0)$$


$$(b) \quad \text{Closed-loop } \left|_{x=0} = \frac{\alpha_1}{1 + \alpha_1 k}$$

$$\text{Closed-loop } \left|_{x=\Delta x} = \frac{\alpha_1}{1 + \alpha_1 k} \quad (\text{around } x=0)$$


12.15 (a)

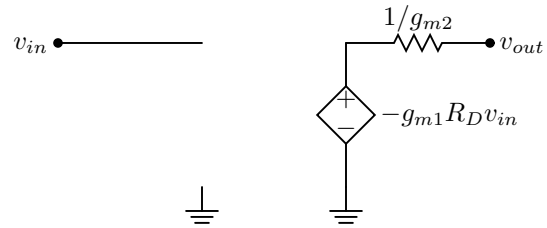


(b)

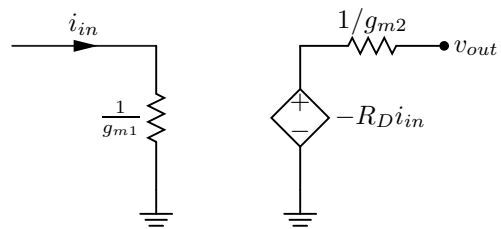

(c)


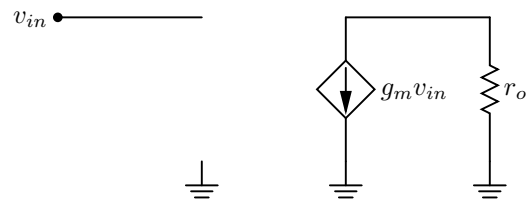


(d)

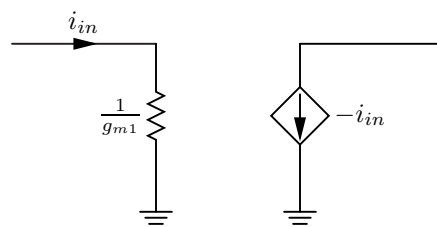


16.

$\lambda > 0$

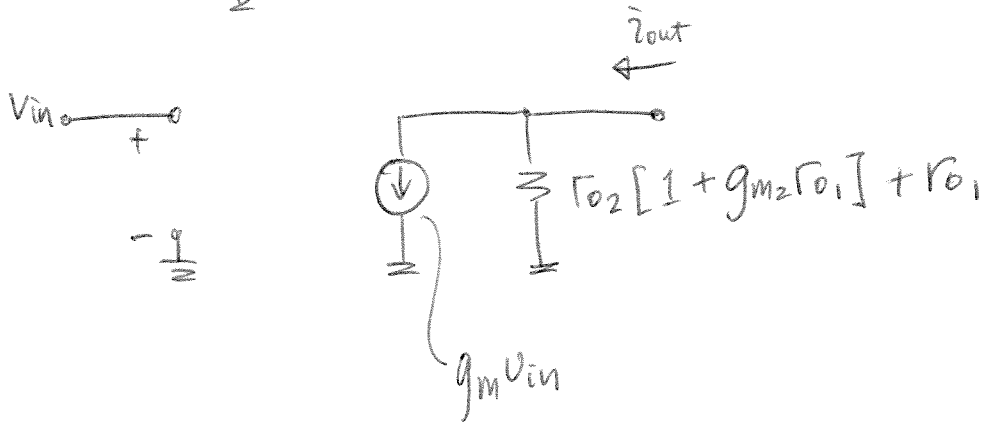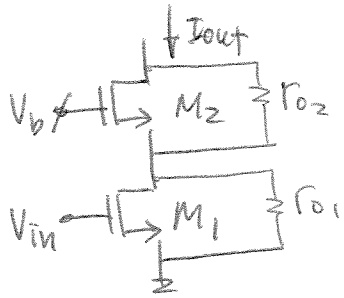



17.

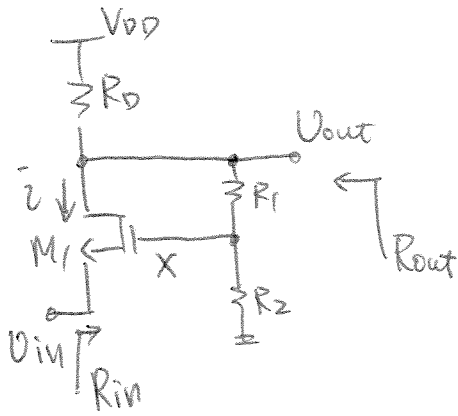


$$-V_{out} = \bar{i} [R_D \parallel (R_1 + R_2)]$$

$$\bar{i} = g_{m1}(V_x - V_{in}) = g_{m1} \left( V_{out} \times \frac{R_2}{R_1 + R_2} - V_{in} \right)$$

Combining the equations above yields:

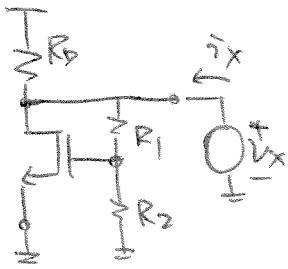
$$\frac{V_{out}}{V_{in}} = \frac{g_{m1} [R_D \parallel (R_1 + R_2)]}{1 + \frac{R_2}{R_1 + R_2} g_{m1} [R_D \parallel (R_1 + R_2)]} \triangleq A_v$$



By KCL,

$$\bar{i}_x = \frac{V_x}{R_1 + R_2} + \frac{V_x}{R_D} + g_{m1} \left( V_x \frac{R_2}{R_1 + R_2} \right)$$
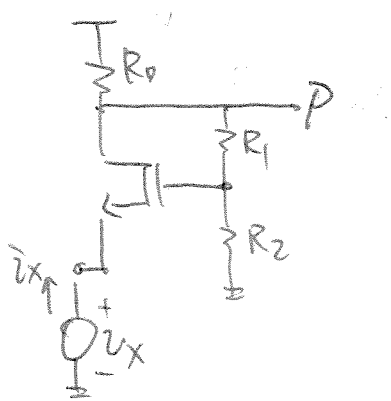
$$\Rightarrow \frac{V_x}{\bar{i}_x} = R_{out} = [(R_1 + R_2) \parallel R_D] \left[ 1 + g_{m1} \frac{R_2}{R_1 + R_2} (R_D \parallel (R_1 + R_2)) \right]$$



By KCL,

$$\bar{i}_x = g_{m1} \left( v_x - v_p \frac{R_2}{R_1 + R_2} \right)$$



$$\Rightarrow v_p = \left( v_x - \frac{\bar{i}_x}{g_{m1}} \right) \left( \frac{R_1 + R_2}{R_2} \right) \quad \text{--- (1)}$$

$$\bar{i}_x = \frac{v_p}{R_0 \parallel (R_1 + R_2)} \quad \text{--- (2)}$$

Substitute (1) into (2) & solve for  $\frac{v_x}{\bar{i}_x}$ :


$$\frac{v_x}{\bar{i}_x} = R_{in} = \frac{1}{g_{m1}} \left[ 1 + g_{m1} \left\{ R_0 \parallel (R_1 + R_2) \right\} \frac{R_2}{R_1 + R_2} \right]$$

Model:

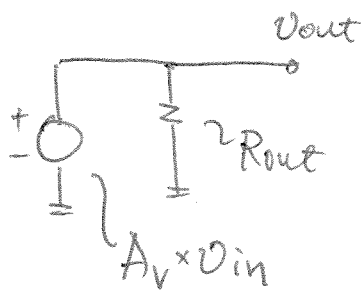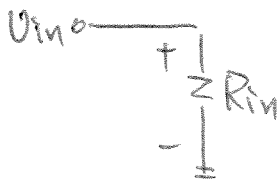

- 12.18
- (a)
    - Sense mechanism: Voltage at the source of  $M_3$
    - Return mechanism: Voltage at the gate of  $M_2$
  - (b)
    - Sense mechanism: Voltage at the source of  $M_3$
    - Return mechanism: Voltage at the gate of  $M_2$
  - (c)
    - Sense mechanism: Current flowing through  $R_1$
    - Return mechanism: Voltage at the gate of  $M_2$
  - (d)
    - Sense mechanism: Current flowing through  $R_1$
    - Return mechanism: Voltage at the gate of  $M_2$
  - (e)
    - Sense mechanism: Voltage divider formed by  $R_1$  and  $R_2$
    - Return mechanism: Voltage at the gate of  $M_2$
  - (f)
    - Sense mechanism: Voltage at the source of  $M_3$
    - Return mechanism: Voltage at the gate of  $M_2$

19. (a)

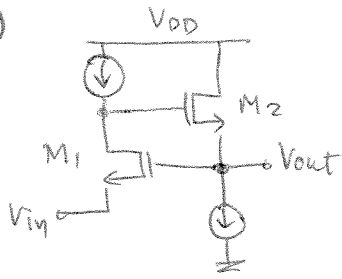


Sense Mechanism:

Voltage sensing at  $V_{out}$ .

Return Mechanism:

Voltage to Gate of  $M_1$ .

(b)

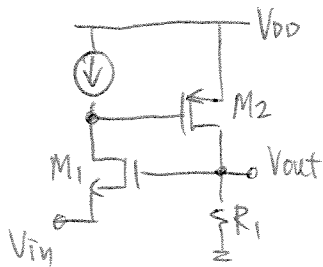


Sense Mechanism:

Voltage output from  $M_2$ .

Return Mechanism:

Voltage to Gate of  $M_1$ .

(c)

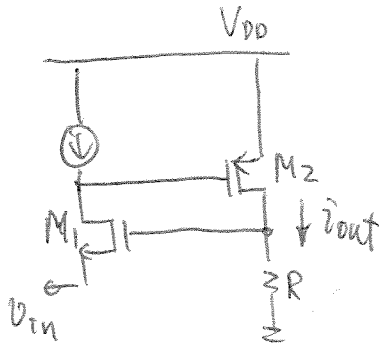


Sense Mechanism:

$R_1$

Return Mechanism:

Voltage to Gate of  $M_1$ .

(d)

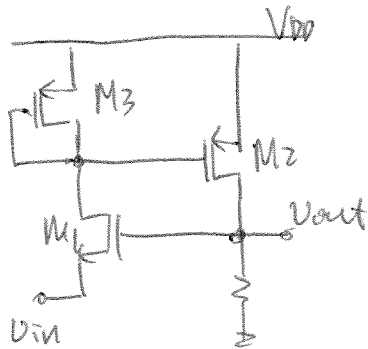

Sense Mechanism:

Voltage output of  $M_2$


Return Mechanism:

Voltage to Gate of  $M_1$


- 12.20 (a) • Sense mechanism: Voltage at the gate of  $M_2$   
• Return mechanism: Current through  $M_2$
- (b) • Sense mechanism: Voltage at the gate of  $M_2$   
• Return mechanism: Current through  $M_2$
- (c) • Sense mechanism: Voltage at the source of  $M_2$   
• Return mechanism: Current through  $M_2$
- (d) • Sense mechanism: Voltage at the gate of  $M_2$   
• Return mechanism: Current through  $M_2$

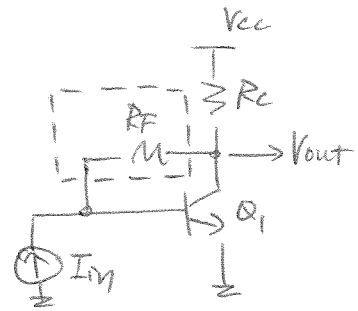21. (a) Sense Mechanism:  
 Resistor ( $R_F$ ) - Voltage

Return Mechanism:  
 Current through  $R_F$ .




(b)

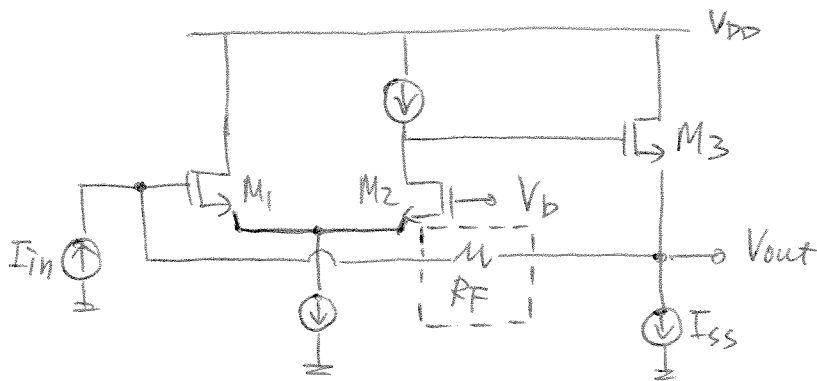

Sense Mechanism:  
 Resistor ( $R_F$ ) - Voltage

Return Mechanism:  
 Current through  $R_F$

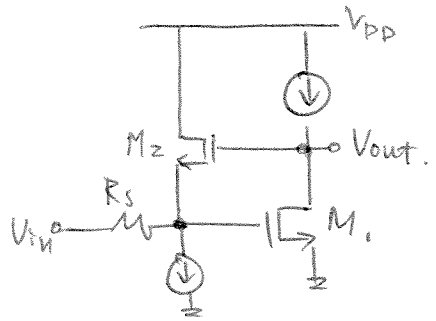22. (a) First, recognize that both input & output are voltages.



\*  $V_{in}$  primarily drives the Gate of  $M_1$ .

Sequence: Suppose  $V_{in}$  increases by  $\Delta V_{in}$

$\Rightarrow V_{out}$  drops by  $+g_{m1} \Delta V_{in} \times r_{o1}$  (Common-Source)

$\Rightarrow$  Source of  $M_2$  decreases by same amount (Source follower)

$\therefore V_{in} \uparrow \Rightarrow V_{M_2, D} \downarrow \Rightarrow V_{M_1, G} \downarrow$   
 $\Rightarrow$  effective  $V_{in}$  driving  $M_{1, G} \downarrow$

$\Rightarrow$  negative feedback

(b)  $V_{in} \uparrow \Rightarrow V_{out} \downarrow \Rightarrow V_{M_2, G} \uparrow$

$\Rightarrow$  effective  $V_{in}$  driving  $M_{1, G} \uparrow$

$\Rightarrow$  positive feedback.

$$(c) \quad v_{in} \uparrow \Rightarrow v_{out} \downarrow \Rightarrow v_{M_1, G} \downarrow$$

$\Rightarrow$  effective  $v_{in}$  driving  $M_1, G \downarrow$

$\Rightarrow$  negative feedback.

$$(d) \quad v_{in} \uparrow \Rightarrow v_{out} \uparrow \text{ (common-base, } M_1)$$

$\Rightarrow v_{M_1, S} \downarrow$

$\Rightarrow$  effective  $v_{in}$  driving  $M_1, S \downarrow$

$\Rightarrow$  negative feedback.



12.23 If  $I_{in}$  increases, then the voltage at the gate of  $M_1$  will increase, meaning  $I_{D1}$  will increase. This will cause the drain voltage of  $M_1$  to decrease, meaning  $I_{D2}$  will decrease and  $V_{out}$  will increase. This will cause the voltage at the gate of  $M_1$  to decrease, which counters the original increase, meaning there is negative feedback.

- Fig. 12.83 (a)  $V_{in} \uparrow, V_{S1} \uparrow, V_{G3} \uparrow, V_{out} \downarrow, V_{G3} \downarrow \Rightarrow$  negative feedback.
- (b)  $V_{in} \uparrow, V_{S1} \uparrow, V_{G3} \uparrow, V_{out} \downarrow, V_{G3} \uparrow \Rightarrow$  positive feedback.
- (c) Same as (b), positive feedback.
- (d) Same as (a), negative feedback.
- (e)  $V_{in} \uparrow, V_{S1} \uparrow, V_{out} \uparrow, V_{G2} \uparrow, V_{out} \downarrow \Rightarrow$  negative feedback.
- (f)  $V_{in} \uparrow, V_{S1} \uparrow, V_{G3} \uparrow, V_{out} \downarrow, V_{G3} \uparrow \Rightarrow$  positive feedback.

- Fig. 12.84 (a)  $V_{in} \uparrow, V_{G2} \uparrow, V_{out} \uparrow, V_{G2} \downarrow \Rightarrow$  negative feedback.
- (b)  $V_{in} \uparrow, V_{G2} \uparrow, V_{out} \downarrow, V_{G2} \uparrow \Rightarrow$  positive feedback.
- (c) Same as (b), positive feedback.
- (d)  $V_{in} \uparrow, V_{G2} \uparrow, V_{out} \downarrow, V_{G2} \uparrow \Rightarrow$  positive feedback.

- Fig. 12.85 (a)  $I_{in} \uparrow, V_{G1} \uparrow$  (consider  $I_{in}$  flows through an equivalent small-signal resistance of  $1/g_{m2}$  at the gate of  $M_1$ ),  $V_{out} \downarrow, V_{G1} \downarrow \Rightarrow$  negative feedback.
- (b)  $I_{in} \uparrow, V_{G1} \uparrow, V_{out} \downarrow, V_{G1} \uparrow \Rightarrow$  positive feedback.
- (c)  $I_{in} \uparrow, V_{G1} \uparrow, V_{out} \downarrow, V_{G1} \downarrow \Rightarrow$  negative feedback.
- (d)  $I_{in} \uparrow, V_{S1} \uparrow, V_{out} \uparrow, V_{S1} \downarrow \Rightarrow$  negative feedback.

- Fig. 12.86 (a)  $I_{in} \uparrow, V_{BE1} \uparrow, V_{out} \downarrow, V_{BE1} \downarrow \Rightarrow$  negative feedback.
- (b)  $I_{in} \uparrow, V_{G3} \uparrow, V_{out} \uparrow, V_{G3} \uparrow \Rightarrow$  positive feedback.

25.

(Without feedback)

$$\frac{V_{out}}{V_{in}} = A_{o.L.} = g_m R_D$$


Feedback factor,  $k$ :

$$k = \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow A_{c.L.} = \left. \frac{V_{out}}{V_{in}} \right|_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} \cdot k} = \frac{g_m R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$

$$R_{in, closed} = \frac{1}{g_{m1}} \left( 1 + \frac{R_2}{R_1 + R_2} g_m R_D \right)$$
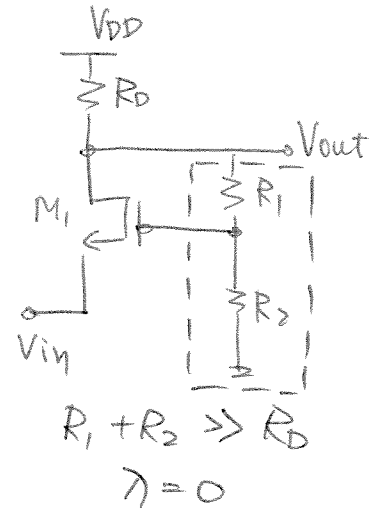
$$R_{out, closed} = \frac{R_D}{1 + \frac{R_2}{R_1 + R_2} g_m R_D}$$




26.

(Without feedback)

$$A_{o.L.} = g_m R_D$$

Feedback factor,  $k$  :

$$k = \frac{C_1}{C_1 + C_2}$$

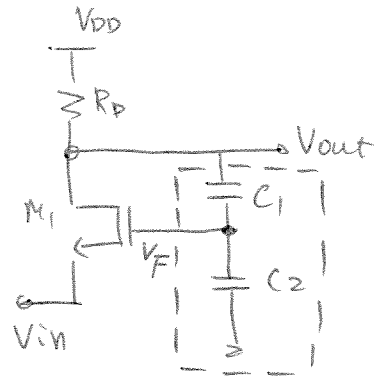

$\lambda = 0$   
 $C_1, C_2$  small.

$$\Rightarrow A_{c.L.} = \left. \frac{V_{out}}{V_{in}} \right|_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} k} = \frac{g_m R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D}$$

$$R_{in, closed} = \frac{1}{g_m} \left[ 1 + \frac{C_1}{C_1 + C_2} g_m R_D \right]$$

$$R_{out, closed} = \frac{R_D}{1 + \frac{C_1}{C_1 + C_2} g_m R_D}$$

$$A_{OL} = g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} \right)$$


$K = 1$  (since the output is fed back directly to the inverting input)

$$\frac{v_{out}}{v_{in}} = \frac{g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} \right)}{1 + g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} \right)}$$

$$R_{out,open} = \frac{1}{g_{m5}} \parallel r_{o5}$$

$$R_{out,closed} = \frac{\frac{1}{g_{m5}} \parallel r_{o5}}{1 + g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} \right)}$$

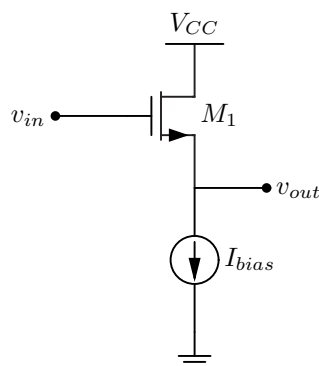Let's recall the gain and output impedance of a simple source follower, as shown in the following diagram.



$$A_v = \frac{g_{m1} r_{o1}}{1 + g_{m1} r_{o1}}$$

$$R_{out} = \frac{1}{g_{m1}} \parallel r_{o1}$$

We can see that the gain of the circuit in Fig. 12.90 is the gain of a simple source follower multiplied by a factor of

$$\frac{g_{m1} (r_{o2} \parallel r_{o4})}{1 + g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} \right)}$$

This factor is less than 1, which means that the gain is reduced. However, we do get an improvement in output resistance, which is reduced by a factor of

$$1 + g_{m1} (r_{o2} \parallel r_{o4}) \left( \frac{g_{m5} r_{o5}}{1 + g_{m5} r_{o5}} \right)$$

12.28 (a)  $V_{in} \uparrow, V_{G5} \uparrow, V_{out} \downarrow, V_{G5} \uparrow \Rightarrow$  positive feedback.

(b)

$$A_{loop} = \boxed{-g_{m1}g_{m5} (r_{o2} \parallel r_{o4}) r_{o5}}$$

Since the loop gain is negative, the feedback is positive.

12.29

$$\begin{aligned}A_{OL} &= g_{m1}g_{m5} (r_{o1} \parallel r_{o3}) r_{o5} \\K &= 1 \\ \frac{v_{out}}{v_{in}} &= \boxed{\frac{g_{m1}g_{m5} (r_{o1} \parallel r_{o3}) r_{o5}}{1 + g_{m1}g_{m5} (r_{o1} \parallel r_{o3}) r_{o5}}} \\ R_{in,open} &= R_{in,closed} = \boxed{\infty} \\ R_{out,open} &= r_{o5} \\ R_{out,closed} &= \boxed{\frac{r_{o5}}{1 + g_{m1}g_{m5} (r_{o1} \parallel r_{o3}) r_{o5}}}\end{aligned}$$

Like the circuit in Problem 12.27, the closed loop gain is approximately (but slightly less than) 1. Looking at the equations, the closed loop gain of this circuit will typically be larger than the closed loop gain of the circuit in Problem 12.27.

The output impedance of this circuit is not quite as small as the output impedance of the circuit in Problem 12.27. Despite the loop gain being larger, the open loop output impedance is significantly higher than that of Problem 12.27, so that overall, the output impedance is slightly higher in this circuit.

12.30 (a)  $I_{in} \uparrow, V_{G2} \uparrow, V_{out} \uparrow, V_{S1} \uparrow, V_{G2} \uparrow \Rightarrow$  positive feedback.

(b)

$$A_{loop} = - \frac{g_{m1} g_{m2} R_D \left( R_F + \frac{1}{g_{m1}} \right)}{\left[ 1 + g_{m2} \left( R_F + \frac{1}{g_{m1}} \right) \right] (1 + g_{m1} R_F)}$$

Since the loop gain is negative, the feedback is positive.




31.

(a)  $\bar{v}_{in} \uparrow \Delta \Rightarrow \Delta \bar{v}_{in}$  mostly  
flows in  $\frac{1}{g_{m1}} \Rightarrow V_{G,M2} \uparrow$   
(Common Gate)

$\Rightarrow V_{out} \downarrow$  (Common Source)

$\Rightarrow R_F$  momentarily demands  
more current from  $\bar{v}_{in}$

$\Rightarrow$  Negative feedback.

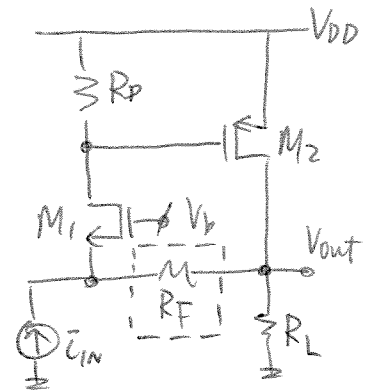

$$\lambda = 0$$

$$R_F \gg 1.$$

(b)  $R_{o.L.} = \left. \frac{V_{out}}{\bar{v}_{in}} \right|_{o.L.} = -R_D \times g_{m2} R_L$

(c)  $k$  (feedback factor) =  $\frac{-1}{R_F}$

$$\Rightarrow R_{c.L.} = \frac{R_{o.L.}}{1 + R_{o.L.} \times k} = \frac{-R_D \times g_{m2} R_L}{1 + \frac{R_D}{R_F} g_{m2} R_L}$$


32.

$$R_{e.l.} = \frac{-g_{m2} R_D R_L}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$

$$\text{loop gain} = \frac{g_{m2} R_D R_L}{R_F}$$

$$r_{in} \approx \frac{1}{g_{m1}}$$

$$\Rightarrow r_{in|c.l.} = \frac{1/g_{m1}}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$

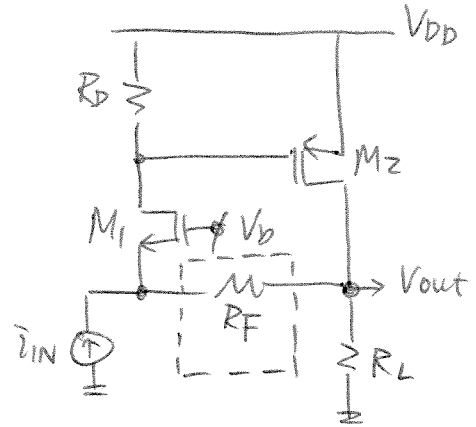

$$r_{out} \approx R_L \quad (R_F \text{ large})$$

$$r_{out|c.l.} = \frac{R_L}{1 + \frac{g_{m2} R_D R_L}{R_F}}$$


33.

$$R_{oL} = \frac{V_{out}}{\bar{v}_{IN}} \text{ (no feedback)}$$

$$= R_D$$

$K$  (feedback factor)
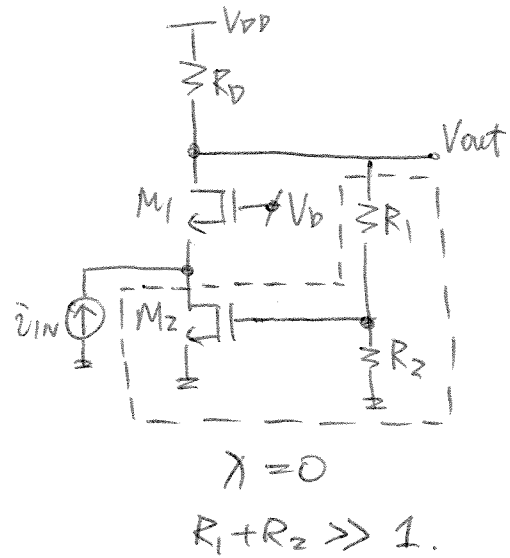
$$= g_{m2} \times \frac{R_2}{R_1 + R_2}$$



$$\Rightarrow R_{c.L.} = \frac{V_{out}}{\bar{v}_{IN}} = \frac{R_D}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

$$r_{in|c.L.} = \frac{1/g_{m1}}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

$$r_{out|c.L.} = \frac{R_D}{1 + R_D \times g_{m2} \frac{R_2}{R_1 + R_2}}$$

34.

$$R_{o.l.} = \frac{V_{out}}{\bar{v}_{in}} \text{ (no feedback)}$$

$$= R_D$$


$K$  (feedback factor)

$$= g_{m2} \times \frac{C_1}{C_1 + C_2}$$

$$\Rightarrow R_{c.l.} = \frac{V_{out}}{\bar{v}_{in}} = \frac{R_D}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$

$$\Gamma_{in|c.l.} = \frac{g_{m1}}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$


$$\Gamma_{out|c.l.} = \frac{R_D}{1 + R_D \times g_{m2} \frac{C_1}{C_1 + C_2}}$$

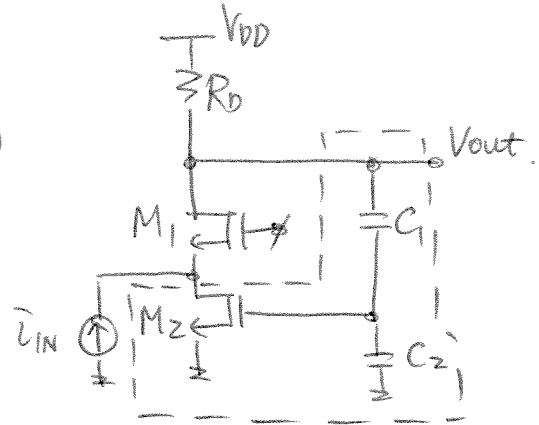

35.

$$(a) G_{OL} = \frac{i_{out}}{v_{in}} = g_m A_1$$

(common emitter)

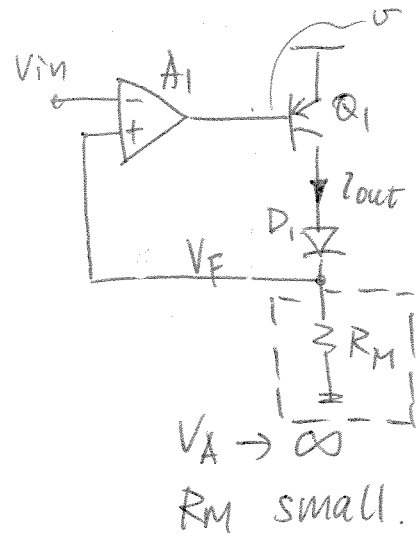

(b)  $K$  (feedback factor)


$$\Rightarrow V_F = i_{out} \times R_M$$

$$\Rightarrow K = \frac{V_F}{i_{out}} = R_M$$


$$\therefore \text{Loop Gain} = G_{OL} K = g_m A_1 R_M$$

$$G_{CL} = \frac{G_{OL}}{1 + G_{OL} K} = \frac{g_m A_1}{1 + g_m A_1 R_M}$$

36.

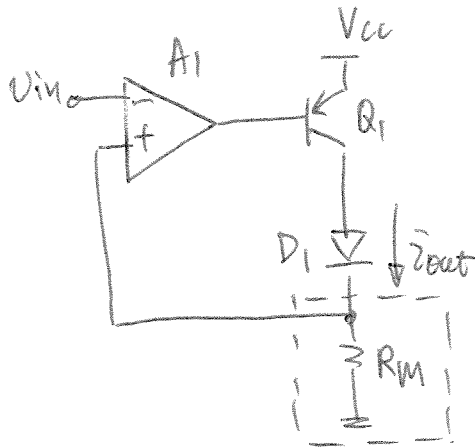

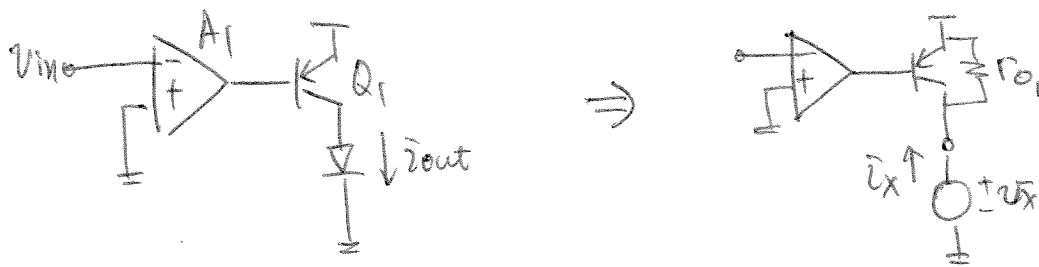Since  $R_M$  is small, the following circuit results:




$$\therefore R_{out, OPEN} = \frac{v_x}{i_x} = r_{o1}$$


$$G_{OL} = \frac{i_{out}}{v_{in}} = A_1 g_{m1} \quad k = R_M$$

$$\begin{aligned} \therefore R_{out, CLOSED} &= R_{out, OPEN} (1 + G_{OL} k) \\ &= r_{o1} (1 + A_1 g_{m1} R_M) \end{aligned}$$

37.

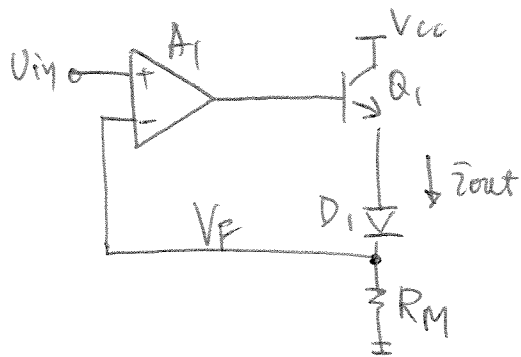

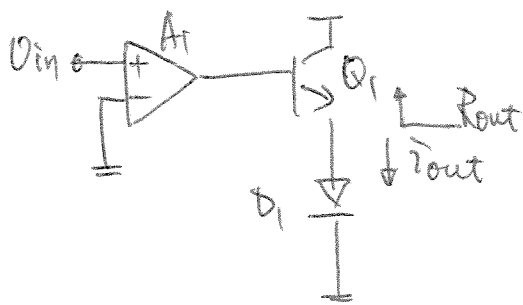Since  $R_M$  is small, the open-loop equivalent becomes the following:



$$G_{OL} = \frac{\bar{z}_{out}}{v_{in}} \approx A_1 g_{m_1}$$

$$R_{out} = \frac{r_T}{\beta + 1} \approx \frac{1}{g_{m_1}}$$

$$K = \frac{V_F}{i_{out}} = R_M$$

$$\Rightarrow G_{CL} = \frac{G_{OL}}{1 + G_{OL}K} = \frac{A_1 g_{m_1}}{1 + g_{m_1} A_1 R_M}$$

$$\text{Loop Gain} = G_{OL}K = g_{m_1} A_1 R_M$$

$$R_{out, \text{closed}} = \frac{1}{g_{m_1}} (1 + g_{m_1} A_1 R_M)$$

This circuit provides a much lower output resistance which in general is non-desirable (ideally any current source should have high impedance.)

38.

Using procedure in Ex 12.21


$$G_{o.l.} = \frac{\bar{i}_{out}}{V_{in}} = g_{m2} R_C \times g_{m1}$$

$K$  (feedback factor)

$$= \frac{V_F}{\bar{i}_{out}} = R_M$$

$$\Rightarrow \text{loop gain} = G_{o.l.} \times K = g_{m1} g_{m2} R_C R_M$$
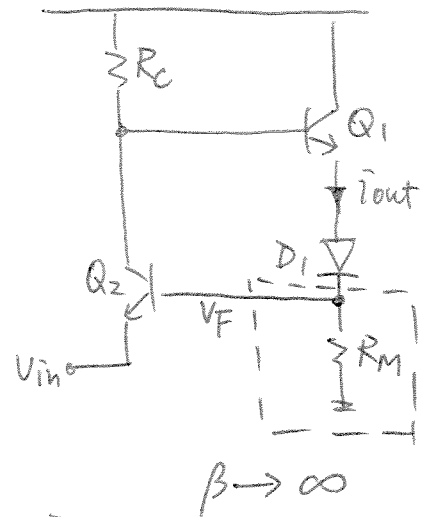
$$\Rightarrow \text{closed-loop gain } G_{c.l.} = \frac{g_{m1} g_{m2} R_C}{1 + g_{m1} g_{m2} R_C R_M}$$



Using procedure in Ex. 12.22

$$G_{o.l.} = g_{m1} g_{m2} R_C$$

$$K = R_M$$

$$r_{in|o.l.} = \frac{1}{g_{m1}}$$

$$r_{out|o.l.} \cong \frac{1}{g_{m2}}$$

$$r_{in|c.l.} = \frac{1}{g_{m1}} (1 + g_{m1} g_{m2} R_C R_M)$$

$$r_{out|c.l.} = \frac{1}{g_{m2}} (1 + g_{m1} g_{m2} R_C R_M)$$



39.


(a)  $\bar{i}_{IN} \uparrow \Delta \Rightarrow$  Most of  $\bar{i}_{IN}$  flows into  $1/g_{m1}$

$\Rightarrow V_{G,M2} \uparrow$  (Common Gate)

$\Rightarrow V_x \uparrow$  (Source Follower)

$\Rightarrow R_F$  momentarily provides more current to Source of  $M_1$

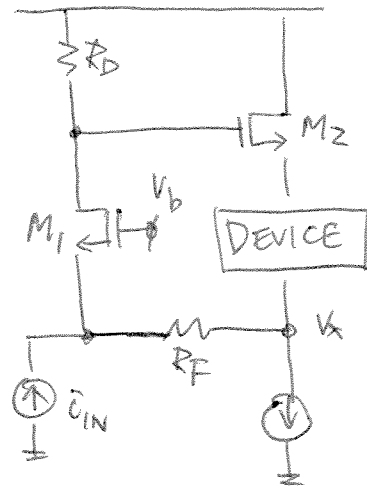$\Rightarrow V_{G,M2} \uparrow \Rightarrow$  Positive feedback.




(b)

$$V_a \times g_{m2} \times R_D = V_b$$

$$\Rightarrow \text{loop gain} = -\frac{V_b}{V_a} = -g_{m2} R_D.$$

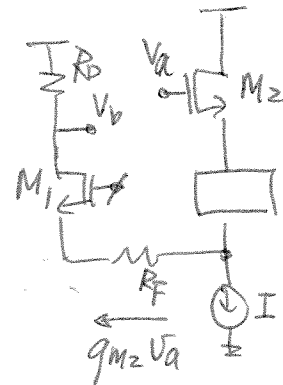Since loop gain is negative, feedback is positive.





12.40 (a)

$$\begin{aligned}
 A_{OL} &= g_{m2} (R_C \parallel r_{\pi 2}) \\
 A_{loop} &= \frac{g_{m1} g_{m2} (R_F \parallel R_M) (R_C \parallel r_{\pi 2})}{1 + g_{m1} R_F} \\
 &= \frac{g_{m2} (R_F \parallel R_M) (R_C \parallel r_{\pi 2})}{\frac{1}{g_{m1}} + R_F} \\
 &\approx g_{m2} (R_C \parallel r_{\pi 2}) \frac{R_F \parallel R_M}{R_F} \quad (\text{since } R_F \text{ is very large}) \\
 \frac{i_{out}}{i_{in}} &= \boxed{\frac{g_{m2} (R_C \parallel r_{\pi 2})}{1 + g_{m2} (R_C \parallel r_{\pi 2}) \frac{R_F \parallel R_M}{R_F}}} \\
 R_{in,open} &= \frac{1}{g_{m1}} \parallel r_{\pi 1} \\
 R_{in,closed} &= \boxed{\frac{\frac{1}{g_{m2}} \parallel r_{\pi 1}}{1 + g_{m2} (R_C \parallel r_{\pi 2}) \frac{R_F \parallel R_M}{R_F}}} \\
 R_{out,open} &= R_{out,closed} = \boxed{\infty} \quad (\text{since } V_A = \infty)
 \end{aligned}$$


(b)

$$\begin{aligned}
 A_{OL} &= -g_{m2} R_M (R_C \parallel r_{\pi 2}) \\
 A_{loop} &\approx g_{m2} (R_C \parallel r_{\pi 2}) \frac{R_F \parallel R_M}{R_F} \quad (\text{same as (a)}) \\
 \frac{v_{out}}{i_{in}} &= \boxed{-\frac{g_{m2} R_M (R_C \parallel r_{\pi 2})}{1 + g_{m2} (R_C \parallel r_{\pi 2}) \frac{R_F \parallel R_M}{R_F}}} \\
 R_{in,open} &= \frac{1}{g_{m1}} \parallel r_{\pi 1} \\
 R_{in,closed} &= \boxed{\frac{\frac{1}{g_{m1}} \parallel r_{\pi 1}}{1 + g_{m2} (R_C \parallel r_{\pi 2}) \frac{R_F \parallel R_M}{R_F}}} \\
 R_{out,open} &= R_M \parallel R_F \\
 R_{out,closed} &= \boxed{\frac{R_M \parallel R_F}{1 + g_{m2} (R_C \parallel r_{\pi 2}) \frac{R_F \parallel R_M}{R_F}}}
 \end{aligned}$$

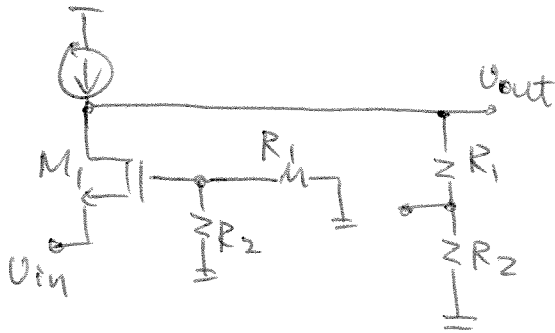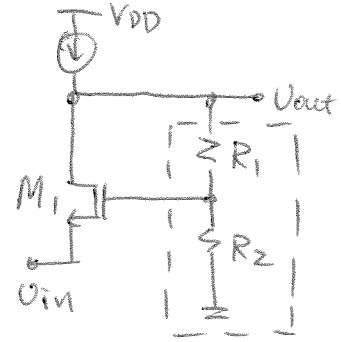41. Breaking the feedback network results in the following circuit:



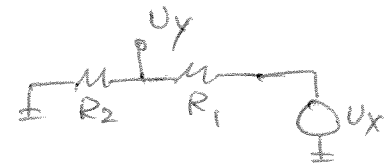Feedback factor  
 $= K = \frac{V_y}{V_x} = \frac{R_2}{R_1 + R_2}$



$$A_{o.L.} = +g_{m1} (R_1 + R_2)$$


$$\text{Loop Gain} = A_{o.L.} K = g_{m1} R_2$$

$$\therefore A_{c.L.} = \frac{A_{o.L.}}{1 + A_{o.L.} K} = \frac{g_{m1} (R_1 + R_2)}{1 + g_{m1} R_2}$$

$$R_{in, \text{closed}} = \frac{1}{g_{m1}} (1 + g_{m1} R_2)$$

$$R_{out, \text{closed}} = \frac{R_1 + R_2}{1 + g_{m1} R_2}$$

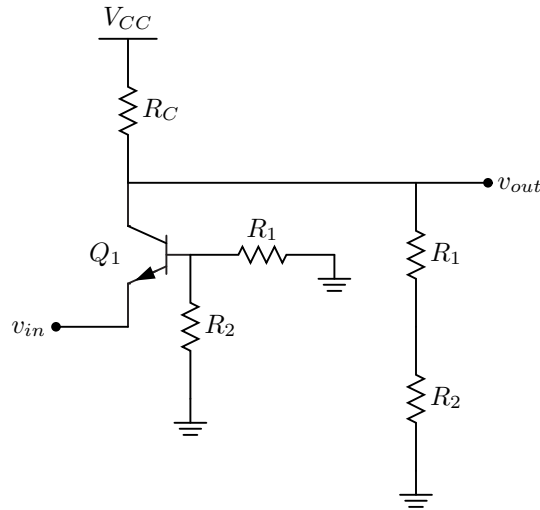12.42 We can break the feedback network as shown here:



$$A_{OL} = \frac{R_C \parallel (R_1 + R_2)}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}}$$

$$K = \frac{R_2}{R_1 + R_2}$$

$$\frac{v_{out}}{v_{in}} = \frac{\frac{R_C \parallel (R_1 + R_2)}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}}}{1 + \frac{R_2}{R_1 + R_2} \frac{R_C \parallel (R_1 + R_2)}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}}}$$


$$R_{in,open} = \frac{r_{\pi 1} + R_1 \parallel R_2}{1 + \beta}$$

$$R_{in,closed} = \left( \frac{r_{\pi 1} + R_1 \parallel R_2}{1 + \beta} \right) \left( 1 + \frac{R_2}{R_1 + R_2} \frac{R_C \parallel (R_1 + R_2)}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}} \right)$$

$$R_{out,open} = R_C \parallel (R_1 + R_2)$$

$$R_{out,closed} = \frac{R_C \parallel (R_1 + R_2)}{1 + \frac{R_2}{R_1 + R_2} \frac{R_C \parallel (R_1 + R_2)}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}}}$$

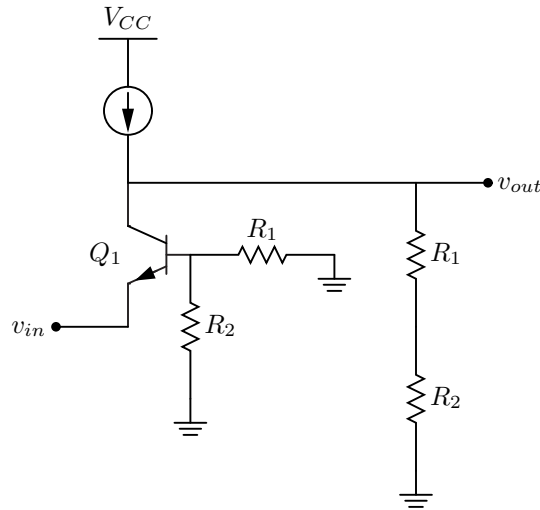12.43 We can break the feedback network as shown here:



$$A_{OL} = \frac{R_1 + R_2}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}}$$

$$K = \frac{R_2}{R_1 + R_2}$$

$$\frac{v_{out}}{v_{in}} = \frac{\frac{\frac{R_1 + R_2}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}}}{1 + \frac{R_2}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}}}}$$


$$R_{in,open} = \frac{r_{\pi 1} + R_1 \parallel R_2}{1 + \beta}$$

$$R_{in,closed} = \left( \frac{r_{\pi 1} + R_1 \parallel R_2}{1 + \beta} \right) \left( 1 + \frac{R_2}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}} \right)$$

$$R_{out,open} = R_1 + R_2$$

$$R_{out,closed} = \frac{R_1 + R_2}{1 + \frac{R_2}{\frac{1}{g_{m1}} + \frac{R_1 \parallel R_2}{1 + \beta}}}$$

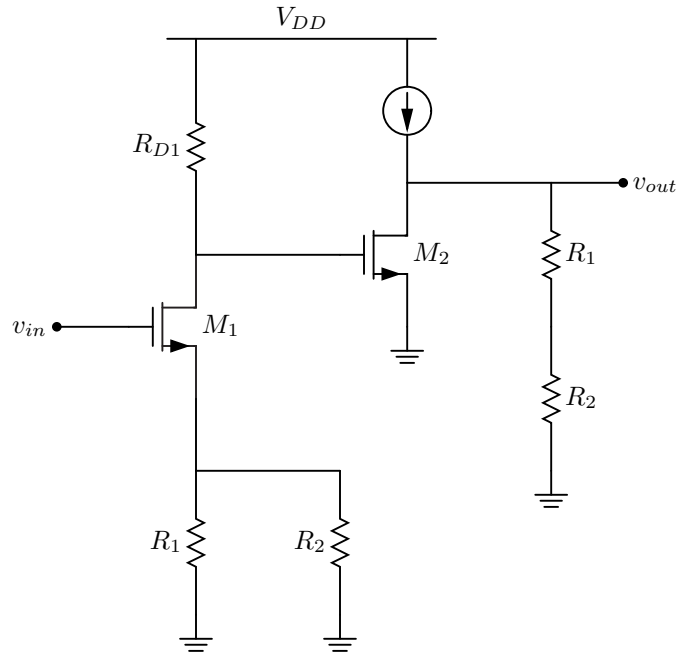12.44 We can break the feedback network as shown here:



$$A_{OL} = \frac{g_{m1}g_{m2}R_{D1}(R_1 + R_2)}{1 + g_{m1}(R_1 \parallel R_2)}$$

$$K = \frac{R_2}{R_1 + R_2}$$


$$\frac{v_{out}}{v_{in}} = \frac{\frac{g_{m1}g_{m2}R_{D1}(R_1+R_2)}{1+g_{m1}(R_1 \parallel R_2)}}{1 + \frac{g_{m1}g_{m2}R_{D1}R_2}{1+g_{m1}(R_1 \parallel R_2)}}$$

$$R_{in,open} = R_{in,closed} = \boxed{\infty}$$

$$R_{out,open} = R_1 + R_2$$

$$R_{out,closed} = \boxed{\frac{R_1 + R_2}{1 + \frac{g_{m1}g_{m2}R_{D1}R_2}{1+g_{m1}(R_1 \parallel R_2)}}$$

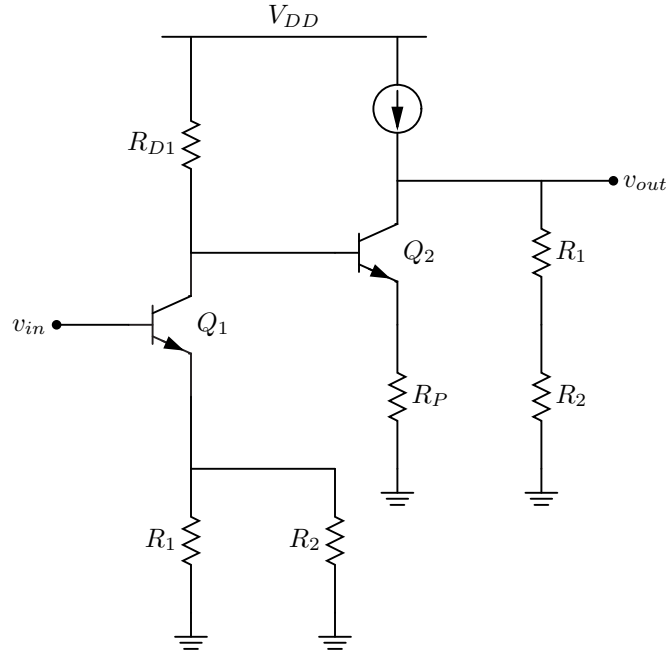12.45 We can break the feedback network as shown here:



$$A_{OL} = \frac{g_{m1}g_{m2} [R_{D1} \parallel (r_{\pi 2} + (1 + \beta) R_P)] (R_1 + R_2)}{[1 + g_{m1} (R_1 \parallel R_2)] (1 + g_{m2} R_P)}$$

$$K = \frac{R_2}{R_1 + R_2}$$

$$\frac{v_{out}}{v_{in}} = \frac{\frac{g_{m1}g_{m2} [R_{D1} \parallel (r_{\pi 2} + (1 + \beta) R_P)] (R_1 + R_2)}{[1 + g_{m1} (R_1 \parallel R_2)] (1 + g_{m2} R_P)}}{1 + \frac{g_{m1}g_{m2} [R_{D1} \parallel (r_{\pi 2} + (1 + \beta) R_P)] R_2}{[1 + g_{m1} (R_1 \parallel R_2)] (1 + g_{m2} R_P)}}$$


$$R_{in,open} = r_{\pi 1} + (1 + \beta) (R_1 \parallel R_2)$$

$$R_{in,closed} = \left\{ r_{\pi 1} + (1 + \beta) (R_1 \parallel R_2) \right\} \left\{ 1 + \frac{g_{m1}g_{m2} [R_{D1} \parallel (r_{\pi 2} + (1 + \beta) R_P)] R_2}{[1 + g_{m1} (R_1 \parallel R_2)] (1 + g_{m2} R_P)} \right\}$$

$$R_{out,open} = R_1 + R_2$$

$$R_{out,closed} = \frac{R_1 + R_2}{1 + \frac{g_{m1}g_{m2} [R_{D1} \parallel (r_{\pi 2} + (1 + \beta) R_P)] R_2}{[1 + g_{m1} (R_1 \parallel R_2)] (1 + g_{m2} R_P)}}$$

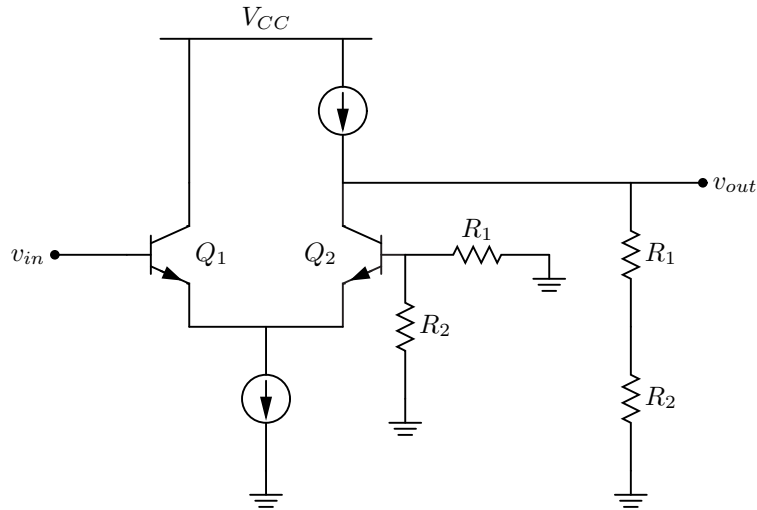12.46 We can break the feedback network as shown here:



$$A_{OL} = \left( \frac{\frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}}{\frac{1}{g_{m1}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right) \left( \frac{R_1 + R_2}{\frac{1}{g_{m2}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right)$$

$$K = \frac{R_2}{R_1 + R_2}$$

$$\frac{v_{out}}{v_{in}} = \frac{\left( \frac{\frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}}{\frac{1}{g_{m1}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right) \left( \frac{R_1 + R_2}{\frac{1}{g_{m2}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right)}{1 + \left( \frac{\frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}}{\frac{1}{g_{m1}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right) \left( \frac{R_2}{\frac{1}{g_{m2}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right)}$$

$$R_{in,open} = r_{\pi 1} + (1 + \beta_1) \left( \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2} \right)$$


$$R_{in,closed} = \left[ r_{\pi 1} + (1 + \beta_1) \left( \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2} \right) \right] \left[ 1 + \left( \frac{\frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}}{\frac{1}{g_{m1}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right) \left( \frac{R_2}{\frac{1}{g_{m2}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right) \right]$$

$$R_{out,open} = R_1 + R_2$$

$$R_{out,closed} = \frac{R_1 + R_2}{1 + \left( \frac{\frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}}{\frac{1}{g_{m1}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right) \left( \frac{R_2}{\frac{1}{g_{m2}} + \frac{r_{\pi 2} + R_1 \parallel R_2}{1 + \beta_2}} \right)}$$




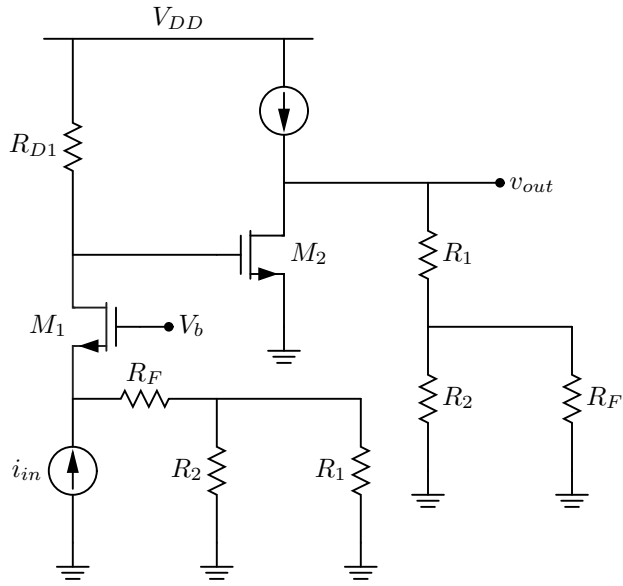12.47 We can break the feedback network as shown here:



$$A_{OL} = -g_{m2} [r_{o2} \parallel (R_1 + R_2 \parallel R_F)] R_{D1} \frac{R_F + R_1 \parallel R_2}{\frac{1}{g_{m1}} + R_F + R_1 \parallel R_2}$$

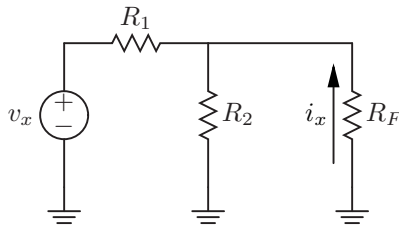To find the feedback factor  $K$ , we can use the following diagram:



$$K = \frac{i_x}{v_x} = -\frac{R_2}{(R_1 + R_2 \parallel R_F)(R_2 + R_F)} = -\frac{R_2 \parallel R_F}{R_F(R_1 + R_2 \parallel R_F)}$$

$$\frac{v_{out}}{i_{in}} = \frac{g_{m2} [r_{o2} \parallel (R_1 + R_2 \parallel R_F)] R_{D1} \frac{R_F + R_1 \parallel R_2}{\frac{1}{g_{m1}} + R_F + R_1 \parallel R_2}}{1 + \left\{ g_{m2} [r_{o2} \parallel (R_1 + R_2 \parallel R_F)] R_{D1} \frac{R_F + R_1 \parallel R_2}{\frac{1}{g_{m1}} + R_F + R_1 \parallel R_2} \right\} \left\{ \frac{R_2 \parallel R_F}{R_F(R_1 + R_2 \parallel R_F)} \right\}}$$



$$R_{in,open} = \frac{1}{g_{m1}} \parallel (R_F + R_1 \parallel R_2)$$

$$R_{in,closed} = \frac{\frac{1}{g_{m1}} \parallel (R_F + R_1 \parallel R_2)}{1 + \left\{ g_{m2} [r_{o2} \parallel (R_1 + R_2 \parallel R_F)] R_{D1} \frac{R_F + R_1 \parallel R_2}{\frac{1}{g_{m1}} + R_F + R_1 \parallel R_2} \right\} \left\{ \frac{R_2 \parallel R_F}{R_F(R_1 + R_2 \parallel R_F)} \right\}}$$

$$R_{out,open} = r_{o2} \parallel (R_1 + R_2 \parallel R_F)$$

$$R_{out,closed} = \frac{r_{o2} \parallel (R_1 + R_2 \parallel R_F)}{1 + \left\{ g_{m2} [r_{o2} \parallel (R_1 + R_2 \parallel R_F)] R_{D1} \frac{R_F + R_1 \parallel R_2}{\frac{1}{g_{m1}} + R_F + R_1 \parallel R_2} \right\} \left\{ \frac{R_2 \parallel R_F}{R_F(R_1 + R_2 \parallel R_F)} \right\}}$$

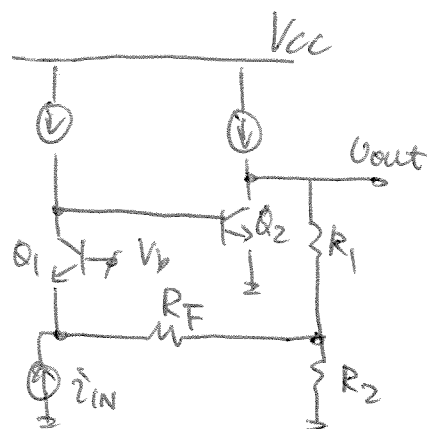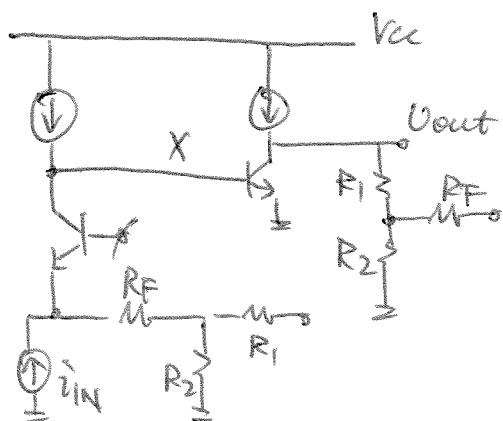48. Breaking the feedback network results in the following circuit:




$$R_{OL} = \frac{U_{out}}{i_{IN}} = \frac{v_{out}}{v_x} \times \frac{v_x}{i_{IN}} = [-g_{m2}(R_1 + R_2)] \times [g_{m1}, r_{\pi 2} \left\{ \frac{1}{g_{m1}} \parallel (R_F + R_2) \right\}]$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \parallel (R_F + R_2)$$

$$R_{out, OPEN} = R_1 + R_2$$
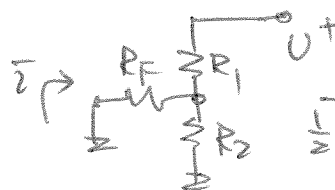
$$K = \frac{v}{v} = - \frac{(R_2 \parallel R_F) / R_F}{R_1 + (R_2 \parallel R_F)}$$





$$\therefore R_{CL} = \frac{R_{OL}}{1 + R_{OL}K}$$

$$R_{in, CLOSED} = \frac{\frac{1}{g_{m1}} \parallel (R_F + R_2)}{1 + R_{OL}K}$$

$$R_{out, CLOSED} = \frac{R_1 + R_2}{1 + R_{OL}K}$$

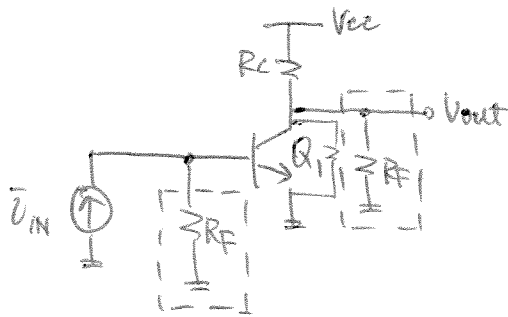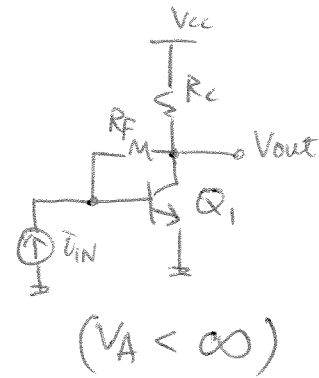49. The feedback network consists of  $R_F$ .

Using the method discussed in lecture, break the circuit as follows:



This is the open-loop circuit with consideration of I/O loading.

- By inspection,

$$v_{out} = i_c \times (R_C \parallel R_F \parallel r_o)$$

$$= -g_m (i_{in} \times (R_F \parallel r_{\pi})) \times (R_C \parallel R_F \parallel r_o)$$

$$\Rightarrow R_{o.l.} = \frac{v_{out}}{i_{in}} = -g_m (R_F \parallel r_{\pi}) (R_C \parallel R_F \parallel r_o) \quad \text{--- (1)}$$

$$R_{in, open} = (R_F \parallel r_{\pi}) \quad R_{out, open} = (R_C \parallel R_F \parallel r_o)$$

- Feedback factor  $k$ :

$$k = \frac{v_x}{i_x} = -\frac{1}{R_F}$$



$$\therefore R_{o.L.} = \frac{R_{o.L.}}{1 + R_{o.L.} \times K} = \frac{-g_m(R_F \parallel r_{\pi})(R_C \parallel R_F \parallel r_o)}{1 + \frac{g_m(R_F \parallel r_{\pi})(R_C \parallel R_F \parallel r_o)}{R_F}}$$



$$R_{in,CLOSED} = \frac{(R_F \parallel r_{\pi})}{1 - \frac{R_{o.L.}}{R_F}}$$

$$R_{out,CLOSED} = \frac{(R_C \parallel R_F \parallel r_o)}{1 - \frac{R_{o.L.}}{R_F}}$$

where  $R_{o.L.}$  is given by (1).

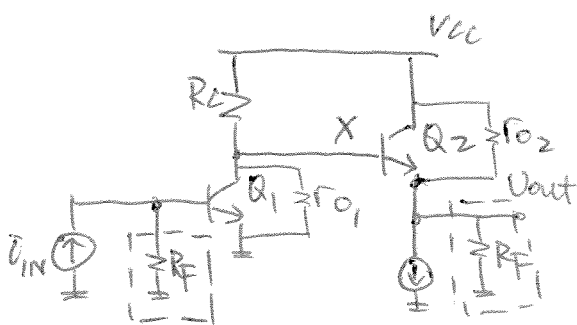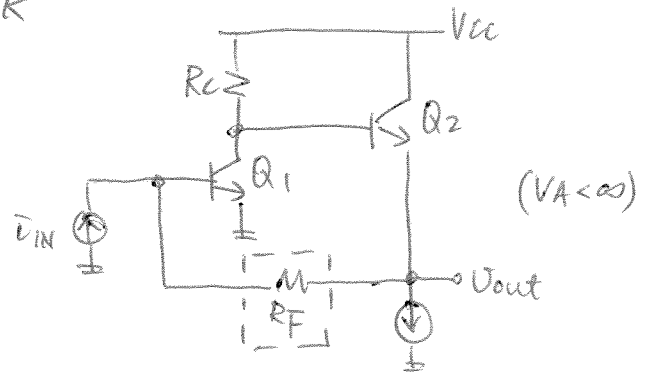50. The feedback network consists of  $R_F$ .

Using the method discussed in lecture, break the circuit as follows:



This is the open-loop circuit with consideration of I/O loading.

- Gain of common-emitter stage:

$$\frac{v_X}{v_{IN}} = -g_{m1}(R_F \parallel r_{\pi 1}) \times \left\{ R_C \parallel r_{o1} \parallel \left[ r_{\pi 2} + (\beta_2 + 1)(R_F \parallel r_{o2}) \right] \right\}$$

- Gain of emitter-follower stage:

$$\frac{v_{OUT}}{v_X} = \frac{g_{m2}(R_F \parallel r_{o2})}{1 + g_{m2}(R_F \parallel r_{o2})}$$


$$\Rightarrow R_{o.L.} = \frac{v_X}{v_{IN}} \cdot \frac{v_{OUT}}{v_X} \quad \text{--- (1)}$$

$$R_{in, OPEN} = R_F \parallel r_{\pi 1}$$

$$R_{out, OPEN} \cong R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}}$$

- Feedback factor  $k$ :
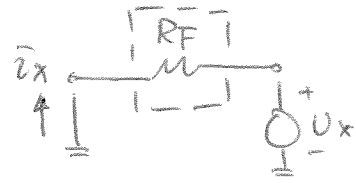
$$k = \frac{v_x}{\bar{v}_x} = -\frac{1}{R_F}$$





$$\therefore R_{o,L} = \frac{R_{o,L}}{1 + R_{o,L} \times k} = \frac{R_{o,L}}{1 - R_{o,L}/R_F}$$

$$R_{in,CLOSED} = \frac{(R_F \parallel \Gamma_{\pi_1})}{1 - \frac{R_{o,L}}{R_F}} \quad R_{out,CLOSED} = \frac{R_F \parallel r_{o2} \parallel \frac{1}{g_{m2}}}{1 - \frac{R_{o,L}}{R_F}}$$

where  $R_{o,L}$  is given by (1).

51.

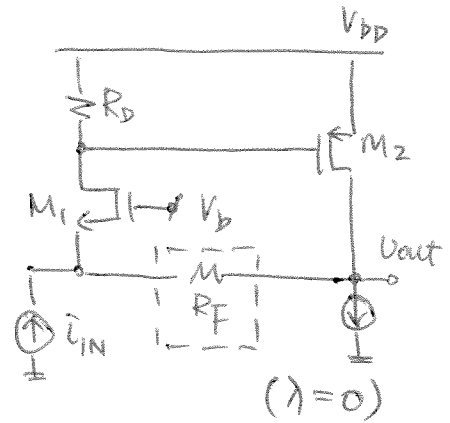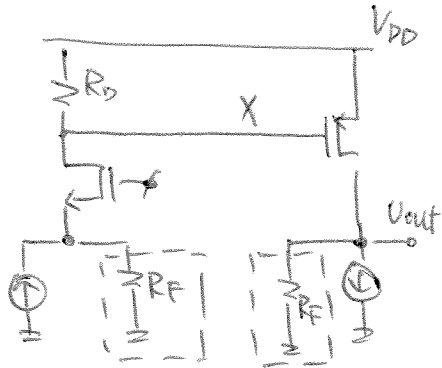(a) Breaking the feedback loop results in the following circuit:



$$R_{o.l.} = \frac{v_x}{i_{in}} \cdot \frac{v_{out}}{v_x}$$


$$= g_{m1} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \times (-g_{m2} R_F)$$

$$R_{in, OPEN} = \frac{1}{g_{m1}} \parallel R_F$$

$$R_{out, OPEN} = R_F$$

- Feedback factor  $k$ :

$$k = \frac{v_x}{v_x} = -\frac{1}{R_F}$$

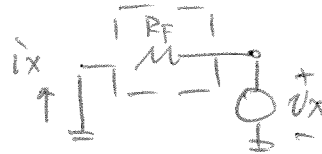



$$\Rightarrow R_{c.l.} = \frac{R_{o.l.}}{1 + R_{o.l.} \times k} = \frac{-g_{m1} g_{m2} R_D R_F \left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$

$$R_{in, CLOSED} = \frac{\left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$

$$R_{out, CLOSED} = \frac{R_F}{1 + g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right)}$$



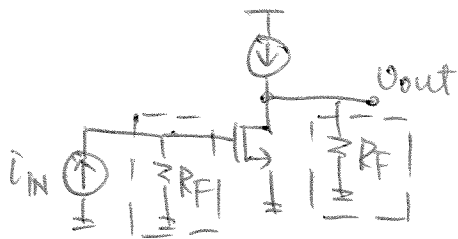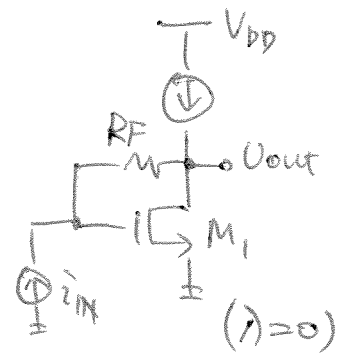(b) Breaking the feedback loop results in the following circuit:




$$R_{o.L.} = \frac{V_{out}}{i_{in}} = -g_m R_F R_F = -g_m R_F^2$$

$$R_{in, OPEN} = R_F \quad R_{out, OPEN} = R_F$$

- Feedback factor  $K$ :

$$K = \frac{V_x}{i_x} = -\frac{1}{R_F}$$

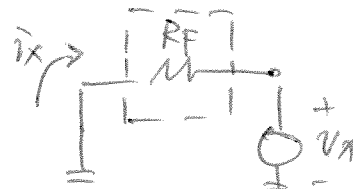


$$\Rightarrow R_{c.L.} = \frac{-g_m R_F^2}{1 + g_m R_F}$$


$$R_{in, CLOSED} = \frac{R_F}{1 + g_m R_F}$$

$$R_{out, CLOSED} = \frac{R_F}{1 + g_m R_F}$$

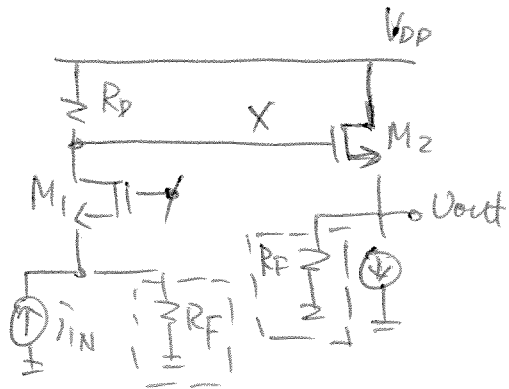(c) Breaking the feedback loop results in the following circuit:


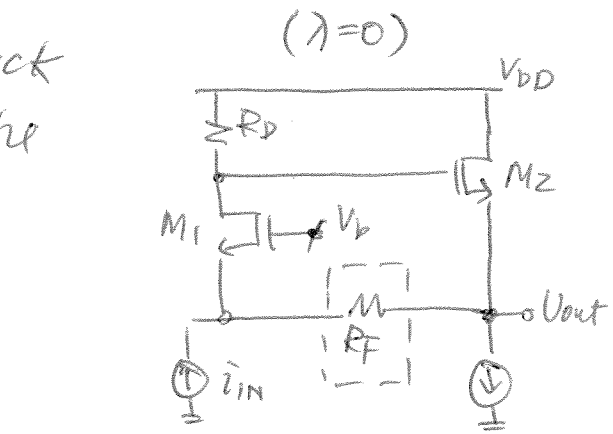
$$R_{in, OPEN} = \left( \frac{1}{g_{m1}} \parallel R_F \right)$$




$$\begin{aligned} R_{o.L.} &= \frac{V_{out}}{i_{IN}} = \frac{V_x}{i_{IN}} \cdot \frac{V_{out}}{V_x} \\ &= g_{m1} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \times \\ &\quad g_{m2} \left( R_F \parallel \frac{1}{g_{m2}} \right) \end{aligned}$$

$$R_{out, OPEN} = \left( R_F \parallel \frac{1}{g_{m2}} \right)$$

- Feedback factor  $K$ :

$$K = \frac{V_x}{i_x} = -\frac{1}{R_F}$$

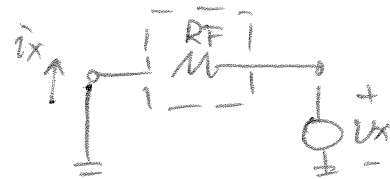



(Note: Feedback is positive.)

$$\begin{aligned} \Rightarrow R_{c.L.} &= \frac{R_{o.L.}}{1 + R_{o.L.} \times K} \\ &= \frac{g_{m1} g_{m2} R_D \left( \frac{1}{g_{m1}} \parallel R_F \right) \left( \frac{1}{g_{m2}} \parallel R_F \right)}{1 - g_{m1} g_{m2} \left( \frac{R_D}{R_F} \right) \left( \frac{1}{g_{m1}} \parallel R_F \right) \left( \frac{1}{g_{m2}} \parallel R_F \right)} \end{aligned}$$

$$R_{in, CLOSED} = \frac{\left( \frac{1}{g_{m1}} \parallel R_F \right)}{1 - \frac{R_{o.L.}}{R_F}}$$

$$R_{out, CLOSED} = \frac{\left( \frac{1}{g_{m2}} \parallel R_F \right)}{1 - \frac{R_{o.L.}}{R_F}}$$

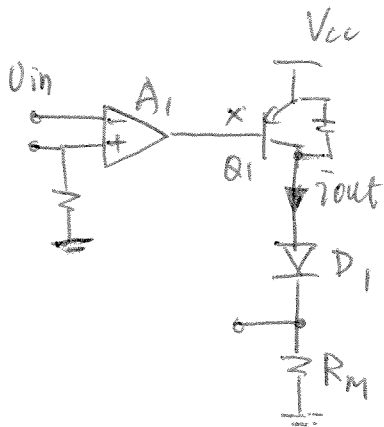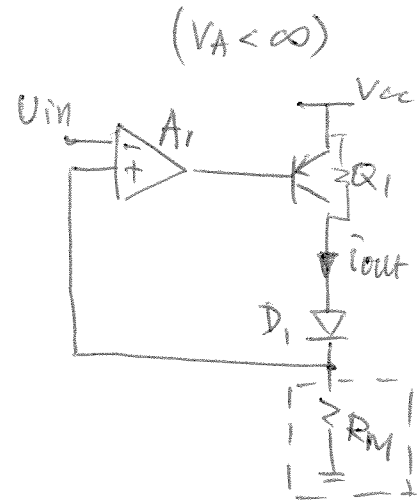
52. Breaking the feedback network (i.e.  $R_M$ ) results in the following circuit:



$$G_{OL} = \frac{\bar{i}_{out}}{U_{in}} = \frac{\bar{i}_{out}}{U_x} \times \frac{U_x}{U_{in}} \quad (1)$$

$$= \underbrace{g_{m1} \times \frac{[R_L + R_M] \parallel r_{o1}}{(R_L + R_M)}}_{\text{(current division)}} \times (-A_1)$$

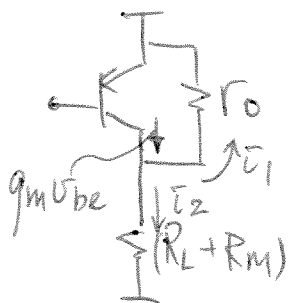Note: current ( $g_m V_{be}$ ) splits between  $r_o$  &  $[R_L$  (impedance of  $D_1$ ) +  $R_M$ ]




$$g_m V_{be} = \bar{i}_1 + \bar{i}_2$$

$$R_{in, OPEN} \rightarrow \infty$$

$$R_{out, OPEN} = r_{o1} + R_M$$

- Feedback factor  $K$ :

$$K = \frac{U_x}{\bar{i}_x} = R_M$$

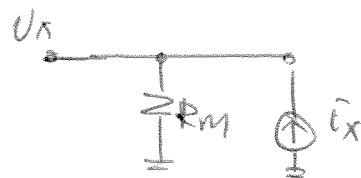



$$\therefore G_{o.l.} = \frac{G_{o.l.}}{1 + G_{o.l.} \times K} = \frac{G_{o.l.}}{1 + G_{o.l.} \times R_M}$$

$$R_{in, CLOSED} \rightarrow \infty$$

$$R_{out, CLOSED} = (T_{o1} + R_M)(1 + G_{o.l.} \times R_M)$$

where  $G_{o.l.}$  is given by (1)

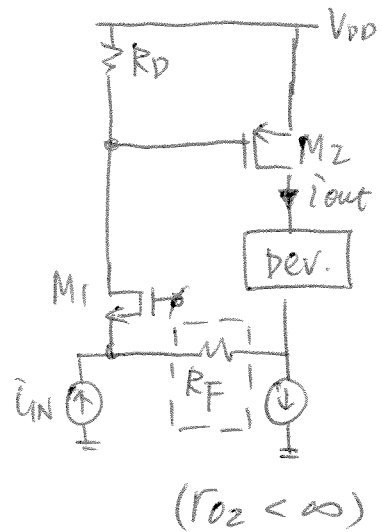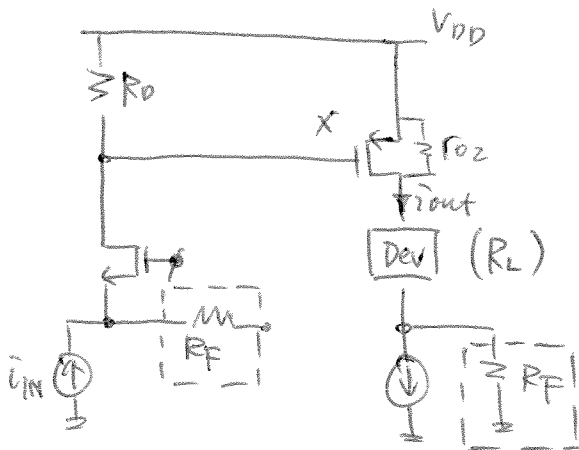53. Breaking the feedback loop results in the following circuit :



$$A_{I, o.l.} = \frac{\bar{i}_{out}}{\bar{i}_{in}} = \frac{\bar{i}_{out}}{V_x} \times \frac{V_x}{\bar{i}_{in}}$$

$$= -g_{m2} \times \frac{(R_L + R_F) \parallel r_{o2}}{(R_L + R_F)} \times R_D$$

$$R_{in, open} = \frac{1}{g_{m1}}$$

$$R_{out, open} = r_{o2} + R_F$$

- Feedback factor  $K$  :

$$K = \frac{\bar{i}_y}{\bar{i}_x} = -1$$




$$\Rightarrow A_{I, c.l.} = \frac{A_{I, o.l.}}{1 + A_{I, o.l.} \times K} = \frac{A_{I, o.l.}}{1 - A_{I, o.l.}}$$

$$R_{in, closed} = \frac{1/g_{m1}}{1 - A_{I, o.l.}}$$

$$R_{out, closed} = (r_{o2} + R_F)(1 - A_{I, o.l.})$$

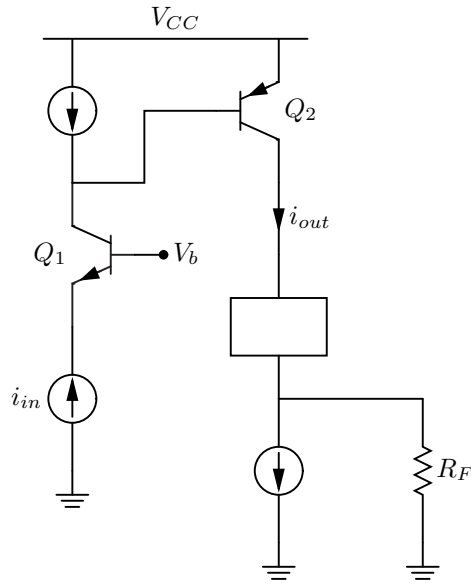12.54 We can break the feedback network as shown here:



$$A_{OL} = -\beta_2$$

$$K = -1 \text{ (by inspection)}$$


$$\frac{i_{out}}{i_{in}} = \boxed{-\frac{\beta_2}{1 + \beta_2}}$$

$$R_{in,open} = \frac{1}{g_{m1}} \parallel r_{\pi 1}$$

$$R_{in,closed} = \boxed{\frac{\frac{1}{g_{m1}} \parallel r_{\pi 1}}{1 + \beta_2}}$$

$$R_{out,open} = R_{out,closed} = \boxed{\infty} \text{ (since } V_A = \infty \text{)}$$

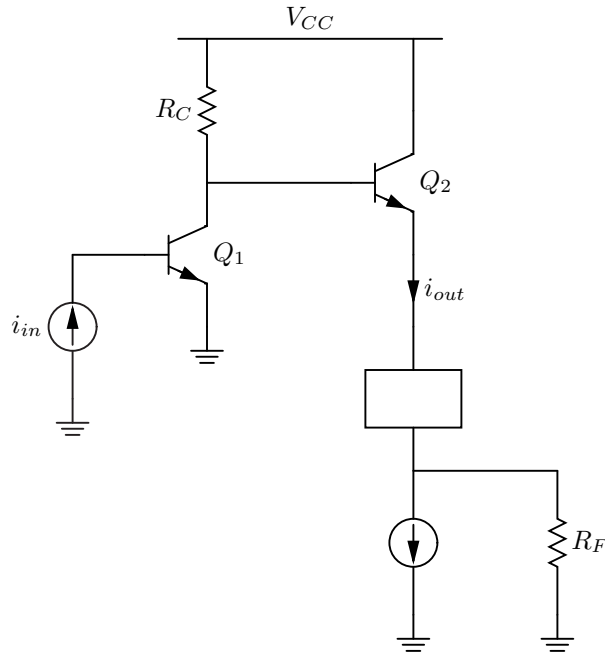12.55 We can break the feedback network as shown here:



We can find  $A_{OL} = \frac{i_{out}}{i_{in}}$  by using current dividers to determine how much of  $i_{in}$  goes to  $i_{out}$ . Let's assume the device has some small-signal resistance  $R_L$ .

$$A_{OL} = -\beta_1\beta_2 \frac{R_C}{R_C + r_{\pi 2} + (1 + \beta_2)(R_L + R_F)}$$

$$K = -1 \text{ (by inspection)}$$

$$\frac{i_{out}}{i_{in}} = \frac{\beta_1\beta_2 \frac{R_C}{R_C + r_{\pi 2} + (1 + \beta_2)(R_L + R_F)}}{1 + \beta_1\beta_2 \frac{R_C}{R_C + r_{\pi 2} + (1 + \beta_2)(R_L + R_F)}}$$

$$R_{in,open} = r_{\pi 1}$$


$$R_{in,closed} = \frac{r_{\pi 1}}{1 + \beta_1\beta_2 \frac{R_C}{R_C + r_{\pi 2} + (1 + \beta_2)(R_L + R_F)}}$$

$$R_{out,open} = \frac{r_{\pi 2} + R_C}{1 + \beta_2} + R_F$$

$$\approx \frac{1}{g_{m2}} + \frac{R_C}{1 + \beta_2} + R_F$$


$$R_{out,closed} = \left( \frac{r_{\pi 2} + R_C}{1 + \beta_2} + R_F \right) \left\{ 1 + \beta_1\beta_2 \frac{R_C}{R_C + r_{\pi 2} + (1 + \beta_2)(R_L + R_F)} \right\}$$

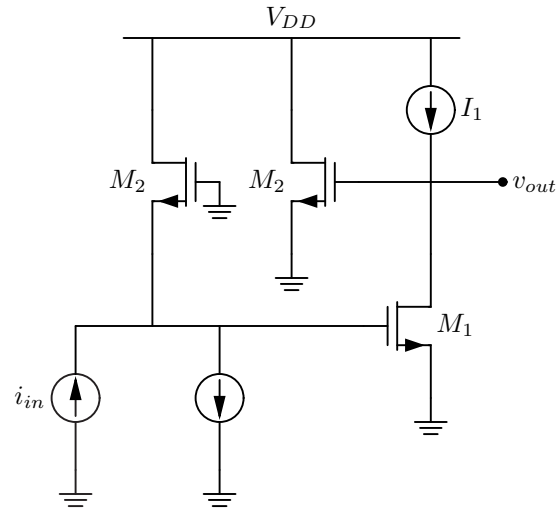12.56 (a) We can break the feedback network as shown here:



$$A_{OL} = -g_{m1}r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)$$

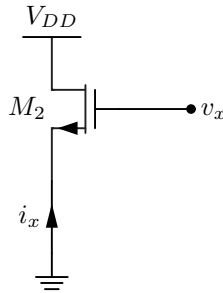To find the feedback factor  $K$ , we can use the following diagram:



$$K = \frac{v_x}{i_x} = -g_{m2}$$

$$\frac{v_{out}}{i_{in}} = \frac{g_{m1}r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)}{1 + g_{m1}g_{m2}r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

$$R_{in,open} = \frac{1}{g_{m2}} \parallel r_{o2}$$


$$R_{in,closed} = \frac{\frac{1}{g_{m2}} \parallel r_{o2}}{1 + g_{m1}g_{m2}r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

$$R_{out,open} = r_{o1}$$

$$R_{out,closed} = \frac{r_{o1}}{1 + g_{m1}g_{m2}r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$




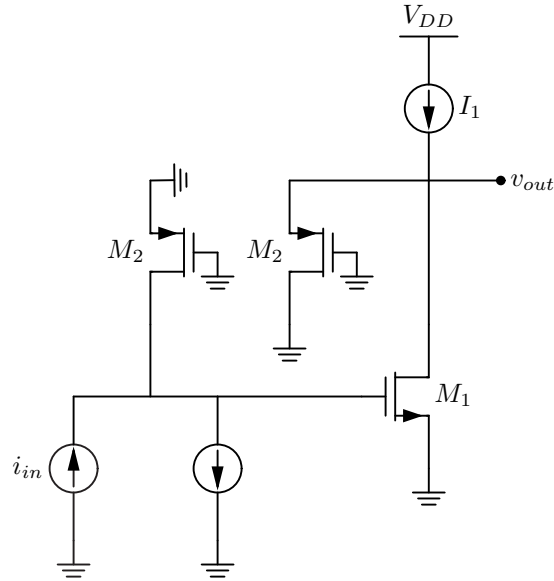(b) We can break the feedback network as shown here:



$$A_{OL} = -g_{m1}r_{o2} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)$$

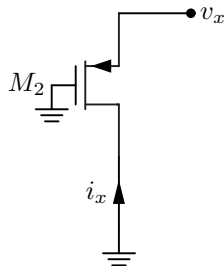To find the feedback factor  $K$ , we can use the following diagram:



$$K = \frac{v_x}{i_x} = -g_{m2}$$

$$\frac{v_{out}}{i_{in}} = \frac{g_{m1}r_{o2} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}{1 + g_{m1}g_{m2}r_{o2} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$


$$R_{in,open} = r_{o2}$$

$$R_{in,closed} = \frac{r_{o2}}{1 + g_{m1}g_{m2}r_{o2} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

$$R_{out,open} = r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2}$$


$$R_{out,closed} = \frac{r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2}}{1 + g_{m1}g_{m2}r_{o2} \left( r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

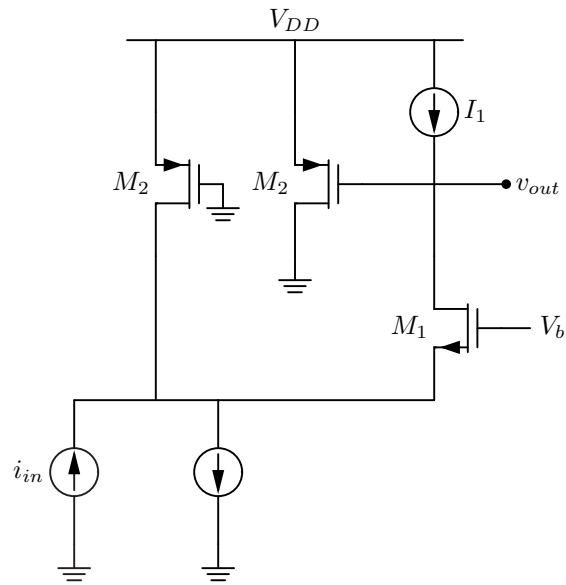(c) We can break the feedback network as shown here:



$$A_{OL} = g_{m1}r_{o1} \left( \frac{1}{g_{m1}} \parallel r_{o2} \right)$$

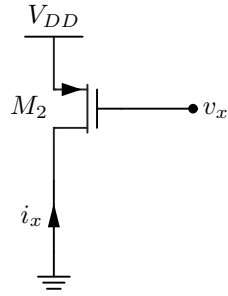To find the feedback factor  $K$ , we can use the following diagram:



$$K = \frac{i_x}{v_x} = g_{m2}$$

$$\frac{v_{out}}{i_{in}} = \frac{g_{m1} r_{o1} \left( \frac{1}{g_{m1}} \parallel r_{o2} \right)}{1 + g_{m1} g_{m2} r_{o1} \left( \frac{1}{g_{m1}} \parallel r_{o2} \right)}$$

$$R_{in,open} = \frac{1}{g_{m1}} \parallel r_{o2}$$


$$R_{in,closed} = \frac{\frac{1}{g_{m1}} \parallel r_{o2}}{1 + g_{m1} g_{m2} r_{o1} \left( \frac{1}{g_{m1}} \parallel r_{o2} \right)}$$

$$R_{out,open} = r_{o1} + (1 + g_{m1} r_{o1}) r_{o2}$$


$$R_{out,closed} = \frac{r_{o1} + (1 + g_{m1} r_{o1}) r_{o2}}{1 + g_{m1} g_{m2} r_{o1} \left( \frac{1}{g_{m1}} \parallel r_{o2} \right)}$$

57.


(a)

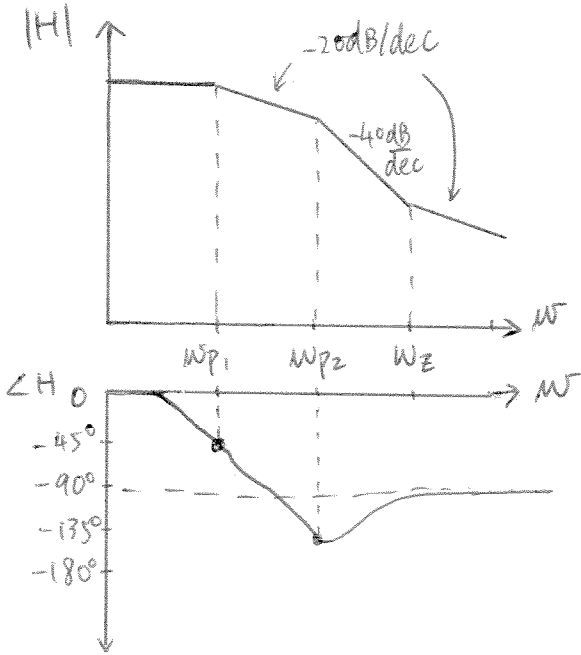


(b)

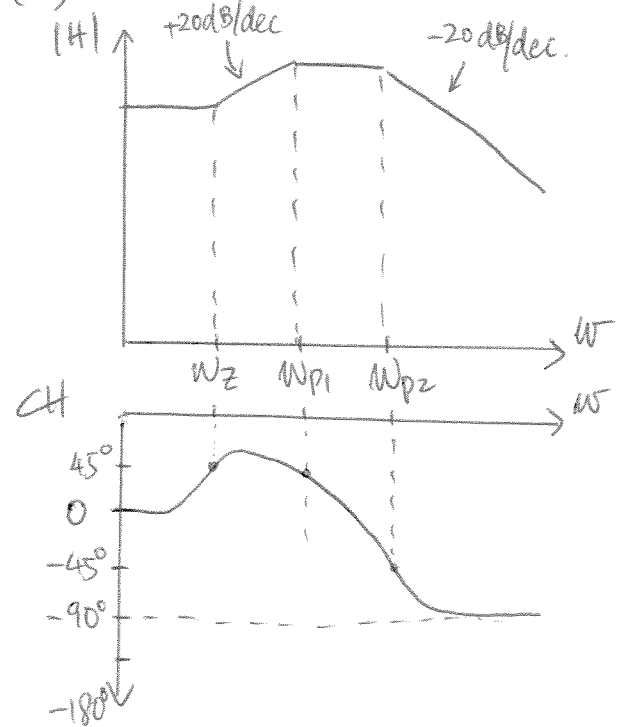

(c)

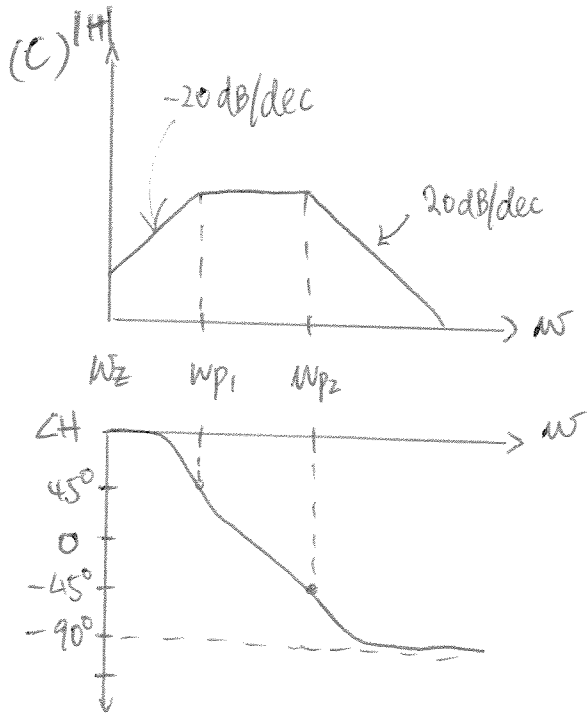


(d)

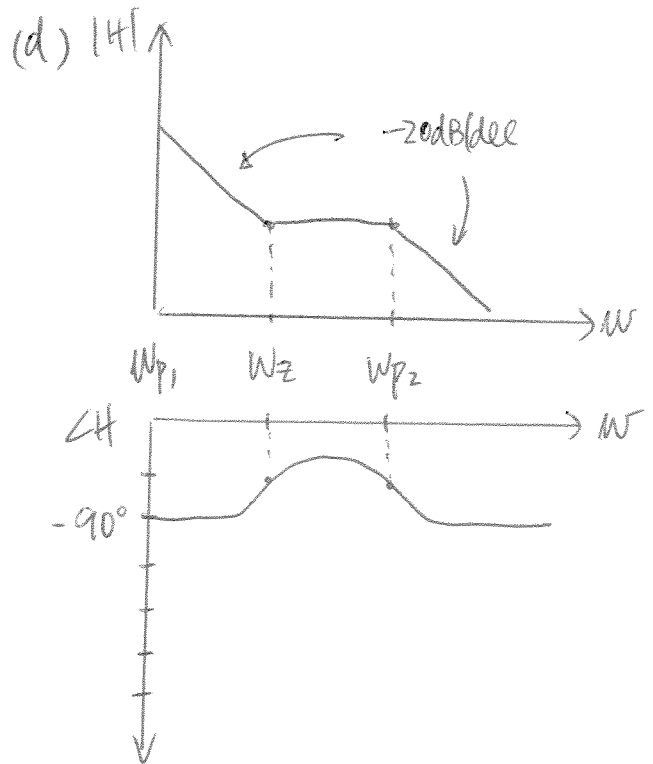


58. As  $\omega_z$  comes closer to  $\omega_{p1}$  or  $\omega_{p2}$ , it cancels out the effect (i.e.  $-20\text{dB/dec}$  decrease) — pole-zero cancellation. It would appear as if nothing occurred at that overlapping frequency.

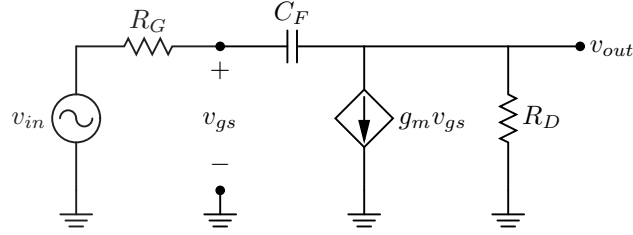12.59 Let's draw the small-signal model and find  $\frac{v_{out}}{v_{in}}(s)$ .



$$\begin{aligned} \frac{v_{in} - v_{gs}}{R_G} &= (v_{gs} - v_{out}) sC_F \\ (v_{gs} - v_{out}) sC_F &= g_m v_{gs} + \frac{v_{out}}{r_{o1}} \\ v_{gs} (sC_F - g_m) &= v_{out} \left( \frac{1}{r_{o1}} + sC_F \right) \\ v_{gs} &= \frac{1 + sC_F r_{o1}}{r_{o1} (sC_F - g_m)} \\ \frac{v_{in}}{R_G} &= v_{gs} \left( \frac{1}{R_G} + sC_F \right) - v_{out} sC_F \\ \frac{v_{in}}{R_G} &= v_{out} \left[ \left( \frac{1 + sC_F r_{o1}}{r_{o1} (sC_F - g_m)} \right) \left( \frac{1}{R_G} + sC_F \right) - sC_F \right] \\ v_{in} &= v_{out} \left[ \left( \frac{1 + sC_F r_{o1}}{r_{o1} (sC_F - g_m)} \right) (1 + sC_F R_G) - sC_F R_G \right] \\ v_{in} &= v_{out} \left[ \frac{(1 + sC_F r_{o1}) (1 + sC_F R_G) - sC_F R_G r_{o1} (sC_F - g_m)}{r_{o1} (sC_F - g_m)} \right] \\ \frac{v_{out}}{v_{in}}(s) &= \boxed{\frac{r_{o1} (sC_F - g_m)}{(1 + sC_F r_{o1}) (1 + sC_F R_G) - sC_F R_G r_{o1} (sC_F - g_m)}} \end{aligned}$$

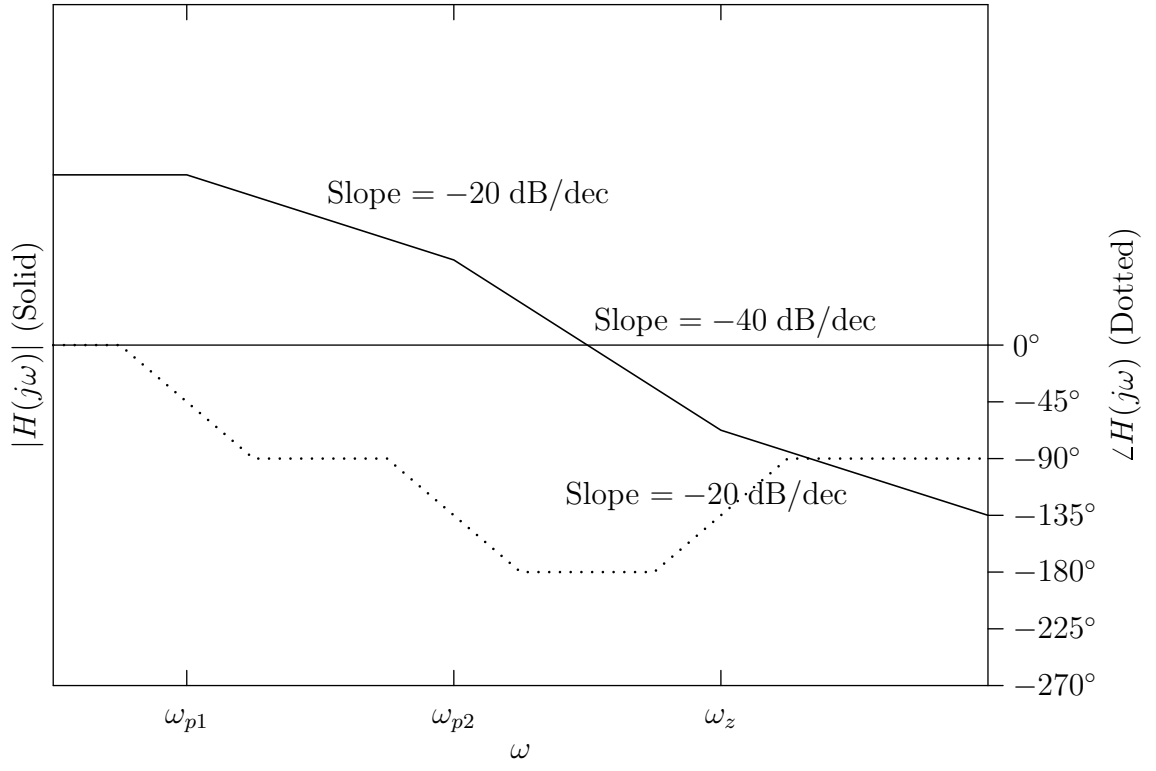
From the transfer function, we can see that we'll have one zero and two poles (since the numerator is of degree 1 and the denominator is of degree 2).



60. By Nyquist Criterion, decreasing  $K$  ( $K \rightarrow 0$ ) eventually leads to  $|KH| < 1$  at  $\angle H = -180^\circ$ , which implies stability.



61.

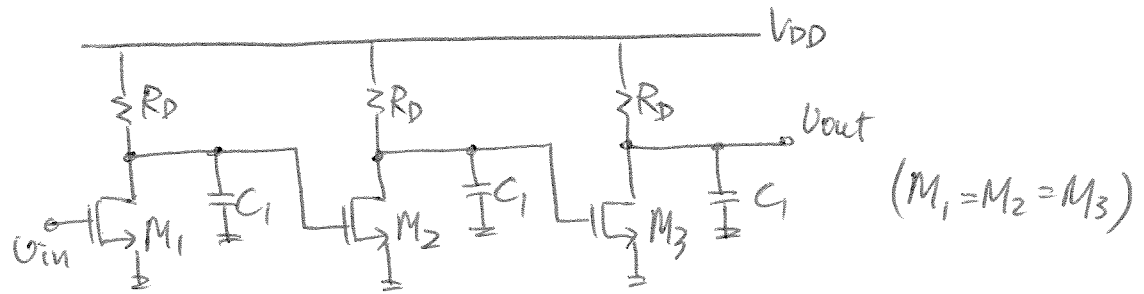

$$H(s) = \frac{V_{out}}{V_{in}}(s) = \frac{(-g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3} \quad \text{where } \omega_p = \frac{1}{R_D C_1}$$

$$\begin{aligned} \Rightarrow \angle H(j\omega) &= \angle (-g_m R_D)^3 - \angle \left(1 + j\frac{\omega}{\omega_p}\right)^3 \\ &= 0 - 3 \tan^{-1}\left(\frac{\omega}{\omega_p}\right) \end{aligned}$$

$$\therefore \angle H \Big|_{\omega=0.1\omega_p} = -3 \tan^{-1}\left(\frac{0.1\omega_p}{\omega_p}\right) \cong -17.1^\circ$$

$$62. \quad H(s) = \frac{(-g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3} \quad (M_1 = M_2 = M_3)$$

$$\Rightarrow |H| \Big|_{\omega=\omega_p} = \frac{|g_m R_D|^3}{\left|(1 + j \frac{\omega_p}{\omega_p})^3\right|} = \frac{(g_m R_D)^3}{(\sqrt{1+1})^3} = \frac{(g_m R_D)^3}{\sqrt{8}}$$

$$\begin{aligned} \Rightarrow 20 \log |H| \Big|_{\omega=\omega_p} &= 20 \log (g_m R_D)^3 - 20 \log \sqrt{8} \\ &\cong 20 \log (g_m R_D)^3 - (9 \text{ dB}) \end{aligned}$$

$\therefore |H|$  falls by 9 dB due to the three coincident poles.

12.63 We'll drop the negative sign in  $H(s)$  as done in Example 12.38.

$$H(s) = \frac{(g_m R_D)^3}{\left(1 + \frac{s}{\omega_p}\right)^3}$$

$$\angle H(j\omega) = -3 \tan^{-1} \left( \frac{\omega}{\omega_p} \right)$$


$$-3 \tan^{-1} \left( \frac{\omega_{PX}}{\omega_p} \right) = -180$$

$$\omega_{PX} = \sqrt{3}\omega_p$$

$$|KH(j\omega_{PX})| = 0.1 \frac{(g_m R_D)^3}{\left[ \sqrt{1 + \left( \frac{\omega_{PX}}{\omega_p} \right)^2} \right]^3} < 1$$



$$g_m R_D < \sqrt[3]{80} = \boxed{4.31}$$

64.

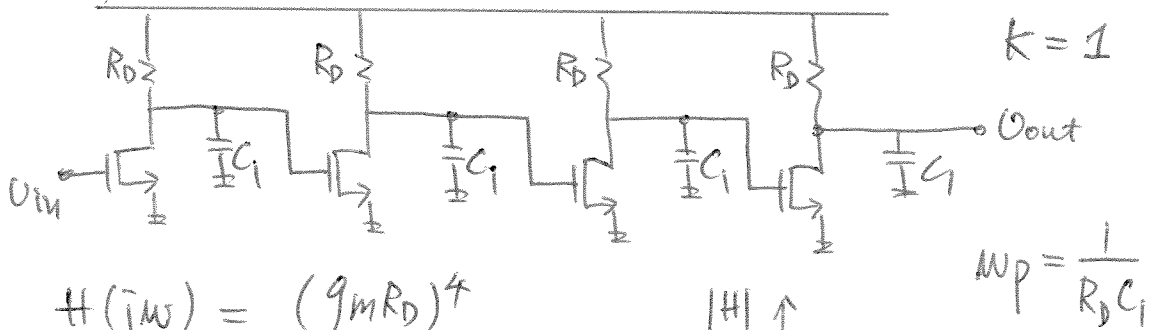

$$H(j\omega) = \frac{(g_m R_D)^4}{(1 + j \frac{\omega}{\omega_p})^4}$$
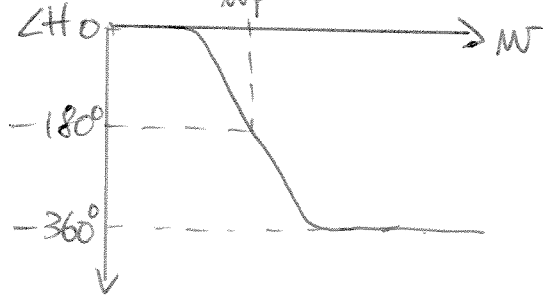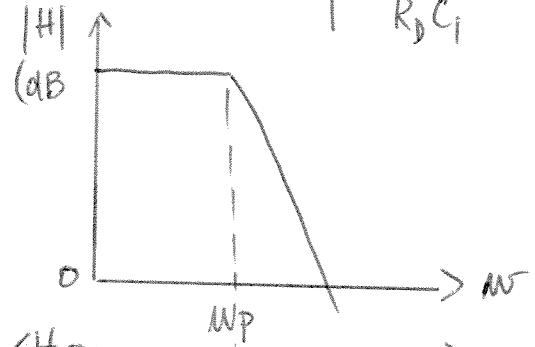
$$\angle H = -4 \tan^{-1} \left( \frac{\omega}{\omega_p} \right)$$



- To guarantee stability,

$$|KH| < 1 \text{ when } \angle H = -180^\circ$$

$$\angle H = -180^\circ = -4 \tan^{-1} \left( \frac{\omega}{\omega_p} \right) \Rightarrow \omega = \omega_p$$

$$|KH| \Big|_{\omega=\omega_p} = \frac{(g_m R_D)^4}{(\sqrt{1+1})^4} < 1$$

$$\Rightarrow g_m R_D < \sqrt{2}$$

This four-pole system implies a lower upper-limit ( $=\sqrt{2}$ ) on  $g_m R_D$ , which makes sense since  $|H|$  drops faster here.

12.65

$$\begin{aligned}H(s) &= \frac{A_0}{1 + \frac{s}{\omega_0}} \\|KH(\omega_{GX})| &= \frac{A_0}{\sqrt{1 + \left(\frac{\omega_{GX}}{\omega_0}\right)^2}} = 1 \\ \omega_{GX} &= \omega_0 \sqrt{A_0^2 - 1} \\ \angle H(j\omega_{GX}) &= -\tan^{-1}\left(\frac{\omega_{GX}}{\omega_0}\right) \\ &= -\tan^{-1}\left(\frac{\omega_0 \sqrt{A_0^2 - 1}}{\omega_0}\right) \\ &= -\tan^{-1}\left(\sqrt{A_0^2 - 1}\right) \\ \text{Phase Margin} &= \angle H(j\omega_{GX}) + 180^\circ \\ &= \boxed{180^\circ - \tan^{-1}\left(\sqrt{A_0^2 - 1}\right)}\end{aligned}$$

The phase margin can be anything from  $90^\circ$  to  $180^\circ$ , depending on the value of  $A_0$  (smaller  $A_0$  means larger phase margin).

$$\begin{aligned}
 H(s) &= \frac{A_0}{1 + \frac{s}{\omega_0}} \\
 |KH(\omega_{GX})| &= 0.5 \frac{A_0}{\sqrt{1 + \left(\frac{\omega_{GX}}{\omega_0}\right)^2}} = 1 \\
 \omega_{GX} &= \omega_0 \sqrt{\left(\frac{A_0}{2}\right)^2 - 1} \\
 \angle H(j\omega_{GX}) &= -\tan^{-1}\left(\frac{\omega_{GX}}{\omega_0}\right) \\
 &= -\tan^{-1}\left(\frac{\omega_0 \sqrt{\left(\frac{A_0}{2}\right)^2 - 1}}{\omega_0}\right) \\
 &= -\tan^{-1}\left(\sqrt{\left(\frac{A_0}{2}\right)^2 - 1}\right) \\
 \text{Phase Margin} &= \angle H(j\omega_{GX}) + 180^\circ \\
 &= \boxed{180^\circ - \tan^{-1}\left(\sqrt{\left(\frac{A_0}{2}\right)^2 - 1}\right)}
 \end{aligned}$$

The phase margin can be anything from  $90^\circ$  to  $180^\circ$ , depending on the value of  $A_0$  (smaller  $A_0$  means larger phase margin).

67. All three scenarios will become stable eventually (depending on how far  $w_{ax}$  is from  $w_{px}$ , &  $w_{qx} < w_{px}$ .)

12.68 With a factor of  $K = 0.5$ , the magnitude Bode plot of  $KH$  will simply be the magnitude plot of  $H$  shifted down by 6 dB (since  $20 \log 0.5 = -6$  dB). Since the slope of the magnitude plot between  $\omega_{p1}$  and  $\omega_{p2}$  is  $-20$  dB/dec, this means that  $\omega_{GX}$  will be shifted left by  $\frac{6}{20} = 0.3$  decades, or a factor of  $10^{0.3} = 2$ .

Thus, the new value of  $\omega_{GX}$ , which we'll call  $\omega'_{GX}$ , is  $\omega'_{GX} = \frac{\omega_{GX}}{2} = \frac{\omega_{p2}}{2}$ .


Now, we need to find  $\angle H(j\omega_{GX})$ .

$$\begin{aligned} \angle H(j\omega) &= -\tan^{-1}\left(\frac{\omega}{\omega_{p1}}\right) - \tan^{-1}\left(\frac{\omega}{\omega_{p2}}\right) \\ \angle H(j\omega_{GX}) &= \angle H\left(j\frac{\omega_{p2}}{2}\right) \\ &= -\tan^{-1}\left(\frac{\omega_{p2}}{2\omega_{p1}}\right) - \tan^{-1}\left(\frac{\omega_{GX}}{2\omega_{p2}}\right) \\ &= -90^\circ - \tan^{-1}(0.5) \\ &= -116^\circ \\ \text{Phase Margin} &= 180^\circ + \angle H(j\omega_{GX}) \\ &= 180^\circ - 116^\circ \\ &= \boxed{63^\circ} \end{aligned}$$




69. When  $k$  drops by a factor of 2, the phase margin improves. This is because a lower  $k$  corresponds to shifting the amplitude part of  $kH$  down by 6 dB. (The phase  $\angle kH$  remains unchanged, since phase is only dependent on pole location and is independent of amplitude of  $kH$ .)

Thus, the gain  $|kH|$  drops to 0 dB at a lower frequency. This results in a larger phase margin.

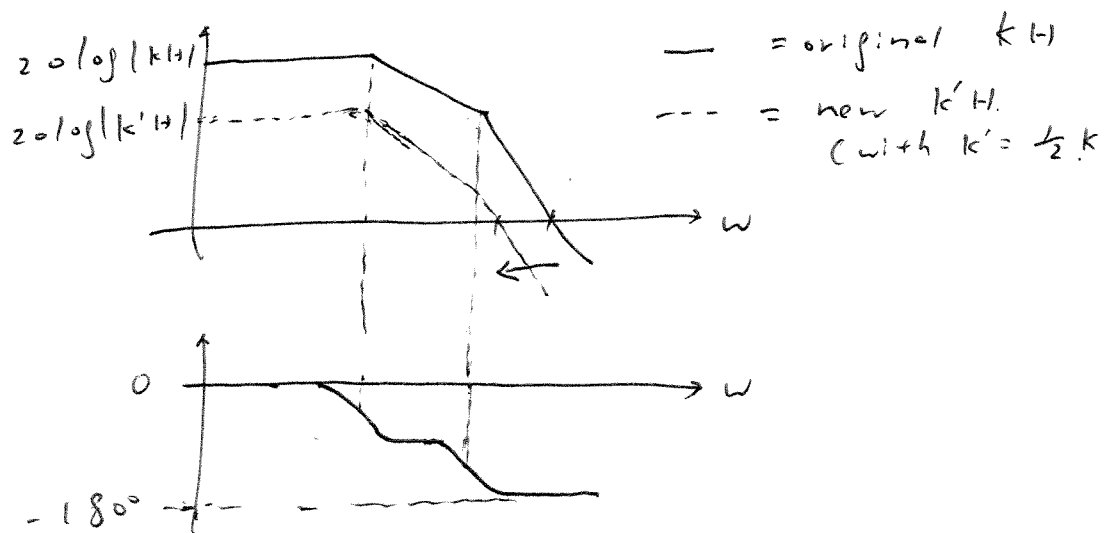

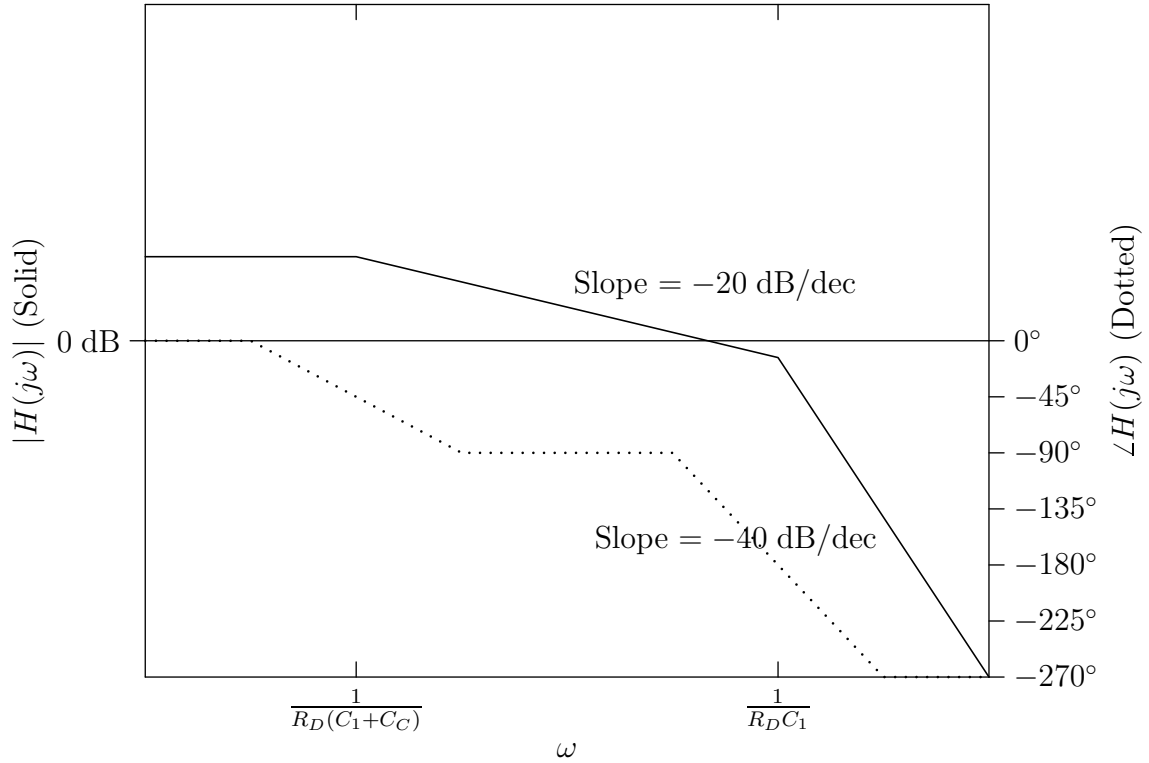12.70 The compensation capacitor allows us to push the pole associated with that node to a lower frequency (while the other poles do not change). This will cause the gain to start dropping sooner, so that  $\omega_{GX}$  decreases. By adjusting  $C_C$  properly, we can reduce  $\omega_{GX}$  enough so that the phase is at  $-135^\circ$  at  $\omega_{GX}$ . This results in the following Bode plots:



12.71

$$\begin{aligned}A_{OL} &\approx g_{m1} (r_{o2} \parallel r_{o4}) \\ &= g_{m1} \left( \frac{2}{\lambda_n I_{SS}} \parallel \frac{2}{\lambda_p I_{SS}} \right) \\ &= 50\end{aligned}$$

$$g_{m1} = 3.75 \text{ mS}$$

$$K = \frac{R_2}{R_1 + R_2} = \frac{R_2}{10 (r_{o2} \parallel r_{o4})}$$

$$\begin{aligned}\frac{v_{out}}{v_{in}} &= \frac{g_{m1} (r_{o2} \parallel r_{o4})}{1 + g_{m1} \frac{R_2}{10 (r_{o2} \parallel r_{o4})} (r_{o2} \parallel r_{o4})} \\ &= 4\end{aligned}$$

$$R_2 = \boxed{30.667 \text{ k}\Omega}$$

$$R_1 = \boxed{102.667 \text{ k}\Omega}$$

72. Open loop gain,  $A_0 = \beta_m R_D$   
(assuming  $R_1 + R_2$  is very large.)

$$\text{i.e. } \beta_m R_D = 10$$

$$\begin{aligned} \text{Closed-loop gain} &= \frac{\beta_m R_D}{1 + \left(\frac{R_2}{R_1 + R_2}\right) \beta_m R_D} \\ &= 2 \end{aligned}$$

$$\therefore \frac{10}{1 + \left(\frac{R_2}{R_1 + R_2}\right) \times 10} = 2$$

$$\frac{R_2}{R_1 + R_2} = 0.4$$

$$\begin{aligned} \text{Closed-loop input impedance} &= \frac{1}{\beta_m} \left[ 1 + \frac{R_2}{R_1 + R_2} \times 10 \right] \\ &= 50 \Omega. \end{aligned}$$

$$\therefore \frac{1}{\beta_m} \times 5 = 50$$

$$\beta_m = 0.15 //$$

$$\therefore R_D = 100 \Omega //$$

$$\begin{aligned} \therefore R_1 + R_2 &= 10 \times 100 \Omega \\ &= 1 \text{ k}\Omega. \end{aligned}$$

$$\therefore R_2 = 400 \Omega //$$

$$R_1 = 600 \Omega //$$

$$A_{OL} = -g_{m2}R_{D1}R_{D2} = -10 \text{ k}\Omega$$

$$K = -\frac{1}{R_F}$$

$$\begin{aligned} \frac{v_{out}}{i_{in}} &= -\frac{g_{m2}R_{D1}R_{D2}}{1 + \frac{g_{m2}R_{D1}R_{D2}}{R_F}} \\ &= -\frac{10 \text{ k}\Omega}{1 + \frac{10 \text{ k}\Omega}{R_F}} \\ &= -1 \text{ k}\Omega \end{aligned}$$

$$R_F = \boxed{1.111 \text{ k}\Omega}$$

$$R_{in,open} = \frac{1}{g_{m1}}$$

$$\begin{aligned} R_{in,closed} &= \frac{1}{g_{m1}} \left( 1 + \frac{g_{m2}R_{D1}R_{D2}}{R_F} \right)^{-1} \\ &= \frac{1}{g_{m1}} \left( 1 + \frac{10 \text{ k}\Omega}{1.111 \text{ k}\Omega} \right)^{-1} \\ &= 50 \text{ }\Omega \end{aligned}$$

$$g_{m1} = \boxed{2 \text{ mS}}$$

$$R_{out,open} = R_{D2}$$

$$\begin{aligned} R_{out,closed} &= \frac{R_{D2}}{1 + \frac{g_{m2}R_{D1}R_{D2}}{R_F}} \\ &= \frac{R_{D2}}{1 + \frac{10 \text{ k}\Omega}{1.111 \text{ k}\Omega}} \\ &= 200 \text{ }\Omega \end{aligned}$$

$$R_{D2} = \boxed{2 \text{ k}\Omega}$$

$$\begin{aligned} g_{m2} &= \frac{A_{OL}}{R_{D1}R_{D2}} \\ &= \boxed{5 \text{ mS}} \end{aligned}$$

74. Assuming  $R_F$  is very large,

$$\text{open-loop gain} = R_D (f_{m2} R_C)$$

$$= 10 \text{ k}\Omega$$

$$\text{closed-loop gain} = \frac{10 \text{ k}\Omega}{1 + \frac{10 \text{ k}\Omega}{R_F}}$$

$$= 1 \text{ k}\Omega.$$

$$\therefore R_F = 1.11 \text{ k}\Omega //$$

$$\text{closed-loop input impedance} = \frac{1}{f_{m1}} (1 + \beta)^{-1} = 50 \Omega.$$

$$f_{m1} = 2 \text{ mS} //$$

$$\text{closed-loop output impedance} = \frac{R_C}{10}$$

$$\therefore R_C = 2000 \Omega //$$

$$R_D = 1 \text{ k}\Omega.$$

$$\therefore f_{m2} = 5 \text{ mS} //$$

$$75. \text{ a) open-loop gain} = R_c (f_m R_m)$$

$$= 20 \text{ k}\Omega.$$

$$f_m = \frac{I}{V_T}$$

$$\therefore f_m = \frac{1 \text{ mA}}{26 \text{ mV}} = 38.5 \text{ ms}$$

$$\therefore R_c R_m = \frac{20 \text{ k}\Omega}{38.5 \text{ ms}}$$

$$\text{open-loop output impedance} = R_m \quad (-: V_o = \infty)$$

$$\therefore R_m = 500 \Omega //$$

$$R_c = 1040 \Omega //$$

---

$$\text{b) closed-loop gain} = \frac{20 \text{ k}\Omega}{1 + \frac{20 \text{ k}\Omega}{R_F}}$$

$$= 1 \text{ k}\Omega$$

$$\therefore R_F = 1053 \Omega //$$

$$\text{c) closed-loop input impedance} = \frac{\frac{1}{38.5 \text{ ms}}}{1 + \frac{20 \text{ k}}{1053}}$$

$$= 1.30 \Omega //$$

$$\text{closed-loop output impedance} \approx (500) \left( \frac{1}{20} \right)$$

$$= 25 \Omega //$$

12.76 See Problem 44 for derivations of the following expressions.

$$\begin{aligned}
 A_{OL} &= \frac{g_{m1}g_{m2}R_{D1}(R_1 + R_2)}{1 + g_{m1}(R_1 \parallel R_2)} = 20 \\
 \frac{v_{out}}{v_{in}} &= \frac{\frac{g_{m1}g_{m2}R_{D1}(R_1+R_2)}{1+g_{m1}(R_1 \parallel R_2)}}{1 + \frac{g_{m1}g_{m2}R_{D1}R_2}{1+g_{m1}(R_1 \parallel R_2)}} \\
 &= \frac{20}{1 + 20\left(\frac{R_2}{R_1+R_2}\right)} \\
 &= 4 \\
 \frac{R_2}{R_1 + R_2} &= 0.2 \\
 R_{out,open} &= R_1 + R_2 = 2 \text{ k}\Omega \\
 R_2 &= \boxed{400 \Omega} \\
 R_1 &= \boxed{1.6 \text{ k}\Omega}
 \end{aligned}$$

Lacking any additional constraints, we can pick any  $g_{m1}$ ,  $g_{m2}$ , and  $R_{D1}$  so that  $A_{OL} = 20$ . Let's pick  $g_{m1} = g_{m2} = \boxed{2 \text{ mS}}$ . This gives us  $R_{D1} = \boxed{4.1 \text{ k}\Omega}$ .

If we are also required to minimize the power consumption of the amplifier, we need to minimize the current consumption of each stage. This requires minimizing  $g_{m1}$  and  $g_{m2}$  and maximizing  $R_{D1}$  while keeping all transistors in saturation.



12.77 See Problem 46 for derivations of the following expressions.

$$A_{OL} = \frac{g_{m1}g_{m2} \left( \frac{1}{g_{m2}} + \frac{R_1 \parallel R_2}{\beta_2 + 1} \right)}{1 + g_{m1} \left( \frac{1}{g_{m2}} + \frac{R_1 \parallel R_2}{\beta_2 + 1} \right)} (R_1 + R_2) = 2$$

$$g_{m1} = g_{m2} = \frac{I_{SS}}{2V_T} = \frac{1}{52} \text{ S}$$

$$K = \frac{R_2}{R_1 + R_2}$$

$$R_{out,closed} = \frac{R_1 + R_2}{1 + KA_{OL}}$$

$$= \frac{R_1 + R_2}{1 + \frac{2R_2}{R_1 + R_2}}$$

$$= \frac{(R_1 + R_2)^2}{1 + 3R_2}$$

Looking at this expression for  $R_{out,closed}$ , we can see that it will be minimized for very small values of  $R_1$ . This will force  $R_2$  to be larger in order to meet the required  $A_{OL}$ , but since  $R_{out}$  depends more strongly on  $R_1$  than  $R_2$ , we should focus on minimizing  $R_1$ .

In fact, we can actually set  $R_1 = \boxed{0}$ . We can then solve the  $A_{OL}$  equation to find  $R_2 = \boxed{208 \Omega}$ , which means  $R_{out} = 69.33 \Omega$ .

12.78 See Problem 50 for derivations of the following expressions. Assume  $\beta = 100$ .

$$A_{OL} = -\frac{g_{m1}g_{m2}(R_F \parallel r_{\pi1})R_F\{R_C \parallel [r_{\pi2} + (1 + \beta)R_F]\}}{1 + g_{m2}R_F}$$

$$\frac{v_{out}}{i_{in}} = \frac{A_{OL}}{1 - \frac{A_{OL}}{R_F}} = -1 \text{ k}\Omega$$

$$R_{in} = \frac{R_F \parallel r_{\pi1}}{1 - \frac{A_{OL}}{R_F}} = 50 \Omega$$

$$g_{m1} = g_{m2} = \frac{1}{26} \Omega$$

$$r_{\pi1} = r_{\pi2} = \frac{\beta}{g_m} = 2.6 \text{ k}\Omega$$

We have two equations ( $\frac{v_{out}}{i_{in}} = -1 \text{ k}\Omega$  and  $R_{in} = 50 \Omega$ ) and two unknowns ( $R_F$  and  $A_{OL}$ ). Solving, we get:

$$R_F = \boxed{1.071 \text{ k}\Omega}$$

$$A_{OL} = 15167$$


$$R_C = \boxed{535.2 \Omega}$$

$$1. \quad A_v = \frac{g_{m1} R_L}{1 + g_{m1} R_L}$$

$$(a) \quad 0.8 = \frac{g_{m1} (85\Omega)}{1 + g_{m1} (85\Omega)}$$

$$\Rightarrow g_{m1} = 0.5 = \frac{I_c}{V_T} = \frac{I_1}{V_T}$$

$$\therefore I_1 = 13 \text{ mA}$$

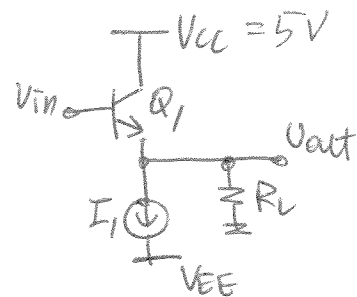

$$P_{\text{LOAD}} = 0.5 \text{ W}$$

$$R_L = 85\Omega$$

(Assume  $V_{\text{out}}$

biased at

$$V_{\text{BE(ON)}} \approx 800 \text{ mV}$$

(b) When  $V_{\text{in}} = V_p = V_{\text{cc}}$ ,  $V_{\text{out}} \approx V_{\text{cc}} - V_{\text{BE(ON)}}$

$$I_{c1} = I_1 + \frac{V_{\text{out}}}{R_L} \Rightarrow I_{c1} = I_1 + \frac{5 - 0.8}{85} \approx 0.54 \text{ A}$$

$$\Rightarrow g_{m1} = \frac{I_{c1}}{V_T} = \frac{0.54 \text{ A}}{0.026 \text{ V}} = 20.8 \text{ S}$$


$$\Rightarrow A_v \Big|_{V_{\text{in}}=V_p} = \frac{g_{m1} R_L}{1 + g_{m1} R_L} = \frac{(20.8 \text{ S})(85\Omega)}{1 + (20.8 \text{ S})(85\Omega)} \approx 0.99$$

2.

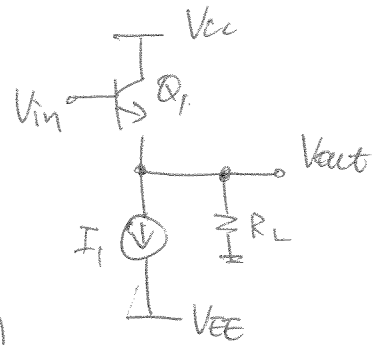(a)  $I_1 = V_p / R_L$        $V_p \gg V_T$

$$A_v = \frac{I_c R_L}{I_c R_L + V_T}$$

$$= \frac{\frac{I_c}{I_1} V_p}{\frac{I_c}{I_1} V_p + V_T} = \frac{V_p}{V_p + V_T} \quad (\approx 1)$$



(b) When  $V_{out} = V_p$ ,  $I_{c1} = I_1 + \frac{V_{out}}{R_L} = \frac{V_p}{R_L} + \frac{V_p}{R_L}$   
 $= \frac{2V_p}{R_L}$


$$\therefore A_v = \frac{\left(\frac{2V_p}{R_L}\right) R_L}{\left(\frac{2V_p}{R_L}\right) R_L + V_T} = \frac{2V_p}{2V_p + V_T} \quad \left(\approx \frac{2V_p}{2V_p} = 1\right)$$

$$\Delta A_v = \frac{\frac{2V_p}{2V_p + V_T} - \frac{V_p}{V_p + V_T}}{\frac{V_p}{V_p + V_T}} = \frac{V_T}{2V_p + V_T} \quad \left(\approx \frac{V_T}{V_p}\right)$$

3.  $A_v = 0.7$        $R_L = 4\Omega$

$Q_1$  shuts off when:

$$I_1 = \frac{V_P}{R_L}$$

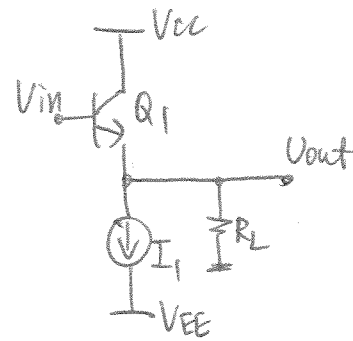

• Suppose  $V_{out} = V_P \sin \omega t$ .       $(\omega = \frac{2\pi}{T})$

$$P_{R_L, AVG} = \frac{1}{T} \int_0^T \frac{(V_{out})^2}{R_L} dt = \frac{1}{T} \int_0^T \frac{V_P^2 \sin^2 \omega t}{R_L} dt$$


$$\therefore \text{Largest power (average)} = \frac{1}{2} \frac{(I_1 R_L)^2}{R_L} = \frac{1}{2} V_P^2 / R_L$$

$$A_v = 0.7 = \frac{g_{m1} R_L}{1 + g_{m1} R_L} \Rightarrow g_{m1} = \frac{A_v}{(1 - A_v) R_L} = \frac{0.7}{(1 - 0.7)(4)} = 0.58 \text{ S}$$

$$\Rightarrow I_{C1} (= I_1) = g_{m1} V_T = 0.015 \text{ A}$$

$$\therefore P_{AV, MAX} = \frac{1}{2} I_1^2 R_L = \frac{1}{2} (0.015 \text{ A})^2 (4\Omega) = 0.45 \text{ W}$$
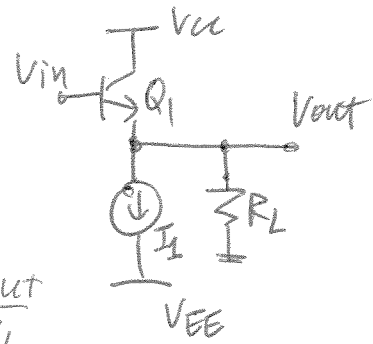
$$4. A_v = \frac{g_{m1} R_L}{1 + g_{m1} R_L} \quad (g_m = \frac{I_{C1}}{V_T})$$



- $Q_1$  shuts off when  $I_1 = -\frac{V_{out}}{R_L}$   
 $\Rightarrow V_p = I_1 \times R_L$

$$g_{m1} = \frac{A_v}{(1 - A_v) R_L} = \frac{I_{C1}}{V_T} \Rightarrow I_{C1} = \frac{V_T A_v}{R_L (1 - A_v)} (= I_1)$$

- Power delivered to  $R_L$ :

$$P_{R_L} = \frac{1}{T} \int_0^T \frac{V_{out}^2}{R_L} dt = \frac{1}{T} \int_0^T \frac{V_p^2 \sin^2 \omega t}{R_L} dt$$

$$= \frac{1}{2} \frac{V_p^2}{R_L}$$

$$\therefore \text{Maximum power} = \frac{1}{2} \left( \frac{I_1 R_L}{R_L} \right)^2$$

$$= \frac{1}{2} \left[ \frac{V_T A_v}{(1 - A_v)} \right]^2 \cdot \frac{1}{R_L}$$

5.

(a) By KCL,

$$I_1 = I_{S1} \cdot \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) + \frac{V_{cc} - V_{out}}{R_L}$$


$$\Rightarrow V_{in} = V_{out} + V_T \ln\left(\frac{I_1}{I_{S1}} - \frac{V_{cc} - V_{out}}{I_{S1} R_L}\right)$$

$$= 0 \quad (\text{X}) \text{—no solution}$$

$$\therefore V_{out} = 5 - I_1 R_L = 4.84 \text{ V}$$

(i.e.  $Q_1$  is off.)

Assume  $V_{cc} = 5 \text{ V}$

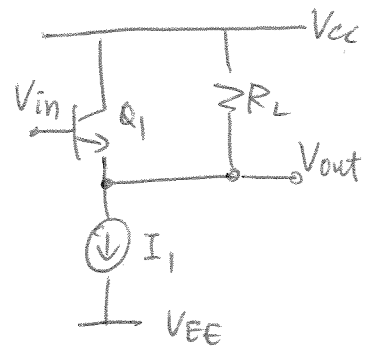

$$I_{S1} = 5 \cdot 10^{-17} \text{ A}$$

$$R_L = 8 \Omega$$

$$I_1 = 20 \text{ mA}$$

$$(b) (0.01)I_1 = I_1 - \frac{V_{cc} - V_{out}}{R_L}$$

$$\Rightarrow V_{out} = 4.84 \text{ V}$$

$$I_{C1} = (0.01)I_1 = I_{S1} \exp\left(\frac{V_{in} - V_{out}}{V_T}\right)$$

$$\Rightarrow V_{in} = V_{out} + V_T \ln\left(0.01 \frac{I_1}{I_{S1}}\right)$$

$$= 4.84 + (0.026) \ln\left(0.01 \frac{20 \text{ mA}}{5 \cdot 10^{-17} \text{ A}}\right)$$

$$\approx 5.59 \text{ V}$$

(exceeds  $V_{cc}$ )

6.

(a) Calculate  $V_{BE}$  for

$V_{in} = 1V:$

$$I_{C1} = I_1 + \frac{V_{out}}{R_L}$$

$$\Rightarrow I_{S1} \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) = I_1 + \frac{V_{out}}{R_L}$$

Solving by iteration for  $V_{out}$  gives:

$$V_{out} \approx 0.113V$$

$$\therefore V_{BE} \Big|_{V_{in}=1V} = V_{in} - V_{out} = 1 - 0.113 = 0.887V$$


$V_{in} = -1V:$

$$I_{C1} = I_1 + -\frac{V_{out}}{R_L} \Rightarrow I_{S1} \exp\left(\frac{V_{in} - V_{out}}{V_T}\right) = I_1 - \frac{V_{out}}{R_L}$$

Solving by iteration for  $V_{out}$  gives:

$$V_{out} \approx -1.95V$$

$$\therefore V_{BE} \Big|_{V_{in}=-1V} = V_{in} - V_{out} = -1 - (-1.95) = 0.95V$$

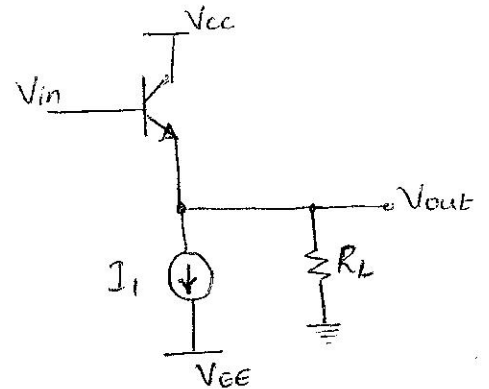


$$I_{S1} = 6 \cdot 10^{-17} A$$

$$R_L = 8 \Omega$$

$$I_1 = 25 mA$$

$$V_p = 1V$$

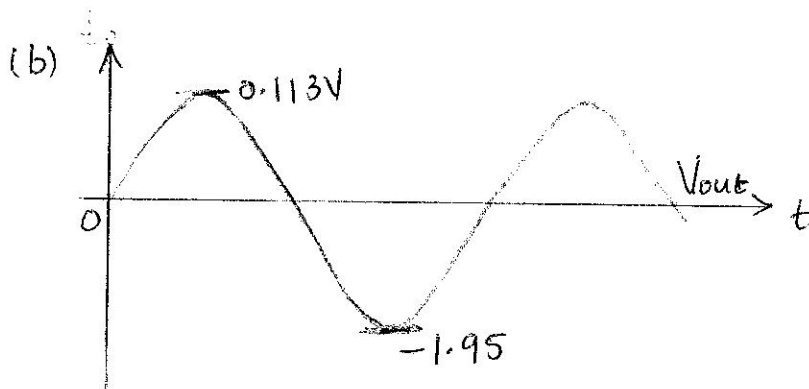



7. Determine  $V_p$  such that

$$V_{BE} \Big|_{V_{in}=+V_p} - V_{BE} \Big|_{V_{in}=-V_p} = 10 \text{ mV}$$

$$\Rightarrow (V_p^+ - V_{out,+}) - (V_p^- - V_{out,-}) = 10 \text{ mV}$$

$$I_S \exp\left(\frac{V_p^+ - V_{out,+}}{V_T}\right) = I_1 + \frac{V_{out,+}}{R_L} \quad \text{--- (1)}$$


$$I_S \exp\left(\frac{V_p^- - V_{out,-}}{V_T}\right) = I_1 - \frac{V_{out,-}}{R_L} \quad \text{--- (2)}$$

Iterate (1) & (2). This gives:

$$V_p \approx 0.7 \text{ V}$$

$$\Rightarrow \text{Nonlinearity} = \frac{10 \text{ mV}}{0.7 \times 2} \approx 0.007.$$

8.

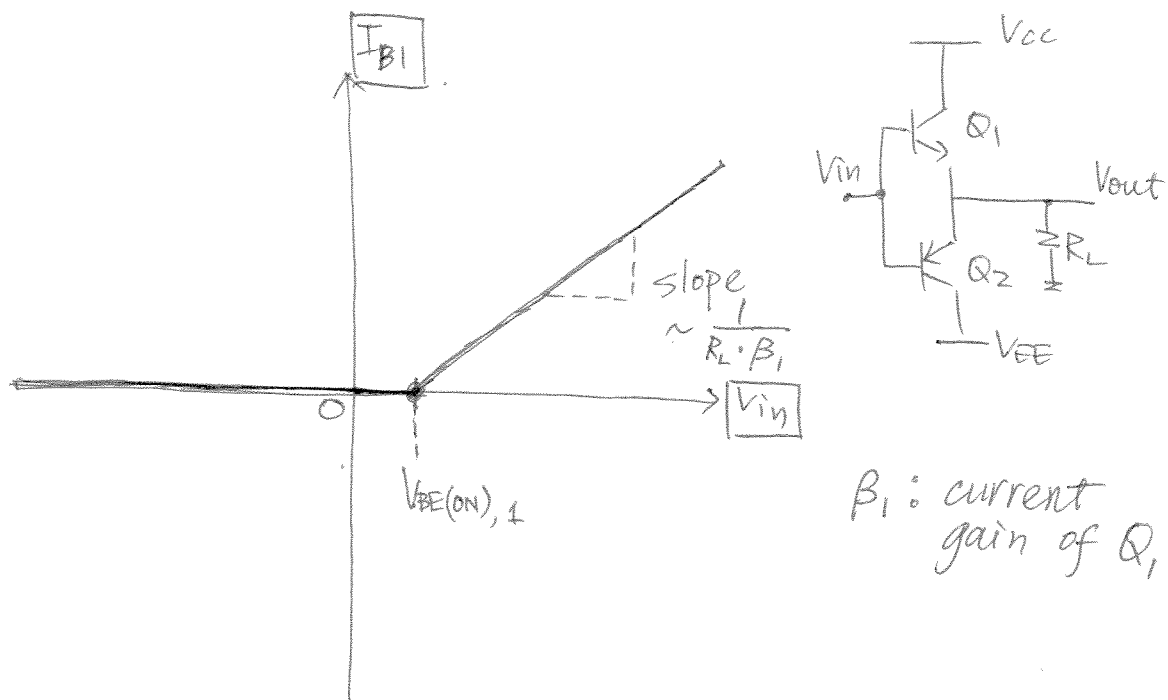

•  $Q_1$  is on whenever  $V_{in} \geq V_{BE(ON),1}$ . In this region,

$$V_{out} = V_{in} - V_{BE(ON),1}$$

$$I_{C1} = \frac{V_{out}}{R_L}$$

$$\therefore I_{B1} = \frac{I_{C1}}{\beta} = \frac{V_{out}}{\beta R_L} = \frac{V_{in} - V_{BE(ON),1}}{\beta R_L}$$

9.

(a) To guarantee  $Q_1$  on,

$$\bullet V_{out} \approx V_{in} - V_{BE(ON)1} = -800 \text{ mV}$$


$$\Rightarrow I_{C1} = I_1 + \frac{V_{out}}{R_L} \quad (Q_2 \text{ is off})$$

$$\bullet I_{C1} \geq 0 \Rightarrow I_1 + \frac{V_{out}}{R_L} \geq 0$$

$$\Rightarrow I_1 + \frac{-800 \text{ mV}}{R_L} \geq 0$$

$$\therefore I_1 R_L \geq 800 \text{ mV}$$

————— ①

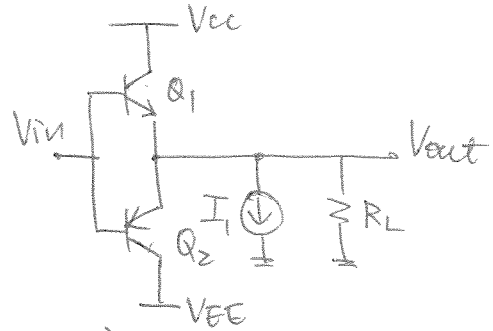

$$I_{S2} = 6 \cdot 10^{-17} \text{ A}$$

$$R_L = 8 \Omega$$

(b) When  $Q_2$  turns on,

$$-\frac{V_{out}}{R_L} - I_1 = I_{C2}$$

$$\Rightarrow -\frac{V_{out}}{R_L} - \left(\frac{800 \text{ mV}}{R_L}\right) = I_{S2} \exp\left(\frac{V_{BE2}}{V_T}\right)$$


$$\begin{aligned} \Rightarrow V_{out} &= -R_L I_{S2} \cdot \exp\left(\frac{V_{BE2}}{V_T}\right) - 0.8 \\ &= -(8 \Omega)(6 \cdot 10^{-17} \text{ A}) \exp\left(\frac{0.8}{0.026}\right) - 0.8 \\ &\approx -0.81 \text{ V} \end{aligned}$$

$$\therefore V_{in} = V_{out} - |V_{BE(ON)2}| = -0.81 - 0.8 = -1.61 \text{ V}$$

10. Consider two scenarios:

- In gain regions ( $|V_{in}| \geq |V_{BE(on)}|$ ),  $V_{out}$  tracks  $V_{in}$ .
- In dead zone, both transistors shut off.

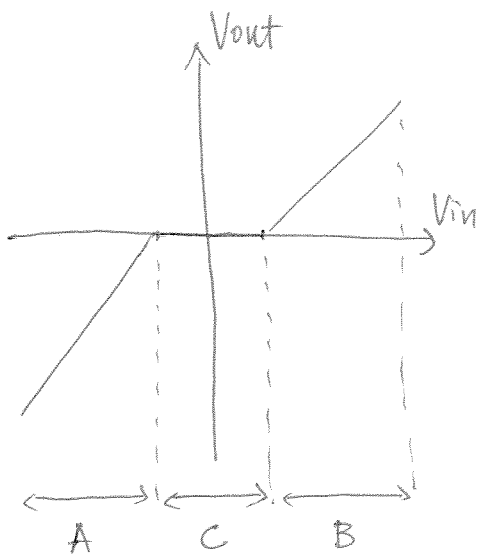In both cases,  $V_{out}$  has an important role. Current source  $I_1$  affects the input/output characteristic by modulating  $V_{out}$ :



I/O characteristic of push-pull stage.

Consider region A:

$$I_{C2} + I_1 = \frac{-V_{out}}{R_L}$$

$\therefore I_1 \uparrow \downarrow \Rightarrow |V_{BE2}| = |V_{out} - V_{in}|$  stays relatively constant.

( $Q_2$  absorbs/sinks all the currents from  $I_1$  in order to have the same  $|V_{BE2}|$ )

Consider region B:

$$I_{C1} = I_1 + \frac{V_{out}}{R_L}$$

$\therefore I_1 \uparrow \downarrow \Rightarrow |V_{BE1}| = |V_{in} - V_{out}|$  stays relatively constant.

( $Q_1$  provides/sources current to  $I_1$  in order to have  $|V_{BE1}|$  constant.)

Consider region C: (Dead zone).

$$I_1 = -\frac{V_{out}}{R_L} \quad (\text{Both transistors off})$$



$$\therefore I_1 \uparrow \Rightarrow V_{out} \downarrow$$

$$I_1 \downarrow \Rightarrow V_{out} \uparrow$$

i.e. In the dead zone,  $V_{out}$  is predominantly controlled by  $I_1$ . One can use this to control  $V_{out}$  and effectively shift the region of dead zone.

( $\because V_{out}/v_{in=0} \neq 0$  anymore)

11.

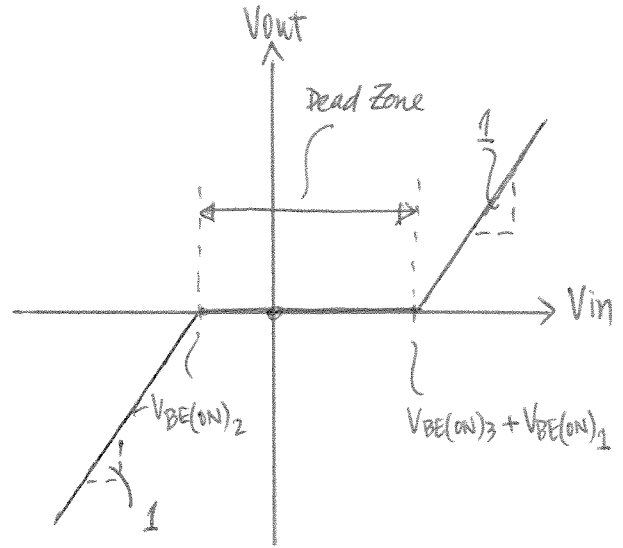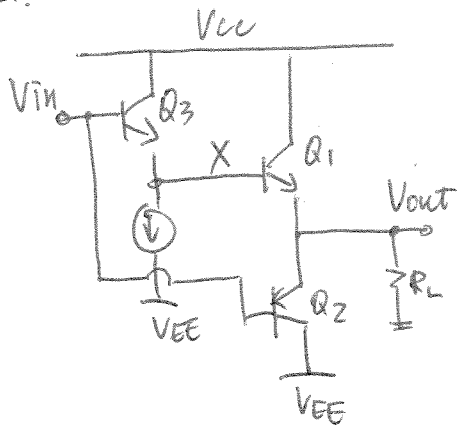



### Analysis

Dead Zone

$$= |V_{BE(ON)2}| + V_{BE(ON)3} + V_{BE(ON)1}$$

- $(0 < V_{in} < V_{BE(ON)3} + V_{BE(ON)1})$ :  
 $Q_1$  is OFF ( $V_{in} < V_{BE(ON)1}$ )  
 $Q_2$  is OFF ( $V_{BE2}$  reverse-biased) }  $\Rightarrow V_{out} = 0$
- $(-|V_{BE(ON)2}| < V_{in} < 0)$ :  
 $Q_1, Q_2$  OFF. }  $V_{out} = 0$
- $(V_{BE(ON)3} + V_{BE(ON)1} < V_{in} < V_{cc})$   
 $Q_1$  ON }  $V_{out} = V_{in} - V_{BE(ON)3} - V_{BE(ON)1}$   
 $Q_2$  OFF }
- $(-|V_{EE}| < V_{in} < -|V_{BE(ON)2}|)$   
 $Q_2$  ON }  $V_{out} = V_{in} + |V_{BE(ON)2}|$   
 $Q_1$  OFF }

12.

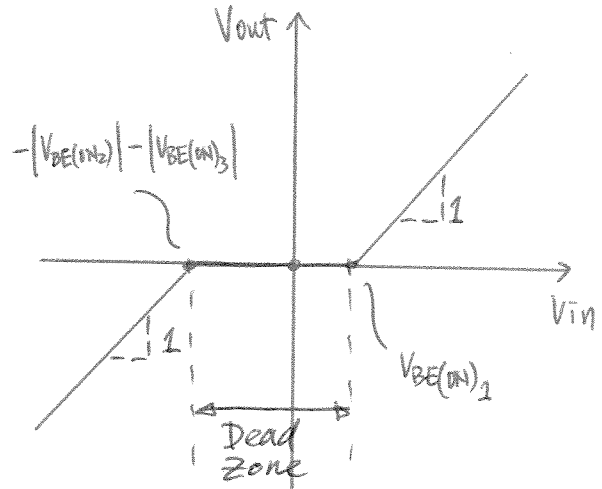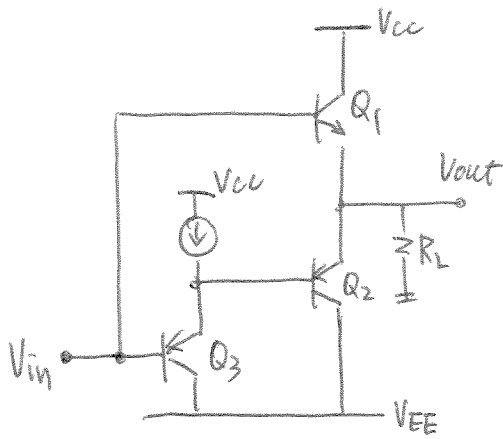

$$\underline{-V_{EE} < V_{in} < -(|V_{BE(on)2}| + |V_{BE(on)3}|) :}$$

$$\Rightarrow \left. \begin{array}{l} Q_2, Q_3 \text{ ON} \\ Q_1 \text{ OFF} \end{array} \right\} V_{out} = V_{in} + |V_{BE(on)3}| + |V_{BE(on)2}|$$

$$\underline{-(|V_{BE(on)2}| + |V_{BE(on)3}|) < V_{in} < V_{BE(on)1} :}$$

$$\Rightarrow Q_1, Q_2 \text{ OFF} \Rightarrow V_{out} \cong 0$$

$$\underline{V_{BE(on)1} < V_{in} < V_{CC} :}$$

$$\Rightarrow \left. \begin{array}{l} Q_1 \text{ ON} \\ Q_2, Q_3 \text{ OFF} \end{array} \right\} V_{out} = V_{in} - V_{BE(on)1}$$

$$\text{Dead Zone} = V_{BE(on)1} + |V_{BE(on)2}| + |V_{BE(on)3}|$$

13.

(a)

$$\underline{-|V_{EE}| < V_{in} < -|V_{t,p}| :}$$


$$\Rightarrow \left. \begin{array}{l} M_1 \text{ OFF} \\ M_2 \text{ ON} \\ \text{(saturation)} \end{array} \right\} V_{out} = V_{in} + V_{sg,2}$$

$$\underline{V_{cc} > V_{in} > V_{t,n} :}$$

$$\Rightarrow \left. \begin{array}{l} M_1 \text{ ON} \\ M_2 \text{ OFF} \end{array} \right\} V_{out} = V_{in} - V_{gs,1}$$

$$\underline{-|V_{t,p}| < V_{in} < V_{t,n} :}$$
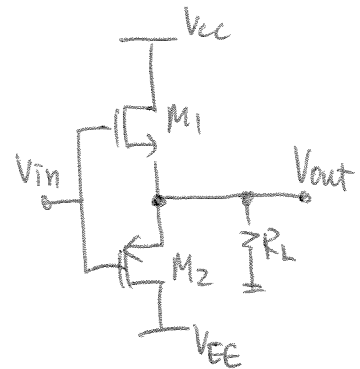
$$M_1, M_2 \text{ OFF} \Rightarrow V_{out} = 0$$




Ignore body effect.

$\Rightarrow M_1$  &  $M_2$  can never on at the same time.

FOR MOS,  $I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{gs} - |V_t|)^2$  - saturation region.

$$\Rightarrow M_1 \text{ ON: } \frac{V_{out}}{R_L} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{t,n})^2, V_{out} > 0$$
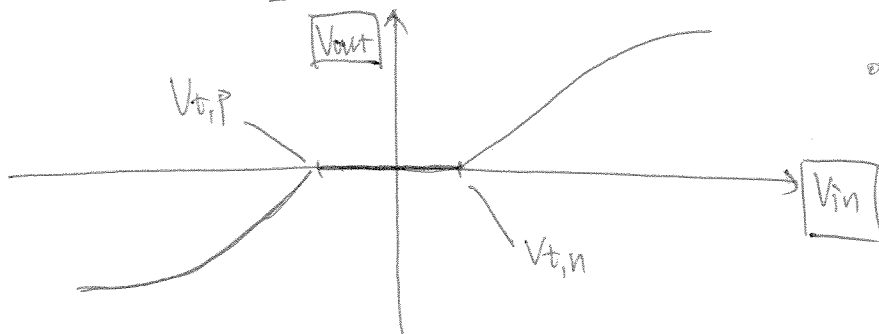
$$M_2 \text{ ON: } -\frac{V_{out}}{R_L} = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{out} - V_{in} - V_{t,p})^2, V_{out} < 0$$




• Solve for  $V_{out}$  in both cases.



(b) Outside dead zone

⇒ either  $M_1$  or  $M_2$  is on.


• For positive inputs:

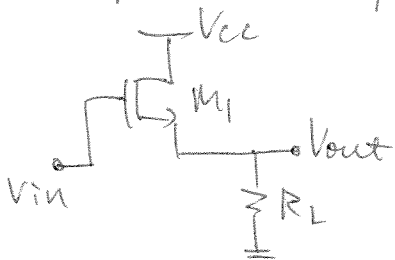

Source follower:

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m1}}{1 + g_{m1}R_L}$$

• For negative inputs:


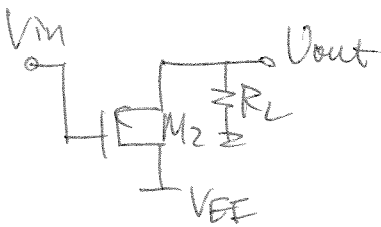


Source follower:

$$\therefore \frac{V_{out}}{V_{in}} = \frac{g_{m2}}{1 + g_{m2}R_L}$$

14. Dead zone :



$$V_{out} \in [-|V_{BE(on)2}|, V_{BE(on)3} + V_{BE(on)1}]$$

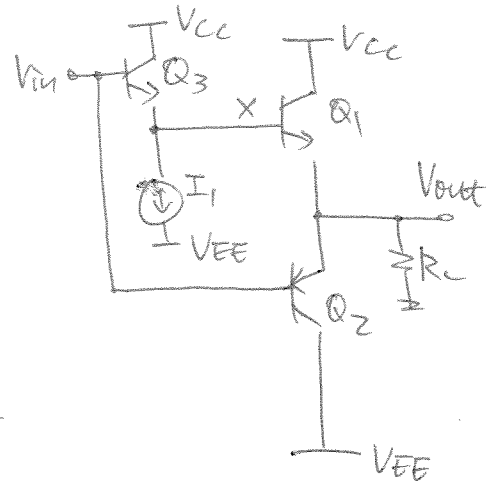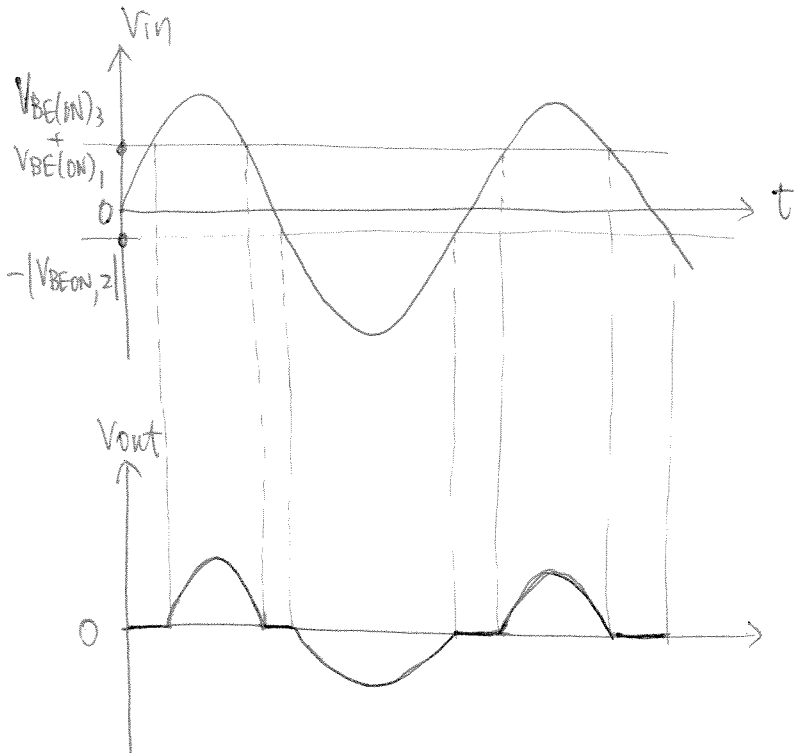




15.

Dead zone:

$$V_{out} \in [-(|V_{BE,ON,2}| + |V_{BE,ON,3}|), V_{BE,ON,1}]$$

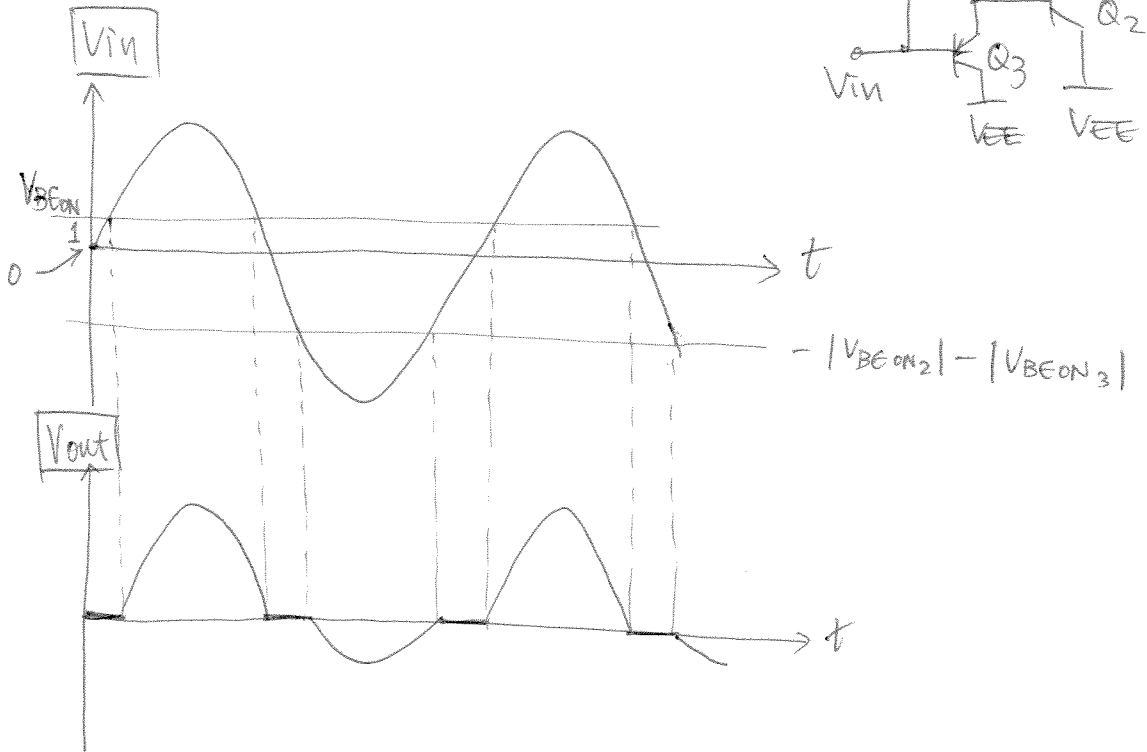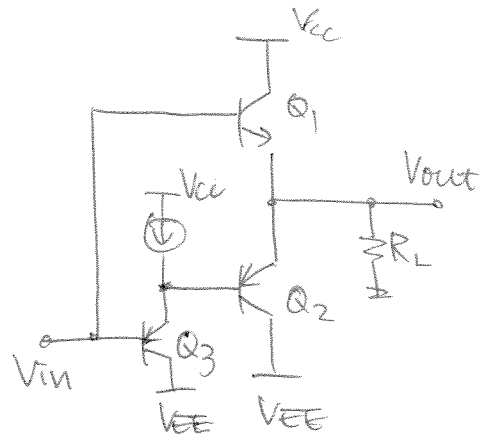

(b.)  
(a)

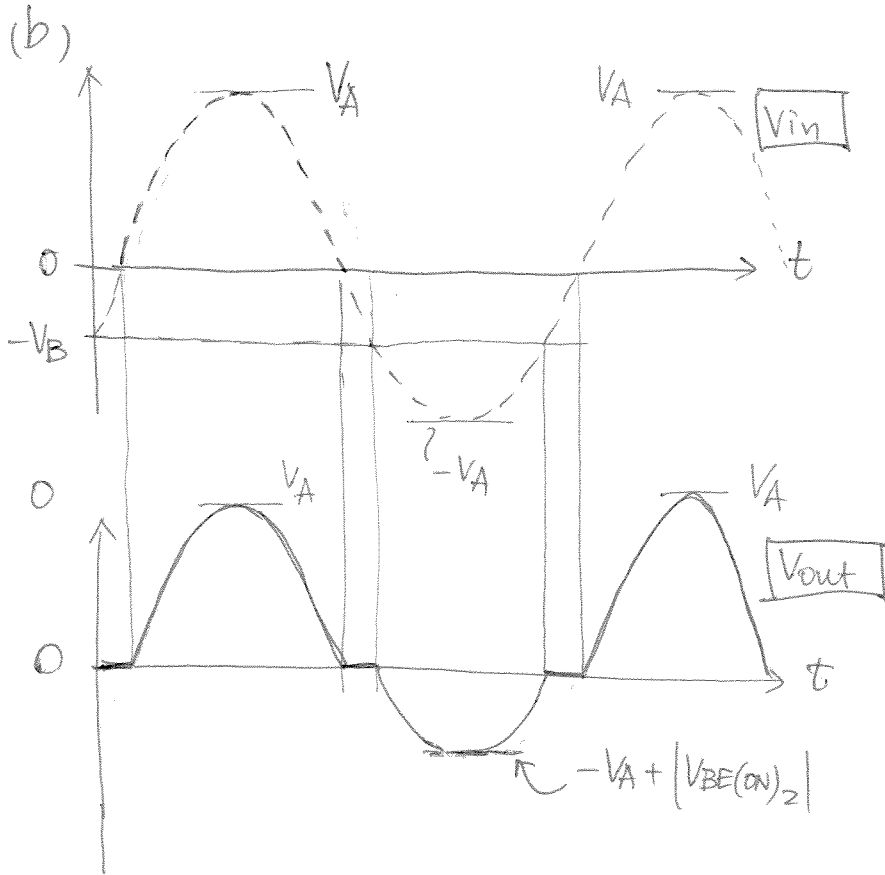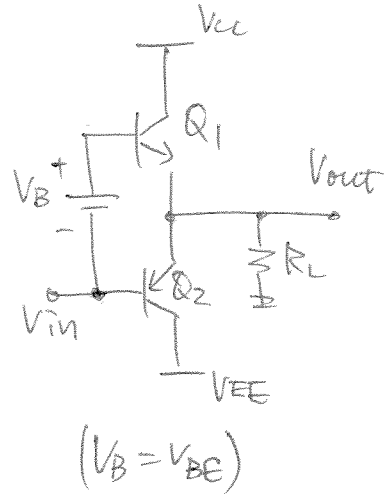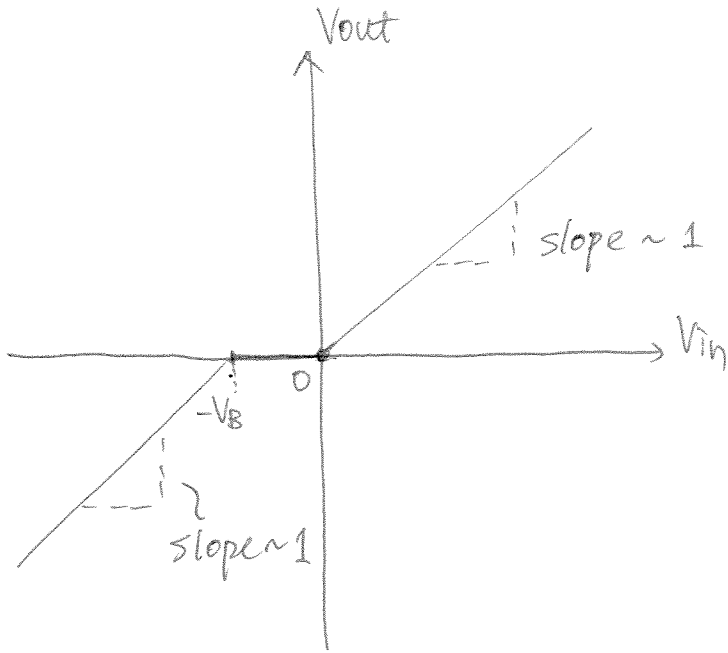

17.

•  $V_{out} = 0$ :

$$\Rightarrow I_{C1} = I_{C2} = I_{BIAS}$$

$$\Rightarrow I_{S1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = I_{S2} \exp\left(\frac{V_{out} - V_{in}}{V_T}\right)$$

$$\ln\left(\frac{I_{S1}}{I_{S2}}\right) + \frac{V_{in} + V_B - V_{out}}{V_T} = \frac{V_{out} - V_{in}}{V_T}$$

• For  $V_{out} = 0$ ,  $V_T = 0.026$  V:

$$\Rightarrow \ln\left(\frac{5}{8}\right) + \frac{V_{in} + V_B}{0.026} = +\frac{V_{in}}{0.026}$$


• Given  $I_{C2} = 5$  mA

$$\Rightarrow I_{S2} \exp\left(\frac{-V_{in}}{0.026}\right) = 5 \text{ mA} \Rightarrow V_{in} = -0.83 \text{ V}$$

$$I_{C1} = I_{S1} \exp\left(\frac{V_{in} + V_B - V_{out}}{V_T}\right) = (5 \cdot 10^{-7} \text{ A}) \exp\left(\frac{-0.83 + V_B}{V_T}\right)$$

$$\Rightarrow V_B = 0.83 + 0.026 \ln\left(\frac{5 \text{ mA}}{5 \cdot 10^{-7} \text{ A}}\right)$$

$$\approx 1.67 \text{ V}$$

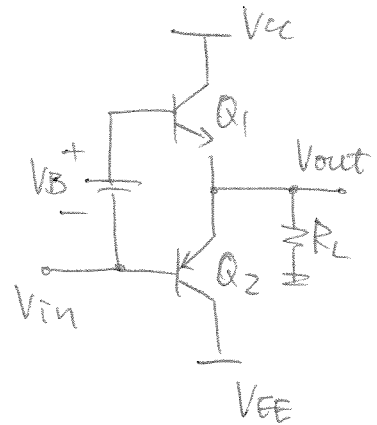

$$I_{S1} = 5 \cdot 10^{-17} \text{ A}$$



$$I_{S2} = 8 \cdot 10^{-17} \text{ A}$$

$$I_{BIAS} = 5 \text{ mA}$$

$$(V_{out} = 0)$$

18.

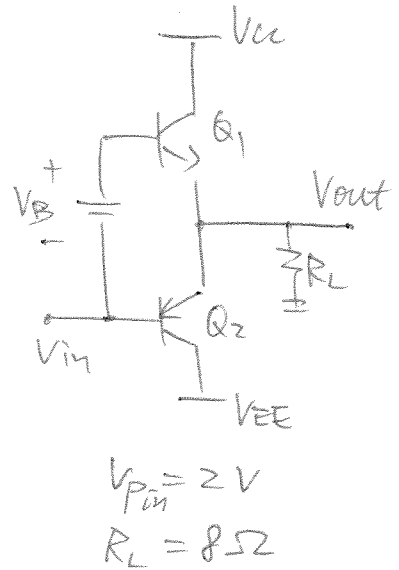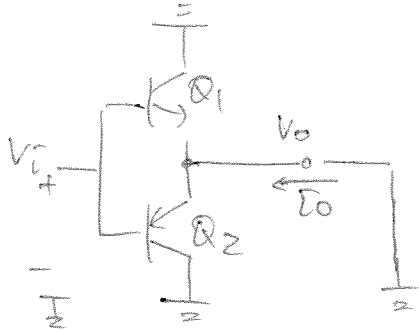(a) Equivalent circuit (small-signal) around  $V_{out} = 0$  :



$$\begin{aligned}\bar{i}_o &= -g_{m1} V_i + (-V_i) g_{m2} \\ &= -(g_{m1} + g_{m2}) V_i\end{aligned}$$

$$\therefore G_m = \frac{\bar{i}_o}{V_i} = -(g_{m1} + g_{m2})$$

$$\therefore A_v = \frac{V_o}{V_i} = \frac{\bar{i}_o \times R_L}{V_i} = -(g_{m1} + g_{m2}) R_L$$

$$\begin{aligned}(b) A_v &= -(g_{m1} + g_{m2}) R_L = -\left(\frac{I_{c1}}{V_T} + \frac{I_{c2}}{V_T}\right) R_L \\ &= -\left(\frac{5mA}{0.026V} + \frac{5mA}{0.026V}\right) (85\Omega) = -3.08\end{aligned}$$



$$\Rightarrow |V_o|_P = |V_i A_v|_P = |(2V)(-3.08)| = 6.16V$$

(Assume  $V_{cc}$  is large enough)

$$(c) \quad I_{c1} = I_{c2} + \frac{V_{out}}{R_L}$$


$$\begin{aligned} I_{c1, peak} &= I_{c2} + \frac{V_P}{R_L} \\ &= 5 \text{ mA} + \frac{6.16 \text{ V}}{8.52} \\ &= 775 \text{ mA} \end{aligned}$$

19.

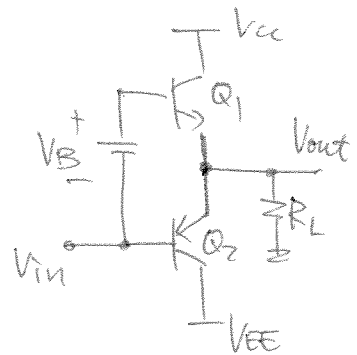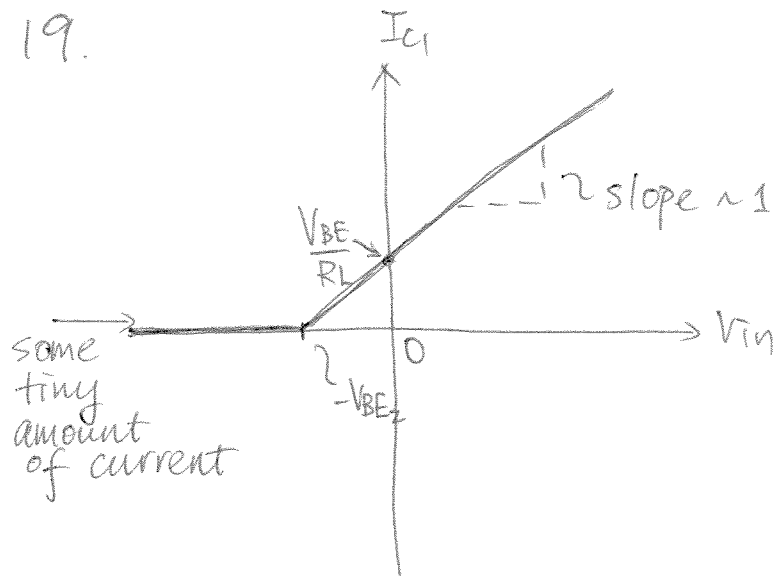



$$V_{out} = V_{in} + |V_{BE2}|$$
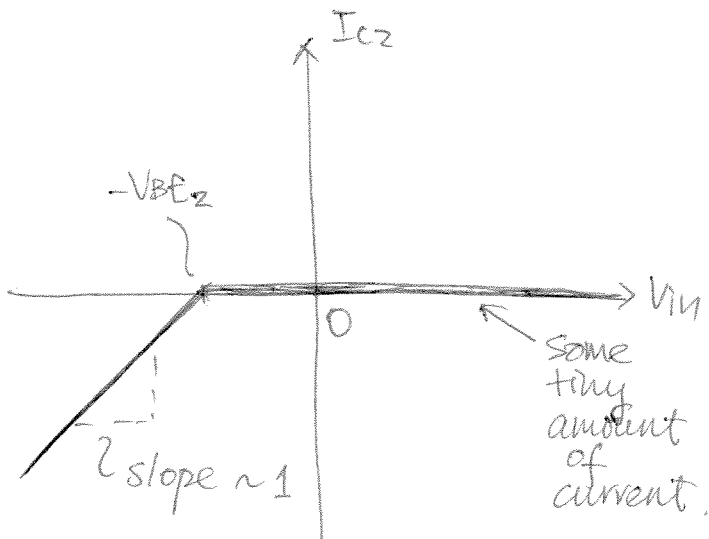
$$\Rightarrow I_{c1} = I_{c2} + \frac{V_{out}}{R_L}$$





20.

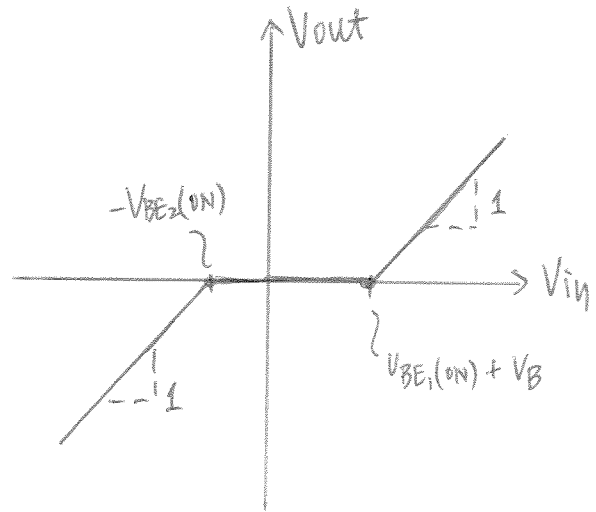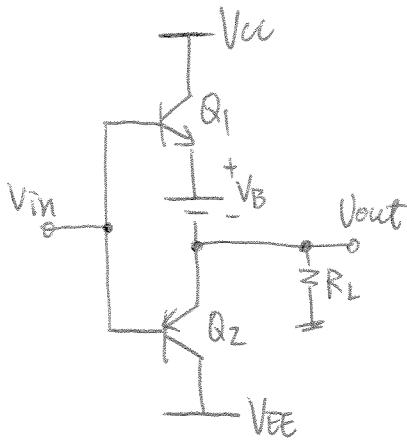

• To analyze such circuit, assume  $V_{out} = 0$ :

$$\Rightarrow -V_{BE2(ON)} < V_{in} < V_{BE1(ON)} + V_B$$

$$(V_{BE1(ON)} + V_B) < V_{in} \quad \therefore \quad V_{out} = V_{in} - V_{BE1(ON)} - V_B$$

$$V_{in} < -V_{BE2(ON)} \quad \therefore \quad V_{out} = V_{in} + |V_{BE2(ON)}|$$

$$21. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow V_T \left[ \ln \frac{I_{C1}}{I_{S_{Q1}}} + \ln \frac{I_{C2}}{I_{S_{Q2}}} \right] = V_T \left[ \ln \frac{I_{D1}}{I_{S_{D1}}} + \ln \frac{I_{D2}}{I_{S_{D2}}} \right]$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S_{Q1}} I_{S_{Q2}}} = \frac{I_{D1} I_{D2}}{I_{S_{D1}} I_{S_{D2}}}$$

$\therefore$  If  $I_{S_{Q1}} I_{S_{Q2}} = I_{S_{D1}} I_{S_{D2}}$ ,  
then  $I_{C1} I_{C2} = I_{D1} I_{D2}$

$$22. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow V_T \ln\left(\frac{I_{C1} I_{C2}}{I_{S,R1} I_{S,R2}}\right) = V_T \ln\left(\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}\right)$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,R1} I_{S,R2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{————— (1)}$$

$$I_1 = I_{D1} = I_{D2} = 1 \text{ mA}; \quad I_{S,R} = 16 I_{S,D}$$

$$V_{out} = 0 \Rightarrow I_{C1} = I_{C2} \quad \text{————— (2)}$$

Substitute all into (1):

$$\frac{I_{C1} I_{C1}}{(16 I_{S,D})^2} = \frac{(1 \text{ mA})^2}{(I_{S,D})^2} \Rightarrow I_{C1} = I_{C2} = 16 \text{ mA}$$

$$23. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{—————} \quad \textcircled{1}$$

$$I_{C1} = I_{C2} = 5 \text{ mA} \quad \text{—————} \quad \textcircled{2}$$

$$I_{S,Q} = 8 I_{S,D} \quad \text{—————} \quad \textcircled{3}$$

Substitute all into  $\textcircled{1}$ :

$$\frac{(5 \text{ mA})^2}{(8 I_{S,D})^2} = \frac{I_{D1} I_{D2}}{(I_{S,D})^2} \Rightarrow I_1 = I_D = 0.625 \text{ mA}$$

$$24. \quad V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} = \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \quad \text{--- ①}$$

$$I_1 = I_D = 2 \text{ mA}$$

$$I_{S,Q1} = 8 I_{S,D1} \quad ; \quad I_{S,Q2} = 16 I_{S,D2}$$

Substitute all into ①:

$$\frac{I_{C1} I_{C2}}{(8 I_{S,D1})(16 I_{S,D2})} = \frac{(2 \text{ mA})^2}{I_{S,D1} I_{S,D2}}$$

$$\Rightarrow I_{C1} = I_{C2} \cong 22.6 \text{ mA}$$

$$25. V_{BE1} + |V_{BE2}| = V_{D1} + V_{D2}$$

$$\Rightarrow \frac{kT_Q}{q} \left[ \ln \left( \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} \right) \right] = \frac{kT_D}{q} \left[ \ln \left( \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right) \right]$$

Suppose  $T_D = (T_Q + \Delta T)$ :

$$\Rightarrow T_Q \left[ \ln \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}} - \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right] = \Delta T \cdot \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}$$


$$\Rightarrow I_{C1} \cdot I_{C2} = I_{S,Q1} \cdot I_{S,Q2} \cdot \left( \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right)^{1 + \frac{\Delta T}{T_Q}}$$

Typically,  $\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} > 1$

$\Rightarrow$  A  $\Delta T$  introduces a factor  $\left( \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} \right)^{\frac{\Delta T}{T_Q}} < 1$ ,

implying that the  $I_{C1} I_{C2}$  product drops corresponding to a change (positive) in temperature.


26. Small Signal:

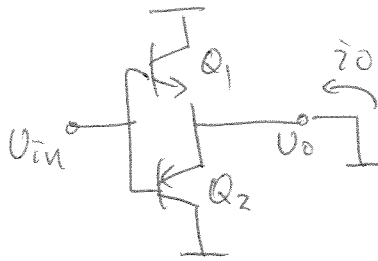

$$G_m = \frac{i_o}{v_{in}} = -(g_{m1} + g_{m2})$$

$$\Rightarrow \frac{v_o}{v_{in}} = \frac{i_o R_L}{v_{in}} = +(g_{m1} + g_{m2}) R_L$$

27. Small-signal:

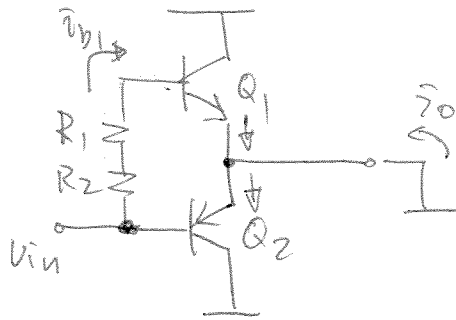

$$\bar{i}_o = -g_{m1} U_{be1} + g_{m2} |U_{be2}| \quad (\bar{i}_o = \bar{i}_{c2} - \bar{i}_{c1})$$

$$|U_{be2}| = v_{in}$$

$$U_{be1} = v_{in} - \bar{i}_{b1} (R_1 + R_2) = v_{in} - \frac{\bar{i}_{c1}}{\beta_1} (R_1 + R_2)$$

$$= v_{in} - \frac{\bar{i}_{c2} - \bar{i}_o}{\beta_1} (R_1 + R_2)$$

$$= v_{in} + \frac{g_{m2} v_{in} + \bar{i}_o}{\beta_1} (R_1 + R_2)$$

$$\therefore g_{m1} \left[ v_{in} + \frac{g_{m2} v_{in} + \bar{i}_o}{\beta_1} (R_1 + R_2) \right] + \bar{i}_o = -g_{m2} v_{in}$$


Solving for  $\frac{\bar{i}_o}{v_{in}}$  gives:

$$G_m = \frac{\bar{i}_o}{v_{in}} = - \frac{\left[ g_{m1} + \frac{g_{m1} g_{m2}}{\beta_1} (R_1 + R_2) + g_{m2} \right]}{1 + \frac{g_{m1} (R_1 + R_2)}{\beta_1}}$$



$R_{out}$ :
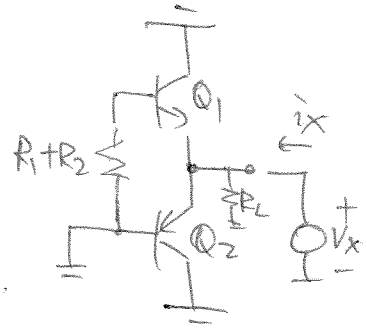
$$\frac{V_x}{i_x} = R_{out} = \left( r_{\pi 2} \parallel \frac{1}{g_{m2}} \right) \parallel \left[ \left( r_{\pi 1} + R_1 + R_2 \right) \parallel \frac{1}{g_{m1}} \right] \parallel R_L$$



$\therefore A_v = G_m R_{out}$

$$= - \left[ \frac{g_{m1} + \frac{g_{m1} g_{m2} (R_1 + R_2)}{\beta_1} + g_{m2}}{1 + \frac{g_{m1} (R_1 + R_2)}{\beta_1}} \right] \cdot \left\{ \left[ r_{\pi 2} \parallel \frac{1}{g_{m2}} \right] \parallel \left[ \left( r_{\pi 1} + R_1 + R_2 \right) \parallel \frac{1}{g_{m1}} \right] \parallel R_L \right\}$$


(28) Small Signal gain  
around  $V_{out} = 0$ :

$$A_v = +(g_{m1} + g_{m2}) R_L$$



$$0.8 = (I_{C1} + I_{C2}) \frac{R_L}{V_T}$$

If  $I_{C1} = I_{C2} = I_{BIAS}$ , then
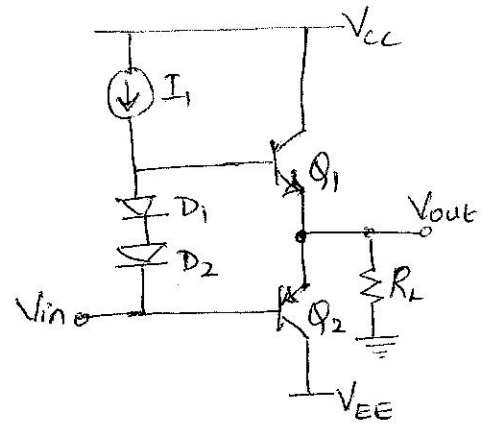
$$I_C = \frac{0.8}{2} \times \frac{V_T}{R_L} = 0.4 \frac{V_T}{R_L} = \frac{0.0104}{R_L} = 1.3 \text{ mA}$$



29. Small-signal equivalent:

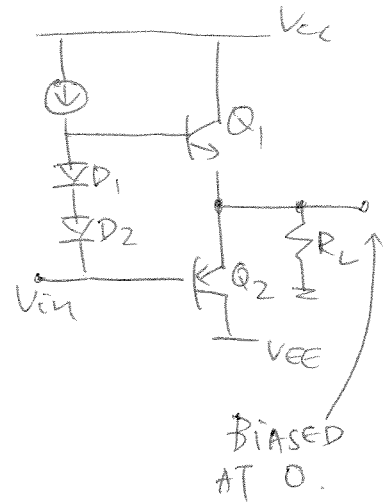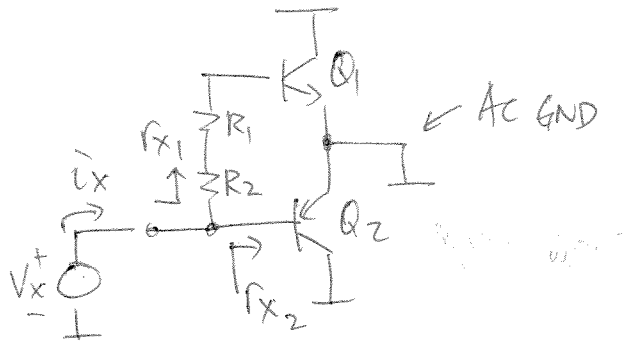

$$R_{in} = \frac{V_x}{I_x} = r_{x1} \parallel r_{x2}$$

$$= (R_1 + R_2 + r_{\pi 1}) \parallel r_{\pi 2}$$

•  $R_1$  &  $R_2$  can be neglected when  $r_{\pi 1} \gg (R_1 + R_2)$


30.  $I_{C1} = I_{C2} = 10 \text{ mA}$

$I_{C3} = I_{C4} = 1 \text{ mA}$


$\beta_1 = 40 \quad \beta_2 = 20$

$R_L = 8 \Omega$

$R_{D1} = R_{D2} = 0$

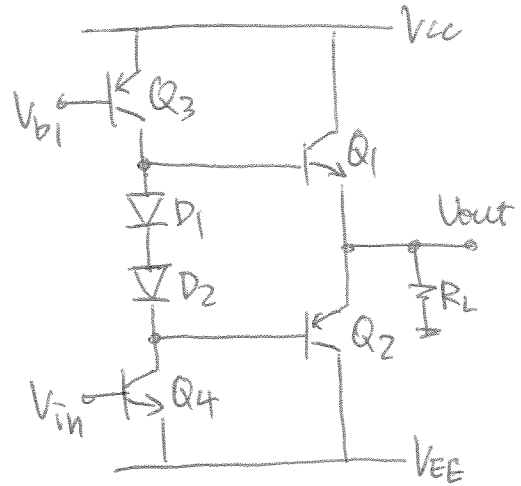

Small-signal

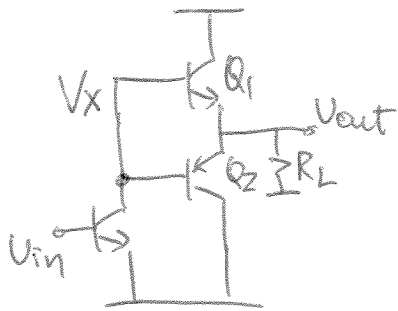

$$A_V = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}}$$

$$= -g_{m4} \left[ (g_{m1} + g_{m2}) (r_{\pi 1} \parallel r_{\pi 2}) R_L + (r_{\pi 1} \parallel r_{\pi 2}) \right] \times \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$= -g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

$$\therefore A_V = - \frac{I_{C4}}{V_T} \left( \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} \right) \left( \frac{I_{C1}}{V_T} + \frac{I_{C2}}{V_T} \right) R_L$$

$$= - \frac{1 \text{ mA}}{0.026} [35] \cdot \left( 2 \times \frac{10 \text{ mA}}{V_T} \right) (8)$$

$$\approx -8.3$$

31.

$$\frac{V_{out}}{V_{in}} = -g_{m4} (\Gamma_{\pi_1} \parallel \Gamma_{\pi_2}) (g_{m_1} + g_{m_2}) R_L \quad (\Gamma_{\pi} = \frac{\beta}{g_m})$$

When  $g_{m_1} \approx g_{m_2}$  : ( $\Rightarrow \Gamma_{\pi}$ )

$$\begin{aligned} \frac{V_{out}}{V_{in}} &\hat{=} -g_{m4} R_L (2g_{m_1}) \left( \frac{\beta_1}{g_{m_1}} \parallel \frac{\beta_2}{g_{m_1}} \right) \\ &= -g_{m4} R_L (2g_{m_1}) \left[ \frac{1}{g_{m_1}} \cdot \frac{\beta_1 \beta_2}{\beta_1 + \beta_2} \right] \\ &= - \frac{2\beta_1 \beta_2}{\beta_1 + \beta_2} g_{m4} R_L \end{aligned}$$

(32) From eqn. (13.23), Small-signal gain of the output stage is:

$$\left| \frac{V_{out}}{V_{in}} \right| = + g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$


$$\approx + g_{m4} R_L \times \frac{2\beta_1 \beta_2}{\beta_1 + \beta_2}$$

$$\Rightarrow A = + \frac{I_{C4}}{V_T} (8\Omega) \times \frac{2(40)(20)}{40+20}$$

$$\Rightarrow I_{C4} \approx I_{C3}$$

$$= \frac{4V_T}{(8\Omega)} \cdot \frac{40+20}{2(40)(20)}$$
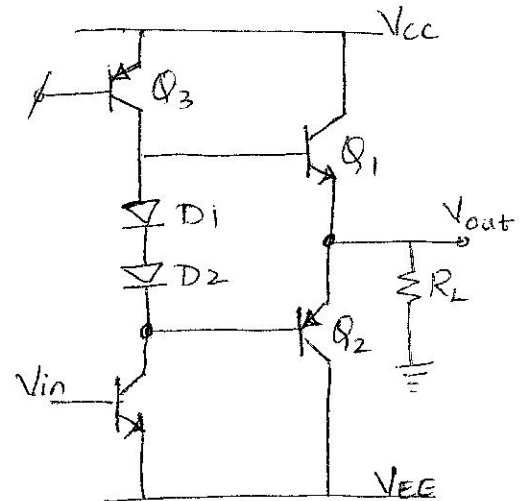
$$= \underline{\underline{0.49 \text{ mA}}}$$



$$A_V = \frac{V_{out}}{V_{in}} = 4$$

$$\beta_1 = 40$$

$$\beta_2 = 20$$


$$R_L = 8\Omega$$

33) From equation 13.27,

$$\frac{V_x}{I_x} = \frac{1}{g_{m1} + g_{m2}} + \frac{r_{o3} \parallel r_{o4}}{(g_{m1} + g_{m2})(r_{\pi1} \parallel r_{\pi2})}$$

If  $g_{m1} \approx g_{m2} = g_m$ :
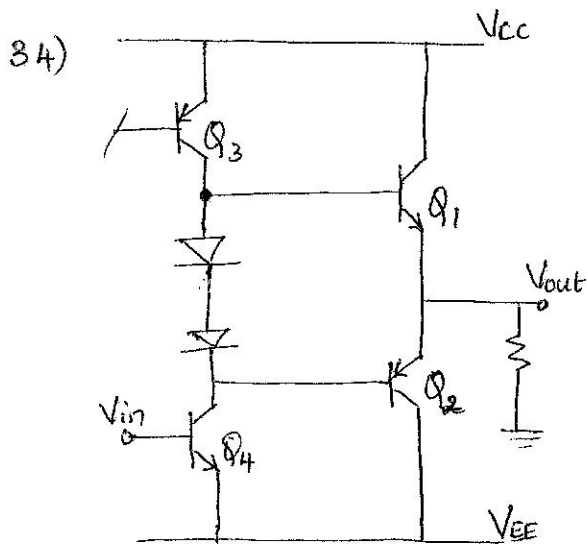
$$\begin{aligned} \frac{V_x}{I_x} &\approx \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2g_m \left( \frac{\beta_1}{g_m} \parallel \frac{\beta_2}{g_m} \right)} \\ &= \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2g_m \left( \frac{1}{g_m} \frac{\beta_1 \beta_2}{\beta_1 + \beta_2} \right)} \\ &= \frac{1}{2g_m} + \frac{r_{o3} \parallel r_{o4}}{2\beta_1 \beta_2} (\beta_1 + \beta_2) \end{aligned}$$




$$I_3 = I_4 = 1 \text{ mA}$$

$$I_1 = I_2 = 8 \text{ mA}$$

$$V_{A3} = 10 \text{ V}$$

$$V_{A4} = 15 \text{ V}$$

(a) Small-Signal Equivalent

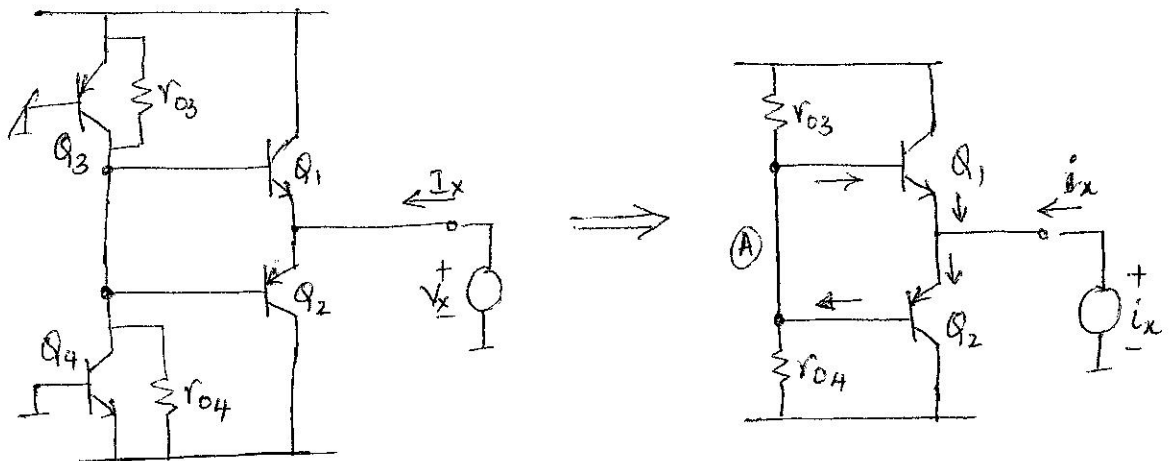

$$V_{eb} = V_x \frac{(r_{\pi 1} \parallel r_{\pi 2})}{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{O3} \parallel r_{O4})}$$

$$V_{be} = V_A - V_x$$

$$i_x + i_{c1} = i_{e2} \Rightarrow i_x = i_{e2} - i_{c1} = g_{m2} V_{eb} - g_{m1} V_{be}$$

$$\therefore i_x = [g_{m2} + g_{m1}] V_x \frac{(r_{\pi 1} \parallel r_{\pi 2})}{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{O3} \parallel r_{O4})}$$

$$\Rightarrow \frac{V_x}{i_x} = R_{out} = \frac{(r_{\pi 1} \parallel r_{\pi 2}) + (r_{O3} \parallel r_{O4})}{[g_{m1} + g_{m2}] (r_{\pi 1} \parallel r_{\pi 2})}$$



$$r_{\pi 1} = \frac{\beta_1 V_T}{I_{C1}} = 130 \Omega$$

$$r_{\pi 2} = \frac{\beta_2 V_T}{I_{C2}} = 65 \Omega$$

$$r_{o3} = \frac{V_{A3}}{I_{C3}} = 10 \text{ k}\Omega$$

$$r_{o4} = \frac{V_{A4}}{I_{C4}} = 15 \text{ k}\Omega$$

$$g_{m1} = 0.31 \text{ S}$$

$$g_{m2} = 0.31 \text{ S}$$

$$\Rightarrow R_{out} = \frac{43.3 + 6000}{(0.62)(43.3)} \approx 225.1 \Omega$$

(b) Effective  $R_{out} = R_{out, a} \parallel 8 \Omega \approx 8 \Omega$

$$G_m = \frac{i_o}{V_A} \cdot \frac{V_A}{V_{in}}$$


$$= -g_{m4} (r_{\pi 1} \parallel r_{\pi 2} \parallel r_{o3}) \cdot (g_{m1} + g_{m2})$$

$$\therefore A_v = G_m R_{out}$$

$$= -g_{m4} (r_{\pi 1} \parallel r_{\pi 2} \parallel r_{o3}) (g_{m1} + g_{m2}) R_{out}$$

$$= -0.038 [130 \parallel 65 \parallel 10 \text{ k}] [0.62] (8)$$


$$\approx -8.1$$

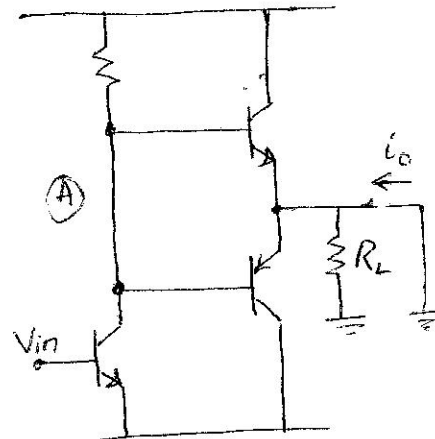

$$g_{m4} = \frac{I_{C4}}{V_T} = 0.038 \text{ S}$$

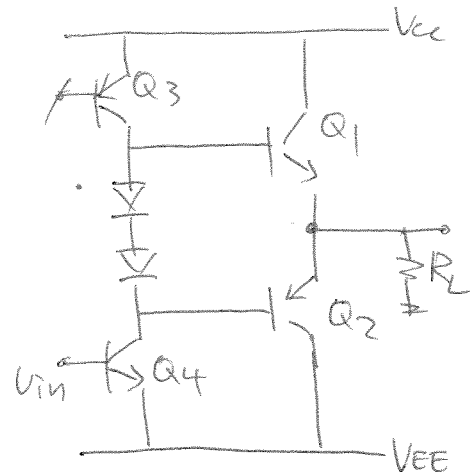35. Max current delivered  
 by  $Q_1 = I_{C3} \beta_1 = 1 \text{ mA} \cdot 40$   
 $= 40 \text{ mA. (} Q_4 \text{ off)}$

Max current delivered  
 by  $Q_2 = I_{C4} \cdot \beta_2$   
 $= 1 \text{ mA} \cdot 20$   
 $= 20 \text{ mA. (} Q_3 \text{ off)}$



$$I_{C3} = I_{C4} = 1 \text{ mA}$$


$$\beta_1 = 40 \quad \beta_2 = 20$$

36.  $P = 0.5 \text{ W}$      $R_L = 8 \Omega$   
 $\beta_1 = 40$      $\beta_2 = 20$ .

$$P_{\text{AVG}} = \frac{1}{2} \frac{V_p^2}{R_L} = 0.5$$

$$\Rightarrow V_p^2 = 2(0.5)R_L$$
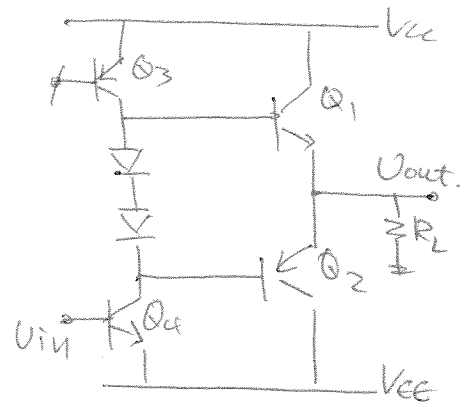
$$\Rightarrow V_p = \sqrt{R_L} = 2\sqrt{2}$$



At positive  $V_p$ ,  $I_{c1} = \frac{V_p}{R_L} = \frac{2\sqrt{2}}{8} = 0.35 \text{ A}$ .

At negative  $V_p$ ,  $I_{c2} = \frac{V_p}{R_L} \Rightarrow I_{c2} = 0.35 \text{ A}$ .

- At  $+V_p$ , all of  $I_{c3}$  supports the base current of  $Q_1$

$$\Rightarrow I_{c3} = I_{B1} = \frac{I_{c1}}{\beta_1} = \frac{0.35 \text{ A}}{40} = 8.75 \text{ mA}$$

- At  $-V_p$ , all of  $I_{c4}$  supports the base current of  $Q_2$

$$\Rightarrow I_{c4} = I_{B2} = \frac{I_{c2}}{\beta_2} = \frac{0.35 \text{ A}}{20} = 17.5 \text{ mA}$$

$$37) \quad P_{AVG} = 0.5W \quad R_L = 8\Omega \quad V_{CC} = 5V$$

$$\Rightarrow 0.5W = \frac{1}{2} \frac{V_p^2}{R_L}$$

$$\Rightarrow V_p = 2\sqrt{2} \text{ V}$$


$$P_{Q1} = \frac{1}{T} \int_0^{T/2} I_{C1} V_{CE1} dt$$

$$= \frac{1}{T} \int_0^{T/2} \left( \frac{V_p \sin \omega t}{R_L} \right) (V_{CC} - V_p \sin \omega t) dt$$

$$= \frac{1}{T} \int_0^{T/2} \left[ \frac{V_{CC} V_p}{R_L} \sin \omega t \right] dt - \frac{V_p^2}{2R_L}$$

$$= \frac{V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{4} \right) = \frac{2\sqrt{2}}{8} \left( \frac{5}{\pi} - \frac{2\sqrt{2}}{4} \right)$$

$$\approx 0.31W$$

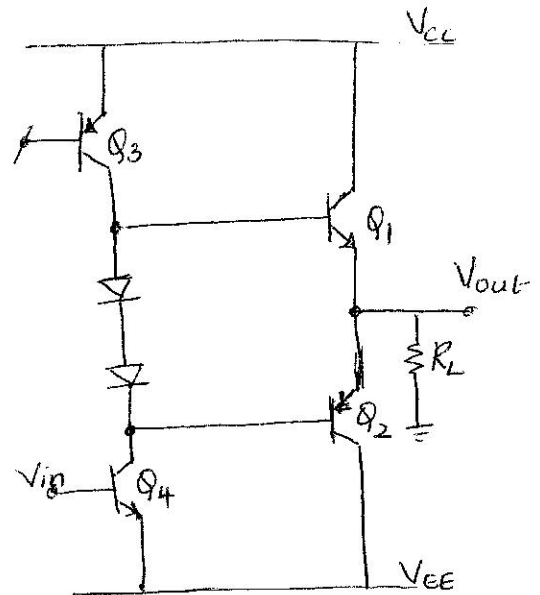

38)  $P_{Q,MAX} = 0.75W$ ,  $R_L = 8\Omega$ ,  $V_{CC} = 5V$

- Out of all 4 transistors,  $Q_1$  &  $Q_2$  must sustain the most currents

$$P_{Q,MAX} = V_{CE} \times I_{C1,MAX} = (V_{CC} - V_{OUT}) I_{C1,MAX}$$

(INST)

$$\Rightarrow P_{Q,MAX} = \frac{1}{T} \int_0^{T/2} \frac{V_P \sin \omega t}{R_L} \cdot (V_{CC} - V_P \sin \omega t) dt$$

(AVG)


$$= \frac{1}{T} \int_0^{T/2} \left( \frac{V_{CC} V_P}{R_L} \sin \omega t \right) dt - \frac{V_P^2}{2R_L}$$

$$= \frac{V_P}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)$$

$$\Rightarrow \frac{dP_Q}{dV_P} = \frac{V_{CC}}{\pi R_L} - \frac{V_P}{2R_L} = 0 \text{ when } V_P = \frac{2V_{CC}}{\pi} = 3.18V$$

$$P_{Q/V_P} = \frac{2V_{CC}}{\pi} = 0.32W$$
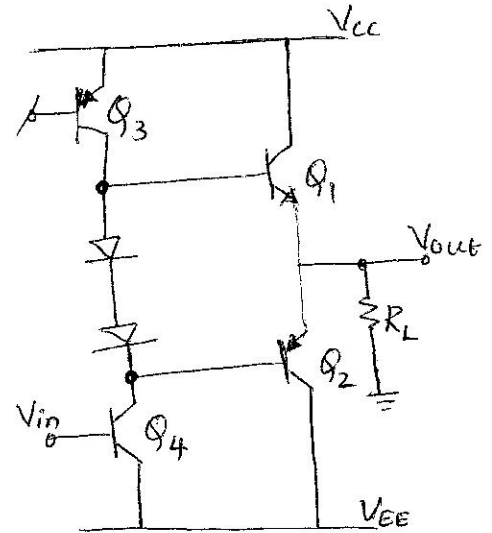
$$\therefore P_{R_L,MAX} = \frac{1}{2} \frac{V_P^2}{R_L} = 0.63W$$



$$39. P_{Q1, \text{MAX}} = \left( \frac{V_{CC}}{\pi} - \frac{2V_{CC}}{4\pi} \right) \cdot \frac{2V_{CC}}{\pi R_L} \leq 0.75 \text{ W}$$

$$\Rightarrow V_{CC, \text{MAX}} = 7.7 \text{ V}$$


$$\Rightarrow V_{P, \text{MAX}} = \frac{2V_{CC, \text{MAX}}}{\pi} = 4.9 \text{ V}$$

$$\Rightarrow P_{R_L, \text{MAX}} = \frac{1}{2} \frac{V_{P, \text{MAX}}^2}{R_L} = 1.5 \text{ W}$$

$$\begin{aligned}
 40. \quad I_1 &= I_{C1} + I_{E2} \\
 &= I_{C1} + \frac{\beta_1 + 1}{\beta_1} I_{C2} \\
 &= I_{C1} + \frac{\beta_1 + 1}{\beta_1} I_{B1} \\
 &= \beta_1 I_{B1} + \frac{\beta_1 + 1}{\beta_1} I_{B1}
 \end{aligned}$$

$$\begin{aligned}
 \Rightarrow I_{B1} &= \frac{I_1}{\beta_1 + \frac{\beta_1 + 1}{\beta_1}} = \frac{0.005}{40 + \frac{41}{40}} \\
 &= 0.12 \text{ mA}
 \end{aligned}$$
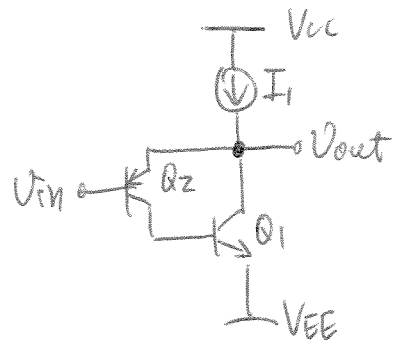
$$\Rightarrow I_{B2} = \frac{I_{C2}}{\beta_2} = \frac{I_{B1}}{\beta_2} = 0.0024 \text{ mA}$$




$$\begin{aligned}
 I_1 &= 5 \text{ mA} \\
 \beta_1 &= 40 \\
 \beta_2 &= 50.
 \end{aligned}$$

41.  $V_{in} = 0.5 \text{ V}$   
 $I_{S2} = 6 \cdot 10^{-17} \text{ A}$

$$I_{B1} = I_{C2} = 0.12 \text{ mA}$$


$$\Rightarrow I_{C2} = I_{S2} \cdot \exp\left(\frac{V_{out} - V_{in}}{V_T}\right)$$
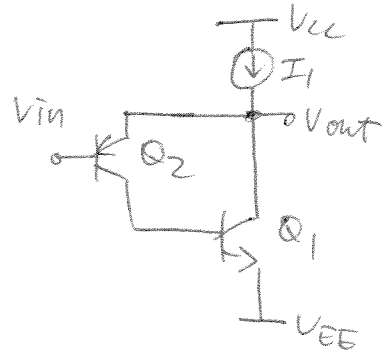
$$\begin{aligned} \therefore V_{out} &= V_T \ln\left(\frac{I_{C2}}{I_{S2}}\right) + V_{in} \\ &= 0.026 \ln\left(\frac{0.12 \text{ mA}}{6 \cdot 10^{-17} \text{ A}}\right) + 0.5 \\ &\hat{=} 1.24 \text{ V} \end{aligned}$$





42.

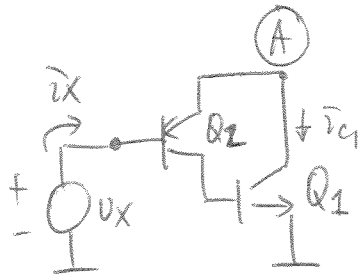

$$\bar{v}_{c2} = \bar{v}_x \beta_2$$

$$\bar{v}_{c1} = -g_{m2} v_{eb2} = \bar{v}_{e2} = \bar{v}_{c2} + \bar{v}_{b2} = \bar{v}_x (\beta_2 + 1)$$


$$v_{eb2} = v_A - v_x$$

$$\text{where } v_A = v_x - \bar{v}_x r_{\pi 2}$$

$$\therefore \bar{v}_{b1} = -g_{m2} (\bar{v}_x r_{\pi 2})$$

$$\bar{v}_{c1} = \bar{v}_{b1} + \bar{v}_{b1} \beta_1 = -g_{m1} \bar{v}_x r_{\pi 2} (1 + \beta_1)$$
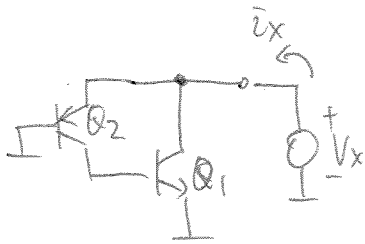
$$\Rightarrow \frac{v_x}{\bar{v}_x} \rightarrow \infty \quad (R_{in})$$



$$\bar{v}_x = \bar{v}_{e2} + \bar{v}_{c1}$$

$$= \bar{v}_{e2} + \bar{v}_{b1} \beta_1$$

$$= \bar{v}_{e2} + \bar{v}_{c2} \beta_1$$

$$= \bar{v}_{c2} + \bar{v}_{b2} + \bar{v}_{c2} \beta_1$$

$$= \bar{v}_{c2} (1 + \beta_1 + \frac{1}{\beta_1})$$

$$= v_x g_{m2} (1 + \beta_1 + \frac{1}{\beta_1})$$

$$\Rightarrow R_{out} = \frac{v_x}{i_x} = \frac{1}{g_{m2} (1 + \beta_1 + \frac{1}{\beta_1})}$$

$$= 0.005 \Omega$$

$$g_{m2} = \frac{I_{B2} \beta_2}{V_T}$$

$$= 4.6 \text{ S}$$

$$43) R_{out} = 1 \Omega \quad \beta_1 = 40 \quad \beta_2 = 50$$

$$R_{out} = 1 = \frac{1}{g_{m2} \left(1 + \beta_1 + \frac{1}{\beta_1}\right)}$$

$$\Rightarrow g_{m2} = 0.024 \text{ S} = \frac{I_{B2} \beta_2}{V_T}$$

$$\Rightarrow I_{B2} = 0.012 \text{ mA}$$


$$I_1 = I_{C1} + I_{E2} = I_{B1} \beta_1 + (I_{C2} + I_{B2})$$

$$= I_{C2} \beta_1 + I_{B2} (\beta_2 + 1)$$

$$= I_{B2} \beta_2 \beta_1 + I_{B2} (\beta_2 + 1)$$

$$= 0.012 [50 \times 40 + 50 + 1]$$

$$= 24.6 \text{ mA}$$

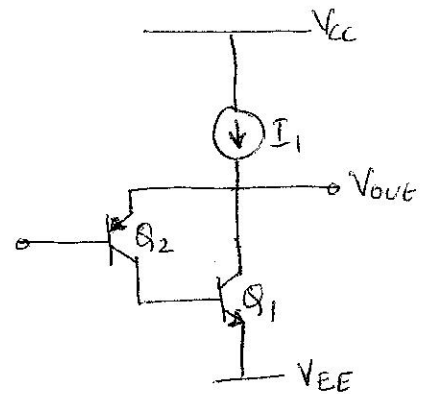

44)


$$V_p = 0.5 \text{ V}, \quad R_L = 8 \Omega$$

$$P_{R_L} = \frac{V_p^2}{2R_L} = \frac{0.25}{16} = 0.0156 \text{ W}$$

$$P_I = -I \times V_{EE} = 0.14 \text{ W}$$

$$P_{Q_1} = I_1 \left( V_{CC} - \frac{V_p}{2} \right) = 0.1225 \text{ W}$$
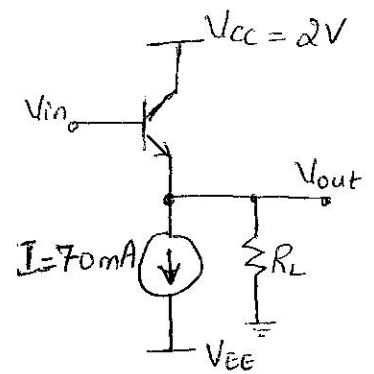
$$\therefore \eta = \frac{P_{R_L}}{P_{R_L} + P_I + P_{Q_1}} = \frac{0.0156}{0.2781} = 5.6\%$$



$$45. P_{R_L} = \frac{V_P^2}{2R_L} = \frac{(V_{CC} - V_{BE})^2}{2R_L}$$

$$P_{Q_1} = I_1 \left( V_{CC} - \frac{V_{CC} - V_{BE}}{2} \right)$$

$$P_I = +I_1 |V_{EE}|$$

• Assume

$$|V_{CC}| = |V_{EE}|,$$

$$I_1 = V_P / R_L$$

$$= \frac{V_{CC} - V_{BE}}{R_L}$$

$$\begin{aligned} \therefore \eta &= \frac{P_{R_L}}{P_{R_L} + P_{Q_1} + P_I} = \frac{\frac{(V_{CC} - V_{BE})^2}{2R_L}}{\frac{(V_{CC} - V_{BE})^2}{2R_L} + I_1 \left[ V_{CC} - \frac{V_{CC} - V_{BE}}{2} + |V_{EE}| \right]} \\ &= \frac{\frac{1}{2R_L}}{\frac{1}{2R_L} + \frac{3V_{CC} - V_{BE}}{2R_L(V_{CC} - V_{BE})}} \\ &= \frac{1}{1 + \frac{3V_{CC} - V_{BE}}{V_{CC} - V_{BE}}} \approx \frac{V_{CC} - V_{BE}}{3V_{CC} - V_{BE}} \end{aligned}$$

$$46. \eta = \frac{\frac{V_p^2}{2R_L}}{\frac{V_p^2}{2R_L} + \frac{2V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{4} \right)}$$
$$= \frac{\pi}{4} \frac{V_p}{V_{CC}}$$

$$\Rightarrow \eta \Big|_{V_p = V_{CC} - V_{BE}} = \frac{\pi}{4} - \frac{\pi}{4} \cdot \frac{V_{BE}}{V_{CC}}$$

$$\begin{aligned}
 47. \quad \eta &= \frac{\frac{(V_p/2)^2}{2R_L}}{\frac{(V_p/2)^2}{2R_L} + \frac{2(V_p/2)}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p/2}{4} \right)} \\
 &= \frac{V_p^2/8R_L}{\frac{V_p^2}{8R_L} + \frac{V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{8} \right)} = \frac{1/8R_L}{\frac{1}{8R_L} + \frac{1}{R_L} \left( \frac{V_{CC}}{V_p\pi} - \frac{1}{8} \right)} \\
 &= \frac{1}{1 + \left( \frac{8V_{CC}}{V_p\pi} - 1 \right)} = \frac{\pi}{8} \frac{V_p}{V_{CC}} \approx 39\%.
 \end{aligned}$$

48.

$$V_{CC} = 3V$$

$$P_{R_L} = 0.2W$$

$$R_L = 8\Omega$$

$$P_{R_L} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p = \sqrt{2P_{R_L} \times R_L} = 1.8V$$

$$\therefore \eta = \frac{P_{R_L}}{P_{R_L} + \frac{2V_p}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_p}{4} \right)} = \frac{0.2}{0.2 + \frac{3 \cdot 6}{8} \left( \frac{3}{\pi} - \frac{1.8}{4} \right)}$$

$$\approx 46.8\%$$


49. Power = 1 W  
 $R_L = 8\Omega$

$$P_{LOAD} = \frac{1}{2} \frac{V_p^2}{R_L} = 1 W$$

$$\Rightarrow V_p = 4 V \Rightarrow I_1 = \frac{V_p}{R_L} = 0.5 mA$$

(Note: the problem does not specify small-signal voltage gain, so choose  $V_p = I_1 R_L$ )
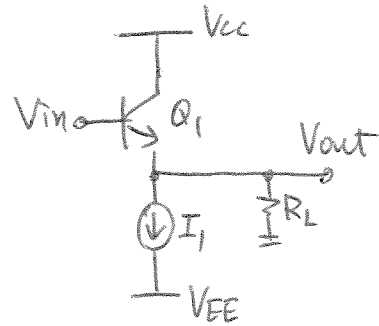
$$\begin{aligned} P_{Q_1} (\text{power rating}) &= I_1 (V_{cc}) \\ &= (0.5 mA)(5V) \\ &= 2.5 mW \end{aligned}$$





50.  $A_V = 0.8$   
 $R_L = 4 \Omega$


$$A_V = \frac{R_L}{R_L + \frac{1}{g_{m_1}}} = \frac{4}{4 + \frac{0.026}{I_{C_1}}} = 0.8$$

$$\Rightarrow I_{C_1} = 26 \text{ mA}$$

$$\therefore I_1 = I_{C_1} = 26 \text{ mA} \quad (V_{out} \text{ biased at } 0 \text{ V.})$$

$$\begin{aligned} \text{Max Output Swing} &= I_1 R_L \\ &\approx (26 \text{ mA})(8 \Omega) \\ &= 0.208 \text{ V} \end{aligned}$$
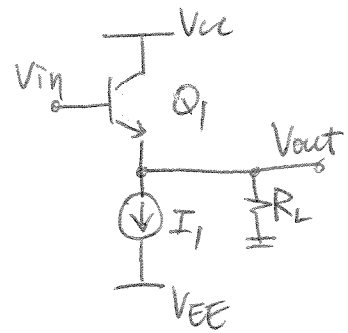
$$\begin{aligned} P_{Q_1} (\text{power rating}) &= I_1 V_{CC} (V_p = 0) \\ &= (26 \text{ mA})(5 \text{ V}) = 130 \text{ mW} \end{aligned}$$




51.  $A_v = 0.6$   
 $R_L = 8 \Omega$   
 $r_{D_1} = r_{D_2} = 0$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_{m_1}}} = \frac{(8 \Omega)}{(8 \Omega) + \frac{0.026 V}{I_{Q_1}}}$$

$$= 0.6$$
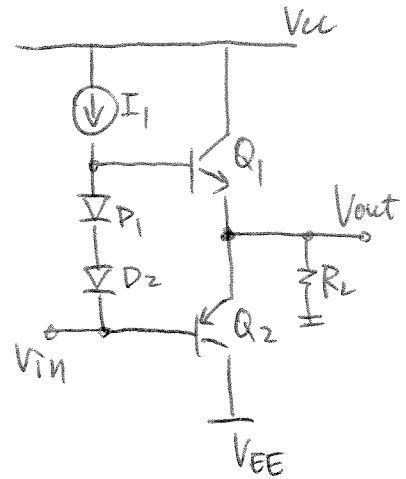
$$\Rightarrow I_{Q_1} = I_{Q_2} = 4.8 \text{ mA}$$



( $V_{out}$  biased at 0V.)

52. Power = 1 W (to load)

$$R_L = 8 \Omega$$

$$|V_{BE}| \approx 0.8 \text{ V}$$

$$\beta_1 = 40$$

$$P_L = \frac{1}{2} \frac{V_p^2}{R_L} = 1 \text{ W}$$


$$\Rightarrow V_p = 4 \text{ V}$$

$\therefore$  Min allowable supply =  $V_p + |V_{BE}| = 4.8 \text{ V}$   
voltage

• At  $+V_p$ , all of  $I_1$  goes to base of  $Q_1$

$$\Rightarrow I_1 = I_{B_1} = \frac{I_{C_1}}{\beta_1} = \frac{V_p}{R_L} \cdot \frac{1}{\beta_1} \quad (Q_2 \text{ off})$$
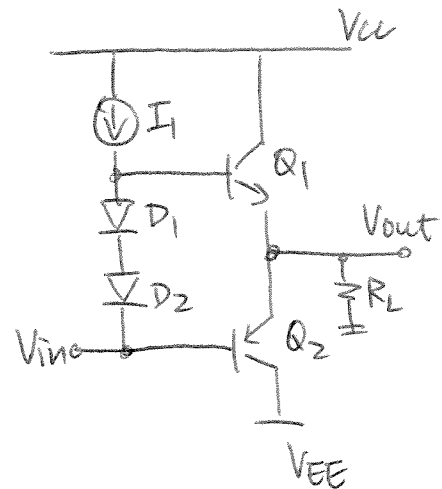
$$= \frac{4}{8} \cdot \frac{1}{40} = \frac{1}{80} = 12.5 \text{ mA}$$




53.  $P_{Q, \text{MAX}} = 2 \text{ W}$   
 $R_L = 8 \Omega$ .

For this circuit,

$$P_{\text{AVG}, \text{MAX}} = \frac{V_{cc}^2}{\pi^2 R_L} \quad \left( V_p = \frac{2V_{cc}}{\pi} \right)$$

$$= 2 \text{ W}$$

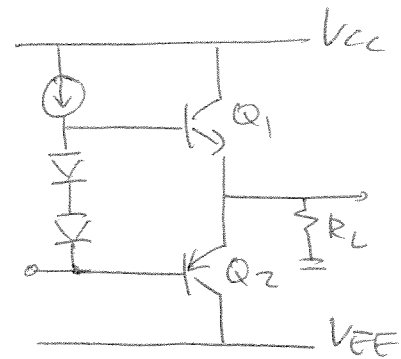

$$\Rightarrow V_{cc} \Big|_{\text{MAX}} = 12.6 \text{ V} \quad \Rightarrow V_p \Big|_{\text{MAX}} = \frac{2 \cdot 12.6}{\pi} = 8.02 \text{ V}$$

$$\therefore P_{R_L \text{ MAX}} = \frac{V_{p \text{ MAX}}^2}{2R_L} = \frac{(8.02)^2}{2 \cdot 8} = 4.02 \text{ W}$$

54. For this circuit,

$$P_{Q,MAX} = 2W$$

$$R_L = 4\Omega$$

$$P_{AVG,MAX} = \frac{V_{CC}^2}{2R_L} \quad \left( V_p = \frac{2V_{CC}}{\pi} \right)$$

$$\Rightarrow V_{CC,MAX} = \sqrt{\frac{\pi^2 R_L P_{Q,MAX}}{1}} = 8.9 V$$

$$\Rightarrow V_{p,MAX} = \frac{2V_{CC,MAX}}{\pi} = 5.6 V$$

$$\therefore P_{R_L,MAX} = \frac{V_{p,MAX}^2}{2R_L} = \frac{32}{2(4)} = 4W$$

$$55) A_v = 4 \quad R_L = 8 \Omega \quad I_{C1} \approx I_{C2} \quad \beta_1 = 40 \quad \beta_2 = 20$$

Suppose we want 1st-stage (CE amplifier) to have

$$\text{gain} = 5 \implies \text{2nd stage gain} = 0.8$$

$$\implies 0.8 = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$0.8 = \frac{8}{8 + \frac{1}{2g_m}} \implies g_{m1} = \frac{1}{4} S \implies I_{C1} = I_{C2} = 6.5 \text{ mA}$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = \frac{40(0.026)}{6.5 \text{ mA}} \parallel \frac{20(0.026)}{6.5 \text{ mA}} \approx 133 \Omega$$

$$\begin{aligned} \bullet A_v = 4 &= g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L \\ &= \frac{I_{C4}}{V_T} (133)(0.5)8 \end{aligned}$$

$$\implies I_{C4} = I_{C3} = \frac{4 V_T}{8(133)(0.5)} = 0.488 \text{ mA}$$

Max  $I_{Q1}$  when all of  $I_{C3}/I_{C4}$  supports base current of  $Q_1$

$$\implies I_{Q1, \text{MAX}} = I_{C4} = 0.488 \text{ mA}$$

$$56) A_v = 4 \quad R_L = 4 \Omega \quad I_{C1} \approx I_{C2}$$

$$\beta_1 = 40 \quad \beta_2 = 20$$

1st stage gain = 5 (CE amplifier).

2nd stage gain = 0.8

$$* 0.8 = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} = \frac{4}{4 + \frac{1}{2g_{m1}}}$$

$$\Rightarrow g_{m1} = 0.5 S \quad \Rightarrow I_{C1} = I_{C2} = 13 mA$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = 80 \parallel 40 = 26.7 \Omega$$

$$* A_v = 4 = g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

$$= \frac{I_{C4}}{V_T} (26.7) (1) (4)$$


$$\Rightarrow I_{C4} = I_{C3} = \frac{4 V_T}{(26.7)(1)(4)} = 0.974 mA$$

\* Max  $I_{Q1}$  ( $I_{Q1, MAX}$ ) when  $I_{C4} = I_{Q1, MAX} = 0.974 mA$

\* For a reduction of 2x the  $R_L$ , we have to provide

$$\rightarrow 2x \text{ current to base of } Q_1 \left( \frac{0.974}{0.488} \approx 2 \right)$$

57.  $P_{RL} = 2W$        $\beta_1 = 40$   
 $R_L = 8\Omega$        $\beta_2 = 20$   
 $|V_{BE}| = 0.8V$

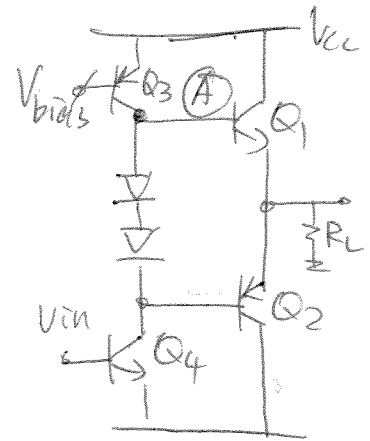

(a)  $P_{RL} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p \approx 5.6V$

• At  $+V_p$ ,  $V_A = V_p + |V_{BE}|$ .

• For  $Q_3$  in active region,  $V_A \leq V_{bias}$

$$\Rightarrow V_{CC} \geq V_{bias} + |V_{BE}| = V_p + 2|V_{BE}|$$

$$\geq 5.6 + 1.6 = 7.2V.$$

(b)  $I_p = \frac{V_p}{R_L} = 0.7A$ . ( $= I_{E1}$ ), ( $= I_{E2}$ )

$$\Rightarrow I_{B1} = \frac{I_{E1}}{1 + \beta_1} = 17mA.$$

$\therefore$  We bias  $Q_3$  &  $Q_4$  with  $I_C = 17mA$ .



$$(c) P_{AV} = \frac{V_P}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)$$
$$= \frac{5.6}{8} \left( \frac{5}{\pi} - \frac{5.6}{4} \right) = 3.66 \text{ W}$$

$$(d) P_{I_{Q3}} = 2V_{CC} \times I_{Q3} = 10 \times 17 \text{ mA} = 170 \text{ mW}$$

$$P_{AV, Q_1} = \frac{V_P}{R_L} \left( \frac{V_{CC}}{\pi} - \frac{V_P}{4} \right) = 3.66 \text{ W}$$

$$P_{R_L} = 2 \text{ W}$$

$$\Rightarrow \eta = \frac{P_{R_L}}{P_{I_{Q3}} + 2 \cdot P_{AV, Q_1} + P_{R_L}}$$
$$= \frac{2}{170 \text{ m} + 3.66 \times 2 + 2} = 0.21 = 21\%$$


58.

(a)  $A_V = 5$     $R_L = 4\Omega$     $\beta_1 = 40$     $\beta_2 = 20$ .

Assume  $I_{C1} \approx I_{C2}$ .

$$\frac{V_{out}}{V_{in}} = \frac{R_L}{(g_{m1} + g_{m2})^{-1} + R_L} = 0.8$$
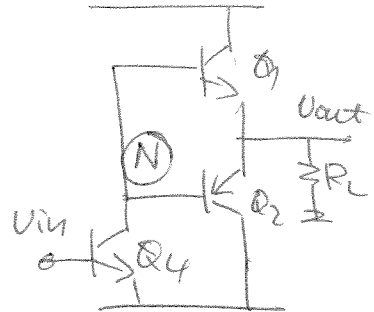
$$\Rightarrow 2g_{m1}^{-1} = 1 \Rightarrow I_{C1} = 2V_T = 0.052 \text{ A.}$$



$$\Rightarrow \frac{V_{out}}{V_{in}} = +g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L = 5$$

Assume  $g_{m1} \approx g_{m2}$ :

$$\Rightarrow I_{C4} = V_T \frac{5}{(r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L}$$

$$= V_T \times \frac{5}{(r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} \times 2) R_L}$$

$$= 0.026 \frac{5}{(6.7\Omega) (2 \times 2) (4)}$$

$$\approx 1.2 \text{ mA.}$$

$$\Rightarrow \text{Max } I \text{ by } Q_1 = \beta_1 \times I_{C4} = 48 \text{ mA}$$

$$\Rightarrow P_{R_L} = \frac{1}{2} I^2 R_L = 24 \times 4 \text{ mW} = 96 \text{ mW, BELOW requirement!}$$

$$(b) P = 5 \text{ W} = \frac{1}{2} \frac{V_p^2}{R_L} \Rightarrow V_p = 6.3 \text{ V}$$

$$\Rightarrow I_p = \frac{V_p}{R_L} = 1.6 \text{ A}$$

$$\Rightarrow I_{B2, \text{MAX}} = \frac{I_p}{\beta_2} = \frac{1.6}{20} = 79 \text{ mA}$$

$\Rightarrow I_{C2}$  must equal 79 mA to allow max output swing  $V_p$

$$\Rightarrow g_{m4} = \frac{I_{C4}}{V_T} = 3.04 \text{ S}$$

Suppose 2nd stage gain = 0.8 ( $I_{C1} = I_{C2}$ )

$$\Rightarrow \frac{v_{out}}{v_{in}} = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}} \Rightarrow g_{m1} = 0.5 \text{ S}$$



$$= 0.8 \Rightarrow I_{C1} = I_{C2} = 13 \text{ mA}$$

$$r_{\pi 1} \parallel r_{\pi 2} = \frac{\beta_1 V_T}{I_{C1}} \parallel \frac{\beta_2 V_T}{I_{C2}} = 26.7 \Omega$$



$$\therefore \frac{v_{out}}{v_{in}} = -(3.04)(26.7 \Omega)(0.5 + 0.5)4$$

$$= -324 \text{ !! (Huge! Impractical)}$$

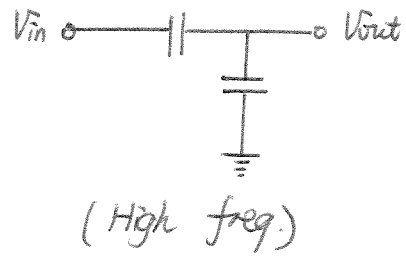
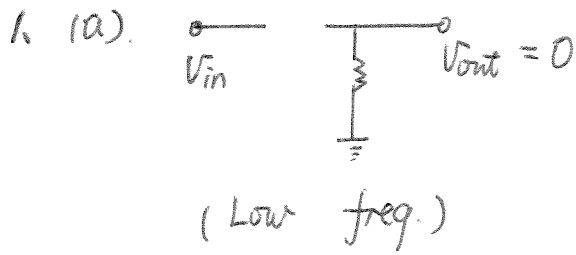
• Even when the 2nd stage gets close to 1, we still need huge gain from first stage.





This is a high pass filter.

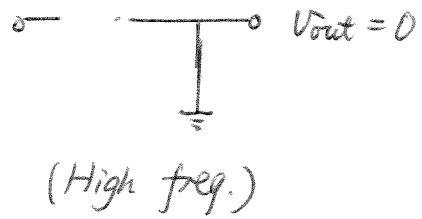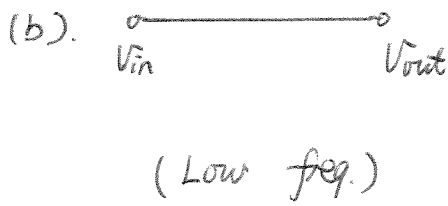



This is a low pass filter.

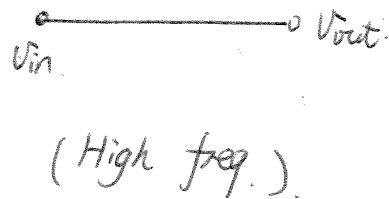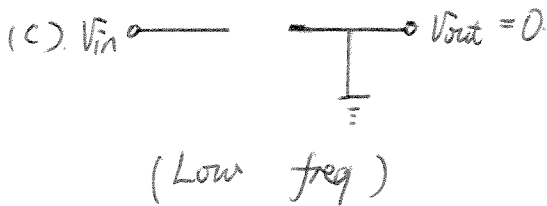


This is a high pass filter.

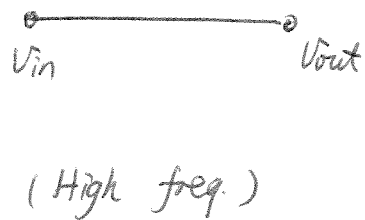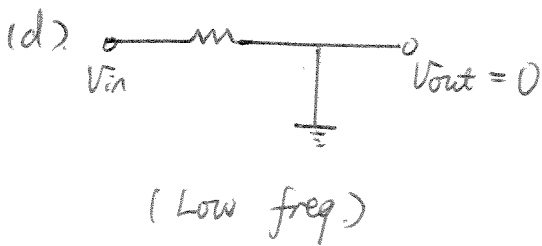

This is a high pass filter.

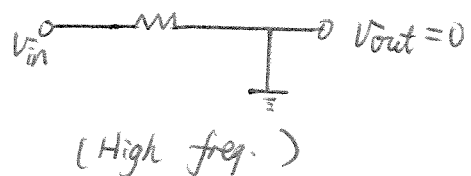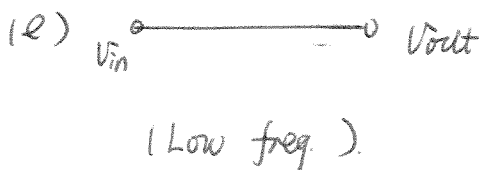


This is a low pass filter.

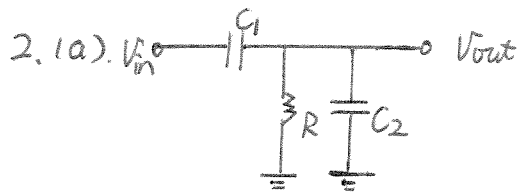

$$V_{out} = \frac{R // \frac{1}{sC_2}}{\frac{1}{sC_1} + R // \frac{1}{sC_2}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{C_1}{C_1 + C_2} s}{s + \frac{1}{R(C_1 + C_2)}}$$

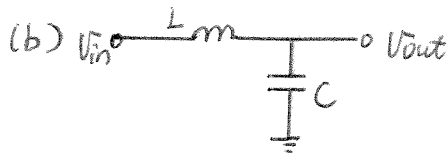
zero = 0; pole =  $-\frac{1}{R(C_1 + C_2)}$



$$V_{out} = \frac{\frac{1}{sC}}{sL + \frac{1}{sC}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{1/\sqrt{LC}}{s^2 + \frac{1}{LC}}$$

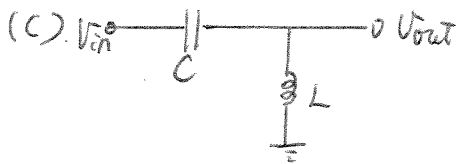
zero: No finite zero; poles =  $\pm i\sqrt{\frac{1}{LC}}$



$$V_{out} = \frac{sL}{sL + \frac{1}{sC}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{s^2 \frac{L}{C}}{s^2 + \frac{1}{LC}}$$

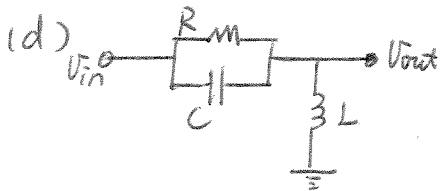zeros: Two zeros at 0; poles =  $\pm i\sqrt{\frac{1}{LC}}$




$$V_{out} = \frac{sL}{sL + R // \frac{1}{sC}} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{s(s + \frac{1}{RC}) (RC)^2}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

zeros: 0,  $-\frac{1}{RC}$
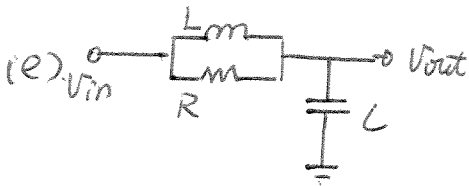
$$\text{poles} = \frac{-\frac{1}{RC} \pm \sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}}{2}$$



$$V_{out} = \frac{\frac{1}{sC}}{\frac{1}{sC} + sL // R} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{RC} (s + \frac{R}{L})}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

zero =  $-\frac{R}{L}$ ; poles =  $\frac{-\frac{1}{RC} \pm \sqrt{(\frac{1}{RC})^2 - \frac{4}{LC}}}{2}$


B.

Since  $\frac{V_{out}}{V_{in}} = \frac{1}{(s+a)(s+b)}$ , where  $a$  and  $b$

are real and positive, the transfer function contains no finite zero and two real poles on the left hand plane. But, after reviewing Problem #2 we discover that **NONE** of the networks yield this case.

(4)

(a)

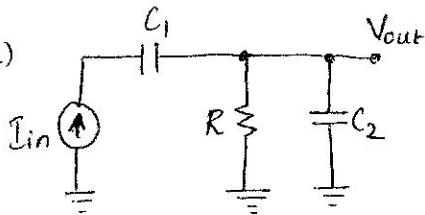


$$\frac{V_{out}}{I_{in}} = \frac{1/C_2}{s + 1/(RC_2)}$$

Zero: No finite zero

Pole:  $-1/(RC_2)$

(b)

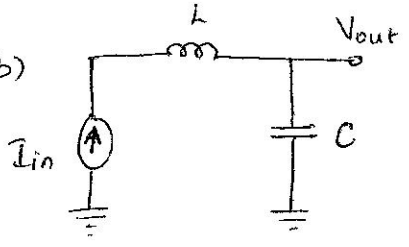


$$\frac{V_{out}}{I_{in}} = \frac{1}{sC}$$

Zero: No finite zero

Pole: 0

(c)

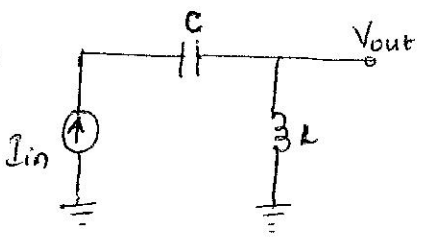


$$\frac{V_{out}}{I_{in}} = sL$$

Zero: 0

Pole: No finite Pole

(d)

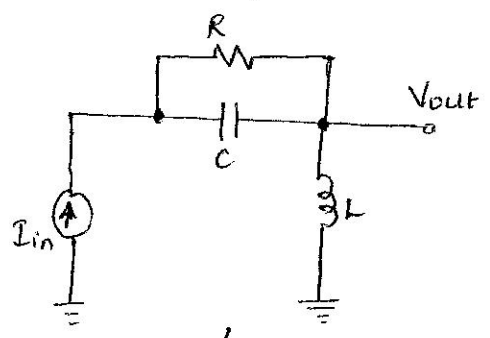


$$\frac{V_{out}}{I_{in}} = sL$$

Zero: 0

Pole: No finite Pole


(e)

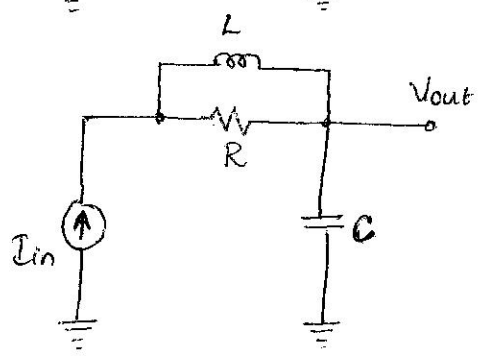

$$\frac{V_{out}}{I_{in}} = \frac{1}{sC}$$

Zero: No finite zero

Pole: 0

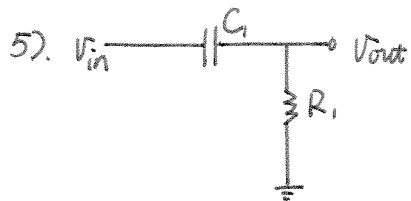

$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1 + \frac{1}{sC_1}} = \frac{s}{s + \frac{1}{R_1 C_1}}$$

$$\text{zero} = 0; \quad \text{pole} = -\frac{1}{R_1 C_1}$$

$$\frac{dP}{dC_1} = \frac{1}{(R_1 C_1)^2} \cdot \frac{1}{R_1} = \frac{1}{R_1 C_1^2}$$

$$S_{C_1}^P = \frac{\frac{dP}{P}}{\frac{dC_1}{C_1}} = \frac{dP}{dC_1} \cdot \frac{C_1}{P} = -\frac{1}{R_1 C_1^2} \cdot C_1 \cdot (R_1 C_1) = -1$$


Similarly

$$S_{R_1}^P = -1$$

As for the sensitivity of zero, since the zero is at 0, which

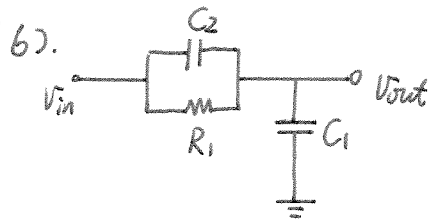is independent of  $R_1$  and  $C_1$ ,  $S_{R_1}^z = S_{C_1}^z = 0$ .





$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{sC_2}}{\frac{1}{sC_2} + R_1 \parallel \frac{1}{sC_2}}$$

$$= \frac{1}{R_1 C_2} \cdot \frac{s + \frac{1}{R_1 C_2}}{R_1 (C_1 + C_2) \left[ s + \frac{1}{R_1 (C_1 + C_2)} \right]}$$

$$\text{zero} = -\frac{1}{R_1 C_2}, \quad \text{pole} = -\frac{1}{R_1 (C_1 + C_2)}$$

$$\frac{dP}{dR_1} = [R_1 (C_1 + C_2)]^{-2} \cdot (C_1 + C_2) = -\frac{C_1 + C_2}{R_1 (C_1 + C_2)} \cdot P = -\frac{P}{R_1}$$

$$S_{R_1}^P = \frac{\frac{dP}{P}}{\frac{dR_1}{R_1}} = \frac{dP}{dR_1} \cdot \frac{R_1}{P} = -1.$$

$$\frac{dP}{dC_1} = [R_1 (C_1 + C_2)]^{-2} \cdot R_1 = -\frac{P}{C_1 + C_2}$$

$$S_{C_1}^P = \frac{\frac{dP}{P}}{\frac{dC_1}{C_1}} = \frac{dP}{dC_1} \cdot \frac{C_1}{P} = -\frac{C_1}{C_1 + C_2}$$


Conversely,

$$S_{C_2}^P = -\frac{C_2}{C_1 + C_2}.$$

From Problem 5).

$$S_{R_1}^Z = S_{C_2}^Z = -1.$$

7)

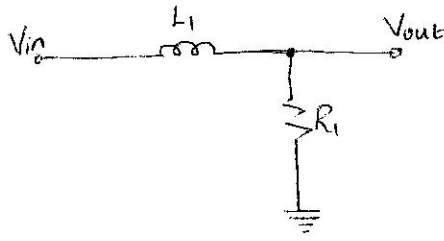

$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1 + L_1 s} = \frac{R_1/L_1}{s + R_1/L_1}$$


$$\text{Pole} = -\frac{R_1}{L_1}$$

$$dP = \frac{\partial P}{\partial R_1} \cdot dR_1 + \frac{\partial P}{\partial L_1} dL_1 = -\frac{1}{L_1} dR_1 + \frac{R_1}{L_1^2} dL_1$$

$$\Rightarrow \frac{dP}{P} = \frac{dR_1}{R_1} - \frac{dL_1}{L_1}$$

$$\left| \frac{dP}{P} \right| \leq 5\% \quad , \quad \text{and} \quad \left| \frac{dR_1}{R_1} \right| \leq 3\%$$

$$\Rightarrow \left| \frac{dL_1}{L_1} \right| \leq 2\%$$

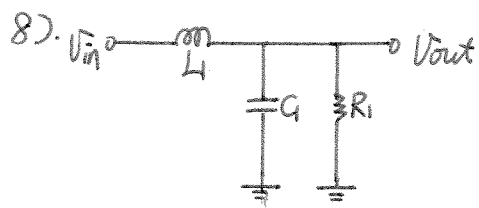

$$\begin{aligned}
 \text{a). } V_{out} &= V_{in} \cdot \frac{R_1 // \frac{1}{Cs}}{R_1 // \frac{1}{Cs} + sL} \\
 &= V_{in} \cdot \frac{\frac{R_1}{R_1Cs + 1}}{\frac{R_1}{R_1Cs + 1} + sL}
 \end{aligned}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1}{R_1Cs + 1} \cdot \frac{1}{sL + \frac{R_1}{R_1Cs + 1}} = \frac{1}{4C} \cdot \frac{1}{s^2 + \frac{1}{RC}s + \frac{1}{4C}}$$

$$\text{b). poles} = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{4C}}}{2}$$

$$\text{For them to be real} \Rightarrow \left(\frac{1}{RC}\right)^2 - \frac{4}{4C} \geq 0$$

$$\Rightarrow \frac{1}{RC} \geq \frac{2}{\sqrt{4C}}$$

14.8

(c)

$$\omega_{p1,2} = \frac{1}{2} \left[ \frac{-1}{R_1 C_1} \pm \sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}} \right]$$

$$\frac{\partial \omega_{p1,2}}{\partial R_1} = -\frac{1}{2} \left[ \frac{1}{R_1^2 C_1} \pm \frac{-2}{R_1^3 C_1^2} \frac{1/2}{\sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}} \right]$$

$$\frac{\partial \omega_{p1,2}}{\omega_{p1,2}} = \frac{-\frac{1}{2} \frac{\partial R_1}{R_1} \left[ \frac{1}{R_1 C_1} \pm \frac{-1}{R_1^2 C_1^2 \sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}} \right]}{\frac{1}{2} \left[ \frac{-1}{R_1 C_1} \pm \sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}} \right]}$$

$$\Rightarrow S_{R_1}^{\omega_{p1,2}} = - \frac{\frac{1}{R_1 C_1} \pm \frac{-1}{R_1^2 C_1^2 \sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}}}{\frac{-1}{R_1 C_1} \pm \sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}}$$

$$\frac{\partial \omega_{p1,2}}{\partial C_1} = -\frac{1}{2} \left[ \frac{1}{R_1 C_1^2} \pm \left( \frac{-2}{R_1 C_1^3} + \frac{4}{L_1 C_1^2} \right) \frac{1/2}{\sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}} \right]$$



$$\frac{\partial \omega_{p1,2}}{\omega_{p1,2}} = \frac{-\frac{1}{2} \frac{\partial C_1}{C_1} \left[ \frac{1}{R_1 C_1} \pm \left( \frac{-2}{R_1 C_1^2} + \frac{4}{L_1 C_1} \right) \frac{1/2}{\sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}} \right]}{\frac{1}{2} \left[ \frac{-1}{R_1 C_1} \pm \sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}} \right]}$$

$$\Rightarrow S_{C_1}^{\omega_{p1,2}} = - \frac{\frac{1}{R_1 C_1} \pm \left( \frac{-1}{R_1 C_1^2} + \frac{2}{L_1 C_1} \right) \frac{1}{\sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}}}{\frac{-1}{R_1 C_1} \pm \sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}}$$

$$\frac{\partial \omega_{p1,2}}{\partial L_1} = \pm \frac{1}{4} \left( \frac{4}{L_1^2 C_1} \right) \frac{1}{\sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}} \Rightarrow \frac{\partial \omega_{p1,2}}{\omega_{p1,2}} = \pm \frac{\partial L_1}{L_1} \frac{1}{L_1 C_1} \frac{1}{\sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}}$$

$$\Rightarrow S_{L_1}^{\omega_{p1,2}} = \pm \frac{\frac{1}{L_1 C_1} \frac{1}{\sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}}}{\frac{-1}{R_1 C_1} \pm \sqrt{\left(\frac{1}{R_1 C_1}\right)^2 - \frac{4}{L_1 C_1}}}$$

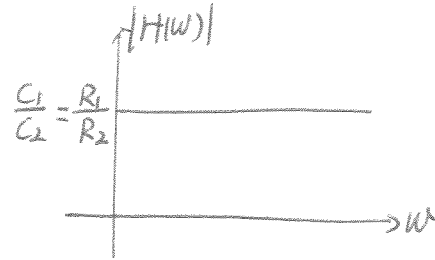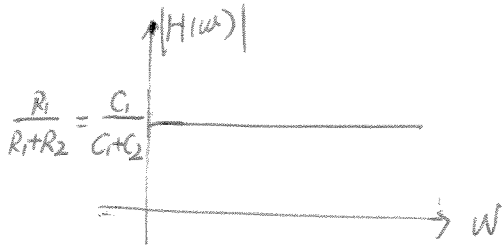9). If the zero and pole coincide, they will neutralize each other, and also render the transfer function flat.



$$10). \quad H(s) = \frac{\alpha s^2 + \beta s + \gamma}{s^2 + \frac{W_n}{Q} s + W_n^2}$$

$$P_{1,2} = -\frac{W_n}{2Q} \pm jW_n \sqrt{1 - \frac{1}{4Q^2}}$$

$$\text{If } Q = \frac{1}{2}, \text{ then } P_{1,2} = -\frac{W_n}{2Q}.$$

11.

$$|H(j\omega)|^2 = \frac{Y^2}{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2}$$

No peaking means no local minimum for  $(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2$ , which is also known as  $D(\omega)$ .

A local min exists if  $\frac{\partial D(\omega)}{\partial \omega} = 0$ .

$$\frac{\partial D(\omega)}{\partial \omega} = \left(\frac{\partial D(\omega)}{\partial \omega^2}\right) \left(\frac{\partial \omega^2}{\partial \omega}\right), \quad \frac{\partial D(\omega)}{\partial \omega^2} = -2(\omega_n^2 - \omega^2) + \left(\frac{\omega_n}{Q}\right)^2$$

$$\frac{\partial \omega^2}{\partial \omega} = 2\omega, \text{ so } \frac{\partial D(\omega)}{\partial \omega} = 2\omega \left[ -2(\omega_n^2 - \omega^2) + \left(\frac{\omega_n}{Q}\right)^2 \right] = 0$$

$$\text{Solving for } \omega, \text{ we have } \omega = 0, \pm \sqrt{\omega_n^2 - \frac{1}{2} \left(\frac{\omega_n}{Q}\right)^2}$$

Will bring  $D(\omega)$  to its min value.

At  $\omega=0$ , we have the DC value of the transfer function.

However if  $Q^2 < \frac{1}{2}$  or  $Q < \frac{1}{\sqrt{2}}$ ,  $\omega_n^2 - \frac{1}{2} \left(\frac{\omega_n}{Q}\right)^2$  becomes negative, which is not physical. Therefore, there is no peaking for  $Q < \frac{1}{\sqrt{2}}$ . And at  $Q = \frac{1}{\sqrt{2}}$ , we have  $\omega = \pm 0$ , which corresponding to the DC value of the transfer function, not peaking. Therefore, the only option left is for  $Q > \frac{1}{\sqrt{2}}$ , and that is the condition for peaking.

$$12). |H(j\omega)|^2 = \frac{\gamma^2}{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2}$$

If  $Q > \sqrt{2}/2$ , it will peak at  $\omega_0 = \omega_n \sqrt{1 - 1/(2Q)^2}$

$$H(j\omega) = \frac{\gamma}{\sqrt{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q}\omega\right)^2}}$$

$$\Rightarrow H(j\omega_0) = \frac{\gamma}{\sqrt{\left[\omega_n^2 - \left(\omega_n \sqrt{1 - \frac{1}{2Q^2}}\right)^2\right]^2 + \left(\frac{\omega_n}{Q} \omega_n \sqrt{1 - \frac{1}{2Q^2}}\right)^2}}$$


$$= \frac{\gamma}{\sqrt{\left(\omega_n^2 \cdot \frac{1}{2Q^2}\right)^2 + \frac{\omega_n^4}{Q^2} \left(1 - \frac{1}{2Q^2}\right)}}$$

$$= \frac{\gamma}{\sqrt{\frac{\omega_n^4}{4Q^4} + \frac{\omega_n^4}{Q^2} - \frac{\omega_n^4}{2Q^4}}}$$

$$= \frac{Q\gamma}{\omega^2 \sqrt{1 - \frac{1}{4Q^2}}}$$

Normalize to passband  $\Rightarrow \frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}}$

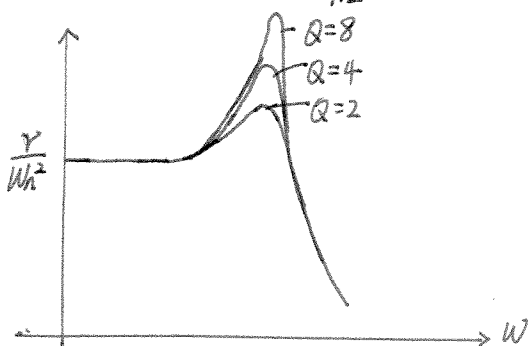$Q=2$ , peak =  $\frac{2}{\sqrt{1 - \frac{1}{4 \cdot 2^2}}} = 2.07$ ;  $Q=4$ , peak = 4.03;  $Q=8$ , peak = 8.02





13)


$$H(s) = \frac{\beta s}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2}, \quad H(j\omega) = \frac{j\beta\omega}{\omega_n^2 + j\frac{\omega_n}{Q}\omega - \omega^2}$$

$$|H(j\omega)| = \frac{\beta\omega}{\sqrt{(\omega_n^2 - \omega^2)^2 + (\frac{\omega_n\omega}{Q})^2}}$$


At  $\omega = \omega_n$ ,

$$|H(j\omega_n)| = \frac{\beta\omega_n}{\frac{\omega_n}{Q}\omega_n} = \frac{Q}{\omega_n}\beta$$

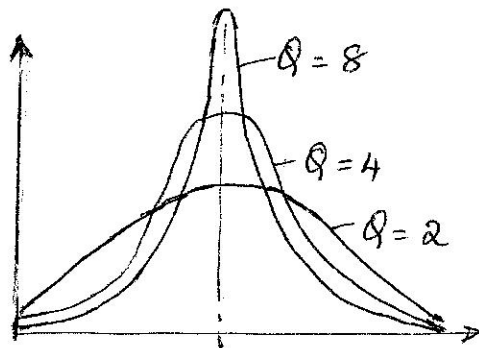
So if we normalize to  $\beta$ , we get  $\frac{Q}{\omega_n}$





14)

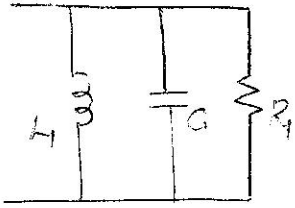

Assume  $R$  is never negative

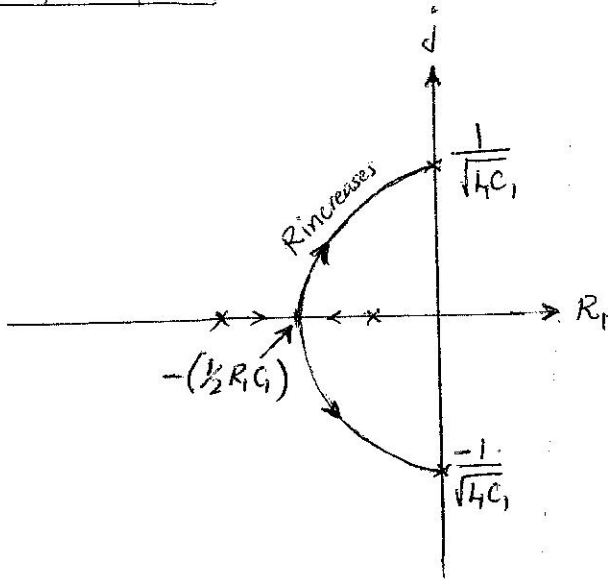

15).

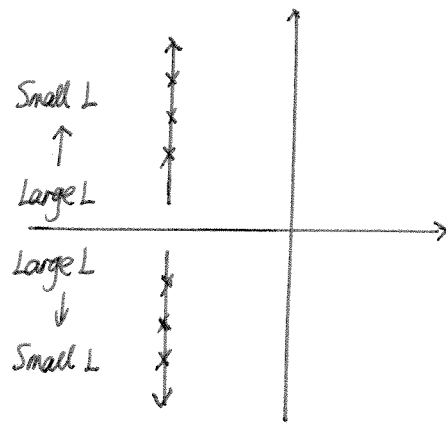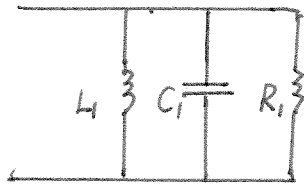

16.

$$1 \text{ dB peaking} \Rightarrow \frac{Q^2}{\left(1 - \frac{1}{4Q^2}\right)} = (1.1)^2 = 1.21$$

$$Q^2 = 1.21 \left(1 - \frac{1}{4Q^2}\right) \Rightarrow 4Q^4 - 4(1.1)^2 Q^2 + (1.1)^2 = 0$$


$$Q^2 = 0.85704, 0.35296, Q = 0.925765, 0.59410$$

$Q = 0.925765$ , since  $Q > \frac{1}{\sqrt{2}}$  for peaking

$$Q = \frac{\omega_n}{\beta} = \frac{RC}{\sqrt{LC}} = R\sqrt{\frac{C}{L}} = 0.925765$$

17.

Sallen and Key filter

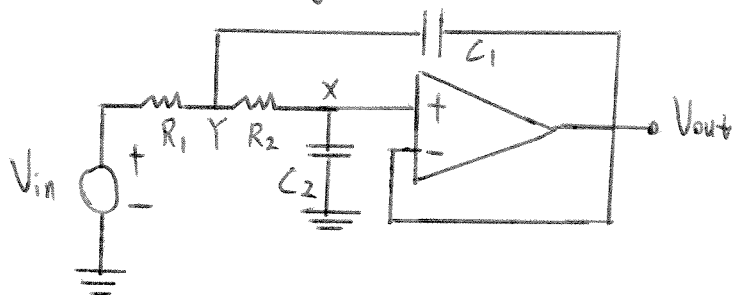

$$H(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 + R_2) C_2 s + 1}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{\frac{R_1 R_2 C_1}{C_2}}$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$H(s) = \left( s^2 + \frac{(R_1 + R_2) C_2}{R_1 R_2 C_1 C_2} s + \frac{1}{R_1 R_2 C_1 C_2} \right)^{-1}$$

$$P_{1,2} = -\frac{(R_1 + R_2)}{R_1 R_2 C_1} \pm \sqrt{\left( \frac{R_1 + R_2}{R_1 R_2 C_1} \right)^2 - \frac{4}{R_1 R_2 C_1 C_2}}$$

$$P_{1,2} = -\frac{1}{2(R_1 // R_2) C_1} \pm \sqrt{\left( \frac{1}{(R_1 // R_2) C_1} \right)^2 - \frac{4}{R_1 C_1 R_2 C_2}}$$

Assuming  $\frac{4}{R_1 C_1 R_2 C_2} > \frac{1}{[(R_1 // R_2) C_1]^2}$

$$P_{1,2} = -\frac{1}{2(R_1 // R_2) C_1} \pm j 2 \sqrt{\frac{1}{R_1 C_1 R_2 C_2} - \frac{1}{4[(R_1 // R_2) C_1]^2}}$$

17.

a)  $R_1: 0 \rightarrow \infty$


When  $R_1 = 0$ , Poles are at  $\pm\infty$ , so no finite poles. As  $R_1 \uparrow$ ,  $\frac{1}{R_1 C_1 R_2 C_2}$  approaches 0, and

$\frac{1}{4[(R_1/R_2)C_1]^2}$  approaches  $\frac{1}{4[R_2 C_1]^2}$ . There exists

a  $R_1$  such that  $\frac{1}{R_1 C_1 R_2 C_2} = \frac{1}{4[(R_1/R_2)C_1]^2} \Rightarrow$

$$P_{1,2} = -\frac{1}{2(R_1/R_2)C_1}$$

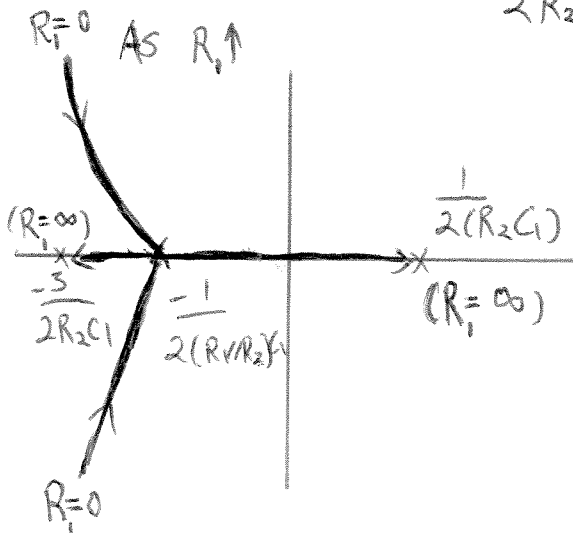As  $R_1 \rightarrow \infty$ ,  $P_{1,2} = -\frac{1}{2R_2 C_1} \pm \frac{1}{R_2 C_1} = -\frac{3}{2R_2 C_1}, \frac{1}{2R_2 C_1}$



17. b)

$R_2$  from  $0 \rightarrow \infty$

When  $R_2 = 0$ ,  $P_{1,2}$  are at  $\pm \infty$

$$\text{As } R_2 \uparrow, \frac{-1}{2(R_1 // R_2)C_1} \rightarrow -\frac{1}{2R_1C_1}$$

$$\frac{1}{R_1C_1R_2C_2} \rightarrow 0, \text{ and } \frac{1}{4[(R_1 // R_2)C_1]^2} \rightarrow \frac{1}{4[R_1C_1]^2}$$


$$\text{For a certain } R_2, \frac{1}{R_1C_1R_2C_2} = \frac{1}{4[(R_1 // R_2)C_1]^2}$$

$$\text{and } P_{1,2} = \frac{-1}{2(R_1 // R_2)C_1}$$

Finally, when  $R_2 = \infty$ ,

$$P_{1,2} = -\frac{1}{2R_1C_1} \pm 2\sqrt{\frac{1}{4[R_1C_1]^2}} = -\frac{1}{2R_1C_1} \pm \frac{1}{R_1C_1}$$
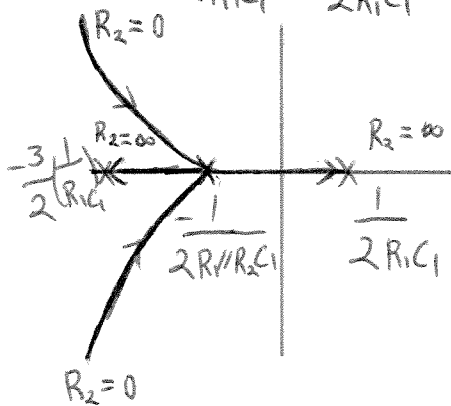
$$P_{1,2} = -\frac{3}{2} \frac{1}{R_1C_1}, \frac{1}{2R_1C_1}$$




17. c)

As  $C_1: 0 \rightarrow \infty$

When  $C_1 = 0$ , poles are at  $\pm \infty$

As  $C_1 \uparrow$ , poles approach 0.

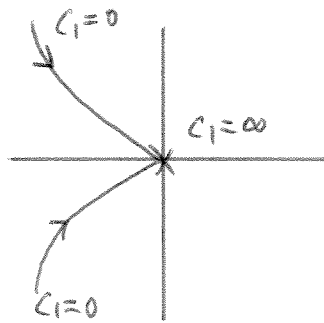


d) As  $C_2: 0 \rightarrow \infty$

When  $C_2 = 0$ , poles are at  $\pm \infty$


When  $C_2 = \infty$ , poles:  $-\frac{1}{2(R_1//R_2)C_1} \pm \frac{1}{R_1//R_2 C_1} = -\frac{3}{2} \left( \frac{1}{R_1//R_2 C_1} \right)$

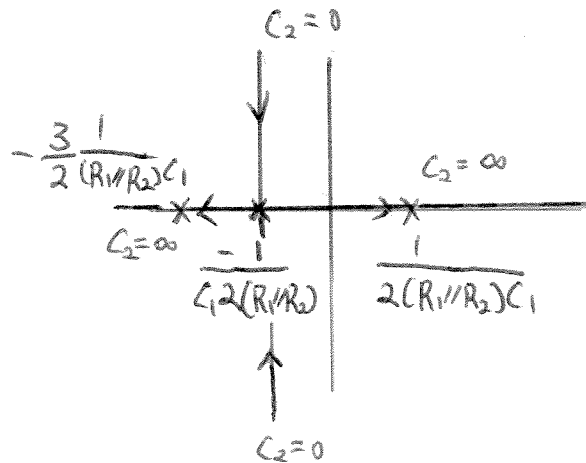$\pm \frac{1}{2 R_1//R_2 C_1}$  (note, real part doesn't depend on  $C_2$ ).





18)

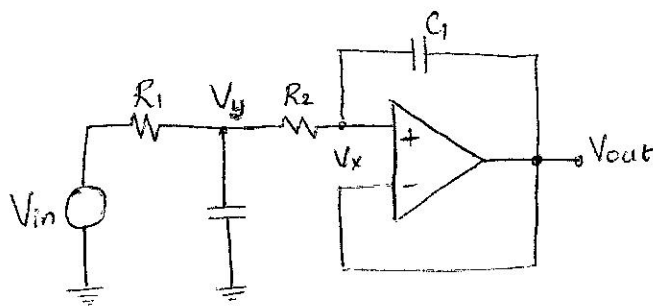


Assuming an ideal op-amp,  $V_x = V_{out}$ . Therefore, no current will flow through  $C_1$ . Moreover, since the input impedance of an op-amp (ideal) is infinite, no current will flow through  $R_2$  as well, which means  $V_y = V_x = V_{out}$

$$\Rightarrow V_y = V_{out} = \frac{1/C_2 s}{R_1 + 1/C_2 s} * V_{in}$$

Not very useful since it's only a simple single pole low-pass filter. We can implement it with passive components, instead of op-amp.

19.

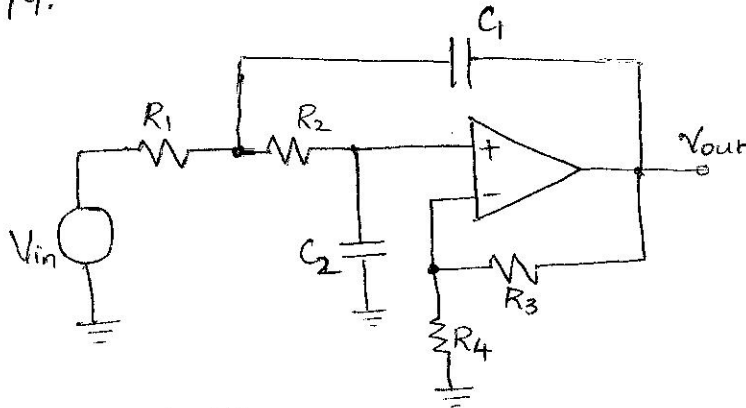

$$K = 4, \quad C_1 = C_2$$

$$Q = 4$$

$$K = 1 + \frac{R_3}{R_4} = 4 \Rightarrow \frac{R_3}{R_4} = 3, \quad \frac{C_1}{C_2} = 1$$

$$\frac{1}{Q} = \sqrt{\frac{R_1 C_1}{R_2 C_1}} + \sqrt{\frac{R_2 C_2}{R_1 C_1}} - \sqrt{\frac{R_1 C_1}{R_2 C_2}} \frac{R_3}{R_4}$$

$$\frac{1}{Q} = \sqrt{\frac{R_1}{R_2}} + \sqrt{\frac{R_2}{R_1}} - 3 \sqrt{\frac{R_1}{R_2}} \Rightarrow \sqrt{\frac{R_2}{R_1}} - 2 \sqrt{\frac{R_1}{R_2}} = \frac{1}{Q}$$

$$\frac{1}{Q} = \left(\frac{R_1}{R_2}\right)^{-1/2} - 2 \left(\frac{R_1}{R_2}\right)^{1/2} \Rightarrow \text{Squaring both sides} \Rightarrow$$

$$\frac{1}{Q^2} = 4 \left(\frac{R_1}{R_2}\right) - 4 + \left(\frac{R_1}{R_2}\right)^{-1} \Rightarrow \frac{1}{16} = 4 \left(\frac{R_1}{R_2}\right) - 4 + \left(\frac{R_2}{R_1}\right)$$

$$\left(\frac{1}{16} + 4\right) \frac{R_1}{R_2} = \frac{R_1}{R_2} \left(4 \frac{R_1}{R_2} + \frac{R_2}{R_1}\right) \Rightarrow 4.0625 \frac{R_1}{R_2} = 4 \left(\frac{R_1}{R_2}\right)^2 + 1$$

$$4 \left(\frac{R_1}{R_2}\right)^2 - 4.0625 \left(\frac{R_1}{R_2}\right) + 1 = 0, \quad \frac{R_1}{R_2} = 0.41908, \quad 0.59655$$

This leads to a negative  $Q$ .

$$S_{R_1}^Q = -\frac{1}{2} \left[ \sqrt{\frac{R_1 C_2}{R_2 C_1}} - \sqrt{\frac{R_2 C_2}{R_1 C_1}} - (K-1) \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right] Q$$

$$S_{R_1}^Q = -\frac{1}{2} \left[ \sqrt{0.41908} - \sqrt{1/0.41908} - 3 \sqrt{0.41908} \right] 4$$

$$S_{R_1}^Q = 5.68$$

20)

$$H(s) = \frac{1}{R_1 R_2 C_1 C_2 s^2 + (R_1 + R_2) C_2 s + 1}$$

$$Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$\frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}} = 1.122 \Rightarrow Q^2 = (1.122)^2 \left(1 - \frac{1}{4Q^2}\right)$$

$$\Rightarrow 3.3058Q^4 - 4Q^2 + 1 = 0$$

$$Q^2 = 0.85704, 0.35296$$

$$Q = \pm 0.925765, \pm 0.5941$$

In order to peak,  $Q > \frac{1}{\sqrt{2}} \Rightarrow Q = 0.925765$

$$\Rightarrow \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}} = 0.925765$$

$$\text{let } \frac{C_1}{C_2} = 1 \Rightarrow \frac{1}{R_1 + R_2} \sqrt{R_1 R_2} = 0.925765$$

$$\Rightarrow R_1 R_2 = (0.925765)^2 (R_1 + R_2)^2$$

$$\frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2 = 0.85704 (R_1 + R_2)$$

$$R_1 \parallel R_2 = 0.85704 (R_1 + R_2)$$

Only if  $\frac{C_1}{C_2} = 1$

21)


$$S_{R_1}^Q = 2, \quad C_2 = C_1, \quad Q = f\left(\sqrt{\frac{R_2}{R_1}}\right)$$

Range of  $Q$  and  $\sqrt{R_2/R_1}$

$$S_{R_1}^Q = -\frac{1}{2} \left[ \sqrt{\frac{R_1 C_2}{R_2 C_1}} - \sqrt{\frac{R_2 C_2}{R_1 C_1}} - (K-1) \sqrt{\frac{R_1 C_1}{R_2 C_2}} \right] Q$$

$$S_{R_1}^Q = -\frac{1}{2} + Q \sqrt{\frac{R_2 C_2}{R_1 C_1}} \Rightarrow 2 = -\frac{1}{2} + Q \sqrt{\frac{R_2}{R_1}}$$
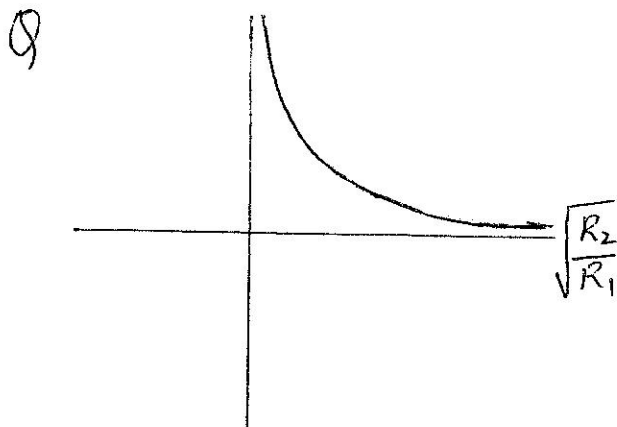
$$\Rightarrow 2.5 = Q \sqrt{\frac{R_2}{R_1}}, \quad Q = \frac{2.5}{\sqrt{R_2/R_1}}$$




$\left(\frac{R_2}{R_1}\right)$  can't be negative

Range:  $0 < Q < \infty$

$$0 < \sqrt{\frac{R_2}{R_1}} < \infty$$

If the transfer function does not want to experience peaking, then  $0 < Q \leq \frac{1}{\sqrt{2}} \Rightarrow 3.5356 \leq \sqrt{\frac{R_2}{R_1}} < \infty$

22.

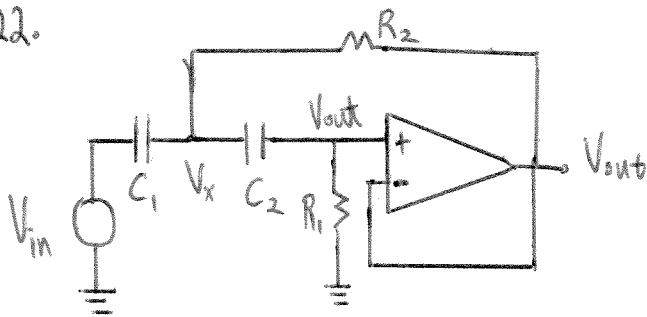

Assuming an ideal  
op amp.

$$1) (V_x - V_{in})C_1 s + (V_x - V_{out})\left(C_2 s + \frac{1}{R_2}\right) = 0, \text{ nodal equation at } V_x.$$

$$2) (V_x - V_{out})C_2 s - \frac{V_{out}}{R_1} = 0, \text{ nodal equation at } V_{out}.$$

$$2) \Rightarrow V_x = V_{out} \left[ \frac{C_2 s + 1/R_1}{C_2 s} \right] \quad (A) \quad \text{The stuff in the bracket becomes "A"}$$

$$1) \Rightarrow (A V_{out} - V_{in})C_1 s + (A V_{out} - V_{out})\left[C_2 s + \frac{1}{R_2}\right] = 0$$

$$\Rightarrow A V_{out} C_1 s + V_{out} (A-1) (C_2 s + 1/R_2) = V_{in} C_1 s$$

$$A-1 = \frac{1}{R_1 C_2 s}, \quad A = \frac{C_2 s + 1/R_1}{C_2 s}$$

substitute (A-1) and A into 1)  $\Rightarrow$

$$\left(\frac{C_2 s + 1/R_1}{C_2 s}\right) C_1 s V_{out} + \left(C_2 s + \frac{1}{R_2}\right) \frac{1}{R_1 C_2 s} V_{out} = V_{in} C_1 s$$

22.

$$\frac{V_{out}}{V_{in}} = \frac{C_1 S}{\frac{C_1}{C_2} \left( C_2 S + \frac{1}{R_1} \right) + \frac{1}{R_1 C_2 S} \left( C_2 S + \frac{1}{R_2} \right)}$$

Rearranging

$$H(s) = \frac{V_{out}}{V_{in}} = \frac{S^2}{S^2 + \left( \frac{C_1 + C_2}{C_2 R_1 C_1} \right) S + \frac{1}{R_2 C_2 R_1 C_1}}$$

$$\omega_n^2 = \frac{1}{R_2 C_2 R_1 C_1}, \quad Q = \frac{C_1 + C_2}{C_2 R_1 C_1}$$

$$\omega_n = \frac{1}{\sqrt{R_2 C_2 R_1 C_1}}, \quad Q = \sqrt{\frac{C_2 C_1 R_1}{R_2}} \left( \frac{1}{C_1 + C_2} \right)$$

23.

$$Q = \frac{1}{C_1 + C_2} \sqrt{\frac{C_2 C_1 R_1}{R_2}} \Rightarrow \frac{1}{Q} = (C_1 + C_2) \sqrt{\frac{R_2}{C_2 C_1 R_1}}$$

$$1) \frac{d}{dQ} \left[ \frac{1}{Q} \right] = -\frac{1}{Q^2} \Rightarrow d \left[ \frac{1}{Q} \right] = -\frac{1}{Q^2} dQ$$

$$2) \frac{d \left[ \frac{1}{Q} \right]}{dR_2} = \frac{1}{2} \frac{C_1 + C_2}{\sqrt{C_2 C_1 R_1 R_2}} \Rightarrow d \left[ \frac{1}{Q} \right] = \frac{1}{2} \frac{C_1 + C_2}{\sqrt{C_2 C_1 R_1 R_2}} dR_2$$

Equating 1) and 2) and multiple 2) by  $\frac{R_2}{R_2}$

$$-\frac{dQ}{Q^2} = \frac{1}{2} \frac{(C_1 + C_2) R_2}{\sqrt{C_2 C_1 R_1 R_2}} \frac{dR_2}{R_2}$$

$$\frac{dQ}{Q} / \frac{dR_2}{R_2} = -\frac{Q}{2} \frac{(C_1 + C_2)}{\sqrt{C_1 C_2 R_1}} \sqrt{\frac{R_2}{R_2}}$$

$$S_{R_2}^Q = -\frac{Q}{2} \frac{(C_1 + C_2)}{\sqrt{C_1 C_2 R_1}} = -\frac{1}{2}$$

$$\frac{1}{Q} = (C_1 + C_2) \sqrt{\frac{R_2}{C_2 C_1 R_1}} = C_1 \sqrt{\frac{R_2}{C_2 C_1 R_1}} + C_2 \sqrt{\frac{R_2}{C_2 C_1 R_1}}$$

$$\frac{\partial \left( \frac{1}{Q} \right)}{\partial C_1} = \frac{1}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} - \frac{C_2}{2 C_1} \sqrt{\frac{R_2}{C_2 R_1 C_1}}, \quad \frac{d \left( \frac{1}{Q} \right)}{dQ} = -\frac{1}{Q^2}$$

$$\text{Rearranging} \Rightarrow -\frac{\partial Q}{Q^2} = \frac{\partial C_1}{C_1} \left( \frac{C_1 - C_2}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

$$\frac{\partial Q}{Q} / \frac{\partial C_1}{C_1} = S_{C_1}^Q = -Q \left( \frac{C_1 - C_2}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

23.

Similarly:

$$S_{C_2}^R = -R \left( \frac{C_2 - C_1}{2} \sqrt{\frac{R_2}{C_2 R_1 C_1}} \right)$$

$$S_{R_1}^R = R \left( \frac{C_1 + C_2}{2} \sqrt{\frac{R_2}{C_2 C_1 R_1}} \right) = \frac{1}{2}$$



24.

$$\frac{V_{out}(s)}{V_{in}} = \frac{\alpha s^2}{s^2 + \frac{\omega_n s}{Q} + \omega_n^2}$$


Cross-multiply.

$$V_{out} s^2 + V_{out} \frac{\omega_n s}{Q} + V_{out} \omega_n^2 = V_{in} \alpha s^2$$

Rearranging

$$V_{out} = V_{in} \frac{\alpha}{\omega_n^2} s^2 - V_{out} \frac{s^2}{\omega_n^2} - V_{out} \frac{s}{Q \omega_n}$$

Block diagram:

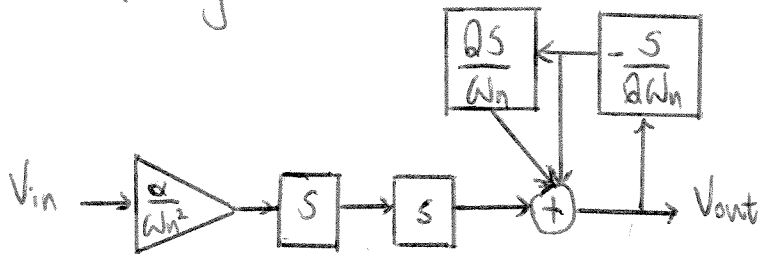

25.

$$Q = 2, \omega_n = (2\pi)(2 \times 10^6)$$

$$R_6 = R_3, R_1 = R_2, C_1 = C_2$$

$$100 \text{ pF} < \text{Total } C < 1 \text{ nF}, \quad 1 \text{ k}\Omega < \text{Total } R < 50 \text{ k}\Omega$$

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right), \quad \omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\text{Since } R_6 = R_3 \Rightarrow \omega_n^2 = \left( \frac{1}{R_1 C_1} \right)^2 = (2\pi \times 2 \times 10^6)^2$$

$$\frac{1}{R_1 C_1} = 2\pi \times 2 \times 10^6 = \omega_n$$

$$Q = \frac{R_4 + R_5}{R_4} = 2 \Rightarrow R_5 = R_4$$

$$\text{Let } C_1 = C_2 = 100 \text{ pF}, \quad R_1 = \frac{1}{(2\pi)(2 \times 10^6)(100 \text{ pF})} = 795.77 \Omega$$

$$\text{So } R_1 = R_2 = 795.77 \Omega, \quad C_1 = C_2 = 100 \text{ pF.}$$

Since  $R_3, R_4, R_5, R_6$  don't affect  $Q$  and  $\omega_n$ ,  
let them be  $500 \Omega$  each.

$$\text{Total } R: (4)(500) + (2)(795.77) = 3.6 \text{ k}\Omega$$

$$\text{Total } C: 100 \text{ pF} + 100 \text{ pF} = 200 \text{ pF.}$$

26.


$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \frac{1}{R_1 C_1}, \quad \omega_n^2 = \frac{R_6}{R_3} \cdot \frac{1}{R_1 R_2 C_1 C_2}$$

$$Q = \omega_n \left( \frac{R_4 + R_5}{R_4} \right) R_1 C_1, \quad \omega_n = \sqrt{\frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)}$$

$$Q = \sqrt{\frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)} \left( \frac{R_4 + R_5}{R_4} \right) R_1 C_1$$

$$Q = \sqrt{\frac{R_6}{R_3}} \sqrt{\frac{R_1 C_1}{R_2 C_2}} \left( \frac{R_4 + R_5}{R_4} \right)$$

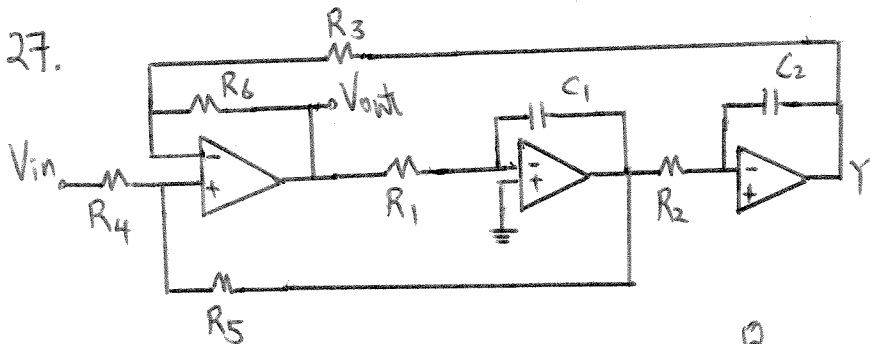If  $R_6 = R_3$ ,  $Q$  doesn't depend on  $R_6$  and  $R_3$ ,  
hence zero sensitivity.



Low pass, low freq gain of 2.  $S_{R_3, R_6}^Q = 0$

$$\frac{V_Y}{V_{in}} = \left( \frac{\alpha S^2}{S^2 + \frac{\omega_n}{Q} S + \omega_n^2} \right) \left( \frac{1}{R_1 R_2 C_1 C_2 S^2} \right) \quad \text{Low pass transfer function}$$

Low freq gain:  $\frac{\alpha}{\omega_n^2 R_1 R_2 C_1 C_2}$ , where  $\alpha = \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right)$

and  $\omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$

Therefore, low freq gain:  $\frac{\alpha}{\frac{R_6}{R_3}} = \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) \left( \frac{R_3}{R_6} \right)$

$$S_{R_3, R_6}^Q = \frac{Q}{2} \frac{|R_3 - R_6|}{1 + R_5/R_4} \sqrt{\frac{R_2 C_2}{R_3 R_6 R_1 C_1}}$$

To obtain  $S_{R_3, R_6}^Q = 0$ ,  $R_3 = R_6$ , however this makes the low freq gain:  $2 \left( \frac{R_5}{R_4 + R_5} \right) \neq 2$ .

Therefore, it's impossible a low freq gain of 2 if  $S_{R_3, R_6}^Q = 0$ .

28.

Peaking: 1 dB,  $R_3 = R_6$

Normalized Peak Value:  $\frac{Q}{\sqrt{1 - (4Q^2)^{-1}}} = 1.01$

solving for  $Q^2$ :  $0.8570, 0.3880$  (not possible for peaking)

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right), \left( \frac{\omega_n}{Q} \right)^2 = \left( \frac{R_4}{R_4 + R_5} \right)^2 \left( \frac{1}{R_1 C_1} \right)^2$$

$$\omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right) = \frac{1}{R_1 R_2 C_1 C_2} \quad (\text{since } R_6 = R_3)$$

$$\text{Therefore, } Q^2 = \left( \frac{R_1 C_1}{R_2 C_2} \right) \left( \frac{R_4 + R_5}{R_4} \right)^2 = 0.8570$$

$$\text{Low pass gain: } 2 \frac{R_5}{R_4 + R_5} = \alpha \quad (\text{since } R_6 = R_3)$$


$$\text{So } \frac{\alpha}{2} = \frac{R_5}{R_4 + R_5}, \frac{R_4}{R_4 + R_5} = 1 - \frac{\alpha}{2} \Rightarrow \frac{R_4 + R_5}{R_4} = \left( 1 - \frac{\alpha}{2} \right)^{-1}$$

$$\text{So } \left( \frac{R_1 C_1}{R_2 C_2} \right) \left( 1 - \frac{\alpha}{2} \right)^{-2} = 0.8570, \text{ if } \alpha = 1 \Rightarrow \frac{R_1 C_1}{R_2 C_2} = 0.214.$$

However, can't go down any further without knowing

more information.

29.

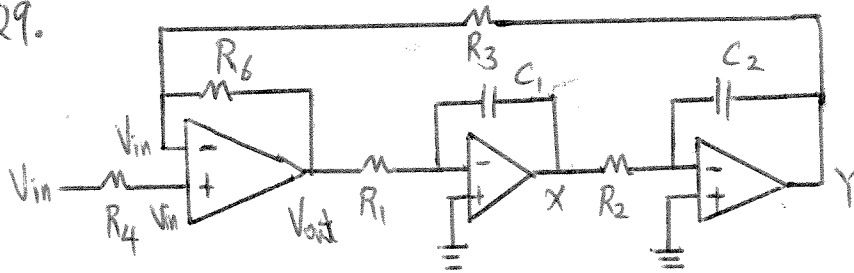

$$V_x = -\frac{V_{out}}{R_1} \left( \frac{1}{C_1 s} \right), \quad V_Y = -\frac{V_x}{R_2} \left( \frac{1}{C_2 s} \right), \quad V_{out} = V_{in} - \frac{(V_Y - V_{in}) R_6}{R_3}$$

$$\text{Substituting } V_x \text{ into } V_Y \Rightarrow V_Y = \frac{V_{out}}{R_1} \left( \frac{1}{C_1 s} \right) \left( \frac{1}{R_2 C_2 s} \right)$$

Substituting  $V_Y$  into  $V_{out}$  and rearranging:

$$\frac{V_{out}}{V_{in}} = \frac{(R_1 C_1)(R_2 C_2) s^2 \left( 1 + \frac{R_6}{R_3} \right)}{(R_1 C_1)(R_2 C_2) s^2 + \frac{R_6}{R_3}}$$

$$\frac{V_{out}}{V_{in}} = \frac{s^2 \left( 1 + \frac{R_6}{R_3} \right)}{s^2 + \frac{R_6}{R_3} \left( \frac{1}{R_1 C_1 R_2 C_2} \right)}$$


Simplifying

$$\omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 C_1 R_2 C_2} \right), \quad Q = \infty$$

$$\alpha = \left( 1 + \frac{R_6}{R_3} \right)$$

30.

TOW-Thomas Biquad:

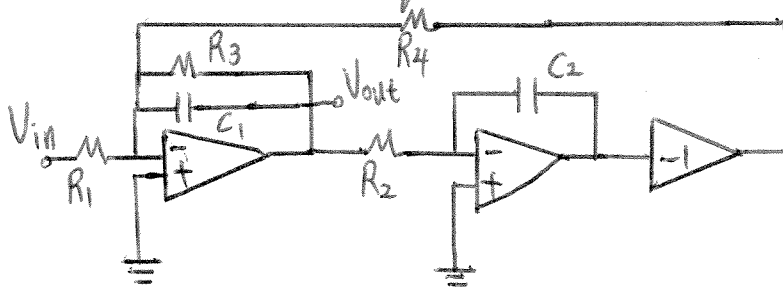

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q^{-1} = \frac{1}{R_3} \sqrt{\frac{R_2 R_4 C_2}{C_1}}$$

$$\frac{\partial \omega_n}{\partial R_2} = -\frac{1}{2} \frac{1}{R_2 \sqrt{R_2 R_4 C_1 C_2}} = -\frac{1}{2} \frac{\omega_n}{R_2}$$

$$\frac{\partial \omega_n}{\omega_n} / \frac{\partial R_2}{R_2} = S_{R_2}^{\omega_n} = -\frac{1}{2}$$

Since  $R_2, R_4, C_1, C_2$  are equivalent in  $\omega_n$ 's definition, all of their sensitivities =  $-\frac{1}{2}$

Sensitivities of  $Q$ :

$$\frac{\partial Q}{\partial R_3} = \frac{1}{\sqrt{R_2 R_4 C_2}} \left( \frac{R_3}{R_3} \right) \Rightarrow \frac{\partial Q}{Q} = \frac{\partial R_3}{R_3} \Rightarrow S_{R_3}^Q = 1$$

$$\frac{\partial Q}{\partial C_1} = \frac{1}{2} R_3 \left( \frac{C_1}{R_2 R_4 C_2} \right)^{-\frac{1}{2}} \left( \frac{1}{R_2 R_4 C_2} \right) \frac{C_1}{C_1} \Rightarrow \frac{\partial Q}{Q} = \frac{1}{2} \frac{\partial C_1}{C_1} \Rightarrow S_{C_1}^Q = \frac{1}{2}$$

$$\frac{\partial Q}{\partial R_2} = -\frac{1}{2} R_3 \left( \frac{C_1}{R_2 R_4 C_2} \right)^{-\frac{1}{2}} \frac{C_1}{R_4 C_2} \left( \frac{1}{R_2^2} \right) \Rightarrow \frac{\partial Q}{Q} = -\frac{1}{2} \frac{\partial R_2}{R_2} \Rightarrow S_{R_2}^Q = -\frac{1}{2}$$

30.

Since  $R_2, R_4$  and  $C_2$  are equivalent in the expression

$$S_{R_2, R_4, C_2}^Q = -\frac{1}{2}$$


$$\text{So, } S_{R_2, R_4, C_1, C_2}^{\omega_1} = -\frac{1}{2}, \quad S_{R_1, R_3}^{\omega_1} = 0$$

$$S_{R_2, R_4, C_2}^Q = -\frac{1}{2}, \quad S_{C_1}^Q = \frac{1}{2}, \quad S_{R_3}^Q = 1$$

$$S_{R_1}^Q = 0$$



31.

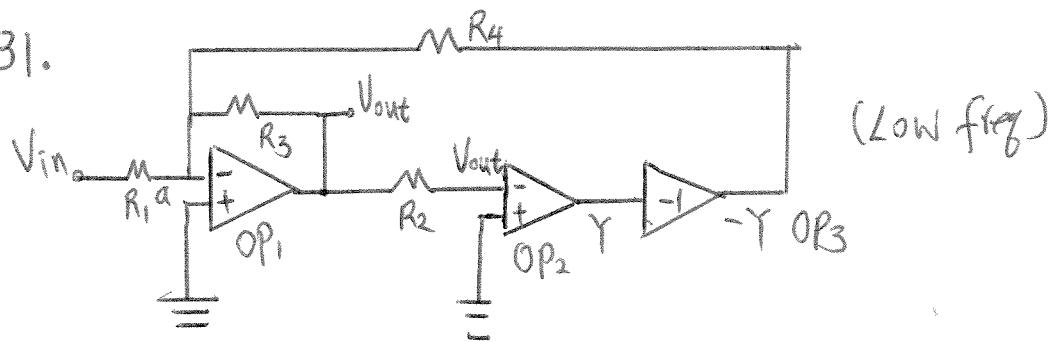

$V_{out}$  equals zero because of OP2's negative feedback.

Likewise,  $V_a$  equals to zero as well.

So, summing all the currents thru  $R_3$ , we have

$$-\left(\frac{0 - V_Y}{R_4} + \frac{V_{in}}{R_1}\right) R_3 = V_{out} = 0$$

$$\Rightarrow \frac{V_{in}}{R_1} = \frac{V_Y}{R_4} \Rightarrow \frac{V_Y}{V_{in}} = \frac{R_4}{R_1}$$

32.

$$\frac{V_Y}{V_{in}} = \frac{R_3 R_4}{R_1} \left( \frac{1}{R_2 R_3 R_4 C_1 C_2 S^2 + R_2 R_4 C_2 S + R_3} \right)$$

$$\omega_n = (2\pi)(10 \text{ MHz}), \quad R_3 = 1\text{K}, \quad R_2 = R_4, \quad C_1 = C_2$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = \frac{1}{R_3} \sqrt{\frac{R_2 R_4 C_2}{C_1}}$$

Peaking: 1dB

$$\frac{Q}{\sqrt{1 - (4Q^2)^{-1}}} = 1.1, \quad Q^2 = 0.8570$$


$$\omega_n = \frac{1}{\sqrt{(R_2 C_1)^2}} = (2\pi)(10 \times 10^6) \Rightarrow \frac{1}{R_2 C_1} = (2\pi)(10 \times 10^6)$$

$$\frac{1}{Q} = \frac{1}{1000} \sqrt{R_2^2} = \frac{1}{Q} = \frac{R_2}{1000} \Rightarrow \begin{array}{l} R_2 = 1166.860 \text{ ohm} \\ R_2 = 1.2 \text{ K}\Omega \end{array}$$

Solving for  $C_1$  we have:  $C_1 = 13.64 \text{ pf}$ .

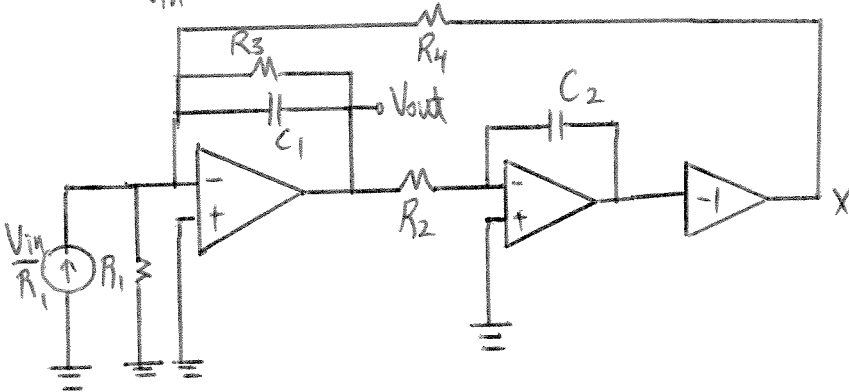33.

$$\frac{V_Y}{V_{in}} = \frac{R_3 R_4}{R_1} \left( \frac{1}{R_2 R_3 R_4 C_1 C_2 S^2 + R_2 R_4 C_2 S + R_3} \right)$$



When  $R_1$  and  $V_{in}$  are replaced with its Norton equivalent, we see that the "upper" terminal of  $R_1$  is at virtual ground. Since  $R_1$ 's two terminals are at the same potential, no current will flow through it, therefore it can be seen as an open. So  $R_1$  is not in the signal path, and therefore will not affect the frequency response. However, since its magnitude is embedded in the Norton current source, it will affect the DC gain.

34.


$$Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4} \quad (\text{for circuit diagram, please refer to Problem \# 35})$$

For  $Z_{in}$  to be inductive, the following combinations will work.

<u>1</u>	<u>2</u>	<u>3</u>
$Z_5 = R$	$Z_5 = R$	$Z_5 = R$
$Z_4 = R$	$Z_4 = C$	$Z_4 = C$
$Z_3 = R$	$Z_3 = R$	$Z_3 = R$
$Z_2 = C$	$Z_2 = C$	$Z_2 = R$
$Z_1 = R$	$Z_1 = C$	$Z_1 = R$

Any other combination will result in DC path blockage at a node. Moreover, in #2 it's assumed that the input can provide a DC bias.

35.

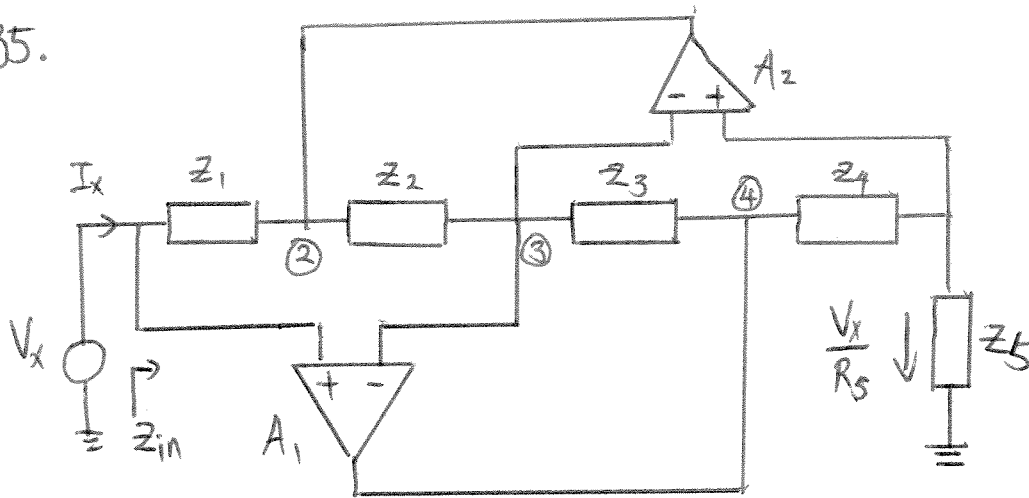

$$z_{in} = \frac{z_1 z_3 z_5}{z_2 z_4}$$

For  $z_{in}$  to be Capacitive, the following combinations can be used.

<u>1</u>	<u>2</u>	<u>3</u>	<u>4</u>	<u>5</u>
$z_5 = C$	$z_5 = C$	$z_5 = R$	$z_5 = R$	$z_5 = R$
$z_4 = R$	$z_4 = R$	$z_4 = R$	$z_4 = R$	$z_4 = C$
$z_3 = R$	$z_3 = R$	$z_3 = R$	$z_3 = C$	$z_3 = C$
$z_2 = R$	$z_2 = C$	$z_2 = R$	$z_2 = R$	$z_2 = R$
$z_1 = R$	$z_1 = C$	$z_1 = C$	$z_1 = R$	$z_1 = C$

Any other combination results in a DC path blockage at a node. Moreover, in # 2, 3, 5, it is assumed that the input node will produce a DC bias.

36.

$$z_{in} = \frac{z_1 z_3 z_5}{z_2 z_4}$$

$$z_5 = R_x + \frac{1}{Cs}, \quad z_4 = R_x, \quad z_3 = R_x, \quad z_2 = R_x,$$

$$z_1 = \frac{1}{Cs}$$

$$z_{in} = \frac{\frac{R_x}{Cs} (R_x + \frac{1}{Cs})}{R_x^2} = \frac{1}{Cs R_x} (R_x + \frac{1}{Cs})$$

$$z_{in} = \frac{1}{Cs} + \frac{1}{Cs^2 R_x}$$

$$V_{out} = \frac{V_{in} [s^2 [C^2 R_x] + Cs]}{[s^2 [C^2 R_x] + sC + R_1 [s^3 C^3 R_x]}$$

$$\frac{V_{out}}{V_{in}} = \frac{sC R_x + 1}{s^2 R_1 R_x C^2 + sC R_x + 1}$$

37. 
$$Z_{in} = \frac{Z_1 Z_3 Z_5}{Z_2 Z_4}$$
 (for circuit diagram, please refer to problem # 35)

Let  $Z_5$  be a capacitor,  $Z_2$  and  $Z_4$  be large resistors and  $Z_1$  and  $Z_3$  be small resistors compared to  $Z_2$  and  $Z_4$ .

For example, let  $Z_1$  and  $Z_3$  equal  $50\Omega$  and  $Z_2$  and  $Z_4$  equal  $5k\Omega$ . Then there's a  $(100)^2 = 10000$  multiplication factor onto  $C_5$ .

38.

Butterworth filter: roll-off of 1dB @  $\omega = 0.9\omega_0$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (0.9)^{2n}}} = 0.9 \Rightarrow 2n = \frac{\log(0.2345679)}{\log(0.9)}$$

$$n = 6.88$$


So we need a 7th order.



39.

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (0.9)^{2n}}}$$

$n=0$	$\Rightarrow$	$-3 \text{ dB}$
$n=1$	$\Rightarrow$	$-2.577 \text{ dB}$
$n=3$	$\Rightarrow$	$-1.851 \text{ dB}$
$n=5$	$\Rightarrow$	$-1.299 \text{ dB}$
$n=7$	$\Rightarrow$	$-0.895 \text{ dB}$
$n=9$	$\Rightarrow$	$-0.607 \text{ dB}$
$n=11$	$\Rightarrow$	$-0.408 \text{ dB}$
$n=13$	$\Rightarrow$	$-0.272 \text{ dB}$
$n=15$	$\Rightarrow$	$-0.180 \text{ dB}$

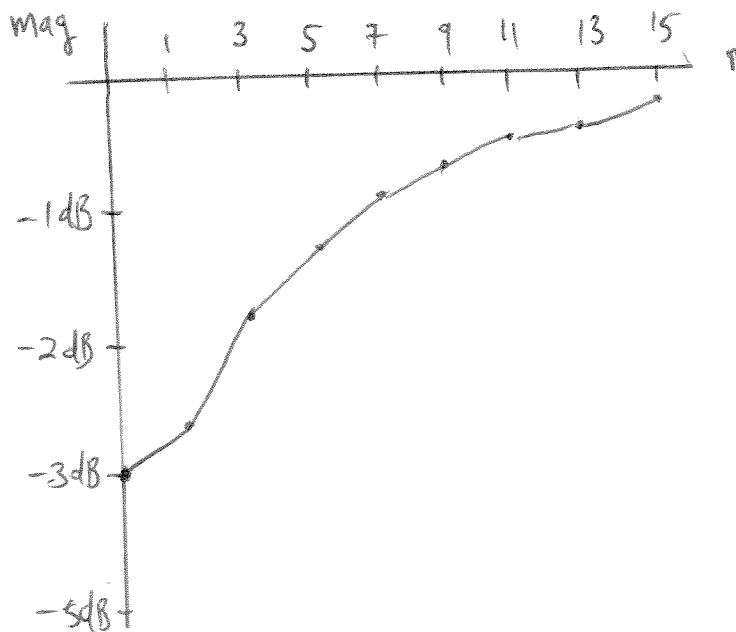

40.

$1.1W_0$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (1.1)^{2n}}} = 0.1 \Rightarrow 2n = \frac{\log(99)}{\log(1.1)}$$

$n = 24.106$  so needs  $n = 25$ .

$n=0 \Rightarrow -3 \text{ dB}$

$n=1 \Rightarrow -3.4439 \text{ dB}$

$n=3 \Rightarrow -4.427 \text{ dB}$

$n=5 \Rightarrow -5.555 \text{ dB}$


$n=7 \Rightarrow -6.810 \text{ dB}$


$n=9 \Rightarrow -8.169 \text{ dB}$

$n=11 \Rightarrow -9.61 \text{ dB}$

$n=13 \Rightarrow -11.112 \text{ dB}$

$n=15 \Rightarrow -12.66 \text{ dB}$

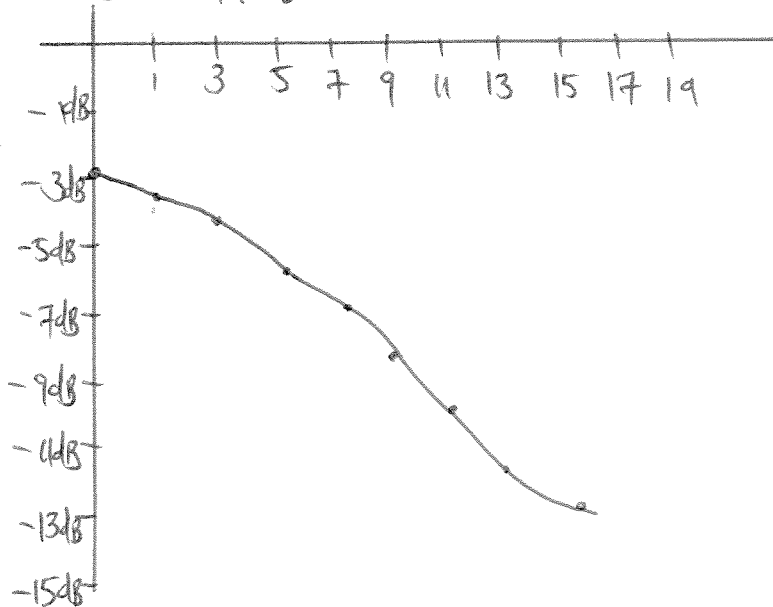

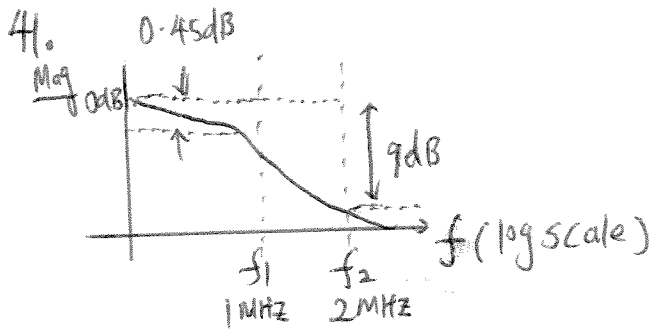

$$|H(f)| = \frac{1}{\left(1 + \left(\frac{2\pi f}{\omega_0}\right)^6\right)^{\frac{1}{2}}}$$

$$|H(5\text{MHz})| = 0.02438$$

$$\text{Suppression: } 20 \log(0.02438) = -32.26 \text{ dB}$$

42.

Low-pass Butterworth: Passband flatness of 0.5 dB  
 $f_1 = 1 \text{ MHz}$ ,  $f_2 = 2 \text{ MHz}$ , order  $< 5$

$$-0.5 \text{ dB} = 20 \log(x) \Rightarrow x = 0.944$$

$$|H(\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_0}\right)^{2n}}} = 0.944 \Rightarrow \frac{1}{\left(1 + \left(\frac{1}{f_0}\right)^{2n}\right)} = (0.944)^2$$

@  $f = 1 \text{ MHz}$

$$\Rightarrow 1 + \frac{1}{(f_0)^{2n}} = \frac{1}{(0.944)^2} \Rightarrow f_0 = 10^{\frac{0.91306}{2n}}$$

for  $n=1$ ,  $f_0 \approx 2.86 \text{ MHz}$

for  $n=5$ ,  $f_0 \approx 1.234 \text{ MHz}$

Therefore, for greatest attenuation  $n=5$

$$\text{So } H(2 \text{ MHz}) = \frac{1}{\sqrt{1 + \left(\frac{2}{1.234}\right)^{10}}} = 0.089$$


$$20 \log(0.089) = -21.0 \text{ dB at } n=5$$

43.

$$P_k = \omega_0 \exp\left(\frac{j\pi}{2}\right) \exp\left(j \frac{2k-1}{2n} \pi\right), \quad k=1, 2, \dots, n$$

The poles lie on a circle because all of their magnitude, which is the distance from the origin to the poles, are the same ( $\omega_0$ ) with each  $k$ ; only the phase, which is the angle the poles make with the positive real axis, differ. Therefore, a circle is formed.

44.

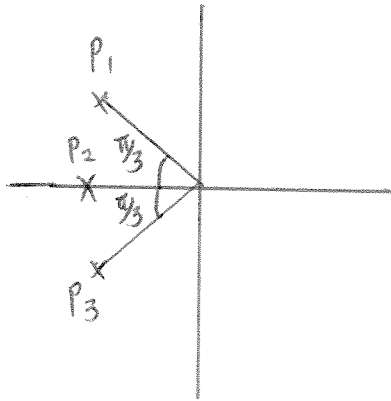

$$P_1 = 2\pi(1.45 \text{ MHz}) \left[ \cos\left(\frac{2\pi}{3}\right) + j \sin\left(\frac{2\pi}{3}\right) \right]$$

$$P_2 = (2\pi)(1.45 \text{ MHz})$$

$$P_3 = (2\pi)(1.45 \text{ MHz}) \left[ \cos\left(\frac{2\pi}{3}\right) - j \sin\left(\frac{2\pi}{3}\right) \right]$$

$$H(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{[2\pi(1.45 \text{ MHz})]^2}{s^2 - [4\pi(1.45 \text{ MHz}) \cos\left(\frac{2\pi}{3}\right)]s + [2\pi(1.45 \text{ MHz})]^2}$$

KHN Low pass Transfer function:

$$\frac{\alpha s^2}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2} \cdot \frac{1}{R_1 R_2 C_1 C_2 s^2} = \frac{\alpha / (R_1 R_2 C_1 C_2)}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2}$$

$$\frac{\alpha}{R_1 R_2 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2, \quad \omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right) = [2\pi \times 1.45 \times 10^6]^2$$

$$\frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right) = -(4\pi \times 1.45 \times 10^6 \times \cos\left(\frac{2\pi}{3}\right))$$

$$\frac{\alpha}{R_1 R_2 C_1 C_2} = \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$$

Let  $R_6 = R_3$ ,  $R_2 = 4R_1$ ,  $C_1 = C_2$ 

$$\omega_n^2 = \left( \frac{1}{4R_1 C_1} \right)^2 = (2\pi \times 1.45 \times 10^6)^2 \Rightarrow \frac{1}{2R_1 C_1} = 2\pi \times 1.45 \times 10^6$$

44.

Let  $R_1 = 5K \Rightarrow C_1 = 10.98pf$ ,  $R_2 = 20K$ ,  $C_2 = 10.98pf$

$$\frac{\omega_H}{Q} = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right) = 9110618.7$$

$$\Rightarrow \frac{R_4}{R_4 + R_5} = \frac{1}{2}$$


$$\frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) \left( \frac{1}{R_1 R_2 C_1 C_2} \right) = \left( \frac{1}{2} \right) (2) (2\pi \times 1.45 \times 10^6)^2 = (2\pi \times 1.45 \times 10^6)^2$$

let  $R_5$  and  $R_4$  be  $1K$  apiece.

So  $R_5 = R_4 = R_6 = R_3 = 1K$

$R_1 = 5K$ ,  $R_2 = 20K$

$C_1 = C_2 = 10.98pf$

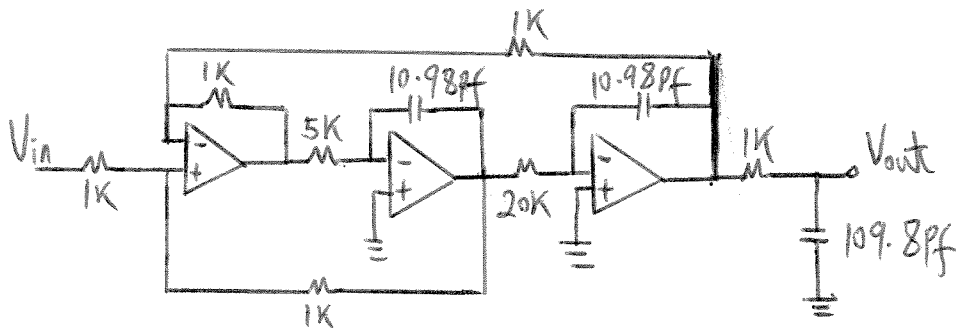

45.

ToW-Thomas Biquad

$$\frac{V_Y}{V_{in}} = \frac{R_3 R_4}{R_1} \left( \frac{1}{R_2 R_3 R_4 C_1 C_2 s^2 + R_2 R_4 C_2 s + R_3} \right)$$

$$\frac{V_Y}{V_{in}} = \frac{1 / (R_1 R_2 C_1 C_2)}{s^2 + 1 / (R_3 C_1) s + 1 / (R_2 R_4 C_1 C_2)}$$

$$\frac{V_Y}{V_{in}} = \frac{(2\pi \times 1.45 \times 10^6)^2}{s^2 - (4\pi \times 1.45 \times 10^6 \times \cos(29/3))s + (2\pi \times 1.45 \times 10^6)^2}$$


$$\frac{1}{R_1 R_2 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2, \quad \frac{1}{R_2 R_4 C_1 C_2} = (2\pi \times 1.45 \times 10^6)^2$$

$$\frac{1}{R_3 C_1} = 2\pi \times 1.45 \times 10^6$$

Let  $R_1 = R_2 = R_3 = R_4$ ,  $C_1 = C_2$

Let  $R_3 = 5K \Rightarrow C_1 = 21.95 \text{ pF}$

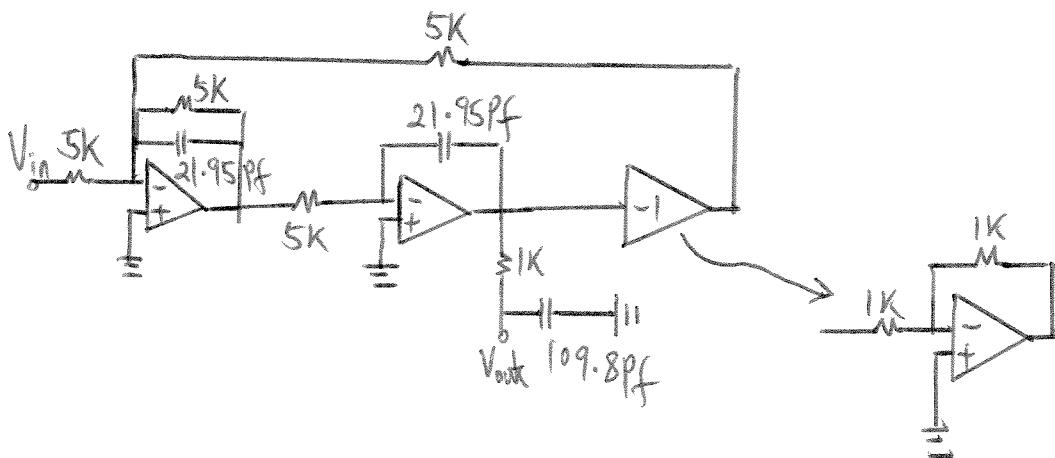So  $R_1 = R_2 = R_3 = R_4 = 5K$ , and  $C_1 = C_2 = 21.95 \text{ pF}$





46.

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \epsilon^2 C_n^2\left(\frac{\omega}{\omega_0}\right)}} \quad n=4$$

$$\epsilon = 0.2$$

$$C_n\left(\frac{\omega}{\omega_0}\right) = \cos\left(n \cos^{-1}\frac{\omega}{\omega_0}\right) = \cos\left(4 \cos^{-1}\frac{\omega}{\omega_0}\right)$$

$$C_n^2\left(\frac{\omega}{\omega_0}\right) = \cos^2\left(n \cos^{-1}\frac{\omega}{\omega_0}\right) = \frac{1}{2} \left(1 + \cos\left(2n \cos^{-1}\frac{\omega}{\omega_0}\right)\right)$$


$$2n \cos^{-1}\frac{\omega}{\omega_0} = \pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.924$$

$$2n \cos^{-1}\frac{\omega}{\omega_0} = 3\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.383$$


$$2n \cos^{-1}\frac{\omega}{\omega_0} = 0, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 1$$

$$2n \cos^{-1}\frac{\omega}{\omega_0} = 2\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0.707$$

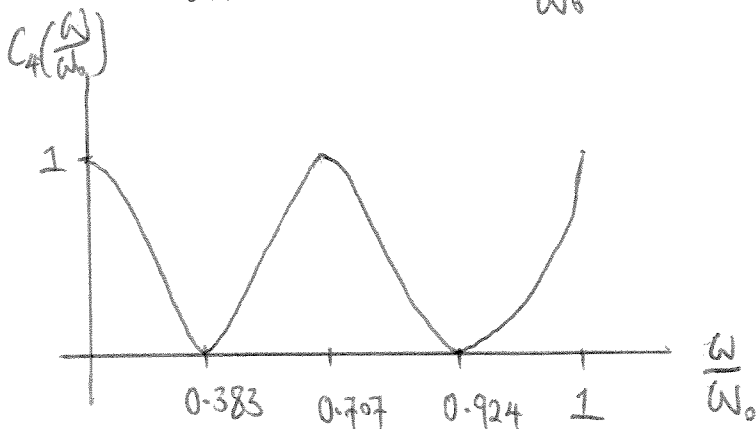
$$2n \cos^{-1}\frac{\omega}{\omega_0} = 4\pi, \quad n=4 \Rightarrow \frac{\omega}{\omega_0} = 0$$



46.

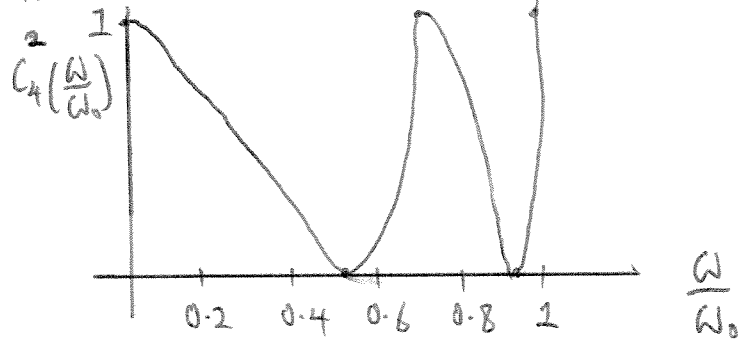
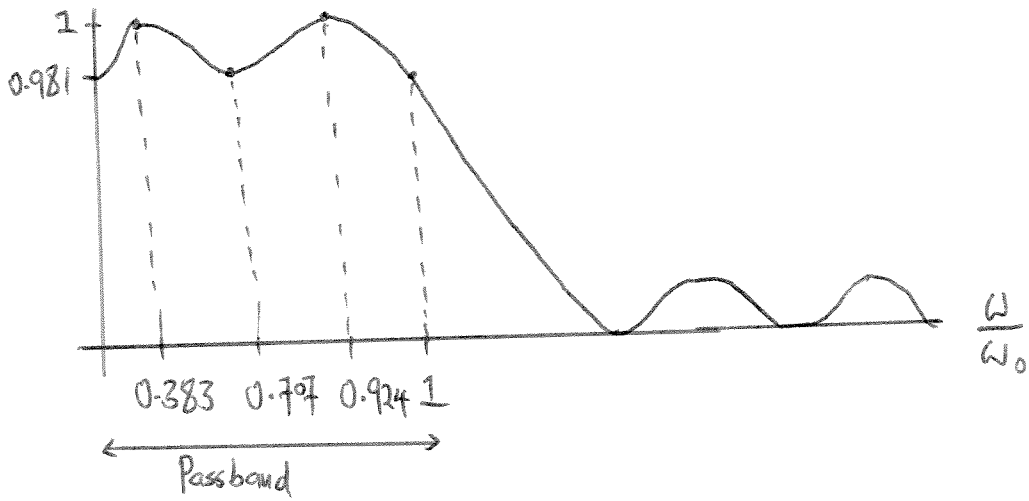
$$H(j\omega) = \frac{1}{\sqrt{1 + (0.2)^2 [C_4^2(\frac{\omega}{\omega_0})]}}$$



47. Chebyshev: 25 dB at 5 MHz.

$$n=5, \quad \omega_0 = 2 \text{ MHz}, \quad \frac{\omega}{\omega_0} = \frac{5}{2}$$

$$\frac{1}{\sqrt{1 + \epsilon^2 \cosh^2(n \cosh^{-1} \frac{\omega}{\omega_0})}} = -25 \text{ dB} = 0.056234$$

$$\Rightarrow \frac{1}{1 + \epsilon^2 (115939 \times 10^6)} = 0.0031622771$$

$$\Rightarrow \epsilon^2 = 1.9777 \times 10^{-4}$$

$\Rightarrow$  Minimum Ripple

$$\frac{1}{\sqrt{1 + (1.9777 \times 10^{-4})}} = 0.99990 = -8.6 \times 10^{-4} \text{ dB.}$$

$$48. \quad n=6$$

$$\cosh^2\left(6 \cos^{-1}\left(\frac{5}{2}\right)\right) = 36590401$$

$$\frac{1}{\sqrt{1 + \epsilon^2 (36590401)}} = 0.056234$$

$$\epsilon^2 = 8.615 \times 10^{-6}$$

$$\text{Minimum Ripple} = \frac{1}{\sqrt{1 + 8.615 \times 10^{-6}}} = -374 \times 10^{-5} \text{ dB}$$

Smaller than when  $n=5$ .

$$49. \quad \epsilon = 0.509, \quad n = 4$$

$$P_{1,4} = -0.140\omega_0 \pm 0.983j\omega_0$$

$$P_{2,3} = -0.337\omega_0 \pm 0.407j\omega_0$$

$$H_{1,4}(s) = \frac{0.986\omega_0^2}{s^2 + 0.28\omega_0 s + 0.986\omega_0^2} = \frac{\alpha / (R_1 R_2 C_1 C_2)}{s^2 + \frac{\omega_n}{Q} s + \omega_n^2}$$

$$Q = 3.55$$

$$\omega_n = (2\pi)(4.965 \text{ MHz})$$

$$\omega_n^2 = [(2\pi)(4.965 \times 10^6)]^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\frac{\omega_n}{Q} = (0.28)(5 \text{ MHz})(2\pi) = (1.4 \text{ MHz})(2\pi) = \frac{R_4}{R_4 + R_5} \left( \frac{1}{R_1 C_1} \right)$$

$$\frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) \left( \frac{1}{R_1 R_2 C_1 C_2} \right) = \frac{R_6}{R_3} \left( \frac{1}{R_1 R_2 C_1 C_2} \right)$$

$$\Rightarrow \frac{R_5}{R_4 + R_5} \left( 1 + \frac{R_6}{R_3} \right) = \frac{R_6}{R_3}$$

$$\Rightarrow \frac{R_5}{R_4 + R_5} = \frac{\frac{R_6}{R_3}}{1 + \frac{R_6}{R_3}}$$

$$\Rightarrow 1 - \alpha = \frac{\frac{R_6}{R_3}}{1 + \frac{R_6}{R_3}}, \quad \alpha = \frac{R_4}{R_4 + R_5}$$

$$\Rightarrow \frac{R_6}{R_3} = \frac{1 - \alpha}{\alpha}$$

$$\text{Let } \alpha = 0.5 \Rightarrow \frac{R_6}{R_3} = 1$$

49.

$$\Rightarrow \omega_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 C_1 R_2 C_2} \right) = \frac{1}{R_1 C_1 R_2 C_2} \quad (*)$$

$$\text{Since } \frac{\omega_n}{\omega} = \alpha \left( \frac{1}{R_1 C_1} \right) = 14 \times 10^6 \times 2\pi, \quad \alpha = 0.5$$

$$\Rightarrow \frac{1}{R_1 C_1} = 1.76 \times 10^7 \quad (1)$$

Consider (\*)

$$\Rightarrow \frac{1}{R_2 C_2} = \omega_n^2 \cdot R_1 C_2 = 5.53 \times 10^7 \quad (2)$$

$R_6 = R_3 = R_5 = R_4 = 1k$ . According to (1), (2), choose

$$R_1 = 5k, \quad C_1 = 11.368p$$

$$R_2 = 5k, \quad C_2 = 3.62p$$

$$\text{For } H_{2,3}(s) = \frac{0.279\omega_0^2}{s^2 + 0.674\omega_0 s + 0.279\omega_0^2}$$

$$\omega_n = (2\pi) (2.64 \times 10^6)$$

$$\frac{\omega_n}{\omega} = (2\pi) (0.674 \times 5 \times 10^6) = (2\pi) (3.37 \times 10^6)$$

$$\text{Let } \alpha = 0.5$$

$$49. \frac{W_n}{Q} = (\alpha) \left( \frac{1}{R_1 C_1} \right)$$

$$\Rightarrow \frac{1}{R_1 C_1} = \frac{W_n}{Q} \cdot \frac{1}{\alpha} = 4.23 \times 10^7 \quad (3)$$


$$\frac{R_6}{R_3} = 1, \quad W_n^2 = \frac{R_6}{R_3} \left( \frac{1}{R_1 C_1 R_2 C_2} \right) = \frac{1}{R_1 C_1 R_2 C_2}$$

$$\Rightarrow \frac{1}{R_2 C_2} = W_n^2 \cdot R_1 C_1 = 6.50 \times 10^6 \quad (4)$$

Consider (3) (4), choose

$$R_1 = 5K, \quad C_1 = 4.72p; \quad R_2 = 5K, \quad C_2 = 30.78p$$

$$R_6 = R_3 = R_5 = R_4 = 1K.$$

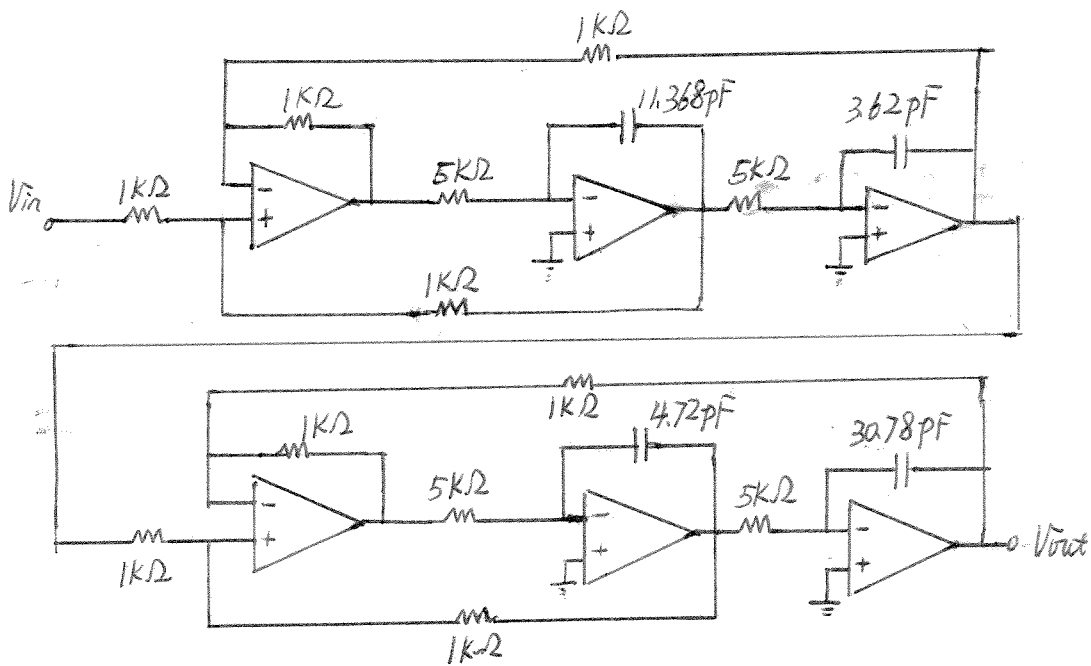

50. Tow Thomas

Low Pass Transfer Function

$$P_{1,4} = \frac{V_4}{V_{in}} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + \frac{1}{R_3 C_1} s + \frac{1}{R_2 R_4 C_1 C_2}} = \frac{0.986 \omega_0^2}{s^2 + 0.28 \omega_0 s + 0.986 \omega_0^2}$$

$$\frac{1}{R_1 R_2 C_1 C_2} = \frac{1}{R_2 R_4 C_1 C_2} = [(2\pi)(4.965 \times 10^6)]^2 \quad (*)$$

$$\frac{1}{R_3 C_1} = 2\pi \times 1.4 \times 10^6$$

Let  $R_3 = 5K$ ,  $C_1 = 22.736P$

Let  $C_1 = C_2$ ,  $C_2 = 22.736P$

$$\left. \begin{array}{l} R_1 = R_2 \stackrel{+}{\Rightarrow} R_1 = R_2 = R_4 = 1.4K \\ R_3 = 5K, C_1 = C_2 = 22.736P \end{array} \right\} \text{for } P_{1,4}$$

$$P_{2,3} = \frac{0.279 \omega_0^2}{s^2 + 0.674 \omega_0 s + 0.279 \omega_0^2} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + \frac{1}{R_3 C_1} s + \frac{1}{R_2 R_4 C_1 C_2}}$$

$$\frac{1}{R_1 R_2 C_1 C_2} = \frac{1}{R_2 R_4 C_1 C_2} = [(2\pi)(2.64 \times 10^6)]^2 \quad (*)$$


$$\frac{1}{R_3 C_1} = (2\pi)(3.37 \times 10^6)$$



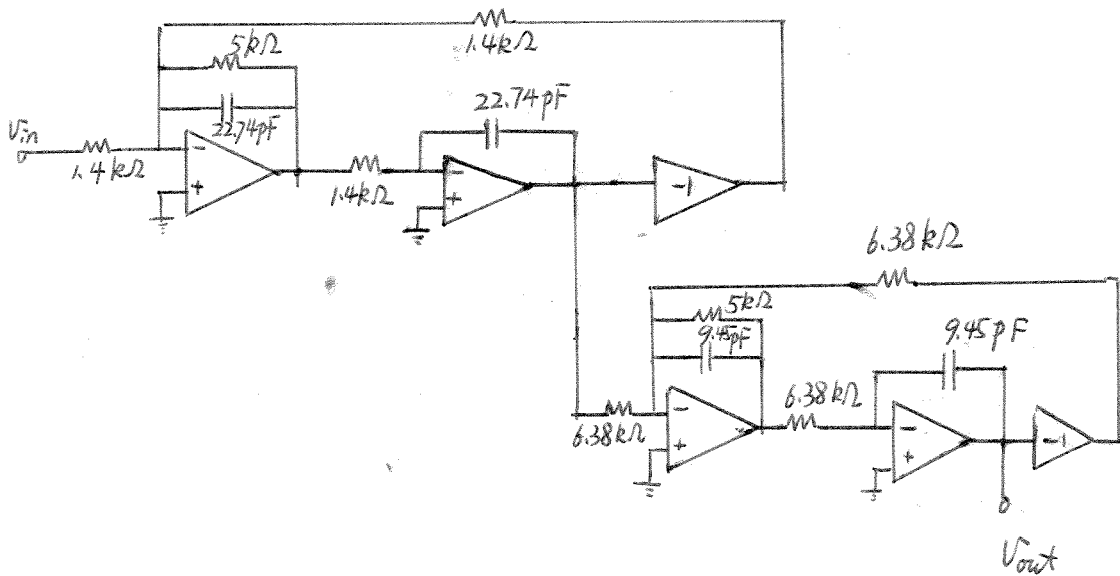
50. Let  $R_3 = 5K$ ,  $C_1 = 9.45 p$

Let  $C_1 = C_2 = 9.45 p$ ,  $R_1 = R_2 \xrightarrow{(*)} R_1 = R_2 = R_4 = 6.38K$ .

For  $P_{14}$  .  $\left\{ \begin{array}{l} R_1 = R_2 = R_4 = 6.38K, R_3 = 5K \\ C_1 = C_2 = 9.45 p. \end{array} \right.$




51.

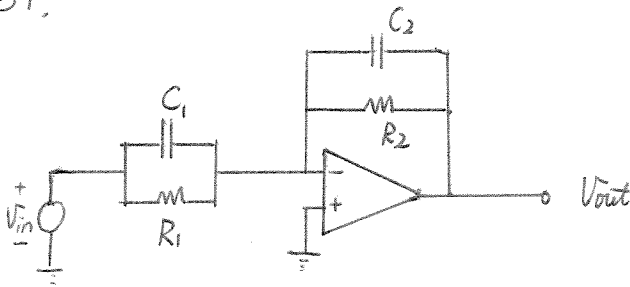

High pass,  $1\text{MHz} \Rightarrow 10\text{dB atten}$

$f > 5\text{MHz}$ , gain = 1

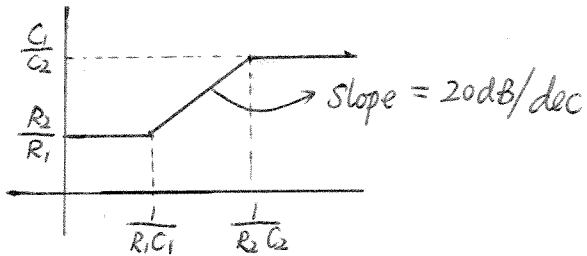

$$\frac{1}{R_2 C_2} = (5\text{MHz})(2\pi)$$

$$\text{Let } \frac{C_2}{C_1} = 1, \quad \frac{R_2}{R_1} = -10\text{dB} = 0.316$$


$$\text{So } \frac{1}{0.316} = 3.1623, \quad \frac{5\text{MHz}}{3.1623} = 1.58\text{MHz}$$

$$\Rightarrow \frac{1}{R_1 C_1} = (1.58\text{MHz})(2\pi)$$

$$\text{Choose } C_2 = 31.83\text{pF} \Rightarrow R_2 = 1\text{k}\Omega$$

$$C_1 = 31.83\text{pF} \Rightarrow R_1 = 3.16\text{k}\Omega$$

52.

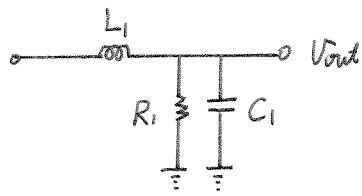

Peaking : 1dB

bandwidth: 100MHz

 $L_1 < 100\text{nH}$ 

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{L_1 C_1}}{s^2 + \frac{1}{R_1 C_1} s + \frac{1}{L_1 C_1}} = \frac{\gamma}{s^2 + \frac{\omega_n}{Q} s + \omega_n^2} \Big|_{s=j\omega} = \frac{\gamma}{(j\omega)^2 + \frac{\omega_n}{Q} (j\omega) + \omega_n^2}$$

$$H(j\omega) = \frac{\gamma}{(\omega_n^2 - \omega^2) + \frac{\omega_n}{Q} \omega j}$$

$$|H(j\omega)| = \frac{\gamma}{\sqrt{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega_n}{Q} \omega\right)^2}}$$

$$\text{At } \omega_1, |H(j\omega_1)| = \frac{\gamma}{\sqrt{(\omega_n^2 - \omega_1^2)^2 + \left(\frac{\omega_n}{Q} \omega_1\right)^2}} = \frac{\gamma}{\omega_n^2 \sqrt{2}}$$

$$\Rightarrow \sqrt{\frac{(\omega_n^2 - \omega_1^2)^2 + \left(\frac{\omega_n}{Q} \omega_1\right)^2}{\omega_n^4}} = \sqrt{2}$$

$$\Rightarrow (\omega_n^2 - \omega_1^2)^2 + \left(\frac{\omega_n}{Q} \omega_1\right)^2 = 2\omega_n^4 \quad (*)$$

$$\frac{Q}{\sqrt{1 - (4Q^2)^{-1}}} = 1.1 \Rightarrow Q = 0.9258, 0.5941 (< \frac{1}{\sqrt{2}}, \text{ can't produce peaking})$$

$$\text{So } Q = 0.9258.$$

$$\text{Solve } (*) \text{ gives } \omega = \sqrt{1.5} \omega_n.$$

$$\omega = \sqrt{1.5} \frac{1}{\sqrt{L_1 C_1}} = (127) (100 \times 10^6) \quad (1)$$


52.

$$\frac{W_n}{Q} = \frac{1}{R_1 C_1} \Rightarrow Q = R_1 C_1 \frac{1}{\sqrt{4C_1}} = R_1 \sqrt{\frac{C_1}{4}} = 0.9258 \quad (2)$$

$$\text{Let } L_1 = 90 \text{ nH} \stackrel{(1)}{\Rightarrow} C_1 = 42.22 \text{ pF} \stackrel{(2)}{\Rightarrow} R_1 = 42.74 \Omega.$$

53.  $\omega_n = (2\pi)(50\text{MHz})$ ,  $Q = 1.5$ , Low frequency gain = 2.

$C = 10\text{pF}$  to  $100\text{pF}$ .

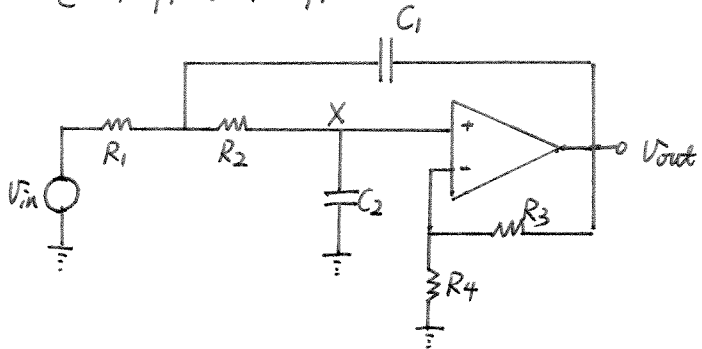

$$\frac{V_{out}}{V_{in}} = \frac{1 + \frac{R_3}{R_4}}{R_1 R_2 C_1 C_2 S^2 + (R_1 C_2 + R_2 C_2 - R_1 \frac{R_3}{R_4} C_1) S + 1}$$

$$= \frac{(1 + \frac{R_3}{R_4}) / (R_1 R_2 C_1 C_2)}{S^2 + \frac{(R_1 C_2 + R_2 C_2 - \frac{R_1 R_3}{R_4} C_1) S + \frac{1}{R_1 R_2 C_1 C_2}}{R_1 R_2 C_1 C_2}}$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \frac{\omega_n}{Q} = \frac{R_1 C_2 + R_2 C_2 - R_1 \frac{R_3}{R_4} C_1}{R_1 R_2 C_1 C_2}$$

Low frequency gain  $(1 + \frac{R_3}{R_4}) = 2$ , Let  $\frac{R_3}{R_4} = 1$ .

$$\frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \omega_n = (2\pi)(50 \times 10^6) \quad \text{①}$$

$$R_1 C_2 + R_2 C_2 - R_1 C_1 = \frac{\omega_n}{Q} (R_1 R_2 C_1 C_2) = \frac{1}{(1.5)(2\pi)(50 \times 10^6)} \quad \text{②}$$

Let  $C_1 = C_2 = 10\text{pF}$

$$\text{②} \Rightarrow R_2 = \frac{1}{(1.5)(2\pi)(50 \times 10^6)} \cdot \frac{1}{C_2} = 212.2 (\Omega)$$

$$\text{①} \Rightarrow R_1 = \sqrt{[(2\pi)^2 (50 \times 10^6)^2 \cdot R_2 C_1 C_2]} = 477.5 (\Omega)$$

Let  $R_3 = R_4 = 1\text{k}\Omega$ .

54.  $W_{3dB} = (30 \times 10^6) (2Z)$ , gain = 2, sensitivities no greater than 1.

$$H(s) = \frac{K W_n^2}{s^2 + \frac{W_n}{Q} s + W_n^2}, \quad s = j\omega \Rightarrow$$

$$H(j\omega) = \frac{K W_n^2}{W_n^2 - \omega^2 + \frac{W_n}{Q} \omega j}$$

$$|H(j\omega)| = \frac{K W_n^2}{\sqrt{(W_n^2 - \omega^2)^2 + \left(\frac{W_n}{Q} \omega\right)^2}}$$

$$|H(j\omega)| = \frac{K}{\sqrt{2}} \Rightarrow \frac{W_n^2}{\sqrt{(W_n^2 - \omega^2)^2 + \left(\frac{W_n}{Q} \omega\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\Rightarrow (W_n^2 - \omega^2)^2 + \left(\frac{W_n}{Q} \omega\right)^2 = 2W_n^4$$

$$\Rightarrow W_n^4 \left(1 - \frac{\omega^2}{W_n^2}\right)^2 + W_n^4 \left[\left(\frac{1}{Q}\right)^2 \cdot \left(\frac{\omega}{W_n}\right)^2\right] = 2W_n^4$$

$$\Rightarrow \left[1 - \left(\frac{\omega}{W_n}\right)^2\right]^2 + \left(\frac{1}{Q}\right)^2 \left(\frac{\omega}{W_n}\right)^2 = 2$$

$$\Rightarrow \left(\frac{\omega}{W_n}\right)^4 + \left[\left(\frac{1}{Q}\right)^2 - 2\right] \left(\frac{\omega}{W_n}\right)^2 - 1 = 0$$

$$S_{R_2, C_1, C_2, R_1}^{W_n} = -\frac{1}{2} \quad (\text{sensitivities of } W_n \text{ all } < 1)$$

$$S_{R_1}^Q = -S_{R_2}^Q = -\frac{1}{2} + Q \sqrt{\frac{R_2 C_2}{R_1 C_1}}$$

$$S_{C_1}^Q = -S_{C_2}^Q = -\frac{1}{2} + Q \left( \sqrt{\frac{R_1 C_2}{R_2 C_1}} + \sqrt{\frac{R_2 C_2}{R_1 C_1}} \right) = \frac{1}{2} + Q \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

$$S_K^Q = QK \sqrt{\frac{R_1 C_1}{R_2 C_2}} = 2Q \sqrt{\frac{R_1 C_1}{R_2 C_2}}$$

Let  $\sqrt{\frac{R_1 C_2}{R_2 C_1}} = 1$ , and  $Q = \frac{1}{2}$ ,

$$S_K^Q = 2 \cdot \left(\frac{1}{2}\right) = 1, \quad S_{C_1}^Q = \frac{1}{2} + \frac{1}{2} = 1$$

$$S_{C_2}^Q = -1, \quad S_{R_1}^Q = -\frac{1}{2} + \frac{1}{2} = 0, \quad S_{R_2}^Q = 0$$

Since  $Q = \frac{1}{2}$ ,

$$\left(\frac{\omega}{\omega_n}\right)^4 + 2 \left(\frac{\omega}{\omega_n}\right)^2 - 1 = 0$$

$$\Rightarrow \left(\frac{\omega}{\omega_n}\right)^2 = 0.4142$$

$$\Rightarrow \omega = \sqrt{0.4142} \omega_n$$

Since  $R_1 C_1 = R_2 C_2$ ,

$$\omega_n = \frac{1}{\sqrt{(RC)^2}} = \frac{1}{R_1 C_1}$$

$$\Rightarrow \sqrt{0.4142} \omega_n = \frac{\sqrt{0.4142}}{R_1 C_1} = (2\pi)(30 \times 10^6) \quad \textcircled{1}$$

$$\text{Also } \frac{1}{Q\omega_n} = R_1 C_2 + R_2 C_2 - R_1 C_1 = R_1 C_2 \quad \textcircled{2}$$

$$\Rightarrow \frac{R_1 C_1}{R_1 C_2} = \frac{\frac{1}{\omega_n}}{\frac{1}{Q\omega_n}} = Q = \frac{1}{2}$$


$$\Rightarrow \frac{C_1}{C_2} = \frac{1}{2}$$

$$\text{Let } R_1 = 1K\Omega \xrightarrow{\textcircled{1}} C_1 = \frac{\sqrt{0.4142}}{(2\pi)(30 \times 10^6) \cdot R_1} = 3.4pF$$

$$\Rightarrow C_2 = 2C_1 = 6.8pF$$


$$\Rightarrow R_2 = R_1 \frac{C_1}{C_2} = 500\Omega$$

And as before,  $R_3 = R_4 = 1K\Omega$ .

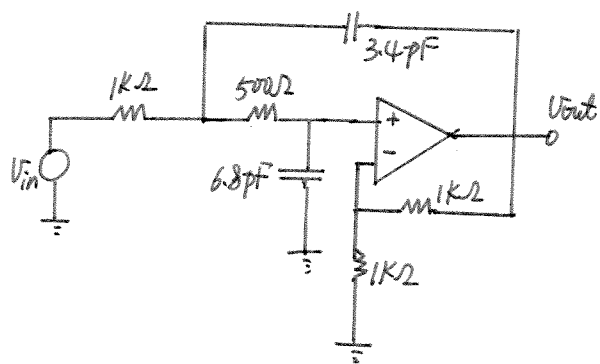

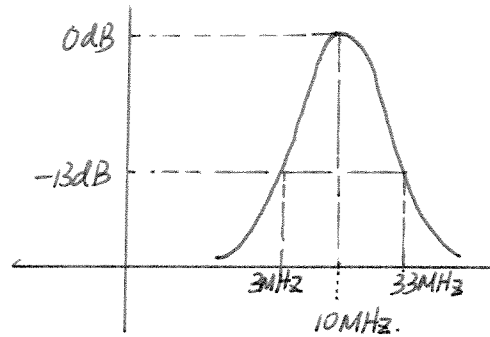55. 10MHz, Gain=1 (peak),  $R_6=R_3$ , -13dB @ 3MHz, 33MHz.

$$\frac{V_x}{V_{in}} = \frac{\alpha S^2}{S^2 + \frac{\omega_n}{Q} S + \omega_n^2} \cdot \frac{-1}{R_1 C_1}$$



$$1 = \left(\frac{\alpha}{R_1 C_1}\right) \cdot \frac{Q}{\omega_n}, \quad \alpha = \frac{R_5}{R_4 + R_5} \left(1 + \frac{R_6}{R_3}\right), \quad \frac{\omega_n}{Q} = \frac{R_4}{R_4 + R_5} \cdot \frac{1}{R_1 C_1}$$

$$\text{since } R_6 = R_3, \quad \alpha = 2 \frac{R_5}{R_4 + R_5} \Rightarrow \frac{\alpha}{2} = \frac{R_5}{R_4 + R_5}$$

$$\Rightarrow \frac{R_4}{R_4 + R_5} = 1 - \frac{\alpha}{2} \Rightarrow \frac{Q}{\omega_n} = \frac{R_1 C_1}{1 - \frac{\alpha}{2}}$$

$$\Rightarrow \left(\frac{\alpha}{R_1 C_1}\right) \cdot \left(\frac{R_1 C_1}{1 - \frac{\alpha}{2}}\right) = 1 \Rightarrow \alpha = 1 - \frac{\alpha}{2}$$

$$\Rightarrow \alpha = \frac{2}{3}, \quad \frac{R_5}{R_4 + R_5} = \frac{1}{3}$$

$$\Rightarrow R_5 = \frac{1}{2} R_4$$

$$\left. \begin{array}{l} \frac{\omega_n}{Q} = \left(\frac{2}{3}\right) \left(\frac{1}{R_1 C_1}\right) \\ \omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \end{array} \right\} \Rightarrow \frac{3}{2} \frac{R_1 C_1}{\sqrt{R_1 R_2 C_1 C_2}} = Q$$

$$\Rightarrow \frac{3}{2} \sqrt{\frac{R_1 C_1}{R_2 C_2}} = Q$$

$$\text{Let } R_1 C_1 = R_2 C_2 \Rightarrow Q = \frac{3}{2}, \quad \omega_n = \frac{1}{R_1 C_1}$$



$$H(j\omega) = \frac{\frac{2}{3}\omega^2}{\frac{\omega}{\omega_n} \sqrt{(\omega_n^2 - \omega^2)^2 + (\frac{2}{3}\omega_n\omega)^2}} = \frac{\frac{2}{3}\omega^2}{\frac{\omega}{\omega_n} \sqrt{\omega_n^4 - \frac{14}{9}(\omega_n\omega)^2 + \omega^4}}$$

$$H(j\omega) = 1$$

$$\Rightarrow \frac{4}{9}\omega^2 = \omega_n^2 - \frac{14}{9}\omega^2 + \frac{\omega^4}{\omega_n^2}$$

$$\Rightarrow \omega_n^4 - 2\omega^2\omega_n^2 + \omega^4 = 0$$

$$\Rightarrow \omega_n^2 = \omega^2 = [(2\pi)(10\text{MHz})]^2$$


$$\text{As derived, } \omega_n = \frac{1}{R_1 C_1}$$

$$\text{Let } R_1 = 5\text{k}\Omega \Rightarrow C_1 = 3.183\text{pF.}$$


$$\text{Let } R_2 = R_1 = 5\text{k}\Omega \Rightarrow C_2 = C_1 = 3.183\text{pF}$$

$$\text{Let } R_4 = 5\text{k}\Omega \Rightarrow R_5 = \frac{1}{2}R_4 = 2.5\text{k}\Omega.$$
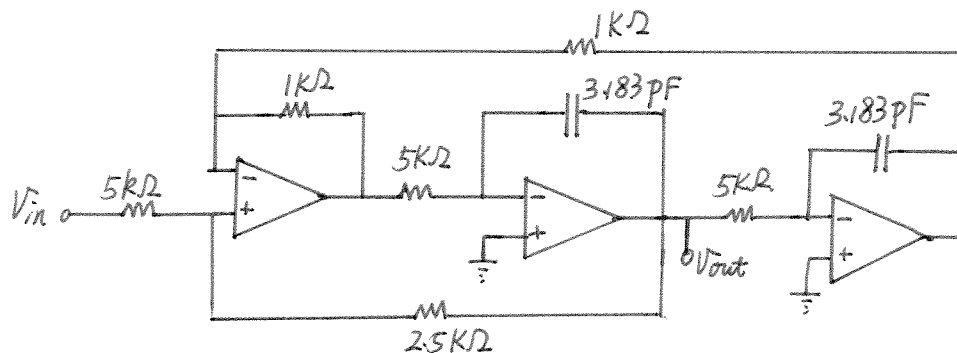
$$\text{Let } R_3 = R_6 = 1\text{k}\Omega.$$



56.

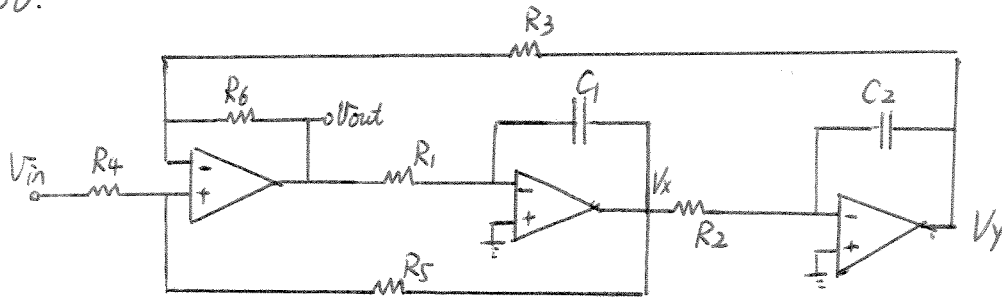

Low pass, 
$$\frac{V_y}{V_{in}} = \frac{\alpha S^2}{S^2 + \frac{W_n}{Q} S + W_n^2} \cdot \frac{1}{R_1 R_2 C_1 C_2 S^2}$$

$$= \frac{\alpha}{(S^2 + \frac{W_n}{Q} S + W_n^2) (R_1 R_2 C_1 C_2)}$$

$$H(S) = \frac{\alpha / (R_1 R_2 C_1 C_2)}{S^2 + \frac{W_n}{Q} S + W_n^2}$$

$$H(jW) = \frac{\alpha / (R_1 R_2 C_1 C_2)}{(W_n^2 - W^2) + j \frac{W_n}{Q} W}$$

$$|H(jW)| = \frac{\alpha / (R_1 R_2 C_1 C_2)}{\sqrt{(W_n^2 - W^2)^2 + (\frac{W_n W}{Q})^2}}$$

$$|H(W_{3dB})| = \frac{\alpha / (R_1 R_2 C_1 C_2)}{\sqrt{(W_n^2 - W_{3dB}^2)^2 + (\frac{W_n W_{3dB}}{Q})^2}} = \frac{\alpha}{W_n^2 (R_1 R_2 C_1 C_2) \sqrt{2}}$$

$$\Rightarrow \frac{\sqrt{(W_n^2 - W_{3dB}^2)^2 + (\frac{W_n W_{3dB}}{Q})^2}}{W_n^2} = \sqrt{2}$$

$$\Rightarrow 1 - 2 \left( \frac{W_{3dB}}{W_n} \right)^2 + \left( \frac{W_{3dB}}{W_n} \right)^4 + \frac{1}{Q^2} \left( \frac{W_{3dB}}{W_n} \right)^2 = 2$$

$$\Rightarrow \left(\frac{\omega_{3dB}}{\omega_n}\right)^4 + \left(\frac{1}{Q^2} - 2\right) \left(\frac{\omega_{3dB}}{\omega_n}\right)^2 - 1 = 0$$

$$Q = 1.5 \Rightarrow \left(\frac{\omega_{3dB}}{\omega_n}\right)^4 - 1.556 \left(\frac{\omega_{3dB}}{\omega_n}\right)^2 - 1 = 0$$

$$\Rightarrow \left(\frac{\omega_{3dB}}{\omega_n}\right)^2 = 2.0446, -0.4891 \text{ (impossible)}$$

$$\Rightarrow \omega_{3dB} = 1.43 \omega_n$$

$\Rightarrow$  Low pass corner = 14.3 MHz.

High pass:

$$\frac{V_{out}}{V_{in}}(s) = \frac{\alpha s^2}{s^2 + \frac{\omega_n}{Q}s + \omega_n^2}$$

$$|H(j\omega)| = \frac{\alpha \omega^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + \left(\frac{\omega \omega_n}{Q}\right)^2}}$$

$$|H(j\omega_{3dB})| = \frac{\alpha \omega_{3dB}^2}{\sqrt{(\omega_n^2 - \omega_{3dB}^2)^2 + \left(\frac{\omega_{3dB} \omega_n}{Q}\right)^2}} = \frac{\alpha}{\sqrt{2}}$$


$$\Rightarrow \left(\frac{\omega_n}{\omega_{3dB}}\right)^4 + \left(\frac{1}{Q^2} - 2\right) \left(\frac{\omega_n}{\omega_{3dB}}\right)^2 - 1 = 0$$

Since  $Q = 1.5$

$$\Rightarrow \left(\frac{\omega_n}{\omega_{3dB}}\right)^2 = 2.0446 \Rightarrow \omega_{3dB} = \frac{\omega_n}{1.43}$$

$\Rightarrow \omega_{3dB} = 7 \text{ MHz. (high pass corner)}$

57.

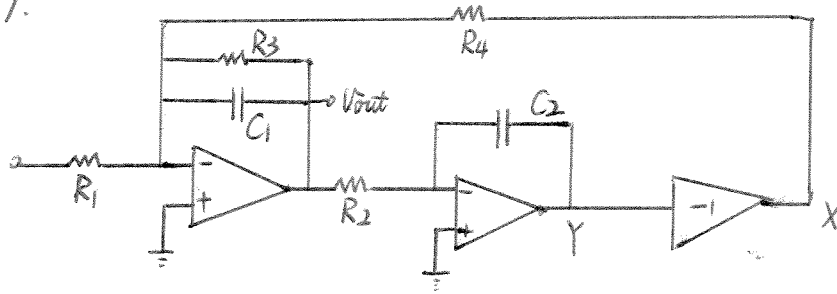

$$\omega_n = 10 \text{ MHz},$$

$$-13 \text{ dB} = 3 \text{ MHz},$$

$$33 \text{ MHz}.$$

$$\frac{V_{out}}{V_{in}} = - \frac{R_2 R_3 R_4}{R_1} \left( \frac{C_2 S}{R_2 R_3 R_4 C_1 C_2 S^2 + R_2 R_4 C_2 S + R_3} \right)$$

Same as in #55,  $Q = \frac{10}{6.684} = 1.5.$

$$\frac{V_{out}}{V_{in}} = - \frac{\frac{1}{R C_1} S}{S^2 + \frac{1}{R_3 C_1} S + \frac{1}{R_2 R_4 C_1 C_2}}$$

$$\frac{\omega_n}{Q} = \frac{1}{R_3 C_1}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$

$$Q = \frac{R_3 C_1}{\sqrt{R_2 R_4 C_1 C_2}} = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\frac{V_{out}}{V_{in}} = \frac{-\beta S}{S^2 + \frac{\omega_n}{Q} S + \omega_n^2},$$

At  $\omega = \omega_n \Rightarrow |H(j\omega_n)| = 1 = \frac{\beta Q}{\omega_n}.$

$$\frac{\beta Q}{\omega_n} = \left( \frac{1}{R C_1} \right) (R_3 C_1) = \frac{R_3}{R_1} = 1$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}} = 15, \quad W_n = \frac{1}{\sqrt{R_2 R_4 C_2 C_1}} = (10 \times 10^6)(2\pi)$$

$$\text{Let } R_2 = R_4 = 1 \text{ k}\Omega.$$

$$\frac{1}{\sqrt{10^6 \times C_1 C_2}} = (10 \times 10^6)(2\pi) \Rightarrow C_1 C_2 = 2.533 \times 10^{-22}$$

$$\text{Let } C_1 = C_2 = 15.9 \text{ pF}$$

$$R_3 \sqrt{\frac{1}{10000 \times 10000}} = 15.$$

$$\Rightarrow R_3 = 1.5 \text{ k}\Omega = R_1$$


$$\text{So : } R_1 = 1.5 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega, R_3 = 1.5 \text{ k}\Omega, R_4 = 1 \text{ k}\Omega.$$

$$C_1 = C_2 = 15.9 \text{ pF}.$$

58. Peaking : 1dB @ 7MHz.

Corner : 3.69MHz

-13.6dB @ 2MHz.

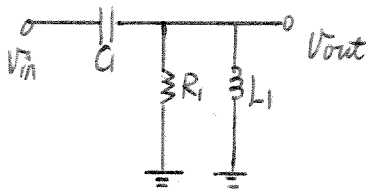

$$\frac{V_{out}}{V_{in}} = \frac{S^2}{S^2 + \frac{1}{R_1 C_1} S + \frac{1}{L_1 C_1}}$$

Peaking 1dB  $\Rightarrow Q = 0.926$ .

$$\frac{\omega_n}{\sqrt{1 - 1/(2Q^2)}} = (2\pi)(7\text{MHz}) \Rightarrow \omega_n = (2\pi)(4.52\text{MHz})$$

$$\frac{\omega_n}{Q} = \frac{(2\pi)(4.52\text{MHz})}{0.926} = (2\pi)(4.88\text{MHz}) = \frac{1}{R_1 C_1}$$

$$\omega_n^2 = [(2\pi)(4.52\text{MHz})]^2 = \frac{1}{L_1 C_1}$$

Let  $C_1 = 100\text{pF}$ ,  $L_1 = 12.4\mu\text{H}$ ,  $R_1 = 326.1\Omega$ .

With simulated inductor


$$Z_{in} = \left( \frac{Z_1 Z_3}{Z_2 Z_4} \right) Z_5 = R_Y R_X C_S$$

Let  $Z_1 = Z_3 = Z_4 = R_Y$ ,  $Z_5 = R_X$ ,  $Z_2 = C_S^{-1}$

Let  $R_Y = 1\text{k}\Omega$ ,  $R_X = 5\text{k}\Omega$ .

$$12.4 \times 10^{-6} = (1000)(5000) C$$

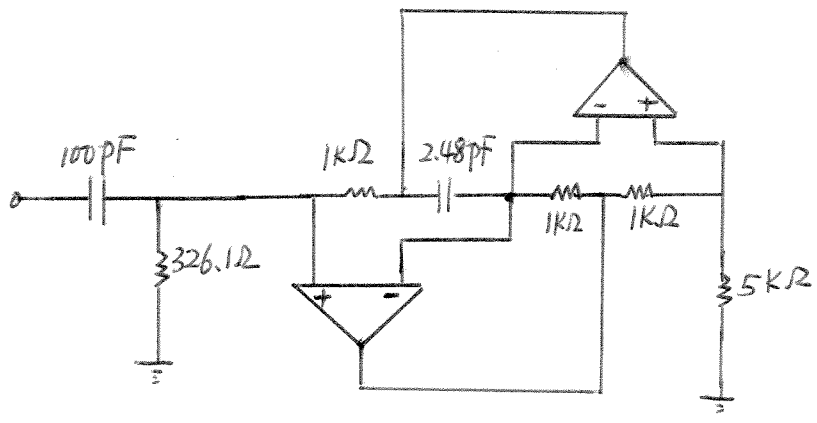$\Rightarrow C = 2.48\text{pF}$  to simulate an L of  $12.4\mu\text{H}$ .



59. Corner @ 16.38 MHz, Peaking 0.5 dB @ 8 MHz.

5.9 dB  $\approx$  6 dB attenuation @ 20 MHz.

$$\frac{V_{out}}{V_{in}} = \frac{1}{R_1 R_x C^2 S^2 + R_1 C S + 1} = \frac{1 / (R_1 R_x C^2)}{S^2 + \frac{S}{R_x C} + \frac{1}{R_1 R_x C^2}}$$

$$0.5 \text{ dB} \Leftrightarrow 1.05292$$

$$\frac{Q}{\sqrt{1 - \frac{1}{4Q^2}}} = 1.05292 \Rightarrow Q = 0.8636$$


$$\omega_n \sqrt{1 - \frac{1}{2Q^2}} = (2\pi)(8 \times 10^6)$$

$$\Rightarrow \omega_n = (2\pi)(13.934 \times 10^6)$$

$$\frac{1}{R_1 R_x C^2} = \omega_n^2, \quad \frac{1}{R_x C} = \frac{\omega_n}{Q} = (2\pi)(16.134 \times 10^6)$$

$$\Rightarrow \frac{1}{R_1 C} = 7.56 \times 10^7$$

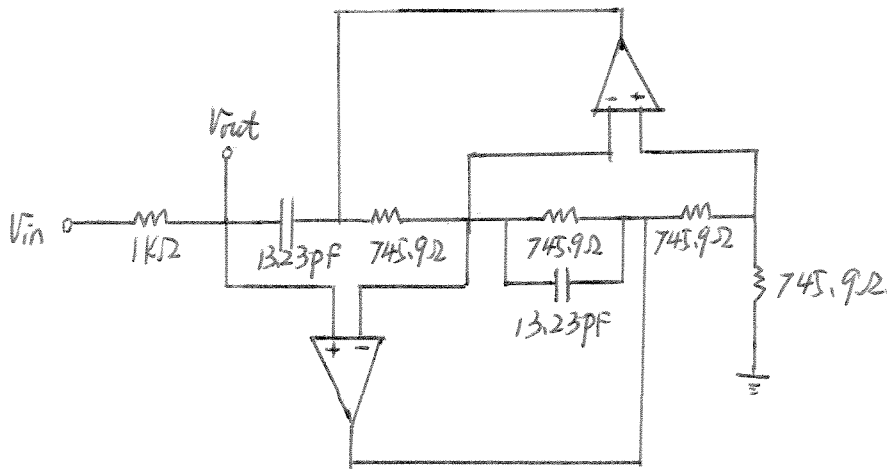Let  $R_1 = 1 \text{ k}\Omega$ ,  $C = 13.23 \text{ pF}$ ,  $R_x = 745.9 \Omega$ .





60. Butterworth

a) Passband 0.5 dB @ 1 MHz,  $-0.5 \text{ dB} \Leftrightarrow 0.944$

Attenuation 12 dB @ 2.5 MHz,  $-12 \text{ dB} \Leftrightarrow 0.2512$ .

$$|H(j\omega)|_{1\text{MHz}}^2 = \frac{1}{1 + \left[\frac{(2\pi)(10^6)}{W_0}\right]^{2n}} = 0.944^2 \quad (1)$$

$$|H(j\omega)|_{2.5\text{MHz}}^2 = \frac{1}{1 + \left[\frac{2\pi \times 2.5 \times 10^6}{W_0}\right]^{2n}} = 0.2512^2 \quad (2)$$

$$(1) \Rightarrow 1 = (0.944)^2 \left[ \left( \frac{2\pi \times 10^6}{W_0} \right)^{2n} + 1 \right]$$

$$\Rightarrow W_0^{2n} = 8.186 \times (2\pi \times 10^6)^{2n} \quad (3)$$

$$(2) \Rightarrow 1 = (0.2512)^2 \left[ \frac{(2\pi \times 2.5 \times 10^6)^{2n}}{8.186 \times (2\pi \times 10^6)^{2n}} + 1 \right]$$

$$\Rightarrow n = 2.62$$

So choose  $n = 3$ .  $(3) \Rightarrow W_0 = 2\pi \times 1.42 \text{ MHz}$ .

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left( \frac{\omega}{2\pi \times 1.42 \times 10^6} \right)^6}}$$

b). Passband: 0.1 dB @ 1 MHz

$$\frac{1}{1 + \left(\frac{2\pi \times 10^6}{\omega_0}\right)^{2n}} = (0.98855)^2 \quad (1)$$

Stopband attenuation: 12 dB @ 2.5 MHz

$$\frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{\omega_0}\right)^{2n}} = (0.2512)^2 \quad (2)$$

$$(1) \Rightarrow \omega_0^{2n} = 42.931 \times (2\pi \times 10^6)^{2n}$$

$$(2) \Rightarrow n = 3.52$$

$$\text{Choose } n = 4 \xrightarrow{(3)} \omega_0 = 2\pi \times 1.6 \text{ MHz.}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{2\pi \times 1.6 \times 10^6}\right)^8}}$$

$$c). \text{ Passband } 1 \text{ dB @ } 1 \text{ MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 10^6}{\omega_0}\right)^{2n}} = (0.90)^2 \quad (4)$$

$$\text{Attenuation } 18 \text{ dB @ } 2.5 \text{ MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{\omega_0}\right)^{2n}} = (0.259)^2 \quad (5)$$

$$(4) \Rightarrow \omega_0^{2n} = 4.263 \times (2\pi \times 10^6)^{2n} \quad (6)$$

$$(5) \Rightarrow n = 3.0$$

$$\text{Choose } n = 3 \xrightarrow{(6)} \omega_0 = 2\pi \times 1.27 \text{ MHz}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{2\pi \times 1.27 \times 10^6}\right)^6}}$$

$$d) \text{ Passband: } 0.5\text{dB @ } 1\text{MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 10^6}{W_0}\right)^{2n}} = 0.944^2 \quad (1)$$

$$\text{Attenuation: } 18\text{dB @ } 2.5\text{MHz} \Rightarrow \frac{1}{1 + \left(\frac{2\pi \times 2.5 \times 10^6}{W_0}\right)^{2n}} = 0.1259^2 \quad (2)$$

$$(1) \Rightarrow W_0^{2n} = 8.186 \times (2\pi \times 10^6)^{2n} \quad (3)$$

$$(2) \Rightarrow n = 3.4$$

$$\text{Choose } n = 4 \Rightarrow W_0 = 2\pi \times 1.3\text{MHz}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{2\pi \times 1.3 \times 10^6}\right)^8}}$$

Chebyshev

$$a) \text{ Passband } 0.5\text{dB @ } 1\text{MHz} \Rightarrow 0.5 = 20 \log(\sqrt{1 + \epsilon^2})$$

$$\Rightarrow \epsilon = 0.3493, W_0 = 1\text{MHz}$$

$$\text{Attenuation } 12\text{dB @ } 2.5\text{MHz}$$

$$\Rightarrow \frac{1}{\sqrt{1 + \epsilon^2 \cosh^2\left[n \cosh^{-1}\left(\frac{\omega}{W_0}\right)\right]}} = 0.2512, \text{ when } \omega = 2.5 \times 10^6 \times 2\pi$$

Since  $\omega, W_0, \epsilon$ , known

$$\Rightarrow n = 1.9733$$

$$\text{Choose } n = 2, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.3493^2 \left(2 \frac{\omega}{W_0}\right)^2}}, W_0 = 2\pi \times 1\text{MHz}$$

b). Passband 0.1 dB @ 1 MHz,  $\omega_0 = 1 \text{ MHz}$

$$\Rightarrow 0.1 = 20 \log(\sqrt{1+\epsilon^2}) \Rightarrow \epsilon = 0.1526.$$

Attenuation 12 dB @ 25 MHz

$$\Rightarrow \frac{1}{1 + 0.1526^2 \cosh^2[n \cosh^{-1}(25)]} = 0.2512^2$$

$$\Rightarrow n = 2.5$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.1526^2 \left(3^2 \left(\frac{\omega}{\omega_0}\right)^2\right)}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

c). Passband 1 dB @ 1 MHz,  $\omega_0 = 1 \text{ MHz}$

$$\Rightarrow 1 = 20 \log \sqrt{1+\epsilon^2} \Rightarrow \epsilon = 0.5089.$$

Attenuation 18 dB @ 25 MHz

$$\Rightarrow \frac{1}{1 + 0.5089^2 \cosh^2[n \cosh^{-1}(25)]} = 0.1259^2 \Rightarrow n = 2.19$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.5089^2 \left(3^2 \left(\frac{\omega}{\omega_0}\right)^2\right)}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

d). Passband 0.5 dB @ 1 MHz  $\Rightarrow \epsilon = 0.3493$

Attenuation 18 dB @ 25 MHz

$$\Rightarrow \frac{1}{1 + 0.3493^2 \cosh^2[n \cosh^{-1}(25)]} = 0.1259^2 \Rightarrow n = 2.43$$

$$\text{Choose } n=3, |H(j\omega)| = \frac{1}{\sqrt{1 + 0.3493^2 \left(3^2 \left(\frac{\omega}{\omega_0}\right)^2\right)}}, \omega_0 = (2\pi)(1 \text{ MHz})$$

61. a) Butterworth in Sallen and Key

$$\pi = 3, \omega_0 = (2\pi)(1.42\text{MHz})$$

$$P_k = \omega_0 \cdot \exp\left(\frac{j\pi}{2}\right) \exp\left(j\frac{2k-1}{2n}\pi\right), \quad k=1,2,3.$$

$$P_1 = \omega_0 \exp\left(j\frac{2\pi}{3}\right) = (2\pi)(1.42\text{MHz}) \times \left(\cos\frac{2\pi}{3} + j\sin\frac{2\pi}{3}\right).$$

$$P_2 = \omega_0 \exp(j\pi) = -(2\pi)(1.42\text{MHz})$$

$$P_3 = \omega_0 \exp\left(j\frac{4\pi}{3}\right) = (2\pi)(1.42\text{MHz}) \times \left(\cos\frac{2\pi}{3} - j\sin\frac{2\pi}{3}\right)$$

$$H_{p,1/3}(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)}$$

$$= \frac{[2\pi \times (1.42\text{MHz})]^2}{s^2 - [4\pi \times (1.42\text{MHz}) \cos\frac{2\pi}{3}]s + [2\pi \times (1.42\text{MHz})]^2}$$

$$\omega_n = 2\pi \times 1.42\text{MHz} \left( = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \right)$$

$$\frac{\omega_n}{Q} = 2\pi \times 1.42\text{MHz} \cdot \cos\left(\frac{2\pi}{3}\right) \Rightarrow Q = \frac{-1}{2 \cos\left(\frac{2\pi}{3}\right)} \left( = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}} \right)$$


$$\text{Let } C_1 = 4C_2, R_1 = R_2, \text{ so that it satisfies } Q = \frac{-1}{2 \cos\left(\frac{2\pi}{3}\right)} = 1$$

$$\text{Also } \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = 2\pi \times 1.42\text{MHz}$$

$$\text{Let } R_1 = R_2 = 1\text{k}\Omega \Rightarrow C_1 = 224\text{pF}, C_2 = 56\text{pF}$$

$$P_2 = -W_0, \quad \frac{1}{R_3 C_3} = (2\pi)(1.42 \text{ MHz})$$
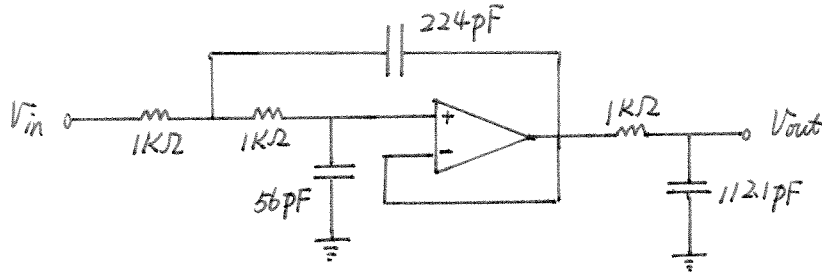
$$\text{Let } R_3 = 1 \text{ k}\Omega \Rightarrow C_3 = 112.1 \text{ pF}$$



Chebyshev in Sallen and Key

$$P_k = -W_0 \sin \frac{(2k-1)\pi}{2n} \sinh \left( \frac{1}{n} \sinh^{-1} \frac{1}{\epsilon} \right) + j W_0 \cos \frac{(2k-1)\pi}{2n} \cosh \left( \frac{1}{n} \sinh^{-1} \frac{1}{\epsilon} \right)$$

$$n=2, \quad W_0 = (2\pi)(1 \text{ MHz}), \quad \epsilon = 0.3493, \quad K=1, 2.$$

$$P_{1,2} = -0.7128 W_0 \pm j 1.0041 W_0$$

$$H_{SK}(s) = \frac{(s-P_1)(s-P_2)}{(s-P_1)(s-P_2)} = \frac{(1.2314)^2 W_0^2}{s^2 + 1.4256 W_0 s + (1.2314)^2 W_0^2}$$

$$W_n = 1.2314 W_0 = (2\pi)(1.2314 \text{ MHz})$$


$$\frac{W_n}{Q} = 1.4256 W_0 \Rightarrow Q = \frac{1.2314}{1.4256} = 0.8638$$

$$W_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$

$$\text{Let } R_1 = R_2 \quad Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 2984.4$$

$$\frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = W_n = 2\pi(1.2314 \text{ MHz}), \Rightarrow \frac{1}{R_1 C_2 \sqrt{2984.4}} = 2\pi(1.2314 \text{ MHz})$$
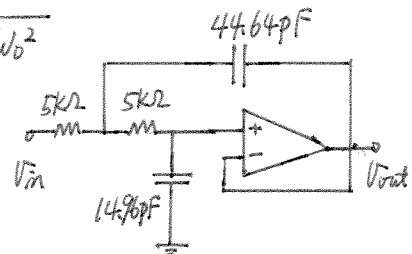
$$\text{Let } R_1 = R_2 = 5 \text{ k}\Omega \Rightarrow C_2 = 14.96 \text{ pF}, \quad C_1 = 44.64 \text{ pF}$$



b). Butterworth with SK

$$n = 4, \omega_0 = (2\pi)(1.6\text{MHz})$$

$$P_k = \omega_0 \exp(j\frac{\pi}{2}) \exp(j\frac{2k-1}{2n}\pi), \quad k=1, 2, 3, 4.$$

$$P_1 = \omega_0 \exp(j\frac{5\pi}{8}), \quad P_2 = \omega_0 \exp(j\frac{7\pi}{8}), \quad P_3 = \omega_0 \exp(-j\frac{5\pi}{8}), \quad P_4 = \omega_0 \exp(-j\frac{7\pi}{8})$$

$$H_{SK1,4}(s) = \frac{(-P_1)(-P_4)}{(s-P_1)(s-P_4)} = \frac{[(2\pi)(1.6 \times 10^6)]^2}{s^2 - [4\pi(1.6 \times 10^6) \cos(\frac{5\pi}{8})]s + [2\pi(1.6 \times 10^6)]^2}$$

$$\omega_n = 2\pi \times 1.6 \times 10^6$$

$$\frac{\omega_n}{\alpha} = (4\pi)(1.6 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow \alpha = 1.31.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \alpha = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}.$$


$$\text{Let } R_1 = R_2, \quad \alpha = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4\alpha^2 = 6.83.$$

$$\omega_n = \frac{1}{\sqrt{6.83} R_1 C_2} = 2\pi \times 1.6 \times 10^6$$

$$\text{Let } R_1 = R_2 = 5\text{K}\Omega \Rightarrow C_2 = 7.61\text{pF}, \quad C_1 = 52\text{pF}.$$

Similarly,  $H_{SK2,3}(s) = \frac{(-P_2)(-P_3)}{(s-P_2)(s-P_3)}$ , it can be derived for  $H_{SK2,3}$ .
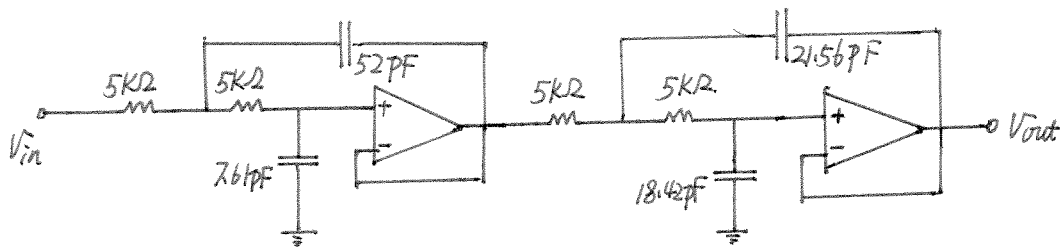
$$R_1 = R_2 = 5\text{K}\Omega, \quad C_2 = 18.42\text{pF}, \quad C_1 = 21.55\text{pF}.$$



(b) Chebyshev in SK.

$$n = 3, \omega_0 = (2\pi)(1 \times 10^6) \cdot \epsilon = 0.1526$$

$$P_1 = -\omega_0(0.9694) \sin\left(\frac{1}{6}\pi\right) + j\omega_0(1.3927) \cos\left(\frac{\pi}{6}\right) = -0.4847\omega_0 + j1.2061\omega_0$$

$$P_2 = -\omega_0(0.9694) \sin\left(\frac{3}{6}\pi\right) + j\omega_0(1.3927) \cos\left(\frac{3\pi}{6}\right) = -0.9496\omega_0$$

$$P_3 = -\omega_0(0.9694) \sin\left(\frac{5}{6}\pi\right) + j\omega_0(1.3927) \sin\left(\frac{5\pi}{6}\right) = -0.4847\omega_0 + j1.2061\omega_0$$

$$H_{SK}(s) = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{1.3^2 \omega_0^2}{s^2 + 0.9694\omega_0 s + (1.3)^2 \omega_0^2}$$

$$\omega_n = 1.3\omega_0$$

$$\frac{\omega_n}{Q} = 0.9694\omega_0 \Rightarrow Q = 1.3410$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 C_1 / C_2}$$

$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = (2Q)^2 = 7.1931$$


$$\omega_n = \frac{1}{\sqrt{7.1931} R_1 C_2} = (1.3)(2\pi)(1 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5 \text{ k}\Omega \Rightarrow C_1 = 9.13 \text{ pF} \Rightarrow C_2 = 65.67 \text{ pF}$$

$$P_2 = (2\pi)(0.9694 \times 10^6), \text{ and}$$

$$\frac{1}{R_3 C_3} = P_2$$
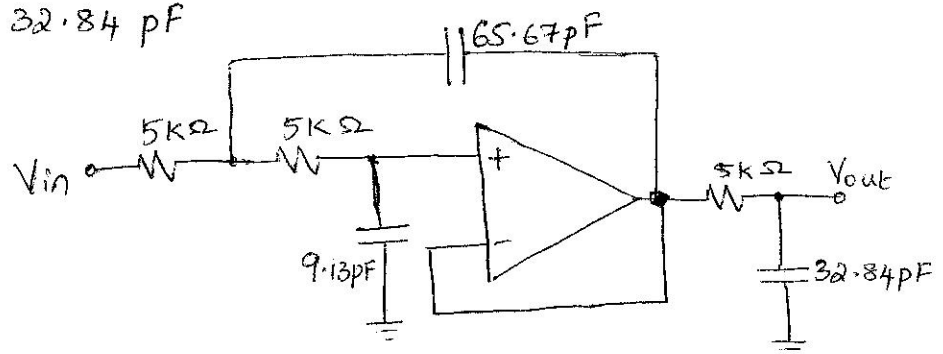
$$\text{Let } R_3 = 5 \text{ k}\Omega \Rightarrow C_3 = 32.84 \text{ pF}$$





c). Butterworth in SK.

$$n=3, \omega_0 = (2\pi)(1.27 \times 10^6)$$

$$P_k = \omega_0 \exp(j\frac{\pi}{2}) \exp(j\frac{2k-1}{2n}\pi), \quad k=1, 2, 3.$$

$$H_{p,3}(s) = \frac{(s-P_1)(s-P_3)}{(s-P_1)(s-P_3)} = \frac{[(2\pi)(1.27 \times 10^6)]^2}{s^2 - [4\pi \times (1.27 \times 10^6) \cos(\frac{2\pi}{3})]s + [2\pi(1.27 \times 10^6)]^2}$$

$$\omega_n = (2\pi)(1.27 \times 10^6)$$

$$\frac{\omega_n}{\omega} = (4\pi)(1.27 \times 10^6) \cos(\frac{2\pi}{3}) \Rightarrow Q=1.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$


$$\text{Let } C_1 = 4C_2, R_1 = R_2$$

$$\omega_n = \frac{1}{2R_1 C_2} = (2\pi)(1.27 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 12.53 \text{ pF}, C_1 = 50.13 \text{ pF}.$$

$$P_2 = -\omega_0 = (2\pi)(1.27 \times 10^6) = \frac{1}{R_3 C_3}$$
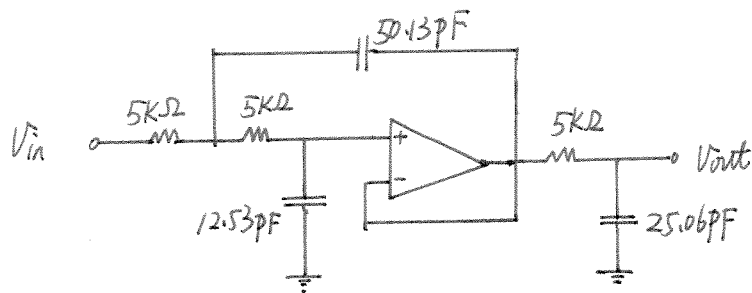
$$\text{Let } R_3 = 5k\Omega \Rightarrow C_3 = 25.06 \text{ pF}$$



c). Chebyshev in SK.

$$n=3, \epsilon \leq 0.5089, \omega_0 = (2\pi)(10^6)$$

$$p_1 = -0.2470\omega_0 + j0.9660\omega_0$$

$$p_2 = -0.4941\omega_0$$

$$p_3 = -0.2470\omega_0 - j0.9660\omega_0$$

$$H_{p,3}(s) = \frac{(-p_1)(-p_3)}{(s-p_1)(s-p_3)} = \frac{[(2\pi)(0.9971 \times 10^6)]^2}{s^2 + (0.4940)(2\pi)(10^6)s + (2\pi \times 0.9971 \times 10^6)^2}$$

$$\omega_n = (2\pi)(0.9971 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.4940)(2\pi \times 10^6) \Rightarrow Q = 2.02.$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$

$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 16.296$$


$$\omega_n = \frac{1}{\sqrt{16.296} R_1 C_2} = (2\pi)(0.9971 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5 \text{ k}\Omega \Rightarrow C_2 = 7.91 \text{ pF} \Rightarrow C_1 = 128.87 \text{ pF}$$

$$R_2 = 2\pi \times 0.4941 \times 10^6 = \frac{1}{R_3 C_3}$$

$$\text{Let } R_3 = 5 \text{ k}\Omega$$

$$\Rightarrow C_3 = 64.42 \text{ pF}$$

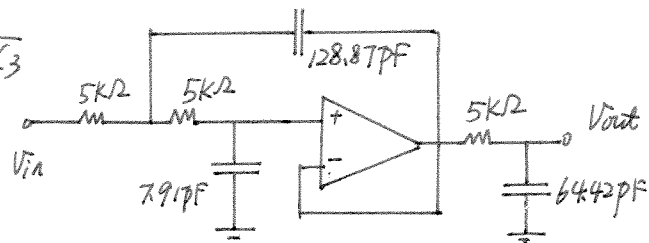

d). Butterworth in SK.

$$n=4, \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$P_k = \omega_0 \exp(j\frac{\pi}{2}) \exp(j\frac{2k-1}{2n}\pi), \quad k=1,2,3,4.$$

$$H_{SK,4}(s) = \frac{(-P_1)(-P_4)}{(s-P_1)(s-P_4)} = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_n = \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$\frac{\omega_n}{\alpha} = 4\pi(1.3 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow Q = 1.31$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}}$$


$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{2} \sqrt{\frac{C_1}{C_2}} \Rightarrow \frac{C_1}{C_2} = 4Q^2 = 6.828$$

$$\omega_n = \frac{1}{\sqrt{6.828} R_1 C_2} = (2\pi)(1.3 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 9.37pF \Rightarrow C_1 = 63.98pF$$

Similarly,  $H_{SK,3}(s) = \frac{(-P_2)(-P_3)}{(s-P_2)(s-P_3)}$ . It can be derived that
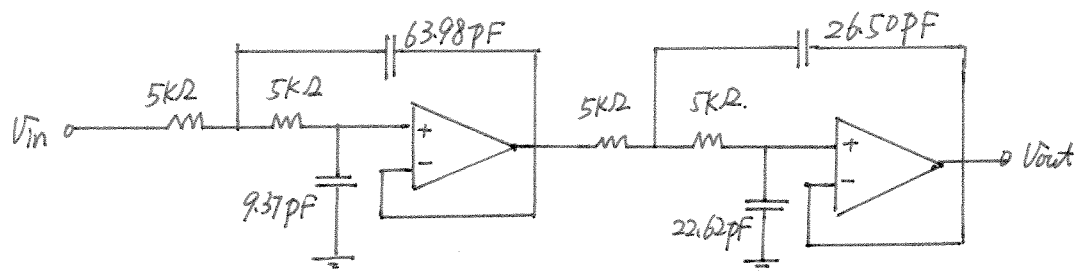
$$R_1 = R_2 = 5k\Omega, \quad C_2 = 22.62pF, \quad C_1 = 26.50pF.$$



d). Chebyshev in SK.

$$n=3, \epsilon=0.3493, \omega_0=(2\pi)(1 \times 10^6)$$

$$P_1 = -\omega_0 0.6265 \sin\left(\frac{1}{8}\pi\right) + j\omega_0(1.1800) \cos\left(\frac{1}{8}\pi\right)$$

$$P_2 = -\omega_0 0.6265$$

$$P_3 = -\omega_0 0.6265 \sin\left(\frac{5}{8}\pi\right) + j\omega_0(1.1800) \cos\left(\frac{5}{8}\pi\right)$$

$$H_{P13} = \frac{(-P_1)(-P_3)}{(s-P_1)(s-P_3)} = \frac{[2\pi \times 1.069 \times 10^6]^2}{s^2 + (0.6265)(2\pi \times 10^6)s + (2\pi \times 1.069 \times 10^6)^2}$$

$$\omega_n = (2\pi)(1.069 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.6265)(2\pi \times 10^6) \Rightarrow Q = 1.7063$$


$$\text{Let } R_1 = R_2 \Rightarrow Q = \frac{1}{R_1 + R_2} \sqrt{R_1 R_2 \frac{C_1}{C_2}} = \frac{1}{2} \sqrt{\frac{Q}{C_2}} \Rightarrow \frac{Q}{C_2} = 4Q^2 = 11.6459$$

$$\omega_n = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} = \frac{1}{\sqrt{11.6459} R_1 C_2} = (2\pi)(1.069 \times 10^6)$$

$$\text{Let } R_1 = R_2 = 5k\Omega \Rightarrow C_2 = 8.73 \text{ pF} \Rightarrow C_1 = 101.62 \text{ pF}$$

$$-P_2 = (0.6265)(2\pi \times 10^6) = \frac{1}{R_3 C_3}$$
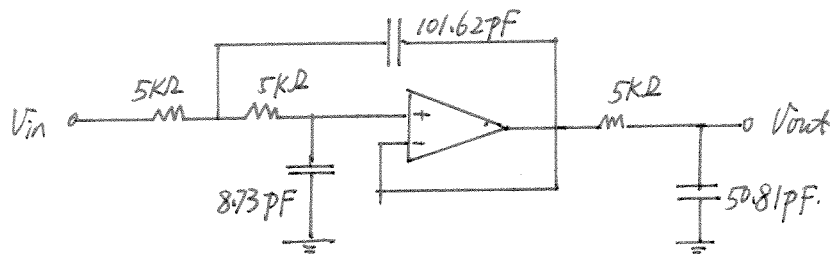
$$\text{Let } R_3 = 5k\Omega \Rightarrow C_3 = 50.81 \text{ pF}$$



62) a). Butterworth TT

$$n=3, \omega_0 = (2\pi)(1.42 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{2\pi}{3}), P_2 = -\omega_0, P_3 = \omega_0 \exp(-j\frac{2\pi}{3})$$

$$H_{P,3} = \frac{[2\pi \times (1.42 \times 10^6)]^2}{s^2 - [4\pi \times (1.42 \times 10^6) \cos(\frac{2\pi}{3})]s + [2\pi \times 1.42 \times 10^6]^2}$$

$$\omega_n = (2\pi)(1.42 \times 10^6)$$


$$Q = \frac{-1}{2 \cos(\frac{2\pi}{3})} = 1$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = R_3 \sqrt{\frac{C_1}{C_2 R_2 R_4}}$$

$$\text{Let } R_2 = R_4 = R_3 = 5K\Omega, \quad C_1 = C_2 = 22.42 \text{ pF}$$

$$-P_2 = + (2\pi)(1.42 \times 10^6) = \frac{1}{R_3 C_3}$$
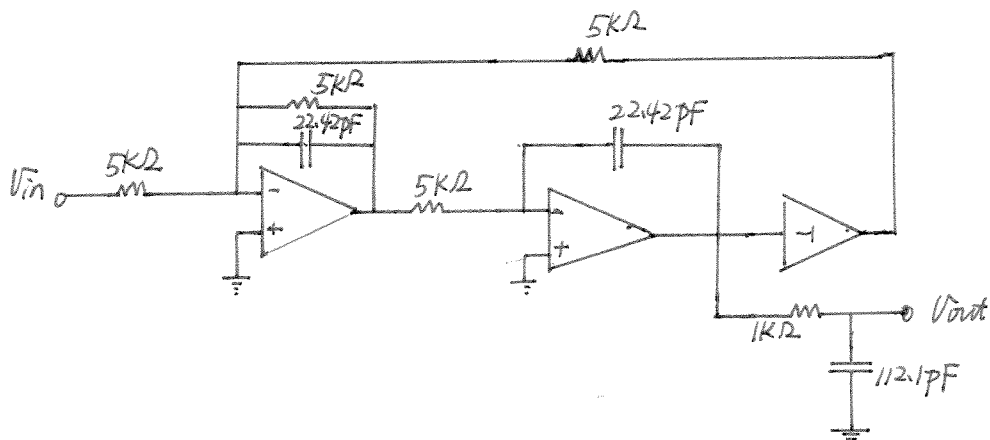
$$\text{Let } R_3 = 1K\Omega \Rightarrow C_3 = 112.1 \text{ pF}$$



$R_1 = R_2 = R_4$ , to match low frequency gain requirement.

a) Chebyshev TT

$$n=2, \omega_0 = (2\pi)(1\text{MHz}), \epsilon = 0.3493$$

$$H_{P_{0.2}} = \frac{(1.2314)^2 \omega_0^2}{s^2 + 1.4256 \omega_0 s + (1.2314)^2 \omega_0^2}$$

$$\omega_n = (2\pi)(1.2314 \times 10^6)$$

$$Q = \frac{1.2314}{1.4256} = 0.8638$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$


$$\text{Let } C_1 = C_2, R_2 = R_4$$

$$\omega_n = \frac{1}{R_2 C_1} = (2\pi)(1.2314 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5\text{k}\Omega, C_1 = C_2 = 25.85\text{pF}$$

$R_1 = R_2 = R_4 = 5\text{k}\Omega$ , to match low frequency gain of unity.
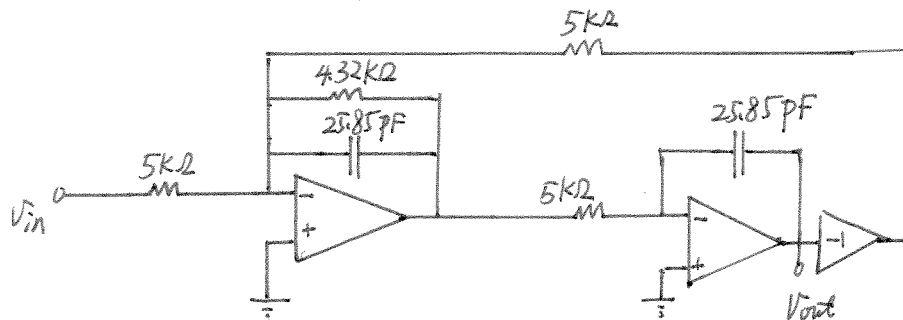
$$Q = \frac{R_3}{R_2} \Rightarrow R_3 = 4.32\text{k}\Omega.$$



b). Butterworth with TT

$$n=4, \omega_0 = (2\pi)(1.6 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{5\pi}{8}), \quad P_4 = \omega_0 \exp(-j\frac{5\pi}{8})$$

$$P_2 = \omega_0 \exp(j\frac{7\pi}{8}), \quad P_3 = \omega_0 \exp(-j\frac{7\pi}{8})$$

$$H_{P_{1,4}} = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_n = \omega_0 = (2\pi)(1.6 \times 10^6)$$

$$\frac{\omega_n}{\alpha} = (4\pi)(1.6 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow \alpha = 1.31$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad \alpha = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\text{Let } R_2 = R_4, C_1 = C_2 \Rightarrow \omega_n = \frac{1}{R_2 C_1} = (2\pi)(1.6 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5\text{K}\Omega \Rightarrow C_1 = C_2 = 19.89\text{pF}$$

$R_1 = R_2 = R_4 = 5\text{K}\Omega$ , to obtain a low-frequency gain of unity.

$$\alpha = \frac{R_3}{R_2} = 1.31 \Rightarrow R_3 = 1.31 R_2 = 6.55\text{K}\Omega$$

Similarly for  $H_{P_{2,3}}$ , it can be derived that  $R_1 = R_2 = R_4 = 5\text{K}\Omega, R_3 = 2.7\text{K}\Omega$

$$C_1 = C_2 = 19.89\text{pF}$$

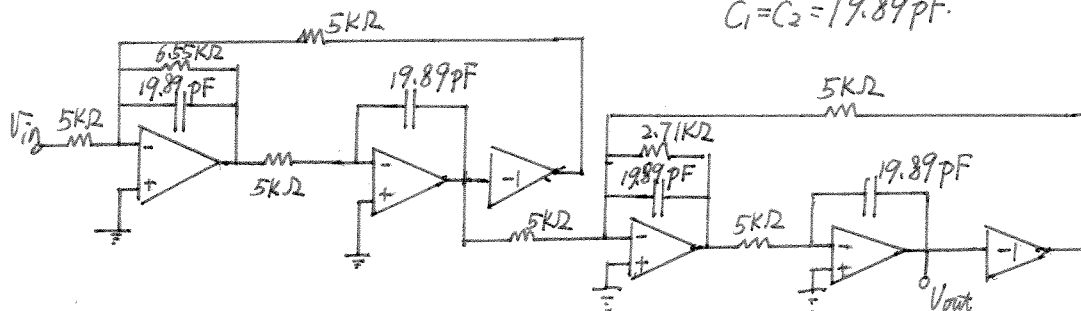

b). Chebyshev with TT

$$n=3, \epsilon = 0.1526, \omega_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = 0.4847\omega_0 \pm j 1.2061\omega_0$$

$$P_2 = -0.9694\omega_0$$

$$H_{p,3}(s) = \frac{(1.3)^2 \omega_0^2}{s^2 + 0.9694\omega_0 s + (1.3)^2 \omega_0^2}$$

$$\omega_n = 1.3\omega_0, \quad \frac{\omega_n}{Q} = 0.9694\omega_0$$

$$Q = \frac{1.3}{0.9694} = 1.3410$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$


$$\text{Let } R_2 = R_4, C_1 = C_2, \quad \frac{1}{R_2 C_1} = (1.3)(2\pi)(10^6)$$

$$\text{Let } R_2 = R_4 = 5\text{K}\Omega, \Rightarrow C_1 = C_2 = 24.49\text{pF}$$

$R_1 = R_2 = R_4 = 5\text{K}\Omega$ , to obtain low-frequency gain of unity.

$$R_3 = Q R_2 = 6.705\text{K}\Omega$$
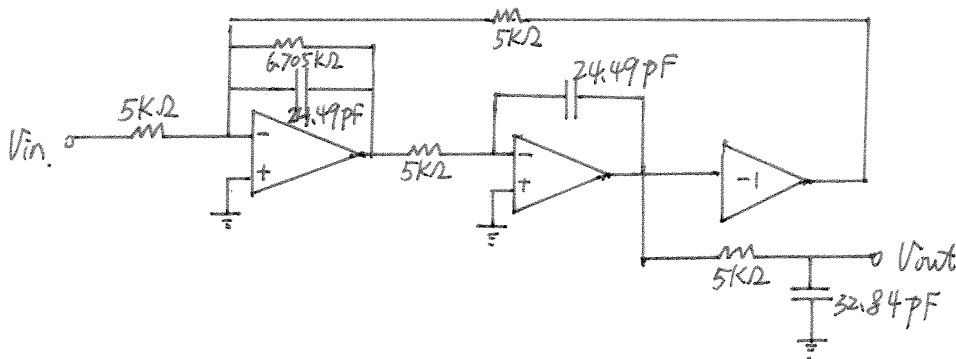
$$-P_2 = (2\pi)(0.9694 \times 10^6) = \frac{1}{R_5 C_5}, \quad \text{Let } R_5 = 5\text{K}\Omega \Rightarrow C_5 = 32.84\text{pF}$$





c) Butterworth with TT

$$n=3, \omega_0 = (2\pi)(1.27 \times 10^6)$$

$$P_1 = \omega_0 \exp(j\frac{2\pi}{3}), \quad P_3 = \omega_0 \exp(-j\frac{2\pi}{3}), \quad P_2 = -\omega_0.$$

$$H_{P_{1,3}}(s) = \frac{[(2\pi)(1.27 \times 10^6)]^2}{s^2 - [(4\pi)(1.27 \times 10^6) \cos(\frac{2\pi}{3})]s + [(2\pi)(1.27 \times 10^6)]^2}$$

$$\omega_n = (2\pi)(1.27 \times 10^6), \quad \frac{\omega_n}{Q} = (4\pi)(1.27 \times 10^6) \cos(\frac{2\pi}{3})$$

$$Q = -\frac{1}{2 \cos(\frac{2\pi}{3})} = 1.$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$

$$\text{Let } R_2 = R_4, \quad C_1 = C_2, \quad \frac{1}{R_2 C_1} = (2\pi)(1.27 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5 \text{ k}\Omega \Rightarrow C_1 = C_2 = 25.06 \text{ pF.}$$

$$R_1 = R_2 = R_4 = 5 \text{ k}\Omega, \text{ to obtain Low-frequency gain of unity.}$$

$$R_3 = Q R_2 = 5 \text{ k}\Omega.$$

$$-P_2 = \omega_0 \Rightarrow \frac{1}{R_5 C_5} = (2\pi)(1.27 \times 10^6)$$
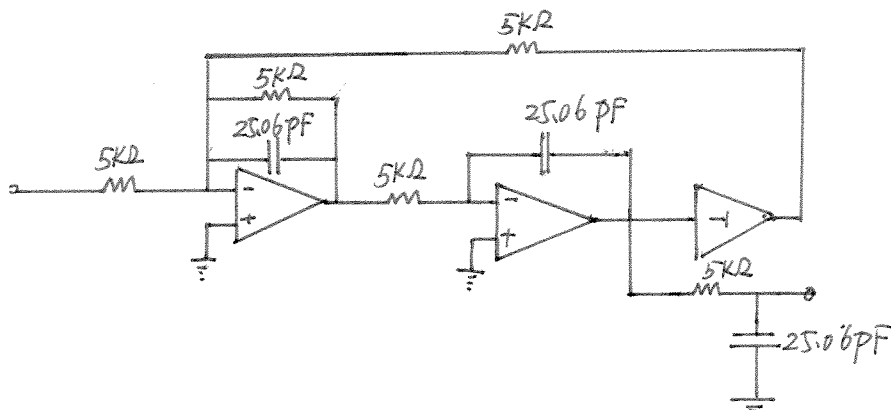
$$\text{Let } R_5 = 5 \text{ k}\Omega \Rightarrow C_5 = 25.06 \text{ pF}$$



c) Chebyshev TT

$$n=3, \epsilon=0.5089, \omega_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = -0.2470 \omega_0 \pm j 0.9660 \omega_0, \quad P_2 = -0.4941 \omega_0$$

$$H_{P_{1,3}}(s) = \frac{[(2\pi)(10.9971 \times 10^6)]^2}{s^2 + (0.4940)(2\pi \times 10^6)s + [2\pi \times 0.9771 \times 10^6]^2}$$

$$\omega_n = (2\pi)(10.9971 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.4940)(2\pi \times 10^6) \Rightarrow Q = 2.02$$

$$Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}, \quad \omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}$$


$$\text{Let } R_2 = R_4, C_1 = C_2 \Rightarrow \frac{1}{R_2 C_1} = (2\pi)(10.9971 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5 \text{ k}\Omega \Rightarrow C_1 = C_2 = 31.92 \text{ pF}$$

$R_1 = R_2 = R_4 = 5 \text{ k}\Omega$ , to obtain Low-frequency gain of unity.

$$R_3 = QR_2 = 10.1 \text{ k}\Omega.$$
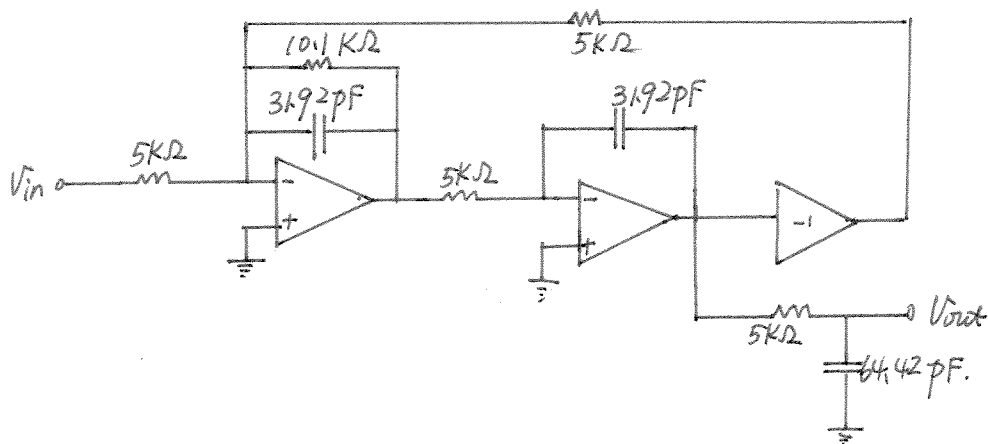
$$-P_2 = (2\pi)(0.4941 \times 10^6) = \frac{1}{R_5 C_5}. \quad \text{Let } R_5 = 5 \text{ k}\Omega \Rightarrow C_5 = 64.42 \text{ pF}.$$



d). Butterworth in TT

$$n=4, \omega_0 = (2\pi)(1.3 \times 10^6)$$

$$P_{1,4} = \omega_0 \exp(\pm j \frac{5\pi}{8}), \quad P_{2,3} = \omega_0 \exp(\pm j \frac{7\pi}{8})$$

$$H_{P_{1,4}}(s) = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{5\pi}{8})]s + \omega_0^2}$$

$$\omega_n = (2\pi)(1.3 \times 10^6)$$

$$\frac{\omega_n}{Q} = (4\pi)(1.3 \times 10^6) \cos(\frac{5\pi}{8}) \Rightarrow Q = -\frac{1}{2\cos(\frac{5\pi}{8})} = 1.31$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$

$$\text{Let } R_2 = R_4, C_1 = C_2, \omega_n = \frac{1}{\sqrt{R_2^2 C_1^2}} = \frac{1}{R_2 C_1} = (2\pi)(1.3 \times 10^6)$$


$$\text{Let } R_2 = R_4 = 5k\Omega \Rightarrow C_1 = C_2 = 24.49 \text{ pF}$$

$$R_1 = R_2 = R_4 = 5k\Omega, \text{ to obtain a low-frequency gain of unity.}$$

$$R_3 = Q R_2 = 6.55k\Omega$$

$$\text{Similarly, } H_{P_{2,3}}(s) = \frac{\omega_0^2}{s^2 - [2\omega_0 \cos(\frac{7\pi}{8})]s + \omega_0^2}$$

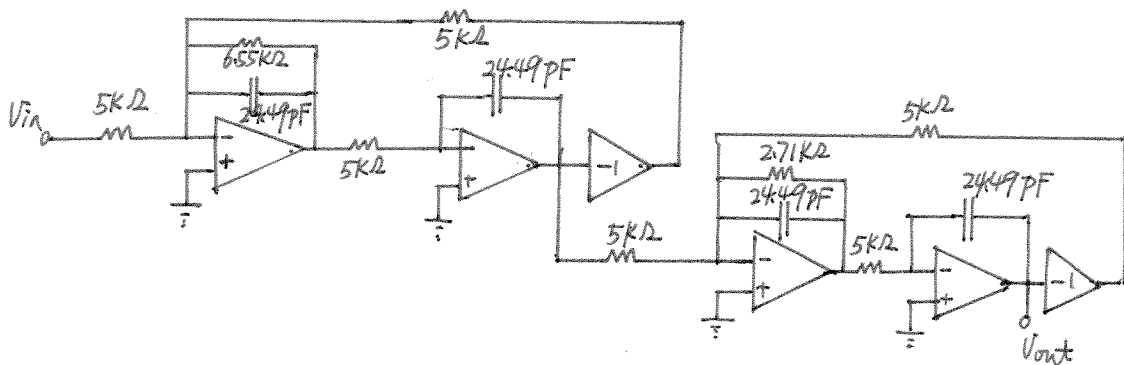It can be obtained that  $R_1 = R_2 = R_4 = 5k\Omega, R_3 = 2.71k\Omega, C_1 = C_2 = 24.49 \text{ pF}$ .



d). Chebyshev TT

$$n=3, \epsilon = 0.3493, \omega_0 = (2\pi)(1 \times 10^6)$$

$$P_{1,3} = -0.3133 \omega_0 \pm j1.022 \omega_0, \quad P_2 = -0.6265 \omega_0$$

$$H_{P_{1,3}} = \frac{[2\pi \times 1.069 \times 10^6]^2}{s^2 + (0.6265)(2\pi \times 10^6)s + (2\pi \times 1.069 \times 10^6)^2}$$

$$\omega_n = (2\pi)(1.069 \times 10^6)$$

$$\frac{\omega_n}{Q} = (0.6265)(2\pi \times 10^6) \Rightarrow Q = \frac{1.069}{0.6265} = 1.7063$$

$$\omega_n = \frac{1}{\sqrt{R_2 R_4 C_1 C_2}}, \quad Q = R_3 \sqrt{\frac{C_1}{R_2 R_4 C_2}}$$


$$\text{Let } R_2 = R_4, \quad C_1 = C_2, \quad \frac{1}{R_2 C_1} = (2\pi)(1.069 \times 10^6)$$

$$\text{Let } R_2 = R_4 = 5 \text{ k}\Omega \Rightarrow C_1 = C_2 = 29.78 \text{ pF}$$


$R_1 = R_2 = R_4 = 5 \text{ k}\Omega$ , to obtain a low-frequency gain of unity.

$$R_3 = Q R_2 = 8.53 \text{ k}\Omega$$
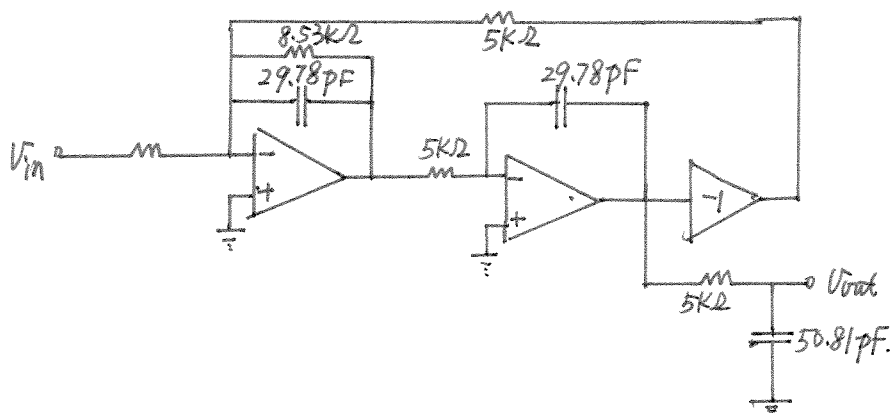
$$-P_2 = 0.6265 \times (2\pi \times 10^6) = \frac{1}{R_5 C_5}, \quad \text{Let } R_5 = 5 \text{ k}\Omega \Rightarrow C_5 = 50.81 \text{ pF}$$



1.

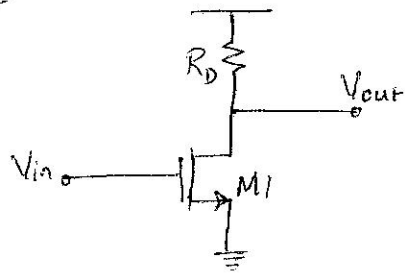

$M_1$  operates in the triode region

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right]$$

$$V_{out} = V_{DD} - R_D I_D$$

$$R_D = 10 \text{ k}$$

$$\left(\frac{W}{L}\right)_1 = \frac{3}{0.18}$$

$$V_{out, min} = ? \quad \text{when } V_{in} = V_{DD}$$

$$V_{out, min} = V_{DD} - R_D I_{D, max}$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right] \times R_D$$


If the second term in the square brackets is neglected. Then

$$V_{out, min} \approx \frac{V_{DD}}{1 + \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH}) R_D}$$

$$= \frac{1.8}{1 + 100 \times 10^{-6} \times \frac{3}{0.18} \times (1.8 - 0.4) \times 10^5}$$

$$V_{out, min} \approx 7.7 \text{ mV}$$

2.

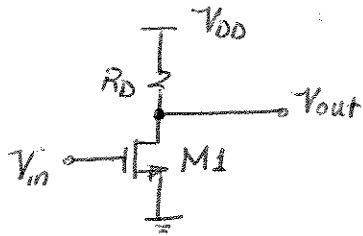

$$V_{out, min} \leq 100 \text{ mV}$$

$$R_D = 5 \text{ k}\Omega$$

$$\left(\frac{W}{L}\right)_{1, min} = ?$$

Output low level establishes for  $V_{in} = V_{DD}$ , driving  $M_1$  into the triode region.

$$I_{D, max} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right]$$

$$V_{out, min} = V_{DD} - R_D \times I_{D, max}$$


$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right] \times R_D$$

$$\left(\frac{W}{L}\right)_1 = \frac{V_{DD} - V_{out, min}}{\frac{1}{2} \mu_n C_{ox} \left[ 2(V_{DD} - V_{TH}) V_{out, min} - V_{out, min}^2 \right] \times R_D}$$

$$\left(\frac{W}{L}\right)_{1, min} = \frac{1.8 - 100 \times 10^{-3}}{\frac{1}{2} \times 100 \times 10^{-6} \left[ 2(1.8 - 0.4) 100 \times 10^{-3} - (100 \times 10^{-3})^2 \right] \times 5 \times 10^3}$$

$$\boxed{\left(\frac{W}{L}\right)_{1, min} = 25}$$

3.

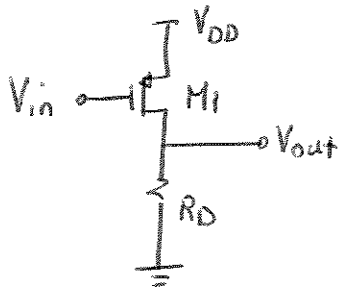

$$\left(\frac{W}{L}\right)_1 = 20/0.18, \quad R_D = 5K$$

$$V_{OL}, V_{OH} = ?$$

$$(1) \quad V_{in} = V_{DD} \rightarrow M_1 \text{ off} \rightarrow I_D = 0 \rightarrow \boxed{V_{out} = V_{OL} = 0}$$

(2)  $V_{in} = 0 \rightarrow M_1$  operates in the triode region

$$I_D = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{SG} - |V_{THP}|) V_{SD} - V_{SD}^2 \right]$$

$$I_{D, \max} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - |V_{THP}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

$$I_{D, \max} = \frac{V_{out}}{R_D} \quad (2)$$

Equating (1) and (2) and neglecting the second order term in the brackets

$$\frac{V_{out}}{R_D} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_1 \times 2(V_{DD} - |V_{THP}|)(-V_{out} + V_{DD})$$

$$V_{out} \left[ \frac{1}{R_D} + \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|) \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|) V_{DD}$$


$$V_{out} = \frac{R_D}{R_D + \frac{1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - |V_{THP}|)}} V_{DD}$$

$$V_{out} = \frac{5000}{5000 + \frac{1}{50 \times 10^{-6} \times \left(\frac{20}{0.18}\right) \times (1.8 - 0.5)}} \times 1.8$$

$$V_{out} = V_{OH} = 1.75 \text{ V}$$



4.

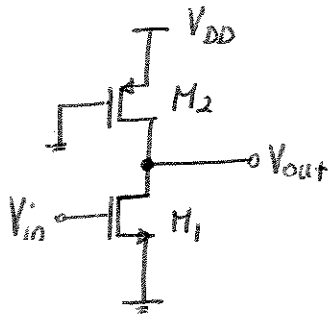

$$\left(\frac{W}{L}\right)_1 = 3/0.18 \quad \left(\frac{W}{L}\right)_2 = 2/0.18$$

(a) if  $V_{in} = V_{DD}$ ,  $M_2$  saturated  $\rightarrow V_{OL} = ?$

(b) if  $V_{in} = V_{out} \rightarrow V_{in} = ?$

$$(a) I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{THP}|)^2$$

$$I_{D2} = \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (1.8 - 0.5)^2, \text{ Note that } V_{SG} = V_{DD}$$

$$I_{D2} = 4.7 \times 10^{-4} \text{ A}$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{GS} - V_{THN}) V_{DS} - V_{DS}^2 \right]$$

$$= \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{THN}) V_{OL} - V_{OL}^2 \right]$$

However  $I_{D1} = I_{D2}$

$$4.7 \times 10^{-4} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{3}{0.18}\right) \left[ 2(1.8 - 0.4) V_{OL} - V_{OL}^2 \right]$$

Neglecting the second-order term yields:

$$\boxed{V_{OL} = 0.2 \text{ V}}$$

As  $(V_{in} - V_{THN}) = (V_{DD} - V_{THN}) = (1.8 - 0.4) = 1.4 > V_{DS1} = V_{OL} = 0.2 \text{ V}$

The assumption of  $M_1$  being in Triode region is correct

We define,  $V_x = V_{in} - V_{TH,N} \rightarrow V_{in} = V_x + V_{TH,N}$

$$\frac{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2} V_x^2 = 2(V_{DD} - |V_{TH,P}|)(V_{DD} - V_{TH,N} - V_x) - (V_{DD} - V_{TH,N} - V_x)^2$$

$$\frac{100}{50} \times \frac{3/0.18}{2/0.18} V_x^2 = 2(1.8 - 0.5)(1.8 - 0.4 - V_x) - (1.8 - 0.4 - V_x)^2$$

$$3V_x^2 = 2.6(1.4 - V_x) - (1.4 - V_x)^2$$

$$3V_x^2 = 3.64 - 2.6V_x - 1.96 + 2.8V_x - V_x^2$$

$$4V_x^2 - 0.2V_x - 1.68 = 0$$

$$V_x = \frac{0.2 \pm \sqrt{0.2^2 + 4 \times 4 \times 1.68}}{8} \rightarrow \boxed{V_x = 0.67 \text{ V}}$$

$$V_{in} = V_x + V_{TH,N} = 0.67 + 0.4 \rightarrow \boxed{V_{in} = V_{out} = 1 \text{ V}}$$

This value of  $V_{out}$  guarantees that  $M_2$  operates in the triode region.

Now, let's investigate the region of operation of  $M_2$

$$V_{SD2} = V_{DD} - V_{out}$$

$$= 1.8 - 0.2$$

$$V_{SD2} = 1.6 \text{ V}$$

$$V_{SG2} - |V_{THP}| = V_{DD} - |V_{THP}|$$

$$= 1.8 - 0.5$$

$$V_{SG2} - |V_{THP}| = 1.3$$

As  $V_{SD2} > V_{SG2} - |V_{THP}|$ ,  $M_2$  operates in the saturation region and the initial assumption is valid.


(b) As  $V_{in} = V_{out} \rightarrow M_1$  is saturated.

We assume that  $M_2$  is in the triode region and check the

validity of this assumption

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{THP}|) \times (V_{DD} - V_{in}) - (V_{DD} - V_{in})^2 \right]$$

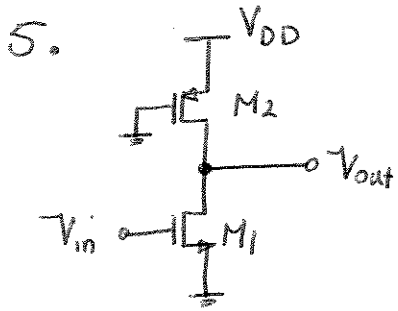

$$V_{OL} \leq 100 \text{ mV}$$

$$\left(\frac{W}{L}\right)_2 = 3/0.18$$

$$\left(\frac{W}{L}\right)_{1, \min} = ?$$

$V_{in} = V_{DD} \rightarrow M_1$  operates in the triode region and  $M_2$  in the saturation.

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{SG} - |V_{TH,P}|)^2$$

$$= \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{3}{0.18}\right) \times (1.8 - 0.5)^2$$

$$I_{D2} = 7.041 \times 10^{-4} \text{ A}$$


$$I_{D1} = I_{D2} = 7.041 \times 10^{-4} \text{ A}$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{GS} - V_{TH,N}) V_{DS} - V_{DS}^2 \right]$$

$$7.041 \times 10^{-4} = \frac{1}{2} \times 100 \times 10^{-6} \left(\frac{W}{L}\right)_1 \left[ 2(1.8 - 0.4) 0.1 - (0.1)^2 \right]$$

$$\left(\frac{W}{L}\right)_{1, \min} = 52.16$$

6)

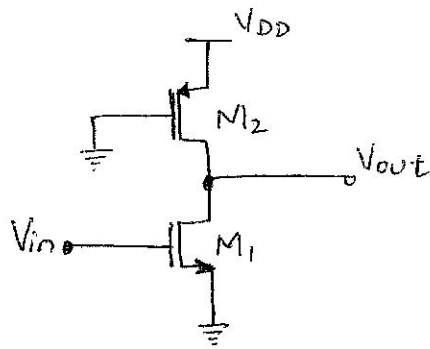

$$V_{OL} \leq 80 \text{ mV}$$

$$\left(\frac{W}{L}\right)_1 = \frac{2}{0.18}$$

$$\left(\frac{W}{L}\right)_{2,\max}$$

$V_{in} = V_{DD} \rightarrow M_1$  operates in the triode region and  $M_2$  in the saturation

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{GS} - V_{TH,N}) V_{DS} - V_{DS}^2 \right]$$

$$I_{D1} = \frac{1}{2} \times (100 \times 10^{-6}) \times \left(\frac{2}{0.18}\right) \times \left[ 2(1.8 - 0.4)0.08 - 0.08^2 \right]$$

$$I_{D1} = 1.2 \times 10^{-4} \text{ A}$$


$$I_{D2} = I_{D1} = 1.2 \times 10^{-4} \text{ A}$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ V_{GS} - |V_{TH2,P}| \right]^2$$

$$1.2 \times 10^{-4} = \frac{1}{2} \times 50 \times 10^{-6} \left(\frac{W}{L}\right)_2 (1.8 - 0.5)^2$$

$$\left(\frac{W}{L}\right)_{2,\max} = 2.84$$

7.

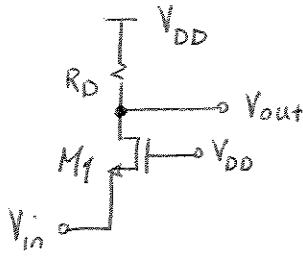

(a) If  $V_{in} = 0$ ,  $V_{DD}$ ,  $V_{out} = ?$

If  $V_{in} = 0 \rightarrow M_1$  operates in the triode region.


$$R_{on1} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH,N})}$$


$$V_{out} \cong \frac{R_{on1}}{R_{on1} + R_D} \times V_{DD} \rightarrow V_{out} \cong \frac{1}{1 + \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH,N}) R_D} \times V_{DD}$$

If  $V_{in} = V_{DD} \rightarrow V_{out} = V_{DD}$

No, this circuit does not invert.

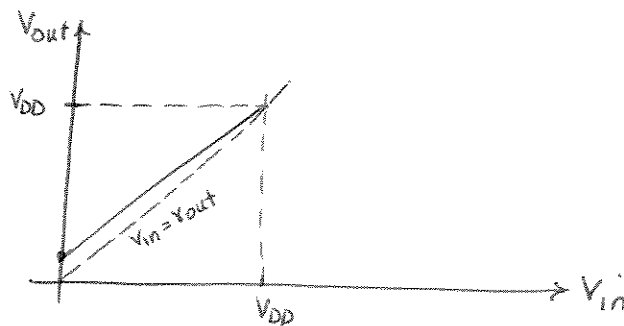(b) A trip point cannot be found for this circuit because  $V_{out} = V_{in}$  line does not intersect the transfer characteristic of this buffer.



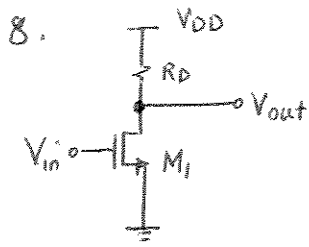

$$\left(\frac{W}{L}\right)_1 = 5/0.18$$

$$R_D = 2\text{K}\Omega$$

$$NM_L, NM_H = ?$$

Small signal gain of the circuit is equal to  $-g_m R_D$

$$\text{and } g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N}) R_D = 1, \quad V_{GS} = V_{IL}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH} = \frac{1}{100 \times 10 \times \frac{5}{0.18} \times 2000} + 0.4$$

$$\boxed{V_{IL} = 0.58\text{V}}$$

To determine  $NM_H$ , we note that  $V_{in}$  drives  $M_1$  into the triode region

$$V_{out} = V_{DD} - R_D I_D$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH,N}) V_{out} - V_{out}^2 \right] R_D \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH,N}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] R_D + 2V_{out}$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1 \quad \text{at } V_{IH}$$

$$-1 = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ -2(V_{in} - V_{TH,N}) + 2V_{out} \right] R_D$$

$$I = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ -V_{in}^2 + V_{TH,N} + 2V_{out} \right] R_D$$

$$\frac{I}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} = -(V_{in} - V_{TH,N}) + 2V_{out}$$

$$V_{out} = \frac{I}{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{2} \rightarrow V_{out} = 0.5V_{in} - 0.11$$

Substituting this in (1) yields:


$$0.5V_{in} - 0.11 = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \left[ 2(V_{in} - 0.4)(0.5V_{in} - 0.11) - (0.5V_{in} - 0.11)^2 \right]$$

$$0.75V_{in}^2 - 0.33V_{in} - 0.6117 = 0$$

$$V_{in} = V_{IH} = 1.15$$
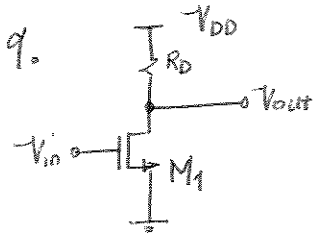
$$NM_H = V_{DD} - V_{IH} = 1.8 - 1.15 \rightarrow \boxed{NM_H = 0.65V}$$





Small signal gain of the inverter is equal to  $-g_m R_D$

and  $g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$

$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N}) R_D = 1$ ,  $V_{GS} = V_{IL}$

$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 1 \rightarrow V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH,N}$

If we double the value of  $\left(\frac{W}{L}\right)_1$  or  $R_D$

$V_{IL} = \frac{1}{100 \times 10^8 \times \frac{5}{0.18} \times 20000 \times 2} + 0.4 \rightarrow \boxed{V_{IL} = 0.49}$

To determine  $NM_H$ , we note that  $V_{in}$  drives  $M_1$  into the triode region

$V_{out} = V_{DD} - R_D I_D$

$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH}) V_{out} - V_{out}^2 \right] R_D$  (1)

$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2 V_{out} + 2(V_{in} - V_{TH}) \frac{\partial V_{out}}{\partial V_{in}} - 2 V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right]$

$\frac{\partial V_{out}}{\partial V_{in}} = -1$  (a)  $V_{IH}$

$V_{out} = \frac{1}{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{2}$

Doubling  $\left(\frac{W}{L}\right)_1$  or  $R_D$  leads to

$$V_{out} = 0.5V_{in} - 0.155$$


Substituting in (1) yields:

$$0.5V_{in} - 0.155 = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \times 2 \left[ 2(V_{in} - 0.4)(0.5V_{in} - 0.155) - (0.5V_{in} - 0.155)^2 \right]$$

$$0.75V_{in}^2 - 0.465V_{in} - 0.251925 = 0$$

$$V_{in} = 0.967 \text{ V} \rightarrow NM_H = 1.8 - 0.967$$

$$NM_H = 0.833 \text{ V}$$

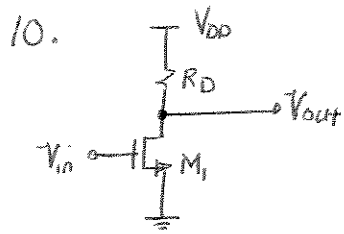

$$\left(\frac{W}{L}\right)_1 = \frac{5}{0.18}$$

$$R_D = 2K$$

$$NM_L \text{ and } NM_H = ? \text{ if } \frac{\partial V_{out}}{\partial V_{in}} = -0.5 \text{ instead of } -1$$

Small signal gain of the inverter is equal to " $-g_m R_D$ "

$$\text{and } g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{TH,N})$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH,N}) R_D = 0.5$$

$$V_{IL} = \frac{1}{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{TH,N} = \frac{1}{2 \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000} + 0.4$$

$$\boxed{V_{IL} = 0.49} \text{ which is less than } 0.58 \text{ obtained in problem 8.}$$

To determine  $NM_H$ , note that  $M_1$  operates in the triode region

$$V_{out} = V_{DD} - R_D I_D$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH}) V_{out} - V_{out}^2 \right] R_D \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{TH}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] R_D$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -0.5 \quad \text{at } V_{IH}$$

$$-0.5 = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ -(V_{in} - V_{TH,N}) + 3V_{out} \right] R_D$$

$$V_{out} = \frac{1}{3\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + \frac{V_{in} - V_{TH,N}}{3} \rightarrow V_{out} = -73.33 \times 10^{-3} + 0.33 V_{in}^0$$

$$\text{or } V_{out} = -\frac{0.22}{3} + \frac{V_{in}}{3}$$

Substituting in (1) yields:

$$-\frac{0.22}{3} + \frac{V_{in}}{3} = 1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times \frac{5}{0.18} \times 2000 \left[ 2(V_{in} - 0.4) \left( -\frac{0.22}{3} + \frac{V_{in}}{3} \right) - \left( -\frac{0.22}{3} + \frac{V_{in}}{3} \right)^2 \right]$$

$$5V_{in}^2 - 2.2V_{in} - 5.59 = 0$$


$$V_{in} = V_{IH} = 1.3$$

$$NM_H = 1.8 - 1.3$$

$$\boxed{NM_H = 0.5V}$$

less than 0.65V obtained in problem 8 because

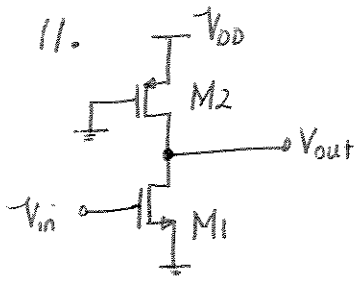$V_{IH}$  is now further pushed up toward  $V_{DD}$ .



$$\left(\frac{W}{L}\right)_1 = \frac{4}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{9}{0.18}$$

To calculate  $V_{IL}$ , we assume that  $M_1$  and  $M_2$  operate in saturation and triode region respectively.

$$I_{D1} = I_{D2} \quad (1)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH,P}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH,P}|) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) - 2(V_{DD} - V_{out}) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) \right]$$

By substituting  $\frac{\partial V_{out}}{\partial V_{in}}$  with "-1" in the above relationship:

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH,P}|) - 2(V_{DD} - V_{out}) \right]$$

$$V_{out} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH,N}) + |V_{TH,P}|}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} = \frac{100 \times 10^{-6} \times 4 / 0.18 (V_{in} - 0.4) + 0.5}{50 \times 10^{-6} \times 9 / 0.18}$$

$$V_{out} = 0.144 + 0.88 V_{in}^{\circ} \quad \text{or} \quad \boxed{V_{out} = \frac{8}{9} V_{in}^{\circ} + \frac{1.3}{9}}$$

Substituting  $V_{out}$  in (1) by the derivation versus  $V_{in}$  gives:

$$136 V_{in}^2 - 108.8 V_{in}^{\circ} - 115.13 = 0$$

$$\boxed{V_{in}^{\circ} = V_{IL} = NM_L = 1.4 V}$$

To calculate  $V_{IH}$ , we assume that  $M_1$  and  $M_2$  operate in the triode and saturation region respectively.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{THN})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{THP}|)^2 \quad (2)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{THN}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = 0$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} - 2(V_{in} - V_{THN}) + 2V_{out} \right] = 0$$

$$V_{out} = \frac{V_{in} - V_{THN}}{2} \quad \text{Substituted in (2) yields:}$$

$$V_{in} = \sqrt{\frac{3}{2} (V_{DD} - |V_{THP}|)} + V_{THN}$$

$V_{in} = 2 \rightarrow V_{out} = 0.8$  This value of  $V_{out}$  puts  $M_2$  into the triode region so our initial assumption is not correct

Now we assume that both  $M_1$  and  $M_2$  operate in the triode region.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{THN})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{THP}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (3)$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{THN}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times$$

$$\left[ 2(V_{DD} - |V_{THP}|) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) - 2(V_{DD} - V_{out}) \left(-\frac{\partial V_{out}}{\partial V_{in}}\right) \right]$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} - 2(V_{in} - V_{THN}) + 2V_{out} \right] = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times$$

$$\left[ 2(V_{DD} - |V_{THP}|) - 2(V_{DD} - V_{out}) \right]$$

$$V_{out} = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN}) - |V_{THP}|}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}$$

$$2 \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 - 1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}$$

$$V_{out} = \frac{8}{7} V_{in} - 1.1$$

After substituting in (3) it leads to:


$$2.1769 V_{in}^2 - 4.19 V_{in} + 0.576 = 0$$

$$\boxed{V_{in} = 1.77 \text{ V}}$$

$V_{out} = 0.93 \text{ V} \rightarrow$  The assumption is correct

$$V_{IH} = 1.77 \text{ V} \rightarrow NM_H = 1.8 - 1.77$$

$$\boxed{NM_H = 0.03 \text{ V}}$$

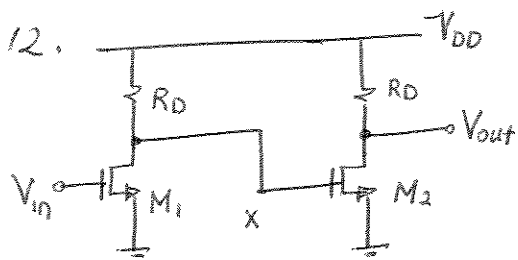

The small signal gain of the circuit is equal to  $-g_m R_D$  and since

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{GS} - V_{THN})$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{THN}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D} + V_{THN} = \frac{2}{5} + 0.4 ; \left(\frac{W}{L}\right)_{1,2} = 5$$

Now we calculate the output of  $M_1$  for  $V_{in} = V_{DD}$ :

$$V_{DD} - R_D I_D = V_{out}$$

$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{THN}) V_{out} - V_{out}^2 \right] R_D = V_{out} ; \left(\frac{W}{L}\right)_{1,2} = 5$$

$$1.8 - \frac{1}{2} \times 100 \times 10^{-6} \times 5 \left[ 2(1.8 - 0.4) \left(\frac{2}{5} + 0.4\right) - \left(\frac{2}{5} + 0.4\right)^2 \right] \times 5000 = \left(\frac{2}{5} + 0.4\right)$$

$$1.8 - 0.25 \times \left[ 2.8(2 + 0.45) - 5 \left(\frac{2}{5} + 0.4\right)^2 \right] = \frac{2}{5} + 0.4$$

$$1.85 - 0.25 \times \left[ 2.8(2.5 + 0.45^2) - 5 \left(\frac{2}{5} + 0.4\right)^2 \right] = 2 + 0.45$$






$$1.85 - 0.25 \times \left[ 5.65 + 1.125^2 - 4 - 1.65 - 0.165^2 \right] = 2 + 0.45$$

$$0.245^2 - 0.45 + 1 = 0$$


$$\Delta < 0!$$



13.

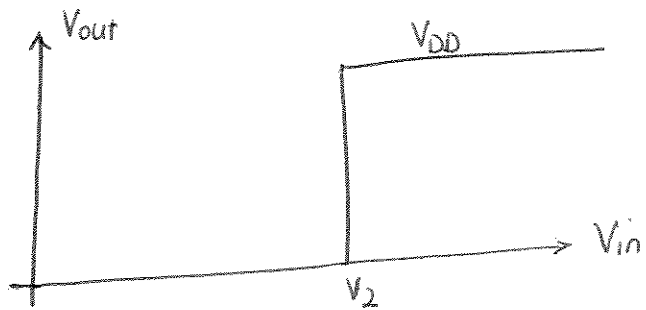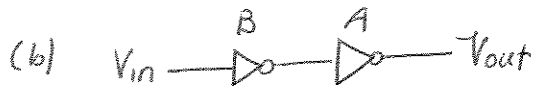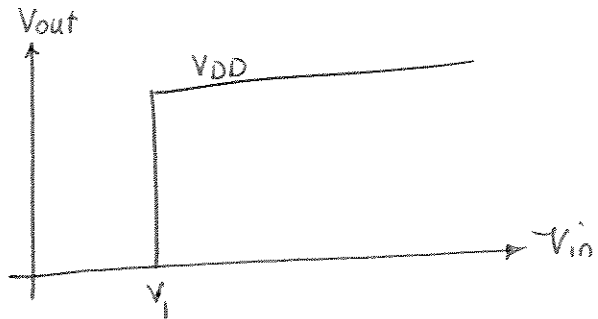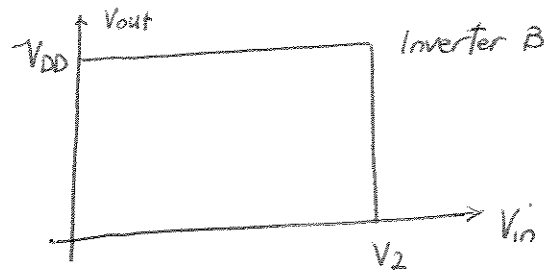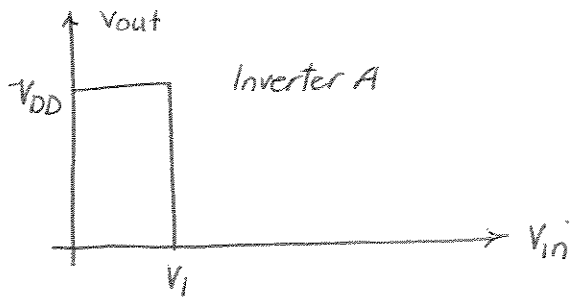

14.

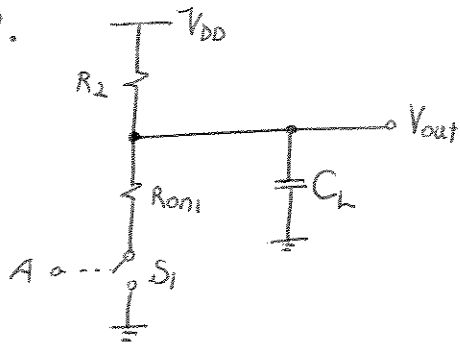

$$R_{on1} \ll R_2 \rightarrow V_{out, min} \approx 0$$

$$(a) \quad V_{out}(t) = V_{out}(\bar{0}) + [V_{DD} - V_{out}(\bar{0})] \left(1 - \exp\left(-\frac{t}{R_2 C_L}\right)\right) \quad t > 0$$

$$\text{Note that } V_{out}(\bar{0}) = 0, \quad V_{out}(\infty) = V_{DD}$$

$$V_{out}(t) = V_{DD} \times \left(1 - \exp\left(-\frac{t}{R_2 C_L}\right)\right) \quad t > 0$$

$$0.95 V_{DD} = V_{DD} \times \left(1 - \exp\left(-\frac{T_{95\%}}{R_2 C_L}\right)\right)$$

$$\boxed{T_{95\%} = 3 R_2 C_L}$$

$$(b) \quad V_{out}(t) = V_{out}(\bar{0}) + [V_{out}(\infty) - V_{out}(\bar{0})] \times \left(1 - \exp\left(-\frac{t}{R_2 C_L}\right)\right)$$

$$V_{out}(t) = V_{DD} + [0 - V_{DD}] \times \left(1 - \exp\left(-\frac{t}{R_2 C_L}\right)\right)$$


$$V_{out}(t) = V_{DD} \exp\left(-\frac{t}{R_2 C_L}\right)$$

$$0.05 V_{DD} = V_{DD} \exp\left(-\frac{T_{0.05}}{R_2 C_L}\right)$$

$$\boxed{T_{5\%} = 3 R_2 C_L}$$

If  $R_{on1} \ll R_2$ , inverter exhibits equal rise and fall time (or low-to-high and high-to-low delay) at the output.

15.

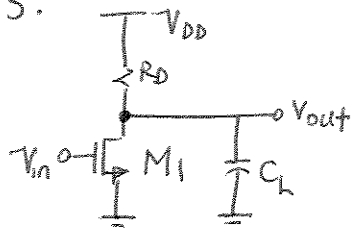

$$C_L = 50 \text{ fF}$$

$$T_R = 100 \text{ pS}$$


$$T_R = 3 \tau_{out}$$

$$R_{D,max} = ?$$

$$T_R = 3 R_D C_L = 100 \text{ pS}$$

$$R_D \leq \frac{100 \text{ pS}}{3 \times 50 \text{ fF}}$$

$$R_D \leq 666.67 \Omega$$

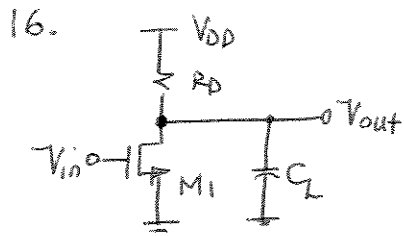

$$C_L = 100 \text{ fF}$$

$$V_{out, \min} = 50 \text{ mV}$$

$$T_R = 200 \text{ pS}$$

$$R_D, \left(\frac{W}{L}\right)_1 = ?$$

$$T_R = 3\tau_{out}$$

$$T_R = 3R_D C_L$$

$$200 \times 10^{-12} = 3 \times R_D \times 100 \times 10^{-15}$$

$$R_D = 666.667 \Omega$$

$V_{in} = V_{DD}$  places  $M_1$  in the triode region

$$V_{out, \min} = V_{DD} - R_D I_{D, \max}$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D \left[ 2(V_{DD} - V_{THN}) V_{out, \min} - V_{out, \min}^2 \right]$$


Neglecting the 2<sup>nd</sup> order term in the square brackets yields:

$$V_{out, \min} = \frac{V_{DD}}{1 + \mu_n C_{ox} \left(\frac{W}{L}\right)_1 R_D (V_{DD} - V_{THN})}$$

$$50 \times 10^{-3} = \frac{1.8}{1 + 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 \times 666.7 \times (1.8 - 0.4)}$$

$$\left(\frac{W}{L}\right)_1 = 375$$

17.

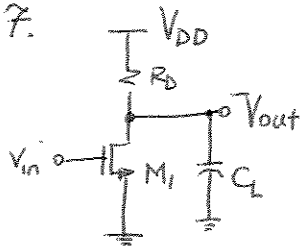

$$C_L = 100 \text{ fF}$$

$$V_{out, \min} \approx 0$$

$$I_{D, \max} \leq 1 \text{ mA}$$

$$T_{R, \min} = 0$$

$$I_{D, \max} = \frac{V_{DD} - V_{out, \min}}{R_D}$$

$$10^{-3} = \frac{1.8 - 0}{R_D}$$

$$R_D = 1.8 \text{ k}\Omega$$

$$V_{out}(t) = V_{out}(\bar{0}) + [V_{out}(\infty) - V_{out}(\bar{0})] \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$

$$V_{out}(t) = V_{out, \min} + [V_{DD} - V_{out, \min}] \times \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$


$$V_{out}(t) = V_{DD} \left(1 - \exp\left(-\frac{t}{R_D C_L}\right)\right) \quad t > 0$$

$$0.1 V_{DD} = V_{DD} \left(1 - \exp\left(-\frac{T_{10\%}}{R_D C_L}\right)\right) \rightarrow T_{10\%} = 0.105 R_D C_L$$

$$0.9 V_{DD} = V_{DD} \left(1 - \exp\left(-\frac{T_{90\%}}{R_D C_L}\right)\right) \rightarrow T_{90\%} = 2.3 R_D C_L$$

$$T_R = T_{90\%} - T_{10\%} = 2.197 R_D C_L = 2.197 \times 1.8 \times 10^3 \times 100 \times 10^{-15}$$

$$T_R = 395.5 \text{ pS}$$

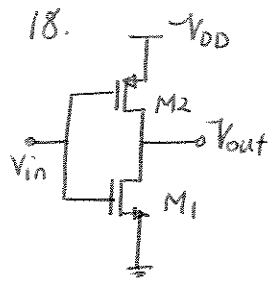

$$\left(\frac{W}{L}\right)_1 = \frac{2}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{3}{0.18}$$

$$I_{D1} = I_{D2}$$

At the trip point  $V_{in} = V_{out}$ ; therefore, both  $M_1$  and  $M_2$  operate in the Saturation region.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in}^o - V_{THN})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in}^o - |V_{THP}|)^2$$


$$V_{in}^o = \frac{V_{DD} - |V_{THP}| + \sqrt{\frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2} \times V_{THN}}}{1 + \sqrt{\frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}}}$$

$$V_{in}^o = \frac{1.8 - 0.5 + \left(\frac{100 \times 2}{50 \times 3}\right)^{1/2} \times 0.4}{1 + \left(\frac{100 \times 2}{50 \times 3}\right)^{1/2}}$$


$$V_{in} = V_{out} = 0.82 \text{ V}$$

$$I_{D1} = I_{D2} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.82 - 0.4)^2$$

$$I_{D1} = I_{D2} = 97 \mu\text{A}$$

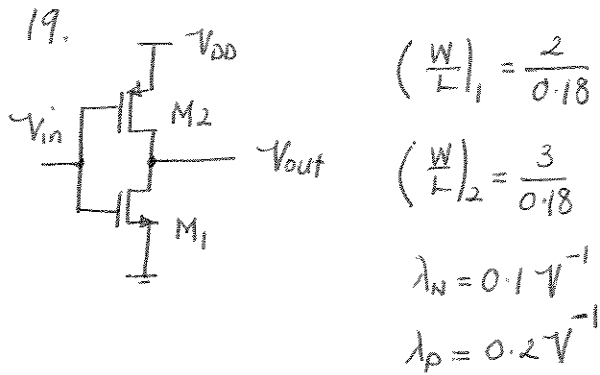

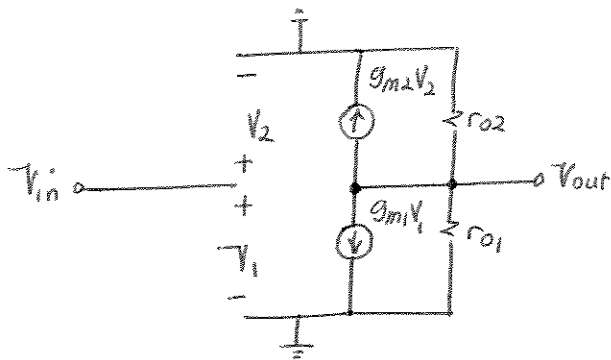Replacing  $M_1$  and  $M_2$  with their small-signal model in the saturation region yields:



$$V_{out} = (-g_{m1}V_1 - g_{m2}V_2)(r_{o1} || r_{o2})$$

$$V_1 = V_2 = V_{in}$$

$$V_{out} = -(g_{m1} + g_{m2})(r_{o1} || r_{o2})V_{in}$$

$$\frac{V_{out}}{V_{in}} = -(g_{m1} + g_{m2})(r_{o1} || r_{o2})$$

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN})^2$$

$$g_{m1} = \frac{\partial I_{D1}}{\partial V_{in}} = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{THN}) = \frac{2I_{D1}}{V_{in} - V_{THN}}$$

$$g_{m1} = \frac{2 \times 9.7 \times 10^{-5}}{(0.817 - 0.4)} \rightarrow \boxed{g_{m1} = 4.641 \times 10^{-4} \text{ S}}$$

$$g_{m2} = \frac{2I_{D2}}{(V_{SG} - |V_{THP}|)} = \frac{2 \times 9.7 \times 10^{-5}}{(1.8 - 0.817 - 0.5)} \rightarrow \boxed{g_{m2} = 4.02 \times 10^{-4} \text{ S}}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)^2 (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_o = \frac{\partial I_D}{\partial V_{DS}} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)^2 (V_{GS} - V_{TH})^2 \lambda \approx \lambda I_D$$

$$r_o \approx \frac{1}{\lambda I_D}$$

$$r_{oN} \approx \frac{1}{0.1 \times 9.7 \times 10^{-5}} = 103.17 \text{ K}\Omega$$

$$r_{oP} \approx \frac{1}{0.2 \times 9.7 \times 10^{-5}} = 51.58 \text{ K}\Omega$$

$$\text{Gain} = \frac{V_{out}}{V_{in}} = - (4.641 \times 10^{-4} + 4.02 \times 10^{-4}) (51.58 \text{ K} \parallel 103.17 \text{ K})$$

$$\boxed{\text{Gain} = -29.8}$$




20.

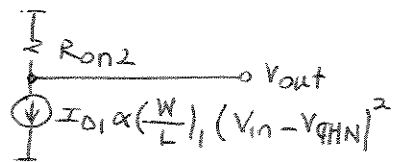(a) Length of  $M_1$  is increased

Let's assume that  $V_{in} < V_{TH1}$ , as a result  $M_1$  is off and  $M_2$  is on operating in the triode region. As  $V_{in}$  increases beyond  $V_{TH1}$ ,  $M_1$  starts pulling current (conducting) in the saturation region while  $M_2$  is still in the triode region, operating as a resistor; therefore,

CMOS inverter can be modelled as follows:



By increasing  $L_1$ ,  $I_{D1}$  is weakened due to the inverse proportionality; as a result, an excess  $V_{in}$  is required to drop  $V_{out}$  to the point where


$V_{out} = V_{in} + |V_{TH2}|$  and  $M_2$  is placed at the edge of saturation.

Therefore characteristic is shifted to the right and it will be steeper at the gain region where both  $M_1$  and  $M_2$  are in saturation region.

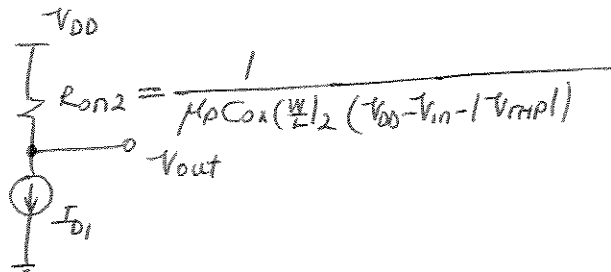
(b) Length of  $M_2$  is increased

Again if we assume that  $V_{in} < V_{TH1}$ ,  $M_1$  is off and  $M_2$  is operating in the triode region with no current. By increasing

$V_{in}$  above  $V_{TH1}$ ,  $M_1$  conducts in the saturation region while  $M_2$  is operating in the triode region. Using the same models as used in part (a) yields:



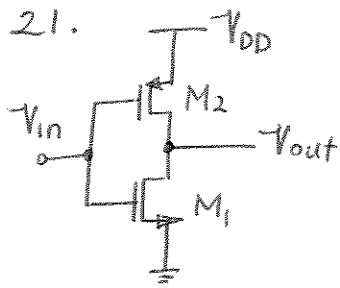
By increasing  $L_2$ ,  $R_{on2}$  becomes larger; as a result, lower value of  $I_{D1}$  causes comparable voltage drop at the output. This will drive  $M_2$  into the saturation with lower current ( $I_{D1}$ ) and, hence, lower value of  $V_{in}$ . Therefore, characteristic is shifted to the left and small signal gain will be higher.



$$\left(\frac{W}{L}\right)_1 = \frac{3}{0.18}$$

$$\left(\frac{W}{L}\right)_2 = \frac{7}{0.18}$$

VTC looks like the following figure

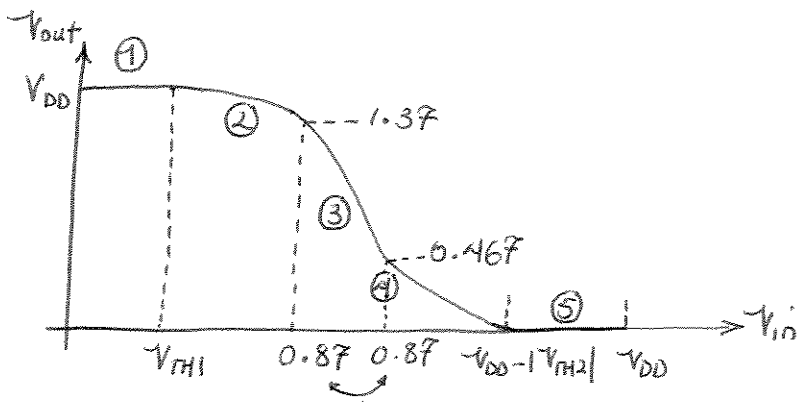

①  $M_1$  off,  $M_2$  in triode region

$$I_{D1} = \emptyset$$

$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|) V_{SD} - V_{SD}^2 \right] = \emptyset$$

$$V_{SD} = 0 \rightarrow V_{out} = V_{DD} \quad (1)$$

②  $M_1$  in saturation,  $M_2$  in triode region

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times (V_{in} - 0.4)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{7}{0.18} \times \left[ 2(1.8 - V_{in} - 0.5) \times (1.8 - V_{out}) - (1.8 - V_{out})^2 \right]$$

$$6(V_{in} - 0.4)^2 = 7 \left[ 2(1.3 - V_{in})(1.8 - V_{out}) - (1.8 - V_{out})^2 \right] \quad (2)$$

If  $V_{out}$  falls significantly,  $M_2$  enters saturation. That is  $V_{out} = V_{in} + |V_{TH2}|$ . Then  $M_2$  is about to exit the triode region.

Replacing  $V_{out}$  by  $V_{in} + |V_{TH2}|$  in (2) leads to:

$$6(V_{in} - 0.4)^2 = 7 \left[ 2(1.3 - V_{in})(1.8 - V_{in} - 0.5) - (1.8 - V_{in} - 0.5)^2 \right]$$

$$6(V_{in} - 0.4)^2 = 7(1.3 - V_{in})^2 \rightarrow \sqrt{\frac{6}{7}} (V_{in} - 0.4) = (1.3 - V_{in})$$

$$V_{in} = 0.867 \text{ V}, \quad V_{out} = 1.37 \text{ V}$$

$$(3) \quad \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_1 V_{out}) = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 [1 + \lambda_2 (V_{DD} - V_{out})]$$

$$-V_{out} = \frac{\mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 - \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2}{\lambda_2 \mu_p C_{ox} \left( \frac{W}{L} \right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 + \lambda_1 \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2}$$

$$-V_{out} = \frac{7(1.3 - V_{in})^2 - 6(V_{in} - 0.4)^2}{7\lambda_2(1.3 - V_{in})^2 + 6\lambda_1(V_{in} - 0.4)^2} \quad (3)$$

in region (3)  $M_1$  and  $M_2$  are both in saturation.

④  $M_1$  in triode region,  $M_2$  in saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times (V_{DD} - V_{in} - |V_{TH2}|)^2 \quad (4)$$
$$6 \left[ 2(V_{in} - 0.4)V_{out} - V_{out}^2 \right] = 7(1.3 - V_{in})^2$$

If  $V_{out}$  falls sufficiently,  $M_1$  enters the triode region. That is, if

$V_{in} = V_{out} + V_{TH1}$ , then  $M_1$  is about to enter the triode region.

By substituting  $V_{in}$  with  $V_{out} + 0.4$  in (4), we have:

$$6 \left[ 2V_{out}^2 - V_{out}^2 \right] = 7(0.9 - V_{out})^2$$

$$V_{out} = 0.467, \quad V_{in} = 0.867$$

As channel length modulation has been neglected in this calculation the value of input voltage that makes CMOS inverter transition from region (2) to (3) is

the same as that which makes inverter transition from region (3) to (4).


The slope in region (3) is infinit; however, we assume a finite slope in that region to emphasize the behavior of inverter as to producing a high gain.

⑤  $M_1$  in triode region,  $M_2$  off

$$I_{D2} = 0, \quad I_{D1} = 0$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = 0 \rightarrow V_{out} = 0$$

22.

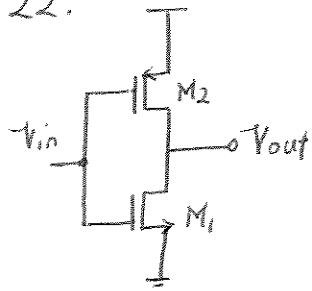

$$V_{in} = V_{out} = 0.5 \text{ V}$$

$M_1$  and  $M_2$  are both in saturation region

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 (0.5 - 0.4)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{W}{L}\right)_2 (1.8 - 0.5 - 0.5)^2$$

$$\left(\frac{W}{L}\right)_1 / \left(\frac{W}{L}\right)_2 = 32$$

23. The value of the trip point has to be larger than the threshold voltage of NMOS transistor,  $0.4\text{ V}$ . Therefore,  $0.3\text{ V}$  cannot be the trip point of such an inverter.


24.

(a) If the inverter exhibits a very high voltage gain around the trip point, the range of input voltage values which guarantees that  $M_1$  and  $M_2$  are in saturation region is very narrow. Therefore this range can be fairly approximated with only one value of input voltage.

(b)  $(W/L)_1 = 3/0.18$  and  $(W/L)_2 = 7/0.18$

To calculate the minimum input voltage at which both transistors operate in saturation we assume

$M_1$  saturation  
 $M_2$  triode

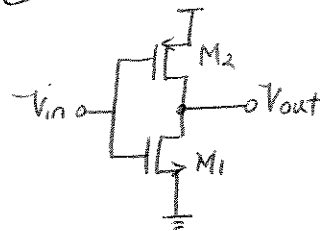

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|)(V_{out} - V_{DD}) - (V_{out} - V_{DD})^2 \right]$$

$V_{out} = V_{in} + |V_{TH2}|$  places  $M_2$  at the edge of saturation

$$2 \times 3 \times (V_{in} - 0.4)^2 = 7 \times \left[ 2(1.8 - V_{in} - 0.5)(1.8 - V_{in} - 0.5) - (1.8 - V_{in} - 0.5)^2 \right]$$

$$V_{in, \min} = 0.867$$

To calculate  $V_{in, \max}$ , we assume that  $M_1$  and  $M_2$  are in triode and saturation region respectively

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1})(V_{out} - V_{out}) \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$



When  $M_1$  is just going to leave the saturation and enters the triode region

$$V_{in} = V_{out} + 0.4^{(V_{TH1})}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times \left[ 2(V_{out} + V_{TH1} - V_{TH1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{7}{0.18} \times (V_{DD} - V_{in} - |V_{TH2}|)^2$$

$$\frac{6}{7} V_{out}^2 = (V_{DD} - V_{out} - |V_{TH1}| - |V_{TH2}|)^2$$

$$\frac{6}{7} V_{out}^2 = (0.9 - V_{out})^2$$

$$V_{out} = 0.467 \text{ V}, \quad V_{in} = 0.867 \text{ V}_{\text{max}}$$

To find the trip point,  $M_1$  and  $M_2$  are assumed to be in saturation.

$$I_{D1} = I_{D2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$


$$2 \times 3 \times (V_{in} - 0.4)^2 = 7 \times (1.8 - V_{in} - 0.5)^2$$

$$V_{in}^0 = 0.867 \text{ (a) trip point}$$







$$V_{in, \text{trip}} - V_{in, \text{min}} = 0$$

$$V_{in, \text{max}} - V_{in, \text{trip}} = 0$$

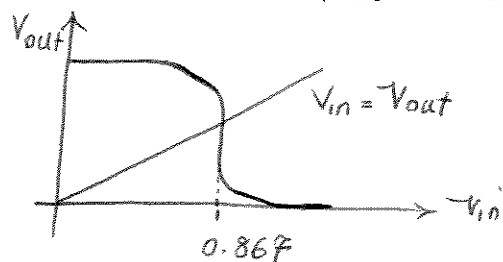
This result is not surprising because VTC of inverter has infinite slope at the region where both  $M_1$  and  $M_2$  are in saturation region



25.

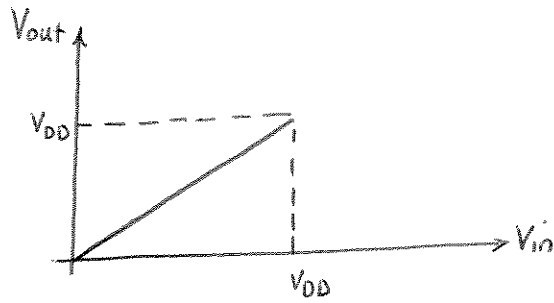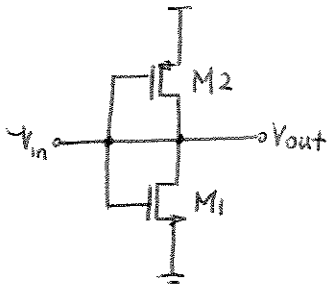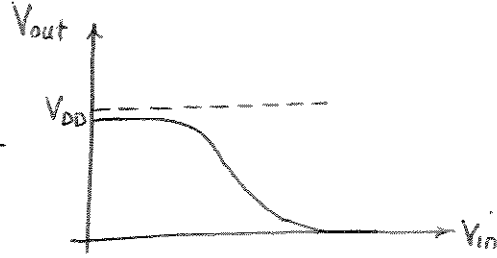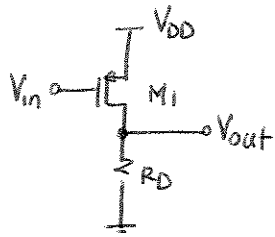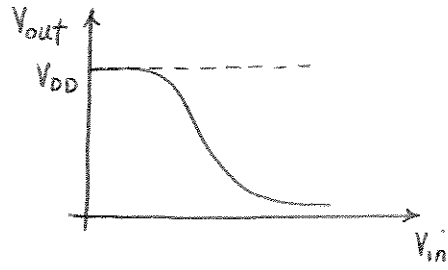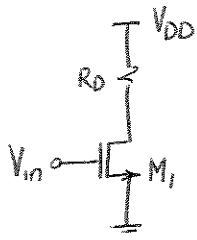

26.

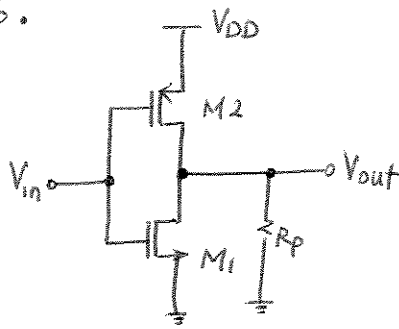


$$R_p = 2K$$

$$V_{OL}, V_{OH}, V_{in, trip} = ?$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

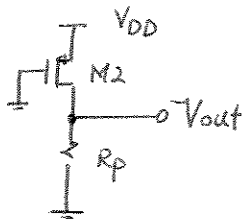To calculate  $V_{OH}$ ,  $V_{in}$  is assumed to be 0V



$$I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$I_{D2} = \frac{V_{out}}{R_p}$$

$$\frac{V_{out}}{R_p} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$V_{out} - 0.28V_{out} - 1.44 = 0$$

$$V_{out} = V_{OH} = 1.348V$$

$$V_{OL} = 0 \text{ because } M_2 \text{ is off for } V_{in} = V_{DD}$$


(a) trip point  $V_{in} = V_{out}$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{2000}$$

$$0.05V_{out}^2 + 0.59V_{out} - 0.3745 = 0 \rightarrow V_{in} = V_{out} = 0.6V$$

27)

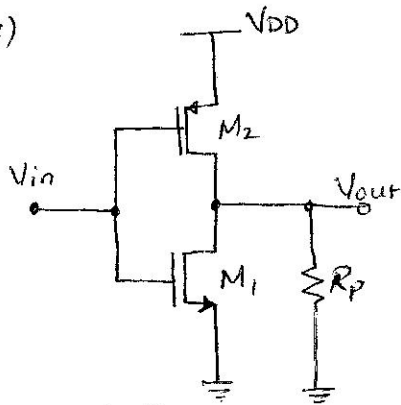

$$R_p = 2k$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

$$V_{in} = V_{out} = 0.6V \text{ @ trip point}$$

With  $R_p$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{2000}$$

$$0.05 V_{out}^2 + 0.59 V_{out} - 0.3745 = 0$$

$$V_{in} = V_{out} = 0.6V$$

$$I_{D1} = \frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \times (0.6 - 0.4)^2$$

$$I_{D1} = 3.33 \times 10^{-5} A$$

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} = 3.33 \times 10^{-5} + \frac{0.6}{2000}$$

$$I_{D2} = 3.35 \times 10^{-4} A$$

$$g_{m1} = \frac{2I_{D1}}{V_{eff1}} = \frac{2 \times 3.33 \times 10^{-5}}{(0.6 - 0.4)} \rightarrow g_{m1} = 333 \mu S$$

$$g_{m2} = \frac{2I_{D2}}{V_{eff2}} = \frac{2 \times 3.35 \times 10^{-4}}{(1.8 - 0.6 - 0.5)} \rightarrow g_{m2} = 957 \mu S$$

$$A_v = -(g_{m1} + g_{m2}) * R_p$$


$$A_v = -(333 \times 10^{-6} + 957 \times 10^{-6}) \times 2000$$

$$A_v = -2.58$$

Without  $R_p$

$$A_v \rightarrow -\infty$$

28.

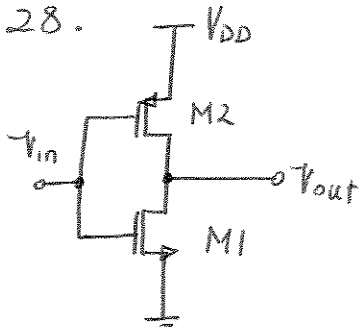

$$\left(\frac{W}{L}\right)_1 = 5/0.18$$

$$\left(\frac{W}{L}\right)_2 = 11/0.18$$

$$NM_L \text{ and } NM_H = ?$$

To calculate  $NM_L$ ,  $M_1$  and  $M_2$  are assumed to operate in the saturation and triode region respectively.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (v_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - v_{in} - |V_{TH2}|)(V_{DD} - v_{out}) - (V_{DD} - v_{out})^2 \right] \quad (1)$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (v_{in} - V_{TH1}) = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ -2(V_{DD} - v_{out}) - 2(V_{DD} - v_{in} - |V_{TH2}|) \right] \times \left[ \frac{\partial v_{out}}{\partial v_{in}} + 2(V_{DD} - v_{out}) \frac{\partial v_{out}}{\partial v_{in}} \right]$$

$$\frac{\partial v_{out}}{\partial v_{in}} = -1, \quad v_{in} = v_{IL}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (v_{IL} - V_{TH1}) = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2V_{OH} - v_{IL} - |V_{TH2}| - V_{DD} \right] \quad (2)$$

Obtaining  $V_{OH}$  from (2) and substituting in (1) yields:

$$v_{IL} = \frac{2\sqrt{\alpha} (V_{DD} - V_{TH1} - |V_{TH2}|)}{(\alpha - 1)\sqrt{\alpha + 3}} - \frac{V_{DD} - \alpha V_{TH1} - |V_{TH2}|}{\alpha - 1}$$

$$\alpha = \frac{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2} = \frac{100}{50} \times \frac{5}{11} = \frac{10}{11}$$

$$v_{IL} = \frac{2\sqrt{10/11} (1.8 - 0.4 - 0.5)}{(10/11 - 1)\sqrt{10/11 + 3}} - \frac{1.8 - (10/11) \times 0.4 - 0.5}{10/11 - 1}$$

$$v_{IL} = 0.7516 \text{ V}$$

To determine  $NM_H$ ,  $M_1$  and  $M_2$  are assumed to operate in the triode and saturation region respectively.

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1})V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}| - V_{in})^2 \quad (3)$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = -\mu_p C_{ox} \left(\frac{W}{L}\right)_2 \times (V_{DD} - V_{in} - |V_{TH2}|)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1 \text{ yields}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ V_{out} - V_{in} + V_{TH1} + V_{out} \right] = -\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)$$

$$100 \times 5 \times \left[ 2V_{out} - (V_{in} - 0.4) \right] = -50 \times 11 \times (1.8 - 0.5 - V_{in})$$

$$V_{out} = 1.05V_{in} - 0.915 \quad (4)$$

Substituting (4) in (3) yields an equation versus  $V_{in}$  as follows:

$$10 \times \left[ 2(V_{in} - 0.4)(1.05V_{in} - 0.915) - (1.05V_{in} - 0.915)^2 \right] = 11 \times (1.3 - V_{in})^2$$

$$1.025V_{in}^2 - 21.115V_{in} + 19.64225 = 0$$

$$V_{in} = V_{IH} = 0.9765 \text{ V}$$

$$NM_H = V_{DD} - V_{IH}$$

$$NM_H = 0.823 \text{ V}$$

$$29. \quad NML = 0.6 \text{ V}$$

$$(W/L)_1 / (W/L)_2 = ?$$

$$V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}$$

$$0.6 = \frac{2\sqrt{a}(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{a+3}} - \frac{1.8 - a \cdot 0.4 - 0.5}{a-1}$$

$$a = 3\sqrt{\frac{a}{a+3}} - \frac{1.3 - 0.4a}{0.6} + 1$$

$$a = \frac{a+3}{9} \times \left[ a-1 + \frac{1.3 - 0.4a}{0.6} \right]^2$$

$$\boxed{a=1}$$

$$(W/L)_1 / (W/L)_2 = \frac{\mu_p C_{ox}}{\mu_n C_{ox}} = \frac{1}{2}$$


$$\boxed{(W/L)_1 / (W/L)_2 = \frac{1}{2}}$$

$$30. V_{IL} = \frac{2\sqrt{a}(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$


$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$

$$a \rightarrow 0 \quad V_{IL} = V_{DD} - |V_{TH2}|$$
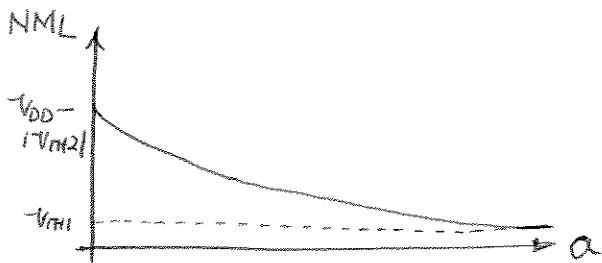
$$a \rightarrow \infty \quad V_{IL} = V_{TH1}$$




If  $a = \frac{\mu_n}{\mu_p} \times \frac{(W/L)_1}{(W/L)_2} \rightarrow 0$ , it implies that PMOS transistor is extremely stronger than NMOS. Therefore, as  $V_{in}$  increases from 0V, the output of inverter stays at  $V_{DD}$  until input reaches  $V_{DD} - |V_{TH2}|$ . At that point, PMOS is cut off and  $V_{out}$  sharply drops to 0V.

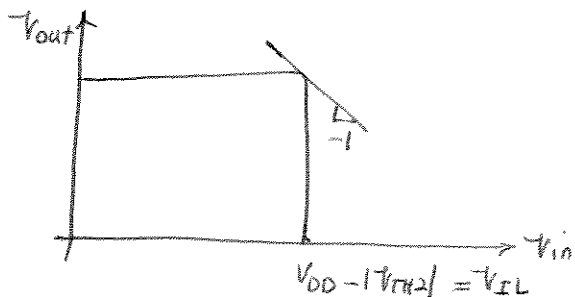

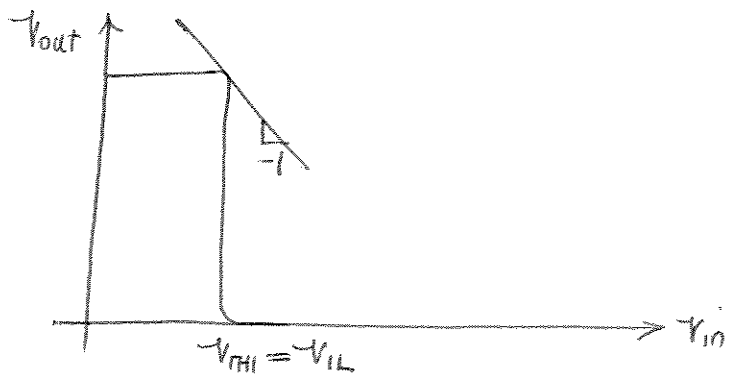When  $a \rightarrow \infty$ , NMOS is prevailing and once input voltage hits the threshold voltage of NMOS, output voltage falls sharply to 0V.






31.

$$NM_H = V_{DD} - \frac{2a(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{1+3a}} + \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$


$$a \rightarrow 0 \quad NM_H = |V_{TH2}|, \quad V_{IH} = V_{DD} - |V_{TH2}|$$
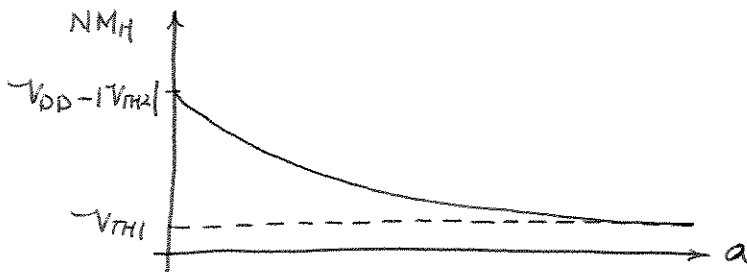
$$a \rightarrow \infty \quad NM_H = V_{DD} - V_{TH1}, \quad V_{IH} = V_{TH1}$$




If  $a = \frac{\mu_n}{\mu_p} \times \frac{(W/L)_1}{(W/L)_2} \rightarrow 0$ , it implies that PMOS transistor is much

stronger than NMOS. Therefore, as  $V_{in}$  increases from 0V, the output of inverter remains at  $V_{DD}$  until input reaches  $V_{DD} - |V_{TH2}|$ . At that point, PMOS is cutoff and  $V_{out}$  sharply drops to 0V.

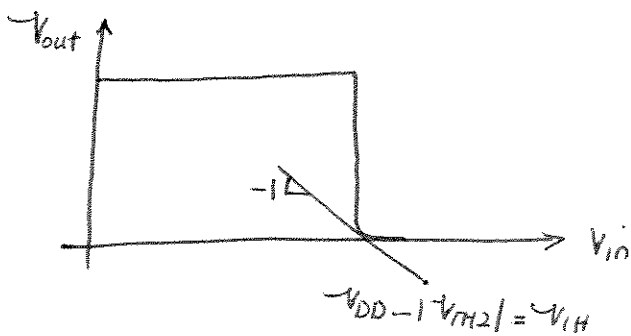


When "a" approaches infinity, NMOS is prevailing and once input voltage hits the threshold voltage of NMOS, output voltage falls sharply to

0V.

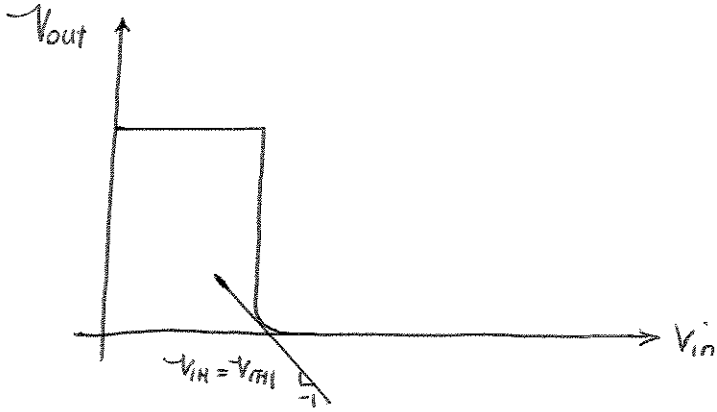

Note that the separation between  $V_{IH}$  and  $V_{IL}$  depends on the slope of VTC in the transition region. If "a" approaches either "0" or infinity, VTC exhibits infinite gain in its transition region. Therefore  $V_{IL}$  and  $V_{IH}$  coincide.

32.

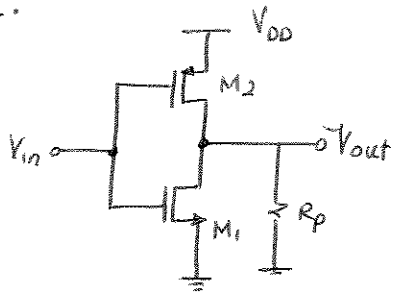

$$R_p = 2k$$

$$NML, NM_H = ?$$

$$\left(\frac{W}{L}\right)_1 = 3/0.18$$

$$\left(\frac{W}{L}\right)_2 = 5/0.18$$

To calculate  $NML$ ,  $M_1$  and  $M_2$  are assumed to be in the saturation and triode region respectively.

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} \quad (V_{in} = V_{IL})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] =$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 + \frac{V_{out}}{R_p} \quad (1)$$

$$\frac{\partial V_{out}}{\partial V_{in}} = -1, \quad V_{in} = V_{IL}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ -2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right] =$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1}) + \frac{1}{R_p} \frac{\partial V_{out}}{\partial V_{in}}$$

$$\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1}) - \frac{1}{R_p} = \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] \quad (2)$$

$$V_{OH} = 1.01 V_{IL} + 0.73$$

Replacing  $V_{out}$  in (1) with its equivalent versus  $V_{IL}$  obtained from (2) yields:

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{IL} - |V_{TH2}|)(V_{DD} - 1.1V_{IL} - 0.73) - (V_{DD} - 1.1V_{IL} - 0.73)^2 \right] =$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1})^2 + \frac{1.1V_{IL} + 0.73}{R_p}$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} \left[ 2(1.8 - V_{IL} - 0.5)(1.8 - 1.1V_{IL} - 0.73) - (1.8 - 1.1V_{IL} - 0.73)^2 \right] =$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} (V_{IL} - 0.4)^2 + \frac{1.1V_{IL} + 0.73}{2000}$$

$$-52.5 \times 10^{-3} V_{IL} - 0.6195 V_{IL} + 0.229875 = 0$$

$$\boxed{V_{IL} = NML = 0.36 \text{ V}} < V_{TH1} \quad \text{NOT ACCEPTABLE!}$$

This is less than threshold voltage of  $M_1$ ; therefore, this answer is not acceptable. It means that  $M_1$  is off and should be left out in this calculation.

$$I_{D1} = 0, \quad I_{D2} = \frac{V_{out}}{R_p}$$

$$\mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD} \right] = -\frac{1}{R_p}$$

$$50 \times 10^{-6} \times \frac{5}{0.18} \times \left[ 2V_{OH} - V_{IL} - 0.5 - 1.8 \right] = -\frac{1}{2000}$$

$$\boxed{V_{OH} = V_{out} = 0.5V_{IL} + 0.97} \quad (3)$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} \times \left[ 2(1.8 - V_{IL} - 0.5)(1.8 - 0.5V_{IL} - 0.97) - (1.8 - 0.5V_{IL} - 0.97)^2 \right] =$$

$$\frac{0.5V_{IL} + 0.97}{2000}$$

$$0.1875 V_{IL}^2 - 0.6225 V_{IL} + 0.192675 = 0$$

$$\boxed{V_{IL} = NML = 0.345 \text{ V}}$$

To determine  $NM_H$ ,  $M_1$  and  $M_2$  are assumed to operate in the triode and saturation region respectively.

$$I_{D2} = I_{D1} + \frac{V_{out}}{R_p} \quad (V_{in} = V_{IH})$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] + \frac{V_{out}}{R_p} \quad (4)$$

$$-\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|) = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] + \frac{\partial V_{out}}{\partial V_{in}} \frac{1}{R_p}$$

$$-\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|) = \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ V_{out} - V_{in} + V_{TH1} + V_{out} \right] - \frac{1}{R_p}$$

$$-50 \times 10^{-6} \times \frac{5}{0.18} \times (1.8 - V_{in} - 0.5) = 100 \times 10^{-6} \times \frac{3}{0.18} \times (2V_{out} - V_{in} + 0.4) - \frac{1}{2000}$$

$$\boxed{V_{out} = \frac{0.1V_{in} + 0.59}{1.2}} \quad (5)$$


Combining equs (4) and (5) yields:

$$\frac{1}{2} \times 50 \times 10^{-6} \times \frac{5}{0.18} (1.8 - V_{in} - 0.5)^2 = \frac{1}{2} \times 100 \times 10^{-6} \times \frac{3}{0.18} \left[ 2(V_{in} - 0.4) \frac{0.1V_{in} + 0.59}{1.2} - \frac{(0.1V_{in} + 0.59)^2}{1.2^2} \right] + \frac{0.1V_{in} + 0.59}{1.2 \times 2000}$$

$$-0.291 V_{in}^2 + 1.3182 V_{in} - 0.75531 = 0$$

$$V_{in} = V_{IH} = 0.673 \text{ V} \rightarrow \boxed{NM_H = V_{DD} - V_{IH} = 1.127 \text{ V}}$$

33.

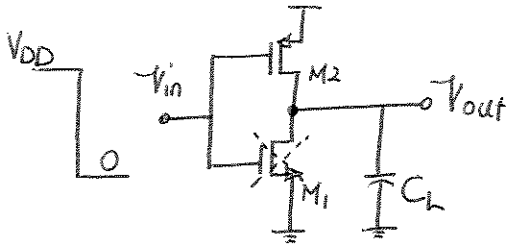

$$V_{out}(t=0) = 0$$

$$(W/L)_2 = 6/0.18$$

$$C_L = 50 \text{ fF}$$

$0 < V_{out} < |V_{TH2}|$ ;  $M_2$  in the saturation

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 = \frac{1}{2} \times 50 \times 10^{-6} \times \frac{6}{0.18} (1.8 - 0.5)^2 = 1.4 \times 10^{-3} \text{ A}$$

$$V_{out}(t) = \frac{I_{D2}}{C_L} \times t$$

$$|V_{TH2}| = \frac{I_{D2}}{C_L} \cdot T_1 \rightarrow T_1 = \frac{C_L \times |V_{TH2}|}{I_{D2}} = 50 \times 10^{-15} \times \frac{1.4 \times 10^{-3}}{1.4 \times 10^{-3}} \times 0.5$$

$$T_1 = 17.75 \text{ pS}$$

$|V_{TH2}| < V_{out} < V_{DD}/2$ ,  $M_2$  in triode

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(-V_{out} + V_{DD}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(-V_{out} + V_{DD}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

$$\frac{1}{(V_{DD} - V_{out}) \left[ 2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out}) \right]} = \frac{1}{2(V_{DD} - |V_{TH2}|) \left[ \frac{1}{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})} + \frac{1}{V_{DD} - V_{out}} \right]}$$

$$\frac{1}{2(V_{DD} - |V_{TH2}|)} \left[ \frac{dV_{out}}{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})} + \frac{dV_{out}}{V_{DD} - V_{out}} \right] = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 dt$$

$$\ln \frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = \mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t + C$$

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = K \cdot \exp \left[ \mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t \right]$$

Time origin is assumed to be at  $t = T_1 = 17.75 \mu s$

$$V_{out}(t=0) = |V_{TH2}| \rightarrow K = 1$$

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = e^{\mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|) t}$$

$$\begin{aligned} \textcircled{a} V_{out} = V_{DD}/2 \quad T_2 &= \frac{\ln(3 - 4|V_{TH2}|/V_{DD})}{\mu_p \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_2 (V_{DD} - |V_{TH2}|)} \\ &= \frac{\ln(3 - 4 \times 0.5/1.8)}{50 \times 10^{-6} \times \frac{1}{50 \times 10^{-75}} \times \frac{6}{0.18} \times (1.8 - 0.5)} \end{aligned}$$

$$T_2 = 1.467 \times 10^{-11}$$

$$T_0 \rightarrow V_{DD/2} = T_1 + T_2 = 17.75 + 14.67$$

$$T_0 \rightarrow V_{DD/2} = 32.43 \mu s$$



34.  $|V_{TH2}| < V_{out} < 0.95V_{DD}$   $M_2$  in Triode

$$\frac{2(V_{DD} - |V_{TH2}|) - (V_{DD} - V_{out})}{V_{DD} - V_{out}} = e^{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|) t}$$

$$\begin{aligned} \textcircled{a} V_{out} = 0.95V_{DD}, \quad T_2 &= \frac{\ln(39 - 40|V_{TH2}|/V_{DD})}{\mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \\ &= \frac{\ln(39 - 40 \times 0.5/1.8)}{50 \times 10^{-6} \times \frac{1}{50 \times 10^{-15}} \times \frac{6}{0.18} \times (1.8 - 0.5)} \end{aligned}$$

$$T_2 = 7.68 \times 10^{-11}$$


$T_1 = 17.75 \mu\text{s}$  from previous problem

$$T_{0 \rightarrow 0.95V_{DD}} = T_1 + T_2 = 17.75 + 76.8$$

$$T_{0 \rightarrow 0.95V_{DD}} = 94.55 \mu\text{s}$$

$$(T_{0 \rightarrow 0.95V_{DD}}) / (T_{0 \rightarrow V_{DD}/2}) \approx 3$$

35.

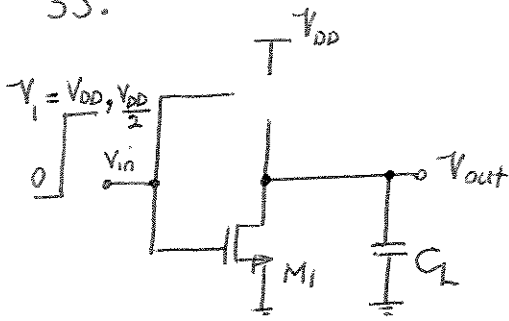

$$V_{out}(t=0) = V_{DD}$$

$$C_L = 30 \text{ fF}$$

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$


$$T_{V_{DD} \rightarrow V_{DD/2}} = ?$$

$$\left(\frac{W}{L}\right)_2 = \text{Not necessary}$$

$$V_i = V_{DD} \text{ or } V_{DD/2}$$

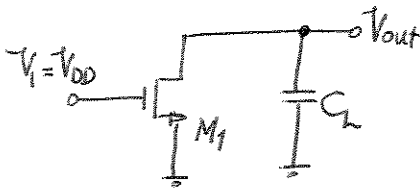(a)  $V_i = V_{DD}$

$$V_{DD} - V_{TH1} \leq V_{out} \leq V_{DD} \quad M_1 \text{ Saturation}$$



$$\frac{V_{DD}}{2} \leq V_{out} \leq V_{DD} - V_{TH1} \quad M_1 \text{ Triode}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)^2 = 5.44 \times 10^{-4} \text{ A}$$

$$dV_{out} = -\frac{I_{D1}}{C_L} \cdot dt$$

$$V_{out}(t) - V_{DD} = -\frac{I_{D1}}{C_L} t \rightarrow V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} t$$

$$T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} = \frac{V_{TH1} \times C_L}{I_{D1}} = \frac{0.4 \times 30 \times 10^{-15}}{5.44 \times 10^{-4}} = 2.2 \times 10^{-11} \text{ s}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1})V_{out} - V_{out}^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - V_{TH1})V_{out} - V_{out}^2} = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 dt$$

$$\frac{1}{[2(V_{DD} - V_{TH1}) - V_{out}]V_{out}} = \frac{1}{2(V_{DD} - V_{TH1})} \left[ \frac{1}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{1}{V_{out}} \right]$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \left[ \frac{dV_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{dV_{out}}{V_{out}} \right] = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 dt$$

$$-\ln \left[ 2(V_{DD} - V_{TH1}) - V_{out} \right] + \ln V_{out} = -\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) t + C$$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = K \cdot \exp \left[ -\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) t \right]$$

$$V_{out}(t=0) = V_{DD} - V_{TH1} \quad \text{Note that time origin is assumed to be } 2.2 \times 10^{-11}$$

$$K = 1 \rightarrow$$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) t}$$

$$V_{out} = \frac{V_{DD}}{2} \rightarrow \frac{V_{DD}/2}{2(V_{DD} - V_{TH1}) - V_{DD}/2} = e^{-\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1}) T_{(V_{DD} - V_{TH1}) \rightarrow V_{DD}/2}}$$


$$T_{(V_{DD} - V_{TH1}) \rightarrow V_{DD}/2} = \frac{\ln \left( 3 - \frac{2V_{TH1}}{V_{DD}} \right)}{\mu_n \frac{C_{ox}}{C_L} \left( \frac{W}{L} \right)_1 (V_{DD} - V_{TH1})}$$

$$= \frac{\ln(3 - 4 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} \times (1.8 - 0.4)} = 2.88 \times 10^{-11} \text{ s}$$

$$T_{V_{DD} \rightarrow V_{DD}/2} = T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} + T_{(V_{DD} - V_{TH1}) \rightarrow V_{DD}/2}$$

$$T_{V_{DD} \rightarrow V_{DD}/2} = 5 \times 10^{-11} = 50.86 \text{ ps}$$

(b)  $V_i = V_{DD}/2$

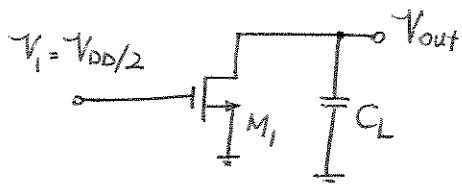

$V_{DD}/2 - V_{TH1} < V_{out} < V_{DD}$   $M_1$  in Saturation

$V_{DD}/2 < V_{out} < V_{DD}$   $M_1$  in Saturation

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD}/2 - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (0.9 - 0.4)^2$$


$$= 6.944 \times 10^{-5}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$V_{DD}/2 = V_{DD} - \frac{I_{D1}}{C_L} \times T_{(V_{DD} \rightarrow V_{DD}/2)} \Rightarrow T_{(V_{DD} \rightarrow V_{DD}/2)} = \frac{(V_{DD}/2) \times C_L}{I_{D1}}$$

$$T_{(V_{DD} \rightarrow V_{DD}/2)} = 3.888 \times 10^{-10}$$

36.

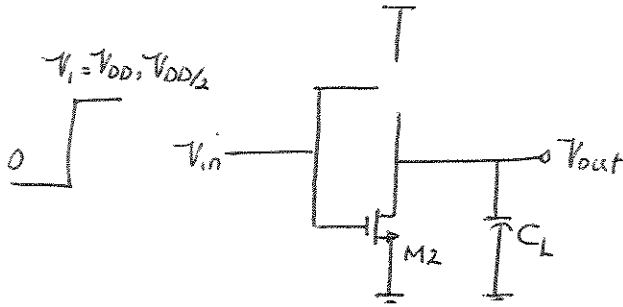

$$V_{out}(0) = V_{DD}$$

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$

$$C_L = 30 \text{ fF}$$

$$T_{V_{DD}} \rightarrow 0.05 V_{DD} = ?$$

(a)  $V_i = V_{DD}$       $V_{DD} - V_{TH1} < V_{out} < V_{DD}$   $M_1$  in Saturation

$0.05 V_{DD} < V_{out} < V_{DD} - V_{TH1}$   $M_1$  in Triode

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)^2 = 5.44 \times 10^{-4} \text{ A}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$T_{V_{DD} \rightarrow V_{DD} - V_{TH1}} = \frac{V_{TH1} \times C_L}{I_{D1}} = \frac{0.4 \times 30 \times 10^{-15}}{5.44 \times 10^{-4}} = 2.2 \times 10^{-11} \text{ S}$$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \left[ \frac{dV_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} + \frac{dV_{out}}{V_{out}} \right] = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 dt$$

$V_{out}(t=0) = V_{DD} - V_{TH1}$  Note that time origin is assumed to be  $2.2 \times 10^{-11} \text{ S}$

$$\frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1}) t}$$

$$V_{out} = 0.05V_{DD}$$

$$\frac{0.05V_{DD}}{2(V_{DD}-V_{TH1})-0.05V_{DD}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD}-V_{TH1}) T_{(V_{DD}-V_{TH1}) \rightarrow 0.05V_{DD}}}$$

$$T_{(V_{DD}-V_{TH1}) \rightarrow 0.05V_{DD}} = \frac{\ln(39 - 40V_{TH1}/V_{DD})}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD}-V_{TH1})}$$

$$= \frac{\ln(39 - 40 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} (1.8 - 0.4)}$$

$$T_{(V_{DD}-V_{TH1}) \rightarrow 0.05V_{DD}} = 131.33 \text{ pS}$$

$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = T_{(V_{DD} \rightarrow V_{DD}-V_{TH1})} - T_{(V_{DD}-V_{TH1}) \rightarrow 0.05V_{DD}}$$

$$= 2.2 \times 10^{-11} + 1.3133 \times 10^{-10}$$

$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = 153.33 \text{ pS}$$

(b)  $V_i = V_{DD}/2$   $V_{DD}/2 - V_{TH1} < V_{out} < V_{DD}$   $M_1$  in Saturation

$0.05V_{DD} < V_{out} < V_{DD}/2 - V_{TH1}$   $M_1$  in Triode

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD}/2 - V_{TH1})^2 = -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{1}{0.18} (0.9 - 0.4)^2$$

$$= 6.944 \times 10^{-5} \text{ A}$$

$$V_{out}(t) = V_{DD} - \frac{I_{D1}}{C_L} \times t$$

$$V_{DD/2} - V_{TH1} = V_{DD} - \frac{I_{D1}}{C_L} T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})}$$

$$T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} = \frac{(V_{DD/2} + V_{TH1}) \times C_L}{I_{D1}}$$

$$T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} = 5.616 \times 10^{-10}$$

for  $0.05V_{DD} < V_{out} < V_{DD/2} - V_{TH1}$

$$C_L \frac{dV_{out}}{dt} = -I_{D1} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD/2} - V_{TH1})V_{out} - V_{out}^2 \right]$$

$$\frac{V_{out}}{2(V_{DD/2} - V_{TH1}) - V_{out}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1}) t}$$

$$V_{out} = 0.05V_{DD} \rightarrow \frac{0.05V_{DD}}{2(V_{DD/2} - V_{TH1}) - 0.05V_{DD}} = e^{-\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1}) \times T}$$

$$\begin{aligned} T_{(V_{DD/2} - V_{TH1} \rightarrow 0.05V_{DD})} &= \frac{\ln(19 - 40V_{TH1}/V_{DD})}{\mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 (V_{DD/2} - V_{TH1})} \\ &= \frac{\ln(19 - 40 \times 0.4 / 1.8)}{100 \times 10^{-6} \times \frac{1}{30 \times 10^{-15}} \times \frac{1}{0.18} (0.9 - 0.4)} \\ &= 2.5 \times 10^{-10} \end{aligned}$$

$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = T_{(V_{DD} \rightarrow V_{DD/2} - V_{TH1})} + T_{(V_{DD/2} - V_{TH1} \rightarrow 0.05V_{DD})}$$


$$T_{(V_{DD} \rightarrow 0.05V_{DD})} = 5.616 \times 10^{-10} + 2.5 \times 10^{-10} = 811.5 \text{ pS}$$

By decreasing  $V_{in}$  from  $V_{DD}$  to  $V_{DD}/2$ , the time it takes the output to reach  $0.05V_{DD}$  will be 5.3 time larger!

$$\frac{T(V_{DD} \rightarrow 0.05V_{DD})(V_{in} = V_{DD})}{T(V_{DD} \rightarrow 0.05V_{DD})(V_{in} = V_{DD}/2)} = \frac{811.5 \text{ p}}{153.33 \text{ p}} \approx 5.3$$



37.

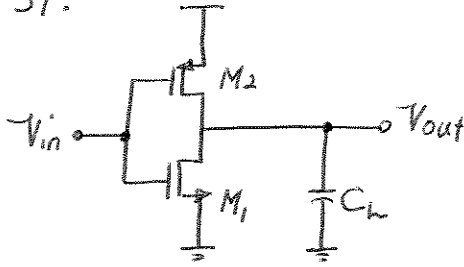

$$\left(\frac{W}{L}\right)_1 = 1/0.18$$

$$\left(\frac{W}{L}\right)_2 = 3/0.18$$

$$C_L = 80 \text{ fF}$$

$$T_{PHL}, T_{PLH} = ?$$

To calculate  $T_{PLH}$ 

$$0 < V_{out} < |V_{TH2}| \quad M_2 \text{ in Saturation}$$

$$|V_{TH2}| < V_{out} < V_{DD}/2 \quad M_2 \text{ in Triode}$$

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$V_{out}(t) = \frac{|I_{D2}|}{C_L} t$$

$$= \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2 t$$

$$V_{out}(T_{PLH1}) = |V_{TH2}|$$

$$T_{PLH1} = \frac{|V_{TH2}| \times C_L}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2}$$

for  $M_2$  operating in Triode region

$$C_L \frac{dV_{out}}{dt} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right]$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

Defining  $V_{DD} - V_{out} = u$  and noting that  $\int \frac{du}{au - u^2} = \frac{1}{a} \ln \frac{u}{a-u}$ ,

$$\frac{-1}{2(V_{DD} - |V_{TH2}|)} \ln \frac{V_{DD} - V_{out}}{V_{DD} - 2|V_{TH2}| + V_{out}} \left| \begin{array}{l} V_{out} = V_{DD}/2 \\ V_{out} = |V_{TH2}| \end{array} \right. = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 T_{PLH2}$$

$$T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$

$$T_{PLH} = T_{PLH1} + T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$T_{PLH} = \frac{80 \times 10^{-15}}{50 \times 10^{-6} \times \frac{3}{0.18} (1.8 - 0.5)} \left[ \frac{2 \times 0.5}{1.8 - 0.5} + \ln \left( 3 - 4 \frac{0.5}{1.8} \right) \right]$$

$$T_{PLH} = 1.0377 \times 10^{-10}$$

To calculate  $T_{PHL}$   $V_{DD} - V_{TH1} < V_{out} < V_{DD}$   $M_1$  in Saturation

$V_{DD}/2 < V_{out} < V_{DD} - V_{TH1}$   $M_1$  in Triode

$$T_{PHL1} = \frac{-\Delta V_{out} \times C_L}{I_{D1}} = \frac{V_{TH1} \times C_L}{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2}$$

after this point in time.

$$C_L \frac{dV_{out}}{dt} = -\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right]$$

$$V_{out}(t=0) = V_{DD} - V_{TH1}$$

$$\frac{1}{2(V_{DD} - V_{TH1})} \ln \frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} \left| \begin{array}{l} V_{out} = V_{DD}/2 \\ V_{out} = V_{DD} - V_{TH1} \end{array} \right. = -\frac{1}{2} \mu_n \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_1 T_{HL2}$$

$$T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \times \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right)$$

$$T_{PHL} = T_{PHL1} + T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \times \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$T_{PHL} = \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} (1.8 - 0.4)} \times \left[ \frac{2 \times 0.4}{1.8 - 0.4} + \ln \left(3 - 4 \frac{0.4}{1.8}\right) \right]$$

$$T_{PHL} = 1.3563 \times 10^{-10}$$

$$38. \quad V_{DD} = 1.8 + 1.8 \times 0.1 = 1.98$$

$$T_{PLH} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{50 \times 10^{-6} \times \frac{3}{0.18} \times (1.98 - 0.5)} \left[ \frac{2 \times 0.5}{1.98 - 0.5} + \ln \left( 3 - 4 \times \frac{0.5}{1.98} \right) \right]$$

$$T_{PLH} = 8.846 \times 10^{-11}$$

$$\text{Decrease in } T_{PLH} = \left| \frac{8.846 \times 10^{-11} - 1.0377 \times 10^{-10}}{1.0377 \times 10^{-10}} \right| \times 100$$

$$= 14.75\%$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (1.98 - 0.4)} \left[ \frac{2 \times 0.4}{1.98 - 0.4} + \ln \left( 3 - 4 \frac{0.4}{1.98} \right) \right]$$

$$T_{PHL} = 1.1767 \times 10^{-10}$$

$$\text{Decrease in } T_{PHL} = \left| \frac{1.1767 \times 10^{-10} - 1.3563 \times 10^{-10}}{1.3563 \times 10^{-10}} \right| \times 100$$

$$= 13.24\%$$

$$39. V_{DD} = 0.9 \text{ V}$$

$$C_L \frac{dV_{out}}{dt} = I_{D2} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$T_{PLH} = \frac{\Delta V_{out} \times C_L}{I_{D2}} = \frac{(V_{DD}/2) \times C_L}{\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2}$$

$$= \frac{0.45 \times 80 \times 10^{-15}}{\frac{1}{2} \times 50 \times 10^{-6} \times \frac{3}{0.18} \times (0.9 - 0.5)^2}$$

$$T_{PLH} = 5.4 \times 10^{-10} = 540 \text{ pS}$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$= \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (0.9 - 0.4)} \times \left[ \frac{2 \times 0.4}{0.9 - 0.4} + \ln \left( 3 - 4 \frac{0.4}{0.9} \right) \right]$$

$$T_{PHL} = 5.186 \times 10^{-10} = 518.6 \text{ pS}$$

$$\text{Increase in } T_{PLH} = \left| \frac{5.4 \times 10^{-10} - 1.0377 \times 10^{-10}}{1.0377 \times 10^{-10}} \right| \times 100$$

$$= 420.38\%$$

$$\text{Increase in } T_{PHL} = \left| \frac{5.186 \times 10^{-10} - 1.3563 \times 10^{-10}}{1.3563 \times 10^{-10}} \right| \times 100$$

$$= 282.36\%$$

$$40. T_{PLH} = T_{PHL} = 80 \text{ ps}$$

$$C_L = 50 \text{ fF}$$

$$\left(\frac{W}{L}\right)_1, \left(\frac{W}{L}\right)_2 = ?$$

$$T_{PLH} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln\left(3 - 4 \frac{|V_{TH2}|}{V_{DD}}\right) \right]$$

$$80 \times 10^{-12} = \frac{50 \times 10^{-15}}{50 \times 10^{-6} \times (1.8 - 0.5) \times \left(\frac{W}{L}\right)_2} \times \left[ \frac{2 \times 0.5}{1.8 - 0.5} + \ln\left(3 - 4 \times \frac{0.5}{1.8}\right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_2 = \frac{2.4}{0.18}}$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \times \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$80 \times 10^{-12} = \frac{50 \times 10^{-15}}{100 \times 10^{-6} \times (1.8 - 0.4) \times \left(\frac{W}{L}\right)_1} \times \left[ \frac{2 \times 0.4}{1.8 - 0.4} + \ln\left(3 - 4 \times \frac{0.4}{1.8}\right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_1 = \frac{1}{0.18}}$$

41.

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$V_{TH1} = 0.4$$

$$\frac{2V_{TH1}}{V_{DD} - V_{TH1}} = \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \rightarrow V_{DD} = V_{TH1} \left[ 1 + \frac{2}{\ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right)} \right]$$

$$V_{TH1} = 0.4 \rightarrow \boxed{V_{DD} = 1.57}$$

$$\frac{2V_{TH1}}{V_{DD} - V_{TH1}} = 0.1 \times \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \rightarrow V_{DD} = V_{TH1} \left[ 1 + \frac{20}{\ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right)} \right]$$

$$V_{TH1} = 0.4 \rightarrow \boxed{V_{DD} = 8.16}$$

$$42. \left(\frac{W}{L}\right)_1 = 1/0.18$$

$$T_{PHL} = 100 \text{ pS}$$

$$C_L = 80 \text{ fF}$$

$$V_{DD} = ?$$

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4\frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$100 \times 10^{-12} = \frac{80 \times 10^{-15}}{100 \times 10^{-6} \times \frac{1}{0.18} \times (V_{DD} - 0.4)} \times \left[ \frac{2 \times 0.4}{V_{DD} - 0.4} + \ln\left(3 - 4\frac{0.4}{V_{DD}}\right) \right]$$

$$V_{DD} = 0.4 + 1.44 \left[ \frac{0.8}{V_{DD} - 0.4} + \ln\left(3 - \frac{1.6}{V_{DD}}\right) \right]$$

$$\boxed{V_{DD} = 2.22}$$



$$43. \quad T_{PHL} = 120 \text{ ps} \quad \left(\frac{W}{L}\right)_1 = ?$$

$$C_L = 90 \text{ fF} \quad V_{TH1} = ?$$

$$V_{DD} = 1.8$$

$$T_{PHL} = 160 \text{ ps} \quad T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$$V_{DD} = 1.5 \text{ V}$$

$$C_L = 90 \text{ fF}$$

$$120 \times 10^{-12} = \frac{90 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.8 - V_{TH1})} \times \left[ \frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{1.8} \right) \right] \quad (1)$$

$$160 \times 10^{-12} = \frac{90 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.5 - V_{TH1})} \times \left[ \frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{1.5} \right) \right] \quad (2)$$

Dividing Equations (1) and (2) yields:

$$0.75 = \frac{1.5 - V_{TH1}}{1.8 - V_{TH1}} \times \frac{\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{1.8} \right)}{\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{1.5} \right)}$$

$$V_{TH1} = 1.8 - \left( \frac{1.5 - V_{TH1}}{0.75} \right) \times \frac{\frac{2V_{TH1}}{1.8 - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{1.8} \right)}{\frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{1.5} \right)}$$

This equation does not lead to a real value for  $V_{TH1}$  so we use another derivation

$$V_{TH1} = 0.45 \times \left\{ 3 - e^{\left[ 0.75 \frac{1.8 - V_{TH1}}{1.5 - V_{TH1}} \times \left[ \frac{2V_{TH1}}{1.5 - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{1.5} \right) \right] - \frac{2V_{TH1}}{1.8 - V_{TH1}} \right]} \right\}$$

$$V_{TH1} = 0.39$$

$$\left(\frac{W}{L}\right)_1 = \frac{1.26}{0.18}$$

44.

$$T_{PHL} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right) \right]$$

$\ln \left( 3 - 4 \frac{V_{TH1}}{V_{DD}} \right)$  is meaningless if  $V_{DD} < 4V_{TH1}/3$ .

Let's consider the case where  $V_{DD} = \frac{4}{3}V_{TH1}$ ; then,  $T_{PHL}$  is the time it takes

for the output to drop from  $V_{DD} = \frac{4}{3}V_{TH1}$  to  $\frac{V_{DD}}{2} = \frac{2}{3}V_{TH1}$ . However,


$$\left( V_{in}^0 = V_{DD} = \frac{4}{3}V_{TH1} \right) - \left( V_{out} = \frac{2}{3}V_{TH1} \right) = \frac{2}{3}V_{TH1} < V_{TH1}. \text{ In other words, } M_1$$

never enters the triode region in the region where  $T_{PHL}$  is calculated. The

logarithmic term is derived from equation in which  $M_1$  was assumed to be in

Triode region. Therefore the logarithmic term is meaningless for  $V_{DD} < \frac{4}{3}V_{TH1}$ .

45.

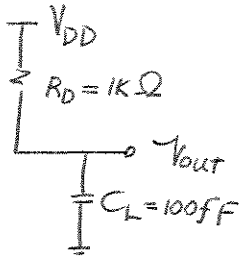

$$V_{R_D} = (V_{DD} - V_{out})$$

$$I_{R_D} = C_L \frac{dV_{out}}{dt}$$

$$P_{R_D}(t) = V_{R_D} \cdot I_{R_D} = C_L (V_{DD} - V_{out}) \frac{dV_{out}}{dt}$$

$$\begin{aligned} E_{R_D} &= \int_{t=0}^{\infty} P_{R_D}(t) dt = \int_{V_{out}=0}^{V_{DD}} (V_{DD} - V_{out}) dV_{out} = \frac{1}{2} C_L V_{DD}^2 \\ &= \frac{1}{2} \times 100 \times 10^{-15} \times (1.8)^2 \end{aligned}$$

$$E_{R_D} = 0.162 \mu J$$

46.  $10^6$  Gates

$$f = 2 \text{ GHz}$$

20% of gates switch in every clock cycle

$C_L = 20 \text{ fF}$  for each gate

$$P_{av} = ?$$

$$P_{av, \text{gate}} = f_{in} C_L V_{DD}^2$$

$$P_{av, \text{total}} = 0.2 \times 10^6 \times f_{in} C_L V_{DD}^2$$

$$= 0.2 \times 10^6 \times 2 \times 10^9 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av, \text{total}} = 25.92 \text{ W}$$

$$47. f = 2 \text{ GHz}$$

$5 \times 10^6$  Transistors with  $W = 1 \mu\text{m}$ ,  $L = 0.18 \mu\text{m}$ ,  $C_{ox} = 10 \text{ fF}/\mu\text{m}^2$

$$C_{\text{gate}} = WLC_{ox}$$

$$C_{\text{Load}} = 5 \times 10^6 C_{\text{gate}}$$

$$= 5 \times 10^6 WLC_{ox}$$

$$= 5 \times 10^6 \times 1 \mu\text{m} \times 0.18 \mu\text{m} \times 10 \text{ fF}/\mu\text{m}^2$$

$$C_{\text{Load}} = 9 \text{ pF}$$

$$P_{\text{av}} = f_{in} C_L V_{DD}^2$$

$$= 2 \times 10^9 \times 9 \times 10^{-9} \times (1.8)^2$$

$$P_{\text{av}} = 58.32 \text{ W}$$

48.

$$V_{DD} = V_{DD} + 0.1 V_{DD} = 1.98$$

$$\left(\frac{W}{L}\right)_1 = 2/0.18$$

$$\left(\frac{W}{L}\right)_2 = 4/0.18$$

$$I_{Peak} \Big|_{V_{DD}=1.8} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(\frac{V_{DD}}{2} - V_{TH1}\right)^2 \left(1 + \lambda_1 \frac{V_{DD}}{2}\right)$$

$$= \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.9 - 0.4)^2$$

$$I_{Peak} \Big|_{V_{DD}=1.8} = 1.388 \times 10^{-4}$$


$$I_{Peak} \Big|_{V_{DD}=1.98} = \frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{2}{0.18}\right) (0.99 - 0.4)^2$$

$$I_{Peak} \Big|_{V_{DD}=1.98} = 1.9338 \times 10^{-4}$$

$$\text{Change in Crowbar Current} = \frac{1.9338 \times 10^{-4} - 1.388 \times 10^{-4}}{1.388 \times 10^{-4}}$$

$$\text{Change in Crowbar Current} = 39.24\%$$

49.

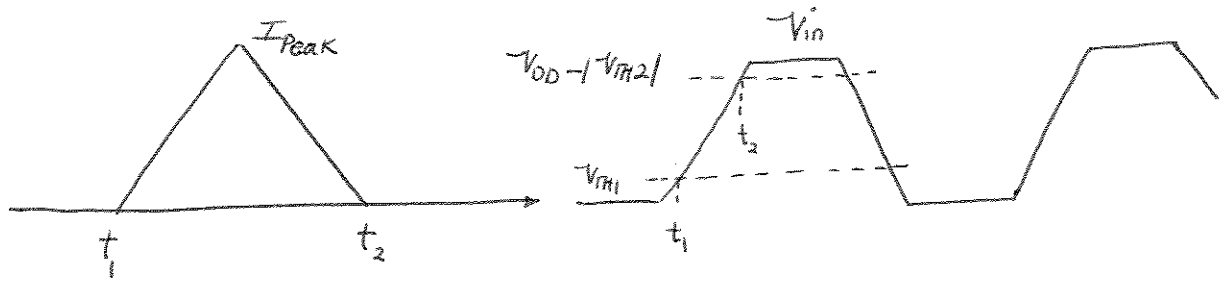

Total Energy drawn from  $V_{DD}$  during the interval  $[t_1, t_2]$  is:

$$E = V_{DD} \times I_{Peak} \times \frac{t_2 - t_1}{2}$$

In a periode the total energy is:

$$E_{tot} = 2 \times V_{DD} \times I_{Peak} \times \frac{t_2 - t_1}{2}$$

$$P_{av} = V_{DD} I_{Peak} (t_2 - t_1) f_1$$

$$\text{Slope of input voltage} = \frac{0.9V_{DD} - 0.1V_{DD}}{t_r} = \frac{0.8V_{DD}}{t_r}$$

$$(t_2 - t_1) = \frac{(V_{DD} - V_{TH1} - |V_{TH2}|) \times t_r}{0.8V_{DD}}$$


$$P_{av} = V_{DD} \times \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(\frac{V_{DD}}{2} - V_{TH1}\right)^2 \times \frac{(V_{DD} - V_{TH1} - |V_{TH2}|)}{0.8V_{DD}} t_r \times f_1$$

$$P_{av} = \frac{1}{1.6} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left(\frac{V_{DD}}{2} - V_{TH1}\right)^2 (V_{DD} - V_{TH1} - |V_{TH2}|) f_1 \cdot t_r$$

$$P_{av} = 1.4 \times 10^{-5} \left(\frac{W}{L}\right)_1 \times t_r \times f_1$$




50.

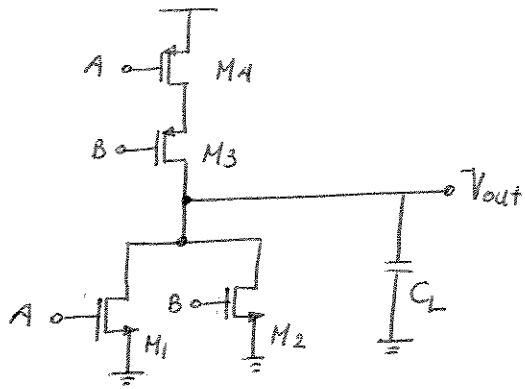

$$C_L = 20 \text{ fF}$$

$$f_i = 500 \text{ MHz}$$

$$P_{av} = ?$$


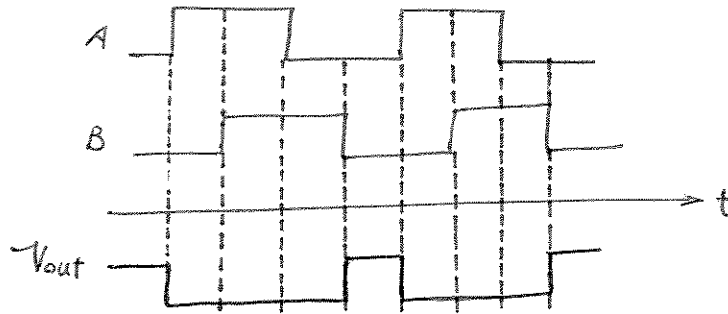


$$P_{av} = f_{in} C_L V_{DD}^2$$

$$= 500 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av} = 3.24 \times 10^{-5} \text{ W}$$

51.

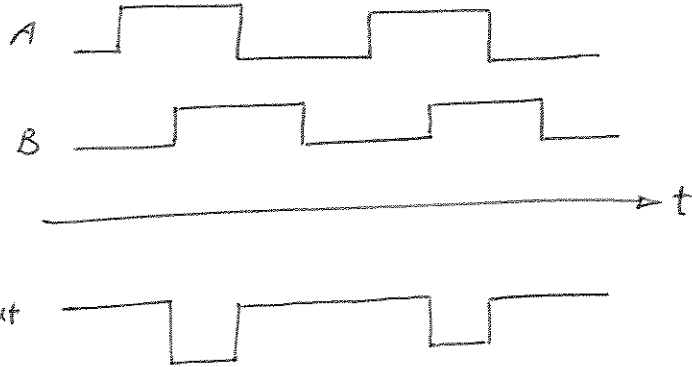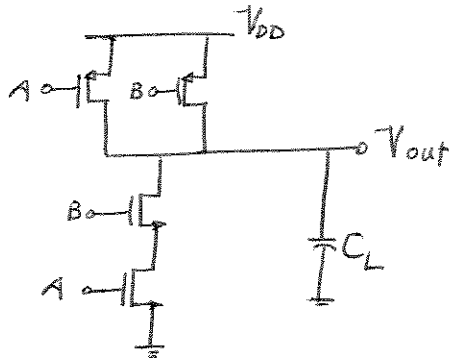


$$P_{av} = f_{in} C_L V_{DD}^2$$


$$= 500 \times 10^6 \times 20 \times 10^{-15} \times (1.8)^2$$

$$P_{av} = 3.24 \times 10^{-5} \text{ W}$$


52.

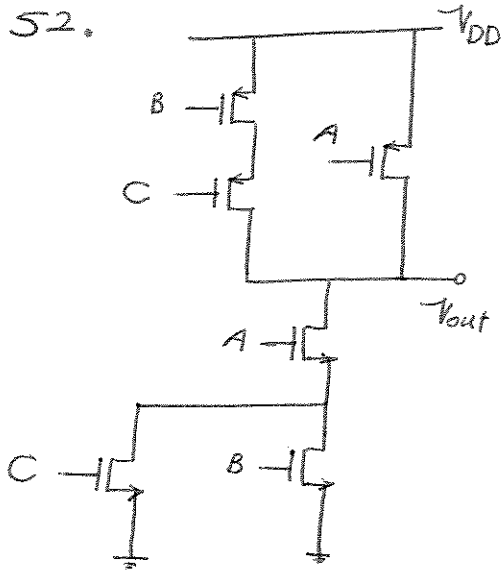


$$V_{out} = \overline{(B+C)A}$$

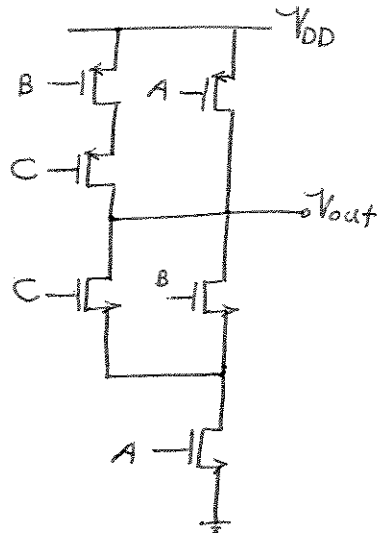


$$V_{out} = \overline{(B+C).A}$$

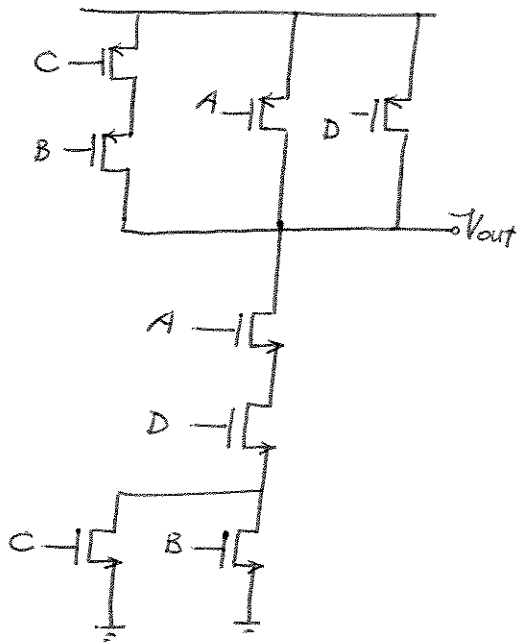

$$V_{out} = \overline{(B+C)D.A}$$

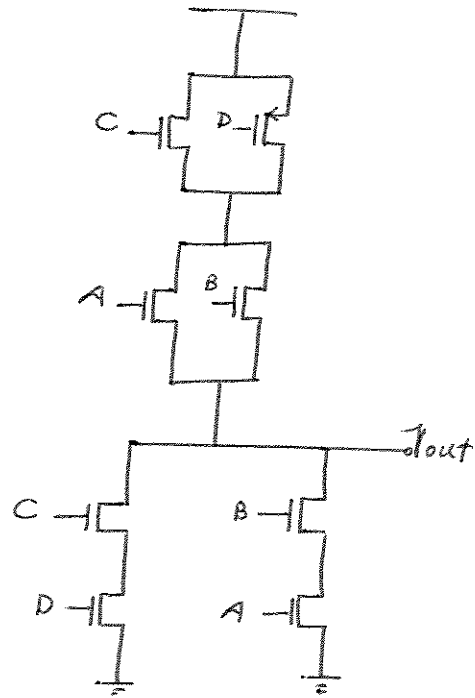


$$V_{out} = \overline{A.B + C.D}$$

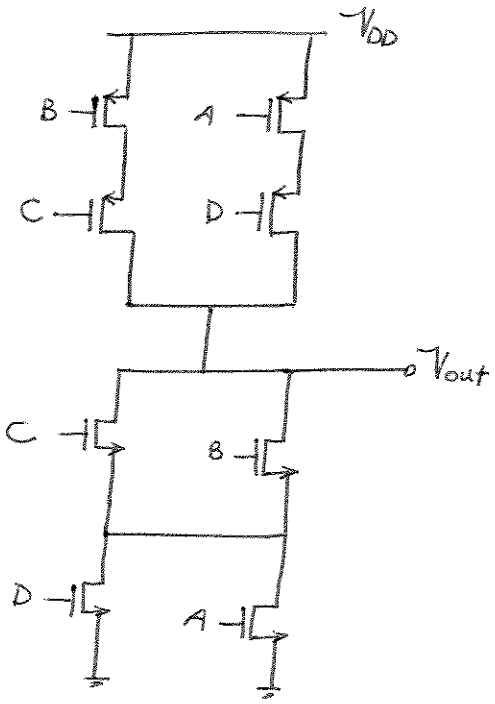

$$V_{out} = \overline{(A+D) \cdot (B+C)}$$

53.

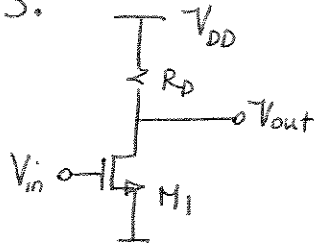

$$P_{\text{static}} = 0.5 \text{ mW}$$

$$V_{OL} = 100 \text{ mV}$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + V_{OL} \times \frac{V_{DD} - V_{OL}}{R_D} = 0.5 \times 10^{-3}$$

$$\frac{(1.8 - 0.1)^2}{R_D} + 0.1 \times \frac{1.8 - 0.1}{R_D} = 0.5 \times 10^{-3}$$

$$\frac{1}{R_D} \times 3.06 = 0.5 \times 10^{-3}$$


$$\boxed{R_D = 6120 \Omega}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1})V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 \times \left[ 2(1.8 - 0.4)0.1 - 0.1^2 \right] = \frac{1.8 - 0.1}{6120}$$

$$\boxed{\left(\frac{W}{L}\right)_1 = \frac{3.7}{0.18}}$$

54.

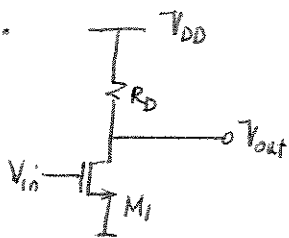

$$P_{\text{static}} = 0.25 \text{ mW}$$

$$NM_L = 600 \text{ mV}$$

$$\text{Small signal gain} = -g_m R_D$$

$$g_m = \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{TH})$$

$$\mu_n C_{ox} \frac{W}{L} (V_{IL} - V_{TH}) R_D = 1$$

$$V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} + V_{TH}$$

$$NM_L = V_{IL} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} + V_{TH}$$

$$\frac{1}{\mu_n C_{ox} \left(\frac{W}{L}\right) R_D} = (NM_L - V_{TH}) \rightarrow \left(\frac{W}{L}\right) R_D = \frac{1}{\mu_n C_{ox} (NM_L - V_{TH})}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[ 2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \mu_n C_{ox} \frac{1}{\mu_n C_{ox} (NM_L - V_{TH})} \times \left[ 2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 \right] = (V_{DD} - V_{OL})$$

$$2(V_{DD} - V_{TH}) V_{OL} - V_{OL}^2 = 2(NM_L - V_{TH})(V_{DD} - V_{OL})$$

$$-V_{OL}^2 - 2(V_{DD} - V_{TH}) V_{OL} - 2(NM_L - V_{TH}) V_{OL} + 2(NM_L - V_{TH}) V_{DD} = 0$$

$$-V_{OL}^2 - 2(V_{DD} + NM_L - 2V_{TH}) V_{OL} + 2(NM_L - V_{TH}) V_{DD} = 0$$

$$V_{OL}^2 - 3.2 V_{OL} + 0.72 = 0$$

$$\boxed{V_{OL} = 0.2435}$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + V_{OL} \times \frac{V_{DD} - V_{OL}}{R_D} = 0.25 \times 10^{-3}$$

$$\frac{(1.8 - 0.24)^2 + 0.24 \times (1.8 - 0.24)}{R_D} = 0.25 \times 10^{-3}$$


$$\boxed{R_D = 11206.55 \Omega}$$

$$\left(\frac{W}{L}\right) = \frac{1}{\mu_n C_{ox} (N_{ML} - V_{TH}) R_D}$$

$$\boxed{\left(\frac{W}{L}\right) = \frac{0.8}{0.18}}$$

$$\left(\frac{W}{L}\right) = \frac{1}{100 \times 10^{-6} (0.6 - 0.4) 11206.55}$$

55.

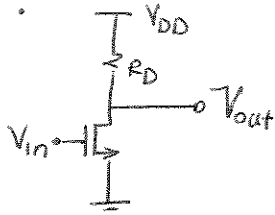

$$V_{OL} = 100\text{mV}$$

$$P_{av} = 0.25\text{mW}$$

$$\frac{(V_{DD} - V_{OL})^2}{R_D} + \frac{V_{OL}(V_{DD} - V_{OL})}{R_D} = P_{av}$$

$$\frac{(1.8 - 0.1)^2 + 0.1 \times (1.8 - 0.1)}{0.25 \times 10^{-3}} = R_D$$

$$R_D = 12240$$


$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) \left[ 2(V_{DD} - V_{TH1})V_{OL} - V_{OL}^2 \right] = \frac{V_{DD} - V_{OL}}{R_D}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L}\right) \times \left[ 2(1.8 - 0.4) \times 0.1 - 0.1^2 \right] = \frac{1.8 - 0.1}{12240}$$

$$\left(\frac{W}{L}\right) = \frac{1.85}{0.18}$$



56.

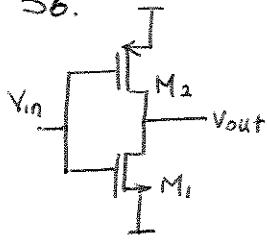

$$V_{in} = V_{out} = 0.8V, \quad I_{D1} = I_{D2} = 0.5mA$$

$$\lambda_n = 0.1V^{-1}$$

$$\lambda_p = 0.2V^{-1}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 (1 + \lambda_n V_{out}) = I_{D1}$$

$$\frac{1}{2} \times 100 \times 10^{-6} \times \left(\frac{W}{L}\right)_1 (0.8 - 0.4)^2 (1 + 0.1 \times 0.8) = 0.5 \times 10^{-3}$$


$$\boxed{\left(\frac{W}{L}\right)_1 = \frac{10.4}{0.18}}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2 [1 + \lambda_p (V_{DD} - V_{out})] = I_{D2}$$

$$\frac{1}{2} \times 50 \times 10^{-6} \times \left(\frac{W}{L}\right)_2 (1.8 - 0.8 - 0.5)^2 [1 + 0.2 \times (1.8 - 0.8)] = 0.5 \times 10^{-3}$$

$$\boxed{\left(\frac{W}{L}\right)_2 = \frac{12}{0.18}}$$

57.

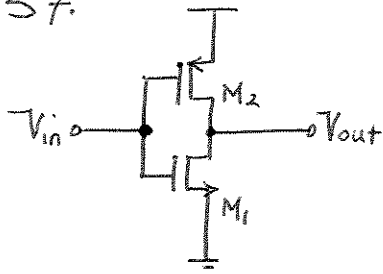

$$NM_L = NM_H = 0.7V$$

$NM_L$ :  $M_1$  in Saturation and  $M_2$  in triode

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - V_{in} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] \quad (1)$$

Differentiating both sides with respect to  $V_{in}$

$$2\mu_n \left(\frac{W}{L}\right)_1 (V_{in} - V_{TH1}) = \mu_p \left(\frac{W}{L}\right)_2 \left[ -2(V_{DD} - V_{out}) - 2(V_{DD} - V_{in} - |V_{TH2}|) \frac{\partial V_{out}}{\partial V_{in}} + 2(V_{DD} - V_{out}) \frac{\partial V_{out}}{\partial V_{in}} \right]$$

$$(a) \quad V_{in} = V_{IL} \quad , \quad \frac{\partial V_{out}}{\partial V_{in}} = -1$$

$$\mu_n \left(\frac{W}{L}\right)_1 (V_{IL} - V_{TH1}) = \mu_p \left(\frac{W}{L}\right)_2 (2V_{OH} - V_{IL} - |V_{TH2}| - V_{DD}) \quad (2)$$

obtaining  $V_{OH}$  from (2), substituting in (1), we arrive at

$$V_{IL} = \frac{2\sqrt{a} (V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{a+3}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$a = \frac{\mu_n \left(\frac{W}{L}\right)_1}{\mu_p \left(\frac{W}{L}\right)_2}$$

$NM_H$ ,  $M_1$  in triode and  $M_2$  in Saturation

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{in} - V_{TH1}) V_{out} - V_{out}^2 \right] = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - V_{in} - |V_{TH2}|)^2$$

Differentiating both sides with respect to  $V_{in}$ :

$$\mu_n \left(\frac{W}{L}\right)_1 \left[ 2V_{out} + 2(V_{in} - V_{TH1}) \frac{\partial V_{out}}{\partial V_{in}} - 2V_{out} \frac{\partial V_{out}}{\partial V_{in}} \right] = 2\mu_p \left(\frac{W}{L}\right)_2 \times (V_{in} - V_{DD} - |V_{TH2}|)$$

Assuming  $\frac{\partial V_{out}}{\partial V_{in}} = -1$ ,  $V_{in} = V_{IH}$ , and  $V_{out} = V_{OL}$  obtaining

$$V_{IH} = \frac{2a(V_{DD} - V_{TH1} - |V_{TH2}|)}{(a-1)\sqrt{1+3a}} - \frac{V_{DD} - aV_{TH1} - |V_{TH2}|}{a-1}$$

$$V_{IL} = NM_L = 0.7$$

$$V_{IH} = V_{DD} - NM_H = 1.8 - 0.7 = 1.1$$

$$0.7 = \frac{2\sqrt{a}(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{a+3}} - \frac{1.8 - 0.4a - 0.5}{a-1}$$

$$0.7(a-1) = \frac{1.8\sqrt{a}}{\sqrt{a+3}} - \frac{1.3 - 0.4a}{1}$$

$$0.7a - 0.7 + 1.3 - 0.4a = \sqrt{\frac{a}{a+3}} \times 1.8$$

$$\frac{0.6 + 0.3a}{1.8} = \sqrt{\frac{a}{a+3}} \rightarrow a^3 + 7a^2 - 20a + 12 = 0$$

$$a = \begin{cases} -9.3 \\ 1.3 \\ 1 \end{cases} \rightarrow \boxed{a = 1.3}$$

$$1.1 = \frac{2a(1.8 - 0.4 - 0.5)}{(a-1)\sqrt{1+3a}} - \frac{1.8 - 0.4a - 0.5}{a-1}$$

$$1.1(a-1) = \frac{1.8a}{\sqrt{1+3a}} - 1.3 + 0.4a$$

$$1.1a - 1.1 + 1.3 - 0.4a = \frac{1.8a}{\sqrt{1+3a}}$$

$$0.2 + 0.7a = \frac{1.8a}{\sqrt{1+3a}}$$


$$147a^3 - 191a^2 + 40a + 4 = 0 \rightarrow \begin{cases} a_1 = 1 \\ a_2 = 0.37 \\ a_3 = -0.073 \end{cases} \rightarrow \boxed{a = 0.37}$$

No it is not possible to design a CMOS inverter with  $NM_L = NM_H = 0.7$ .

The reason is that each value of  $a = \frac{\mu_n C_{ox} (W/L)_1}{\mu_p C_{ox} (W/L)_2}$  specifies a unique set of noise margins ( $NM_L, NM_H$ ).

Remember, the relative strength of NMOS and PMOS determines the noise margins interdependently.

58.

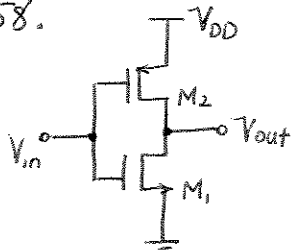

$$T_{PLH} = T_{PHL} = 100 \text{ ps}$$

$$C_L = 50 \text{ fF}$$

 $T_{PLH}$ 

$$|I_{D2}| = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2$$

$$V_{out}(t) = \frac{|I_{D2}|}{C_L} t$$

$$= \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2 t$$

$$T_{PLH1} = \frac{2|V_{TH2}|/C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)^2}$$

$$|I_{D2}| = C_L \frac{dV_{out}}{dt}$$

$$\frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L}\right)_2 \left[ 2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right] = C_L \frac{dV_{out}}{dt}$$

$$\frac{dV_{out}}{2(V_{DD} - |V_{TH2}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 dt$$

$$\frac{-1}{2(V_{DD} - |V_{TH2}|)} \ln \frac{V_{DD} - V_{out}}{V_{DD} - 2|V_{TH2}| + V_{out}} \Bigg|_{V_{out} = |V_{TH2}|}^{V_{out} = V_{DD}/2} = \frac{1}{2} \mu_p \frac{C_{ox}}{C_L} \left(\frac{W}{L}\right)_2 T_{PLH2}$$

$$T_{PLH2} = \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \ln \left( 3 - 4 \frac{|V_{TH2}|}{V_{DD}} \right)$$

$$T_{PLH} = T_{PLH1} + T_{PLH2}$$

$$= \frac{C_L}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2 (V_{DD} - |V_{TH2}|)} \left[ \frac{2|V_{TH2}|}{V_{DD} - |V_{TH2}|} + \ln\left(3 - 4 \frac{|V_{TH2}|}{V_{DD}}\right) \right]$$

$$100 \times 10^{-12} = \frac{50 \times 10^{-15}}{50 \times 10^{-6} \left(\frac{W}{L}\right)_2 (1.8 - 0.5)} \left[ \frac{2 \times 0.5}{1.8 - 0.5} + \ln\left(3 - 4 \frac{0.5}{1.8}\right) \right]$$

$$\boxed{\left(\frac{W}{L}\right)_2 = \frac{1.9}{0.18}}$$

$T_{PHL}$

$$T_{PHL1} = \frac{2V_{TH1} C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})^2}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_1 \left[ 2(V_{DD} - V_{TH1}) V_{out} - V_{out}^2 \right] = -C_L \frac{dV_{out}}{dt}$$

$$\frac{-1}{2(V_{DD} - V_{TH1})} \ln \frac{V_{out}}{2(V_{DD} - V_{TH1}) - V_{out}} \bigg|_{V_{out} = V_{DD}/2}^{V_{out} = V_{DD} - V_{TH1}} = \frac{1}{2} \mu_n C_{ox} / C_L \left(\frac{W}{L}\right)_1 T_{PHL2}$$

$$T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right)$$

$$T_{PHL} = T_{PHL1} + T_{PHL2} = \frac{C_L}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (V_{DD} - V_{TH1})} \left[ \frac{2V_{TH1}}{V_{DD} - V_{TH1}} + \ln\left(3 - 4 \frac{V_{TH1}}{V_{DD}}\right) \right]$$

$$100 \times 10^{-12} = \frac{50 \times 10^{-15}}{100 \times 10^{-6} \left(\frac{W}{L}\right)_1 (1.8 - 0.4)} \times \left[ \frac{2 \times 0.4}{1.8 - 0.4} + \ln\left(3 - 4 \times \frac{0.4}{1.8}\right) \right] \cdot \boxed{\left(\frac{W}{L}\right)_1 = \frac{0.85}{0.18}}$$

Razavi 1e – Fundamentals of Microelectronics

## CHAPTER 16 SOLUTIONS MANUAL

\*\*\*For **Chapter 16** solutions, please refer to **Chapter 7** as the questions are identical in each chapter.