

ISRAEL INSTITUTE OF TECHNOLOGY - TECHNION
ANDREW AND ERNA VITERBI FACULTY OF ELECTRICAL ENGINEERING

Introduction to VLSI Computer Exercise 1

Circuit simulations - Custom Design

Last update: November 7, 2018

Submission in pairs only until 11/12/2018

If you have questions please contact
Nicolás Wainstein - nicolasw@campus.technion.ac.il



Contents

| | | |
|----------|---|-----------|
| 1 | Introduction | 3 |
| 1.1 | Submission | 3 |
| 1.2 | An Overview of VLSI CAD Tools | 3 |
| 1.3 | Design Flow | 3 |
| 1.4 | Getting Started with Cadence Virtuoso | 4 |
| 2 | Schematic of an XOR2 | 5 |
| 2.1 | Create symbol | 7 |
| 2.2 | Create Test Circuit | 8 |
| 3 | Schematic Simulation | 8 |
| 3.1 | Plot the output | 10 |
| 3.1.1 | Using the calculator | 11 |
| 3.1.2 | Using the Output Editor | 11 |
| 3.2 | Parametric sweep | 12 |
| 3.3 | Corner simulations | 12 |
| 3.3.1 | TTSS Corner | 13 |
| 3.3.2 | TTFE Corner | 14 |
| 3.4 | Higher load (FO4) | 14 |
| 3.5 | Power Estimation | 14 |
| 3.5.1 | Static dissipation | 15 |
| 3.5.2 | Dynamic | 15 |
| 3.5.3 | Short Circuit | 15 |
| 3.6 | Sizing | 16 |
| 3.7 | Buffer insertion | 16 |
| 4 | Layout | 17 |
| 4.1 | Placement | 19 |
| 4.2 | DRC | 19 |
| 4.3 | Routing | 20 |
| 4.4 | Layout vs Schematic (LVS) | 21 |
| 5 | Hierarchical Design | 21 |
| 5.1 | Routing | 22 |
| 5.2 | RC Extraction | 22 |
| 5.3 | Extracted Layout Simulation | 23 |

1 Introduction

This is the first of two design labs. The labs are intended to teach you the practicalities of chip design using industry-standard CAD tools from Cadence.

This lab teaches you the basics of how to use the computer-aided design (CAD) tool to design, simulate, and verify schematics and layout of logic gates. It also serves as a stand-alone tutorial to quickly get up to speed with the Cadence tools. The first step is to draw a schematic indicating the connection of transistors to build cells such as NAND gates, NOR gates, and NOT gates.

These cells are simulated by applying digital inputs and checking that the outputs match expectation, while varying some parameters and working conditions. You will also estimate time delays and power dissipation. A symbol for the cell is also created. Then, you will draw a layout indicating how the transistors and wires are physically arranged on the chip. The layout is checked to ensure it satisfies the design rules and that the transistors match the schematic. Finally, you will perform a hierarchical design, both in the schematic level and in the layout level. The design will be simulated and characterized.

1.1 Submission

You are intended to submit electronically (Moodle) a report that includes all the figures/simulations/questions that are asked under the title **Submission** (it may be convenient that you take a look at this subsection before you start to work). There's no need to extend in your answers, be **precise** and **concise**. Try to include waveforms (graphs) that clearly explain the issue, for example zoom-in to the relevant section.

Please, in the first page write down your names, IDs, your lab account and the amount of hours you invested in this work

1.2 An Overview of VLSI CAD Tools

VLSI designers have a wide variety of CAD tools to choose from, each with their own strengths and weaknesses. The leading Electronic Design Automation (EDA) companies include Cadence and Synopsys. Exist some open-source CAD tools such as Electric.

There are two general strategies for chip design. Custom design involves specifying how every transistor is connected and physically arranged on the chip. Synthesized design involves describing the function of a digital chip in a hardware description language such as Verilog or VHDL, then using a computer-aided design tool to automatically generate a set of gates that perform this function, place the gates on the chip, and route the wires to connect the gates. The majority of commercial designs are synthesized today because synthesis takes less engineering time. However, custom design gives more insight into how chips are built and into what to do when things go wrong. Custom design also offers higher performance, lower power, and smaller chip size. The first lab emphasize the fundamentals of custom design, while the next two use logic synthesis and automatic placement to save time.

1.3 Design Flow

Cells are commonly described at three levels of abstraction. The register-transfer level (RTL) description is a Verilog or VHDL file specifying the behaviour of the cell in terms of registers and combinational logic. It often serves as the specification of what the chip should do. The schematic illustrates how the cell is composed from transistors or other cells. The layout shows how the transistors or cells are physically arranged.

Logic verification involves proving that the cells perform the correct function. One way to do this is to simulate the cell and apply a set of 1's and 0's called test vectors to the inputs, then check that the outputs match expectation. Typically, logic verification is done first on the RTL to check that the specification is correct. A test-bench written in Verilog or VHDL automates the process of applying and checking all of the vectors. The same test vectors are then applied to the schematic to check that the schematic matches the RTL. Later, we will use a layout-versus schematic (LVS) tool to check that the layout matches the schematic (and, by inference, the RTL).

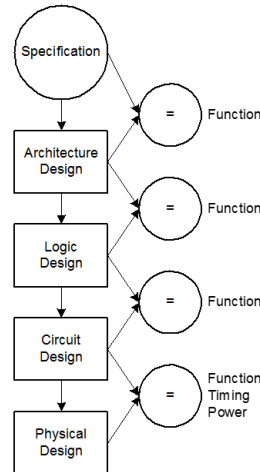


Figure 1: VLSI Design Flow

1.4 Getting Started with Cadence Virtuoso

To initiate Cadence Virtuoso follow these steps:

1. Login to a lab machine (instructions posted separately)
2. In the console type:
 - (a) `cd cadence`
 - (b) `source KIT.cshrc`
 - (c) `cdsprj lab`
 - (d) `virtuoso &` (The ampersand isn't necessary but it makes the terminal window available for further use. Otherwise it is fully dedicated to the process and cannot be used or closed.)
3. The main window will open at the bottom of the screen. Select *'Tools → Library Manager'*. The library manager window will open. ¹
4. Create (don't use the existing one) a library by invoking *File → New → Library...* in the Library Manager. Name the library *lab1_XXXX*, where XXXX is your group lab account. Click *'OK'*.
5. **In the window that opens, select *'Attach to an existing techfile'*, click *'OK'* and then select *ts018_prim* as the Technology Library. Click *'OK'* and you should see your new library appear in the library manager.**
6. **SUGGESTION: save your work periodically.**

¹Don't try to move libraries around or rename them directly in Linux; there is some unexpected behavior and you are likely to break them.

2 Schematic of an XOR2

In this part you will design and simulate an XOR2 gate in the schematic level. The first sections explain how to design your schematic and Section 3 will teach you how to simulate your circuit. We will work with TowerJazz 0.18 μm process with $\lambda = 90 \text{ nm}^2$. **Note: To ease the design, consider \bar{a} and \bar{b} , a and b complements, respectively, as different inputs. Remember to take this into account in your simulations. This means your gate will have 4 inputs.**

Each gate or larger component is called a cell. Cells have multiple views, called ‘*cellviews*’. A *cellview* is an aspect of the cell, such as its schematic, its layout, its simulation model, etc. Common *cellviews* include:

- Schematic: A circuit schematic consisting of ‘*symbol*’ views of other cells.
- Layout: The physical layout of a particular schematic cellview, with objects in the layout typically linked to their schematic counterparts. Layout consists of various layers such as: *polysilicon*, *M1*, *M2*, *Nwell*, *N⁺*, *P⁺*, etc.
- Symbol: A visual representation of the cell, which is used for inserting the cell into other schematics.
- Various Spectre/HSpice simulation models, usually only for discrete components like passives or transistors (we won’t use this tool).
- Simulation states (see Section 3).
- Power and timing data.

For example, your library will, eventually, contain several cells (at least one XOR2 schematics and one for its layout).

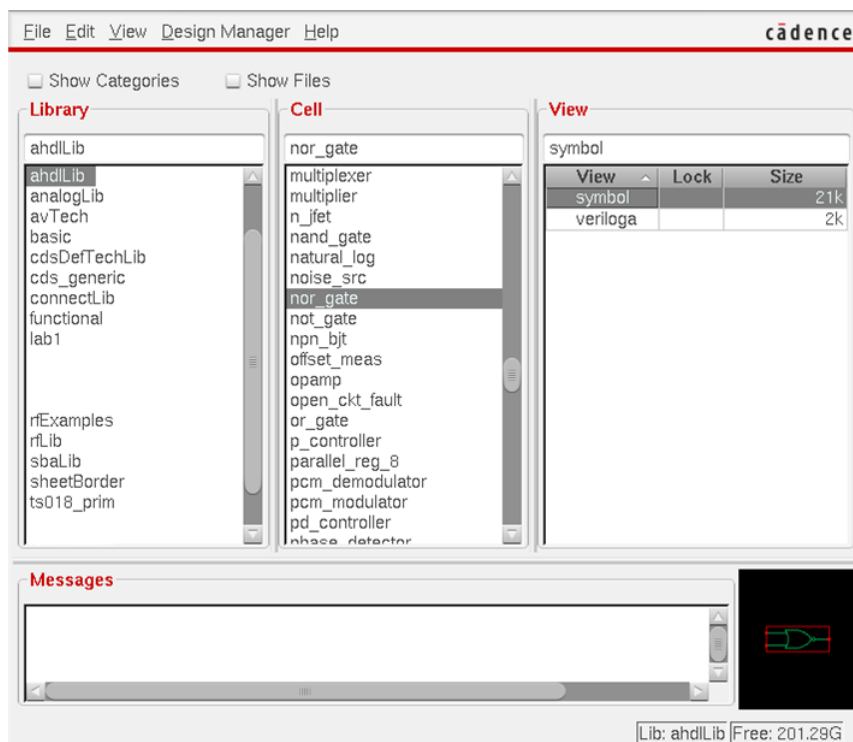


Figure 2: Library Manager

²Remember λ is half of the channel’s width

In the library manager, select your library. Go to ‘*File → New → Cell View*’. In the window that opens give the cellview the name *xor2*. Make sure that the View Name is set to ‘*schematic*’ and that the Library Name is set to your library. Click ‘*OK*’ and a new schematic window will open.

To add a component, *e.g.*, an NMOS transistor, with the schematic window selected, go to ‘*Create → Instance*’ on the menu bar (or click ‘*i*’ on the keyboard) and an ‘*Add Instance*’ window will open. Click ‘*Browse*’ and a window similar to the library manager will open. Navigate to the Tower library, ‘*ts018_prim*’, find the ‘*nmos_18*’ cell, click it and click the ‘*symbol*’ view. Then click inside the schematic window to place it. For now, disregard the values that got filled in the ‘*Add Instance*’ window. Press ‘*ESC*’ on the keyboard to stop placement.

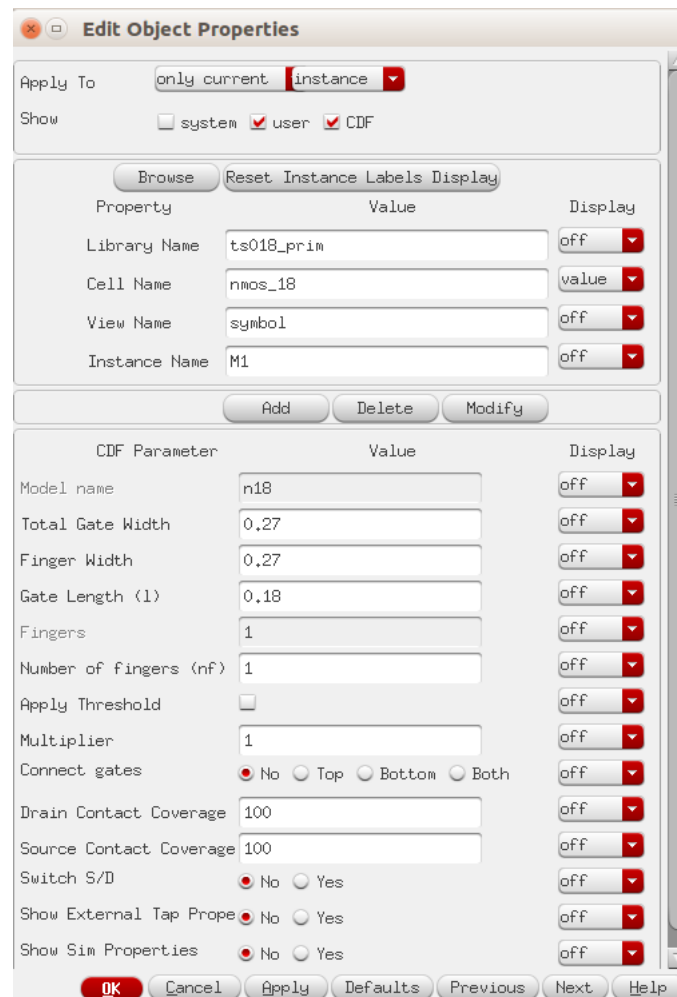


Figure 3: Edit properties

Click on the NMOS and type ‘*q*’. This will open the properties window (Fig. 3). Note ‘*Finger Width*’, ‘*Gate Length*’ and ‘*Fingers*’. Width and length should be obvious. ‘*Fingers*’ refers to the practice of using multiple parallel transistors instead of a single wide one. Let’s make W_N and W_P (NMOS and PMOS width respectively) parametric. For NMOS, in *Finger Width* write `pPar("WN")` and for PMOS `pPar("WP")`. This will allow us to change parameters in higher hierarchies of the design. Leave the length at its default (and smallest) $0.18\mu\text{m}$ value. Click ‘*OK*’. Remember - everything in Linux is case sensitive, so note how you wrote everything. **Note that sizes are in microns, rather than meters or λ units.**

Place all the transistors needed for an static CMOS XOR2 gate (components can be copied by pressing ‘*c*’, clicking, dragging and clicking; for moving components, simply drag them) and connect them using wires by going to ‘*Create → Wire*’ or clicking ‘*w*’ in the keyboard. Note that components

can also be connected by placing their red box terminals together. Then, place V_{DD} and ground, they are both in the *analogLib* library (*vdd* and *gnd* respectively). You can use 'Ctrl+r' to rotate the instances. **Take care in connecting the bulk of each transistor to either gnd or vdd.**

Next, create input and output pins (name them, e.g., a and b for inputs and y for output), go to 'Create → Pin' or click 'p', and then connect them with wires to the gates or output node. Make sure the direction is properly set for inputs and outputs. Save and check your schematic, choose 'File → Check and Save' or press 'Shift+x'.³

You can zoom in and out with the scroll-wheel and fit the whole schematic by pressing 'f' in the keyboard. Also you can zoom in to a desired place by selecting the area with the right click pressed.

Submit:

1. Print screen of the XOR2 schematic and test circuit (FO1).

2.1 Create symbol

Each schematic can have a corresponding symbol to represent the cell in a higher-level schematic. You will need to create a symbol for your XOR2 gate. When creating your symbol, it is a good idea to keep everything aligned to the grid, this will make connecting symbols simpler and cleaner when you need it for another cell. While looking at your XOR2 schematic, choose *Create → Cellview → From Cellview...* In the window that opens, make sure Cell name is *xor2*, 'From View Name' is *schematic*, and 'To View Name' is *symbol*, and click *OK*. Cadence will create a generic symbol based on your pin names. Check that everything is as expected in the Symbol Generation Options window which opens up, and click *OK*. The Symbol L Editing window that opens up may look like Fig. 4.

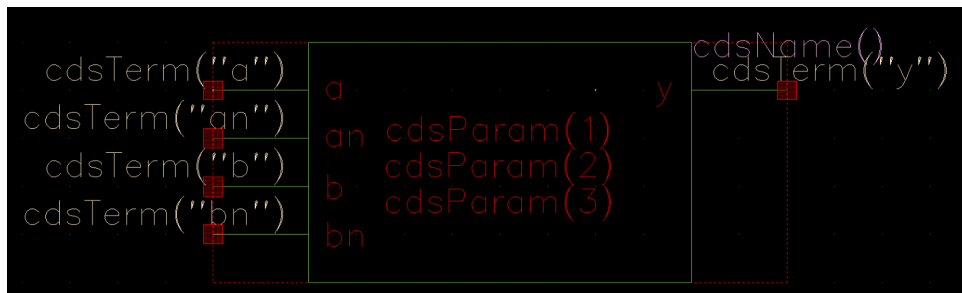


Figure 4: Symbol

A schematic is easier to read when familiar symbols are used instead of generic boxes. Modify the symbol to look like a standard XOR2. Pay attention to the dimensions of the symbol; the overall design will look more readable if symbols are of consistent sizes. Experiment with the arc drawing tool. Finally, choose *Create → Selection Box...* and choose 'Automatic'. This creates a red box around the symbol that will define where to click to select the symbol when it appears in another schematic. Our art work is shown in Fig. 5.

³If you see an error message in the parameter display of the transistors, do not worry, it is just because the tool does not know how to calculate W (yet).

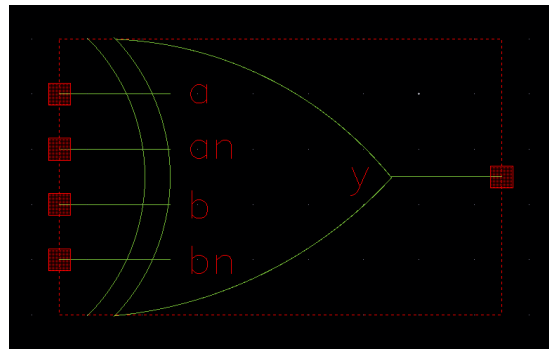


Figure 5: XOR2 Symbol example

2.2 Create Test Circuit

Now let's create a test circuit to simulate the XOR2. Create a new schematic and name it `test_xor2`. Place the XOR2 symbol you created in the last step (it should be on your library `lab1_xxxx`; use '*i*' or *Create* → *instance*), and change its properties (click on it and type '*q*'). They should appear as '*Wn*' and '*Wp*'). Select '*Wn*' to be minimum (the technology spec says the minimum width is $0.22 \mu\text{m}$) and '*Wp*' to be '*r**0.22'. With this last definition we will define the width of the PMOS as a multiple (*r*) of the minimum width of $0.22 \mu\text{m}$. At the output of this XOR2 gate connect one of the inputs of a second same gate as a load. This results in Fan Out of 1 (**FO1**).

Add four voltage sources (use *vpulse* from *analogLib*) to control the inputs of the first XOR2 gate. Think of how you could generate the 4 input possibilities. **Remember that there are two complementary pairs.** All possibilities should occur in one 20 ns^4 lapse. Set properties of the voltage sources (by pressing '*q*') as follows: voltages 1 and 2 to be 0 V and 1.8 V , respectively, or *vice versa*. Rise and fall times to be 100 ps . Play with period, pulse width and delay to generate the input sequence. **You may also use other types of voltage sources.**

Now add a voltage source as the main power supply (*vdc* in *analogLib*) and set the voltage to 1.8 V . Connect the ground and connect a small floating wire to the positive voltage node ('*PLUS*'). Go to *Create* → *Wire Name...* (or press '*L*'), name it *vdd!* (including the exclamation mark, meaning that this is a constant global net rather than a parameter) and select the wire. This action will match *vdd* terminal in our XOR2 with this voltage source. Complete the schematic by selecting a proper voltage for the undriven inputs.

Submit:

2. Explain how you implemented the input sources and include the output waveform that shows the 4 cases.
3. What's the worst case scenario you should simulate for t_{prd} and t_{pfd} (propagation fall and rise delay respectively)?

3 Schematic Simulation

In this section you will simulate the XOR2 schematic. In the `test_xor2` Schematic Cellview go to *Launch* → *ADE GXL* and select *Create New View*. This will open the Virtuoso Analog Design Environment window (from now on, '*simulation window*'). A window like Fig. 6 will pop-up. In this window you will manage design variables and parameters, select simulations that will run and

⁴The tool understands **m** as mili, **u** as micro, **n** as nano, **p** as pico, etc.

setup outputs to be plotted automatically. When properly set up this is a very powerful tool and this exercise will try to show you how to automate things as much as possible.

The left side shows the useful Data View bar. To create a new test, expand the ‘Tests’ item and select ‘Click to add test’. A new window will open (Fig. 7) and a small pop-up window will ask you to select the *cellview* you want to simulate. Choose the *test_xor2* schematic.

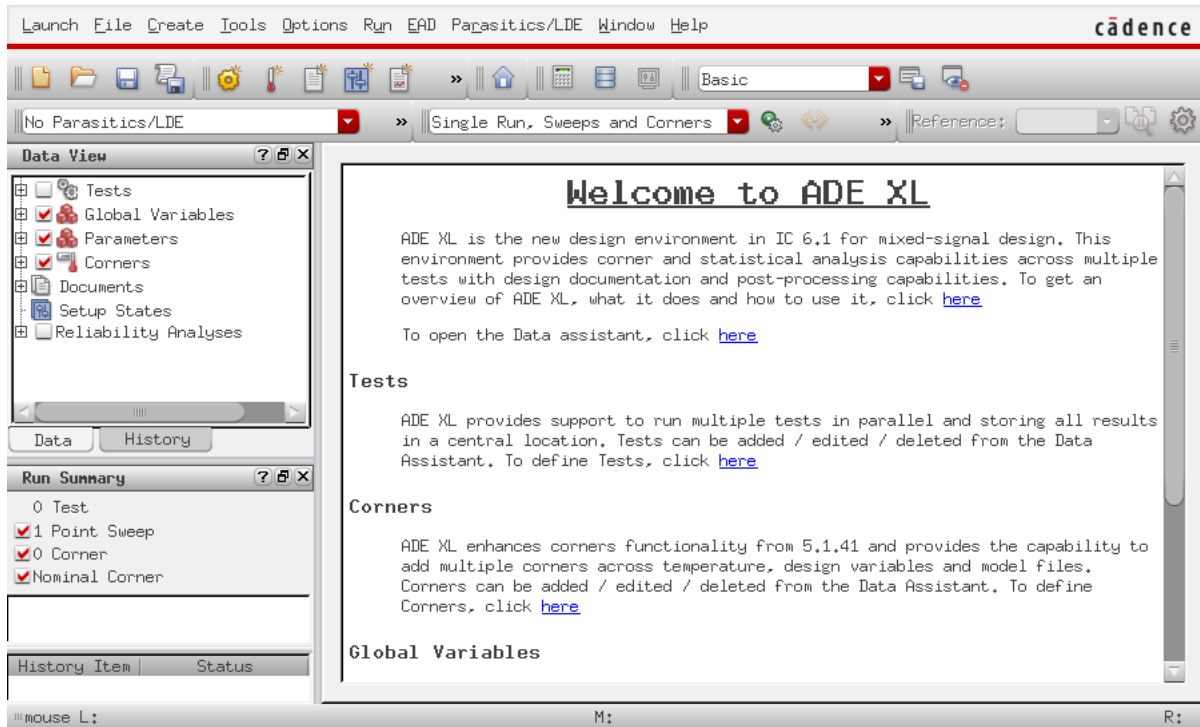


Figure 6: ADE XL Main Window

A brief description of the window in Fig. 7:

- Left side: Design Variables lists all defined parameters and variables. This is now empty but we can quickly import them from the schematic.
- Upper right sub-window: Analyses lists the defined simulations, some of their parameters and whether they are active or not.
- Lower right sub-window: Outputs shows the outputs you define for automatic calculation. These can display values, like DC bias points and results of formulas. It can also list output plots that are automatically plotted after each simulation run.

 


Figure 7: ADE XL Test Editor

Let's go ahead and save the simulation state now, even though it's currently empty. Go to *Session* → *Save State...* Under *Save State Option* select *Cellview*. This will save this simulation state and all its settings and results as another cellview in your cell. You may change the name in 'State' to something meaningful, like 'trise' or 'tfall' which is what we'll first do in the exercise itself. Click 'OK' to save. From now on, it will appear in the library manager as a cellview, and you may even open it without going through the schematic. Make sure to save your simulation state regularly and you won't have to redefine variables and outputs from session to session.

On the right there's a column of buttons. Click the topmost, 'Choose Analyses'. The Analyses window opens. It shows all possible simulations you can run. Let's start with a transient ('tran') simulation. Select it, set 'Stop Time' to 20 ns and make sure to check the 'Enabled' button at the bottom. It's here that you can later turn it off, although this is a fast simulation that doesn't take much time. Click 'OK' and you will see it appear in the Analyses List.

Click on the second button from the top, 'Edit Variables'. In the window that opens click 'Copy From' near 'Cellview Variables' and watch all the parametric values you wrote in the schematic magically appear in the list (in our case, only r appears). Choose 1 for now (we will perform a *Parametric Sweep* later). After writing each value click 'Change' to save it, or it won't be saved!

Go back to the ADE GXL window. The new test should appear beneath the *Tests* tag on the Data View bar. To run the simulation go to *Run* → *Single Run, Sweeps and Corners...* or click the Green-Play button. If you have errors at this point, carefully repeat this part to make sure you got all the setup right, and if there are still any errors seek help from the course or lab staff. Remember to save your state periodically.

3.1 Plot the output

After the simulation finishes successfully, we need to define an output to display the curve. There are different ways to do this. We'll explore two.

In both cases below, we explain selecting the output node of the first XOR2 gate. To compute propagation delay, you will also need to add waveforms of the two inputs of that gate.

3.1.1 Using the calculator

Click the ‘*Setup Outputs*’ button (third from the top) in the simulation window. Name the output ‘out’. Click ‘Open’ next to ‘Calculator’. This is the very powerful and very complicated calculator tool. Fig. 8 shows its window. The second bar from the top allows you to select different types of signals (e.g. vt and it for transient voltage and current respectively, etc.). Select ‘vt’. The schematic window pops up so that you can select the voltage signal of your preference. Select the output of the first XOR2 gate. You are taken back to the calculator window and it should show VT(“/netX”) (or another net name) in the *buffer*.

Go to *Tools* → *Plot* to plot the *buffered* signal (alternatively, click the calculator-wave symbol in the third bar from the top). You should immediately see the voltage waveform. Observe that you can change where the other signals are plotted by changing the option next to the calculator-wave symbol in the calculator window (options include ‘New subwindow’, ‘Append’ and ‘New window’).

The calculator allow us to perform different calculations with the results. It is extremely helpful in more complicated simulations. **Hint:** Explore functions *delay*, *riseTime*, *fallTime*, they can be useful in the following simulations. Using function *delay* you can define t_{pdr} , t_{pdf} , and then $t_d = \frac{t_{pdr} + t_{pdf}}{2}$.

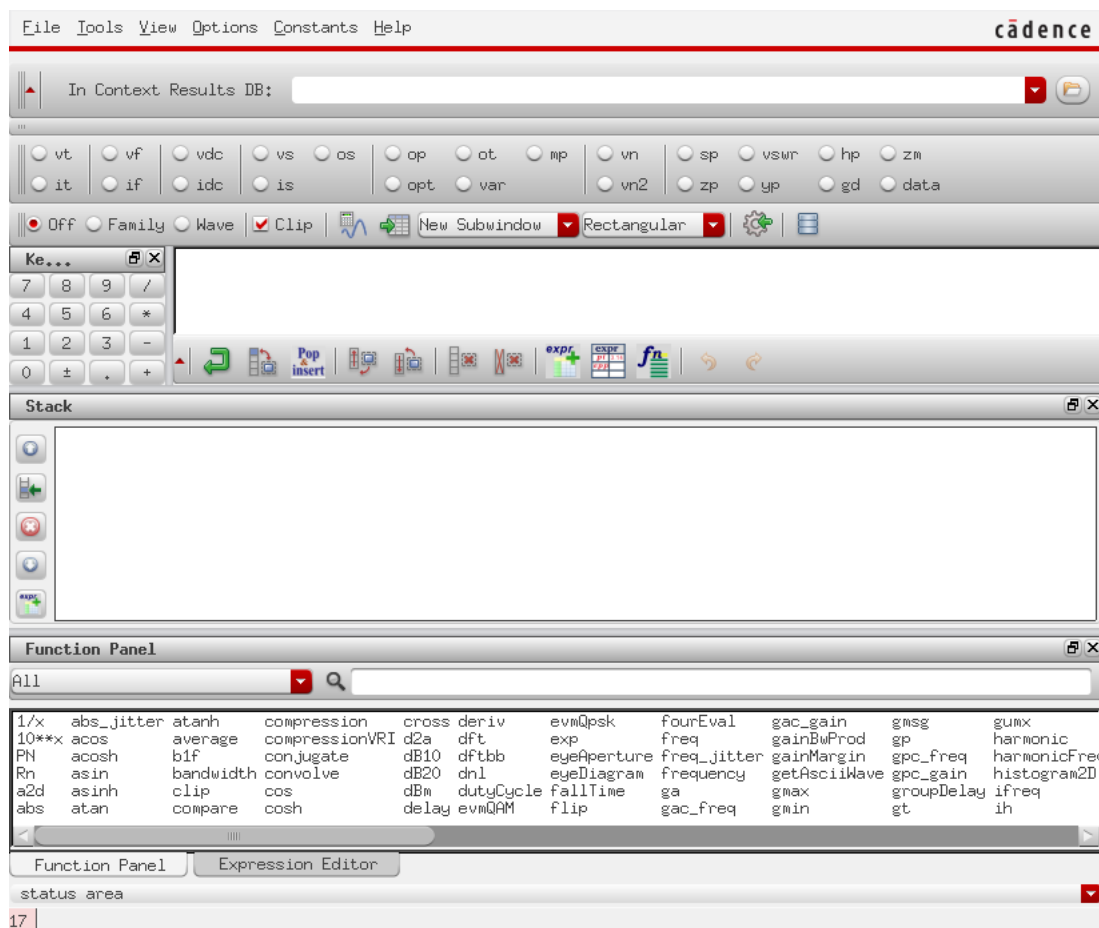


Figure 8: ADE XL Calculator

3.1.2 Using the Output Editor

In this case, instead of opening the calculator, in the ADEXL window, either go to *Outputs* → *Setup...* or click the Setup Output buttons (3rd from above on the right bar). Name the output as you wish, click the button ‘*From schematic*’. The schematic pops up. Select the signal of your preference. By selecting wires in the schematic, voltages will be plotted; by selecting pins, currents will be plotted. Observe the ‘*Type*’ field of each output to make sure it’s what you intend.

3.2 Parametric sweep

Now that we've experimented with the simulations, let's perform a parametric sweep. This powerful tool allows us to observe how the signals change by changing one or more parameters. In our case we observe the effect of PMOS width on propagation delay. **You are required to simulate the worst case scenario from the logic point of view. For this part you may use DC (constant) voltage sources for some inputs and reduce the simulation time.**

In the Data View bar of ADEXL, expand the 'Global Variable' tag. Your design variables should appear. Next to the variable name, click in the value field. A button with ... will appear. Click it, and in the new window (where the initial value 1 is shown) write your desired list of values such as {1, 1.5, 2, 2.5, 3, 3.5, 4} and click 'OK'. Run the simulation as above (*e.g.*, use the green Play button).

The plots are observable in the ADEXL window, Results tab. Click the chart button to see the waveforms. Zoom in (right click and drag) to one of the transitions. Observe how t_{pdf} and t_{pdr} (propagation fall delay and propagation rise delay respectively)⁵ are affected by r , namely by PMOS width. Add horizontal and vertical markers to help you find the relevant points by pressing 'h' and 'v' respectively on the 'Visualization & Analysis' window. Double clicking a marker helps select exact level. Select 50% levels and read out times. Another method is to use the *delay* function as mentioned before.

Look for the r value that yields a symmetric gate, namely where t_{pdf} and t_{pdr} are roughly equal and for the r value that yields to minimum delay. You will need to use those r values in subsequent sections.

Submit:

4. Simulation waveforms of the parametric sweep of r (submit at least 3 cases).
5. Make a table showing t_{pdf} and t_{pdr} for every r .
6. Based on the simulations, what is $W_{P_{opt}}$ (W_P that results in an optimal/minimum delay)?
7. Based on the simulations, what is $W_{P_{sym}}$ (W_P that results in a symmetric gate *i.e.*, equal t_{pdf} and t_{pdr})?
8. How are t_{pdf} and t_{pdr} changed/influenced by the input-order-of-arrival *i.e.*, when the inputs do not arrive simultaneously?
9. Calculate, theoretically and using the technology parameters,⁶ $W_{P_{opt}}$ for minimum propagation delay.

3.3 Corner simulations

You will now perform simulations to observe how environmental changes affect circuit performance. The desired environmental corners for the 0.18 μm process are summarized in Table 1.

| Corner | Voltage | Temperature |
|--------|---------|-------------|
| F | 1.98 | 0 °C |
| T | 1.8 | 70 °C |
| S | 1.62 | 125 °C |

Table 1: Environmental Corners

⁵Remember: propagation delay accounts for *maximum time from the input crossing 50% to the output crossing 50%*

⁶You may use: $\mu_n = 291 \text{ cm}^2/Vs$, $\mu_p = 71 \text{ cm}^2/Vs$, $V_{tn} = 0.5 \text{ V}$, $V_{tp} = -0.42 \text{ V}$, $t_{ox} = 50\text{\AA}$, $\epsilon_{ox} = 3.85$, $C_{ja} = 1.1 \times 10^{-3} \text{ pF}/\mu m^2$

We create a new test to study corners. We will vary only supply voltage and temperature, but leave transistor models in the ‘typical’ mode (if needed, designers can try slow and fast transistors as well, to investigate On Chip Variation, OCV). Under the Tests item on the Data View bar in ADEXL, select Click to add test, select same *test_xor2* schematic, Copy from Cellview and choose the symmetric *r* value found above.

In the schematic window, go to *Window* → *Assistants* → *Variables and Parameters*⁷. The Variables and Parameters bar should be open on the left. Select the voltage source *vdd* and select the ‘Parameter’ tab in the aforementioned bar. On the filter menu select ‘CDF Parameters’. A list with all the *vdc* parameters appears. Right click on ‘DC voltage’ and select ‘Create Parameter’. Go back to the ADE XL window and observe that this parameter appears under ‘Parameters’ tag.

Now we will create a new corner. In ‘Data View’ expand ‘Corners’ tag and click to add a new corner. A window like Fig 9 will open. First we will import the *model files*. Click on ‘Click to add’ below the ‘Model Files’ title. In the window that pops up click the button ‘Import from Tests’, a list of models will appear in the window and press OK.

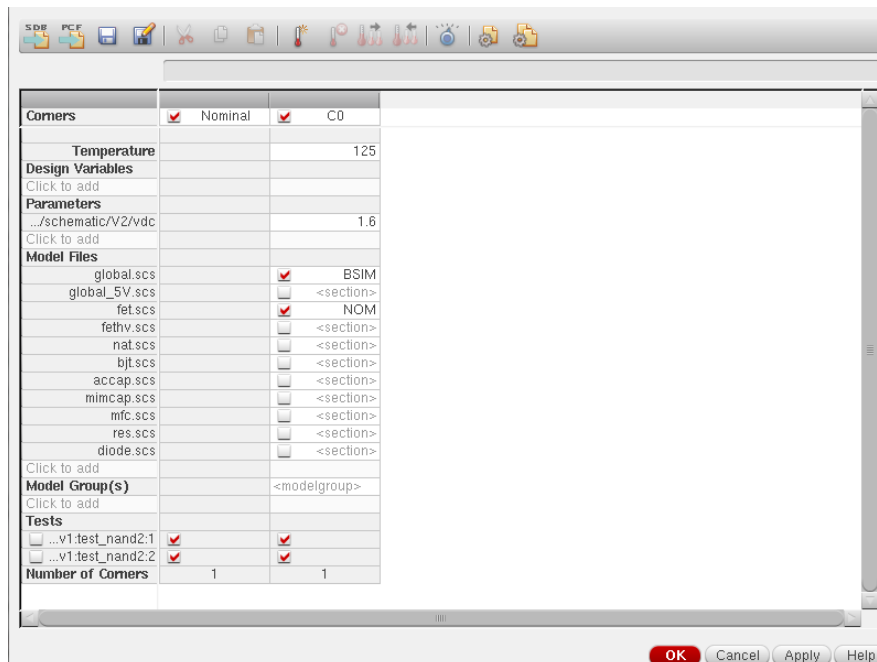


Figure 9: Corners Setup Window

Create a new corner by clicking the thermometer icon. Under the ‘Parameters’ title select ‘Click to add’ and add *vdc*. In ‘Model Files’ under the created corner column, select *global.scs* to be *BSIM* and *fet.scs* to be *NOM* (e.g, nominal). Then, change the temperature and *vdc* values as desired for the specific corner. Repeat the procedure to create corners (TTSS, TTFF, TTTT)⁸ and press OK. Run your simulation as described before.

3.3.1 TTSS Corner

Based on the parameters shown in Table 1 create the corner for TTSS. Simulate the Test Circuit and compare the results with the Typical (TTTT) case.

⁷Sometimes this option is not available in the schematic window. If that is the case, close the schematic and open it from the ADE XL window. Go to *File* → *Open* and select ‘Open in new tab’.

⁸We mark the corner using four letters (which can be T, F or S): [nMOS speed][pMOS speed][Voltage][Temperature].

3.3.2 TTFF Corner

Based on the parameters shown in Table 1 create the corner for TTFF. Simulate the Test Circuit and compare the results with the Typical (TTTT) case.

Submit:

10. Table with results of Corners Simulations.
11. Explain why and how t_{pd} changes in every case.

3.4 Higher load (FO4)

Now create a new schematic to simulate the FO4 case, name it *FO4*. Insert the XOR2 and load it with 4 copies of itself. The circuit should look like Fig. 10(a). Perform the simulations for a typical environment, and observe the changes with respect to the FO1.

Assuming a simple sequential path consisting of one zero-delay flip-flop (as in Fig. 10(b)), one FO4 XOR2 gate driving four (4) FO1 XOR2 gates and a second zero-delay flip-flop, determine the maximum frequency in which we can operate the circuit. **Note that you do not need to draw a new schematic including the FF, nor do you need to simulate it. The requested frequency bound can be computed from the basic combinational logic simulation of Fig. 10(a).**

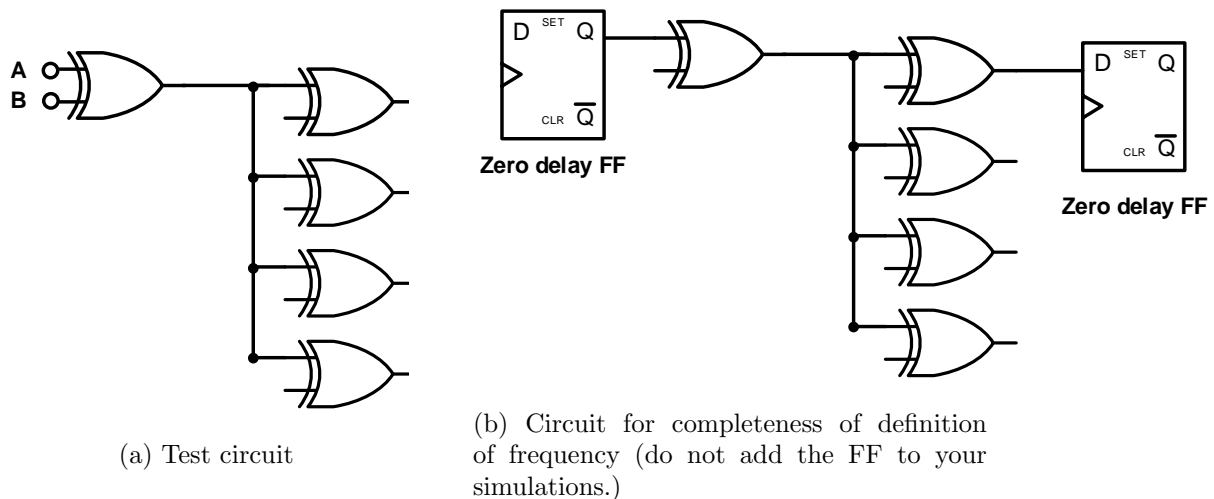


Figure 10: FO4 circuit

Submit:

12. Simulation results of FO4.
13. Explain why and how t_{pd} changes. Relate to the linear delay model (logical effort).
14. What is the maximum frequency that can be achieved in a synchronous circuit as Fig. 10(b) if $t_{setup} = 0$ and $t_{clk-out} = 0$?

3.5 Power Estimation

Static CMOS gates are very power-efficient because they dissipate only leakage power while idle. For a long time power was a secondary consideration behind speed and area. As the transistor has shrunk following Moore's law, the transistor counts and frequencies have increased, power consumption has increased significantly and is now a major design constraint (this is discussed further when we

study scaling later on).

Power dissipation in CMOS circuits consists of two components:

- Static dissipation:
 - subthreshold conduction through OFF transistors (typically, this is the largest contributor)
 - tunneling current through the gate
 - leakage through reverse-biased diodes
- Dynamic dissipation:
 - charge and discharge of load capacitances
 - short circuit current while both PMOS and NMOS are turned weakly ON, typically during a transition.

You will perform simulations to estimate the power. **Use the FO4 test circuit.**

Hint: To perform the simulations of section 3.5.1 and 3.5.3 you will need to select inside nets of the XOR2 instances. This can be done by double-clicking the respective instance and by selecting to open the instance's schematic in the pop-up window.

3.5.1 Static dissipation

Ideally no power is dissipated in an OFF transistor. However, there are several secondary effects that lead to small currents flowing through the OFF transistor. Assuming the leakage current is constant, the static power is:

$$P_{static} = I_{static}V_{DD} \quad (1)$$

Perform a simulation to determine the static power dissipation of the FO4 gate. You can use the calculator to implement Eq. 1.

3.5.2 Dynamic

The dynamic power is determined by the well-known equation:

$$P_{dynamic} = \alpha C_L V_{DD}^2 f \quad (2)$$

Considering $\alpha = \frac{1}{2}$, the technology parameters (to assess C_L and the frequency calculated in the section 3.4 determine $P_{dynamic}$ of the FO4 gate.

3.5.3 Short Circuit

For the purpose of this lab we will determine the short circuit power as the average current supplied by the source (V_{DD}) when the output changes from 20% to 80%, multiplied by the supply voltage V_{DD} .

Submit:

15. Simulation results for short circuit and static dissipation.
16. Calculations of the 3 power estimation cases.
17. What is the best strategy to reduce the dynamic power? Relate to the parameters C_L , V_{DD}^2 and f , and to *scaling*. What are the pros and cons of each strategy?
18. How can you reduce the short circuit power dissipation?

3.6 Sizing

Let us play with cell sizing. In most multistage logical paths the last gate must drive a ‘big’ capacitance, therefore the different gates can be *sized* to reduce the total delay of the path. Consider the circuit in Fig. 11, where a logical path of four XOR2 gates drive a capacitance of 100 fF. Starting from left, each stage is a times bigger than the previous stage.

Create a new schematic, call it *sizing* and implement the circuit. In the first XOR2 gate, use $W_N = W_{MIN}$ and a symmetric W_P ($W_{P_{sym}}$) as determined in Section 3.2 for a symmetric gate. Simulate and perform a parametric sweep of a to find the optimal value that achieves the shortest delay. **Hint: To perform a^n you should write $a**n$ in the respective property field.**

 


Figure 11: Sizing circuit

Submit:

19. What's the optimal a (a_{opt}) for minimum delay?
20. Simulation results (include just 3 cases, including a_{opt}). Explain what happens when $a = 1$.

3.7 Buffer insertion

Buffer insertion is used for driving large capacitance that could result from bigger gates, long wires or I/O. As the name suggests, the idea is to insert buffers in the path between our gate and the big load. Each inverter will be a times bigger than the previous one. In this case we choose $a = 2.6$ (indeed, theoretical optimization would yield the factor e). You will simulate the circuit to find the optimal number of inverters for minimum delay (N_{opt}).

Begin by creating the inverter schematic. Proceed as in Section 2, name the transistor width pPar("Wn") and pPar("Wp") for the NMOS and PMOS respectively. Create the inverter symbol. Then, create a new schematic, call it *buffering*. The circuit should be as Fig. 12. Select $W_N = W_{MIN}$, and W_P for a symmetric XOR2. The first inverter must have the following dimensions: $W_N = aW_{MIN}$ and $W_P = 4aW_{MIN}$ (we assume that this ratio produces an almost symmetric inverter). Calculate the delay as $t_d = \frac{t_{pr} + t_{pf}}{2}$. *Note: the original logical value can be inverted (i.e., you can place an odd number of inverters).*

 


Figure 12: Buffering insertion circuit

Submit:

21. What is the optimal N_{opt} ?
22. Simulation results (include just 3 cases).

4 Layout

In this section we will create the layout of the 2-input XOR gate using the Layout GXL tool of Virtuoso. This tool is very useful and comfortable as it saves time and mistakes compared to manual design of the layout. Among other benefits, it helps to maintain the correlation between the schematic and layout and to prevent DRC mistakes.

We wish to create a layout subject to the following constraints:

1. Minimum area
2. Maximum height of the cell: $8\mu m$
3. Use metal M1 only.
4. Height of GND and VDD rails: $0.72\mu m$.
5. Include NTAP and PTAP in the cell (Ohmic connections to the substrate and n-Well).
6. Input and output pins must be M1.
7. For each input interconnect (if possible) both MOSFET gates with poly.

IMPORTANT: Before you start with the layout, go to the ‘Library Manager’ and copy the schematic into a new cell. Call it *xor2_fix*. In this version we will replace the parametric widths by fixed values. Open the schematic and change the finger width of the PMOS to the numerical value of $r_{opt}W_N$ (as found in Section 3.2). It is important that you work from the transistor schematic view of *xor2* and NOT from *xor2_test*.⁹ Create a new symbol for the *xor2_fix*.

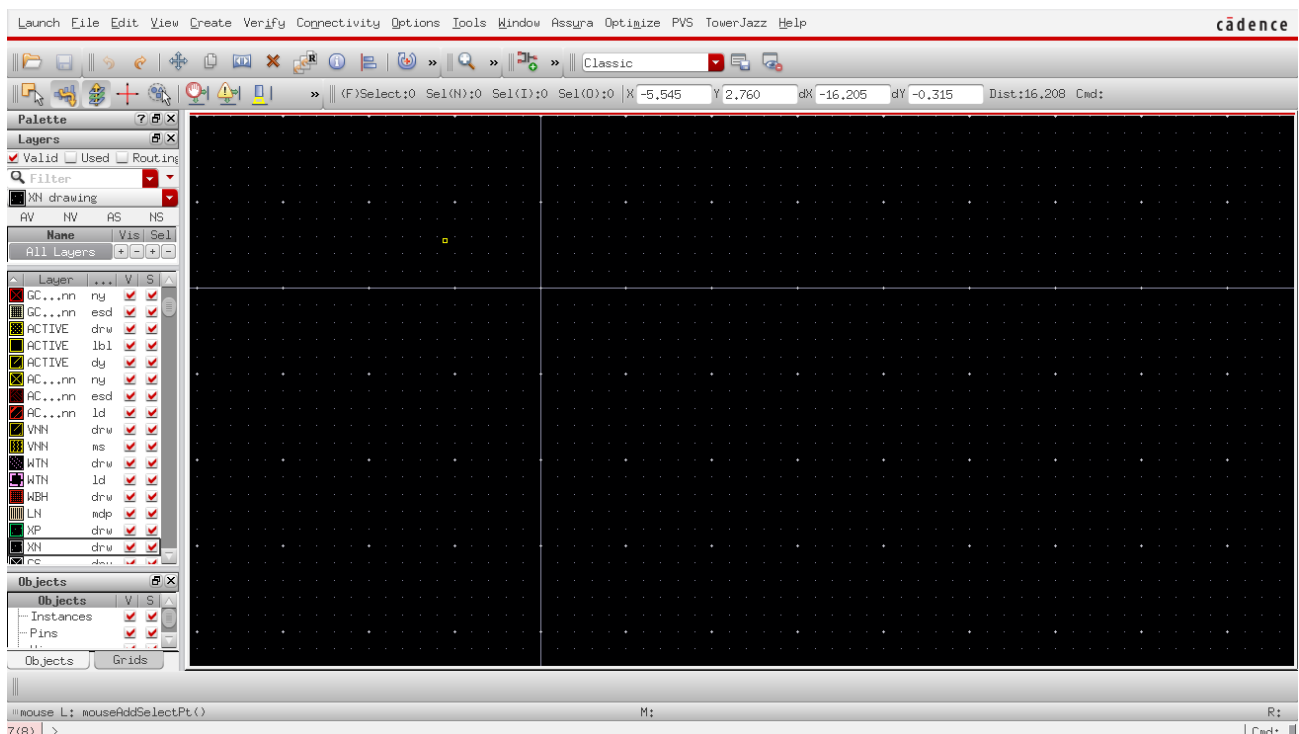


Figure 13: Layout GXL

To start the layout, in the schematic window, go to Launch→Layout GXL, choose the options ‘Layout: Create New’ and ‘Configuration: Automatic’. After a short while, a clean layout window

⁹Copying cell schematics: In Library Manager window, *Edit* → *Copy...*, and select From and To names.

will open aside the schematic as in Fig. 13. At the left side of the layout window we see the 'Palette', where the layers are displayed.

The used layers in TowerJazz $0.18\mu\text{m}$ for this design will be:

- Contact (CS). Has an exact dimension of 0.22×0.22
- Poly (CG). Polysilicon can only be connected to M1.
- Active (ACTIVE). Can only be connected to M1.
- n⁺Select (XN) and p⁺Select (XP).
- n-Well (WN).
- Metal 1 (M1).

Other important things to consider:

- Use only layers with *purpose* of type drawing (drw). Other types may be used for labeling, drc, dummy, etc.
- Obviously, if two polygons **of the same layer** overlap or touch each other, there's a short circuit between them.
- If two polygons **of different layers** overlap or touch, there's no electrical connection between them. One exception is the critical overlap of poly and active, that creates a transistor.

Most used actions in layout design:

- Create rectangle: First you need to choose the layer to which the rectangle will belong. Then go to *Create* → *Shape* → *Rectangle* or press 'r'. Select the first vertex and then the opposite vertex. You can update the dimensions afterwards, so don't worry if it doesn't match the desired dimensions at first.
- Modify dimensions: Select the rectangle you want to modify, and press 'q'. The shape's properties will open. There you can change the height and width.
- Stretch shape: Deselect all by clicking on the black background and go to *Edit* → *Stretch* or press 's'. Select the side of the shape you intend to stretch and click in the desired new place. No dragging.
- Copy: Go to *Edit* → *Copy* or press 'c'. Select the shape you want to copy and then select where you want to place the new copy. *Important: before you paste the shape you can press F3, enabling you to rotate, mirror and change other properties of the copy.*
- Move: Select the shape you intend to move, either drag or go to *Edit* → *Move* or press 'm' and move.
- Delete: Select the shape and press the Delete button of your keyboard.
- Measure dimensions: Go to *Tools* → *Create Ruler* or press 'k'. Select the point first and last point. Afterwards, erase all rulers by going to *Tools* → *Clear All Rulers* or by pressing 'Shift+k'.

4.1 Placement

In the first stage we'll import the transistors and the terminals (namely ports or pins) present in the schematic. The terminals are defined on M1 in our case. Go to the schematic and select all the NMOS transistors. In the layout window, go to *Connectivity* → *Generate* → *Selected From Source*. You can now see the two NMOS transistors in the layout. Place them by clicking the desired position. Press 'Shift+f' to observe the NMOS layers ('Shift+f' display all layers in a hierarchic design as if it were a flat design).

Go to the schematic window and select one of the NMOS transistors in the schematic. Observe that the selected transistor is highlighted also in the layout window. Select any net (wire) in the schematic, and observe what happens in the layout (connected items are selected, and lines appear that indicate connectivity). Repeat the same step to insert the PMOS and the terminals. Observe that the connectivity is highlighted and preserved in the layout. Note also that the tool attempts to preserve relative transistor positions.

Each pair of NMOS is connected in series, and their shared node (source in one, drain in the other) is not connected to anywhere else. But when importing the transistors, they came equipped with a contact on each end. We wish to remove the unnecessary contacts where the NMOS transistors are interconnected. This can be done by the tool, as follows. Place one of the NMOS transistors so that its drain node overlaps the source node of the other NMOS transistor. The tool graciously removes the redundant two contacts, as in Fig. 14.

 


Figure 14: Combine transistors

Do the same with the NMOS transistors. The result should be different, because their interconnecting node is also connected elsewhere. Select the terminals and check that all pins are defined as M1 (drw). If not, change the appropriate property to M1 (drw) (**remember** *purpose 'drawing'*). Now check connectivity, go to *Connectivity* → *Check* → *Against Source*. Verify that all the connections exist besides ground and *vdd*.

4.2 DRC

Design Rule Check (DRC), as the name implies, checks that the layout complies with the design rules of a given IC technology. As we have learned in class, these rules prevent potential fabrication problems.

Before you perform DRC, open a terminal and "mkdir /tmp/username_drc" (where username is your user name account) in a terminal ¹⁰. In the layout window, go to *Assura* → *Run DRC*. A window as in Fig. 15 will open. In 'Technology', select *ts18sl_6M1L* (maximum 6 layers of metal, one top thin layer), in 'Switch Names' write "*3V 6LM BLOCK OA*" (technology file allows 3.3V I/O cells, maximum 6 layers of metal, DRC is applied to the entire block and 'open access' format is employed) and select 'Rule Set' as "*DRC_BLOCK*". Click *OK*. In the progress window that opens, also click *OK*. When the tool finishes (after a while), it will ask if you want to see the results; press 'Yes'.

¹⁰Check in every new session that this folder exists before you perform DRC or LVS.

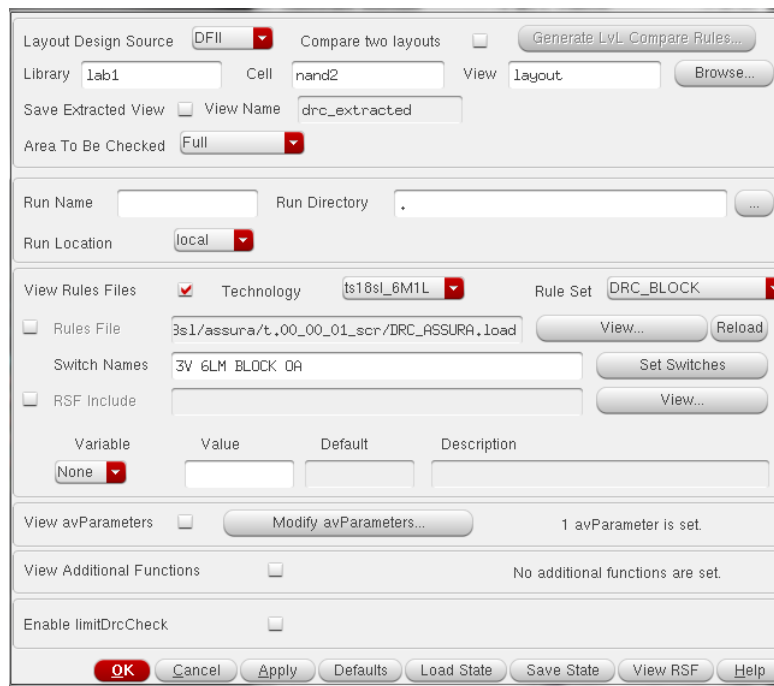


Figure 15: DRC window

A window that describes the errors will open. Each type of error includes also error count. You can click the arrows to observe the mistakes in the layout, one by one. Correct all mistakes, except those of types *LUO*, *GC.A.1-poly island area*, *AA.C.1-coverage* and *M1.A.1-metal island area*. At the end of DRC, select *Assura* → *Close Run*.

4.3 Routing

Now you are going to wire the different elements in your layout. Let's start by using poly to connect a PMOS and an NMOS to the input 'a'. To create a wire go to *Create* → *Wiring* → *Wire* or press 'p'. Select the layer to which the wire will belong, click on the first edge to start drawing, move the cursor to draw, click once to change direction and double click to finish. Observe that the tool automatically changes the layer if you directly click on an existing 'routing' layer such as poly or metal 1.

A contact is necessary to connect poly and M1. You can create the contact stack (consisting of the contact and, if needed, extensions of poly and/or M1 to abide by design rules) by going to *Create* → *Via* or pressing 'o'. In 'Via Definition' select 'M1_PO'. It will bring up the complete stack. Complete all wires and contacts. Make use of the schematic to highlight connections.

Next, create power and ground rails and the ohmic contacts to the P-sub and N-Well (PTAP and NTAP). The TAP stack is composed by ACTIVE, XN or XP, CS and M1. Both rails must have a height of $0.72\mu m$ and equal width (and must cover the cell from side to side, so that we can place cells next to each other without adding extra power rails between them). Finally, you have to indicate that those rails correspond to *vdd* and *gnd*. Go to *Create* → *Pin*. In 'Terminal Name' fill the name as it appears in the schematic (*vdd!* or *gnd!*) and select the respective wire.

After finishing routing (or any time during) run DRC again. **By the end of this part, your work should be free of DRC mistakes apart from errors of type *AA.C*¹¹.** Run another connectivity check by the end of this stage (see 4.1).

¹¹This error indicates that the total area of the active layer is below the expected for a certain section in the chip. This problem is usually solved by *dummy placement* i.e., adding polygons of that layer which doesn't have any functional or electrical purpose.

4.4 Layout vs Sechamtic (LVS)

The next step is to prove that the layout matches the schematic. This is done by extracting the transistors and their connections from the layout, followed by running a layout *versus* schematic tool. In the layout window, go to *Assura* → *Run LVS*. A window similar to Fig. 16 will open.

In ‘*Technology*’ choose *ts18sl_6M1L*. Click ‘OK’ and ‘OK’ again in the process window. Once finished, another window pops up asking if you want to see the report. Click ‘Yes’. **Correct any mistake in the LVS and repeat checking LVS until the design is error free.**

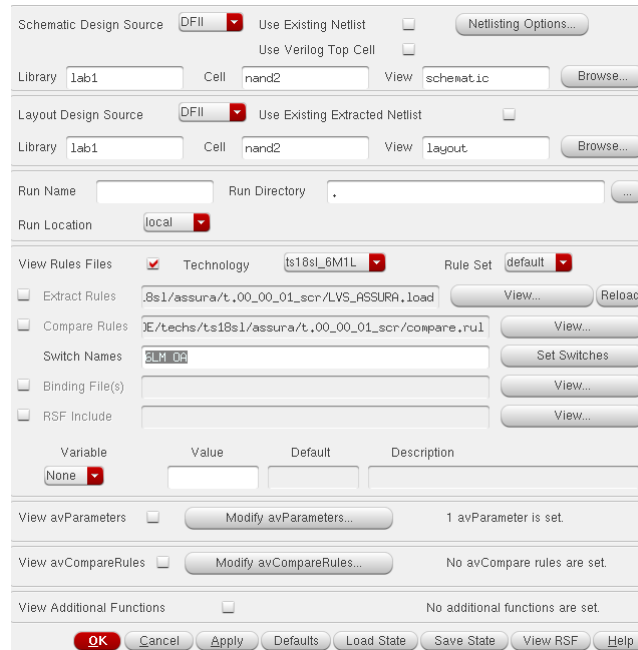


Figure 16: LVS window

Submission from Section 4

23. Layout print-screen **with a rule on each axis showing the cell’s dimensions**.
24. What is the total area of your cell?
25. Explain how does the placement of one NMOS (PMOS) above and aside the other affects the gate performance. Which parameters are changed?
26. Print screen of the DRC and LVS reports.

5 Hierarchical Design


In this section we create a hierarchical layout design. Let’s use the FO4 circuit for these purpose (no flip-flops are needed, only one FO4 and four FO1 gates). **Create a new schematic called *FO4_fix***. Insert the five fixed-width XOR2 gates (*xor2_fix*) as in Fig. 10 and connect them properly. Once done, Check & Save.

Go to *Launch* → *Layout GXL* and choose the options ‘*Layout: Create New*’ and ‘**Configuration: Automatic**’. A clean layout will open. Import your *xor2_fix* layout by going to *Create* → *Instance* or pressing ‘*i*’. Go to your library (*Lab1*) and select your XOR2 layout. Insert all five XOR2 one aside the other horizontally. Note that in practice, we would have created a stronger gate for FO4, but for the purpose of this lab we simply use same layout for all five gates.

Next, match all gates in the layout with each XOR2 in the schematic, as follows. **It is important to maintain a proper order.** In the layout window, go to *Connectivity* → *Define Device Correspondence...* A window like Fig. 17(a) opens up. The left column indicates unbounded instances in the schematic and the right one indicates the unbounded instances in the layout. Make the correspondences by selecting one on each column and then click ‘*Bind*’. If you make a mistake you can select *Filter: All instances* and ‘*Unbind*’ the wrong correspondence.



(a)

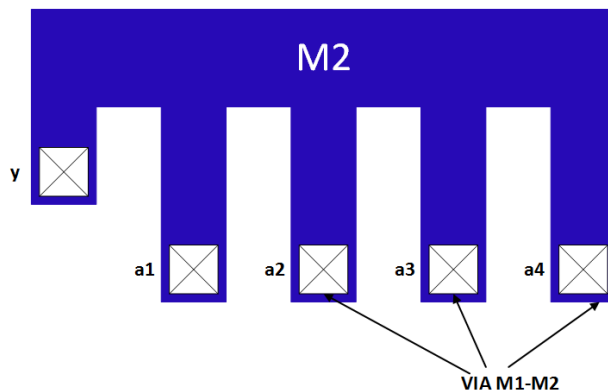

(b)

Figure 17: (a) Define Device Correspondence, (b) Routing in hierarchical design.

5.1 Routing

First, perform a Connectivity Check (as in section 4.1). Observe the output: only the routing should be missing. Prior to adding wires, perform a DRC check and correct all mistakes (if any) except for errors of type AA.C.

Now let’s route all wires. Begin by *vdd* and *gnd*. As they are pins proceed as in section 4.3. They must use metal 1 and have the same height as all XOR2 cells. These will be our power rails. Then proceed to route all other wires. The central wire (output of first XOR2 and input to the other four XOR gates) can be laid out using metal 2 and can go on top of the *vdd* rail (this is not ideal, but easy to do). From the top M2 line, draw stubs of M2 to reach the ‘*y*’ output of the first gate and all four ‘*a*’ inputs of the following four gates. Connect the M2 stubs by means of M1-to-M2 vias. This structure is demonstrated in Fig. 17(b). Check the correspondence by clicking in the schematic. When you have finished the routing, perform DRC and LVS again and repeat fixing until there are no more errors.

5.2 RC Extraction

You will now perform the RC extraction (RCX) of your hierarchical layout. The parasitic extraction tool calculates both the parasitic RC of the devices and the interconnect. The major purpose of parasitic extraction is to create an accurate analog model of the circuit, so that detailed simulations can emulate actual digital and analog circuit responses.

To run the RCX you must have previously run the LVS and corrected all errors. In the layout window go to *Assura* → *Run Quantus QRC*. In the menu that opens, go to the *Setup* tab and in the *Technology* field select *ts18sl.6M1L*. In the field *RuleSet* select *default*. In the *Output* field select *Extracted View*, do not change other parameters in this tab. Now go to the *Extraction* tab, select *Extraction Type* to be *RC*, and fill the *Ref Node* field with your ground pin (e.g., *gnd!*). Click *OK*, the extraction will start, and an extracted view (*av_extracted*) will be created.

5.3 Extracted Layout Simulation

We are ready to simulate the extracted layout and compare it to the previous simulations. Open your *FO4_fix* schematic, and create a new simulation window. Simulate again this circuit as in the first part of the lab. Calculate (extract) the delay (t_{pd}) of this circuit.

Now, we will simulate the extracted circuit. In ADE L, go to *Setup* → *Environment....* In the *Switch View List* add the word *av_extracted* before the word *schematic*. Then, proceed to simulate as always. Calculate (extract) the delay (t_{pd}) of this circuit.

Submission from Section 5

27. Layout print-screen **with a rule on each axis** showing the cell's dimensions.
28. What is the total area?
29. Print-screen of the DRC and LVS results.
30. Explain (shortly) how Place & Route influence the chip's performance. In your answer refer to: area, speed and power.
31. Indicate pros and cons of hierarchical design using 'Standard Cells'. Is it the best layout we could do? In your answer refer to: area, speed and power.
32. Why do we use *constant-height* cells?
33. Submit the waveforms of the delay simulations with and without the RCX for the fixed FO4 circuit. Include a table with the results.
34. What's the increment in the t_{pdr} , t_{pdf} , and t_{pd} considering the parasitics?
35. How could you reduce the parasitics in your layout to reduce the delay?