

1 Introduction

This document guides the hardware engineers to design and test their LPC55(S)xx processor-based designs. The document provides information about board layout recommendations and design checklists to ensure first-pass success and avoid any board bring-up problems.

This guide is released with the relevant device-specific hardware documentation such as data sheets, reference manuals, and application notes available on nxp.com.

2 LPC55(S)xx family comparison

All LPC55Sxx/LPC55xx family is based on Arm[®] Cortex[®]-M33 core, with PowerQuad Accelerator and CASPER Accelerator. The **S** in the middle of part name means this part provides more security features, such as TrustZone Support.

Table 1. LPC55Sxx family core features

Family	Core frequency	Dual core	Power Quad	CASPER
LPC55S0x/LPC550x	96 MHz	—	—	YES
LPC55S1x/LPC551x	150 MHz	—	—	YES
LPC55S2x/LPC552x	150 MHz	YES	YES	YES
LPC55S6x/LPC556x	150 MHz	YES	YES	YES

Table 2. LPC55Sxx/LPC55xx peripherals

Family	Flexcomm	50 MHz HS-SPI	HS USB	FS USB	CAN FD	SDIO
LPC55S0x/LPC550x	8	1	—	—	1	—
LPC55S1x/LPC551x	8	1	1	1	1	—
LPC55S2x/LPC552x	8	1	1	1	—	1
LPC55S6x/LPC556x	8	1	1	1	—	1

Contents

1	Introduction.....	1
2	LPC55(S)xx family comparison.....	1
3	Power supply.....	2
3.1	Introduction.....	2
3.2	Bulk and decoupling capacitors...	5
4	Clock circuitry.....	6
4.1	Introduction.....	6
4.2	Crystal oscillator.....	7
4.3	RTC oscillator.....	8
4.4	Common suggestions for the PCB layout of oscillator circuit.....	9
5	Boot mode configurations.....	10
5.1	Boot mode selection.....	10
6	Debug and programing interface...	11
6.1	Debug connector pinouts.....	13
7	Communication modules.....	14
7.1	CAN interface for CAN-FD module	14
8	Analog.....	15
8.1	ADC impedance.....	15
9	Recommendations.....	16
9.1	Pin descriptions.....	16
9.2	Termination of unused pins.....	17
9.3	PCB.....	18
9.4	General board layout guidelines	18
10	References.....	23



Table 3. LPC55Sxx/LPC55xx Timers

Family	CTimer	SCT	MRT	WWDT	Code WDT	RTC	OS-Timer
LPC55S0x/LPC550x	5	1	1	1	1	1	1
LPC55S1x/LPC551x	5	1	1	1	1	1	1
LPC55S2x/LPC552x	5	1	1	1	—	1	1
LPC55S6x/LPC556x	5	1	1	1	—	1	1

Table 4. LPC55Sxx/LPC55xx analog peripherals

Family	16 bit ADC	Comparator	12 bit DAC
LPC55S0x/LPC550x	1 (10ch)/2 Msps	1 (5 inputs)	—
LPC55S1x/LPC551x	1 (10ch)/2 Msps	1 (5 inputs)	—
LPC55S2x/LPC552x	1 (10ch)/1 Msps	1 (5 inputs)	—
LPC55S6x/LPC556x	1 (10ch)/1 Msps	1 (5 inputs)	—

Table 5. LPC55Sxx/LPC55xx packages

Family	HVQFN 48	HVQFN 64	HTQFP 64	VFBGA 98	HLQFP 100	HLQFP 144	VBGA 196
LPC55S0x/LPC550x	/		/				
LPC55S1x/LPC551x			/	/	/		
LPC55S2x/LPC552x			/	/	/		
LPC55S6x/LPC556x			/	/	/		

For details, see the latest version of the Datasheet and User Manual on www.nxp.com.

3 Power supply

3.1 Introduction

LPC55Sxx series requires single 1.8 to 3.6 V operation voltage supply.

LPC55S0x/LPC550x, LPC55S1x/LPC551x, LPC55S2x/LPC552x and LPC55S6x/LPC556x internal core's voltage are supplied by internal DC/DC regulator, this DC/DC regulator needs external inductance and two or three capacitors. For details, see *Using the DCDC feature* (document [AN12325](#)).

 


Figure 1. Using internal DC/DC converter

The power and ground pins are described in subsequent sections.

 


Figure 2. Power supply pins

NOTE

The capacitors in Figure 2 is only for reference.

Table 6. Power domains and decoupling capacitors

Power domain	Description	Voltage	Bulk/Bypass capacitor for domain			Decoupling capacitor per pin	Characteristics
			Package				
			HTQFP64	VFBGA98	HLFP100		
USB0_3V3	USB0 Analog 3.3 V supply	3.3 V	10 uF	10 uF	10 uF	0.1 uF	X7R Ceramic
USB1_3V3	USB1 Analog 3.3 V supply	3.3 V	10 uF	10 uF	10 uF	0.1 uF	X7R Ceramic
VDD	Single power supply powering I/Os	1.8 - 3.3 V	10 uF	10 uF	10 uF	0.1 uF	X7R Ceramic

Table continues on the next page...

Table 6. Power domains and decoupling capacitors (continued)

Power domain	Description	Voltage	Bulk/Bypass capacitor for domain			Decoupling capacitor per pin	Characteristics
			Package				
			HTQFP64	VFBGA98	HLFP100		
VBAT_DCD C	Supply of DCDC output	—	22 uF + 100 nF + 47 pF				X7R Ceramic
VBAT_PMU	Core supply. For applications with DCDC converter, VDD_PMU and FB are tied at PCB level.						
VDD_PMU	Core supply						
VDDA	Analog supply voltage	3.0 - 3.6 V	10 uF	10 uF	10 uF	0.1 uF	X7R ceramic
VREFP	ADC positive reference	0.985 - VDDA	10 uF	10 uF	10 uF	0.1 uF	X7R Ceramic
VREFN	ADC negative reference		VSS, VSSA and VREFN must be shorted to GND at package level.				
USB0_VSS	USB0 analog 3.3 V ground	GND					
USB1_VSS	USB1 analog 3.3 V ground						
VSS	Ground						
VSS_DCDC	Star ground connections						
VSS_PMU	Star ground connections						
VSSA	Analog ground						
FB	Feedback node						
LX	DCDC power stage output						

3.2 Bulk and decoupling capacitors

The effectiveness of the bulk/bypass and the de-coupling capacitors depends on the optimum placement and connection type. The bulk capacitors are used for a local power supply to the power pin, near the decoupling capacitors and as close as possible to the assigned reference voltage pin. Decoupling capacitors make the current loop between supply, MCU and reference ground as short as possible to reduce high frequency transients and noises. Therefore,

- All decoupling capacitors should be placed as close as possible to each of their respective power supply pin.
- The ground side of the decoupling capacitor should have a via to the pad which goes directly down to the internal ground plane.

- The route distance between the capacitors to the power plane should be as short as possible.

 


Figure 3. Bulk and decoupling capacitor connection

4 Clock circuitry

4.1 Introduction

The LPC55S1x/2x/6x has the following clock sources:

- Internal Free Running Oscillator (FRO). This oscillator provides a selectable 96 MHz output, and a 12 MHz output (divided down from the selected higher frequency) that can be used as a system clock. The FRO is trimmed to +/- 2% accuracy over the entire voltage and temperature range.
- 32 kHz Internal Free Running Oscillator FRO. The FRO is trimmed to +/- 2% accuracy over the entire voltage and temperature range.
- Internal low power oscillator (FRO 1 MHz) trimmed to +/- 15% accuracy over the entire voltage and temperature range.
- Crystal oscillator with an operating frequency of 16 MHz or 32 MHz. Option for external clock input (bypass mode) for clock frequencies of up to 24 MHz.
- Crystal oscillator with 32.768 kHz operating frequency. Option for external clock input (bypass mode) for clock frequencies of up to 100 kHz.
- PLL0 and PLL1 allow CPU operation up to the maximum CPU rate without the need for a high-frequency external clock. PLL0 and PLL1 can run from the internal FRO 12 MHz output, the external oscillator, internal FRO 1 MHz output, or the 32.768 kHz RTC oscillator.
- Clock output function with divider to monitor internal clocks.
- Frequency measurement unit for measuring the frequency of any on-chip or off-chip clock signal.

NOTE

For external crystal oscillator and RTC oscillator, LPC55Sxx have capacitor bank feature. It means that the stabilizing capacitors can be unsoldered on both 32 K and 16 MHz XTAL. We also suggest users to keep the two stabilizing capacitors as **DNP/Do Not Populate** on PCB.

4.2 Crystal oscillator

In the crystal oscillator circuit, only the crystal (XTAL) and the capacitances, **CX1** and **CX2**, need to be connected externally on XTAL32M_P and XTAL32M_N pins, as shown in Figure 4. In bypass mode, an external clock (maximum frequency of up to 24 MHz) can also be connected to XTAL32M_P if XTAL32M_N is left open. External [0 – VH] square signal can be applied on the XTAL32M_P pin from 0 V to 850 mV.

 


Figure 4. Reference oscillator circuit

Table 7. Components of the oscillator circuit

Symbol	Description
XTAL	Quartz crystal/ceramic resonator
CX1	Stabilizing capacitor
CX2	Stabilizing capacitor

For best results, it is very critical to select a matching crystal for the on-chip oscillator. Load Capacitance (CL), Resistance Series (RS), and Drive Level (DL) are important parameters to consider while choosing the crystal. After selecting the proper crystal, the external load capacitor CX1 and CX2 values can also be generally determined by the following expression:

$$CX1 = CX2 = 2CL \square (CPad + CParasitic)$$

Where:

- CL: Crystal load capacitance
- CPad: Pad capacitance of the XTAL32M_P and XTAL32M_N pins (~3 pF)
- CParasitic: Parasitic or stray capacitance of external circuit.

Although $C_{\text{Parasitic}}$ can be ignored in general, the actual board layout and placement of external components influences the optimal values of external load capacitors. Therefore, it is recommended to fine tune the values of external load capacitors on actual hardware board to get the accurate clock frequency. For fine tuning, output the RTC Clock to one of the GPIOs and optimize the values of external load capacitors for minimum frequency deviation. The load capacitors are dependent on the specifications of the crystal and on the board capacitance. It is recommended to have the crystal manufacturer evaluate the crystal on the PCB.

4.2.1 Crystal Printed Circuit Board (PCB) design guidelines


- Connect the crystal and external load capacitors on the PCB as close as possible to the oscillator input and output pins of the chip.
- The length of traces in the oscillation circuit should be as short as possible and must not cross other signal lines.
- Ensure that the load capacitors CX1 and CX2, in case of third overtone crystal usage, have a common ground plane.
- Loops must be made as small as possible to minimize the noise coupled in through the PCB and to keep the parasitic as small as possible.
- Lay out the ground (GND) pattern under crystal unit.
- Do not lay out other signal lines under crystal unit for multi-layered PCB.

4.3 RTC oscillator

In the RTC oscillator circuit, only the 32.768 kHz crystal (XTAL) and the capacitances, **CX1** and **CX2**, need to be connected externally on XTAL32K_P and XTAL32K_N, as shown in Figure 5.

In bypass mode, an external clock (maximum frequency of up to 100 kHz) can also be connected to XTAL32K_P if XTAL32K_N is left open. External [0 – VH] square signal can be applied on the XTAL32K_P pin with 1.1 V +/-10%

 An external signal below 1.0 V or above 1.2 V cannot be applied.



For best results, it is very critical to select a matching crystal for the on-chip oscillator. Load Capacitance (CL), Resistance Series (RS), and Drive Level (DL) are important parameters to consider while choosing the crystal. After selecting the proper crystal, the external load capacitor CX1 and CX2 values can also be generally determined by the following expression:

$$C_{X1} = C_{X2} = 2C_L \square (C_{Pad} + C_{Parasitic})$$

Where:

- C_L : Crystal load capacitance
- C_{Pad} : Pad capacitance of the XTAL32K_P and XTAL32K_N pins (~3 pF)
- $C_{Parasitic}$: Parasitic or stray capacitance of external circuit

Although $C_{Parasitic}$ can be ignored in general, the actual board layout and placement of external components influences the optimal values of external load capacitors.

Therefore, it is recommended to fine tune the values of external load capacitors on actual hardware board to get the accurate clock frequency. For fine tuning, output the RTC Clock to one of the GPIOs and optimize the values of external load capacitors for minimum frequency deviation.

4.3.1 RTC PCB design guidelines


- Connect the crystal and external load capacitors on the PCB as close as possible to the oscillator input and output pins of the chip.
- The length of traces in the oscillation circuit should be as short as possible and must not cross other signal lines.
- Ensure that the load capacitors CX1, CX2, and CX3, in case of third overtone crystal usage, have a common ground plane.
- Loops must be made as small as possible to minimize the noise coupled in through the PCB and to keep the parasitics as small as possible.
- Lay out the GND pattern under crystal unit.
- Do not lay out other signal lines under crystal unit for multi-layered PCB.

4.4 Common suggestions for the PCB layout of oscillator circuit

The crystal oscillator is an analog circuit and must be designed carefully and according to the analog-board layout rules:

- It is recommended to send the PCB to the crystal manufacturer to determine the negative oscillation margin as well as the optimum regarding CXTAL and CEXTAL capacitors. The datasheet includes recommendations for the tank capacitors CXTAL and CEXTAL. These values together with the expected PCB, pin, etc. stray capacity values should be used as an initial point.
- The crystal or resonator oscillator is sensitive to stray capacitance and noise from other signals. It should be placed away from high-frequency devices and traces in order to avoid and reduce the capacitive coupling between the XTAL and EXTAL pins and their PCB traces.
- The main oscillation loop current is flowing between the crystal and the load capacitors. This signal path (Oscillator to CEXTAL to CXTAL to Oscillator) should be kept as short and symmetric tracing as possible. Hence, both the capacitor's ground connections should be direct always to the closer VSS pin using the cooper-pour ground plane and several vias to the ground internal layer in the PCB are mandatory.
- The EXTAL and XTAL pins should only be connected to required oscillator components and must not be connected to any other devices.

Figure 6 shows the recommended placement and routing for the oscillator layout.

 

5 Boot mode configurations

5.1 Boot mode selection

The internal ROM memory is used to store the boot code. After a reset, the Arm processor starts its code execution from this memory. The bootloader code is executed every time the part is powered-ON, is reset, or wakes up from a deep power-down while in a low power mode.

Depending on the values of the CMPA bits, ISP pin, and the image header type definition, the bootloader decides whether to boot from internal flash or run into ISP mode. See **Section 6.5 FFR region definitions** in *LPC55S6x/LPC55S2x/LPC552x User manual* (document [UM11126](#)).

The state of port pin, `PIO0_5`, at **Reset** determines the boot source of the part or if the handler is invoked. The LPC55S6x/LPC55S2x/LPC552x/55S1x will read status of the ISP pins to determine boot source, as shown in [Table 8](#).

Table 8. Boot mode and ISP download modes based on ISP pins

Boot mode	ISP0 (PIO0_5 pin)	Description
Passive boot	HIGH	The LPC55S6x/LPC55S2x/LPC552x will look for valid image in the internal flash, if no valid image is found, the LPC55S6x/LPC55S2x/LPC552x will enter ISP boot mode based on DEFAULT_ISP_MODE bits defined in Table 9.
ISP boot	LOW	One of the serial interfaces (UART0, I2C1, SPI3, HS_SPI, USB0, USB1) is used to download image from host into internal flash. The first valid probe message on USART, I2C, SPI or USB locks in that interface.

[Table 9](#) shows the ISP pin assignments and is the default pin assignment used by the ROM code that cannot be changed.

Table 9. ISP pin assignment

ISP pin	Port pin assignment
ISP0	PIO0_5
USART_ISP mode	

Table continues on the next page...

Table 9. ISP pin assignment (continued)

ISP pin	Port pin assignment
FC0_TXD	PIO0_30
FC0_RXD	PIO0_29
I2C_ISP mode	
FC1_SDA	PIO0_13
FC1_SCL	PIO0_14
SPI ISP mode	
FC3_SCK	PIO0_6
FC3_SSEL0	PIO0_4
FC3_MISO	PIO0_2
FC3_MOSI	PIO0_3
HS_SPI_SCK	PIO1_2
HS_SPI_MISO	PIO1_3
HS_SPI_MOSI	PIO0_26
USB0 ISP mode	
USB0_VBUS	PIO0_22
USB0_DP	Dedicated pin per package
USB0_DM	Dedicated pin per package
USB1 ISP mode	
USB1_VBUS	Dedicated pin per package
USB1_DP	Dedicated pin per package
USB1_DM	Dedicated pin per package

6 Debug and programming interface

This section describes a number of commonly-used debug connectors. Most of the Arm development tools uses one of these pin out's.

When developing your ARM circuit board, it is recommended to use a standard debug signal arrangement to make connection to debugger easier.

The JTAG functions TRST, TCK, TMS, TDI, and TDO, are selected on pins, **PIO0_2** to **PIO0_6**, by hardware when the part is in boundary scan mode.

NOTE

The JTAG functions CANNOT be used for debug mode.

The SWD/SWV pins are overlaid on top of the JTAG pins, as shown in [Table 10](#).

Table 10. JTAG and SWD signal description

JTAG mode	SWD mode	Description	MCU port	Recommendation
TRST	—	JTAG Test Reset	PIO0_2	Pull-Down
TCK	—	JTAG clock into the core	PIO0_3	Z
TMS	—	JTAG Test Mode Select	PIO0_4	Z
TDI	—	JTAG Test Data Input	PIO0_5	Pull-Down
TDO	—	JTAG Test Data Output	PIO0_6	Z
—	SWO	Serial Wire Debug Trace output	PIO0_8	Output, Z
—	SWCLK	Serial Wire Debug clock	PIO0_11	Input, Pull-Down
—	SWDIO	Serial Wire Debug I/O	PIO0_12	Input, Pull-Up
RESET	RESET	Reset MCU	Dedicate Pin	Pull-Up
GND	GND	Ground	Dedicate Pins	—

NOTE

External pull up/down resistors for the JTAG signals can be added in order to increase debugger connection robustness.

 


Figure 7. SWD connector connections

6.1 Debug connector pinouts

As the LPC55Sxx's JTAG only for BSDL scan, you can use an even smaller 0.05" 10-pin connector (Samtec FTSH-105) for debug. Similar to the 20-pin Cortex Debug D ETM connector, both JTAG and Serial-Wire debug protocols are supported in the 10-pin version.

NOTE

The JTAG functions TRST, TCK, TMS, TDI, and TDO, are selected on pins, `PIO0_2` to `PIO0_6`, by hardware when the part is in boundary scan mode. The JTAG functions cannot be used for debug mode.

 


Figure 8. SWD signal connections

7 Communication modules

7.1 CAN interface for CAN-FD module

LPC55S1x have CAN-FD interface, the physical layer characteristics for CAN are specified in ISO-11898-2. This standard specifies the use of cable comprising parallel wires with an impedance of nominally 120 Ω (95 Ω as minimum and 140 Ω as maximum). The use of shielded twisted pair cables is generally necessary for Electro Magnetic Compatibility (EMC) reasons, although ISO-11898-2 also allows for unshielded cable. A maximum line length of 40 meters is specified for CAN at a data rate of 1 Mb. However, at lower data rates, potentially much longer lines are possible. ISO-11898-2 specifies a line topology, with individual nodes connected using short stubs.

Though not exclusively intended for automotive applications, CAN protocol is designed to meet the specific requirements of a vehicle serial data bus: real-time processing, reliable operation in the EMI environment of a vehicle, cost-effectiveness, and required bandwidth. Each CAN station is connected physically to the CAN bus lines through a transceiver device. The transceiver is capable of driving the large current needed for the CAN bus and has current protection against defective CAN or defective stations. [Figure 9](#) shows a typical CAN system with an LPC55(S)0x / LPC55(S)1x microcontroller.

 


Figure 9. CAN physical transceiver circuit

The LPC55Sxx CAN-FD module is a full implementation of the CAN protocol specification, the CAN with Flexible Data rate (CAN FD) protocol and the CAN 2.0 version B protocol, which supports both standard and extended message frames and long payloads up to 64 bytes transferred at faster rates up to 8 Mbps. Like most others CAN physical transceivers, the CANH and CANL are available for the designer to terminate bus depending on the application. [Figure 9](#) and [Figure 10](#) show examples of the CAN node terminations.

 


Figure 10. CAN physical transceiver circuit

8 Analog

8.1 ADC impedance

[Figure 11](#) shows the ADC block diagram of LPC55Sxx.

 


Figure 11. ADC block diagram

The datasheet only shares the RADIN values, as shown in [Table 11](#).

Table 11. ADC input resistance

		Min.	Typical	Max.	Unit
R _i	Input resistance				
	Fast Input Channels				
	PIO0_16/PIO0_23	—	1	2	kΩ
	PIO0_11/PIO0_10	—	1	2	kΩ
	PIO0_12/PIO0_15	—	1	2	kΩ
	PIO1_0/PIO0_31	—	1	2	kΩ
	Standard Input Channels				
	PIO1_9/PIO1_8	—	1.4	3.6	kΩ

9 Recommendations

9.1 Pin descriptions

9.1.1 Pin's pull-up/down and open-drain

All pins have all pull-ups, pull-downs, and inputs turned off at reset except `PIO0_2`, `PIO0_5`, `PIO0_11`, `PIO0_12`, `PIO0_13`, and `PIO0_14` pins. This prevents power loss through pins prior to software configuration. Due to special pin functions, some pins have a different reset configuration. `PIO0_5` and `PIO0_12` pins have internal pull-up enabled by default, and `PIO0_2` and `PIO0_11` have internal pull-down enabled by default. `PIO0_13` and `PIO0_14` are true open drain pins.

9.1.2 ADC pins

Some functions, such as ADC or comparator inputs, are available only on specific pins when digital functions are disabled on those pins. By default, the GPIO function is selected except on pins `PIO0_11` and `PIO0_12`, which are the serial wire debug pins. This allows debug to operate through reset.

9.1.3 Wakeup pins

The external reset pin or three wake-up pins can trigger a wake-up from deep power-down mode. For the wake-up pins, do not assign any function to this pin if it will be used as a wake-up input when using deep power-down mode. If not in deep power-down mode, a function can be assigned to this pin. If the pin is used for wake-up, it should be pulled HIGH externally before entering deep power-down mode. A LOW-going pulse as short as 50 ns causes the chip to exit deep power-down mode wakes up the part.

9.1.4 JTAG function pins

NOTE

The JTAG functions, TRST, TCK, TMS, TDI, and TDO, are selected on pins, `PIO0_2` to `PIO0_6`, by hardware when the part is in boundary scan mode. The JTAG functions cannot be used for debug mode.

9.2 Termination of unused pins

Table 12 shows how to terminate pins that are not used in the application. In many cases, unused pins should be connected externally or configured correctly by software to minimize the overall power consumption of the part.

Unused pins with GPIO function should be configured as outputs set to **LOW** with their internal pull-up disabled. To configure a GPIO pin as output and drive it LOW, select the GPIO function in the **IOCON** register, select output in the GPIO **DIR** register, and write a **0** to the GPIO PORT register for that pin. Disable the pull-up in the pin's **IOCON** register.

In addition, it is recommended to configure all GPIO pins that are not bonded out on smaller packages as outputs driven LOW with their internal pull-up disabled.

Table 12. Termination of unused pins

Pin	Default state	Recommended termination of unused pins
RESET	Input, pull-up	Can be left unconnected if the application does not use it.
All PION _m (not open-drain)	Input, pull-up	Can be left unconnected if driven LOW and configured as GPIO output with pull-up or pull-down disabled by software.
PION _m (I2C open-drain)	Inactive No pull-up or down	Can be left unconnected if driven LOW and configured as GPIO output by software.
XTAL32K_P	—	Connect to ground. When grounded, the RTC oscillator is disabled.
XTAL32K_N	—	Can be left unconnected.
VREFP	—	Tie to VBAT_DCDC

Table continues on the next page...

Table 12. Termination of unused pins (continued)

Pin	Default state	Recommended termination of unused pins
VREFN	—	Tie to VSS
VDDA	—	Tie to VBAT_DCDC
VSSA	—	Tie to VSS
USBn_DP	F	Can be left unconnected.
USBn_DM	F	Can be left unconnected.
USBn_3V3	F	Tied to VBAT_DCDC.
USB1_VBUS	F	Tied to VBAT_DCDC.
USBn_VSS	F	Tied to VSS.


9.3 PCB

For technical reasons, it is best to use a multilayer PCB with a separate layer dedicated to ground (VSS) and another dedicated to the VDD supply. This provides good decoupling and a good shielding effect. For many applications, economic reasons prohibit the use of this type of board. In this case, the major requirement is to ensure a good structure for ground and for the power supply.

9.4 General board layout guidelines

 9.4.1 Traces recommendations

A right angle in a trace can cause more radiation. The capacitance increases in the region of the corner and the characteristic impedance changes. This impedance change causes reflections. Avoid right-angle bends in a trace and try to route them with at least two 45° corners. To minimize any impedance change, the best routing would be a round bend, as shown in [Figure 12](#).



To minimize crosstalk, not only between two signals on one layer but also between adjacent layers, route them 90° to each other. Complex boards need to use vias while routing; you have to be careful when using them. These add additional capacitance and inductance, and reflections occur due to the change in the characteristic impedance. Vias also increase the trace length. While using differential signals, use vias in both traces or compensate the delay in the other trace.

9.4.2 Grounding

Grounding techniques apply to both multi-layer and single-layer PCBs. The objective of grounding techniques is to minimize the ground impedance and thus to reduce the potential of the ground loop from circuit back to the supply.

- Route high-speed signals above a solid and unbroken ground plane.
- Do not split the ground plane into separate planes for analog, digital, and power pins. A single and continuous ground plane is recommended.
- There should be no floating metal/shape of any kind near any area close to the microcontroller pins. Fill copper in the unused area of signal planes and connect these coppers to the ground plane through vias.

 


Figure 13. Eliminating floating metal/shape

9.4.3 EMI/EMC and ESD considerations for layout

These considerations are important for all system and board designs. Though the theory behind this is well explained, each board and system experiences this in its own way. There are many PCB and component related variables involved.

This application note does not go into the electromagnetic theory or explain the whys of different techniques used to combat the effects, but it considers the effects and solutions most recommended as applied to CMOS circuits. EMI is radio frequency energy that interferes with the operation of an electronic device. This radio frequency energy can be produced by the device itself or by other devices nearby. Studying EMC for your system allows testing the ability of your system to operate successfully counteracting the effects of unplanned electromagnetic disturbances coming from the devices and systems around it. The electromagnetic noise or disturbances travels via two media: Conduction and Radiation.

 


Figure 14. Electromagnetic noise propagation

The design considerations narrow down to:

- The radiated & conducted EMI from the board should be lower than the allowed levels by the standards you are following.
- The ability of the board to operate successfully counteracting the radiated & conducted electromagnetic energy (EMC) from other systems around it.

The EMI sources for a system consists of several components such as PCB, connectors, cables and so on. The PCB plays a major role in radiating the high frequency noise. At higher frequencies and fast-switching currents and voltages, the PCB traces become effective antennas radiating electromagnetic energy; e.g., a large loop of signal and corresponding ground. The five main sources of radiation are: digital signals propagating on traces, current return loop areas, inadequate power supply filtering or decoupling, transmission line effects, and lack of power and ground planes. Fast switching clocks, external buses and PWM signals are used as control outputs and in switching power supplies. The power supply is another major contributor to EMI. RF signals can propagate from one section of the board to another building up EMI. Switching power supplies radiate the energy which can fail the EMI test. This is a huge subject and there are many books, articles and white papers detailing the theory behind it and the design criteria to combat its effects.

Every board or system is different as far as EMI/EMC and ESD issues are concerned, requiring its own solution.

However, the common guidelines to reduce an unwanted generation of electromagnetic energy are as shown below:

- Ensure that the power supply is rated for the application and optimized with decoupling capacitors.
- Provide adequate filter capacitors on the power supply source. The bulk/bypass and decoupling capacitors should have low equivalent series inductance (ESL).
- Create ground planes if there are spaces available on the routing layers. Connect these ground areas to the ground plane with vias.

- Keep the current loops as small as possible. Add as many decoupling capacitors as possible. Always apply current return rules to reduce loop areas.
- Keep high-speed signals away from other signals and especially away from input and output ports or connectors.

9.4.4 PCB layer stacking

To reach signal integrity and performance requirements, four-layer PCB is recommended for implementing Ethernet applications and systems. The following layer stack-ups are recommended for four, six, and eight-layer boards, although other options are possible.

 


Figure 15. Electromagnetic noise propagation

9.4.5 Injection current

All pins implement protection diodes that protect against Electro Static Discharge (ESD). In many cases, both digital and analog pins need to be connected to voltages that are higher than the operating voltage of the device pin.

The internal ESD diodes of the microcontroller are designed for short discharge pulses only, and these do not sustain a constant current over time. Therefore, the maximum continuous voltage that drops over them is specified in the DC electrical parameters and the maximum high input voltage should not be higher than $V_{DD} + 0.5\text{ V}$, and the current injection also should be limited as defined in the device data sheet. In other words, the voltage and current of an input signal must be within the electrical parameter allowed. The outcome of violating these specifications causes unexpected behavior, stuck operation or a major damage in the MCU.

10 References

1. *Hardware Design Guidelines for S32K1xx Microcontrollers* (document [AN5426](#))
2. *LPC55S1x User manual* (document [UM11295](#))
3. *LPC55S2x/LPC552x/LPC55S6x/LPC556x User manual* (document [UM11126](#))

How To Reach Us

Home Page:

nxp.com

Web Support:

nxp.com/support

Information in this document is provided solely to enable system and software implementers to use NXP products. There are no express or implied copyright licenses granted hereunder to design or fabricate any integrated circuits based on the information in this document. NXP reserves the right to make changes without further notice to any products herein.

NXP makes no warranty, representation, or guarantee regarding the suitability of its products for any particular purpose, nor does NXP assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters that may be provided in NXP data sheets and/or specifications can and do vary in different applications, and actual performance may vary over time. All operating parameters, including "typicals," must be validated for each customer application by customer's technical experts. NXP does not convey any license under its patent rights nor the rights of others. NXP sells products pursuant to standard terms and conditions of sale, which can be found at the following address: nxp.com/SalesTermsandConditions.

While NXP has implemented advanced security features, all products may be subject to unidentified vulnerabilities. Customers are responsible for the design and operation of their applications and products to reduce the effect of these vulnerabilities on customer's applications and products, and NXP accepts no liability for any vulnerability that is discovered. Customers should implement appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP, the NXP logo, NXP SECURE CONNECTIONS FOR A SMARTER WORLD, COOLFLUX, EMBRACE, GREENCHIP, HITAG, ICODE, JCOP, LIFE VIBES, MIFARE, MIFARE CLASSIC, MIFARE DESFire, MIFARE PLUS, MIFARE FLEX, MANTIS, MIFARE ULTRALIGHT, MIFARE4MOBILE, MIGLO, NTAG, ROADLINK, SMARTLX, SMARTMX, STARPLUG, TOPFET, TRENCHMOS, UCODE, Freescale, the Freescale logo, Altivec, CodeWarrior, ColdFire, ColdFire+, the Energy Efficient Solutions logo, Kinetis, Layerscape, MagniV, mobileGT, PEG, PowerQUICC, Processor Expert, QorIQ, QorIQ Qonverge, SafeAssure, the SafeAssure logo, StarCore, Symphony, VortiQa, Vybrid, Airfast, BeeKit, BeeStack, CoreNet, Flexis, MXC, Platform in a Package, QUICC Engine, Tower, TurboLink, EdgeScale, EdgeLock, eIQ, and Immersive3D are trademarks of NXP B.V. All other product or service names are the property of their respective owners. AMBA, Arm, Arm7, Arm7TDMI, Arm9, Arm11, Artisan, big.LITTLE, Cordio, CoreLink, CoreSight, Cortex, DesignStart, DynamIQ, Jazelle, Keil, Mali, Mbed, Mbed Enabled, NEON, POP, RealView, SecurCore, Socrates, Thumb, TrustZone, ULINK, ULINK2, ULINK-ME, ULINK-PLUS, ULINKpro, µVision, Versatile are trademarks or registered trademarks of Arm Limited (or its subsidiaries) in the US and/or elsewhere. The related technology may be protected by any or all of patents, copyrights, designs and trade secrets. All rights reserved. Oracle and Java are registered trademarks of Oracle and/or its affiliates. The Power Architecture and Power.org word marks and the Power and Power.org logos and related marks are trademarks and service marks licensed by Power.org.

© NXP B.V. 2020.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: salesaddresses@nxp.com

Date of release: 10/2020

Document identifier: AN13033

arm