

**Circuits
from the Lab®**
Reference Designs

Circuits from the Lab® reference designs are engineered and tested for quick and easy system integration to help solve today's analog, mixed-signal, and RF design challenges. For more information and/or support, visit www.analog.com/CN0435.

Devices Connected/Referenced	
CN-0414	Quad-Channel Analog Input with Open-Wire Detection and HART Compatibility for PLC/DCS Applications
CN-0418	Quad-Channel Analog Output and HART Compatibility for PLC/DCS Applications
CN-0416	RS-485 Transceiver
ADALM-UARTJTAG	JTAG and Serial Programmer
EVAL-ADICUP3029	Ultra Low Power, Arduino Form Factor Development Platform for IoT Applications

Analog I/O System with HART and Modbus Connectivity for PLC/DCS Applications

EVALUATION AND DESIGN SUPPORT

Circuit Evaluation Boards

[CN-0414 Circuit Evaluation Board \(EVAL-CN0414-ARDZ\)](#)

[CN-0418 Circuit Evaluation Board \(EVAL-CN0418-ARDZ\)](#)

[CN-0416 Circuit Evaluation Board \(EVAL-CN0416-ARDZ\)](#)

[ADALM-UARTJTAG Board](#)

[Arduino Form-Factor Development Platform \(EVAL-ADICUP3029\)](#)

Design and Integration Files

[PLC/DCS Wiki User Guide](#)

[Schematics, Layout Files, Bill of Materials, Software](#)

CIRCUIT FUNCTION AND BENEFITS

Programmable logic controllers (PLC) and distributed control systems (DCS) are used for monitoring and controlling both smart (HART capable) and analog-only field instruments found in industrial automation applications.

The circuit shown in Figure 1 represents a simple DCS system composed of a host and a single node with two 4-channel isolated analog input boards and two 4-channel isolated analog output boards controlled locally by an Arduino form factor baseboard. The RS-485 transceiver interfaces with a PC or other host, from which the user can exchange data with the node using the Modbus protocol.

Analog input data is read locally and made available over a serial interface utilizing the industry-standard Modbus protocol, ensuring data integrity and compatibility with a range of software applications and libraries. Similarly, analog outputs are set by writing to Modbus registers, which are then translated to analog voltage or current signals.

Each node can have any combination of up to four analog input and output boards. Multinode systems of up to 16 nodes, as shown in Figure 2, can be designed using the hardware and software infrastructure provided. The circuit supports point-to-point HART communication, which can be extended to a multidrop HART network, consisting of several HART devices on the same channel.

Both analog inputs and analog outputs are galvanically isolated per board (groups of four), and analog inputs feature open-wire detection, simplifying fault detection and diagnosis. These features enhance robustness when working in a harsh industrial automation setting.

Rev. 0

Circuits from the Lab® reference designs from Analog Devices have been designed and built by Analog Devices engineers. Standard engineering practices have been employed in the design and construction of each circuit, and their function and performance have been tested and verified in a lab environment at room temperature. However, you are solely responsible for testing the circuit and determining its suitability and applicability for your use and application. Accordingly, in no event shall Analog Devices be liable for direct, indirect, special, incidental, consequential or punitive damages due to any cause whatsoever connected to the use of any Circuits from the Lab circuits. (Continued on last page)

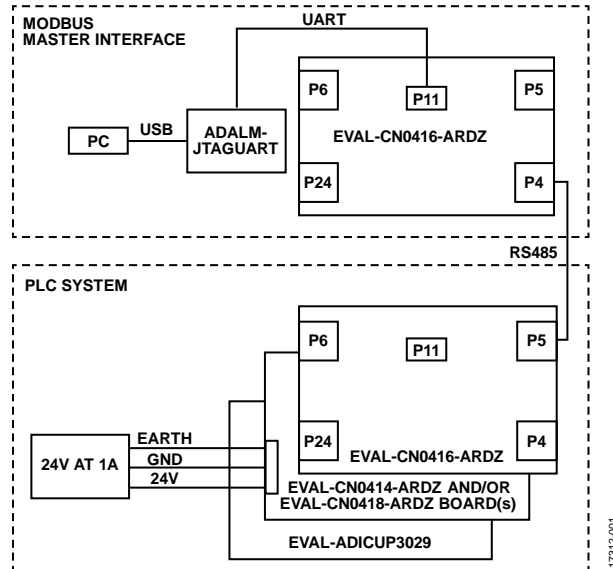


Figure 1. PLC (or Single-Node DCS) Modbus System Functional Block Diagram

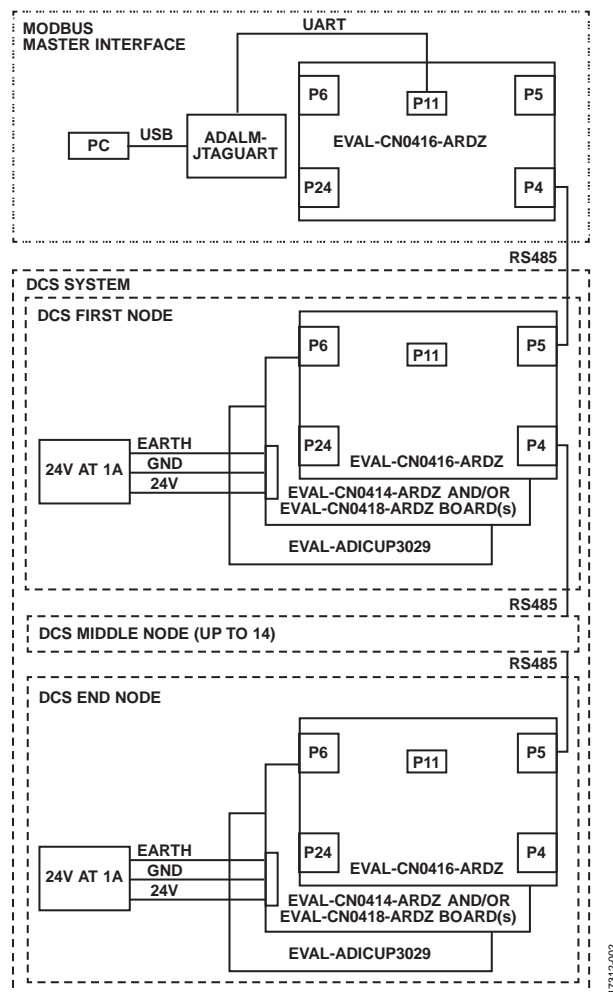


Figure 2. Multinode DCS Modbus System Functional Block Diagram

CIRCUIT DESCRIPTION

The application focuses on demonstrating the development of a PLC/DCS system controlled by a Modbus master and exemplifies how the latest features of key components are used. A single node system is often referred to as a PLC, whereas a larger system is often referred to as a DCS.

Each node can control up to 16 analog field devices, sensors or actuators, either HART-compatible or analog-only, and systems can be extended to include as many as 16 individual nodes. The system can also be used for general-purpose precision analog data acquisition applications such as instrumentation, analog datalogging, or test and measurement.

PLC/DCS Topologies

Several connection topologies are supported. In a single-node (PLC, or single-node DCS) system, the host computer can be connected directly to the USB serial port on the [EVAL-ADICUP3029](#) platform board via a micro-USB cable, which is appropriate for laboratory test and measurement applications where the distance between the host and node is less than 2 m.

In this point-to-point topology, groups of four analog inputs and outputs per board are still isolated from the host computer. Though generally not associated with lab equipment, the Modbus protocol provides a convenient and standard method for communicating with the node. HART connectivity allows configuration of smart sensors and actuators.

As the distance between the host and nodes increases beyond 2 m, signal integrity, noise pickup, and electrical faults become a greater concern. The [EVAL-CN0416-ARDZ](#) provides robust RS-485 connectivity to the host in these situations. In a single-node, point-to-point system, either full or half-duplex communication is supported, over distances up to 1 km, depending on baud rate.

For multinode (better described as a DCS), the [EVAL-CN0416-ARDZ](#) includes daisy-chain ports, switchable half/full-duplex operation, and switchable termination, allowing systems of between 2 and 16 nodes to be assembled.

Because Modbus is used as a serial communication protocol to transmit information between devices over a serial link, a simple, reliable, and robust system can be obtained regardless of the scale. The PLC/DCS application hardware stack is composed of three different reference designs.

Analog Input Board

The [CN-0414](#) shown in Figure 3 is designed to measure four fully differential or eight single-ended voltage and four current signals. The heart of the circuit is an [AD4111](#) low power, low noise 24-bit, Σ - Δ analog-to-digital converter (ADC) with integrated ± 10 V and 20 mA analog front ends.

The voltage inputs support an input range of up to ± 10 V. The [AD4111](#) incorporates a unique feature that enables open wire detection on ± 10 V voltage inputs while operating on a 5 V or

3.3 V single power supply, while previous solutions would typically require a supply greater than ± 10 V.

The current inputs support input ranges of 0 mA to 24 mA. The input impedance of the circuit is 250 Ω (60 Ω internal to the [AD4111](#)), with all inputs referenced to isolated ground. The 250 Ω input impedance on the current inputs is necessary to make the [AD5700-1](#) HART-compliant modem to work in conjunction with the [AD4111](#).

The analog front end of the circuit, the [AD4111](#) and the [AD5700-1](#) are isolated from the processing side through [ADuM5411](#) and [ADuM3151](#), to offer significant space savings over discrete transformer-based solutions.

The [CN-0414](#) board is powered by a 9.5 V to 36 V dc power supply that is typical of industrial automation systems, and therefore makes it easy to retrofit into your system.



Figure 3. Analog Input Board

Analog Output Board

The [CN-0418](#) shown in Figure 4 is a quad channel voltage and current output board based on the [AD5755-1](#) DAC with dynamic power control.

This circuit provides 4 mA to 20 mA current outputs, as well as unipolar or bipolar voltage outputs (± 10 V). The board also includes the [AD5700-1](#) HART modem, to give a complete analog output solution with HART connectivity. External transient protection circuitry is also included, which is important for applications located in harsh industrial environments.

The current and voltage outputs are available on separate pins, but only one is active at a time, thus allowing both output pins to be tied together and connected to a single terminal. Analog outputs are short-circuited, and open-circuit protected.

The [AD5755-1](#) contains integrated dynamic power control using a dc-to-dc boost converter circuit, allowing reduced power consumption in the current output mode.

The [AD5755-1](#) has four CHART pins, corresponding to each of the four output channels. The HART signal can be coupled into

these pins and appears on the corresponding output if that output is enabled.

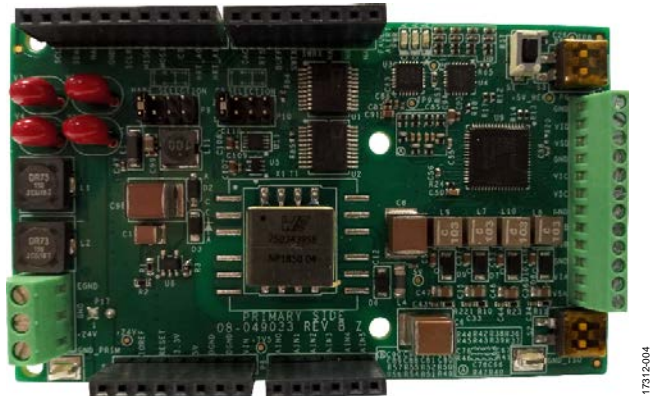


Figure 4. Analog Output Board

RS-485 Transceiver Board

The CN-0416 shown in Figure 5 is an isolated and non-isolated RS-485 transceiver board, which allows easy implementation of data transmission between multiple systems or nodes, especially over long distances.

The circuit uses the ADM2682E RS-485 transceiver for isolated communications and the LTC2865 for non-isolated RS-485 communications. Both can be configured to either full duplex or half-duplex operation and with open or terminated transmission lines.

The circuit has on-board RJ-45 jacks, which allow the use of common CAT5 Ethernet cables for fast physical wiring of nodes. The termination resistance is set by default to the CAT5 cable characteristic impedance of 100 Ω but can be configured to support the standard RS-485 cable impedance of 120 Ω.

The ADM2682E is capable of a data rate up to 16 Mbps and has true fail-safe receiver inputs with adjusted differential voltage threshold. It provides 5 kV signal isolation using the iCoupler data channel and 5 kV power isolation using the isoPower integrated dc-to-dc converter.

The LTC2865 is capable of a data rate up to 20 Mbps and has full fail-safe receiver inputs. An internal window comparator determines the fail-safe condition without the need to adjust the differential input voltage thresholds.



Figure 5. RS-485 Transceiver Board

HART-Compatible Field Devices Wiring

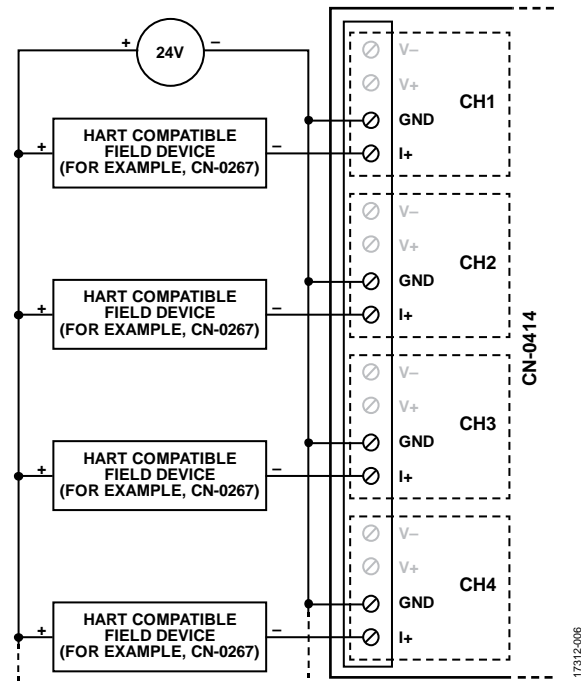


Figure 6. HART-Compatible Field Devices Wiring

HART Networks

HART devices can operate in one of two network configurations, point-to-point or multidrop.

In point-to-point mode, the 4 mA to 20 mA signal is used to communicate one process variable, while additional process variables, configuration parameters, and other device data are transferred digitally using the HART protocol. The 4 mA to 20 mA analog signal is not affected by the HART signal and can be used for control. The HART protocol gives access to secondary variables and other data that can be used for operations, commissioning, maintenance, and diagnostic purposes.

Modbus Protocol

The software running on the EVAL-ADICUP3029 implements the Modbus protocol, a de-facto and open industrial communication standard. Modbus provides a robust means of exchanging data with individual nodes, with CRC error detection ensuring data integrity. Being an open standard, there are numerous open-source and commercial Modbus software libraries available, targeting various platforms (such as Windows®, Linux®, embedded platforms, among others).

The software also provides a simple command-line interface (CLI) mode, allowing systems to be verified manually from a serial terminal, without requiring any additional software on the host.

Getting Started

The following are the basic steps for setup:

1. Plug the USB cable from [EVAL-ADICUP3029](#) to the PC and flash the firmware onto the every used board.
2. Configure the hardware. Follow the [Distributed Control System \(DCS\) Demo Wiki User Guide](#). Ensure that the jumpers and switches are set on each board correctly. Optionally, for analog input boards, connect sensors or signal sources, respectively, for analog output boards connect actuators or multimeters.
3. For each node, stack the platform and shield boards on top of each other in the following order:
 - [EVAL-CN0416-ARDZ](#) (top)
 - [EVAL-CN0414-ARDZ](#) or [EVAL-CN0418-ARDZ](#) (optional)
 - [EVAL-CN0414-ARDZ](#) or [EVAL-CN0418-ARDZ](#) (optional)
 - [EVAL-CN0414-ARDZ](#) or [EVAL-CN0418-ARDZ](#) (optional)
 - [EVAL-CN0414-ARDZ](#) or [EVAL-CN0418-ARDZ](#) (optional)
 - [EVAL-ADICUP3029](#) (bottom)
4. Connect RJ-45 cables between nodes and the RS-485 adapter (which may be the [ADALM-UARTJTAG](#) and [EVAL-CN0416-ARDZ](#)).
5. Connect the RS-485 adapter to the host.
6. Press the 3029_Reset button or power cycle the system.

For complete details, see the [Distributed Control System \(DCS\) Demo Wiki User Guide](#).

Functional Block Diagrams

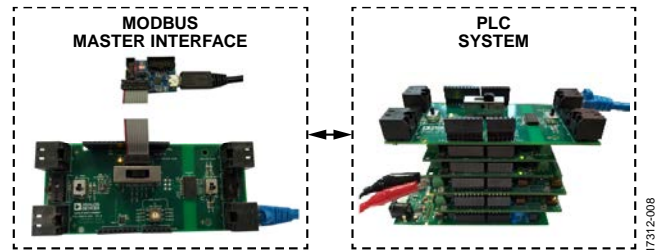


Figure 8. Single-Node PLC Analog I/O System

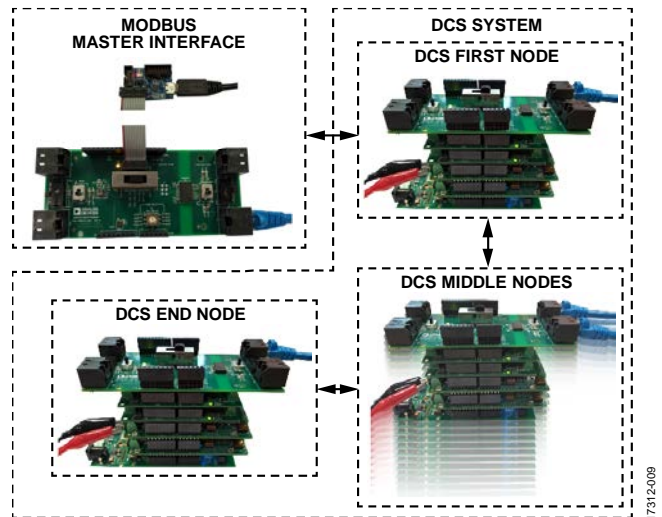


Figure 9. DCS Analog I/O System

LEARN MORE

CN-0414 Design Support Package:

www.analog.com/CN0414-DesignSupport

CN-0418 Design Support Package:

www.analog.com/CN0418-DesignSupport

CN-0416 Design Support Package:

www.analog.com/CN0416-DesignSupport

ADALM-UARTJATG Design Support Package:

www.analog.com/ADALM-UARTJATG-DesignSupport

[EVAL-ADICUP3029 User Guide](#)

[ADICUP3029 GitHub Repository](#)

Data Sheets and Evaluation Boards

[CN-0414 Circuit Evaluation Board \(EVAL-CN0414-ARDZ\)](#)

[CN-0418 Circuit Evaluation Board \(EVAL-CN0414-ARDZ\)](#)

[CN-0416 Circuit Evaluation Board \(EVAL-CN0414-ARDZ\)](#)

[ADALM-UARTJATG Circuit Evaluation Board
\(ADALM-UARTJATG\)](#)

[ADICUP3029 Development Platform \(EVAL-ADICUP3029\)](#)

REVISION HISTORY

7/2019—Revision 0: Initial Version

(Continued from first page) Circuits from the Lab reference designs are intended only for use with Analog Devices products and are the intellectual property of Analog Devices or its licensors. While you may use the Circuits from the Lab reference designs in the design of your product, no other license is granted by implication or otherwise under any patents or other intellectual property by application or use of the Circuits from the Lab reference designs. Information furnished by Analog Devices is believed to be accurate and reliable. However, Circuits from the Lab reference designs are supplied "as is" and without warranties of any kind, express, implied, or statutory including, but not limited to, any implied warranty of merchantability, noninfringement or fitness for a particular purpose and no responsibility is assumed by Analog Devices for their use, nor for any infringements of patents or other rights of third parties that may result from their use. Analog Devices reserves the right to change any Circuits from the Lab reference designs at any time without notice but is under no obligation to do so.

©2019 Analog Devices, Inc. All rights reserved. Trademarks and registered trademarks are the property of their respective owners.
CN17312-0-7/19(0)

