

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

2: Resistor Circuits

2: Resistor Circuits


- **Kirchoff's Voltage Law**

- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Kirchoff's Voltage Law

The five nodes are labelled A , B , C , D , E where E is the reference node.

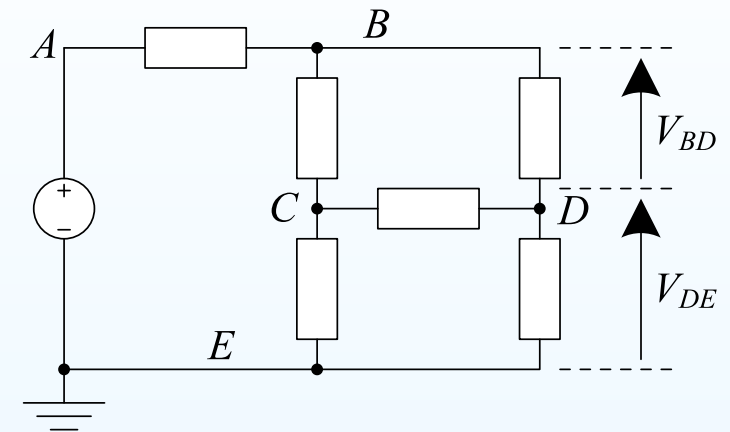Each component that links a pair of nodes is called a *branch* of the network.



2: Resistor Circuits

● Kirchhoff's Voltage Law


- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Kirchoff's Voltage Law

The five nodes are labelled A , B , C , D , E where E is the reference node.

Each component that links a pair of nodes is called a *branch* of the network.

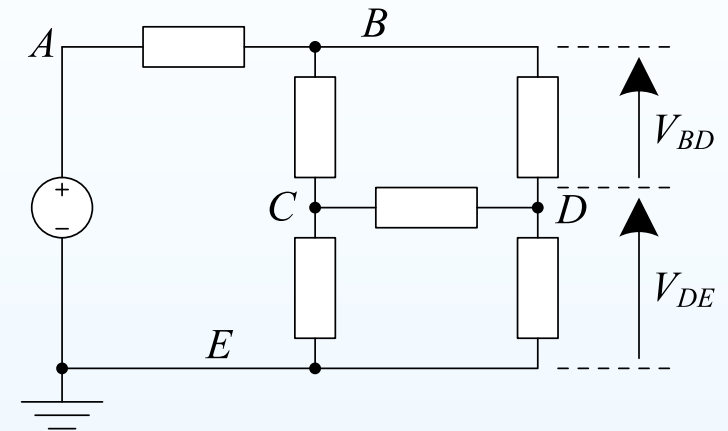Kirchoff's Voltage Law (KVL) is a consequence of the fact that the work done in moving a charge from one node to another does not depend on the route you take; in particular the work done in going from one node back to the same node by any route is zero.



2: Resistor Circuits


- **Kirchoff's Voltage Law**

- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Kirchoff's Voltage Law

The five nodes are labelled A , B , C , D , E where E is the reference node.

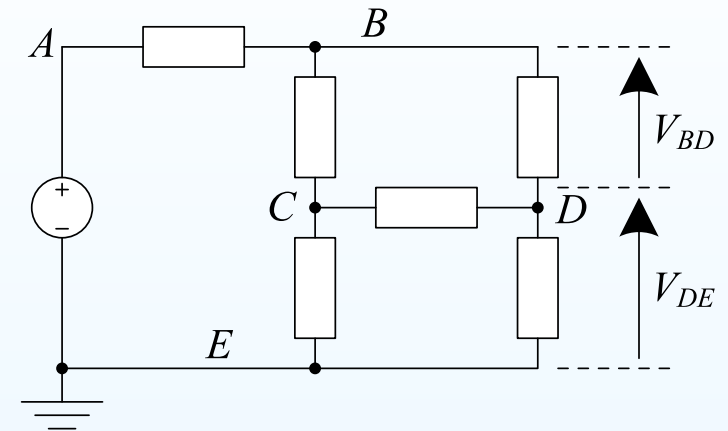Each component that links a pair of nodes is called a *branch* of the network.



Kirchoff's Voltage Law (KVL) is a consequence of the fact that the work done in moving a charge from one node to another does not depend on the route you take; in particular the work done in going from one node back to the same node by any route is zero.

KVL: the sum of the voltage changes around any closed loop is zero.

2: Resistor Circuits


- **Kirchoff's Voltage Law**

- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Kirchoff's Voltage Law

The five nodes are labelled A , B , C , D , E where E is the reference node.

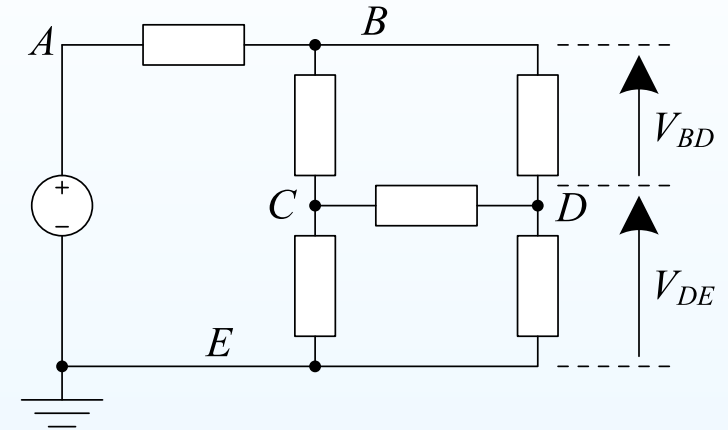Each component that links a pair of nodes is called a *branch* of the network.



Kirchoff's Voltage Law (KVL) is a consequence of the fact that the work done in moving a charge from one node to another does not depend on the route you take; in particular the work done in going from one node back to the same node by any route is zero.

KVL: the sum of the voltage changes around any closed loop is zero.

Example: $V_{DE} + V_{BD} + V_{AB} + V_{EA} = 0$

2: Resistor Circuits


● Kirchhoff's Voltage Law

- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Kirchoff's Voltage Law

The five nodes are labelled A , B , C , D , E where E is the reference node.

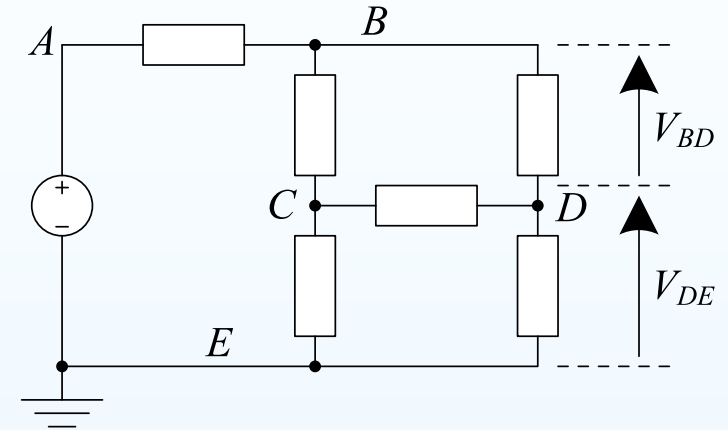Each component that links a pair of nodes is called a *branch* of the network.



Kirchoff's Voltage Law (KVL) is a consequence of the fact that the work done in moving a charge from one node to another does not depend on the route you take; in particular the work done in going from one node back to the same node by any route is zero.

KVL: the sum of the voltage changes around any closed loop is zero.

Example: $V_{DE} + V_{BD} + V_{AB} + V_{EA} = 0$

Equivalent formulation:

$$V_{XY} = V_{XE} - V_{YE} = V_X - V_Y \text{ for any nodes } X \text{ and } Y.$$

Kirchoff's Current Law

2: Resistor Circuits

- Kirchoff's Voltage Law
- **Kirchoff's Current Law**
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance:
Series
- Equivalent Resistance:
Parallel
- Equivalent Resistance:
Parallel Formulae
- Simplifying Resistor
Networks
- Non-ideal Voltage Source
- Summary

Wherever charges are free to move around, they will move to ensure charge neutrality everywhere at all times.

2: Resistor Circuits

- Kirchoff's Voltage Law
- **Kirchoff's Current Law**
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance:
Series
- Equivalent Resistance:
Parallel
- Equivalent Resistance:
Parallel Formulae
- Simplifying Resistor
Networks
- Non-ideal Voltage Source
- Summary

Kirchoff's Current Law

Wherever charges are free to move around, they will move to ensure charge neutrality everywhere at all times.

A consequence is **Kirchoff's Current Law (KCL)** which says that the current going into any closed region of a circuit must equal the current coming out.

2: Resistor Circuits

- Kirchoff's Voltage Law
- **Kirchoff's Current Law**
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Kirchoff's Current Law

Wherever charges are free to move around, they will move to ensure charge neutrality everywhere at all times.

A consequence is **Kirchoff's Current Law (KCL)** which says that the current going into any closed region of a circuit must equal the current coming out.

KCL: The currents flowing out of any closed region of a circuit sum to zero.

Kirchoff's Current Law

2: Resistor Circuits


- Kirchoff's Voltage Law
- **Kirchoff's Current Law**
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Wherever charges are free to move around, they will move to ensure charge neutrality everywhere at all times.

A consequence is **Kirchoff's Current Law (KCL)** which says that the current going into any closed region of a circuit must equal the current coming out.

KCL: The currents flowing out of any closed region of a circuit sum to zero.

Green: $I_1 = I_7$

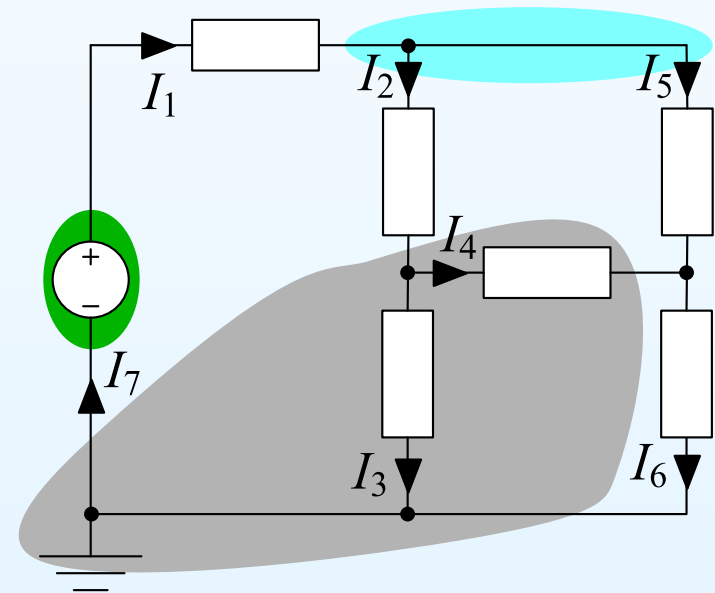

Kirchoff's Current Law

2: Resistor Circuits

- Kirchoff's Voltage Law
- **Kirchoff's Current Law**
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary


Wherever charges are free to move around, they will move to ensure charge neutrality everywhere at all times.

A consequence is **Kirchoff's Current Law (KCL)** which says that the current going into any closed region of a circuit must equal the current coming out.

KCL: The currents flowing out of any closed region of a circuit sum to zero.

Green: $I_1 = I_7$

Blue: $-I_1 + I_2 + I_5 = 0$

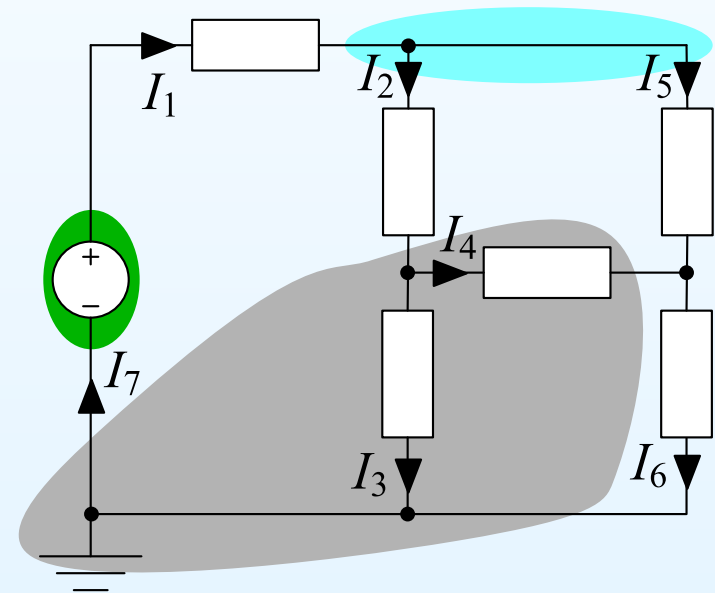

2: Resistor Circuits

- Kirchoff's Voltage Law
- **Kirchoff's Current Law**
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Kirchoff's Current Law

Wherever charges are free to move around, they will move to ensure charge neutrality everywhere at all times.


A consequence is **Kirchoff's Current Law (KCL)** which says that the current going into any closed region of a circuit must equal the current coming out.

KCL: The currents flowing out of any closed region of a circuit sum to zero.

Green: $I_1 = I_7$

Blue: $-I_1 + I_2 + I_5 = 0$

Gray: $-I_2 + I_4 - I_6 + I_7 = 0$

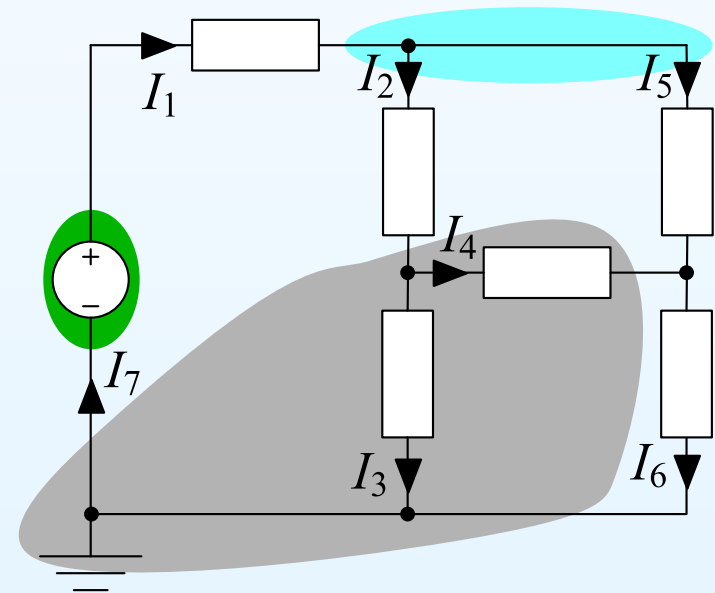

KCL Example

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- **KCL Example**
- Series and Parallel
- Dividers
- Equivalent Resistance:
Series
- Equivalent Resistance:
Parallel
- Equivalent Resistance:
Parallel Formulae
- Simplifying Resistor
Networks
- Non-ideal Voltage Source
- Summary

The currents and voltages in any linear circuit can be determined by using KCL, KVL and Ohm's law.

2: Resistor Circuits


- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

KCL Example

The currents and voltages in any linear circuit can be determined by using KCL, KVL and Ohm's law.

Sometimes KCL allows you to determine currents very easily without having to solve any simultaneous equations:

How do we calculate I ?

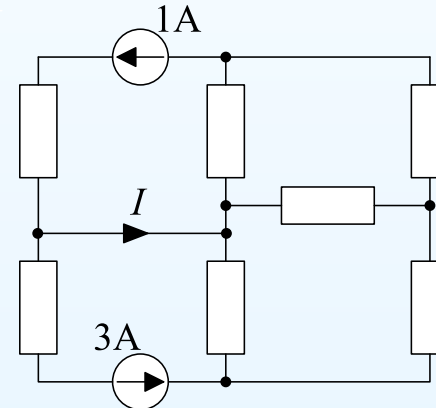

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary


KCL Example

The currents and voltages in any linear circuit can be determined by using KCL, KVL and Ohm's law.

Sometimes KCL allows you to determine currents very easily without having to solve any simultaneous equations:

How do we calculate I ?

$$\text{KCL: } -1 + I + 3 = 0$$

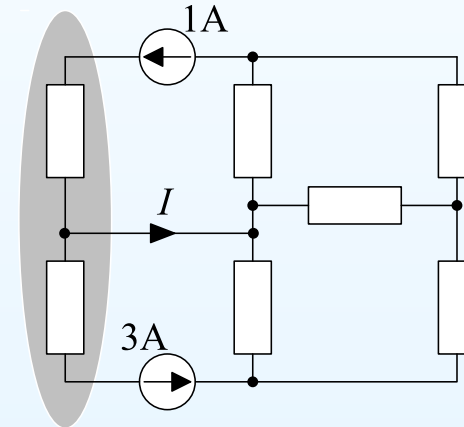

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary


KCL Example

The currents and voltages in any linear circuit can be determined by using KCL, KVL and Ohm's law.

Sometimes KCL allows you to determine currents very easily without having to solve any simultaneous equations:

How do we calculate I ?
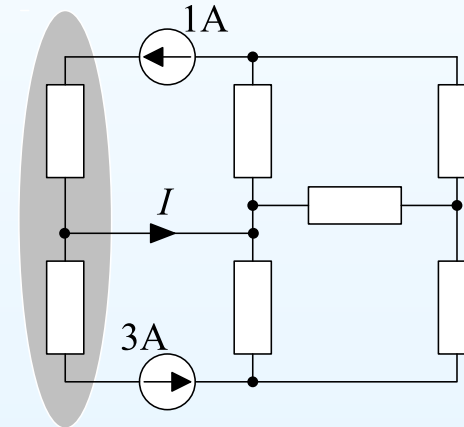
$$\text{KCL: } -1 + I + 3 = 0$$
$$\Rightarrow I = -2 \text{ A}$$



2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary


KCL Example

The currents and voltages in any linear circuit can be determined by using KCL, KVL and Ohm's law.

Sometimes KCL allows you to determine currents very easily without having to solve any simultaneous equations:

How do we calculate I ?
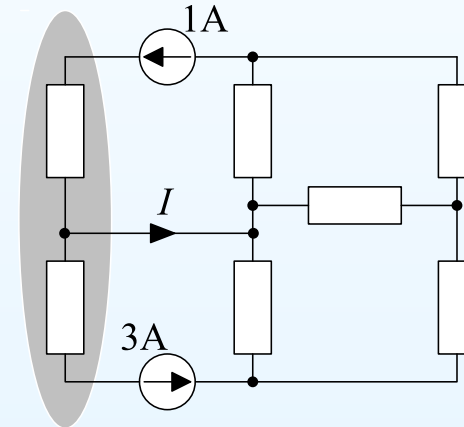
$$\text{KCL: } -1 + I + 3 = 0$$
$$\Rightarrow I = -2 \text{ A}$$




Note that here I ends up negative which means we chose the wrong arrow direction to label the circuit. **This does not matter.** You can choose the directions arbitrarily and let the algebra take care of reality.

Series and Parallel

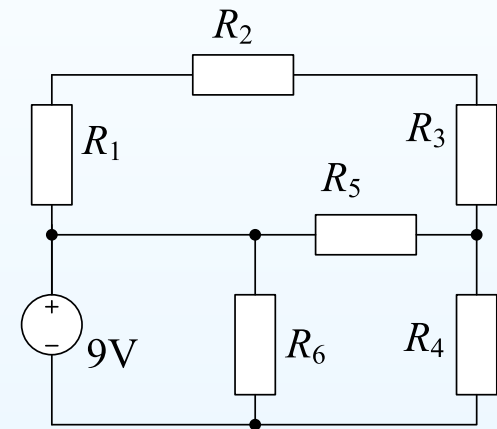2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Series: Components that are connected in a chain so that the same current flows through each one are said to be *in series*.




Series and Parallel

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Series: Components that are connected in a chain so that the same current flows through each one are said to be *in series*.

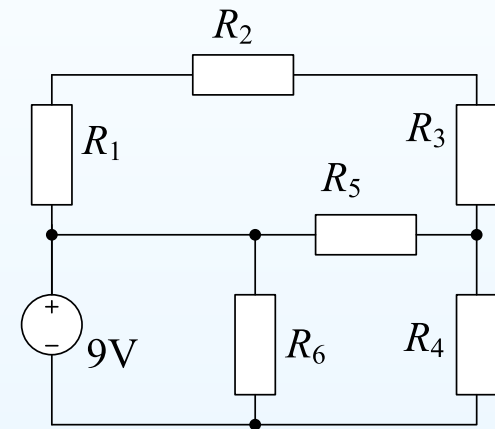R_1, R_2, R_3 are in series and the **same current** always flows through each.



Series and Parallel


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Series: Components that are connected in a chain so that the same current flows through each one are said to be *in series*.

R_1, R_2, R_3 are in series and the **same current** always flows through each.

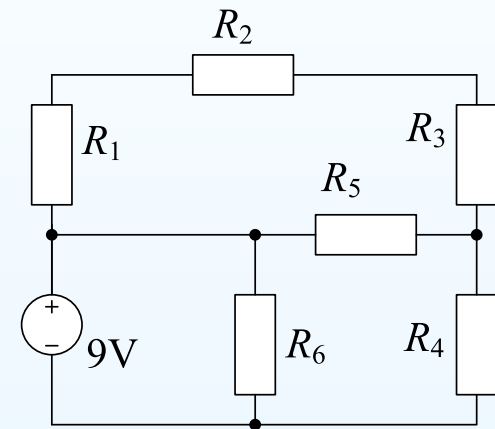Within the chain, each internal node connects to **only two** branches.



Series and Parallel

2: Resistor Circuits


- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Series: Components that are connected in a chain so that the same current flows through each one are said to be *in series*.

R_1, R_2, R_3 are in series and the **same current** always flows through each.

Within the chain, each internal node connects to **only two** branches.

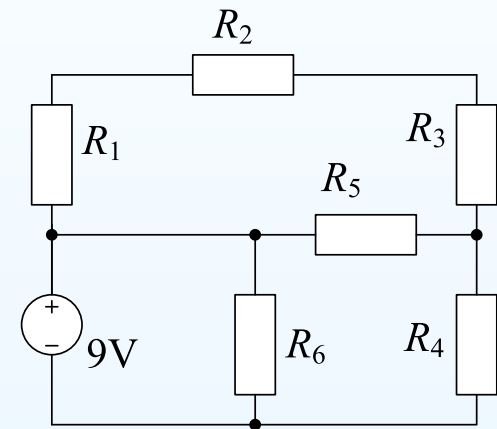R_3 and R_4 are **not** in series and do not necessarily have the same current.



Series and Parallel

2: Resistor Circuits


- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Series: Components that are connected in a chain so that the same current flows through each one are said to be *in series*.


R_1, R_2, R_3 are in series and the **same current** always flows through each.

Within the chain, each internal node connects to **only two** branches.

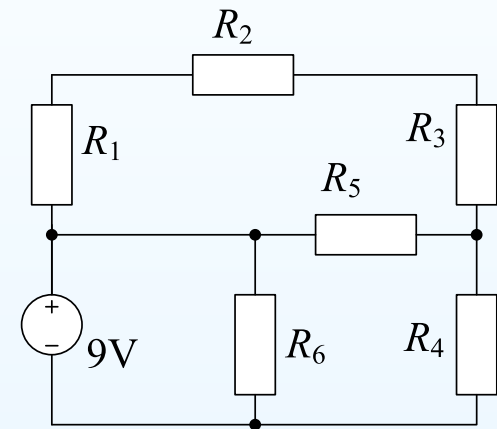R_3 and R_4 are **not** in series and do not necessarily have the same current.



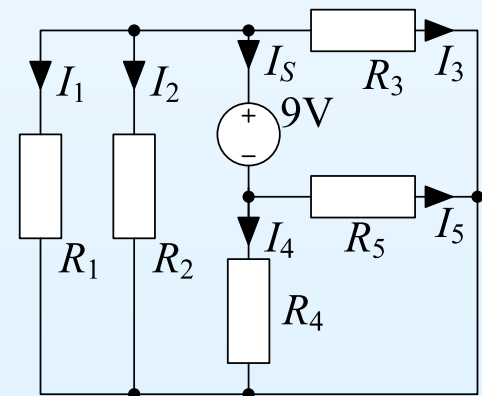Parallel: Components that are connected to the same pair of nodes are said to be *in parallel*.



Series and Parallel

2: Resistor Circuits


- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Series: Components that are connected in a chain so that the same current flows through each one are said to be *in series*.

R_1, R_2, R_3 are in series and the **same current** always flows through each.


Within the chain, each internal node connects to **only two** branches.

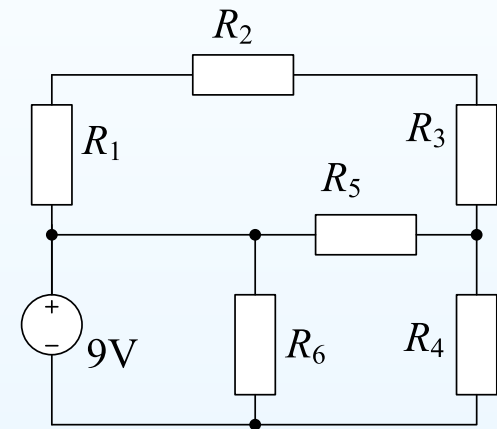R_3 and R_4 are **not** in series and do not necessarily have the same current.



Parallel: Components that are connected to the same pair of nodes are said to be *in parallel*.

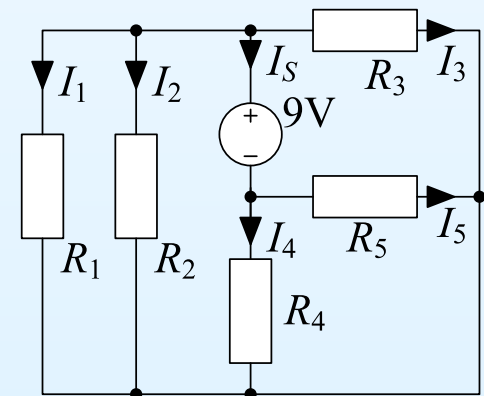R_1, R_2, R_3 are in parallel and the **same voltage** is across each resistor (even though R_3 is not close to the others).



Series and Parallel

2: Resistor Circuits


- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Series: Components that are connected in a chain so that the same current flows through each one are said to be *in series*.

R_1, R_2, R_3 are in series and the **same current** always flows through each.

Within the chain, each internal node connects to **only two** branches.

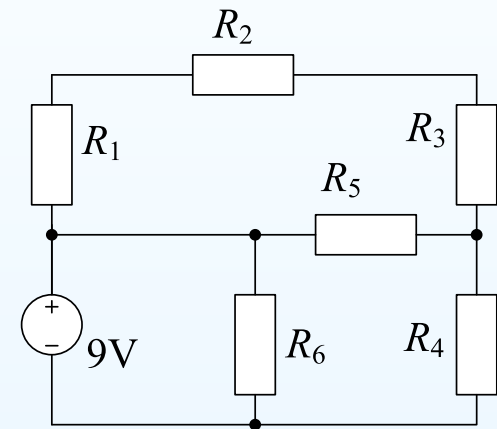
R_3 and R_4 are **not** in series and do not necessarily have the same current.



Parallel: Components that are connected to the same pair of nodes are said to be *in parallel*.

R_1, R_2, R_3 are in parallel and the **same voltage** is across each resistor (even though R_3 is not close to the others).

R_4 and R_5 are also in parallel.

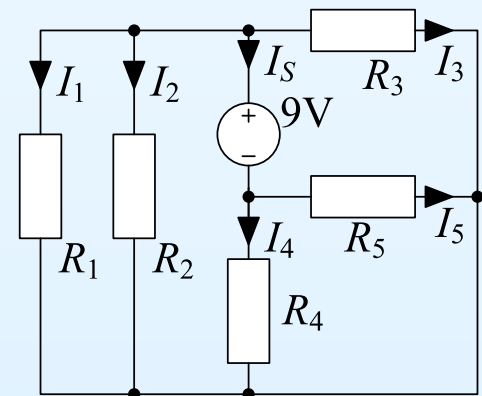


Series Resistors: Voltage Divider

2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

$$V_X = V_1 + V_2 + V_3$$

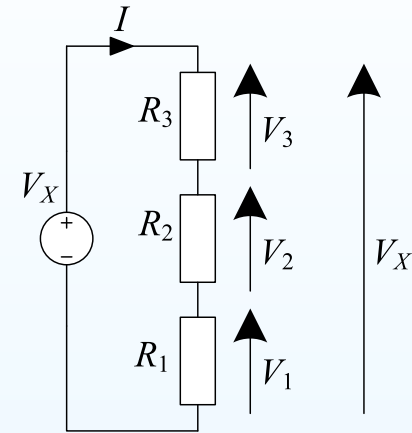


Series Resistors: Voltage Divider

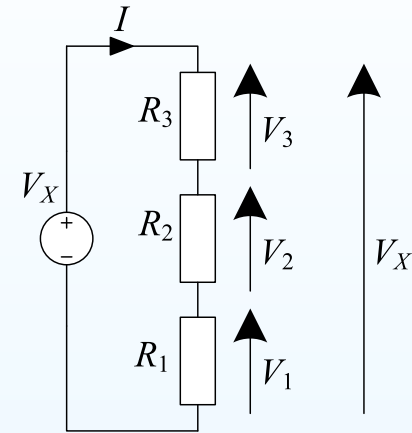2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

$$\begin{aligned}V_X &= V_1 + V_2 + V_3 \\ &= IR_1 + IR_2 + IR_3\end{aligned}$$




Series Resistors: Voltage Divider

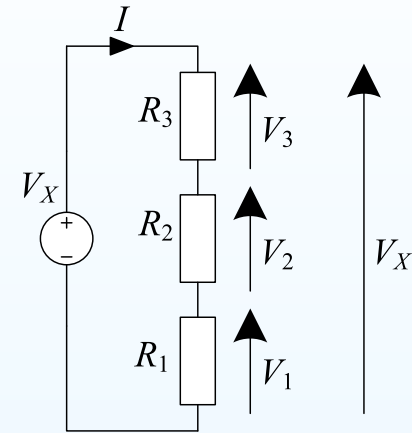2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

$$\begin{aligned}V_X &= V_1 + V_2 + V_3 \\&= IR_1 + IR_2 + IR_3 \\&= I(R_1 + R_2 + R_3)\end{aligned}$$




Series Resistors: Voltage Divider

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

$$\begin{aligned}V_X &= V_1 + V_2 + V_3 \\&= IR_1 + IR_2 + IR_3 \\&= I(R_1 + R_2 + R_3)\end{aligned}$$
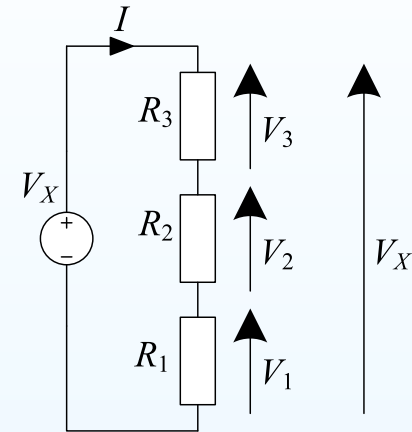
$$\frac{V_1}{V_X} = \frac{IR_1}{I(R_1 + R_2 + R_3)}$$




Series Resistors: Voltage Divider

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

$$\begin{aligned}V_X &= V_1 + V_2 + V_3 \\&= IR_1 + IR_2 + IR_3 \\&= I(R_1 + R_2 + R_3)\end{aligned}$$
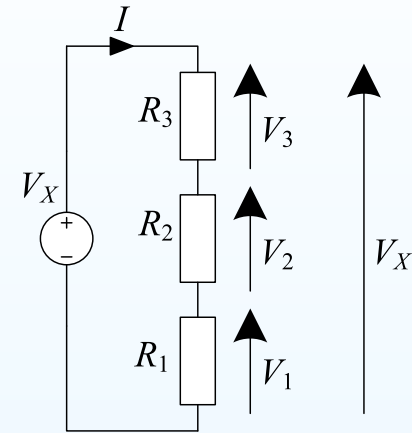
$$\begin{aligned}\frac{V_1}{V_X} &= \frac{IR_1}{I(R_1 + R_2 + R_3)} \\&= \frac{R_1}{R_1 + R_2 + R_3}\end{aligned}$$



2: Resistor Circuits


- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Series Resistors: Voltage Divider

$$\begin{aligned}V_X &= V_1 + V_2 + V_3 \\&= IR_1 + IR_2 + IR_3 \\&= I(R_1 + R_2 + R_3)\end{aligned}$$

$$\begin{aligned}\frac{V_1}{V_X} &= \frac{IR_1}{I(R_1 + R_2 + R_3)} \\&= \frac{R_1}{R_1 + R_2 + R_3} = \frac{R_1}{R_T}\end{aligned}$$

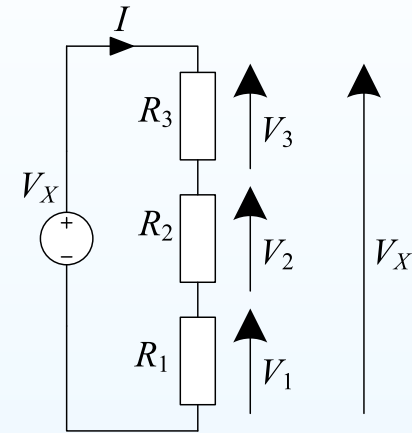where $R_T = R_1 + R_2 + R_3$ is the total resistance of the chain.



2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary


Series Resistors: Voltage Divider

$$\begin{aligned}V_X &= V_1 + V_2 + V_3 \\&= IR_1 + IR_2 + IR_3 \\&= I(R_1 + R_2 + R_3)\end{aligned}$$

$$\begin{aligned}\frac{V_1}{V_X} &= \frac{IR_1}{I(R_1 + R_2 + R_3)} \\&= \frac{R_1}{R_1 + R_2 + R_3} = \frac{R_1}{R_T}\end{aligned}$$

where $R_T = R_1 + R_2 + R_3$ is the total resistance of the chain.

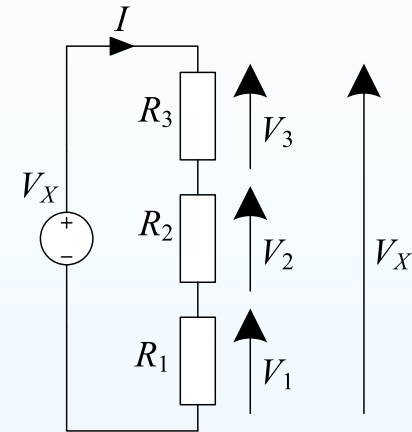V_X is divided into $V_1 : V_2 : V_3$ in the proportions $R_1 : R_2 : R_3$.



Series Resistors: Voltage Divider


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

$$\begin{aligned}V_X &= V_1 + V_2 + V_3 \\&= IR_1 + IR_2 + IR_3 \\&= I(R_1 + R_2 + R_3)\end{aligned}$$

$$\begin{aligned}\frac{V_1}{V_X} &= \frac{IR_1}{I(R_1 + R_2 + R_3)} \\&= \frac{R_1}{R_1 + R_2 + R_3} = \frac{R_1}{R_T}\end{aligned}$$

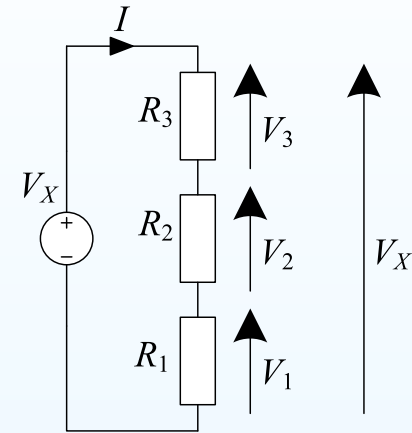
where $R_T = R_1 + R_2 + R_3$ is the total resistance of the chain.



V_X is divided into $V_1 : V_2 : V_3$ in the proportions $R_1 : R_2 : R_3$.

Approximate Voltage Divider:
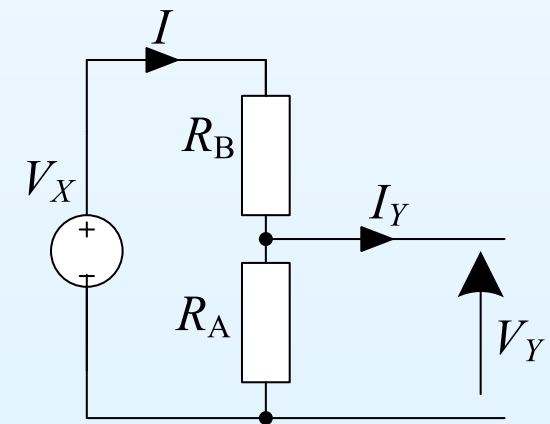
$$\text{If } I_Y = 0, \text{ then } V_Y = \frac{R_A}{R_A + R_B} V_X.$$



Series Resistors: Voltage Divider


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

$$\begin{aligned}V_X &= V_1 + V_2 + V_3 \\&= IR_1 + IR_2 + IR_3 \\&= I(R_1 + R_2 + R_3)\end{aligned}$$

$$\begin{aligned}\frac{V_1}{V_X} &= \frac{IR_1}{I(R_1 + R_2 + R_3)} \\&= \frac{R_1}{R_1 + R_2 + R_3} = \frac{R_1}{R_T}\end{aligned}$$

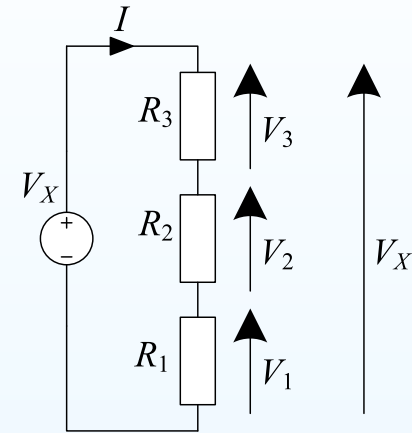where $R_T = R_1 + R_2 + R_3$ is the total resistance of the chain.




V_X is divided into $V_1 : V_2 : V_3$ in the proportions $R_1 : R_2 : R_3$.

Approximate Voltage Divider:

$$\text{If } I_Y = 0, \text{ then } V_Y = \frac{R_A}{R_A + R_B} V_X.$$
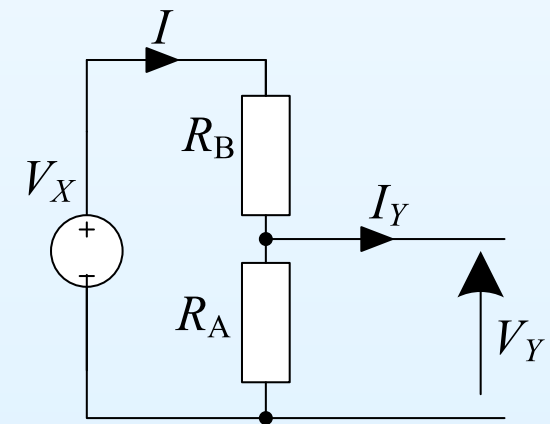
$$\text{If } I_Y \ll I, \text{ then } V_Y \approx \frac{R_A}{R_A + R_B} V_X.$$




Parallel Resistors: Current Divider

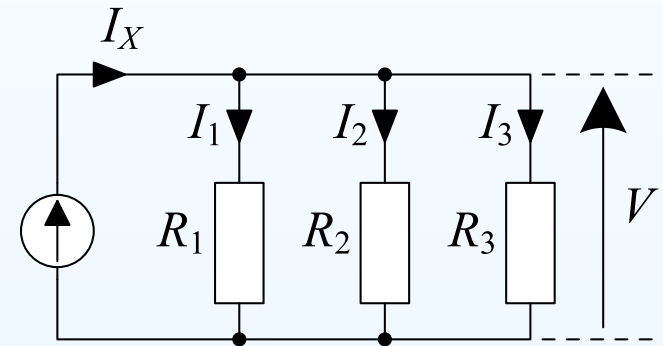2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Parallel resistors all share the same V .




2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Parallel Resistors: Current Divider

Parallel resistors all share the same V .
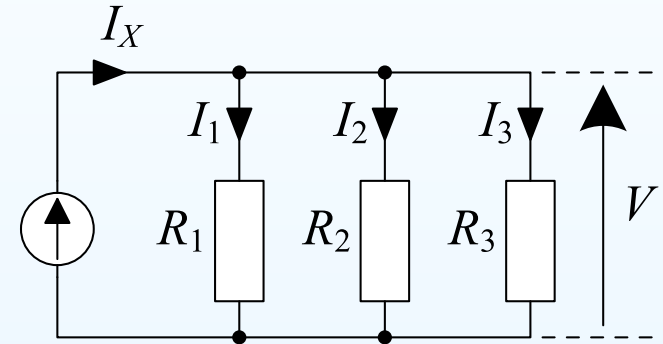
$$I_1 = \frac{V}{R_1} = VG_1 \quad \text{where } G_1 = \frac{1}{R_1} \text{ is the } \textit{conductance} \text{ of } R_1.$$



Parallel Resistors: Current Divider


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Parallel resistors all share the same V .

$$I_1 = \frac{V}{R_1} = VG_1 \quad \text{where } G_1 = \frac{1}{R_1} \text{ is the } \textit{conductance} \text{ of } R_1.$$
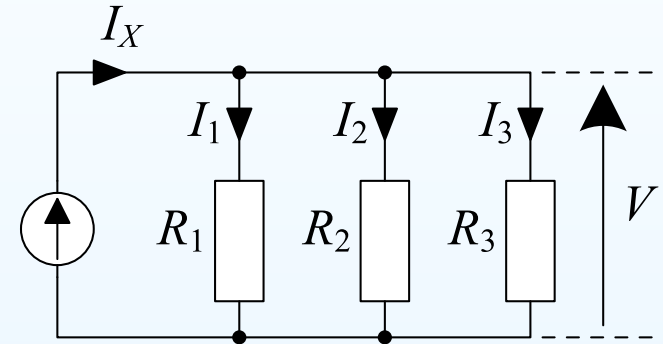
$$\begin{aligned} I_X &= I_1 + I_2 + I_3 \\ &= VG_1 + VG_2 + VG_3 \\ &= V(G_1 + G_2 + G_3) \end{aligned}$$



Parallel Resistors: Current Divider


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Parallel resistors all share the same V .

$$I_1 = \frac{V}{R_1} = VG_1 \quad \text{where } G_1 = \frac{1}{R_1} \text{ is the } \textit{conductance} \text{ of } R_1.$$
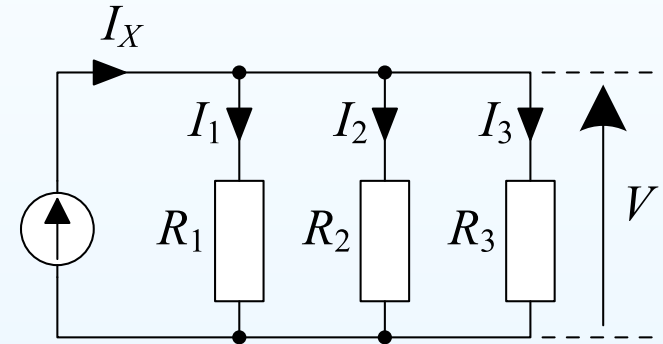
$$\begin{aligned} I_X &= I_1 + I_2 + I_3 \\ &= VG_1 + VG_2 + VG_3 \\ &= V(G_1 + G_2 + G_3) \end{aligned}$$



$$\frac{I_1}{I_X} = \frac{VG_1}{V(G_1 + G_2 + G_3)} = \frac{G_1}{G_1 + G_2 + G_3} = \frac{G_1}{G_P}$$

where $G_P = G_1 + G_2 + G_3$ is the total conductance of the resistors.

Parallel Resistors: Current Divider


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Parallel resistors all share the same V .

$$I_1 = \frac{V}{R_1} = VG_1 \quad \text{where } G_1 = \frac{1}{R_1} \text{ is the } \textit{conductance} \text{ of } R_1.$$
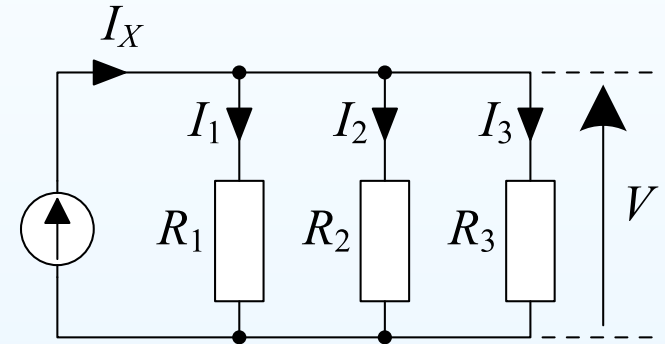
$$\begin{aligned} I_X &= I_1 + I_2 + I_3 \\ &= VG_1 + VG_2 + VG_3 \\ &= V(G_1 + G_2 + G_3) \end{aligned}$$



$$\frac{I_1}{I_X} = \frac{VG_1}{V(G_1 + G_2 + G_3)} = \frac{G_1}{G_1 + G_2 + G_3} = \frac{G_1}{G_P}$$

where $G_P = G_1 + G_2 + G_3$ is the total conductance of the resistors.

I_X is divided into $I_1 : I_2 : I_3$ in the proportions $G_1 : G_2 : G_3$.

Parallel Resistors: Current Divider


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Parallel resistors all share the same V .

$$I_1 = \frac{V}{R_1} = VG_1 \quad \text{where } G_1 = \frac{1}{R_1} \text{ is the } \textit{conductance} \text{ of } R_1.$$
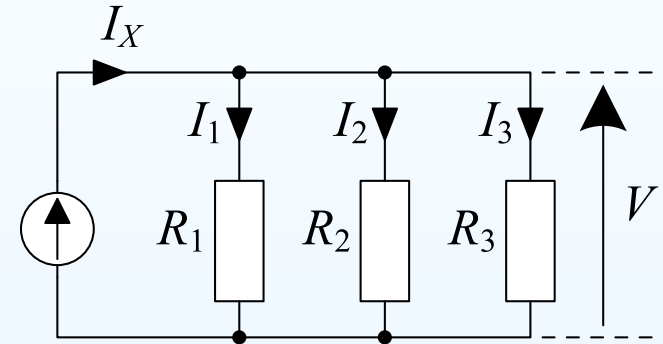
$$\begin{aligned} I_X &= I_1 + I_2 + I_3 \\ &= VG_1 + VG_2 + VG_3 \\ &= V(G_1 + G_2 + G_3) \end{aligned}$$



$$\frac{I_1}{I_X} = \frac{VG_1}{V(G_1 + G_2 + G_3)} = \frac{G_1}{G_1 + G_2 + G_3} = \frac{G_1}{G_P}$$

where $G_P = G_1 + G_2 + G_3$ is the total conductance of the resistors.

I_X is divided into $I_1 : I_2 : I_3$ in the proportions $G_1 : G_2 : G_3$.

Special case for only two resistors:

$$I_1 : I_2 = G_1 : G_2 = R_2 : R_1 \Rightarrow I_1 = \frac{R_2}{R_1 + R_2} I_X.$$


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Equivalent Resistance: Series

We know that $V = V_1 + V_2 + V_3 = I(R_1 + R_2 + R_3) = IR_T$

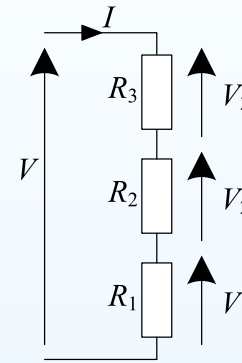So we can replace the three resistors by a single *equivalent resistor* of value R_T without affecting the relationship between V and I .




Equivalent Resistance: Series

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

We know that $V = V_1 + V_2 + V_3 = I(R_1 + R_2 + R_3) = IR_T$

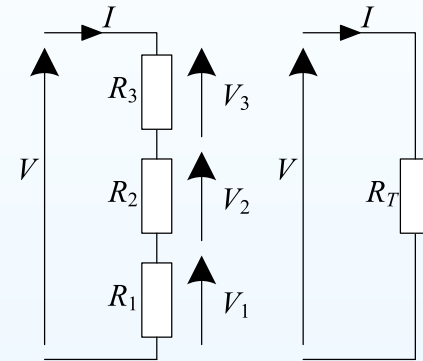So we can replace the three resistors by a single *equivalent resistor* of value R_T without affecting the relationship between V and I .




Equivalent Resistance: Series

2: Resistor Circuits


- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

We know that $V = V_1 + V_2 + V_3 = I(R_1 + R_2 + R_3) = IR_T$

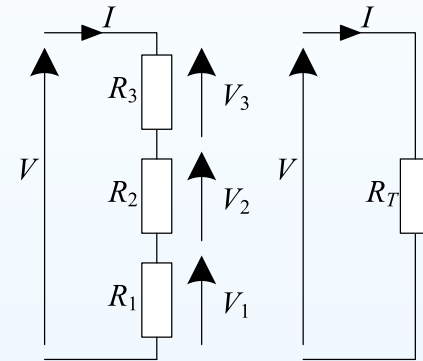So we can replace the three resistors by a single *equivalent resistor* of value R_T without affecting the relationship between V and I .



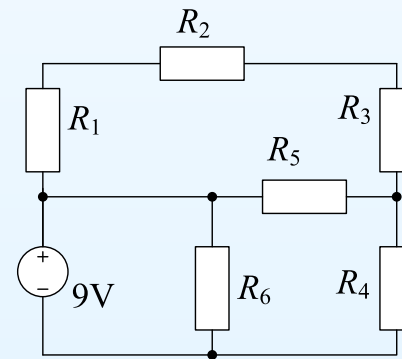Replacing series resistors by their equivalent resistor will not affect any of the voltages or currents in the rest of the circuit.




Equivalent Resistance: Series

2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary


We know that $V = V_1 + V_2 + V_3 = I(R_1 + R_2 + R_3) = IR_T$

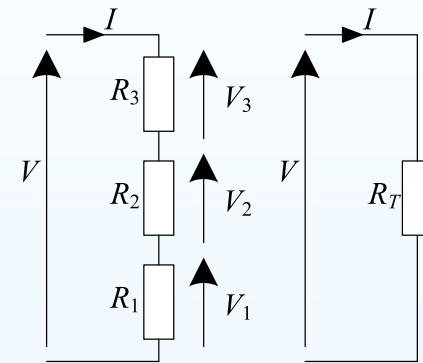So we can replace the three resistors by a single *equivalent resistor* of value R_T without affecting the relationship between V and I .



Replacing series resistors by their equivalent resistor will not affect any of the voltages or currents in the rest of the circuit.

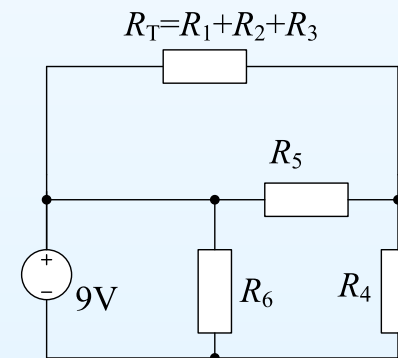However the individual voltages V_1 , V_2 and V_3 are no longer accessible.




Equivalent Resistance: Parallel

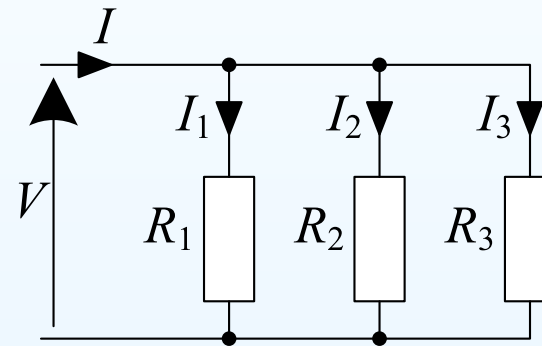2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- **Equivalent Resistance: Parallel**
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Similarly we know that $I = I_1 + I_2 + I_3 = V(G_1 + G_2 + G_3) = VG_P$.




Equivalent Resistance: Parallel

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- **Equivalent Resistance: Parallel**
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Similarly we know that $I = I_1 + I_2 + I_3 = V(G_1 + G_2 + G_3) = VG_P$.

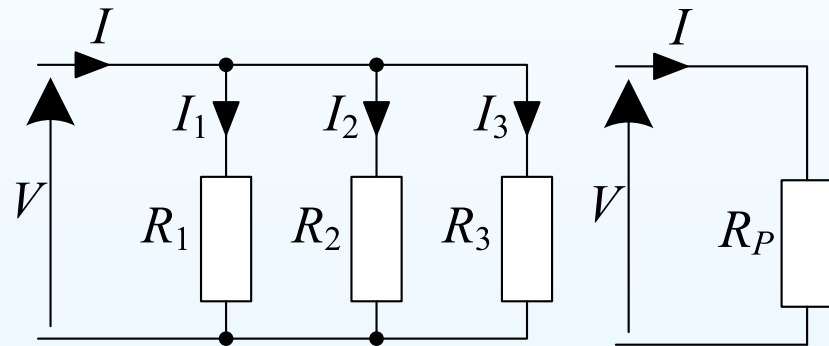So $V = IR_P$ where $R_P = \frac{1}{G_P} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$



Equivalent Resistance: Parallel


2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- **Equivalent Resistance: Parallel**
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Similarly we know that $I = I_1 + I_2 + I_3 = V(G_1 + G_2 + G_3) = VG_P$.

So $V = IR_P$ where $R_P = \frac{1}{G_P} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$

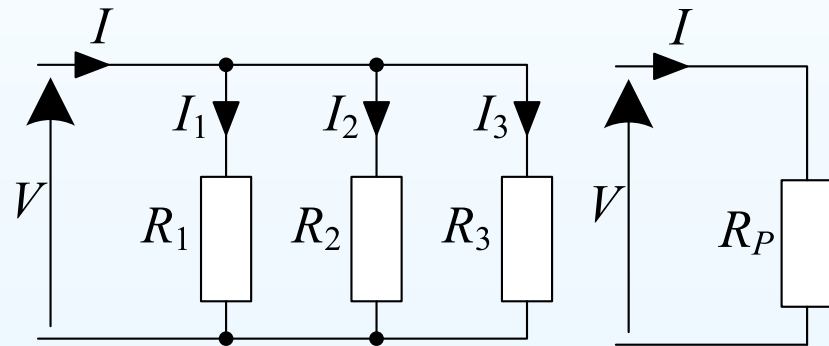We can use a single *equivalent resistor* of resistance R_P without affecting the relationship between V and I .



Equivalent Resistance: Parallel


2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- **Equivalent Resistance: Parallel**
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary


Similarly we know that $I = I_1 + I_2 + I_3 = V(G_1 + G_2 + G_3) = VG_P$.

So $V = IR_P$ where $R_P = \frac{1}{G_P} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$

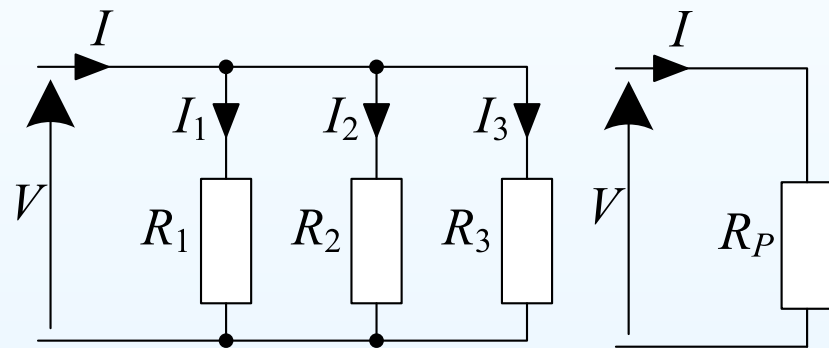We can use a single *equivalent resistor* of resistance R_P without affecting the relationship between V and I .



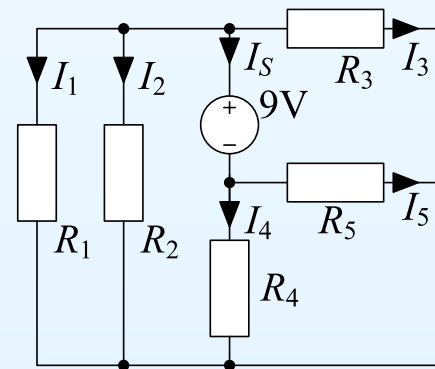Replacing parallel resistors by their equivalent resistor will not affect any of the voltages or currents in the rest of the circuit.



Equivalent Resistance: Parallel


2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- **Equivalent Resistance: Parallel**
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary


Similarly we know that $I = I_1 + I_2 + I_3 = V(G_1 + G_2 + G_3) = VG_P$.

So $V = IR_P$ where $R_P = \frac{1}{G_P} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$

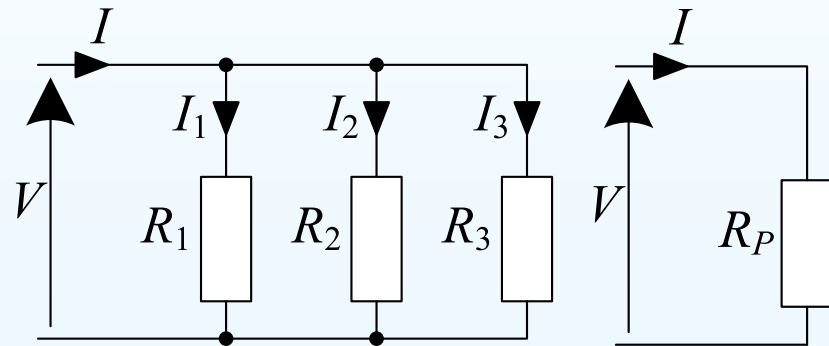We can use a single *equivalent resistor* of resistance R_P without affecting the relationship between V and I .



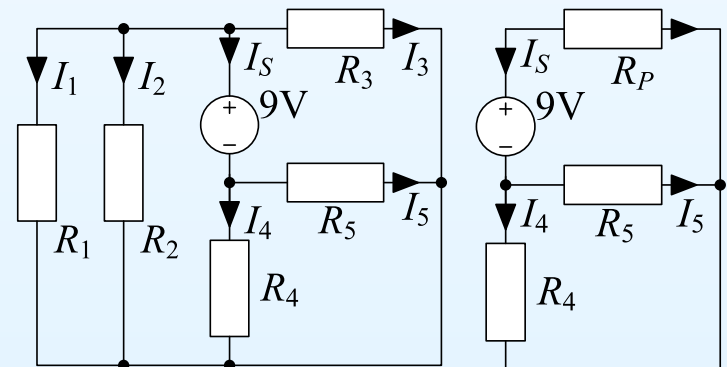Replacing parallel resistors by their equivalent resistor will not affect any of the voltages or currents in the rest of the circuit.



Equivalent Resistance: Parallel


2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- **Equivalent Resistance: Parallel**
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Similarly we know that $I = I_1 + I_2 + I_3 = V(G_1 + G_2 + G_3) = VG_P$.


So $V = IR_P$ where $R_P = \frac{1}{G_P} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$

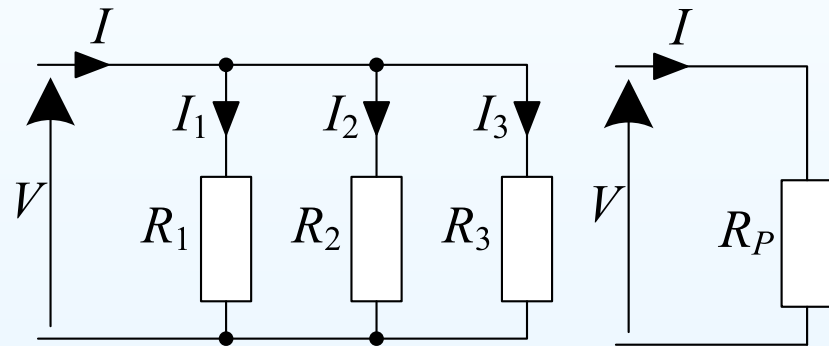We can use a single *equivalent resistor* of resistance R_P without affecting the relationship between V and I .



Replacing parallel resistors by their equivalent resistor will not affect any of the voltages or currents in the rest of the circuit.

R_4 and R_5 are also in parallel.

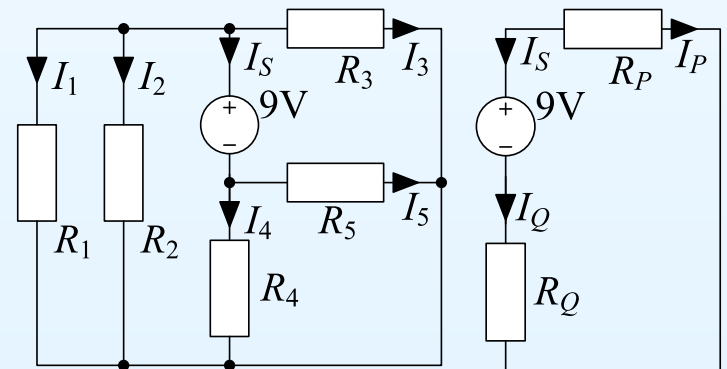

Equivalent Resistance: Parallel


2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- **Equivalent Resistance: Parallel**
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Similarly we know that $I = I_1 + I_2 + I_3 = V(G_1 + G_2 + G_3) = VG_P$.


So $V = IR_P$ where $R_P = \frac{1}{G_P} = \frac{1}{G_1 + G_2 + G_3} = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$

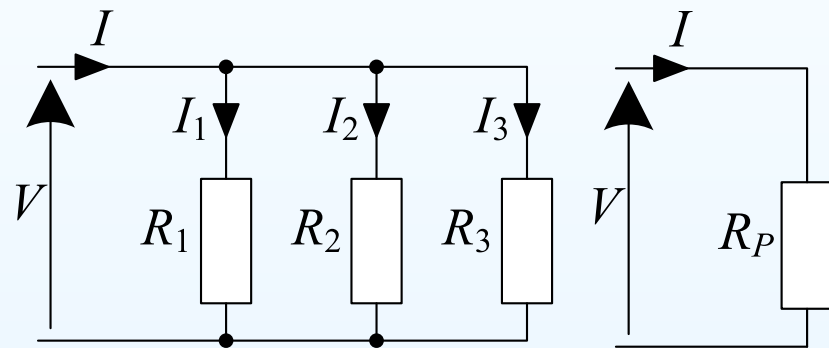We can use a single *equivalent resistor* of resistance R_P without affecting the relationship between V and I .



Replacing parallel resistors by their equivalent resistor will not affect any of the voltages or currents in the rest of the circuit.

R_4 and R_5 are also in parallel.

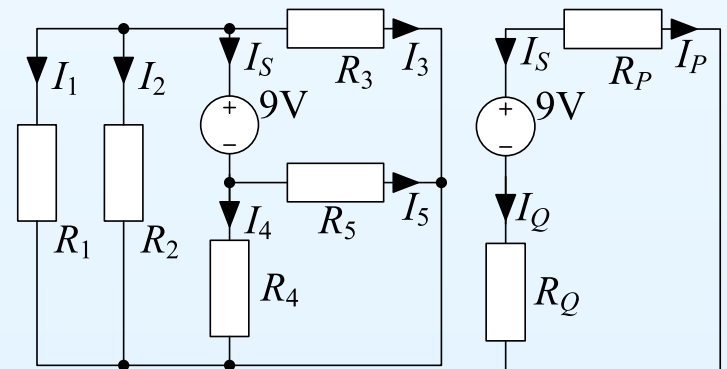

Much simpler - although none of the original currents $I_1, \dots, I_5$ are now accessible. Current I_S and the three node voltages are identical.

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- **Equivalent Resistance: Parallel Formulae**
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Equivalent Resistance: Parallel Formulae

For parallel resistors $G_P = G_1 + G_2 + G_3$

or equivalently $R_P = R_1 || R_2 || R_3 = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$.

These formulae work for any number of resistors.

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- **Equivalent Resistance: Parallel Formulae**
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Equivalent Resistance: Parallel Formulae

For parallel resistors $G_P = G_1 + G_2 + G_3$

or equivalently $R_P = R_1 || R_2 || R_3 = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$.

These formulae work for any number of resistors.

- For the special case of two parallel resistors

$$R_P = \frac{1}{1/R_1 + 1/R_2} = \frac{R_1 R_2}{R_1 + R_2} \text{ ("product over sum")}$$

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- **Equivalent Resistance: Parallel Formulae**
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Equivalent Resistance: Parallel Formulae

For parallel resistors $G_P = G_1 + G_2 + G_3$

or equivalently $R_P = R_1 || R_2 || R_3 = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$.

These formulae work for any number of resistors.

- For the special case of two parallel resistors

$$R_P = \frac{1}{1/R_1 + 1/R_2} = \frac{R_1 R_2}{R_1 + R_2} \text{ ("product over sum")}$$

- If one resistor is a multiple of the other

Suppose $R_2 = kR_1$, then

$$R_P = \frac{R_1 R_2}{R_1 + R_2} = \frac{k R_1^2}{(k+1) R_1} = \frac{k}{k+1} R_1 = \left(1 - \frac{1}{k+1}\right) R_1$$

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- **Equivalent Resistance: Parallel Formulae**
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Equivalent Resistance: Parallel Formulae

For parallel resistors $G_P = G_1 + G_2 + G_3$

or equivalently $R_P = R_1 || R_2 || R_3 = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$.

These formulae work for any number of resistors.

- For the special case of two parallel resistors

$$R_P = \frac{1}{1/R_1 + 1/R_2} = \frac{R_1 R_2}{R_1 + R_2} \text{ ("product over sum")}$$

- If one resistor is a multiple of the other

Suppose $R_2 = kR_1$, then

$$R_P = \frac{R_1 R_2}{R_1 + R_2} = \frac{k R_1^2}{(k+1) R_1} = \frac{k}{k+1} R_1 = \left(1 - \frac{1}{k+1}\right) R_1$$

$$\text{Example: } 1 \text{ k}\Omega || 99 \text{ k}\Omega = \frac{99}{100} \text{ k}\Omega = \left(1 - \frac{1}{100}\right) \text{ k}\Omega$$

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- **Equivalent Resistance: Parallel Formulae**
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Equivalent Resistance: Parallel Formulae

For parallel resistors $G_P = G_1 + G_2 + G_3$

or equivalently $R_P = R_1 || R_2 || R_3 = \frac{1}{1/R_1 + 1/R_2 + 1/R_3}$.

These formulae work for any number of resistors.

- For the special case of two parallel resistors

$$R_P = \frac{1}{1/R_1 + 1/R_2} = \frac{R_1 R_2}{R_1 + R_2} \text{ ("product over sum")}$$

- If one resistor is a multiple of the other

Suppose $R_2 = kR_1$, then

$$R_P = \frac{R_1 R_2}{R_1 + R_2} = \frac{k R_1^2}{(k+1) R_1} = \frac{k}{k+1} R_1 = \left(1 - \frac{1}{k+1}\right) R_1$$

$$\text{Example: } 1 \text{ k}\Omega || 99 \text{ k}\Omega = \frac{99}{100} \text{ k}\Omega = \left(1 - \frac{1}{100}\right) \text{ k}\Omega$$


Important: The equivalent resistance of parallel resistors is always less than any of them.

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Simplifying Resistor Networks

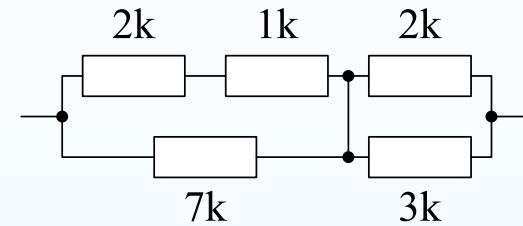Many resistor circuits can be simplified by alternately combining series and parallel resistors.




2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Simplifying Resistor Networks

Many resistor circuits can be simplified by alternately combining series and parallel resistors.

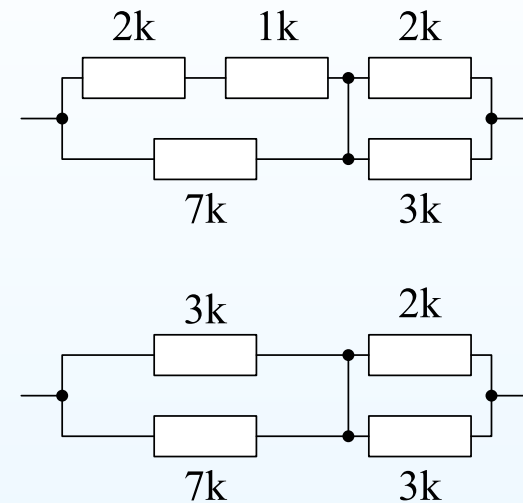Series: $2\text{ k} + 1\text{ k} = 3\text{ k}$



Simplifying Resistor Networks

2: Resistor Circuits



- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Many resistor circuits can be simplified by alternately combining series and parallel resistors.

$$\text{Series: } 2\text{ k} + 1\text{ k} = 3\text{ k}$$

$$\text{Parallel: } 3\text{ k} \parallel 7\text{ k} = 2.1\text{ k}$$
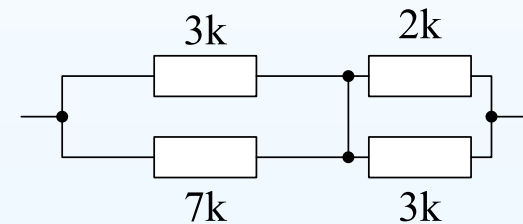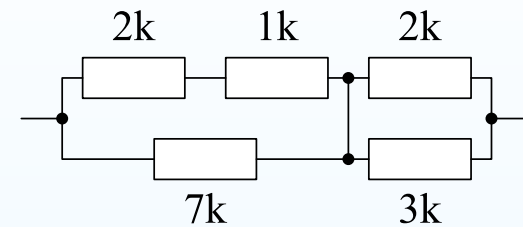
$$\text{Parallel: } 2\text{ k} \parallel 3\text{ k} = 1.2\text{ k}$$



2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Simplifying Resistor Networks




Many resistor circuits can be simplified by alternately combining series and parallel resistors.

$$\text{Series: } 2 \text{ k} + 1 \text{ k} = 3 \text{ k}$$

$$\text{Parallel: } 3 \text{ k} \parallel 7 \text{ k} = 2.1 \text{ k}$$

$$\text{Parallel: } 2 \text{ k} \parallel 3 \text{ k} = 1.2 \text{ k}$$
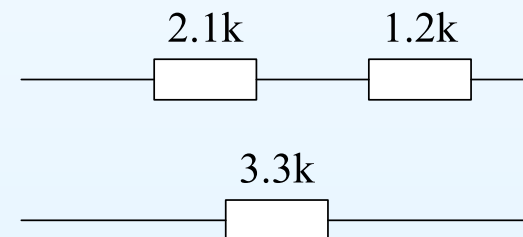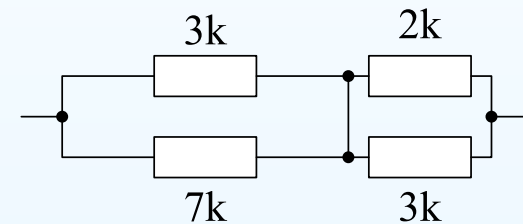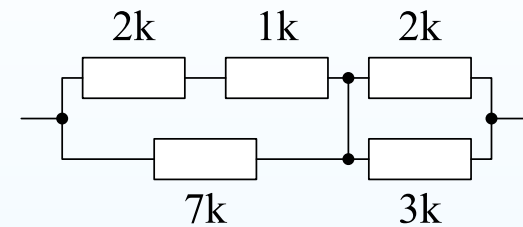
$$\text{Series: } 2.1 \text{ k} + 1.2 \text{ k} = 3.3 \text{ k}$$



Simplifying Resistor Networks

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Many resistor circuits can be simplified by alternately combining series and parallel resistors.





$$\text{Series: } 2\text{ k} + 1\text{ k} = 3\text{ k}$$

$$\text{Parallel: } 3\text{ k} \parallel 7\text{ k} = 2.1\text{ k}$$

$$\text{Parallel: } 2\text{ k} \parallel 3\text{ k} = 1.2\text{ k}$$

$$\text{Series: } 2.1\text{ k} + 1.2\text{ k} = 3.3\text{ k}$$

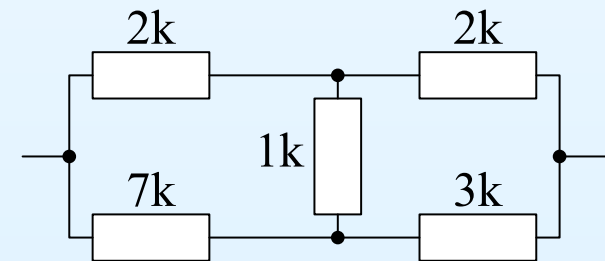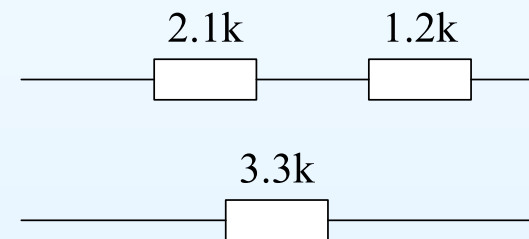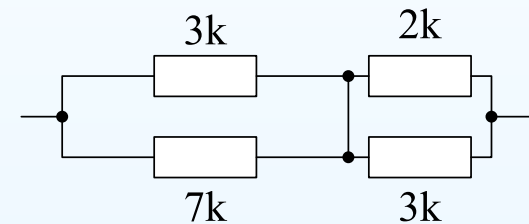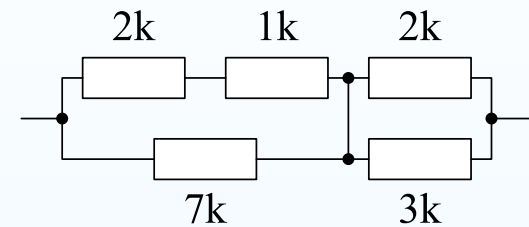Sadly this method does not always work: there are no series or parallel resistors here.




2: Resistor Circuits

- Kirchhoff's Voltage Law
- Kirchhoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Non-ideal Voltage Source

An **ideal** battery has a characteristic that is vertical: battery voltage does not vary with current.

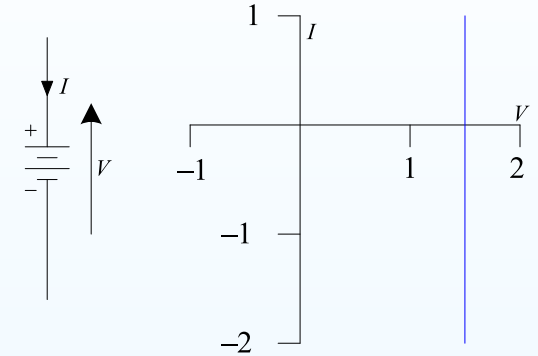Normally a battery is supplying energy so V and I have opposite signs, so $I \leq 0$.




2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Non-ideal Voltage Source


An **ideal** battery has a characteristic that is vertical: battery voltage does not vary with current.

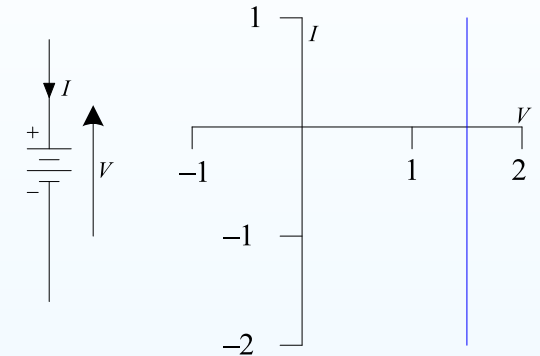Normally a battery is supplying energy so V and I have opposite signs, so $I \leq 0$.



An **real** battery has a characteristic that has a slight positive slope: battery voltage decreases as the (negative) current increases.

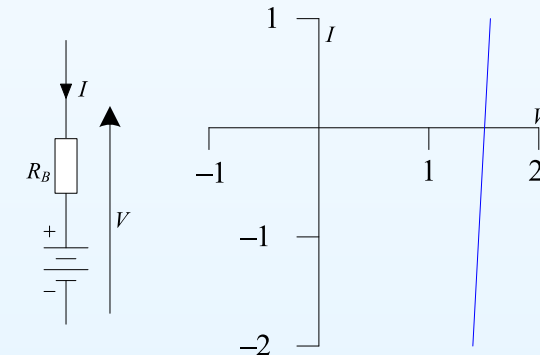Model this by including a small resistor in series. $V = V_B + IR_B$.




2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- Summary

Non-ideal Voltage Source

An **ideal** battery has a characteristic that is vertical: battery voltage does not vary with current.


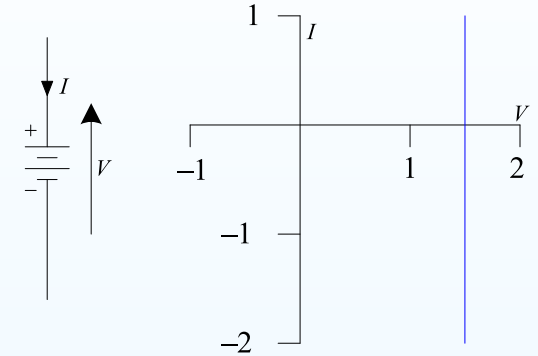
Normally a battery is supplying energy so V and I have opposite signs, so $I \leq 0$.



An **real** battery has a characteristic that has a slight positive slope: battery voltage decreases as the (negative) current increases.

Model this by including a small resistor in series. $V = V_B + IR_B$.

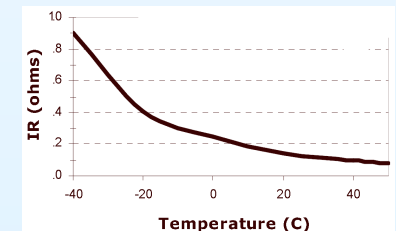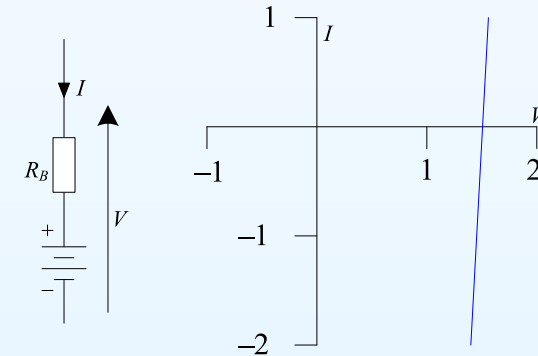The equivalent resistance for a battery increases at low temperatures.



Summary

2: Resistor Circuits

- Kirchoff's Voltage Law
- Kirchoff's Current Law
- KCL Example
- Series and Parallel
- Dividers
- Equivalent Resistance: Series
- Equivalent Resistance: Parallel
- Equivalent Resistance: Parallel Formulae
- Simplifying Resistor Networks
- Non-ideal Voltage Source
- **Summary**

- Kichoff's Voltage and Current Laws
- Series and Parallel components
- Voltage and Current Dividers
- Simplifying Resistor Networks
- Battery Internal Resistance

For further details see Hayt Ch 3 or Irwin Ch 2.