

Surge Protection for Intersil's Standard RS-485 Transceivers

Introduction

This application note presents various protection methods for Intersil's standard RS-485 transceivers.

[AN1977](#) explained, connecting TVS devices directly to the transceiver bus terminals introduces the risk of damaging the transceiver's ESD structures during a surge event. Adding current limiting components in series with the bus terminals lowers the risk. In doing so, the type and number of components being added depends on the surge protection level required for the application. Refer to [AN1976](#), "Important Transient Immunity Tests for RS-485 Networks" for the assignment of protection levels to specific installation classes.

Level 2 (1kV) Surge Protection

An artifact of standard RS-485 transceivers is their asymmetric stand-off voltages of -9V and +14V, which necessitate the use of bidirectional TVS devices with asymmetric breakdown voltages. The only device satisfying this requirement is the SM712, originally designed by Semtech Corporation in 2004.

The SM712 is a bidirectional TVS with asymmetric breakdown, rated with 400W for an 8/20µs current pulse. [Table 1](#) shows the most relevant device parameters.

TABLE 1. SM712 DEVICE PARAMETERS AT +25°C

PARAMETER	SYMBOL	12V TVS	7V TVS	UNIT
Stand-Off Voltage	V _{WM}	12	7	V
Breakdown Voltage	V _{BR}	13.3	7.5	V
Clamping Voltage at I _{PP}	V _C	26	12	V
Peak Pulse Current	I _{PP}	17		A
Derating Factor (Pulse)	DF	0.8 at +85°C		-
Junction Capacitance	C _J	75		pF

When operating the SM712 at the industrial temperature range maximum of +85°C, its power and hence, peak pulse current capability must be derated. While the datasheet provides a derating factor of DF = 0.5 at +85°C, this factor is mainly applicable for average powers of long pulse durations. For short pulses, such as the 8/20µs pulse however, Semtech provides a much higher factor of DF = 0.8, thus allowing for higher pulse currents at +85°C. The derated test voltage of the surge generator is then calculated via [Equation 1](#):

$$V_{PK} = I_{PP} \cdot DF \cdot 84\Omega = 17A \cdot 0.8 \cdot 84\Omega = 1.14kV \quad (EQ.1)$$

This voltage exceeds the IEC61000-4-5, protection Level 2 of 1kV.

To limit the bus currents into the transceiver during a surge event, carbon composite or pulse-proof thick-film resistors

should be inserted between the TVSs and the transceiver. Due to their voltage divider action with the bus termination resistors, their value should be 10Ω or less to minimize bus voltage attenuation during normal operation.

[Figure 1](#) shows a Level 2 surge protection example for Intersil's ISL315xE and ISL848xE families of standard transceivers, and [Table 2](#) shows the associated Bill of Materials (BOM).

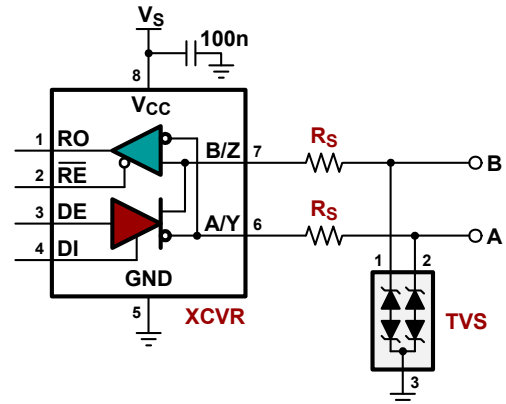


FIGURE 1. IEC61000-4-5, LEVEL 2 (1kV), SURGE PROTECTION

During network planning, the SM712 junction capacitance of 75pF must be considered as it adds an equivalent of seven bus transceivers to each bus node protected. This might require a reduction in bus nodes, or data rate, or both.

TABLE 2. BOM FOR CIRCUIT IN [Figure 1](#)

NAME	FUNCTION	PART NUMBER	VENDOR
XCVR	5V, 115KBPS TRANSCEIVER	ISL3152EIBZ	INTERSIL
TVS	400W (8, 20µs), BIDIRECTIONAL TVS	SM712.TCT	SEMTECH
R _S	10Ω, 0.2W, PULSE-PROOF THICK-FILM RESISTOR	CRCW0603-HP e3 SERIES	VISHAY

Level 3 (2kV) Surge Protection

Higher surge protection levels require overcurrent and overvoltage protectors in addition to the TVS. The Overcurrent Protector (OCP) protects the TVS from high currents exceeding the TVS peak pulse current rating, while the Overvoltage Protector (OVP) protects the OCP against high transient voltages that are above its withstand voltage. [Figure 2 on page 2](#) depicts the principle of a higher level surge protection scheme.

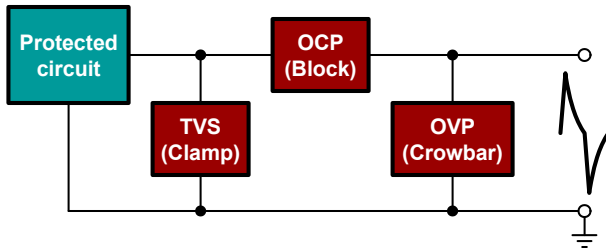


FIGURE 2. HIGH-LEVEL SURGE PROTECTION WITH OVERCURRENT AND OVERVOLTAGE PROTECTORS

The Overcurrent Protector (OCP)

The overcurrent protector consists of a current limiter and an electronic output switch, with predefined levels for trigger current and reset voltage. Its switching characteristic is shown in [Figure 3](#).

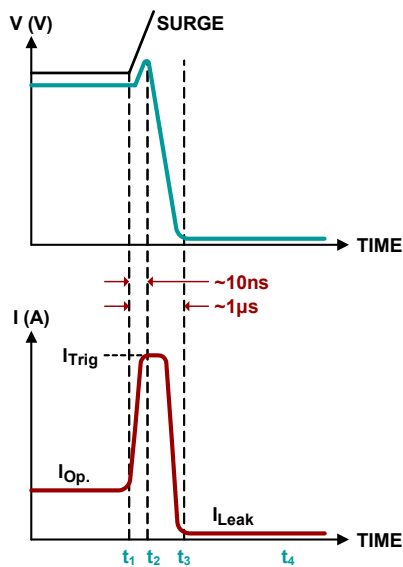


FIGURE 3. OCP SWITCHING CHARACTERISTIC

During normal operation, the device is in the off-state presenting a low resistance to the signal path. When a surge occurs (t_1), the current through the OCP increases up to the trigger level, I_{TRIG} , (t_2). At that point the current limiter activates the internal switch, changing the device resistance from low-impedance to high-impedance. Within $1\mu s$ the OCP current drops to less than $1mA$ (t_3). The device is now in the on-state and remains there for the duration of the transient (t_4). When the transient recedes and the voltage across the OCP drops below the reset threshold, the device returns to the off-state, allowing for normal system operation to proceed.

To match the dynamic characteristic of the OCP with the ones of the TVS and the transceiver, the Bourns overcurrent protector, aka transient blocking unit, TBU-CA065-200-WH was selected for the protection circuit in [Figure 5 on page 3](#). This device provides minimum and maximum current trigger levels of 200mA and 400mA respectively. The 200mA level is well above the maximum line current during normal operation, and the 400mA threshold is low enough to prevent excessive joule heating within the TVS and transceiver ESD structures during a surge event. The

device also has an off-state resistance of less than 10Ω , which attenuates the bus voltage by less than 10%.

The Overvoltage Protector (OVP)

The overvoltage protector is a crowbar device that short-circuits the signal line to ground, thus diverting the majority of the transient energy away from the overcurrent protector. Crowbar devices have a snap-back characteristic, allowing them to conduct huge currents at low voltage drops across the device. This characteristic is utilized in two different technologies: gas discharge tubes and solid-state Thyristor Surge Protection Devices (TSPDs).

The protection scheme in [Figure 5](#) uses the Bourns TSPD TISP4240M3BJR-S as overvoltage protector. Its V-I characteristic is shown in [Figure 4](#).

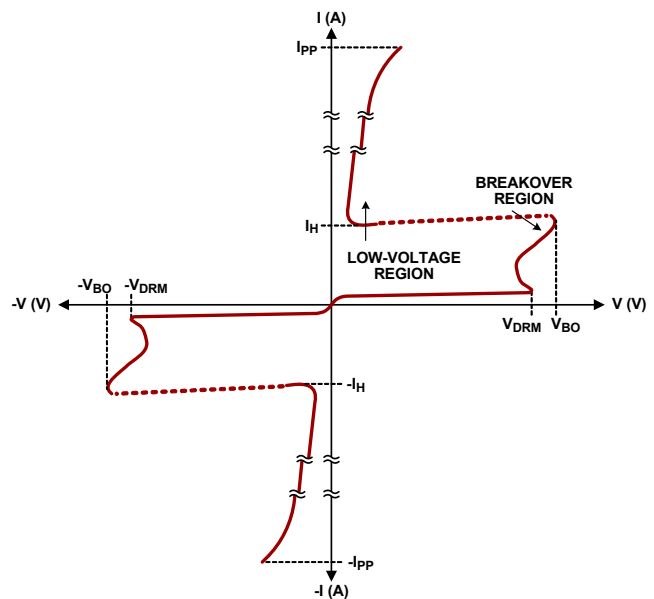


FIGURE 4. V-I CHARACTERISTIC OF THE THYRISTOR SURGE PROTECTION DEVICE

Here, V_{DRM} is the maximum working voltage up to which the TSPD remains in high-impedance (off-state). Above this voltage the device enters the breakover region. When a surge exceeds the breakover voltage, V_{BO} , the device turns on and transitions into the low-voltage region, where it conducts high currents. The TSPD returns to the off-state when the transient current drops below the holding current, I_H .

Unlike TVS devices, whose response time is in the sub-nano seconds range, TSPDs require time to transition from the breakover to the low-voltage region. During this time the overcurrent protector shields the downstream circuitry (TVS and transceiver) from the high currents resulting from the high V_{BO} .

Figure 5 shows the circuit of a Level 3 (2kV) surge protection scheme and Table 3 lists the associated BOM.

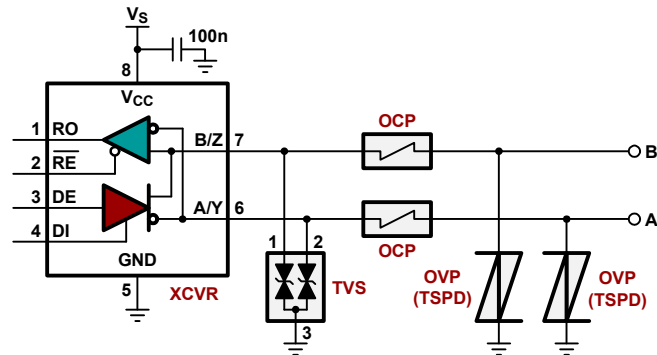


FIGURE 5. IEC61000-4-5, LEVEL 3 (2kV), SURGE PROTECTION

TABLE 3. BOM FOR CIRCUIT IN Figure 5

NAME	FUNCTION	ORDER NO.	VENDOR
XCVR	5V, 115KBPS TRANSCEIVER	ISL3152EIBZ	INTERSIL
TVS	400W (8, 20μs), BIDIRECTIONAL TVS	SM712.TCT	SEMTECH
OCP	200mA TRANSIENT BLOCKING UNIT	TBU-CA065-200-WH	BOURNS
OVP	220A THYRISTOR	TISP4240M3BJR-S	BOURNS

Level 4 (4kV) Surge Protection

While industrial applications rarely demand surge protection above Level 3, communication lines between buildings will benefit from higher protection levels.

The circuit in Figure 7 therefore shows the protection scheme for surge Level 4 (4kV) protection. This circuit is almost identical to the one in Figure 5 with the exception that the thyristor protection devices, rated for 220A, have been replaced by a gas discharge tube, 2038-15-SM-RPLF, rated for 5kA. GDTs typically provide protection to higher overvoltage and overcurrent stress than TSPDs.

Figure 6 shows the switching characteristic of a GDT. When a transient voltage reaches the impulse spark-over voltage, the GDT transitions from the off-state (high impedance) to Arc mode (virtual short). In this mode, the GDT provides a crowbar current

path to ground, thus diverting the transient current away from the protected device.

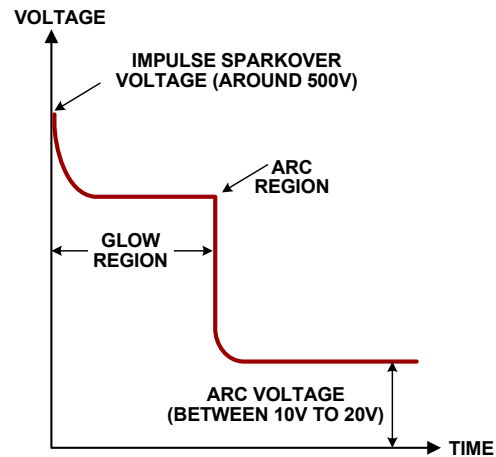


FIGURE 6. GDT SWITCHING CHARACTERISTIC

With increasing voltage across the GDT, the gas in the tube starts ionizing due to the charge developed across it. In this region, known as the glow region, the increasing current flow generates an avalanche effect, transitioning the GDT into a virtual short. During the short-circuit event, the voltage developed across the device is known as the arc voltage. The transition time between the glow and arc region is dependent on the physical characteristics of the GDT.

Figure 7 shows the protection scheme for a Level 4 (4kV) surge protection and Table 4 lists the associated BOM.

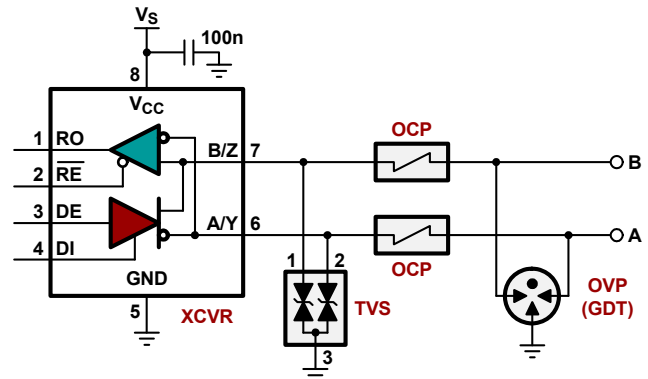


FIGURE 7. IEC61000-4-5, LEVEL 4 (4kV), SURGE PROTECTION

TABLE 4. BOM FOR CIRCUIT IN Figure 7

NAME	FUNCTION	ORDER NO.	VENDOR
XCVR	5V, 115KBPS TRANSCEIVER	ISL3152EIBZ	INTERSIL
TVS	400W (8, 20μs), BIDIRECTIONAL TVS	SM712.TCT	SEMTECH
OCP	200mA TRANSIENT BLOCKING UNIT	TBU-CA065-200-WH	BOURNS
OVP	5kA GAS DISCHARGE TUBE	2038-15-SM-RPLF	BOURNS

Summary

The circuits presented in this application note, provide solid protection against low and high level transients. High-level protection schemes however, have a high component count, thus leading to increased design cost and board space. [Table 5](#) provides a comparison between protection circuits.

TABLE 5. COMPARISON OF PROTECTION SCHEMES

PROTECTION LEVEL	COMPONENT COUNT	BOARD AREA (mm ²)	SOLUTION COST AT 1ku (\$)
1 (500V)	3	8.5	0.37
3 (2kV)	5	91	2.77
4 (4kV)	4	97	3.00

Simpler circuit designs, protecting against surge transients and DC faults, over standard and wide common-mode voltage ranges, can be accomplished using overvoltage protected transceivers. This is discussed in [AN1979](#), "Lightning Protection Simplified with Intersil's Overvoltage Protected (OVP) Transceivers".

Notice

1. Descriptions of circuits, software and other related information in this document are provided only to illustrate the operation of semiconductor products and application examples. You are fully responsible for the incorporation or any other use of the circuits, software, and information in the design of your product or system. Renesas Electronics disclaims any and all liability for any losses and damages incurred by you or third parties arising from the use of these circuits, software, or information.
2. Renesas Electronics hereby expressly disclaims any warranties against and liability for infringement or any other claims involving patents, copyrights, or other intellectual property rights of third parties, by or arising from the use of Renesas Electronics products or technical information described in this document, including but not limited to, the product data, drawings, charts, programs, algorithms, and application examples.
3. No license, express, implied or otherwise, is granted hereby under any patents, copyrights or other intellectual property rights of Renesas Electronics or others.
4. You shall not alter, modify, copy, or reverse engineer any Renesas Electronics product, whether in whole or in part. Renesas Electronics disclaims any and all liability for any losses or damages incurred by you or third parties arising from such alteration, modification, copying or reverse engineering.
5. Renesas Electronics products are classified according to the following two quality grades: "Standard" and "High Quality". The intended applications for each Renesas Electronics product depends on the product's quality grade, as indicated below.
"Standard": Computers; office equipment; communications equipment; test and measurement equipment; audio and visual equipment; home electronic appliances; machine tools; personal electronic equipment; industrial robots; etc.
"High Quality": Transportation equipment (automobiles, trains, ships, etc.); traffic control (traffic lights); large-scale communication equipment; key financial terminal systems; safety control equipment; etc.
Unless expressly designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not intended or authorized for use in products or systems that may pose a direct threat to human life or bodily injury (artificial life support devices or systems; surgical implantations; etc.), or may cause serious property damage (space system; undersea repeaters; nuclear power control systems; aircraft control systems; key plant systems; military equipment; etc.). Renesas Electronics disclaims any and all liability for any damages or losses incurred by you or any third parties arising from the use of any Renesas Electronics product that is inconsistent with any Renesas Electronics data sheet, user's manual or other Renesas Electronics document.
6. When using Renesas Electronics products, refer to the latest product information (data sheets, user's manuals, application notes, "General Notes for Handling and Using Semiconductor Devices" in the reliability handbook, etc.), and ensure that usage conditions are within the ranges specified by Renesas Electronics with respect to maximum ratings, operating power supply voltage range, heat dissipation characteristics, installation, etc. Renesas Electronics disclaims any and all liability for any malfunctions, failure or accident arising out of the use of Renesas Electronics products outside of such specified ranges.
7. Although Renesas Electronics endeavors to improve the quality and reliability of Renesas Electronics products, semiconductor products have specific characteristics, such as the occurrence of failure at a certain rate and malfunctions under certain use conditions. Unless designated as a high reliability product or a product for harsh environments in a Renesas Electronics data sheet or other Renesas Electronics document, Renesas Electronics products are not subject to radiation resistance design. You are responsible for implementing safety measures to guard against the possibility of bodily injury, injury or damage caused by fire, and/or danger to the public in the event of a failure or malfunction of Renesas Electronics products, such as safety design for hardware and software, including but not limited to redundancy, fire control and malfunction prevention, appropriate treatment for aging degradation or any other appropriate measures. Because the evaluation of microcomputer software alone is very difficult and impractical, you are responsible for evaluating the safety of the final products or systems manufactured by you.
8. Please contact a Renesas Electronics sales office for details as to environmental matters such as the environmental compatibility of each Renesas Electronics product. You are responsible for carefully and sufficiently investigating applicable laws and regulations that regulate the inclusion or use of controlled substances, including without limitation, the EU RoHS Directive, and using Renesas Electronics products in compliance with all these applicable laws and regulations. Renesas Electronics disclaims any and all liability for damages or losses occurring as a result of your noncompliance with applicable laws and regulations.
9. Renesas Electronics products and technologies shall not be used for or incorporated into any products or systems whose manufacture, use, or sale is prohibited under any applicable domestic or foreign laws or regulations. You shall comply with any applicable export control laws and regulations promulgated and administered by the governments of any countries asserting jurisdiction over the parties or transactions.
10. It is the responsibility of the buyer or distributor of Renesas Electronics products, or any other party who distributes, disposes of, or otherwise sells or transfers the product to a third party, to notify such third party in advance of the contents and conditions set forth in this document.
11. This document shall not be reprinted, reproduced or duplicated in any form, in whole or in part, without prior written consent of Renesas Electronics.
12. Please contact a Renesas Electronics sales office if you have any questions regarding the information contained in this document or Renesas Electronics products.
(Note 1) "Renesas Electronics" as used in this document means Renesas Electronics Corporation and also includes its directly or indirectly controlled subsidiaries.
(Note 2) "Renesas Electronics product(s)" means any product developed or manufactured by or for Renesas Electronics.

(Rev.4.0-1 November 2017)



SALES OFFICES

Renesas Electronics Corporation

<http://www.renesas.com>

Refer to "<http://www.renesas.com/>" for the latest and detailed information.

Renesas Electronics America Inc.
1001 Murphy Ranch Road, Milpitas, CA 95035, U.S.A.
Tel: +1-408-432-8888, Fax: +1-408-434-5351

Renesas Electronics Canada Limited
9251 Yonge Street, Suite 8309 Richmond Hill, Ontario Canada L4C 9T3
Tel: +1-905-237-2004

Renesas Electronics Europe Limited
Dukes Meadow, Millboard Road, Bourne End, Buckinghamshire, SL8 5FH, U.K
Tel: +44-1628-651-700, Fax: +44-1628-651-804

Renesas Electronics Europe GmbH
Arcadiastrasse 10, 40472 Düsseldorf, Germany
Tel: +49-211-6503-0, Fax: +49-211-6503-1327

Renesas Electronics (China) Co., Ltd.
Room 1709 Quantum Plaza, No.27 ZhichunLu, Haidian District, Beijing, 100191 P. R. China
Tel: +86-10-8235-1155, Fax: +86-10-8235-7679

Renesas Electronics (Shanghai) Co., Ltd.
Unit 301, Tower A, Central Towers, 555 Langao Road, Putuo District, Shanghai, 200333 P. R. China
Tel: +86-21-2226-0888, Fax: +86-21-2226-0999

Renesas Electronics Hong Kong Limited
Unit 1601-1611, 16/F., Tower 2, Grand Century Place, 193 Prince Edward Road West, Mongkok, Kowloon, Hong Kong
Tel: +852-2265-6688, Fax: +852-2886-9022

Renesas Electronics Taiwan Co., Ltd.
13F, No. 363, Fu Shing North Road, Taipei 10543, Taiwan
Tel: +886-2-8175-9600, Fax: +886-2-8175-9670

Renesas Electronics Singapore Pte. Ltd.
80 Bendemeer Road, Unit #06-02 Hyflux Innovation Centre, Singapore 339949
Tel: +65-6213-0200, Fax: +65-6213-0300

Renesas Electronics Malaysia Sdn.Bhd.
Unit 1207, Block B, Menara Amcorp, Amcorp Trade Centre, No. 18, Jln Persiaran Barat, 46050 Petaling Jaya, Selangor Darul Ehsan, Malaysia
Tel: +60-3-7955-9390, Fax: +60-3-7955-9510

Renesas Electronics India Pvt. Ltd.
No.777C, 100 Feet Road, HAL 2nd Stage, Indiranagar, Bangalore 560 038, India
Tel: +91-80-67208700, Fax: +91-80-67208777

Renesas Electronics Korea Co., Ltd.
17F, KAMCO Yangjae Tower, 262, Gangnam-daero, Gangnam-gu, Seoul, 06265 Korea
Tel: +82-2-558-3737, Fax: +82-2-558-5338