

Programmable Gain Element Using the **AD5450/AD5451/AD5452/AD5453** Current Output DAC Family

CIRCUIT FUNCTION AND BENEFITS

In applications where the digital-to-analog (DAC) output voltage range is required to be larger than the input voltage, use a programmable gain circuit. This circuit provides a programmable gain function using a multiplying DAC, the

AD5450/AD5451/AD5452/AD5453, and a fast, low offset operational amplifier, the **AD8065**. External resistors set the maximum gain value and the temperature coefficient, and the DAC resolution sets the programmable gain.

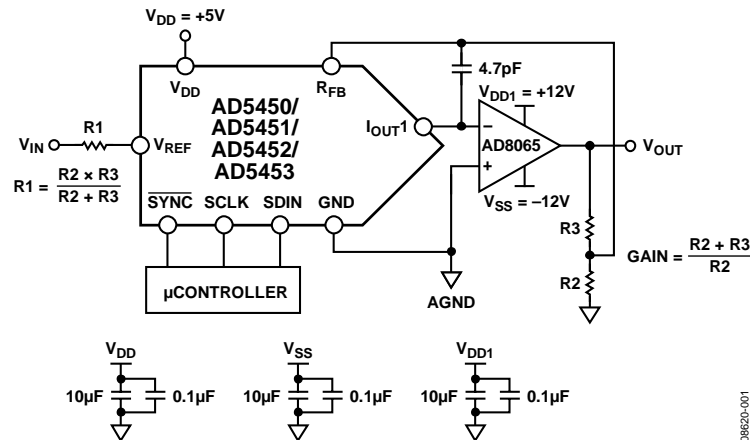


Figure 1. Programmable Gain Circuit Using a Current Output DAC (Simplified Schematic; Decoupling and All Connections Not Shown)

TABLE OF CONTENTS

Circuit Function and Benefits.....	1	Common Variations.....	3
Revision History	2	References.....	3
Circuit Description.....	3		

REVISION HISTORY

11/2017—Rev. A to Rev. B

Changed Document Title from CN0055 to AN-1511... Universal	
Changes to the Circuit Function and Benefits Section	1
Changes to the Circuit Description Section	3
Changes to the Common Variations Section	3

11/2009—Rev. 0 to Rev. A

Updated Format.....	Universal
---------------------	-----------

1/2009—Revision 0: Initial Version

CIRCUIT DESCRIPTION

The circuit shown in Figure 1 is the recommended method of increasing the gain of the circuit. It is recommended that R1, R2, and R3 all have similar temperature coefficients, but they do not need to match the temperature coefficients of the DAC. This approach is recommended in circuits where gains of greater than one are required.

Use Equation 1 to find the output voltage.

$$V_{OUT} = -Gain \times V_{IN} \times \frac{D}{2^N} \quad (1)$$

where:

D is the digital word loaded to the DAC. $D = 0$ to 255 (8-bit [AD5450](#)). $D = 0$ to 1023 (10-bit [AD5451](#)). $D = 0$ to 4095 (12-bit [AD5452](#)). $D = 0$ to 16383 (14-bit [AD5453](#)).

N is the number of bits.

The key benefit of this circuit is its ability to overcome gain temperature coefficient (TC) errors using resistor matching. The TC of the external resistors must match each other but does not need to match that of the DAC internal ladder resistance.

Resistor R1 is required because R1 plus the input impedance of the DAC must equal the total resistance feedback (RFB) plus $R2 \parallel R3$. The input impedance of the DAC is RFB, so

$$R1 + RFB = RFB + R2 \parallel R3 \quad (2)$$

$$R1 = R2 \parallel R3 \quad (3)$$

Choose the values of R1 and R2 so that that the output voltage does not exceed the output range of the operational amplifier for the given supply voltage. Also, note that the bias current of the operational amplifier is multiplied by the total feedback resistance ($RFB + R2 \parallel R3$) to give an associated offset. Thus, when the values of R1 and R2 are too large, they have a significant effect on the overall offset voltage.

The [AD5450/AD5451/AD5452/AD5453](#) products are designed on a complementary metal-oxide semiconductor (CMOS) process and operate from a V_{DD} power supply of 2.5 V to 5.5 V. The [AD8065](#) output amplifier in Figure 1 is driven from a dual power supply voltage (V_{DD1} and V_{SS}), which must be large enough

to accommodate the analog output range of the circuit. Generally, ± 12 V supplies are sufficient. The 4.7 pF capacitor prevents ringing or instability in the closed-loop application.

The input offset voltage of an operational amplifier (op amp) is multiplied by the variable noise gain (due to the code dependent output resistance of the DAC) of the circuit. A change in this noise gain between two adjacent digital codes produces a step change in the output voltage due to the input offset voltage of the amplifier. This output voltage change is superimposed on the desired change in output between the two codes and produces a differential linearity error, which if large enough, may cause the DAC to be nonmonotonic. The [AD8065](#) benefits from both a low input offset voltage and low bias currents to overcome this issue.

COMMON VARIATIONS

The [OP1177](#) is another excellent op amp candidate for the current to voltage (I to V) conversion circuit. It also provides low offset voltage and ultralow bias current. For the selection of the reference, the input voltage is restricted by the rail-to-rail voltage of the op amp selected and the gain set up by the R2 and R3 resistors.

REFERENCES

[ADIsimPower Design Tool](#).

Kester, Walt. 2005. *The Data Conversion Handbook*. Analog Devices. Chapter 3, 7.

MT-015 Tutorial, *Basic DAC Architectures II: Binary DACs*. Analog Devices.

MT-031 Tutorial, *Grounding Data Converters and Solving the Mystery of "AGND" and "DGND."* Analog Devices.

MT-033 Tutorial, *Voltage Feedback Op Amp Gain and Bandwidth*. Analog Devices.

MT-035 Tutorial, *Op Amp Inputs, Outputs, Single-Supply, and Rail-to-Rail Issues*. Analog Devices.

MT-101 Tutorial, *Decoupling Techniques*. Analog Devices.

[Voltage Reference Wizard Design Tool](#).