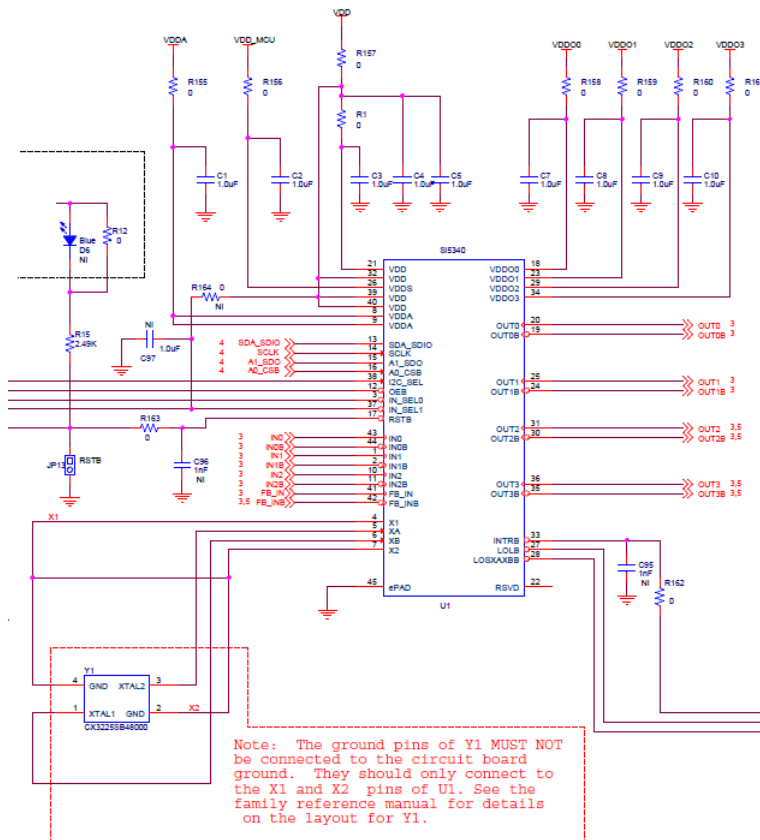


AN1051: Si534x/7x/8x/9x Schematic Review Checklist Application Note

This application note contains a schematic review checklist, which can be used as an initial step in evaluating a Si534x/7x/8x/9x schematic design. Considering the items listed in this document before committing to layout will contribute to a successful design.

Illustrated below is an excerpt from the Si5340-D-EB evaluation board schematic.



KEY POINTS

- This schematic review checklist application note applies to Silicon Labs Si534x/7x/8x/9x clock generators and jitter attenuators.
- This document addresses these topics:
 - Internal/External Crystal Reference
 - External XO/TCXO/OCXO Reference
 - Input Clocks
 - Output Clocks
 - Power Supply Distribution Network
 - Serial Communication
 - Digital I/O

1. Introduction

This schematic review checklist application note applies to Silicon Labs Si534x/7x/8x/9x devices. Examples of such devices are the Si5348, Si5372, Si5386 and Si5395.

Please review this checklist and consider each of the listed topics in your board's schematic design.

It is a good idea when getting started to make sure you have the latest documentation, especially the data sheet and reference manuals. These documents are all available from <http://www.silabs.com>. Evaluation board documentation such as for the Si5395-A-EVB are available at <https://www.silabs.com/documents/public/user-guides/ug335-si5395evb.pdf>.

Note that there are 2 reference documents that apply to every Si534x/7x/8x/9x device. The first is a Reference Manual (RM) or Family Reference Manual (FRM) that contains technical application details such as register programming and layout considerations for each device or device family. Examples are the <https://www.silabs.com/documents/login/reference-manuals/si5395-94-92-family.pdf> and the <https://www.silabs.com/documents/public/reference-manuals/si5348-e-family.pdf>. Unless otherwise noted, the terms RM or Reference Manual will refer to the device-specific reference document.

The second is a stand-alone crystal reference document that applies to *all* Si534x/7x/8x/9x devices. This is the [Si534x/8x Jitter Attenuators Recommended Crystal, TCXO, and OCXOs Reference Manual](#). It is essentially a list of approved crystals and crystal oscillators.

2. Checklist

The following is a checklist of items every designer should review in the schematic and layout.

- Output Clocks
- Input Clocks
- References
- Power Supply Distribution Network
- Serial Communication
- Digital I/O
- CBPro Project File

2.1 Output Clocks

The primary considerations here are proper output terminations, signal integrity, supporting ZDM (Zero Delay Mode) if necessary, and optimizing output clock placement. Please consider using the "Clock Placement Wizard" in CBPro to ensure the output placement is optimized to minimize crosstalk.

1. LVDS Format Output Termination

- LVDS output clocks may be AC coupled or DC coupled
- A 100 ohm differential termination must be used, according to [Figure 2.1 DC Coupled LVDS on page 4](#) and [Figure 2.2 AC Coupled LVDS/LVPECL/Custom Differential on page 4](#). The termination may either be internal to the destination device or an external resistor.

 


Figure 2.1. DC Coupled LVDS

 


Figure 2.2. AC Coupled LVDS/LVPECL/Custom Differential

2. LVPECL Format Output Termination

- LVPECL output clocks must be AC coupled
- 100 ohm differential termination should be used, according to [Figure 2.2 AC Coupled LVDS/LVPECL/Custom Differential on page 4](#). The termination may either be internal to the destination device or an external resistor.
- Shunt resistors to ground or series resistors should NOT be added, according to [Figure 2.3 Shunt Resistors at Source Should NOT Be Used on page 4](#).

 


Figure 2.3. Shunt Resistors at Source Should NOT Be Used

3. CML Format Output Termination

- CML output clocks must be AC coupled.
- 50 ohm termination resistors should be applied to each leg, according to [Figure 2.4 AC Coupled CML Termination on page 5](#).

 


Figure 2.4. AC Coupled CML Termination

- Pull-up resistors at the source should NOT be added, according to [Figure 2.5 Incorrect CML Termination on page 5](#).

 


Figure 2.5. Incorrect CML Termination

4. HCSL Format Output Termination

- HCSL output clocks must be AC coupled.
- The resistor divider termination network in [Figure 2.6 AC Coupled HCSL on page 5](#) should be used. This serves to (1) provide 50 ohm termination to each leg and (2) bias the common-mode level of the HCSL signal to the desired level.

 


Figure 2.6. AC Coupled HCSL

- Shunt resistors to ground or series resistors at the source should NOT be added, according to [Figure 2.7 Incorrect HCSL Terminations on page 6](#).
- DC coupling the output clock with 50 ohms to ground should NOT be done, according to [Figure 2.7 Incorrect HCSL Terminations on page 6](#).

 


Figure 2.7. Incorrect HCSL Terminations

5. Custom Differential Format Output Termination

- Custom differential output clocks must be AC coupled.
- 100 ohm differential termination should be used, according to [Figure 2.2 AC Coupled LVDS/LVPECL/Custom Differential on page 4](#). The termination may either be internal to the destination device or an external resistor.

6. CMOS Format Output Termination

- Series or near end source termination may be required for CMOS outputs. Please see the Reference Manual for the recommended resistor value.
- Differential clocks provide higher performance than CMOS clocks. Please see application note [AN862: Optimizing Si534x Jitter Performance in Next Generation Internet Infrastructure Systems](#).

7. ZDB Mode

- If the device supports ZDB mode, route the nearest shortest route output clock fed back to IN3/FB_IN. Input and output pin polarities are such that no vias are needed to make this connection. The application must get polarity correct.

2.2 Input Clocks

The primary considerations here are signal integrity and optimizing input clock placement.

1. AC-coupling caps per RM recommendations? Ensure that AC coupling capacitors have <math>< 5\ \Omega</math> capacitive reactance at the input clock frequency.
2. Review input terminations per RM recommendations?
3. Input clock connections correct for CMOS? Make sure the Project File selects the Standard input buffer. The Pulsed LVCMOS buffer is only used by exception for low frequency ($\leq 1\ \text{MHz}$) low duty cycle single-ended DC-coupled LVCMOS. Refer to the RM for the recommended termination network to keep the signal at INx within the absolute maximum voltage levels: $-1\text{V} < \text{INx} < 3.8\text{V}$.
4. Please consider the use of a "split termination" for input differential clock signals if the board may be noisy and there is room to do so. A split termination for input clocks is a conservative approach to common-mode (CM) noise suppression. It is a modification of the standard textbook terminations described in the Reference Manual and is discussed in the Knowledge Base article, "[Terminating Differential Transmission Lines to Minimize CM Noise](#)." Below is an illustration modified after the diagram cited in that article.


 


Figure 2.8. Example Split Termination

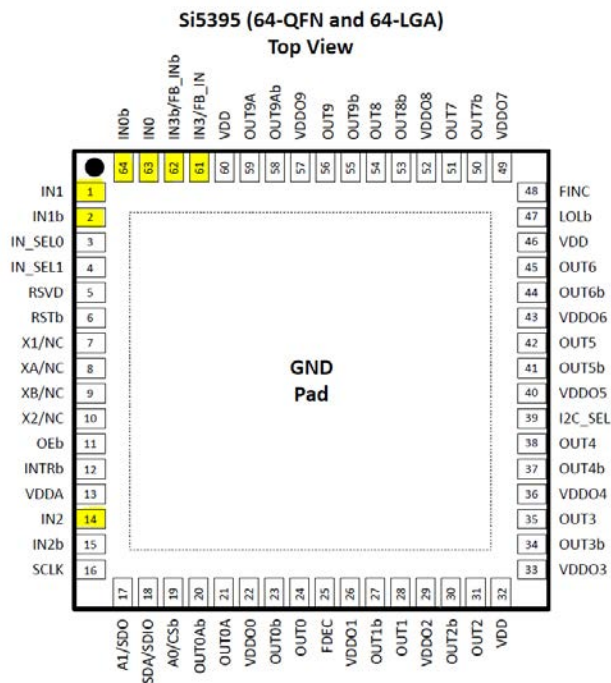5. Connection to the single-pin CMOS clock inputs on Si5348 IN3/IN4 correct per RM?
6. In general, input clock selections are preferred based on maximum distance from XA/XB pins. This reduces the possibility of XA/XB crosstalk to input clock traces in the PCB. For example, see the following figure taken from the Si5395 data sheet.



In this specific example, proximity and orthogonality to the XA and XB pins suggest the preferred input clocks in order would be IN3, IN0, IN1, IN2.

7. If the unused input clocks are declared as being unused in the CBPro project file, their pins can be left as "no connect". AC coupling the unused inputs to ground is also permissible but not required.

8. If the unused input clocks are not declared as being unused in the CBPro project file, then one side of the pair should be pulled up with a resistor, and the other side of the pair should be pulled low with a resistor. But it is always preferable to declare the unused input clocks as unused in the CBPro project file.

2.3 External Crystal/ OCXO,TCXO,XO External Reference/ Internal Reference Device

A crystal or external reference clock is required to be connected at the XA/XB pins for all the jitter attenuators and independent (i.e., no output clock) clock generators. The crystal or external reference determines the close-in phase noise of the output clocks. The items listed here are intended to ensure that the crystal operates properly and that external noise is minimized.

2.3.1 External Crystal Reference

1. Does the crystal selected as the external reference meet the datasheet parameters such as frequency, equivalent series resistance, and shunt capacitance? For a list of suitable crystals, see the *Si534x/8x Jitter Attenuators Recommended Crystal, TCXO and OCXOs Reference Manual* <https://www.silabs.com/documents/public/reference-manuals/si534x-8x-9x-recommended-crystals-rm.pdf>
2. Crystal connected directly to the device's XA and XB pins? Please see the applicable device reference manual for layout details.
3. Make sure that the crystal pins designated X1 and X2 are **not** connected to PCB GND. The guard ring around the crystal connects to the device's X1 and X2 pins only.
4. Make sure there are no crystal external load capacitors.

2.3.3 External Reference Applied to REF/REFb Pins

An external reference may be applied to the REF/REFb pins of the Si5348/88/89 devices.

1. Selection appropriate? The external reference applied to the REF/REFb pins should have the necessary accuracy, wander, and stability for the required application. See application note AN905: *Si534x External References: Optimizing Performance* for guidance at <http://www.silabs.com/support%20documents/technicaldocs/an905.pdf>. For a list of suitable TCXOs/OCXOs, please see the *Si534x/8x Jitter Attenuators Recommended Crystal, TCXO and OCXOs Reference Manual* at <https://www.silabs.com/documents/public/reference-manuals/si534x-8x-9x-recommended-crystals-rm.pdf>
2. AC-coupling caps per RM recommendations?
3. Terminations correct per RM recommendations?
4. Single-ended external references should be connected to the REF pin and not the REFb pin. The unused REFb pin should be bypassed to ground with a capacitor.
5. Because of slow rise/fall times, it is always preferable to avoid using clipped sine wave TCXOs and OCXOs. Instead, the outputs should be CMOS.
6. When the REF pin is being driven by a CMOS signal, it is important to include a feed forward cap in the attenuator circuit, per RM recommendation.
7. When the REF pin is being driven by a CMOS signal, the TCXO/OCXO should be placed close to the REF pin.

2.3.4 Embedded Crystal Devices

Using one of the embedded crystal devices (grades J/K/L/M/E) simplify the schematic and layout since the crystal is internal to the chip. There are no external components required.

If one of the devices on the PCB is an embedded crystal device (e.g. Si5395J-A), be sure that the X1, XA, XB and X2 pins are "no connect" For the Si5395J, these are pins 7, 8, 9 and 10.

2.4 Power Supply Distribution Network

1. 1.8 V to VDD?
2. 3.3 V to VDDA?
3. 1.8, 2.5, or 3.3 V to VDDOn?

Note: "VDDOn" here refers to the VDDO for each output clock buffer. For example, the Si5345 has VDDO0, VDDO1, ... VDDO9.

4. Bypass Capacitors are, generally, not critical. Here are some guidelines:
 - a. VDD: 1 μ F per pin, as close as possible. (The customer EVB uses 1 μ F//0.1 μ F//series to an inductor and shunt 0.1 μ F.)
 - b. VDDA: 1 μ F per pin, as close as possible.
 - c. VDDOn: 1 μ F per pin, as close as possible.
5. Ferrite Bead or Inductor
 - a. Series connected ferrite beads and inductors are usually not needed. However, including zero ohm resistors in the PCB layout to isolate the power supply pins is prudent. The suggested resistor size is 0603 so that a ferrite bead can be accommodated in the footprint if necessary.
 - b. If you have a series ferrite bead or inductor, you may want to consider adding additional bulk capacitance.
 - c. The CEVB 30 Ω inductor on VDD is not needed.

2.5 Serial Communication

1. Are the connections correct for I²C, 3-wire, or 4-wire SPI?
2. If I²C is used, are the bus pull-up resistors present? Only 1 set of resistors should be used (no duplicates with same bus on different schematic pages.)
3. Verify A0/A1 connections are unique for each Silicon Labs device on an I²C bus.
4. Consider including provisions for a male 10-pin header to support the Field Programmer. (Optional but recommended for Field Programmer support.)
5. Ensure that voltage level of the serial interface matches the bit IO_VDD_SEL, which is at addr 0x0943[0]. When the bit equals 0 the external connection should be 1.8V, and when the bit equals 1 the external connection should be 3.3V.

2.6 Digital I/O

1. External pullups and pulldowns:
 - a. Any digital inputs that must be pulled or tied externally? The following cannot be left floating when unused and must be pulled high or low when unused. Refer to the datasheet for further details.
 - i. Si5397: FDEC & OE1b
 - ii. Si5348: FDEC
 - iii. Si5347: FDEC & OE1b
 - b. To be conservative, an external pull-up or pull-down resistor can be added even if the device already has one, since the internal pull-ups and pull-downs are relatively weak. Refer to the datasheet for further details.
 - c. Any unnecessary and just waste power? GPIO outputs (e.g. LOLb, INTRb) are always actively driven high unless they are asserted, so pull-up/down resistors on these pins are unnecessary. Refer to the datasheet for details on each GPIO pin.
2. Recommend that even unused digital I/O be connected to at least a test pad, pin, or via just in case.
3. The status output signals (e.g., LOL) are capable of driving 2 mA. Check to be sure that their load does not demand more current.
4. Most digital inputs (e.g., OEB) have internal pull up/down resistors. Check the data sheet and if the correct pull up/down is in place, the pins can be "no connect".

2.7 CBPro Project File

The assignment of clock I/O, serial port, XAXB reference, etc, in the schematic should be checked against the CBPro project file(s) that will be used on the board.



ClockBuilder Pro

One-click access to Timing tools, documentation, software, source code libraries & more. Available for Windows and iOS (CBGo only).

www.silabs.com/CBPro



Timing Portfolio
www.silabs.com/timing



SW/HW
www.silabs.com/CBPro



Quality
www.silabs.com/quality



Support and Community
community.silabs.com

Disclaimer

Silicon Labs intends to provide customers with the latest, accurate, and in-depth documentation of all peripherals and modules available for system and software implementers using or intending to use the Silicon Labs products. Characterization data, available modules and peripherals, memory sizes and memory addresses refer to each specific device, and "Typical" parameters provided can and do vary in different applications. Application examples described herein are for illustrative purposes only. Silicon Labs reserves the right to make changes without further notice to the product information, specifications, and descriptions herein, and does not give warranties as to the accuracy or completeness of the included information. Without prior notification, Silicon Labs may update product firmware during the manufacturing process for security or reliability reasons. Such changes will not alter the specifications or the performance of the product. Silicon Labs shall have no liability for the consequences of use of the information supplied in this document. This document does not imply or expressly grant any license to design or fabricate any integrated circuits. The products are not designed or authorized to be used within any FDA Class III devices, applications for which FDA premarket approval is required, or Life Support Systems without the specific written consent of Silicon Labs. A "Life Support System" is any product or system intended to support or sustain life and/or health, which, if it fails, can be reasonably expected to result in significant personal injury or death. Silicon Labs products are not designed or authorized for military applications. Silicon Labs products shall under no circumstances be used in weapons of mass destruction including (but not limited to) nuclear, biological or chemical weapons, or missiles capable of delivering such weapons. Silicon Labs disclaims all express and implied warranties and shall not be responsible or liable for any injuries or damages related to use of a Silicon Labs product in such unauthorized applications.

Trademark Information

Silicon Laboratories Inc.®, Silicon Laboratories®, Silicon Labs®, SiLabs® and the Silicon Labs logo®, Bluegiga®, Bluegiga Logo®, ClockBuilder®, CMEMS®, DSPLL®, EFM®, EFM32®, EFR, Ember®, Energy Micro, Energy Micro logo and combinations thereof, "the world's most energy friendly microcontrollers", Ember®, EZLink®, EZRadio®, EZRadioPRO®, Gecko®, Gecko OS, Gecko OS Studio, ISOModem®, Precision32®, ProSLIC®, Simplicity Studio®, SiPHY®, Telegesis, the Telegesis Logo®, USBXpress®, Zentri, the Zentri logo and Zentri DMS, Z-Wave®, and others are trademarks or registered trademarks of Silicon Labs. ARM, CORTEX, Cortex-M3 and THUMB are trademarks or registered trademarks of ARM Holdings. Kell is a registered trademark of ARM Limited. Wi-Fi is a registered trademark of the Wi-Fi Alliance. All other products or brand names mentioned herein are trademarks of their respective holders.



Silicon Laboratories Inc.
400 West Cesar Chavez
Austin, TX 78701
USA

<http://www.silabs.com>