


PRACTICAL

# ELECTRONICS

DECEMBER 1973

20p

## PARTY STROBE LIGHT

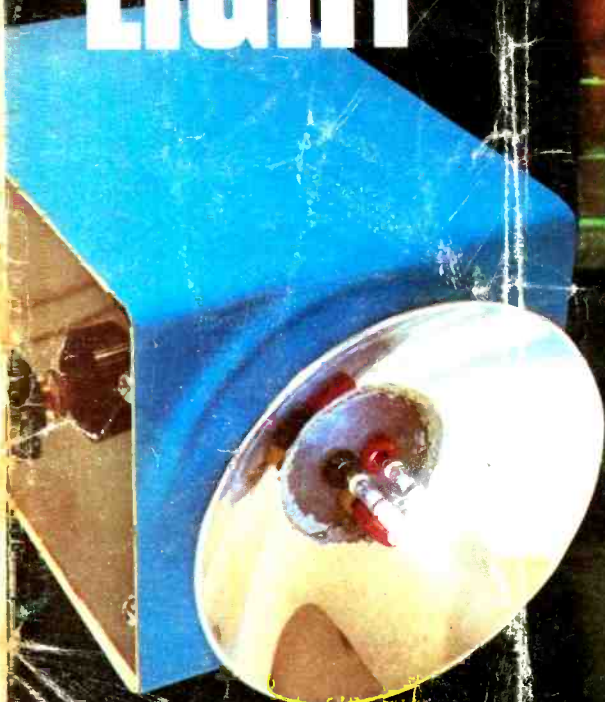


*...and* **VOICE  
OPERATED  
FADER**

**2 PROJECTS FOR PARTIES AND DISCOTHEQUES**

# This Christmas

if your imagination stops at cigars...

...give Antex

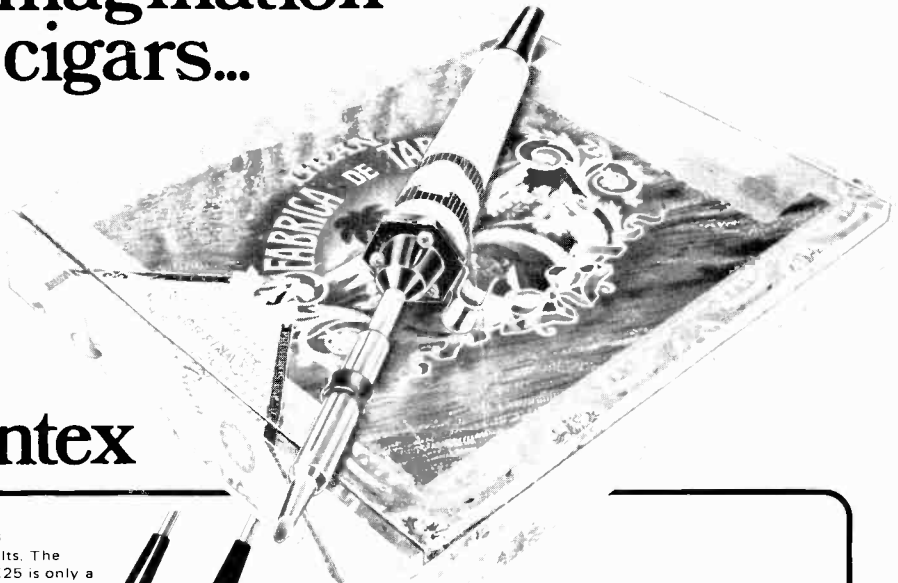

## MODEL X25 Soldering Irons

220-240 Volts or 100-120 Volts. The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live". Tested at 1500v. A.C. This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long life iron-coated bit 1/8". 2 other bits available 3/32" and 3/16". Totally enclosed element ceramic and steel shaft. Bits do not "freeze" and can easily be removed. PRICE £1-93 (rec. retail) P & P 8p. Suitable for production work and as a general purpose iron.



## MODEL CCN

229 volts or 240 volts. The 15 watt miniature model CCN also has negligible leakage. Test voltage 4000v. A.C. Totally enclosed element in ceramic shaft. Fitted long life iron-coated bit 3/32". 4 other bits available 1/8", 3/16", 1/4" and 3/64". PRICE £2-15 (rec. retail) P & P 5p.

MODEL G 18 watt miniature iron, fitted with long-life iron coated bit 3/32". Voltage 240, 220 or 110. PRICE £2-15. (rec. retail) P & P 5p.



MODEL CN Miniature 15 watt soldering iron fitted 3/32" iron coated bit. Many other bits available from 3/64", to 3/16". Voltages 240, 220, 110, 50 or 24. PRICE £1-93. (rec. retail) P & P 5p.





all prices include VAT at 10%


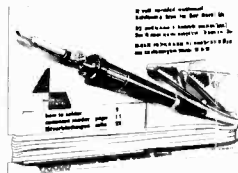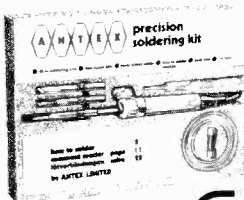
## MODEL SK.2 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32" heat sink, solder, stand and "How to Solder" booklet. PRICE: £2-87. (rec. retail) P & P 8p.



## MODEL MLX KIT

Battery operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder". PRICE £2-27 (rec. retail) P & P 12p.

## MODEL SK.1 KIT

Contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet. PRICE £3-25 (rec. retail) P & P 12p.



From radio or electrical dealers, car accessory shops or in case of difficulty direct from—  
**ANTEX LTD. FREEPOST**  
(no stamp required) **PLYMOUTH**  
**PL1 1BR** Tel: 0752 67377.

Please send the following

.....  
enclose cheque/P.O./Cash (Giro No. 2581000)

NAME .....

ADDRESS .....

PE12

# PRACTICAL ELECTRONICS

VOLUME 9 No. 12 DECEMBER 1973

---

## CONSTRUCTIONAL PROJECTS

- PARTY STROBE** *by M. J. Hughes*  
Freeze motion with this party light 1054
- VOICE OPERATED FADER** *by A. J. Russell*  
Fit "talkthrough" to your discotheque 1057
- P.E. RONDO QUADRAPHONIC SOUND SYSTEM—4** *by R. A. Cole*  
Continuing the mechanical construction and wiring 1072
- P.E. SOUND SYNTHESIZER—11** *by G. D. Shaw*  
Hold, modulation amplifiers, mixer and envelope shaper for keyboard unit 1082
- 9V BATTERY ELIMINATOR** *by A. M. Rudkin*  
A nine volt power-pack in a battery case 1090

## GENERAL FEATURES

- PHASE LOCKED LOOPS—3** *by J. B. Dance*  
Applications of phase locked loop integrated circuits 1060
- LOGIC TUTOR EXPERIMENTS—8** *by M. J. Hughes*  
The full adder 1070
- INGENUITY UNLIMITED**  
Trace Doubler for TTL — Variable Pulse Circuit — Tachometer —  
Screenwasher Timing Unit — Mains Neon Flasher 1093

## NEWS AND COMMENT

- EDITORIAL—Twenty-five Years On** 1053
- BOOK REVIEWS**  
Selected new books we have received 1071
- SPACEWATCH** *by Frank W. Hyde*  
Radio Stars—Siberian Meteorite—Skylab Preliminary Results 1081
- STRICTLY INSTRUMENTAL** *by K. Lenton-Smith*  
Comments on contemporary sounds 1087
- VIEW POINT**  
A reader comments on quadraphony 1097
- INDUSTRY NOTEBOOK** *by Nexus*  
What's happening inside industry 1098
- TRANSISTORS AND CONSTRUCTORS** *by D. Bollen*  
A look back to the early days of the transistor 1101
- PATENTS REVIEW**  
Thought provoking ideas on file at the British Patents Office 1103

Our January issue will be published on Friday, December 14, 1973

---

© IPC Magazines Limited 1973. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, to any part of the world, £2-65. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

# TO SPARK YOUR IMAGINATION!

Kit comprises **EVERYTHING**: Case, cables, coil connectors, Silicon grease, 8-page instruction leaflet.



## the **SPARKRITE** Electronic Ignition Kit only £9.35

Fascinating to build. Fantastic improvement to your car's performance. Complete Capacitive Discharge ignition system, fully proven, components fully guaranteed. Printed circuit design. All metalwork drilled ready. Fitted to car in 15 minutes when built.

- Sustained peak performance. • Up to 20% fuel saving.
- Instant all-weather starting. Faster acceleration, higher top speed.
- Suitable for all engines up to 8 cyls. • Longer spark plug life. • Longer battery life. • Contact breaker burn eliminated. • Purer exhaust gas emission.

A new development from the manufacturers of Gunton Ignition. Price: £9.35 inc. V.A.T. and postage. (12 volt only. State Pos. or Neg. earth). Ready built unit also available £11.55 inc. V.A.T. and postage. **GUARANTEED 5 YEARS.**

**ORDER NOW** To: ELECTRONICS DESIGN ASSOCIATES, 82 Bath Street, Walsall WS1 3DE. Phone: 33652

Please send me one SPARKRITE Kit complete. I enclose P.O./Cheque for £9.35. Or for ready built unit £11.55.

NAME

ADDRESS

(Live near Walsall? Call in for an actual workshop demo. It really is convincing).

PE12

# DISCOUNTS UP TO

# 60%

**FULL 12 MONTH AFTER SALES SERVICE ON PARTS AND LABOUR**  
PLEASE ASK ABOUT OUR 2 YEAR SERVICE CONTRACT

ALL PRICES ARE INCLUSIVE OF V.A.T.

## FANTASTIC OFFER GARRARD SP25 Mk III.

Goldingr G800. Teak finish, plinth and tinted cover with mains lead and DIN plug and screened lead. All fully wired. Please add £1.75 for P. & P. and Ins. **£14.95**

## TURNTABLES

Please add 95p P. & P. & Ins.

BSR MP60	£9.25
Garrard SP25 Mk.III	£9.95
Garrard SL65B	£12.95
Garrard AP76	£16.65
Garrard 401	£27.50
Garrard Zero 100 (Single)	£30.95
Garrard Zero 100 (Auto)	£34.95
Goldingr GL85/P P & C	£65.95
Goldingr G101/P P & C	£21.95
Goldingr GL72	£24.95
Goldingr GL72/P	£31.95
Goldingr GL75	£30.95
Goldingr GL75/P	£38.95
Goldingr GL75 Lid	£4.25
Thorens TD125	£60.95
Thorens TD125 AB Mk.II	£93.95
Thorens TD160 AB & C	£51.95
Thorens TD165 AB & C	£45.95
Condor Auto Cleaner (Star Value)	£1.40 P. & P. 15p

## TUNERS

Please add 95p P. & P. & Ins.

Alpha Highgate FT150	£32.95
Amstrad Multiplex 3000	£33.90
Metrosound FMS 20 Mk. II	£37.75
Metrosound FMS 40	£37.75
Philips RH 621	£72.95
Rogers R/brook FET 4 (Cha)	£32.95
Rogers R/brook FET 4 (Cased)	£36.50
Sinclair cased tuner	£27.50
Teleton GT202 (N/P)	£32.95

## SPEAKERS

£1.65 for P. & P. (Per Pair)

Amstrad Acoustra 1500	£62.90
Amstrad Acoustra 2500	£30.75
Celestion Ditton 15	£50.75
Celestion Ditton 44	£79.45
Goodmans D/Maxim	£40.95
Goodmans Mezo 3	£50.95
Goodmans Havant	£35.25
Keltron KS4	£13.85
Keltron KS8	£22.50
Sinclair Q16	£11.95
Sinclair Q30	£30.95
Wharfedale Denton II	£62.80

## SPEAKER UNITS

Wharfedale Linton Kit	£16.85
Wharfedale Glendale Kit	£29.95
Wharfedale Unit 3	£16.30
Wharfedale Unit 4	£28.70
Wharfedale Dovedale Kit	£44.95

All prices correct at time of press (E. & O. E.) and are subject to alterations



# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. PE12, 174 Pentonville Road, London, N1. Tel. 01-278 1769  
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue Ilford, Essex. Tel. 01-550 1086

Open Monday to Saturday 9.30 a.m. to 6 p.m. **LATE NIGHT FRIDAY 7 p.m.**

**MAIL ORDERS.** Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

## AMPLIFIERS

Please add 95p P. & P. & Ins.

Amstrad 8000 Mk. II	£18.85
Amstrad IC2000 Mk. II	£32.15
Amstrad Integra 4000	£23.95
Alpha Highgate FA400	£39.05
Global 10 + 10	£19.75
Global 20 + 20	£25.95
Keltron 1000	£22.95
Keltron 1500	£25.75
Metrosound ST20E Mk. II	£28.95
Metrosound ST60	£51.95
Rogers R/brook (Ch)	£41.15
Rogers R/brook Mk. III (Ca)	£44.50
Rogers R/bourne (Ch)	£54.25
Rogers R/bourne (Ca)	£56.95
Sinclair 2000	£24.90
Sinclair 3000	£44.95
Sinclair 605	£21.45
Sinclair PRO 60 2 x Z30/PZ5	£16.40
Sinclair PRO 60 2 x Z30/PZ6	£19.45
Sinclair PRO 2 x Z50/PZ8	£25.25
Trans	£25.25
Sinclair AFU Pro80 (Filter Unit)	P.O.A.

Sinclair Stereo 80 Pre-amp P.O.A.  
Sinclair Z30 Amp £3.85  
Sinclair Z50 Amp £4.50  
Sinclair PZ5 Power Supp £4.20  
Sinclair PZ6 Power Supp £6.15  
Sinclair PZ8 Mains Trans £4.95  
Sinclair PZ8 Power Supp £6.15

## TUNER/AMPLIFIERS

Please add £1.10 P. & P. & Ins.

Alpha FR 3000	£61.35
Goodmans Module 80	£62.95
Goodmans Mod 80 Com	£109.95
Goodmans Mod 90	£76.95
Goodmans One-Ten	£92.95
Rogers R/brook (Cha)	£61.95
Rotel 150A	£45.25
Rotel 200A	£57.95
Status STA160	£89.95

## PLINTH & COVERS

£3.35  
For Garrard SP25, 2025 TC, 3000, BSR, McDonald, MP60 £3.08 P. & P. 71p. For AP76, SL72B, SL95B, etc. £4.85 + 71p P. & P.

## CARTRIDGES

Please add 11p P. & P. & Ins.


Goldingr G850	£2.75
Goldingr G800	£3.50
Goldingr G800E	£6.30
Goldingr G800SE	£10.90
Shure M3D	£3.25
Shure M44E	£4.95
Shure M55E	£5.00
Shure 75ED Type 2	£9.25
Shure V15	£25.95
Shure M75EJ Type 2	£7.95
Sonotone 9 TAMC	£1.20
Sonotone V 200E	£8.55
Audio Technica AT66	£3.15
ADC 10E Mk IV	£14.95
Ronette SM500/7	£5.25
Ronette SM500/E	£7.95



# VERO

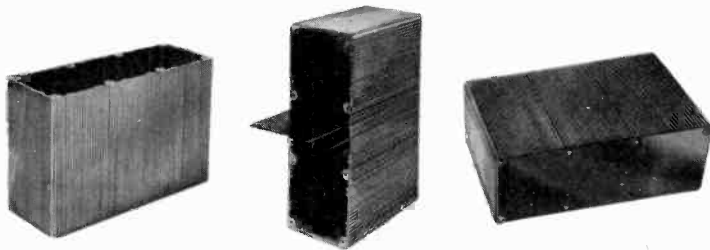
## products available from your local retailer

to assist with all types of home constructor projects



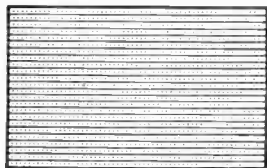
**verobox®**

Six standard sizes of extruded box with built-in guide slots



**Veroboard®**

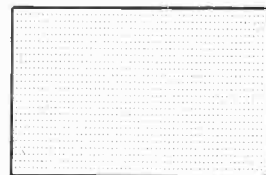
0.1" and 0.15" pitch  
Single-sided, copper clad



Plain boards.  
0.1" and 0.15" pitch.



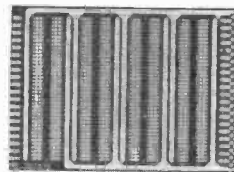
Group Boards for simple component mounting  
0.1" and 0.15" pitch.



D.I.P. Breadboards are the easiest way of mounting your D.I.P.'s.  
0.1" pitch.



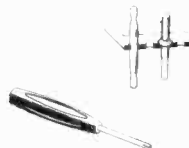Spot-face cutter to simplify cutting of copper track.



Terminal pins for 0.1" and 0.15" pitch boards together with pin insertion tool.

**VERO ELECTRONICS LIMITED**

Industrial Estate, Chandler's Ford, Hampshire SO5 32R  
Chandler's Ford 2952

Telex 47551

# Exciting...the Stereo 21!

Can you really get sound quality like this **FOR LESS THAN £19? YES, YOU CAN! WITH THE NEW**

**STEREO 21**

Until now, richly satisfying sound has always cost a richly satisfying price. *But not any more!* For an almost unbelievable **£18·45**, you can have Stereo 21—audio for the connoisseur! Whatever your taste in music, you can hear it on STEREO 21 the way its composers heard it in their dreams! Beethoven or Mahler . . . Ellington or Jellyroll Morton . . . Das Nibelung or Jesus Christ Superstar . . . Carols from King's College Chapel or the return of a Beatle . . . everything from a prettily fluting baroque organ to the newest pop group at full throttle—STEREO 21 does them all justice!



And have you ever seen a handsomer audio installation? Compact enough to go in a university student's bedroom-study, elegant enough for the suavest penthouse pad in Town, STEREO 21 offers you all the pride of possession as well as a thrilling musical experience!

Top-quality amplifier, BSR turntable, matching speakers. Deck and speaker cabinets you simply wrap round and glue to build. Screw in the amplifier and connect up (all push fit no soldering whatsoever), so simple literally anyone can do it. Except for glue and panel pins all parts supplied including full instructions—all for **£18·45** (plus the cost of post and packing if you buy by mail), and—to round it all off—a money refund if not

satisfied if your pleasure in STEREO 21 is not complete!

**Just think—In only a few days you could be giving your ears the treat of a lifetime—AND introducing your envlous friends to STEREO 21!**

Power Output 2·7 watts per channel and headphone socket with automatic cut-out. Provision for auxiliary inputs—radio, tape, etc., and output for taping discs. Overall dimensions: Speakers approx. 15½ × 8 × 4 in. Complete deck and cover enclose position approx. 15½ × 12 × 6 in.

Personal shoppers and mail order price

**£18·45** INCLUDING VAT / plus £1·60 p. & p.


Diamond stylus, if required, £1·37 extra

Specially selected pair of stereo headphones with individual level controls, and padded earpieces to give optimum. £3·85.

## EMI SPEAKERS AT UNBELIEVABLE PRICES

**950 Kit.** Five matched speakers and crossover unit for handling up to 45 watts, from 20 to 20,000 Hz. Huge—19in × 14in (approx.) high efficiency 16, 500-gauss bass unit built on a heavy diecast frame. The four 10,000 gauss tweeters, each 3½in dia. approx., are fed by the crossover with a critically adjusted signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2in others 0·5in. Recommended list price £44.

**OUR PRICE £25·00 + £1·50 p. & p.**

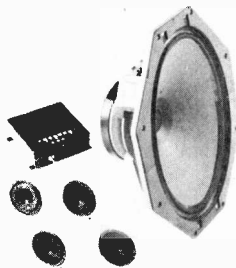

**15in 14A/780.** Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz. Flux 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3in voice coil.

Recommended retail price £40·80.

**OUR PRICE £18·70**  
+ £1·50 p. & p.

**RADIO AND TV COMPONENTS (ACTON) LTD, 21D HIGH STREET ACTON, LONDON W3 6NG · 323 EDGWARE ROAD, LONDON W2**

Edgware: 9 a.m. to 5.30 p.m., half day Thurs.  
Acton: 9.30 a.m. to 5 p.m. Closed all day Wed.; also see opposite.

Mail orders to Acton. Terms C.W.O. All enquiries Stamped Addressed Envelope. Goods not despatched outside U.K.



# RTVC VISCOUNT III

## a boost in the output.

VISCOUNT III now gives you an imposing 20 watts per channel—and the price quoted is actually INCLUSIVE OF VAT!

The money's important, of course, but not nearly so important as *value for money!* And that's something you get in abundance with VISCOUNT III. We design it... we make it... we sell it direct to you—passing on all the economies that come from cutting out middle-men! That's the only way you can get so much quality for so little money!

The unique VISCOUNT III amplifier, plus the Garrard SP25 Mk III deck, plus the magnificent Duo Type III matched speakers (or Duo Type II for a small room) give you an audio installation that will prove unbeatable for listening pleasure! On the brushed aluminium front panel of the amplifier you'll find all the facilities you need—volume, bass, treble and balance controls, plus switches for mono/stereo, on/off function and bass and treble filters. Plus headphone socket on the back. And the teak finish will harmonise and enhance virtually any style of interior decor!

The heart-stopping timbre of Tom Jones at his most virile... the last lingering harmonics of a solo performance by Heifetz or Menuhin... the pathos and the panache of Liza Minelli... the majestic sonorities of the brass band and the elfin subtleties of the virtuoso clavichordist—hear every nuance with a fidelity that you have *never* experienced before!

Come and hear VISCOUNT III! If it's inconvenient to travel, buy by post in the confidence that you won't be disappointed (and with a 24-carat Money-Back Guarantee to give you extra reassurance). Don't settle for second-best!

**SPEAKERS:** Duo Type II Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10 watts 8 ohms. Simulated Teak cabinet. £14.00 a pair. £2.20 p. & p. Duo Type III Size approx. 23½in x 11½in x 9½in. Drive unit 13½in x 8½in with HF speaker. Max. power 20 watts, 8 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32.00 a pair + £3.30 p. & p.

#### PRICES: SYSTEM 1

Viscount III R 102 amplifier	£24.20 + £1 p. & p.
2 Duo Type II speakers	£14.00 + £2.20 p. & p.
Garrard SP25 Mk. III with	
MAG. cartridge plinth & cover	£18.00 + £1.75 p. & p.
total	£56.20

Available complete for only £49.00 – £3.50 p. & p.

#### PRICES: SYSTEM 2

Viscount R 102 amplifier	£24.20 + £1 p. & p.
2 Duo Type III speakers	£32.00 – £3.30 p. & p.
Garrard SP25 Mk III with	
MAG. cartridge plinth & cover	£18.00 + £1.75 p. & p.
total	£74.20

Available complete for £65.00 + £4 p. & p.

STILL ONLY **£49** COMPLETE



### THE TOURIST PUSH-BUTTON CAR RADIO KIT £6.60

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles it covers the full medium and long wave bands. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohms speaker. But the Tourist PB will operate into any loudspeaker from 8 to 15 ohms.

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.


The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale. Chassis size is: 7in wide, 2in high and 4½in deep.

- \* Circuit diagram and comprehensive instructions 55p free with parts.
- \* Fully retractable and lockable car aerial £1.37 post paid.
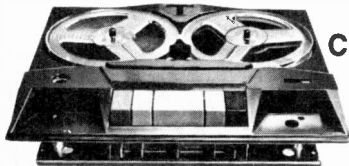
#### CAR RADIO KIT £6.60 p. & p. 55p


Speaker with baffle and fixing strips £1.65. 23p p. & p., post free if bought with the kit. Send stamped addressed envelope for leaflet.

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.


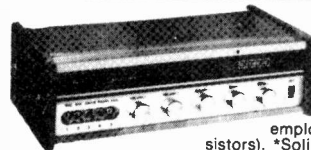
### PE TAPE LINK CONSTRUCTORS

Suitable 3 speed tape deck, **less heads**. Caters up to 5½ins. spools. 240V AC mains. Unused but store soiled hence no warranty. £1 p. & p. **£4.00**



### RELIANT Mk IV £13.50 Mono Amplifier

\*5 Electrically Mixed Inputs. \*3 Individual Mixing controls. \*Separate bass and treble controls common to all 5 inputs. \*Mixer

employing F.E.T. (Field Effect Transistors). \*Solid State Circuitry. \*Attractive Styling.


INPUTS 1. Crystal Mic or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of

medium output equipment (Gram. Tuner, Monitor, Organ, etc.). All 250mV sensitivity. Output 20 watts into 8 ohms (suitable for 15 ohms). Size approx. 12½ x 6 x 3½ ins. £13.50 p. & p. 60p.
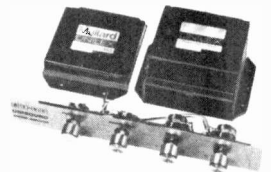
### UNISOUND MODULES

ONLY £7.64 + 55p p. & p.

For the man who wants to design his own stereo—here's your chance to start, with Unisound—pre-amp, power amplifier and control panel. No soldering—just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum.



### IN-CAR ENTERTAINMENT AT HOME

With this elegant stereo 8 track add on unit, audio enthusiasts now have the opportunity to extend their systems to include the playing of 8 track cartridges. Simply select your channel, by push button, four digital lamps indicate channel selected. Mains operated.



The Viscount III, the fabulous Stereo 21 and the Unisound Modules will all accept this unit. **£10.60 p. & p. 90p.** simply connect up.

**ALL PRICES INC. VAT**

SEE OPPOSITE PAGE FOR ADDRESS DETAILS



GIRO NO. 331 7056  
C.W.O. only. P. & P. 10p on orders below £5  
Discount: £10-10%, £20-15% (except net items)  
Export Order enquiries welcome (VAT free)  
Official Orders accepted from  
Educational & Government Departments  
**ALL PRICES INCLUDE VAT**

**SPECIAL RESISTOR KITS**

10E12 1W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3.10 net  
10E12 1W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (CARBON FILM 5%), £3.20 net  
25E12 1W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7.20 net  
25E12 1W KIT: 25 of each E12 value, 10 ohms—1M, a total of 1525 (CARBON FILM 5%), £7.35 net  
20E12 1W KIT: 20 of each E12 value, 10 ohms—1M, a total of 1220 (METAL FILM 5%), £7.50 net  
15E12 1W KIT: 15 of each E12 value, 10 ohms—1M, a total of 915 (METAL FILM 5%), £8.15 net  
10E12 2W KIT: 10 of each E12 value, 10 ohms—1M, a total of 610 (METAL FILM 5%), £12.65 net

**MULLARD POLYESTER CAPACITORS C280 SERIES**

250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 3½p. 0.068µF, 0.1µF, 4½p. 0.15µF, 4½p. 0.22µF, 5½p. 0.33µF, 8p. 0.47µF, 9p. 0.68µF, 11p. 1µF, 15p. 1.5µF, 22p. 2.2µF, 25p.

**MULLARD POLYESTER CAPACITORS C296 SERIES**

400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 0.0047µF, 2½p. 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 3½p. 0.047µF, 0.068µF, 0.1µF, 4½p. 0.15µF, 4½p. 0.22µF, 5½p. 0.33µF, 8p. 0.47µF, 9p. 0.68µF, 11p. 1µF, 15p. 1.5µF, 22p. 2.2µF, 25p.

**MINIATURE CERAMIC PLATE CAPACITORS**

50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8. (µF) 0.01, 0.015, 0.022, 0.033, 0.047, 2½p. each. 0.1, 30V, 4½p.; 0.1, 100V, 5½p.

**POLYSTYRENE CAPACITORS 160V 5%**

(pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 4p. 6800, 10,000, 4½p.

**RESISTORS**

CF—High Stab Carbon Film 5% MF—High Stab Metal Film, 5%  
W. Type Range 1-9 10-49 50-99 100-249 250-499 500-999 1000+ Size mm  
½ CF 22-1M 1 0.8 0.65 0.62 0.55 0.5 0.45 2.4 x 7.5  
½ CF 22-2M2 1 0.8 0.65 0.62 0.55 0.5 0.45 3.9 x 10.5  
½ CF 22-1M 0.8 0.65 0.62 0.55 0.5 0.45 5 x 16  
½ MF 10-2M7 1 0.9 0.8 0.7 0.65 0.65 0.6 3 x 7  
½ MF 10-2M2 1 0.9 0.8 0.7 0.65 0.65 0.6 4.2 x 10.8  
½ MF 10-10M 1.5 1.25 1.25 1.1 1 0.95 0.8 6.6 x 18  
2 MF 10-10M 3 2.5 2.5 2 1.75 1.75 1.6 8 x 17.5  
For value mixing prices, please refer to our catalogue. (price in pence each)  
VALUES AVAILABLE—E12 Series only. Net prices above 100.

**PRESET SKELETON POTENTIOMETERS**

MINIATURE 0-25W Vertical or horizontal 6p each 1K, 2K2, 4K7, 10K, etc. up to 1M Ω  
SUB-MIN 0-05W Vertical, 100 Ω to 220K Ω 5p each

**B. H. COMPONENT FACTORS LTD.**

(P.E.) 61 CHEDDINGTON ROAD, PITSTONE, NR. LEIGHTON BUZZARD, BEDS, LU7 9AQ  
Tel.: Cheddington 668446 (Std. Code 0296)  
PLEASE WRITE FOR FREE CATALOGUE

**Miniature Mullard Electrolytics**

1.0µF 63V	6p	68µF 16V	6p
1.5µF 63V	6p	68µF 63V	12p
2.2µF 63V	6p	100µF 10V	6p
3.3µF 63V	6p	100µF 25V	6p
4.0µF 63V	6p	100µF 63V	14p
4.7µF 63V	6p	150µF 16V	6p
6.8µF 63V	6p	150µF 63V	15p
8.0µF 63V	6p	220µF 6V	4p
10µF 16V	6p	220µF 10V	6p
10µF 25V	6p	220µF 16V	9p
10µF 63V	6p	220µF 63V	21p
15µF 16V	6p	330µF 16V	12p
15µF 63V	6p	330µF 63V	25p
16µF 40V	6p	470µF 6V	4p
22µF 25V	6p	470µF 40V	20p
22µF 63V	6p	680µF 16V	15p
32µF 10V	6p	680µF 40V	25p
33µF 16V	6p	1000µF 16V	20p
33µF 40V	6p	1000µF 25V	25p
32µF 63V	6p	1500µF 6V	4p
47µF 10V	6p	1500µF 16V	25p
47µF 25V	6p	2200µF 10V	25p
47µF 63V	8p	3300µF 6V	4p

**VEROBOARD 0.1 0.15**

2½ x 5"	28p	28p
2½ x 3½"	26p	19p
3½ x 5"	32p	33p
3½ x 3½"	28p	28p
2½ x 1"	7p	7p
2½ x 5" (Plain)	—	14p
2½ x 3½" (Plain)	—	12p
5 x 3½" (Plain)	—	22p
Insertion tool	59p	59p
Track Cutter	44p	44p
Pins, Pkt. 25	10p	10p

**TRANSISTORS**

AC127 16½p	BC212L 12p
AC128 22p	BC213L 12p
BC107 11p	BC214L 17p
BC108 12p	OC44 18p
BC109 13p	OC71 13p
BC148 12p	OC81 16p
BC149 12p	OC170 23p
BC182L 12p	TIS43 33p
BC183L 12p	2N2926 11p
BC184L 13p	2N3702 11p

**POTENTIOMETERS**

Carbon Track 5K Ω to 2M Ω, log or lin. Single, 16½p. Dual Gang 46p. Log Single with Switch 26p.

Slider Pots. 10K, 100K, 500K, 30mm, 34p. 45mm, 47p. 60mm, 55p.

**DIODES**

IN4001 6½p
IN4002 7½p
IN4003 9p
IN4004 9½p
IN4005 12p
IN4006 14p
IN914 7p
IN916 7p
BA100 10p
OAS 42p
OA47 12p
OA81 11p
OA200 8p

**Integrated Circuits**

µA709C 50p
µA741C 55p
µA723C £1
µL914 35p

**PLUGS**

DIN 2 Pin 12p
3 Pin 13p
5 Pin 180° 15p
Std. Jack 14½p
2.5mm Jack 11p
Phono 5½p

**SOCKETS**

DIN 2 Pin 10p
3 Pin 10p
5 Pin 180° 12p
Std. Jack 14½p
2.5mm Jack 11p
Phono 5½p

**ELECTROLYTIC CAPACITORS. Tubular & Large Cans**

(µF/V): 2, 2.25, 2.2, 6.3, 4.7/10, 4.7/25, 4.7/63, 22/10, 22/25, 22/63, 5p. 2/10, 10/10, 50/10, 100/10, 10/25, 50/25, 10/50, 51p. 200/10, 100/25, 50/50, 61p. 500/10, 200/25, 100/50, 9p. 1000/10, 500/25, 200/50, 11p. 2000/10, 1000/25, 500/50, 16½p. 1000/50, 39p. 1000/100, 66p. 2000/25, 27p. 2500/12, 17p. 2500/25, 33p. 2500/50, 62p. 3000/50, 72p. 5000/25, 66p. 5000/50, 94p. 7000/50, 60p. 25,000/25, 74p. Hi-VOLT: 8/350, 14p. 16/350, 19p. 32/350, 25p. 50/250, 18p. 100/500, 33p.

**METALLISED PAPER CAPACITORS**

250V: 0.05µF, 0.1µF, 4½p. 0.25µF, 5½p. 0.5µF, 6½p. 1µF, 9p. 500V: 0.025µF, 0.05µF, 4½p. 0.1µF, 5½p. 0.25µF, 6½p. 0.5µF, 9p. 1000V: 0.01µF, 10p. 0.022µF, 12p. 0.047µF, 0.1µF, 16p. 0.22µF, 31p. 0.47µF, 39p.

**QUANTITY DISCOUNT**

SPECIAL BULK BUY PRICES ARE AVAILABLE BY QUOTATION FOR LARGE PROJECTS AND TRADE

**P.E. SOUND SYNTHESISER**



SIMPLY SEND EXACT DETAILS OF NAME AND NUMBER COPIED FROM THE FACE OF YOUR ACCESS CARD AND LEAVE THE REST TO US.

**'DESIGNER APPROVED KITS'**

The 'RING MODULATOR' I.C. SG 3402G £1-74 each ML3046P 75p each 2N3819 (FET) 46p each ML748CS (8 pin D.I.L.) 60p each ZIJ NOISE DIODE 50p each mini D.I.L. 741's 32p each while stocks last 4p stamp brings latest lists Attractive discounts on quantity purchases.

We stock a full range of professional quality components as specified for this exciting project and many prices are down. 2% M.O. resistors now 3-2p ea. 5% low noise carbon film 1.8p ea. Cermet presets now 37.5p ea. McMurdo Plugs and Sockets. New stock. LOW prices. RP8 35p (limited stock). R58 45p. 10 turn counting dials by Amphenol. Boxed with setting wrench and instructions. £2 each. 10 turn precision pots by Spectrol Reliance £3 each.

**EATON AUDIO P.O. Box No. 3, ST. NEOTS HUNTINGDON PE19 3JB**

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or crossed P.O. payable to Eaton Audio. Minimum order £2. Where P. & P. charges are not shown please add 10p in the £1 to orders under £5. Orders over £5 will be sent free of P. & P. All prices subject to V.A.T.



**for fast, easy reliable soldering**

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

**EASY-TO-USE DISPENSERS**



Size 5 Savbit alloy 18 swg, 18p (illustrated). Size 19A 60/40 alloy 18 swg, 18p Size 15 60/40 alloy 22 swg, 22p


**IDEAL FOR HOME CONSTRUCTORS**

Size 1 cartons in 40/60, 60/40 and Savbit alloys in 7 gauges 25p



Size 12 REEL for Service Engineers and Electricians. 18 swg Savbit alloy. 75p

**BIB WIRE STRIPPER AND CUTTER**

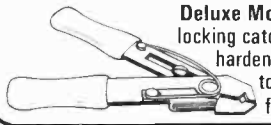

Deluxe Model 9 Automatic opening spring, locking catch, plastic-covered handles. Case hardened and precision ground. Adjusts to most wire sizes. Cuts and strips flex, splits plastic twin flex. 75p

Prices shown are recommended retail, excluding V.A.T. From Electrical and Hardware Shops, if unobtainable, send 10p p&p direct to Multicore Solders Ltd., Hemel Hempstead, Hertfordshire HP2 7EP





**I.L.P. (Electronics) Ltd**

## SECOND GENERATION 25 WATT HYBRID



A brand new hybrid fabrication technique, recently perfected in our laboratories, has enabled us to achieve our latest range of completely integrated devices. We have now finally reduced the modular audio amplifier to a simple input/output device requiring only the addition of a basic unstabilized (split line) power supply. The HY50 takes medium power modules to their logical conclusion by incorporating with it a heatsink, which is designed in special high conductivity alloy sufficient for normal audio use without additional chassis sinking. All this without significantly increasing the size of the module comparable in size to a packet of "King-size" cigarettes. Consistent with modern thinking a triple rated output circuit with a load fuse allows for peak transient response without distortion but ensures the necessary protection.

**OUTPUT POWER:** 25W RMS, 50W peak music power.  
**LOAD IMPEDANCE:** 4-16Ω into 8Ω  
**INPUT SENSITIVITY:** 0dB (0.775V RMS).  
**INPUT IMPEDANCE:** 47kΩ.  
**TOTAL HARMONIC DISTORTION:** Less than 0.1% at 25W typically 0.05.  
**SIGNAL/NOISE RATIO:** better than 75dB.  
**FREQUENCY RESPONSE:** 10Hz-50kHz ± 1dB.  
**SUPPLY VOLTAGE:** ± 25V.  
**SIZE:** 105 x 50 x 25mm.  
Price £5.40 mono £10.80 stereo. Price inclusive of VAT & P. & P.

### SPEC.


## NEW HY5 PREAMPLIFIER

Unchallenged for two years, the HY5, our unique multifunction preamplifier/tone hybrid, has been brought into line with the advancements in our power hybrids.

Like the HY50, the new HY5 has no external components and has been redesigned to run off a split power line with improvements in signal/noise, overload capability and reduced distortion. The output has been increased to match the power module (0dB), and share the same power supply. Overall size is reduced by the use of a new thin film circuitry while the device still retains all the functions of the earlier device.

When combined with the HY50 and power supply only potentiometers are required to complete a simple mono amplifier with input and output facilities expected to be found on Hi-Fi amplifiers.

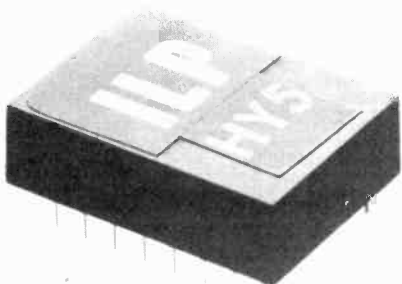The combination of two HY5's two HY50's sharing a common power supply (PSU50) are linked by a balance control to form a complete stereo system.




**INPUTS**  
Magnetic Pick-up 3mV (within 1dB RIAA curve)  
Ceramic Pick-up up to 3mV.  
Microphone 10mV.  
Tuner 250mV.  
Auxiliary 3-100mV.  
Input impedance 47kΩ 1 kHz  
**OUTPUTS**  
Tape 100mV.  
Main output. 0dB (0.775V).
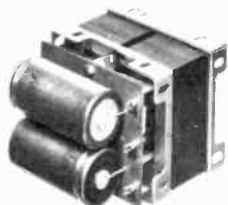
### SPEC.

**ACTIVE TONE CONTROLS**  
Treble ± 12dB at 10kHz  
Bass ± 12dB at 100Hz  
**OVERLOAD CAPABILITY**  
(equalization stage) 40dB on most sensitive input.  
**OUTPUT NOISE LEVEL**  
(below 10mV magnetic input) 68dB.  
**DISTORTION** 0.05% at 1kHz.  
**SUPPLY VOLTAGE** ± 16-25V.  
**SUPPLY CURRENT** 15mA.

Price £4.51 mono £9.02 stereo. Price inclusive of VAT & P. & P.



## POWER SUPPLY PSU50

The new PSU50 has a low profile look being only 2½in high and can be used for either mono or stereo systems.

**SPEC.**  
**OUTPUT VOLTAGE** ± 25V.  
**INPUT VOLTAGE** 210-240V.  
**SIZE:** L. 70 D. 90 H. 60mm.  
Price £5.23. Price inclusive of VAT & P. & P.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT


CANTERBURY 63218

Please note we reserve the right to substitute at our discretion updated versions of advertised designs where applicable.

# Connoisseur
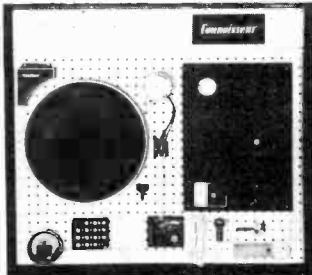
## THE B.D.2 TURNTABLE ASSEMBLY

The Famous B.D.2 belt drive turntable with press button speed change has now been developed to feature a newly designed mat and brushed aluminium trim, and the perspex cover has an easy 'hinged-on, hinged-off' movement. The B.D.2 is available as a chassis unit or spring mounted on a wood plinth.



## B.D.1 TURNTABLE KIT

The B.D.1 well known for its superb performance and quality is available in kit form. Construction is simplicity itself with no soldering required. Now it's so easy to own the best.

Contact your dealer for information or send a stamp for brochure.

# A. R. SUGDEN & CO. (ENGINEERS) LTD

Atlas Mill Road, Brighouse HD6 1ER Telephone: Brighouse (04847) 2142. Telegrams and cables: Connoisseur, Brighouse



## KONTAKT 60

**FOR INACCESSIBLE CONTACTS—More than just a cleaner. KONTAKT 60 guarantees perfect cleaning of contacts chemically in accordance with today's technology.**

**KONTAKT offers the following advantages:—**

1. Dissolves oxides and sulphides the safe way without attacking contact substances.
2. Contains carefully selected solvents which do not attack plastics whereas they do dissolve resinified contact greases and dirt.
3. Contains *no silicone*.
4. Contains a light lubricant in order to avoid the contact paths being corroded.
5. Prevents further oxidation setting in.
6. Prevents "creep" currents.

Because of these outstanding properties **KONTAKT 60** is one of the best and most popular contact cleansing agents in the world.

Users include: Rolls-Royce Ltd., C.E.G.B., South of Scotland Electricity Board, Trinity House Workshops, Kolster Brandes, Mullard, Plessey Cos., etc.

### OTHER KONTAKT PRODUCTS ARE:

- |                                  |                                   |
|----------------------------------|-----------------------------------|
| 70 Protective Lacquer            | 80 Special Siliconized Polish     |
| 72 Insulating Spray              | 100 Antistatic Agent for Plastics |
| 75 Cold Spray for Fault Location | 101 Dehydration Fluid             |

Write for full details of above complete range of Kontakt products to:—

**SPECIAL PRODUCTS DISTRIBUTORS LIMITED**  
81 Piccadilly, London, W1V 0HL. Tel. 01-629 9556



**MULTIMETER** Model C-7081 GN  
Range Doubler 50,000 ohm/volt  
High Sensitivity Meter £12-37.

**TAPE RECORDER LEVEL METER**  
500µA, 55p



**CARDIOID DYNAMIC MICROPHONE**

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £4-95.



4 1/4 in x 3 1/4 in **METER.** 30µA, 50µA or 100µA, £2-86.

**MULTI-METER**  
Model 200H  
20,000 ohm/volt, £5-28.



**3 WATT STEREO AMPLIFIER**  
£4-30

All above prices include 10% V.A.T. Please add 10p for P. & P. on orders under £5. LARGE S.A.E. for List No. 6. Special prices for quantity quoted on request.

## M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

# MAPLIN ELECTRONIC SUPPLIES

★ **SAME DAY SERVICE**

## LARGE or SMALL Centurion

Model 120

**PROJECTS DESERVE A PROFESSIONAL QUALITY INSTRUMENT CASE—4 MODELS**

Model 120 all aluminium two part construction. Top and sides, blue hammer finish, front, rear and base: white. Others: mild steel three part construction. Top, base, sides and detachable rear panel, blue hammer detachable front panel finished in white.



Model 320

Model	W	H	D	Price
120	8	2½	6	£1.85
220	8	6	3½	£2.65
221	8	6	6	£2.80
320	12	8	7½	£5.00

Chassis for model 320 £1.75 extra.  
Please send s.a.e. for free illustrated leaflet.

## ORGAN BUILDERS

MES announce the very latest development in organ circuitry.

### THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in die connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3-7in. x 4-5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested DMO2 (with tremulant) ONLY £14.25

DMO2 (without tremulant) £12.25.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.63 each OR special price for pack of 12: £25.00. S.a.e. please for data sheet.

★ S.a.e. please for full technical details.

Trade enquiries welcome.



MAPLIN: Projected site of London's third airport.

## P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We shall be stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Veroboards.

Send s.a.e. now for our detailed price lists. YOU SIMPLY MUST SEE OUR PRICES!


Spring line reverberation unit (as specified)	£2.89
uA 7815 (15V 1.5A) voltage regulator	£2.30
REc 41A bridge rectifier	£1.06
741C 8-pin DIL	36p
MFC 6040 electronic attenuator	£0.85
SG 3402N for Ring Modulator	£1.89

## CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1	63 6p	68	6-3 6p
1.5	63 6p	68	16 6p
2.2	63 6p	68	63 10p
3.3	63 6p	100	6 6p
4.7	63 6p	100	10 6p
6.8	63 6p	100	25 6p
6.8	63 6p	100	40 6p
10	25 6p	100	63 12p
10	63 6p	150	6-3 6p
15	16 6p	150	16 6p
15	40 6p	150	25 6p
15	63 6p	150	40 10p
22	10 6p	150	63 12p
22	25 6p	220	4 6p
22	63 6p	220	10 6p
33	6-3 6p	220	16 6p
33	16 6p	220	25 10p
33	40 6p	220	40 12p
47	4 6p	220	63 18p
47	10 6p	330	4 6p
47	25 6p	330	10 6p
47	40 6p	330	16 10p
47	63 6p	330	63 22p
		4700	4 22p

## PLUGS AND SOCKETS

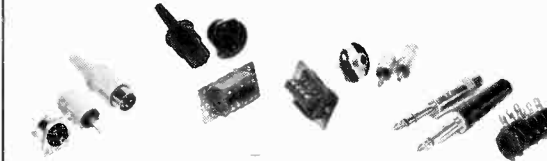

<b>DIN PLUGS</b>	<b>PLUGS</b>	<b>PLUGS</b>	<b>PLUGS</b>
2 pin (1 flat) 8p	P360 3 pin 1.5A chassis plug with 4 pin, 5 pin A line socket. Per pair 24p	R88 8 way chassis socket 52p	Std. 1/2" stereo plug Plastic 18p
3 pin 9p	SA 2190 3 pin 5A chassis plug 17p		Screened 25p
4 pin, 5 pin B (180°), 5 pin B (240°), 6 pin 10p	SA 1862 Line socket for above 19p		Open mono socket 1/2" 10p; Moulded mono socket 1/2" with 2 break contacts 9p
<b>DIN Sockets</b>	<b>McMURDO</b>	<b>JACK</b>	13p; Moulded stereo socket 1/2" with 3 break contacts 18p; 3-5mm. plug plastic 8p; screened 11p; open socket 8p.
2 pin 6p	RP8 8 way chassis plug 38p	Std. 1/2" mono plug Elastic 13p	
3 pin, 4 pin, 5 pin A (180°), 5 pin B (240°), 6 pin 7p		Screened 17p	

## WE KNOW YOU NEED IT!



The MES 1974 CATALOGUE IS STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system, EXCITED by our BIG VALUE discount vouchers, STAGGERED by our UNBEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue.

and leave the rest to us!

## OMNIUM GATHERUM

PP3, 6 etc. battery clip dual min. 9p.  
FP1, 9 etc. battery clip separate per pair 6p.  
Pair crocodile clips 1 red, 1 black insulated sleeve 7p.  
Solder Multicore 22 s.w.g. 10 metres 20p.  
Silicone grease in special dispenser 20ml 48p.  
Red neon 240V panel mounting 25p.  
Lacing Cord Strong rayon cored PVC 25m 48p.  
Panel fuse holders 20mm 20p; 1½in 30p.

**Transformers**  
LT700 min. output transformer Pri. 1-2kΩ Sec. 6Ω 200mW 35p.

**Sub-min. Mains Transformer**  
0-6-5V 100mA 95p. 12-0-12V 50mA 95p.  
Size: Both approx. 30 x 27 x 25mm.  
**Min. Mains Transformer**  
Size: 46 x 31 x 38mm.  
0-12V 250mA, 0-12V 250mA £1.38.

**Mains transformer MT3AT**  
Pri. 200-220-240V, Sec. 12-15-20-24-30V 2A £2.48.

**Mains Transformer MT208AT**  
Pri. 200-220-240V, Sec. 0-15-20V 1A, 0-15-20V 1A £3.10.

Also in stock: Wide range of brass and nylon nuts, bolts and washers plus solder tags, shakproof washers, etc.

## POTENTIOMETERS

Rotary miniature carbon track 1/2" spindle

<b>Single gang Lin or Log</b> 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M, 2M (and 1k Lin) 12p	<b>Single gang with DP switch</b> 250V 2A Log or Lin 5k to 2M as above 28p
<b>Dual gang (Stereo) without switch Log or Lin 5k to 2M as above 38p.</b>	<b>PRESETS</b> Sub-miniature 0-1W Vert or Horiz 100, 250, 500, 1k, 2.5k, 5k, 10k, 25k, 50k, 100k, 250k, 500k, 1M 8p
<b>Wirewound 10% 1W 1/2" spindle 10, 50, 100R 34p; 250, 500, 1k, 5k 33p; 10k, 37p; 25k 40p; 50k 44p.</b>	

## RESISTORS

Carbon Film 1/4W 5% 1Ω to 1M; 10% 1.2M to 10M E12 1p	Carbon Film 1/4W 5% 1Ω to 10Ω; 10% 1.2M to 10M E24 1p
Carbon Film 1/4W 5% 1Ω to 910k E12 & E24 1p	Carbon Film 1/4W 5% 10Ω to 10M E12 3p
Metal Oxide 1/4W 2% 10Ω to 1M E12 & E24 4p	Wirewound 2 1/4W 10% 0-220ohms to 0-470ohms E12 10p
Wirewound 2 1/4W 5% 10hm to 270ohms E12 10p	E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

## TRANSISTORS, DIODES & I.C.'s.

AC127 25p	MFP102 30p	2N3033 18p
AC128 20p	OC25 65p	2N3034 54p
AC176 17p	OC28 85p	2N3055 49p
AD149 50p	OC35 60p	2N3819 24p
AD161/2 60p	OC44 20p	OA90 7p
BC107 10p	OC71 20p	OA91 6p
BC108 10p	T1843 28p	1N914 4p
BC109 10p	2N705 10p	1N4148 4p
BC147 10p	2N1304 30p	1N4001 6p
BC148 10p	2N1711 24p	1N4002 61p
BC149 12p	2N2219 25p	1N4003 7p
BC168 13p	2N2646 45p	1N4004 74p
BC169C 12p	2N2905 33p	1N4006 8p
BC182L 12p	2N2907 25p	1N4006 81p
BC204 14p	2N2906 10p	1N4007 8p
BC209C 14p	2N2926V 10p	W005 30p
BD131 54p	2N2926G 10p	W04 33p
BD132 67p	741C 8-pin DIL 36p	
BD131/2 £1-50	741C 14-pin DIL 45p	
BF194 15p	DIL Sockets 8-pin 20p	
BFY31 16p	14-pin 15p	

See our catalogue for our full range of transistors, 74 series I.C.'s bridges, etc.

## SWITCHES

Rotary with adjustable atop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 24p.  
Mains rotary DPDT 250V 2A 20p.

<b>Push to make non-locking 12p</b>	<b>Slide Miniature DPDT 8p</b>
<b>Toggle 250V 1.5A with ON/OFF plate 25p.</b>	<b>Sub-miniature toggle DPDT (12 x 12.5 x 14mm excl. toggle) 250V 3A 61p</b>

# VAT

Please add 10% to the final total.

**Post and Packing FREE in U.K.**  
(10p handling charge on orders under 50p.)

Orders and enquiries for catalogues to MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. Tel.: Southend-on-Sea (0702) 44101.

# TRANSFORMERS

**SAFETY MAINS ISOLATING TRANSFORMERS**  
Prim. 120/240V. Sec 120/240V Centre Tapped and Screened  
**ALSO AVAILABLE WITH 115/120V SEC. WINDING**

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P
07	20	1 8	7.0 x 6.0 x 6.0	1.94 30
149	60	3 12	9.9 x 7.7 x 8.6	2.88 36
150	100	5 8	9.9 x 8.9 x 8.6	3.16 52
151	200	8 0	12.1 x 9.3 x 10.2	5.31 52
152	250	13 12	12.1 x 11.8 x 10.2	7.01 67
153	350	15 0	14.0 x 10.8 x 11.8	9.40 82
154	500	19 8	14.0 x 13.4 x 11.8	13.55 *
155	750	29 0	17.2 x 14.0 x 14.0	19.26 *
156	1000	38 0	17.2 x 16.6 x 14.0	24.97 *
158	2000	60 0	21.6 x 15.3 x 18.1	41.25 *

## AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Tops	P & P
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.02 22
64	75	2 4	7.0 x 6.7 x 6.1	0-115-210-240	2.00 30
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	2.42 36
66	300	6 4	9.9 x 9.6 x 8.6	"	4.70 52
67	500	12 8	12.1 x 11.2 x 10.2	"	6.98 67
84	1000	19 8	14.0 x 13.4 x 14.3	"	12.69 82
93	1500	30 4	14.0 x 15.9 x 14.3	"	18.39 *
95	2000	32 0	17.2 x 16.6 x 14.0	"	24.00 *
73	3000	40 0	21.6 x 13.4 x 18.1	"	32.67 *

## CASED AUTO TRANSFORMERS

115 500W enclosed transformer, with mains lead and two 115V outlets sockets, £9.49, P & P 67p. 20W version, £2.02, P & P 22p.

## LOW VOLTAGE SERIES (ISOLATED)

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	P & P	
111	0.5	0.25	8	4.8 x 2.9 x 3.5 0-12V at 0.25A x 2	1.02 22	
113	1.0	0.5	1	4	6.1 x 5.8 x 4.8 0-12V at 0.5A x 2	1.22 22
71	2	1	12	7.0 x 6.4 x 6.1 0-12V at 1A x 2	1.60 30	
218	4	2	12	8.3 x 7.7 x 7.0 0-12V at 2A x 2	2.24 36	
70	6	3	8	8.9 x 8.0 x 7.7 0-12V at 3A x 2	2.70 42	
108	8	4	5	8	9.9 x 8.9 x 8.6 0-12V at 4A x 2	3.00 52
72	10	5	6	4	9.9 x 9.6 x 8.6 0-12V at 5A x 2	3.55 52
116	12	6	12	9	9.9 x 10.2 x 8.6 0-12V at 5A x 2	4.30 52
17	16	8	12	12	12.1 x 9.9 x 10.2 0-12V at 8A x 2	5.48 52
115	20	10	11	8	14.0 x 9.6 x 11.8 0-12V at 10A x 2	6.98 67
187	30	15	8	14	14.0 x 12.1 x 11.8 0-12V at 15A x 2	12.90 82
226	60	30	32	0	17.2 x 15.3 x 14.0 0-12V at 30A x 2	23.72 *

## 30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P
112	0.5	1	4	6.1 x 5.8 x 4.8 0-12-15-20-24-30V	1.22 22
79	1.0	2	4	8.0 x 6.7 x 6.1	1.62 30
3	2.0	3	4	8.9 x 7.7 x 7.7	2.43 36
20	3.0	4	8	9.9 x 8.3 x 8.6	2.99 42
21	4.0	6	4	9.9 x 9.6 x 8.6	3.55 52
51	5.0	6	12	12.1 x 8.6 x 10.2	4.42 52
117	6.0	8	0	12.1 x 9.3 x 10.2	5.28 52
88	8.0	12	0	12.1 x 11.8 x 10.2	6.82 67
89	10.0	13	12	14.0 x 10.2 x 11.8	8.36 67

## 50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P
102	0.5	1	12	7.0 x 6.4 x 6.1 0-19-25-33-40-50V	1.60 30
103	1.0	2	12	8.3 x 7.4 x 7.0	2.34 36
104	2.0	3	8	7.9 x 8.9 x 8.6	3.25 42
105	3.0	6	12	9.9 x 10.2 x 8.6	4.41 52
106	4.0	10	0	12.1 x 10.5 x 10.2	5.84 52
107	6.0	12	0	14.0 x 10.2 x 11.8	8.63 67
118	8.0	18	0	14.0 x 12.7 x 11.8	11.27 97
119	10.0	25	0	17.2 x 12.7 x 14.0	14.13 *

## 60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P
124	0.5	2	4	7.0 x 6.7 x 6.1 0-24-30-40-48-60V	1.62 36
126	1.0	3	4	8.9 x 7.7 x 7.7	2.26 36
127	2.0	6	4	9.9 x 9.6 x 8.6	3.55 42
125	3.0	8	12	12.1 x 9.9 x 10.2	5.41 52
123	4.0	13	12	12.1 x 11.8 x 10.2	6.98 67
40	5.0	12	0	14.0 x 12.7 x 11.8	8.28 67
120	6.0	15	8	14.0 x 12.1 x 11.8	10.12 82
121	8.0	25	0	14.0 x 14.7 x 11.8	11.40 *
122	10.0	25	0	17.2 x 12.7 x 14.0	16.75 *
189	12.0	29	0	17.2 x 14.0 x 14.0	18.75 *

## MINIATURE TRANSFORMERS WITH SCREENS


Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P	
238	200	1	2	2.8 x 2.6 x 2.0	3-0.3	1.10 10
212	1A, 1A	1	4	6.1 x 5.8 x 4.8	0-6, 0-6	1.27 22
13	100	1	4	3.9 x 2.6 x 2.9	0-0.9	64 10
235	330, 330	1	4	4.8 x 2.9 x 3.5	0.9, 0.9	1.27 10
207	500, 500	1	00	6.1 x 5.4 x 4.8	0-8.9, 0-8.9	1.70 22
208	1A, 1A	1	12	7.0 x 6.4 x 6.1	0-8.9, 0-8.9	2.28 30
236	200, 200	1	4	4.8 x 2.9 x 3.5	0-15, 0-15	1.27 10
214	300, 300	1	4	6.1 x 5.8 x 4.8	0-20, 0-20	1.34 22
221	700 (d.c.)	1	8	7.0 x 6.1 x 6.1	20-12, 0-12-20	1.20 30
206	1A, 1A	1	12	8.3 x 7.7 x 7.0	0-15-20, 0-15-20	3.08 38
203	500, 500	2	4	3.7 x 0 x 7.0	0-15-27, 0-15-27	2.36 38
204	1A, 1A	3	4	8.9 x 7.7 x 7.7	0-15-27, 0-15-27	2.39 38

\*Carriage via B.R.S.

**PLEASE ADD 10% FOR V.A.T. INCLUDING P & P.**

**BARRIE electronics**  
3, THE MINORIES, LONDON EC3N 1BJ  
TELEPHONE: 01-488 3316/8  
NEAREST TUBE STATIONS ALDGATE & ALDGATE EAST

## CASED AMPLIFIERS

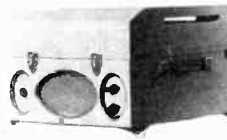

Polished wooden cabinet 14 x 13 x 9in containing a sensitive (20µV) 4 valve amplifier with tone and volume controls. 3 watts output to the 7 x 4in non-standard tape deck. Supplied in good working condition with circuit diagram. Mains operated. £3 (£1 up to 200 miles, £1.20 over). Cassette £1. Spare head 40p. Amplifier chassis only. Complete and tested £1.65 (35p).

## 71b BARGAIN PARCELS

Hundreds of new components—resistors, capacitors, crystals, pots, switches, PC boards containing transistors and diodes, etc., loads of odds and ends. Only £1.65 (40p).

## COMPUTER PANELS

31b assorted panels £1 (30p); 71b £1 (40p); 561b £13 (c/pd). 12 top quality panels containing power transistors, IC's, trim pots, etc. £1 (30p); 100 boards £12 (£1).

## ADD 10% TO TOTAL FOR VAT

Carr. in brackets; small parts 5p

## GREENWELD ELECTRONICS (PE7)

24 Goodhart Way, West Wickham, Kent; SHOPS AT: 21 Deptford Broadway SE8, Tel. 01-692 2009; Also 38 Lower Addiscombe Road, Croydon.

## BAKER 12" MAJOR £9-90

30-14,500 cps. Double cone woofer and tweeter loudspeaker. Baker ceramic magnet assembly, flux density 145,000 gauss. BASS RESONANCE 40 cps 20 watt RMS.

## MAJOR MODULE KIT £12.50

30-17,000 cps. woofer, tweeter, crossover and baffle as illustrated. Size 19in x 13in.

NOTE—When ordering state 3 or 8 or 15 ohms.

## BAKER LOUSPEAKERS 100% BRITISH MADE

Regent 12 in. 15W	£8.80	Superb 12 in. 20W	£16.50
Major 12 in. 20W	£9.90	Group 95 12 in. 25W	£8.80
Deluxe 12 in. 15W	£11.00	Group 95 12 in. 35W	£9.90

NEW. Group 50/12  
12 in. 50 Watt £17.80

## BAKER LOUSPEAKER CO., BENSHAM MANOR PASSAGE

THORNTON HEATH, SURREY Tel. 01-684-1665  
PRICES INCLUDE VAT. HI-FI ENCLOSURE PLANS 42p

## STEREO IC DECODER

HIGH PERFORMANCE PHASE LOCKED LOOP (as in 'W.W.' July '72)

## MOTOROLA MC130P

## EX STOCK DELIVERY

Specn. Separation: 40dB 50Hz—15kHz. Distortion: 0.3%. I/P level: 560mV rms. O/P level: 485mV rms per channel. Input impedance: 50k. Power requirements: 8-12V at 16mA. Will drive up to 75mA stereo 'on' lamp or LED. Simple to build.

**KIT COMPRISES FIBREGLASS PCB** (Printed and tinned), Resistors, I.C., Capacitors, Preset Potm. and Instructions. Only £3.98 post free + V.A.T.

## LIGHT EMITTING DIODE (Red)

Suitable as stereo 'on' indicator. For above with panel mounting clip and instructions. Only 29p + p.p. + V.A.T.  
MC130P only £2.77 + p.p. 6p + V.A.T.  
14 PIN DIL SOCKETS. 16p each + V.A.T.


NOTE—As the supplier of the original decoder kit, of which we have sold literally thousands, our customers can benefit from our wide experience.

**Fi-Comp Electronics**  
BURTON ROAD, EGGINGTON, DERBY DE6 6GY

**YES, YOU'VE GOT THE WHOLE WIDE WORLD IN YOUR HANDS! ALMOST UNBELIEVABLE!** Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and **SEE** for yourself that the incredible **Russians** have done it all **NOW!** It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** You probably remember radio sets like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only **£18.50**—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with **£80** radios! \*Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call. Volume controlled from a whisper to a roar—would fit a hall! Much wider band spread for absolute "pinpoint" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, **EVERY WAVE-BAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth during 24 hours a day including all normal transmissions. **VHF: FM/USW, AM: LW, MW, SW**, gets, locally, local & new stations not yet operational, and messages from all over the world! Expensive **TURRET TUNER** side control waveband selection unit (as used on expensive T.V.'s!). Every waveband clicks into position giving incredible ease of station tuning! Get the push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39 in approx. It's also a fabulous **CAR RADIO**. Can be used through extension amplifier, tape recorder or public address system. **SIZE 13in x 10in x 4 1/2in** overall approx. Magnificently designed, in highly polished cases. Made to give years of perfect service. Purer & sweeter tone than ever. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE**, manual with simple operating instructions & circuit diagram. **PLUS** ultra sensitive earphone for personal listening. **ONLY £18.50** (with mains/battery eliminator £2.25 extra) **BOX, POST, ETC. 45p. NO MORE TO PAY! BUT WAIT**, for only 75p extra you get the sensational "COMPUTERISED" **WORLD TUNING GUIDE** (it enables you to zone and time in a flash for transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING!**) **PLUS** Standard "longlife" batteries and Converter Plug. (Sorry—We cannot change these to radios for any earlier model already purchased.) Send quickly to Uxbridge Road address, or call at either Store. But **HURRY!** **SHOPERTUNITIES SAVE YOU £££'s.**

**THOUSANDS OF MILES REDUCED TO INCHES?**  
**1973 RUSSIAN RADIO TECHNOLOGY**  
**SHRINKS THE WORLD! \*COMPUTERISED?**

**THIS FANTASTIC EARTH SHRINKER**



**YES, 24,901 miles SHRUNK TO ONLY 13" x 10" x 4 1/2" inches approx?**

**BRAND NEW FABULOUS ASTRAD 17**  
**PORTABLE RADIO & COMMUNICATIONS RECEIVER**



**28 TRANSISTORS AND DIODES!**  
**WAVEBANDS:**  
**STANDARD LONG and MEDIUM**  
**Plus 5 SHORT WAVEBANDS**  
**Plus ULTRA SHORT WAVES**  
**(V.H.F. AM, FM, MW, LW, USW.)**

**\*MUST YOU PAY UP TO £80?**

**FIRST TIME EVER!**  
 \*NOW AVAILABLE WITH fabulous "COMPUTERISED" **WORLD TUNING GUIDE!**  
**NO MORE GUESSWORK—INSTANT DATA** at your fingertips—enables you to **ZONE & TIME IN A FLASH** for transmissions the world over!

**THIS OFFER ONLY FROM US!**

**BOX POST ETC. 45p**  
**£18.50**  
**MAINS/BATTERY ELIMINATOR £2.25 extra**

**BUY ONE FROM US!** **SAVE £23.03 NOW!**

**Fabulous BRAND NEW SOLID STATE** **This equipment's got EVERYTHING!**

**BATTERY/MAINS AC Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER**



**RECOMMENDED RETAIL PRICE**

**OUR PRICE £20.97** **CARR. ETC. 50p**

**WITH REMOTE CONTROL MICROPHONE**

Shopertunities "thunder" ahead with an offer that's **FANTASTIC** (even by our standards!). We've snapped up 500 magnificent machines. Latest sensation in the world of sound! First-class makers! Fabulous **VHF, AM/FM Radio AND Cassette Tape Recorder & Player** combined & it also runs off standard batteries or mains. (Simply plug in the 220/240V AC line cord). Record and play back anything, anywhere! **IMPORTERS' RECOMMENDED RETAIL PRICE £43.97! WE OFFER AT UNDER HALF PRICE!** Wonderful features: ★ Press-button Keyboard Control Panel or latest **MASTER SWITCH CONTROL!** ★ "MAGIC EYE" Visual Battery check/recording level indicator or built-in automatic Leveller! ★ Separate **ON/OFF** and **HI-LO** volume controls! ★ Heavy duty built-in speaker! ★ Earphone (for personal listening or "monitoring") and extension speaker socket! ★ Remote control microphone! ★ Built-in swivel telescopic extension aerial (24in approx.)! Magnificently made case with carry handle. (**DESIGNS VARY SLIGHTLY.**) Takes standard 30, 60, 90 or 120-minute Cassette Tapes, obtainable everywhere. **AND** the amazing built-in full circuit **VHF, AM/FM Radio** gives you superb clarity of tone, incredible station selection. Unique rotating Station Selector Dial—gets, locally, local city and regional stations in every part of the country, plus B.B.C. National, V.H.F. Picks up dozens of foreign stations! Fabulous in your car! You could pay **£££'s more** for a Car Radio or Car Cassette player **ALONE!** £20.97, carr. etc., 50p—**NO MORE TO PAY!** Complete with simple instructions, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE.** Send quickly, test on mail order 7 day approval from receipt of goods, refund if not delighted. Or call. **BONUS OFFER:** Batteries and Cassette Tape 28p extra if required.

**Callers: ACCESS & BARCLAY CARDS ACCEPTED AT BOTH STORES**

**FIRST TIME EVER! \*SAVE £16.02!**

**BRAND NEW AC/DC BATTERY/MAINS**

**Cassette TAPE RECORDER & PLAYER**



**FIRST CLASS MAKERS**

**WE COULD CHARGE UP TO £26.97!**

**OUR PRICE £10.95** **POST ETC. 50p**

**With remote control microphone.**

**THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! NOW** a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and incredible Shopertunities bring it to you for **ONLY £10.95**. Due to our cut price we cannot name first-class makers—but rest assured you're getting one of the **BEST!** Expensive "PIANO KEYBOARD" CONTROL PANEL (or latest **MASTER SWITCH** control) **AND AUTOMATIC LEVEL CONTROL.** No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! (Takes 30, 60 or 90 minute standard cassette tapes obtainable everywhere.) Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid Rewind! Fast forward! Beautiful one from a whisper to a roar! Complete—record anywhere, indoors or out! Runs on standard batteries **AND 220/240V AC** mains. Separate jacks for remote control microphone, etc. Size 9 1/2in x 5in x 2 1/2in approx. Design can vary slightly. With carry handle. **WRITTEN GUARANTEE** and full instructions. (Importers recommended selling price £26.97!) **OUR PRICE ONLY £10.95**, post, etc. 50p. **NO MORE TO PAY!** Send quickly, on mail order 7 day approval from receipt of goods—refund if not delighted. Or call at either of our stores. **BONUS OFFER** (Rationed 1 per customer)—Cassette tape. Standard batteries **AND** microphone stand 55p extra if required.

Order by post to Uxbridge Road address or call at either store. Bargains galore at both stores.—(COMMERCIAL TRAVELLERS PLEASE NOTE: Merchandising office at Holborn Store.)

**SHOPERTUNITIES LTD.**

Dept. PE/NC/33, 164 UXBIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) BOTH OPEN MON. TO SAT. 9 A.M. TILL 6 P.M.



# -the lowest prices!

**BRAND NEW TEXAS GERM. TRANSISTORS**  
 Coded and Guaranteed  
 Pak No. EQVT  
 T1 8 203713 OC71  
 T2 8 D1374 OC73  
 T3 8 D1216 OC81D  
 T4 8 20381T OC81  
 T5 8 20382T OC82  
 T6 8 20344B OC44  
 T7 8 20345B OC45  
 T8 8 20378 OC78  
 T9 8 20399A 2N1302  
 T10 8 20417 AF117  
 All 55p each pak

**ND120 NIXIE DRIVER TRANSISTOR.**  
 Suitable replacement for BSX21, C407, 2N1893 120vcb.  
 1 25 100+  
 0-10 0-17 0-16

Sil. trans. suitable for P.E. Organ. Metal TO-18 Fgvt. ZTX300 8p each. Any Quantity.

**GP100 TO3 METAL CASE GERMANIUM**  
 Vebo=80V. Vcco=50V. I.C.=10 amps. Plot=30W. hfe=30-170.  
 Replaces the majority of Germanium power transistors in the OC, AD and NKT range.  
 1 25 100+  
 0-48 0-44 0-40

**GP300 TO3 METAL CASE SILICON**  
 Vebo=100V. Vcco=60V. I.C.=15 amps. Plot=115W. hfe=20. 100IT=1MHz. Suitable replacement for 2N3055, BDY11 or BDY20.  
 1 25 100+  
 0-55 0-53 0-61

**NEW 7th EDITION TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK, 50p each.

**A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE ESTOCK. SEND FOR FREE LIST.**

**UT46 UNIJUNCTION TRANSISTORS**  
 Direct replacement for TIR 43rand BEN 3000 also electrically equivalent to 2N2646.  
 1 25 100+  
 0-30 0-28 0-22

**GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8. BSY-27/28/95A.** All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906, DCY70. When ordering please state preference NPN or PNP.  
 20 For 0-55  
 50 For 1-10  
 100 For 1-82  
 500 For 8-25  
 1000 For 14-30

**[SIL. G.P. DIODES 3p]**  
 300mW 30 0-55  
 40PIV(Min.) 100 1-65  
 Sub-Min. 500 5-50  
 Full Tested 1,000 9-90  
 Ideal for Organ Builders

**R2400 TO3 NPN SILICON HIGH VOLTAGE**  
 Vebo=250V. Vcco=100V. I.C.=6 amps. Plot=30W. hfe=typ. 20. IT=3MHz.  
 1 25 100+  
 0-55 0-50 0-44

**ADI61/162**  
 PNP M/P COMP. (GERM. TRANS. OR LOW PER PAIR.)

**LOOK FOR OUR AUDIO AND ELECTRONIC COMPONENTS ADVERTISEMENTS PRACTICAL WIRELESS EVERYDAY ELECTRONICS AND RADIO CONSTRUCTOR**

**SILICON PHOTO TRANSISTOR.** TO-18 Lens end NPN Sim. to BPX25 and P21. BRAND NEW. Full data available. Fully guaranteed.  
 Qty. 1-24 25-99 100up  
 Price each 44p 40p 35p

## INTEGRATED CIRCUIT PAKS

Manufacturers' "Full Outs" which include Functional and Part-Functional Units. These are classed as "out-of-spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00=	12x7400	0-55	UIC46=	5x7446	0-55	UIC86=	5x7486	0-55
UIC01=	12x7401	0-55	UIC48=	5x7448	0-55	UIC90=	5x7490	0-55
UIC03=	12x7402	0-55	UIC50=	12x7450	0-55	UIC91=	5x7491	0-55
UIC04=	12x7403	0-55	UIC51=	12x7451	0-55	UIC92=	5x7492	0-55
UIC04=	12x7404	0-55	UIC53=	12x7453	0-55	UIC93=	5x7493	0-55
UIC05=	12x7405	0-55	UIC54=	12x7454	0-55	UIC94=	5x7494	0-55
UIC06=	8x7406	0-55	UIC55=	12x7455	0-55	UIC95=	5x7495	0-55
UIC07=	8x7407	0-55	UIC60=	12x7460	0-55	UIC96=	5x7496	0-55
UIC10=	12x7410	0-55	UIC70=	8x7470	0-55	UIC100=	5x74100	0-55
UIC20=	12x7420	0-55	UIC72=	8x7472	0-55	UIC121=	5x74121	0-55
UIC30=	12x7430	0-55	UIC73=	8x7473	0-55	UIC122=	5x74122	0-55
UIC40=	12x7440	0-55	UIC74=	8x7474	0-55	UIC123=	5x74123	0-55
UIC41=	5x7441	0-55	UIC76=	8x7476	0-55	UIC151=	5x74151	0-55
UIC42=	5x7442	0-55	UIC80=	5x7480	0-55	UIC154=	5x74154	0-55
UIC43=	5x7443	0-55	UIC82=	5x7482	0-55	UIC193=	5x74193	0-55
UIC44=	5x7444	0-55	UIC83=	5x7483	0-55	UIC199=	5x74199	0-55
UIC45=	5x7445	0-55	UIC83=	5x7483	0-55	UICX1=	25 Assorted 74's 1-85	

Paks cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

## QUALITY TESTED SEMICONDUCTORS

Pak No.	Description	Price 5p
Q 1 20	Red spot transistors pnp	0-55
Q 2 16	White spot R.F. transistors pnp	0-55
Q 3 4	OC77 type transistors	0-55
Q 4 6	Matched transistors OC44/45/81/81D	0-55
Q 5 4	OC75 transistors	0-55
Q 6 5	OC73 transistors	0-55
Q 7 4	AC128 transistors pnp high gain	0-55
Q 8 4	AC126 transistors pnp	0-55
Q 9 7	OC81 type transistors	0-55
Q 10 7	OC71 type transistors	0-55
Q 11 2	AC127/128 Complementary pairs pnp/npn	0-55
Q 12 3	AF116 type transistors	0-55
Q 13 3	AF117 type transistors	0-55
Q 14 3	OC171 H.F. type transistors	0-55
Q 15 7	2N2926 Sil. Epoxy transistors mixed colours	0-55
Q 16 2	GET880 low noise Germanium transistors	0-55
Q 17 5	npn 2 x ST.141 & 3 x ST.140	0-55
Q 18 4	MADT'82 x MAT 100 & 2 x MAT 120	0-55
Q 19 3	MADT'S 2 x MAT 101 & 1 x MAT 121	0-55
Q 20 4	OC44 Germanium transistors A.F.	0-55
Q 21 4	AC127 npn Germanium transistors	0-55
Q 22 20	NKT transistors A.F. R.F. coded	0-55
Q 23 10	OA202 Silicon diodes sub-min.	0-55
Q 24 8	OA81 diodes	0-55
Q 25 15	IN914 Silicon diodes 75PIV 75mA	0-55
Q 26 8	OA85 Germanium diodes sub-min 1N69	0-55
Q 27 2	10A 600 PIV Silicon rectifiers 18425R	0-55
Q 28 2	Silicon power rectifiers BYZ13	0-55
Q 29 4	Silicon transistors 2 x 2N696, 1 x 2N697, 1 x 2N698	0-55
Q 30 7	Silicon switch transistors 2N706	0-55
Q 31 6	Silicon switch transistors 2N708, npn	0-55
Q 32 3	pnp Silicon transistors 2 x 2N131, 1 x 2N132	0-55
Q 33 3	Silicon npn transistors 2N1711	0-55
Q 34 7	Silicon npn transistors 2N2369, 500MHz (code P397)	0-55
Q 35 3	Silicon pnp TO-5. 2 x 2N2904 & 1 x 2N2905	0-55
Q 36 7	2N3646 TO-18 plastic 300MHz npn	0-55
Q 37 3	2N3055 Silicon transistors	0-55
Q 38 7	pnp transistors 4 x 2N3703, 3 x 2N3702	0-55

## ELECTRONIC SLIDE-RULE

The MK Slide Rule, designed to simplify Electronic calculations features the following scales:— Conversion of Frequency and Wavelength. Calculation of L, C and fo of Tuned Circuits. Reactance and Self Inductance. Area of Circles. Volume of Cylinders. Resistance of Conductors. Weight of Conductors. Decibel Calculations. Angle Functions. Natural Logs and "e" Functions. Multiplication and Division. Squaring, Cubing and Square Roots. Conversion of kW and Hp. A must for every electronic engineer and enthusiast. Size: 22cm x 4cm. Complete with case and instructions. Price each: £3-69

## NEW LOW PRICED TESTED S.C.R.'S

PIV	5p	10p	200	400	600	800
1A TO3	0-22	0-27	0-27	0-32	0-42	0-63
3A TO66	0-27	0-27	0-32	0-42	0-52	0-70
5A TO66	0-39	0-52	0-54	0-59	0-75	0-88
6A TO64	0-39	0-52	0-54	0-62	0-75	0-88
7A TO48	0-52	0-55	0-62	0-67	0-84	0-89
10A TO48	0-55	0-63	0-67	0-68	1-07	1-32
10A TO48	0-58	0-62	0-67	0-77	0-87	1-00
30A TO48	1-27	1-54	1-78	1-93		4-40

## SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
	D07	8016	Plastic 8016	8016	8010	8010	T048
50	0-05	0-06	0-06	0-08	0-15	0-21	0-40
100	0-05	0-07	0-08	0-10	0-17	0-23	0-75
200	0-06	0-10	0-07	0-12	0-22	0-25	1-00
400	0-08	0-15	0-08	0-15	0-30	0-38	1-35
600	0-09	0-17	0-10	0-18	0-36	0-45	1-90
800	0-12	0-19	0-11	0-20	0-38	0-55	2-10
1000	0-14	0-30	0-12	0-25	0-48	0-65	2-60
1200		0-35	0-30	0-58	0-75	3-00	

**POST OFFICE TELEPHONE DIALS** 60p each.

**F.E.T.'S**  
 2N3819 31p 2N5458 35p  
 2N3820 55p 2N5459 44p  
 2N3821 30p 2N5460 88p  
 8N3823 31p MFP105 41p

**CADMIUM CELLS**  
 ORP12 48p  
 ORP60, ORP61 44p each

**FREE**  
 One 55p Pak of your own choice free with orders valued £4 or over

**DIACS FOR USE WITH TRIACS.**  
 BR100 (132) 41p each

**TRIACS**  
 VBOM 2A 9A 10A TO-6 TO-66 TO-48  
 3p 5p 8p  
 100V 3p 55 88  
 200V 55 88 99  
 400V 77 88 1-21

**2N3055**  
 115 WATT SIL POWER NPN 55p EACH

All prices include V.A.T. Giro No. 388-7006  
 Please send all orders direct to warehouse and despatch department

# BI-PAK

## P.O. BOX 6, WARE, HERTS

Postage and packing add 11p. Overseas add extra for airmail. Minimum order 55p. Cash with order please.  
**Guaranteed Satisfaction or Money Back**



# WILMSLOW AUDIO

**THE Firm for speakers!**

## SPEAKERS


EMI 13 x 8, 3, 8 or 15 ohm	£2-03
EMI 13 x 8, 150 d/c 3, 8 or 15 ohm	£2-25
EMI 13 x 8, 450 u/w 3, 8 or 15 ohm	£3-60
EMI 13 x 8 type 350 8 ohm	£3-25
EMI 6 1/2 in (3x55) 4 or 8 ohm	£2-80
EMI 8 x 5 d/cone roll/s 8 ohm	£2-50
Baker Group 25 3, 8 or 15 ohm	£3-60
Baker Group 35 3, 8 or 15 ohm	£7-50
Baker De Luxe 12in d/cone	£3-82
Baker Major 12in	£7-50
Kef 127	£4-47
Kef T15	£5-50
Kef B110	£3-16
Kef B200	£7-42
Kef B139	£10-72
Kef DN8	£1-92
Kef DN9	£1-37
Kef DN12	£4-12
Kef DN13	£2-75
Fane Pop 100W 8/15 ohm	£12-45
Fane Pop 60W 8/15 ohm	£12-28
Fane Pop 50W 8/15 ohm	£10-17
Fane Pop 25/25W 8/15 ohm	£5-84
Fane Pop 15W 8/15 ohm	£4-40
Fane Crescendo 15in 8 or 15 ohm	£27-50
Fane Crescendo 12A 100W 8 or 15 ohm	£24-20
Fane Crescendo 12B 75W bass 8 or 15 ohm	£24-20
Fane 30TT 8in d/c roll/s 8 or 15 ohm	£3-85
Fane 30BT 8in d/c cone 8 or 15 ohm	£2-54
Goodmans Axent 100 tweeter	£8-60
Goodmans 8P 8 or 15 ohm	£3-80
Goodmans 10P 8 or 15 ohm	£4-48
Goodmans 12P 8 or 15 ohm	£11-55
Goodmans 15P 8 or 15 ohm	£17-95
Goodmans 18P 8 or 15 ohm	£29-70
Goodmans Twinaxiom 8	£8-78
Goodmans Twinaxiom 10	£7-81
Eiac 9 x 5, 59RM109 15 ohm, 59RM114 8 ohm	£2-53
Eiac 6 1/2 in d/c roll/s 8 ohm	£3-22
Eiac 6 1/2 in d/c cone 8 ohm	£2-59
Eiac 4in tweeter TW4	£1-21
Wharfedale Bronze 8 RS/DD	£3-11
Wharfedale Super 8 RS/DD	£5-50
Wharfedale Super 10 RS/DD	£9-80
Coral 6 1/2 in d/cone roll/s 8 ohm	£2-42
Siran 6 1/2 in 3 or 8 ohm	£1-44
Richard Allan 12in d/c 3 or 15 ohm	£1-26
10in x 6in 3, 8 or 15 ohm	£1-82
8in x 5in 3 or 8 ohm	£1-38
7in x 4in 3 or 8 ohm	£1-38
2 1/2 in 64 ohm or 70mm 80 ohm	£1-38
Adastr Hiten 10in 10W 8 or 15 ohm	£2-80
Eagle DT33 dome tweeter	£2-45
Eagle HT15 tweeter	£3-86
Eagle CT5 tweeter	£1-25
Eagle CT10 tweeter	£2-54
Eagle MHT10 tweeter	£3-74
Eagle FR4	£4-45
Eagle Xover CN23, 28, 216	£1-15
Sp. matching transformer 3-15 ohm	£1-10
Celestion MF1000 25W horn 8 or 15 ohm	£10-45
Celestion PS8 (for Unilux)	£2-16
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00

Car Stereo speakers—ask for leaflet.

## SPEAKER KITS

Wharfedale Unit 3	£8-25
Wharfedale Unit 4	£14-50
Wharfedale Unit 5	£21-00
Richard Allan Tweeikit	£7-33
Richard Allan Triple 8	£10-76
Richard Allan Triple Assem.	£16-20
Richard Allan Super Triple	£19-36
Goodmans DIN 20	£8-58
Fane Mode One	£3-00

Kefkit 2 £24-75  
 Kefkit 3 £35-50  
 Peerless 2-8 £5-50  
 Peerless 10-2 £2-47  
 Peerless 20-2 £10-41  
 Helme XLK 25 (pair) £18-17  
 Helme XLK 50 (pair) £37-18  
 Stephen speaker kits and cabinets—send for free booklet "Choosing a Speaker"  
**PRICES INCLUDE VAT.**  
 Free with orders over £7—Hi-Fi Loudspeaker Enclosure 'book. All units guaranteed new and perfect. Prompt despatch. Carriage and insurance: speakers 35p each, speaker kits 75p each, tweeters and cross-overs 20p each.

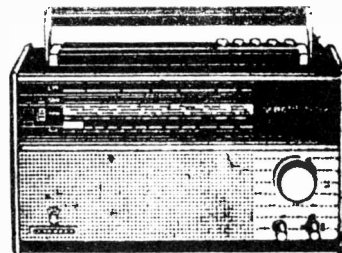

## RADIOS/CASSETTES/AMPS

Grundig RF310	£21-25
Grundig Signal 500	£27-00
Grundig Mariner TR865	£32-00
Grundig Elite Boy 500	£27-00
Grundig Melody Boy 500	£27-00
Grundig Melody Boy 1000	£38-75
Grundig Yacht Boy 210	£34-25
Grundig RF430 mains	£27-00
Grundig RF310 mains	£22-75
Grundig Top Boy	£16-75
Grundig Satellit 1000	£121-00
Grundig C230 cassette	£28-00
Grundig C402 cassette	£27-00
Tandberg TP41	£37-75
BASF 8301 radio/cassette	£58-00
Bush VTR178 5 band (inc. AIR)	£28-00
Trio KA2000A	£33-00
Trio KA2002	£41-00
ITT/KB Colt	£3-95
ITT/KB Golf Preset	£21-25
ITT/KB Weekend Auto	£18-00
ITT/KB Europa	£10-45
ITT/KB SL53 cassette	£22-82
ITT/KB Studio 60M cassette	£29-32
ITT/KB Studio 73 stereo cassette	£44-00
Koyo KTR1664 8 waveband	£40-00
Koyo KTR1770 11 waveband	£56-50
Koyo KTR1883 5 band (inc. AIR)	£23-50
TEC 200 Radio/Cassette	£31-00

Prices include VAT.  
 Carriage and insurance 75p. FREE with each radio—world radio stations book.

## PA/DISCO AMPLIFIERS (carr. and ins. £1)

Baker 100W	£46-00
Linear 30/40	£25-00
Linear 40/80	£30-00
Linear 80/100	£35-00

**FREE with speaker orders over £7**

"Hi Fi Loudspeaker Enclosures" book. All units guaranteed new and perfect. Prompt despatch.

Carriage and insurance 35p per speaker (tweeters and crossovers 20p). ALL PRICES QUOTED INCLUDE VAT.

## WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. Radios, etc.: 10 Swan Street, Wilmslow, Cheshire, SK9 1HF. Telephone: Wilmslow 29599.

## 4-STATION INTERCOM



£8-75

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 17p.

**MAINS INTERCOM (new model)**  
 No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £18-95. P. & P. 60p extra.

## INTERCOM/BABY ALARM



£4-85

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft connecting wire. Complete with battery. P. & P. 33p.



£4-25

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 27p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/12)  
 169 KENSINGTON HIGH STREET, LONDON, W.8

## UNDERSTANDING SOLID-STATE ELECTRONICS

Basic course in semiconductor theory, Texas Inst. Price £1-40

104 EASY TRANSISTOR PROJECTS YOU CAN BUILD by R. M. Brown. Price £1-30.

INTEGRATED CIRCUIT POCKET BOOK by R. G. Hibberd. Price £2-60.

HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER by P. J. Guy. Price £1-60.

50 PHOTOELECTRIC CIRCUITS AND SYSTEMS by P. S. Smith. Price £1-35.

COLOUR TV WITH PARTICULAR REF. TO PAL SYSTEM by G. N. Patchett. Price £3-10.

GETTING STARTED WITH TRANSISTORS by L. E. Garner. Price £1-30.

TRANSISTOR AUDIO AND RADIO CIRCUITS by Mullard. Price £1-90.

FOUNDATIONS OF WIRELESS AND ELECTRONICS by M. G. Scroggie. Price £2-00.

THE RADIO AMATEUR'S HANDBOOK 1973 by A.R.R.L. Price £2-95.

BEGINNER'S GUIDE TO PRACTICAL ELECTRONICS by R. H. Warring. Price £1-60.

ELECTRONIC ORGAN SERVICING GUIDE by R. G. Middleton. Price £2-40.

\*ALL PRICES INCLUDE POSTAGE\*

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET  
 LONDON W2 1NP

Phone 01-723 4185  
 Closed Saturday 1 p.m.



# COMPREHENSIVE HOME CONSTRUCTOR KITS

# AS SPECIFIED IN THE **P.E. RONDO**

## COMPLETE QUADRAPHONIC HI-FI SYSTEM

CBS SQ* MATRIX DECODER <small>*TM CBS INC.</small>	COMPLETE KIT	<b>£8.00</b>	POST FREE + V.A.T. 80p INC. CBS LICENCE FEE +
PREAMPLIFIER BOARD	COMPLETE KIT	<b>£3.00</b>	POST FREE + V.A.T. 30p
MASTER VOL./TONE/ BALANCE BOARD	COMPLETE KIT	<b>£8.50</b>	POST FREE + V.A.T. 85p
POWER AMP. BOARD & HEATSINK (STEREO PAIR)	COMPLETE KIT PER BOARD	<b>£7.50</b>	POST FREE + V.A.T. 75p
POWER SUPPLY BOARD COMPLETE		<b>£5.00</b>	POST FREE + V.A.T. 50p
MAIN SMOOTHING CAPACITORS		<b>0.75</b>	POST FREE + V.A.T. 7p
MAINS TRANSFORMER	COMPLETE KIT	<b>£6.25</b>	POST FREE + V.A.T. 62p
CHASSIS—PUNCHED & DRILLED	COMPLETE KIT	<b>£2.25</b>	POST FREE + V.A.T. 22p
WOODEN CASE		<b>£1.75</b>	POST FREE + V.A.T. 17p
HARDWARE PACK		<b>£2.00</b>	POST FREE + V.A.T. 20p
CONTROL SECTION FACIA		<b>£3.50</b>	POST FREE + V.A.T. 35p

THE COMPLETE P.E. RONDO SYSTEM IS AVAILABLE AS PUBLISHED

# SONAX

## ELECTRONICS

SPENCER HOUSE  
BRETENHAM ROAD  
EDMONTON  
LONDON, N.18

Telephone  
**01-807 5544**

TRADE ENQUIRIES WELCOME

PLEASE SEND ME:

CBS SQ DECODER  
PREAMPLIFIER BOARD  
MASTER VOLUME BOARD  
POWER AMP. BOARDS  
POWER SUPPLY BOARD  
SMOOTHING CAPACITORS  
MAINS TRANSFORMER  
CHASSIS  
WOODEN CASE  
HARDWARE PACK  
CONTROL FACIA

BLOCK CAPITALS PLEASE

NAME .....

ADDRESS .....

PLEASE TICK BOX


MONEY  
ENCLOSED

£ .....

CHEQUE  
P.O.  
MONEY ORDER

P.E. 12

# BIG Discounts

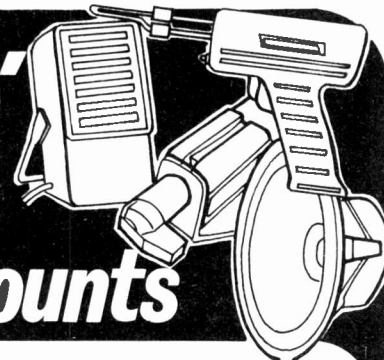

## ALL PRICES INCLUDE V.A.T.

SPEAKER BARGAINS		GODMANS 6 1/2 in 8 ohm Dual cone	
EMI 13in x 8in 3, 8 or 15 ohm		1-60	
Plain	2-05	FANE, 7in x 4in, 3 or 8 ohm	1-00
With Co-Axial Tweeter	2-20	8in Dual Cone 8 ohm	2-40
Twin Tweeter	3-55	CELESTION 8in, 15 ohm	1-85
Type 360, 8 ohm, 20W	8-00	ADASTRA 10in, 8 or 15 ohm,	2-75
6 1/2in, 8 ohm, 10W	2-70	10W	
8in, 8 ohm, 10W	3-75	BAKER GROUP 25 12in, 8 or	6-45
12in, 8 ohm, 20W	5-50	15 ohm, 25W	0-25
8in x 5in, C/Mag. 5W	1-20		P. & P. 0-25
8in x 5in, Dual cone 8 ohm,		5in, 8 ohm, 5W C/Mag.	0-85
10W	2-45	2 1/2in, 8 ohm or 64 ohm	0-80
ELAC 8in 8 ohm Dual cone	2-10		P. & P. 0-10
<b>TWEETER AND CROSSOVER</b>		Dome Tweeter 8 ohm, 30W	
EMI 3 1/2in, 3 or 8 ohm C/Mag.	1-00	Crossovers CN23 (3 ohm), CN28	4-00
Cone Tweeter 8 or 15 ohm, 10W	1-90	(8 ohm), CN216 (16 ohm)	1-00
Cone Tweeter 8 ohm, 3W	1-00		P. & P. 0-10
Horn Tweeter 8 ohm, 20W	3-50		
<b>KIT FORM CABINETS, TEAK VENEER</b>		12in x 11in cutout	
ANTEX CN240 15W		18in x 11in x 9in with 13in x	8-25
8in x 5in or 6 1/2in and 3 1/2in		8in cutout for EMI 350	4-25
cutout	2-45		P. & P. each 0-35
17in x 10in x 6in with 8in or			
<b>MICROPHONES</b>		TW206	
CM20 Crystal Hand	0-50	CONDENSER MIKE 600 ohm,	5-75
CM70 Planet stick metal,		uni-dir	
switch crystal	1-55	Cassette Stick Mike with R.	7-90
DM160 Dynamic uni-dir, ball		Control on/off switch (2-5	
metal	3-95	and 3-5mm J/Ply)	
UD130 50K/600 ohm, uni-dir,			P. & P. 0-15
ball metal	4-50		
<b>SOLDERING IRONS</b>		spare Bib, etc.)	
ANTEX CN240 15W	1-60	X25 25W (low leakage)	2-65
SK1 Kit (15 watt iron, 2			1-10
			P. & P. 0-10
<b>CARTRIDGES</b>		BSR 8CSM Stereo ceramic	
ACOS GP91/28C or GP91/38C		SX5H Stereo crystal	2-25
Stereo comp.	1-00	SX5M Stereo crystal	1-60
GP93/1 Stereo crystal	1-35	X5H Mono/stereo	1-25
GP94/1 Stereo crystal	1-75	X5M Mono/stereo	1-95
GP95/1	1-35	GOLDRING G800	3-85
GP96/1	1-75	G850	2-95
GP101	0-75	GOLDRING G800/G850	1-95
			P. & P. 0-05
<b>SONOTONE 9THAC Stereo ceramic, diam.</b>		STYLI FOR ABOVE	
19-TI Stereo crystal	0-60	Sapphire 85p	1-25
		D. Diamond	
<b>BATTERY ELIMINATORS</b>		socket 6, 7.5 or 9 d.c. output	
240V input 6, 7.5 or 9 300mA	2-20	at 300mA	2-20
12V d.c. input (fits in car lighter)			P. & P. 0-10
<b>TAPES</b>		7in 65p	
5in	45p	70p	110p
5 1/2in	55p	85p	0-30
		4 or more lot	0-30
<b>LOW NOISE CASSETTES</b>		Cassette Head Cleaner	
C60	1-5	6-10	0-85
C90	35p	33p	P. & P. 1-5 each
C120	45p	43p	6-10 lot
	55p	52p	0-15
		11-20 post free	0-03
<b>PLASTIC LIBRARY CASES for</b>		7in Reels	
5in Reels	0-18	CASSETTE CASES	0-10
6 1/2in Reels	0-22	P. & P. 1-3 each 5p; 4 or more	0-20
<b>BIB ACCESSORIES</b>		<b>SPECIAL OFFER</b>	
Tape Editing Kit, Ref. 23	1-30	BUSH Stereo System with Independent	
Recording Tape Splicer, Ref. 20	1-15	Volume, Bass and Treble controls	
Cassette Tape, Editing, Ref. 24	1-40	on each Speaker for optimum repro-	
Cassette Salvage Kit, Ref. 29	0-40	duction. Using Garrard 2025TC Auto	
12" x Cassette Case, Ref. 34	1-00	Change Deck in deluxe teak plinth	
Stylus Balance, Ref. 32A	1-15	and cover. Today's Value £49.50.	
Spirit Level, Ref. 46	0-50	OUR PRICE £27.50 + £1.50 P. & P.	
Hi-Fi Stereo Test Cassette	1-80	12 months' Guarantee by the Maker.	
Groove-Kleen Record Cleaner	1-90	<b>THIS IS A BARGAIN NOT TO</b>	
	P. & P. 0-10	<b>BE MISSED!</b>	

Send 25p for COMPLETE CATALOGUE, refundable upon first order.  
ALL OUR MERCHANDISE IS FULLY GUARANTEED

## Riversdale Electronics

Mail Order Department PE/12  
P.O. Box 470, Manchester M60 4BU.

# RST VALVE MAIL ORDER CO.


16a WELLFIELD ROAD, LONDON SW16 2BS  
SPECIAL EXPRESS MAIL ORDER SERVICE

Express postage 1p per transistor, over ten post free  
INTEGRATED CIRCUITS 5p + 1p each added

5p	10p	15p	20p	25p	30p	35p	40p	45p	50p	55p	60p	65p	70p	75p	80p	85p	90p	95p	1.00	1.05	1.10	1.15	1.20	1.25	1.30	1.35	1.40	1.45	1.50	1.55	1.60	1.65	1.70	1.75	1.80	1.85	1.90	1.95	2.00	2.05	2.10	2.15	2.20	2.25	2.30	2.35	2.40	2.45	2.50																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																																				
IN21	AF212	BY210	OAZ2909	ZS170	AS223	BY211	OAZ210	ZS271	AS224	BY212	OAZ211	ZS107	AS225	BY213	OAZ222	ZS108	AS226	BY214	OAZ223	ZS109	AS227	BY215	OAZ224	ZS110	AS228	BY216	OAZ430	ZS316	AS434	BY422	OAZ431	ZS317	AS435</

# RAYMER ELECTRONICS
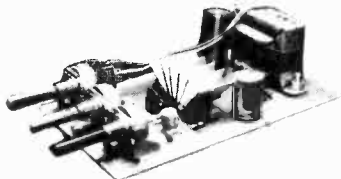
## MICROCHIP SERIES HIGH FIDELITY MODULES



### RE 500

Advanced integrated Hi-Fi Amplifier only requires connection to mains speaker and input.

Specifications: load imp 4-16 ohm. Output: 5 watts. Frequency response 20Hz to 35kHz  $\pm 3\text{dB}$ .

Total distortion less than 1%.


I/P Imp 100k ohm Nom.

£6-30. Post free.

Size: 140 x 80 x 45mm.

## MICROCHIP I.C.

5 watts RMS

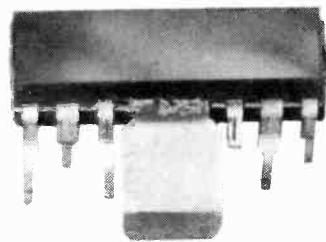


A general purpose Audio i.c. for the constructor capable of 5 watts RMS O/P at less than 1% total distortion, forms an ideal basis for an excellent Hi-Fi system.

Free Data I.C. £1-50.

Data, Printed Circuit Board, 75p. Post paid.

## RE 602S

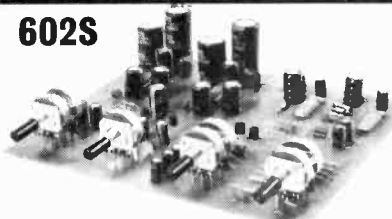

This amplifier forms an ideal basis for the construction of an advanced stereo system at minimum cost with complete ease of assembly. Designed for use with magnetic preamp inputs and main amplifiers on same PCB.

Specifications:

Power O/P 5W RMS per channel (simultaneously).

Total distortion less than 1%.

Active tone controls.

Bass  $\pm 10\text{dB}$ , Treble  $\pm 12\text{dB}$  @ 100Hz-10kHz.

Freq. response 20Hz to 35kHz  $\pm 3\text{dB}$ .

Sensitivity for full O/P 35mV (Ceramic), 3mV (Magnetic).

Input impedance 60K and 200K Ohms.

Load impedance 8-16 ohms.

Operating Voltage 18-28 Volts D.C.

£16-50. Post free.

Power Supply Extra (RE 30 psu)

## COMPLETE QUADRAPHONIC AMPLIFIER KIT : RE 4K

A Hi-Fi kit comprising CBS SQ decoder, preamplifier and four channel main amplifier. All modules built and tested.

Specifications:

Similar to the Quadrix system (see below) but with four channel main amplifier giving 40 watts total peak power.

This is an opportunity to experience quadrasonic sound at the very minimum of cost.



(Power Amp only shown)

£39-00. Post free

Power Supply Extra (RE 35 psu)

### POWER SUPPLIES RE 30 PSU

Input 240V AC  
O/P 26V DC of 0.6 Amps  
£3-60. Post free

### RE 35 PSU

Input 240V AC  
O/P 26V DC of 1.2 Amps  
£4-60. Post free

## RE QUADRIX

This is a high quality CBS specification SQ decoder with Hi-Fi stereo amplifier. Designed to allow the conversion of any stereo system to full quadrasonic performance with minimum cost. Extraordinary new presence and reality of sound. More than 20 Watts total peak power.

Specifications:

#### Decoder

I/P impedance 40K ohms  
O/P impedance <300 ohms  
Nominal I/P 100mV RMS  
Front separation > 60dB  
Rear separation > 20dB

#### Amplifier

Power O/P 5W RMS per channel (simultaneously)  
Distortion at full O/P less than 1%  
Sensitivity for full O/P 100mV  
Active tone control Bass  $\pm 10\text{dB}$ , Treble  $\pm 12\text{dB}$  @ 100Hz-10kHz  
Load impedance 8-16 ohms



£49-00. Post free

**Special Offer** SQ records (full quadrasonic sound) available direct. Comprehensive list free on request.

### GUARANTEE

ALL PRODUCTS ARE GUARANTEED AGAINST FAILURE FOR A PERIOD OF 12 MONTHS AND WILL BE SERVICED FREE OF CHARGE IF PURCHASED DIRECT AND REFUNDED TO US FOR REPAIR.

NAME .....

ADDRESS .....

PLEASE SEND .....

(enclose PO/cheque/M.O.) .....

**RAYMER ELECTRONICS LTD.**  
Stanley Road, Cambridge CB5 8LB, England.  
(0223) 54414. Reg. No. 1021295

PLEASE ADD  
10% FOR V.A.T.

# LARGE STOCKS, ATTRACTIVE DISCOUNTS DEPENDABLE SERVICE

Everything brand new and to makers' specifications.

# ELECTROVALUE

## Electronic Component Specialists

### TRANSISTORS BY SIEMENS AND NEWMARKET

2N3055 npn silicon power	60p
AC153K pnp germanium low power	32p
AC176K npn germanium low power	32p
AD161 npn germanium medium power	42p
AD162 pnp germanium medium power	40p
AF139 pnp germanium UHF	49p
NPN: BC107 13p, BC108 12p, BC109 13p, BC167 11p, BC168 10p, BC169 11p.	
PNP: BC177 21p, BC178 19p, BC179 21p, BC257 12p, BC258 11p, BC259 13p.	

Standard groupings available.

BD135 npn medium power	37p
BD136 pnp medium power	38p

### DIODES

OA90, OA91, OA95, 6p each; OA200, 9p; OA202, 10p.


Other semiconductors: AC128, 17p; AF117, 32p; BFY51, 19p. Full lists and technical data will be found in Catalogue No. 6. See also amendments list.

Send S.A.E. for latest supplement of additional lines and price amendments to our No. 6 Catalogue

**ZENER DIODES** full range E24 values: 400mV: 2.7V to 36V, 14p each; 1W: 6.8V to 82V, 21p each; 1.5W: 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

### DIN PLUGS AND SOCKETS

by Hirshmann, 4A rating

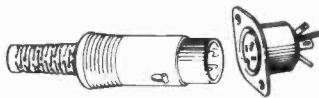


2 way LS —socket 10p, plug 12p  
3 way scr.—socket 10p, plug 12p  
5 way scr.—socket 11p, plug 15p

### TRANSISTOR ACCESSORIES

TO3 cover, 7p; Heat sinks 1°C/W, type 6W1, undrilled, 60p.
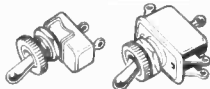
### SWITCHES

1011 SPST toggle, 20p; 409 DPDT toggle, 29p (these are chrome plated, 2.5A rating); 7201 sub-miniature DPDT 250V a.c./2A, 48p.




### ROTARY SWITCHES

Radiospares Miniature Mako-switch (in assembly kit form). Shaft, 48p. Wafers, MBB-2P5W, IP11W: BBM1P12W, 2P6W, 3P4W, 4P3W, 6P2W, 32p each.

### WAVECHANGE SWITCHES

IP12W, 2P6W, 3P4W, 413W, 24p each.

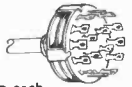

### ELECTROLYTIC CAPACITORS

Rated voltage:	3V	6.3V	10V	16V	25V	40V	63V	100V
Capacity $\mu$ F	0.47	—	—	—	—	—	10p	7p
	1.0	—	—	—	—	—	10p	7p
	2.2	—	—	—	—	—	7p	8p
	4.7	—	—	10p	—	—	7p	8p
	10	—	—	—	—	—	7p	8p
	22	—	7p	7p	—	—	7p	9p
	47	7p	—	8p	8p	—	7p	12p
	100	8p	7p	7p	7p	—	9p	11p
	220	7p	8p	8p	8p	—	10p	17p
	470	8p	9p	9p	10p	—	12p	24p
	1,000	10p	12p	12p	17p	—	20p	40p
	2,200	14p	17p	22p	25p	—	36p	40p
	4,700	25p	28p	37p	41p	—	—	—
	10,000	40p	43p	—	—	—	—	—

Prices subject to amendment by the manufacturer.

### RESISTORS - 10%, 5%, 2%

Code	Power	Tolerance	Range	Values available	i to 9	10 to 99	100 up
C	1/20W	5%	82 $\Omega$ - 220K $\Omega$	E12	9	8	7.5
C	1/8W	5%	4.7 $\Omega$ - 470K $\Omega$	E24	1	0.9	0.75 nett
C	1/4W	5%	4.7 $\Omega$ - 10M $\Omega$	E12	1	0.9	0.75 nett
C	1/2W	5%	4.7 $\Omega$ - 10M $\Omega$	E24	1.2	1	0.95 nett
C	1W	5%	4.7 $\Omega$ - 10M $\Omega$	E12	2.5	2	1.6 nett
MO	1/2W	2%	10 $\Omega$ - 1M $\Omega$	E24	4	3	2 nett
WW	1W	10%	120 $\Omega$ - 3.9 $\Omega$	E12	7	7	6
WW	3W	5%	1 $\Omega$ - 10K $\Omega$	E12	7	7	6
WW	7W	5%	1 $\Omega$ - 10K $\Omega$	E12	9	9	8

Codes: C = carbon film, high stability, low noise. MO = metal oxide, Electroslit TR5, ultra low noise. WW = wire wound, Plessey.

Values: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82

E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

### POLYCARBONATE—5% TOLERANCE

250V up to 0.1  $\mu$ F: 100V, 0.1  $\mu$ F and above.  
0.01; 0.012; 0.015; 0.018; 0.022; 0.027; 0.033; 0.047; 0.056; 4p each.  
0.068; 0.082; 0.1; 0.12; 0.15; 4p each.  
0.18; 0.22; 5p each.  
0.27; 0.33; 6p.  
0.39 7p.  
0.47 8p.  
0.56 10p.  
0.68 11p.  
1  $\mu$ F 13p.  
Prices subject to amendment by the manufacturer.


**Minitron Digital Counter**  
Type 3015F. Seven Filament segment indicators: to make 0-9 + decimal point. Compatible with standard logic modules, nett £2.  
Decoder driver type FLL 121T nett £1.36. DIL socket, nett £2.

Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.)
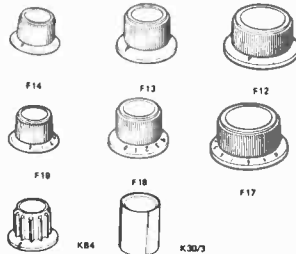
### KNOBS

All grub screw fitting for  $\frac{1}{8}$ in shafts. Black. For other types —see Catalogue No. 6, p. 54.

F.14 (20mm) pack of 2, 32p; F.13 (26mm) pack of 2, 38p; F.12 (33mm) pack of 2, 40p; F.19 (20mm) pack of 2, 32p; F.18 (26mm) pack of 2, 38p; F.17 (33mm) pack of 2, 40p; KB.4 (20mm) pack of 4, 40p; K30/3 (17mm) aluminium, 24p each.



### POTENTIOMETERS

Rotary, carbon track, double wiper

SINGLE P20 100  $\Omega$  to 2.2M  $\Omega$ , 12p; P20 log. 4.7K  $\Omega$  to 2.2Meg, 12p; JP20 log. 4.7K  $\Omega$ , to 2.2M  $\Omega$ , 12p; Dual gang lin. 4.7K  $\Omega$  to 2.2M  $\Omega$ , 42p; Dual log. 4.7K  $\Omega$  to 2.2M  $\Omega$ , 42p; Log/antilog, 10K, 22K, 47K, 1M  $\Omega$  only, 42p; Dual antilog, 10K only, 42p. Any type with 2A D.P. mains switch, 12p extra.

Only decades of 10, 22 and 47 available in ranges quoted.


DUAL CONCENTRIC DP20 in any combination of P20 values, 60p; with switch, 72p.

SLIDER Lin. or log. 10K to 1 meg. in all popular values, each 26p.

Control knobs blk./white/red/yel./gr./blue/dk. grey/lt. grey, 5p each.

CARBON SKELETON PRE-SETS

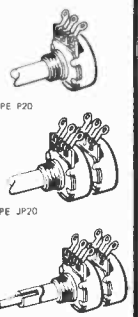Small high quality, PR lin. 100  $\Omega$ , 220  $\Omega$ , 470  $\Omega$ , 1K, 2K2, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 5M, 10M  $\Omega$ . Vertical or horizontal mounting, 5p each.



### TRANSFORMERS—MAINS

MT3 30V/2A plus 4 taps	£2-85
MT103 50V/1A plus 4 taps	£2-55
MT104 50V/2A plus 4 taps	£3-50
MT127 60V/2A plus 4 taps	£3-80
I3T05 13V/1A, CT	£1-25
28T05 12+12V, 2-0-2V.	£1-65

### BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World." Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14-90 Plus 60p part cost of carr.

Equaliser Assembly, £2.  
Loudspeaker Unit 59RM109, £2-45.  
Cabinet Kit (to Baxandall design), £10-45.

### DISCOUNTS

All items offered for sale in accordance with our stated terms of business, copy of which available on request. Not allowed on net price items. 10% on orders for £5 or more, 15% on orders of £15 or more. Prices subject to alteration without prior notice. Prices quoted DO NOT include V.A.T. Orders received from U.K. customers must be accompanied by an additional 10% of the nett value for V.A.T.

Overseas orders are exempt.


POSTAGE AND PACKING FREE

SURCHARGE 10p on small mail orders under £2. Overseas orders carriage and insurance charged at cost. U.S.A. CUSTOMERS please contact ELECTROVALUE, AMERICA, P.O. BOX 27, Swarthmore, PA 19081.

# ELECTROVALUE

(Dept. PE12, 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB)  
Hours: 9—5.30, Sat. 1 p.m. Tel.: Egham 3603 Telex 264475  
Eng. Reg. No. 1047769 Registered Office: 28 St. Jude's Rd., Englefield Green, Egham, Surrey TW20 0HB
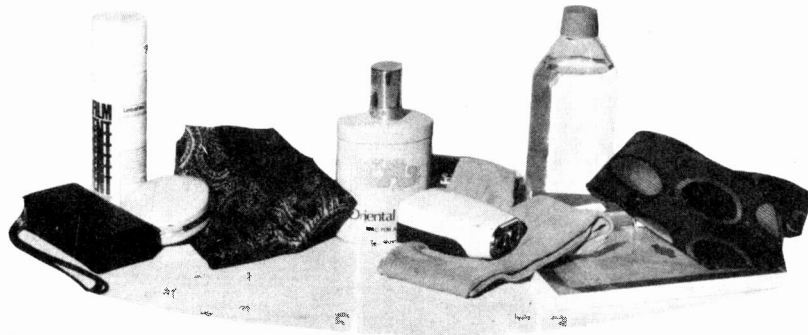
# If you're stuck for original Christmas presents ideas



## AMTRON offers you a choice of 200



Amtron produce a range of 200 electronic kits which provide something of interest for both dabbler and expert. A few examples are: Power Supplies; Pre-amplifiers;


L.F. Instruments; Amateur & Radio control transmitters and receivers; Measuring Instruments; I.C. Digital Equipment etc. Complete blister packs contain full instructions plus solder.

*THE BIG NAME IN  
ELECTRONIC KITS*



AMTRON U.K. LTD · 4 & 7 CASTLE STREET · HASTINGS · SUSSEX · TEL HASTINGS 2875
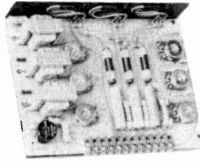
### Mk III Sound to Light Unit Chassis Version




The audio drive voltage is derived directly from the amplifier output or across the speaker load. The unit converts the audio-frequency signals into a three-coloured light display when used with coloured flood lamps or similar; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size: 9in x 7in x 3in. Price £27.50.


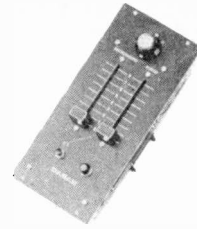
### MN3 3 Channel I.C. Mixer Kit

Three channel I.C. audio mixer kit MN3 is specially designed for the home constructor or educational project. Suitable for use in domestic audio, discotheque and simple p.a. applications. The MN3 mixer kit has the following features: Advanced design using 5 ICs; Slider fader level controls mounted directly to p.c. board; Full range Bass and Treble controls; Uses top grade components with fibreglass ready-drilled and tinned printed circuit board and the unit may be operated from twin 9V batteries (PP3) if required.

As optional extras, an attractive ready-punched facia panel and control knobs are available. The unit is available as a ready built mixer with facia. Size: 9.5in x 4.8in x 1.5in (with facia). Construction manual available separately at 25p. Kit Price £11.



### STL/1 Single Channel Sound to Light Unit


Single channel "Sound to Light" unit with 60mm slider fader controls for audio trigger level and background load dimmer. This unit is switchable for response to High, Mid, and Low frequency audio signals, selected by facia control. A D.J. "pulse-flash" push button is fitted for manual flashing of the lamp load together with neon load indicator. Maximum Load: 1kW at 240V a.c. Size: 8in x 3.6in x 3in. Price £14.30.

### Practical Electronics "Scorpio" Electronic Ignition System Kit



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc. Case size: 7.25in x 4.5in x 2in approx. Complete assembly and wiring manual 25p. Price £12.10.

### STL/3 Sound to Light Unit

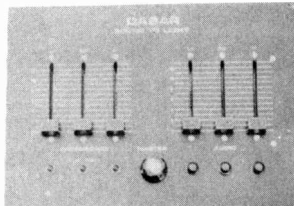

The performance of this unit is similar to the Mk III chassis version above, but is provided with an attractive black anodised facia panel and designed to mount directly into equipment desks or cabinets. High, Mid, and Low frequency channel sensitivity controls employ 60mm slider faders for present-day attractive appearance and ease of use. Size: 11in x 8.5in x 4in. Price £42.35.

## AUDIO EFFECTS

CREATE "PHASE" EFFECT ON YOUR RECORDS, TAPES, ETC., UNIQUE CIRCUITRY ENABLES YOU TO CREATE PHASE EFFECT AT THE TURN OF A KNOB. OPERATES FROM 9V BATTERY (NOT SUPPLIED). COMPLETE KIT OF COMPONENTS WITH PRINTED CIRCUIT BOARD AND FULL INSTRUCTIONS. KIT PRICE £2.86.

All prices quoted include postage and VAT. S.A.E. for further details.

**DABAR ELECTRONIC PRODUCTS**  
98 LICHFIELD STREET, WALSALL  
STAFFS WS1 1UZ



## become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

**free!**

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**  
P.O. BOX 156, JERSEY

NAME: \_\_\_\_\_

ADDRESS: \_\_\_\_\_

EB 123

BLOCK CAPS please

### TRANSISTORS

AC126 14p	AF180 45p	BC158 14p	BF180 32p	BFY51 21p
AC127 16p	AF181 43p	BC159 14p	BF181 32p	2N3053 23p
AC128 14p	AF239 44p	BC177 20p	BF184 35p	2N3054 57p
AC141K 24p	BC107 12p	BC183L 14p	BF185 35p	2N3055 60p
AC142K 24p	BC108 10p	BC184L 12p	BF186 45p	TIP29 66p
AC176 20p	BC109 12p	BC187 22p	BF194 15p	TIP30 75p
AC187 18p	BC113 25p	BC294 16p	BF195 15p	TI591 48p
AC187K 24p	BC114 30p	BC440 50p	BF196 15p	
AC188K 24p	BC115 20p	BC460 68p	BF197 15p	
AD142 45p	BC116 20p	BD124 80p	BF200 32p	
AD149 45p	BC117 15p	BD131 60p	BF258 40p	
AD161 34p	BC125 14p	BD132 60p	BF259 40p	
AD162 34p	BC142 25p	BD139 63p	BF337 23p	
AF115 21p	BC143 25p	BCX32 £2.00	BF42 44p	
AF116 21p	BC147 13p	BF115 25p	BF44 44p	OA91 7p
AF117 21p	BC148 13p	BF121 35p	BFX84 40p	OA202 9p
AF118 49p	BC149 13p	BF158 19p	BFX88 30p	1N4148 4p
AF139 40p	BC154 20p	BF167 20p	BFX89 67p	BY127 11p
AF178 45p	BC157 14p	BF179 39p	BFY50 21p	1N4006 8p

### RESISTORS METAL FILM

5% TOL.  
1/4W, 1/2W, 1W, E12 values to 2.7M all 1p each.  
1W to 10M E12 values 3p each;  
2W to 10M E12 values 4p each;  
5W wire wound, 10W wire wound 8p and 9p each. See Cat. for values.

### POTENTIOMETERS-CARBON TRACK

5K, 10K, 25K, 50K, 100K, 250K, 500K, 1M.  
Log or lin less switch 11p  
Log or lin with switch 23p  
Dual log less switch 250K.  
500K, 1M, 2M, only 39p  
Dual lin less switch 5K, 10K, 25K, 50K, 100K, only 39p  
Dual log with switch 10K, 100K, 250K, 500K, 1M only 55p

### JACK PLUGS AND SOCKETS

Standard insulated 11p; Standard screened 18p;  
Stereo insulated 22p; Stereo screened 30p;  
3.5mm insulated 8p; 3.5mm screened 12p;  
Standard socket switched 17p; Stereo socket switched 21p; 3.5mm socket switched 6p;  
Standard line socket 15p; Stereo line socket 22p;  
3.5mm line socket 10p.

### PHONO-D.I.N. PLUGS AND SOCKETS

Phono plug insulated 7p; Phono plug screened 11p; Phono line socket screened 12p; Metal coax plug 8p; 2, 3, 5 pin 180°, 240°, D.I.N. plugs 12p; 4, 6, 7 pin plugs 15p; 2, 3, 5 pin 180° line sockets 13p; 2, 3, 5 pin 180° chassis sockets 7p.

### CABLES AND SCREENED WIRES

Min. mike cable single 7p/metre; Min. twin mike cable 11p/metre; Pick up wire single 7p/metre; Pick up wire twin 11p/metre; Stereo screened twin 10p/metre; 4 core individually screened 14p/metre; Speaker wire twin coded 6p/metre.

## E. A. HALL (ELECTRONICS)

The Manse, Little Brington, Northampton NN7 4HX

Mail Order Only. C.W.O. Postage and packing 10p per order. Detailed Catalogue 6p. Please add V.A.T. on total order incl. postage and packing. Many other items in our catalogue.

# NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT  
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN - PNP
- 4 Transistor Push Pull Amplifier
- 3 Transistor Push Pull Amplifier
- 7 Transistor Loud-speaker Radio MW/LW
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- One Transistor Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier
- Parts price list and plans 40p (free with parts)

TOTAL BUILDING COSTS

**£7-23** P.P. & INS. 44p  
(Overseas P.P. £1-85p)  
(+10% VAT 72p)

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 3 1/2" Loudspeaker ● Mica Baseboard ● 3 1/2-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs ● Ready Wound MW/LW/FW Coils ● Ferrite Rod ● 6 1/2 yards of wire ● 1 yard of sleeving, etc. ● Plans 50p.

## NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange. Attractive all white case with red grille and carrying strap. Size 9 1/2in x 7in x 2 1/2in approx. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£6-95** P.P. & INS. 44p  
(+10% VAT 89p) (OVERSEAS P. & P. £1-85)



## NEW EVERYDAY SERIES

Build this exciting New series of designs

**EV5** 5 Transistors and 2 diodes. MW/LW. Powered by 4 1/2 volt Battery. Ferrite rod aerial, tuning condenser, volume control, and loudspeaker. Attractive case with red speaker grille. Size 9in x 5 1/2in x 2 1/2in approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£2-73** P.P. & INS. 30p  
(+10% VAT 27p) (OVERSEAS P. & P. £1-25)

**EV6** Case and looks as above. 6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod 3" aerial, loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£3-60** P.P. & INS. 30p  
(+10% VAT 36p) (OVERSEAS P. & P. £1-25)

**EV7** Case and looks as above. 7 transistors and 3 diodes. Six wavebands. MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3" Loudspeaker. Parts price list and easy build plans 20p. Free with parts.


TOTAL BUILDING COSTS **£4-08** P.P. & INS. 31p  
(+10% VAT 40p) (OVERSEAS P. & P. £1-85p)

## ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

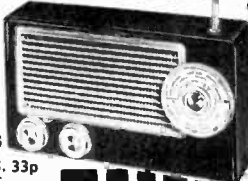TOTAL BUILDING COSTS **£6-98** P.P. & INS. 47p  
(+10% VAT 69p) (OVERSEAS P. & P. £1-85)



## ROAMER TEN WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS. MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND. VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND. Latest 4" 2 watt Ferrite Magnet Loudspeaker. Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

TOTAL BUILDING COSTS **£8-50** P.P. & INS. 52p  
(+10% VAT 85p) (OVERSEAS P. & P. £1-85)

Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£8-50** P.P. & INS. 52p  
(+10% VAT 85p) (OVERSEAS P. & P. £1-85)



## EDU-KIT

Build Radios, Amplifiers, etc. from easy stag diagrams

Five units including master unit to construct.

Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: Fine tone 3" moving coil Speaker: Terminal Strip: Ferrite Rod Aerial: 2 Plugs and Sockets: Battery Clips: 4 Tag Boards: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).


TOTAL BUILDING COSTS **£5-50** P.P. & INS. 33p  
(+10% VAT 55p) (OVERSEAS P. & P. £1-85)

## RADIO EXCHANGE LTD

\*Callers side entrance "Lavelle" shop  
\*Open 10-1. 2.30-4.30. Mon.-Fri. 9-12 Sat.
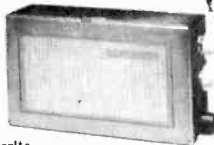
## POCKET FIVE

3 Tunable wavebands. MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, moving coil loudspeaker. Attractive Black and Gold Case. Size 5 1/2in x 1 1/2in x 3 1/2in approx. Plans and parts price list 15p (FREE with parts).



Total Building Costs **£2-28** P.P. & INS. 26p  
(+10% VAT 22p) (OVERSEAS P. & P. £1-25)



## TRANSONA FIVE

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (FREE with parts).

Total Building Costs **£2-50** P.P. & INS. 26p  
(+10% VAT 25p) (OVERSEAS P. & P. £1-25)

## TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

8 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£4-48** P.P. & INS. 33p  
(+10% VAT 44p) (OVERSEAS P. & P. £1-25)

## ROAMER SIX CASE AND LOOKS AS TRANS EIGHT

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS **£3-98** P.P. & INS. 31p  
(+10% VAT 39p) (OVERSEAS P. & P. £1-85)

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA  
Tel. 0234 52867 Reg. No. 788372

I enclose £ \_\_\_\_\_ for \_\_\_\_\_


Name \_\_\_\_\_

Address \_\_\_\_\_

P.E.58
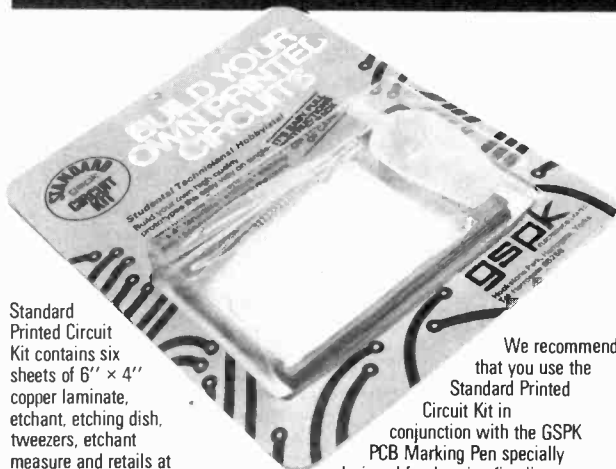
# THE D-I-Y ELECTRONICS KIT FOR STUDENTS, TECHNICIANS AND HOBBYISTS

Now available from all leading electrical shops, the complete D-I-Y printed circuit kit. Save time and money with this latest development by GSPK in the field of home electronics.




Standard Printed Circuit Kit contains six sheets of 6" x 4" copper laminate, etchant, etching dish, tweezers, etchant measure and retails at **£4.95** including VAT plus postage and packaging -30p.

We recommend that you use the Standard Printed Circuit Kit in conjunction with the GSPK PCB Marking Pen specially designed for drawing fine line etchant resistant circuits on copper laminate. Recommended retail price including VAT is **£1.35** plus postage and packaging-15p.



The GSPK Signal Booster is designed to improve car radio reception in towns and built-up areas. It's also claimed to eliminate any loss of signal caused by rear mounted aerials with long leads. The solid state unit is plugged into the aerial lead and takes its power supply from the car battery. Is manufactured in positive and negative earth versions and costs **£3.29** including VAT plus postage and packaging-15p.

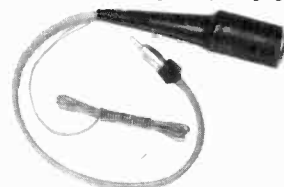

Our products are available from all leading electrical stores or write direct to-

**gspk**  
(Sales) Limited,

Hookstone Park, Harrogate, Yorkshire HG2 7BU

## A DEXTER DIMMASWITCH

ALLOWS COMPLETE

LIGHTING CONTROL

The DEXTER DIMMASWITCH is an attractive Dimma unit which simply replaces the normal light switch. It is available as a complete "ready to install" unit or "simple to assemble" kit. Two models are available controlling up to 300W or 600W of all lights, except fluorescents, at mains 200-250V, 50Hz. All DEXTER DIMMASWITCH models have built-in radio interference suppression.

600 watt **£3.52** Kit form **£2.97**  
300 watt **£2.97** Kit form **£2.42**

All plus 12p post and packing  
Prices include VAT. Please send c.w.o. to:

### DEXTER & COMPANY

1 ULVER HOUSE  
19 KING STREET  
CHESTER CH1 2AH  
Tel: 0244-25883

AS SUPPLIED  
TO H.M. GOVERNMENT  
DEPARTMENTS, HOSPITALS,  
LOCAL AUTHORITIES,  
ETC

## P.C.B.: For Mullard Transistor Audio and Radio Circuits Handbook

The following boards are now available: 1st Edition: paper base laminate. 10W H.Q. audio amp, p. 102, **66p.** 25W H.Q. audio amp, p. 106, **70p.** 10/25W H.Q. audio pre-amp, p. 108, **73p.**

2nd Edition: fibreglass laminate. 10W Audio Amp, p. 122, **69p.** 15/20W Audio Amp, p. 126, **73p.** 25W Audio Amp, p. 128, **73p** (incorporates protection circuit, p. 130).

Universal pre-amp, mono, p. 148, **78p.** Universal pre-amp, stereo, p. 148, **£1-48.**

No other circuits are available.

Price includes P. & P. but add VAT.

Remittance (not cash or stamps) with order. Allow 14 days for cheque clearance otherwise prompt despatch subject to stocks.

All boards are roller tinned, drilled and have component ident. printed on reverse.

### BRIBOND PRINTED CIRCUITS LIMITED


Regd. in England 593908

Terminus Road, Chichester  
Sussex

## INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!  
HANDY!  
TIDY!

DISCOUNT PRICES

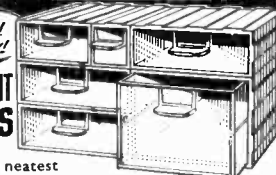

Newest, neatest system ever devised for storing small parts and components:

resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/1D and 2D have removable space dividers. Build up any size cabinet for wall, bench or table top.

5 SIZES ALL INTERLOCK

### BUY AT TRADE PRICES!

**SINGLE UNITS (1D)** (5ins x 2½ins x 2½ins) **£1-40 DOZEN.**

**DOUBLE UNITS (2D)** (5ins x 4½ins x 2½ins) **£2-30 DOZEN.**

**TREBLE (3D)** **£2-50 for 8.**

**DOUBLE TREBLE 2** drawers, in one outer case (6D2), **£3-60 for 8, EXTRA LARGE SIZE (6D1) £3-40 for 8.**

### PLUS QUANTITY DISCOUNTS!

Orders £10 and over DEDUCT 5% in the £  
Orders £20 and over DEDUCT 7½% in the £  
Orders £50 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES

Please add 10% V.A.T. to total remittance

**FLAIRLINE SUPPLIES** (Dept. PE12) 124 Cricklewood  
Broadway, London, N.W.2  
Tel. 01-484 4844



# BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD

## COMPLETE TELEPHONES



EX G.P.O. NORMAL  
HOUSEHOLD TYPE

**ONLY £1.05**

POST & PACKING 45p EACH



## TELEPHONE DIALS

Standard Post Office type.  
Guaranteed in working order.

**ONLY 27½p**

POST & PACKING 16½p

## TESTED AND GUARANTEED PAKS

B79	4	IN4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic	55p
B81	10	Reed Switches, 1" long dia. Highspeed P.O. type	55p
B99	200	Mixed Capacitors. Approx. quantity, counted by weight Post & packing 15p.	55p
H4	250	Mixed Resistors. Approx. quantity counted by weight Post & packing 15p.	55p
H7	40	Virewound Resistors. Mixed types and values	55p
H9	2	OCP71 Light Sensitive Photo Transistor	55p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	55p
H30	20	1 Watt Zener Diodes. Mixed Voltages 6B-43V	55p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	55p
H38	30	Short lead Transistors. NPN Silicon Planar types	55p
H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945	55p
H40	20	BFY 50/2, 2N696, 2N1613, NPN Silicon uncodded TO-5	55p
H41	2	BD131/BD132 Complementary Plastic Transistors	55p

## UNMARKED UNTESTED PAKS

B1	50	Germanium Transistors PNP, AF and RF	55p
B66	150	Germanium Diodes Min. glass type	55p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	55p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	55p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	55p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	55p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	55p
H16	15	Experimenters' Pak of Integrated Circuits. Data supplied	55p
H17	20	3 amp. Silicon Stud Rectifiers, mixed volts	55p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	55p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	55p

## MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1.10 each**



OVER  
**1,000,000**

TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

## SILICON PLANAR PLASTIC TRANSISTORS

Unmarked, untested, factory clearance. A random sampling showed these to be of remarkably high quality.

Audio PNP, similar to ZTX500, 2N3702/3, BCY70, etc.

Audio NPN, similar to ZTX300, 2N3708/9, BC107/8/9, BC168/9, etc.

Please state Audio NPN or Audio PNP when ordering.

ALL AT 500 for £3.30, 1,000 for £5.50, 10,000 for £44.

P & P 11p per 1,000

## OUR VERY POPULAR 4p TRANSISTORS

TYPE "A" PNP Silicon Alloy, TO-5 can.

TYPE "B" PNP Silicon, plastic encapsulation.

TYPE "E" PNP Germanium AF or RF.

TYPE "F" NPN Silicon plastic encapsulation.

TYPE "G" NPN Silicon, similar ZTX300 range.

TYPE "H" PNP Silicon, similar ZTX500 range.

**RELAYS FOR  
8 VARIOUS TYPES £1.10**  
P & P 27½p

## Our famous PI Pak is still leading in value for money

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors

PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. Only 55p.

11p P & P on this Pak.



## A CROSS HATCH GENERATOR FOR £3.85 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This was a project in the September 1972 edition of Television.

**This complete kit of parts costs £3.85, post paid.**

A MUST for Colour T.V. Alignment.

## Electronic Transistor Ignition

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features: Transistor and conventional switchability, burglar prooflock-up and automatic alarm, negative and positive compatibility. This project was a "star" feature in the September edition of "Electronics Today International" magazine. Our kit is recommended by the ETI magazine. Complete kit including P. & P. £7.92 Ready built & tested unit £3.02 EXTRA

## FREE CATALOGUE FOR



TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS

## PLASTIC POWER TRANSISTORS NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min. 15	HFE Min. 15	
1-12	13-25	26-50	
40 watt	22p	20p	18p
90 watt	26p	24p	22p

Range 2	VCE Min. 40	HFE Min. 40	
1-12	13-25	26-50	
40 watt	33p	31p	29p
90 watt	38p	36p	33p

Complementary pairs matched for gain at 3 amps. 11p extra per pair. Please state NPN or PNP on order.

**INTEGRATED CIRCUITS.** We stock a large range of I.C.s at very competitive prices (from 11p each). These are all listed in our FREE Catalogue, see coupon below.

**METRICATION CHARTS** now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 15p, Wall Chart, 18p.

## LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 16p each } Now new low  
16 pin type at 18p each } profile type.

## BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:

**B.P.I. Transistor Equivalents and Substitutes:** This includes many thousands of British, U.S.A., European and C.V. equivalents. **40p**

**The Iffife Radio Valve & Transistor Data Book 9th Edition: P & P 233p.** Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. **75p**

Send for lists of publications.

**N.B.—Books are void of V.A.T.**

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME .....

ADDRESS .....

**ALL PRICES INCLUDE 10% V.A.T.**  
MINIMUM ORDER 55p. CASH WITH ORDER PLEASE. Add 11p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.  
**BUY THESE GOODS WITH ACCESS**

# BI-PRE-PAK LTD

Co. Reg. No. 820919

DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX

TELEPHONE: SOUTHEND (0702) 46344

## AUDIOTRONIC MODEL ATM.1

Top value 1,000 o.p.v. pocket multimeter.  
Ranges: 0/10/50/250/1,000V. A.C. and D.C.  
D.C. Current 0-1mA/100mA.  
Resistance: 0/150 Kohms.  
Decibels: -10 to +22dB.  
Size: 90 x 60 x 28mm.  
Complete with test leads.  
£3-95. Post 15p.



## RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 O.P.V. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2-5/10/50/250/500/1,000V d.c. 2-5/10/50/250/500/1,000V a.c. D.c. current 100mA/1/10/100mA/1A. Resistance 300 ohms/3/30/300K/3mΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £4-95. Post 25p.



## MODEL 500 80,000 O.P.V.

with overload protection mirror scale 0/0-5/2-5/20/25/100/250/500/1,000V d.c. 0/2-5/10/25/100/250/500/1,000V a.c. 0/500μA/5/50/500mA. 12 amp. d.c. 0/60/126 Meg./60 Meg. Ω. 110-50. Post paid. Leather case £1-75.



## U4812 MULTIMETER

Extremely sturdy instrument for general electrical use. 687 O.P.V. 0/0-3/1-5/7-5/30/60/150/300/600/900V d.c. and 75mV. 0/0-3/1-5/7-5/30/60/150/300/600/900V a.c. 0/300μA/1-5/6/15/60/150/600mA/1/5/6 amp. d.c. 0/1-5/15/60/150/600/600A. 1/5/6 amp. a.c. 0/200Ω/3k/30kΩ. Accuracy kΩ edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9-75. Post 25p.



## HIOKI MODEL 700X

100,000 O.P.V. Overload protection. Mirror scale. 0-3/0-5/1-2/1-5/6/12/30/60/120/300/600/1,200V. A.C. 1-5/3/6/12/30/60/150/300/600/1,200V a.c. 15/30μA/3/6/30/60/150/300mA/6/12 amp. d.c. 2K/200K/2 Meg./20 Meg. ohm -20 to +63dB. £14-95. Post 20p.



## MODEL C-7080 EN

Giant 6in mirror scale. 20,000 O.P.V. 0/0-25/1/2-5/10/50/250/1,000/5,000V d.c. 0/2-5/10/50/250/1,000/5,000V a.c. 0/500μA/1/10/100/500mA/10 amp. d.c. 0/2K/200K/20 meg. -20 to +60dB. £13-95. Post 30p.



## TMK MODEL TV-50K 48 ranges

mirror scale, 50K/V d.c. 3K/V a.c. D.c.: Volts 0-125, 0-25, 2-5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. Volts: 1-5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. Current: 25, 50μA, 2-5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω. Decibels: -20 to +81-5dB. £8-50. Post 17p.



## TE-65 VALVE VOLTMETER

28 ranges. D.c. volts 1-5-1,500V a.c. volts 1-5-1,500V. Resistance up to 1,000 megohms. 200/240V a.c. operation. Complete with probe and instructions. £17-50. Post 30p. Additional probes available: R.F. £2-12; H.V. £2-50.



## TE16A Transistorised Signal Generator

5 ranges 400Hz-30kHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide easy to read scale. 800kHz modulation. 5 1/2 x 3 1/2 in. Complete with instructions and leads. £8-97. Post 25p.



## MODEL8-100TR MULTIMETER/TRANSISTOR

TESTER. 100,000 O.P.V. mirror scale/overload protection. 0/0-120/6/3/12/30/120/600V d.c. 0/6/30/120/600V a.c. 0/12/600μA/1/2/300mA/12 amp. d.c. 0/10 K/1 MEG/100 MEG. -20 to +50dB. 0-01-2 MFD. Transistor tester measures Alpha, beta and Ico. Complete with batteries, instructions and leads. £14-95. Post 25p.



## LB3 TRANSISTOR TESTER

Tests ICO and B. Pnp/npn. Operates from 9V battery. Complete with all instructions, etc. £3-95. Post 20p.



## LB4 TRANSISTOR TESTER

Tests PNP or NPN transistors. Audio indication. Operates on two 1.5V batteries. Complete with all instructions, etc. £4-50. Post 20p.



## KAMODEN HM720B F.E.T.V.O.M.

Input impedance 10MΩ. Ranges: 0/0-25/1/2-5/10/50/250/1,000V d.c. 0/2-5/10/50/250/1,000V a.c. 0/25/50/250/250/500mA d.c. -20 to +62dB. 0/5k/50k/500k/5MΩ/500MΩ. £14-95. Post 30p.



## KAMODEN 78-200 MULTITESTER

High sensitivity tester. 200,000 o.p.v. Overload protection. Mirror scale. Ranges: 0/0-66/0-3/3/30/120/600/1,200V d.c. 0/8/12/60/300/11,200V a.c. 0/16μA/1/2mA/120mA/600mA/12A d.c. 0/32A. 0/2kΩ/200kΩ/2MΩ/200MΩ. £18-95. Post 30p.



## 370 WTR MULTIMETER

Features a.c. current ranges. 20,000 O.P.V. 0/0-5/2-5/10/50/250/500/1,000V d.c. 0/2-5/10/50/250/500/1,000V a.c. 0/50μA/1/10/100mA/1/10 amp. d.c. 0/100mA/1/10 amp. a.c. 0/5K/50K/500K/5MEG/50MEG. -20 to +62dB. £17-50. Post 25p.




## KAMODEN HM-350 TRANSISTOR TESTER

High quality instrument to test Reverse Leak current and D.C. current. Amplification factor of NPN, PNP, transistors, diodes, SCR's, etc. 4" x 4" clear scale meter. Operates from internal batteries. Complete with instructions, leads and carrying handle. £12-50. Post 30p.


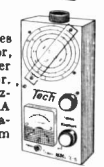
## MODEL TE15 GRID DIP METER

Transistorised. Operates as Grid Dip, Oscillator, Absorption Wave Meter and Oscillating Detector. Frequency range 440kHz-280MHz in 9 coils. 500μA meter. 9V battery operation. Size 180mm x 80mm x 40mm. £15-00. Post 20p.



## TMK LAB TESTER

100,000 O.P.V. 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 ΩV d.c. 5/Volt a.c. D.c. volts: 0-5, 2-5, 5, 10, 25, 50, 1,000V. A.c. volts: 3, 10, 50, 250, 500, 1,000V. D.c. current: 10, 100μA, 10, 100, 500mA, 2-5, 10A. Resistance: 1K, 10K, 100K, 10 meg. 100 meg. Decibels: -10 to +49dB. Plastic case with carrying handle. size 7 1/2 in x 6 1/2 in x 3 1/2 in. £18-95. P. & F. 25p.



## 240° Wide Angle 1ma Meters

MW1-6 60mm square £3-97  
MW1-8 80mm square £4-97  
P. & F. 15p.



## TESS SINE SQUARE WAVE AUDIO GENERATORS

Size: 20c/s to 200 kc/s on 4 bands. Square: 20c/s to 30 kc/s. Output impedance 5,000 ohms. 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads. £17-50. Carr. 37p.




## ARF-500 AF/RF SIGNAL GENERATOR

All transistorised, compact, fully portable. AF sine wave 18 Hz to 220 KHz. AF square wave 18 Hz to 100 KHz. Output sine/square: 10V. P.P. RF 100 KHz to 200 MHz. Output 1V. maximum. Operation 220/240V. A.C. Complete with instructions and leads. £29-95. Post 50p.



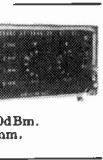
## MODEL AT201 DECADE ATTENUATOR

Frequency range 0-200KHz. Attenuator 0-11dB, 0-1dB step. Impedance 600 ohms. Max. input power 30dBm. Size 180mm x 90mm x 56mm. £12-50. Post 37p.


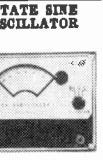
## BELOU AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR

Size 18-200,000 Hz; Square: 18-500 Hz. Output max. +10dB (10 K ohms) Operation internal batteries. Attractive 2-tone case 7 1/2 in x 6 in x 2 in. Price £17-50. Carr. 71p.



## TE-40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: 0/1-003/1-3/1/3/10/30/100/300V. R.M.S. 4cps. -1-2 Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V. a.c. £17-50. Carr. 25p.




## TMK MODEL 117 F.E.T. ELECTRONIC VOLTMETER

Battery-operated, 11 meg input, 26 ranges. Large 4 1/2 in mirror scale. Size 5 1/2 in x 4 1/2 in. D.C. volts 0-3-200V. A.C. volts 3-300V R.M.S. 8-0-800V P.P. D.C. Current 0-12-12MA. Resistance up to 2,000 ohm. Decibels -20 to +51dB. Complete with leads/instructions. £17-50. P. & F. 20p.


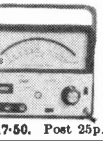
## MODEL 449A IN-CIRCUIT TRANSISTOR TESTER

Checks  $\alpha$  and  $\beta$  in/out. Checks Ico. Checks diodes in/out. Checks SCR, etc. Beta HI 10-500 LO 2-50 Icco 0-5000μA. 220/240V a.c. operation. £17-50. Post 25p.



## KAMODEN HMG-500 INSULATION RESISTANCE TESTER

Range 0-1,000 Megohms, 500 Volt. Battery operated. Wide range clear meter 4 1/2 x 4". Complete with deluxe carrying case, batteries, instructions. £19-95. Post 30p.



## MODEL U4811 SUB-STANDARD MULTI-RANGE VOLT AMMETER

Sensitivity 330 ohms/Volt a.c. and d.c. Accuracy 0-5% d.c. 1% a.c. Scale length 165mm. 0/300/750μA/1-5/3/7-5/15/30/75/150/300/750mA/1-5/3/7-5 amp. d.c. 0/3/7-5/15/30/75/150/300/750V/1-5/3/7-5/15-30/75/150/300/750V d.c. 0/750mV/1-5/3/7-5/15-30/75/150/300/750V a.c. Automatic cut out. Supplied complete with test leads, manual and test certificates. £40. Post 50p.



## MCA.320 AUTOMATIC VOLTAGE STABILISER

Input 88-125V a.c. or 175-250V a.c. Output 120V a.c. or 240V a.c. 200VA rating. £11-97. Post 60p.



## PS.200 REGULATED P.S.U.

Solid state. Variable output 0-20V d.c. up to 2 amp. Independent meters to monitor voltage and current. Output 220/240V. a.c. Size 7 1/2 in x 5 1/2 in x 3 1/2 in. £19-95. Post 25p.



## PS.100B REGULATED POWER SUPPLY

Solid state. Output 6, 9 or 12V d.c. up to 3 amps. Meter to monitor current. Input 220/240V a.c. Size 4 1/2 in x 3 1/2 in x 6 1/2 in. £11-97. Post 25p.



## MODEL TE-300. 30,000 O.P.V. Mirror scale, overload protection

0/0-6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30μA/60μA/300mA/600mA. 0/8K/80K/800K/8 meg. ohm -20 to +63dB. £7-50. Post 15p.



## MODEL TE-200. 20,000 O.P.V. Mirror scale, overload protection.

0/0-6/3/15/60/300/1,200V d.c. 0/10/50/250/1,000V a.c. 0/50μA/250μA. 0/60K/6 meg Ω. -20 to +62dB. £4-95. Post 15p.



## GI-5 PULSE OSCILLOSCOPE

For display of pulsed and periodic waveforms in electronic circuits. VERT. AMP. Bandwidth 10MHz. Sensitivity at 100kHz V. RMS/mm. 0-1-25. HOR. AMP. Bandwidth 500kHz. Sensitivity at 100kHz. V. RMS/mm. 0-3-25. Pre-set triggered sweep 1-3,000μsec.; free running 20-200,000Hz in nine ranges. Calibrator pips. 220mm x 360mm x 430mm, 115-230V a.c. operation. £39. Carr. paid.



## TO-3 PORTABLE OSCILLOSCOPE

8in tube, Y amp. Sensitivity 0-1V p-p/CM. Bandwidth 1-5cps-1.5MHz. Input imp. 2 meg Ω 25pF X amp. sensitivity 0-9V. p-p/CM. Bandwidth 1-5cps-800kHz. Input imp. 2 meg Ω 20pF. Time base, 5 ranges 10cps-300kHz. Synchronisation. Internal/external. Illuminated scale 140mm x 215mm x 330mm. Weight 15 1/2 lb. 220/240V a.c. Supplied brand new with handbook. £52-50. Carr. 50p.



## RUSSIAN CI-16 DOUBLE BEAM OSCILLOSCOPE

5MHz Pass Band. Separate Y1 and Y2 amplifiers. Rectangular 5in x 4in C.R.T. Calibrated triggered sweep from 0-2μsec to 100 millisee per cm. Free running time base 50 Hz-1MHz. Built-in time base calibrator and amplitude calibrator. Supplied complete with all accessories and instruction manual £37. Carr. paid.



## POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range available ex-stock. Single hole fixing, 1/2in dia. shafts. Bulk quantities available.



25 WATT. 10/25/50/100/250/500/1000 ohms £1-15. P. & F. 10p.

50 WATT. 10/25/50/100/250/500/1000/2500 or 5000 ohms. £1-62. P. & F. 10p.

100 WATT. 1-5/10/25/50/100/250/500/1000 or 2500 ohms. £2-34. P. & F. 15p.

## 230 VOLT A.C. 50 CYCLES RELAYS

Brand new. 3 sets of changeover contacts at 5 amp. rating. 40p each. Post 12p (100 lots £30) Quantities available.



ALL PRICES ARE SUBJECT TO 10% VAT



**HIGH QUALITY CONSTRUCTION KITS**  
 Appointed stockists at all branches  
 Complete with comprehensive, easy to follow instructions, and covered by full guarantee  
 Post and packing 15p per kit

AF20	Mono transistor amplifier	£4.80
AF30	Mono transistor pre-amplifier	£2.85
AF310	Mono amplifier, two two for stereo	£5.91
ATS	Automatic light control	£2.98
AT30	Photo cell switching unit	£3.70
AT50	400W Trac light dimmer/speed control	£4.80
AT55	1.300W Trac light dimmer/speed control	£5.70
AT65	2.200W Trac light dimmer/speed control	£6.90
AT80	Psychedic light control, single channel	£7.80
AT85	Psychedic light control, 3 channel	£14.95
HF81	Medium wave transistor radio	£3.33
MF75	FM transistor receiver	£2.88
HF210	FM tuner unit	£1.77
HF225	De Luxe FM tuner unit	£24.12
HF330	Stereo decoder for HF310/HF325	£9.96
HF395	Aerial amplifier for AM/FM bands I, II, III	£1.77
GP310	Stereo pre-amp for use with 2x AF310	£21.27
NT10	Tremolo unit for guitars etc.	£7.50
NT15	Power supply 100 mA 9V stab. 12V unstab.	£8.15
NT300	Professional stabilized power supply 2x 30 Volt, 2.2 Amp	£12.81
NT305	Transistor converter, 12V/5V AC/DC to 6V, 7.5V or 9V DC	£4.50
NT310	Power supply 240V AC to 2x 18V DC at 2 Amps	£4.80
NT315	Power supply 240V AC to 4x 5-15V DC 500 mA	£9.57

**NEW FROM JOSTY KIT!**

'Amateur Electronics'—The professional book for the amateur—covers the subject from basic principles to advanced electronic techniques. **OUR PRICE £8.30** complete with circuit board for making the kits listed below.

AE1	100 mW output stage	£1.65
AE2	Fro-amplifier	£1.28
AE3	Diode-receiver	£2.00
AE4	Flasher	£1.09
AE5	Astable multivibrator	£1.05
AE6	Monostable multivibrator	£1.02
AE7	RC generator	£1.08
AE8	Base filter	99p
AE9	Treble filter	99p
AE10	RC filter	99p

**"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS**

Excellent quality at low cost. All models—input 230v. 50/60 c/s. Variable output 0-260v.

**MODEL S-260 GENERAL PURPOSE BENCH MOUNTING**



1A	£8.75 (30p)
2.5A	£10.00 (35p)
8A	£19.95 (50p)
10A	£28.10 (75p)
12A	£29.50 (£1)
20A	£61.25 (£1.25)
25A	£78.50 (£1.30)
40A	£103.10 (£1.50)

**MODEL S-260B**

Panel mounting	
1A	£8.75 (30p)
2.5A	£10.00 (35p)

(Postage and packing is shown in brackets)

**AUTO TRANSFORMERS**

0/115/230V. Step up or step down. Fully shielded.

80W	£2.95	P. & P. 18p
160W	£3.00	P. & P. 18p
300W	£4.00	P. & P. 23p
500W	£5.80	P. & P. 33p
1000W	£8.25	P. & P. 38p
1500W	£11.25	P. & P. 43p
2250W	£16.00	P. & P. 50p
5000W	£40.00	P. & P. £1P.

**REFLEX HORN SPEAKER RUH.6**

Built in driver unit. Impedance 16 ohm. Power rating 10W. Response 380-7,000Hz. Approx. size 7 1/2" x 6 1/2". Weatherproof and shock proof.

**OUR PRICE £4.97 P. & P. 30p**

**BYD.5 VERNIER TUNING DIAL**

Approx. 7-1 ratio planetary drive vernier dials. Log scale 0-180 degrees. Blank scales 1 to 5. Scale width 4 1/4". Dial size 5 1/2" x 3 1/2". Overall size 7 1/4" x 4 1/4" x 1 1/2" deep including knob and coupling. 1 1/2" dia. shaft.

**OUR PRICE £1.62 P. & P. 15p**

**3-STATION INTERCOM KE.630**



Master and two substations. Can be used on desk or wall mounted. Complete with cable and batteries

**OUR PRICE £5.25 Carr. Paid**

**SEW CLEAR PLASTIC PANEL METERS**

USED EXTENSIVELY BY INDUSTRY, GOVT. DEPT'S., EDUCATIONAL AUTHORITIES, ETC.

Over 200 ranges in stock—other ranges to order. Quantity discounts available. Send for fully illustrated brochure.

**TYPE SW.100 100mm x 80mm Fronts**

50µA	£4.15
50-0-50µA	£3.95
100µA	£3.95
100-0-100µA	£3.90
500µA	£3.70
1mA	£3.60
20V d.c.	£3.60
50V d.c.	£3.60
300V d.c.	£3.60
1 amp. d.c.	£3.60

**Type SD.880 82-6mm x 110mm Fronts**

10mA	£3.10
50mA	£3.10
100mA	£3.10
500µA	£3.10
1 amp.	£3.10
5 amp.	£3.10
10 amp.	£3.10
5V d.c.	£3.10
10V d.c.	£3.10
20V d.c.	£3.10
50V d.c.	£3.10
300V d.c.	£3.10
15V a.c.	£3.10
300V a.c.	£3.30
VU Meter	£2.50

**Type SD.480 46mm x 59-5mm Fronts**

50µA	£2.80
50-0-50µA	£2.80
100µA	£2.75
100-0-100µA	£2.75
200µA	£2.70
500µA	£2.65
1mA	£2.60
5mA	£2.60
10mA	£2.60
50mA	£2.60
100mA	£2.60
500mA	£2.60

**Type MR.45P. 2 1/2" square Fronts.**

50µA	£2.70	5 amp.	£2.40
50-0-50µA	£2.65	10V d.c.	£2.40
100µA	£2.60	20V d.c.	£2.40
100-0-100µA	£2.50	50V d.c.	£2.40
200µA	£2.50	300V d.c.	£2.40
500µA	£2.45	15V d.c.	£2.40
500-0-500µA	£2.40	300V d.c.	£2.40
1mA	£2.40	5 Meter 1mA	£2.60
10mA	£2.40	VU Meter	£2.70
50mA	£2.40	1 amp. a.c.*	£2.40
100mA	£2.40	5 amp. a.c.*	£2.40
500mA	£2.40	10 amp. a.c.*	£2.40
1 amp.	£2.40	20 amp. a.c.*	£2.40
		30 amp. a.c.*	£2.40

**Type MR.88P. 1 1/2" 82mm square Fronts.**

200µA	£2.25
300µA	£2.25
500µA	£2.25
750µA	£2.25
1 amp.	£2.25
2 amp.	£2.25
5 amp.	£2.25
10 amp.	£2.25
10 amp.	£2.25
3V d.c.	£2.25
50µA	£2.55
50-0-50µA	£2.50
100µA	£2.45
100-0-100µA	£2.45
200µA	£2.25
500µA	£2.25
500-0-500µA	£2.25
1mA	£2.25
1-0-1mA	£2.25
2mA	£2.25
5mA	£2.25
10mA	£2.25
20mA	£2.25
50mA	£2.25
100mA	£2.25
150mA	£2.25

50µA	£2.55
50-0-50µA	£2.50
100µA	£2.45
100-0-100µA	£2.45
200µA	£2.25
500µA	£2.25
500-0-500µA	£2.25
1mA	£2.25
1-0-1mA	£2.25
2mA	£2.25
5mA	£2.25
10mA	£2.25
20mA	£2.25
50mA	£2.25
100mA	£2.25
150mA	£2.25

**EA.41 REVERBERATION AMPLIFIER**

Self contained, transistorised, battery operated. Simply plug in microphone, guitar, etc., and out—put into your amplifier. Volume control, depth of reverberation control. Beautiful walnut cabinet. 7 1/2" x 3 1/2" x 4 1/2".

**OUR PRICE £7.50 P. & P. 15p**

**1021 STEREO LISTENING STATION**

For balancing and gain selection of loudspeaks, with additional facility for stereo switching, 2 gain controls, speaker on-off slide switch, stereo headphone sockets 6 1/2" x 4 1/4" x 2 1/4".

**OUR PRICE £2.25 P. & P. 20p**

**Type MR.85P. 4 1/4" x 4 1/4" Fronts**

50µA	£3.90
50-0-50µA	£3.60
1 amp.	£3.60
5 amp.	£3.60
15 amp.	£3.60
30 amp.	£3.95
10V d.c.	£3.90
20V d.c.	£3.90
50V d.c.	£3.90
150V d.c.	£3.90
300V d.c.	£3.90
15V a.c.	£3.95
300V a.c.	£3.95
8 Meter 1mA	£3.90
VU Meter	£4.55
1 amp. a.c.*	£3.90
5 amp. a.c.*	£3.90
10 amp. a.c.*	£3.90
20 amp. a.c.*	£3.90
30 amp. a.c.*	£3.90

**Type SD.640 63-5mm x 86mm Fronts**

50µA	£3.05
50-0-50µA	£3.05
100µA	£3.00
100-0-100µA	£3.00
200µA	£3.00
500µA	£2.95
1mA	£2.90
5mA	£2.90
10mA	£2.90
50mA	£2.90
100mA	£2.90
500µA	£2.90
1mA	£2.90
5 amp.	£2.90
10 amp.	£2.90
50V d.c.	£2.90
20V d.c.	£2.90
50V d.c.	£2.90
300V d.c.	£2.90
15V a.c.*	£2.90
300V a.c.*	£2.90
VU Meter	£3.15

**Type MR.65P. 3 1/4" x 3 1/4" Fronts**

50µA	£2.70
50-0-50µA	£2.15
100µA	£2.15
100-0-100µA	£2.10
200µA	£2.05
500µA	£2.05
1mA	£2.00
5mA	£2.00
10mA	£2.00
50mA	£2.00
100mA	£2.00
500µA	£2.00
1mA	£2.00
5 amp.	£2.00
10 amp.	£2.00
50V d.c.	£2.00
20V d.c.	£2.00
50V d.c.	£2.00
300V a.c.	£2.00
15V a.c.*	£2.00
300V a.c.*	£2.00
5 amp. a.c.*	£2.00
10 amp. a.c.*	£2.00
20 amp. a.c.*	£2.00
30 amp. a.c.*	£2.00

**Type MR.88P. 1 1/2" 82mm square Fronts.**

200µA	£2.25
300µA	£2.25
500µA	£2.25
750µA	£2.25
1 amp.	£2.25
2 amp.	£2.25
5 amp.	£2.25
10 amp.	£2.25
10 amp.	£2.25
3V d.c.	£2.25
50µA	£2.55
50-0-50µA	£2.50
100µA	£2.45
100-0-100µA	£2.45
200µA	£2.25
500µA	£2.25
500-0-500µA	£2.25
1mA	£2.25
1-0-1mA	£2.25
2mA	£2.25
5mA	£2.25
10mA	£2.25
20mA	£2.25
50mA	£2.25
100mA	£2.25
150mA	£2.25

**Type PE.70. 3 1/2" 82mm x 1 1/2" 82mm x 2 1/2" deep.**

50µA	£3.75
50-0-50µA	£3.60
100µA	£3.60
100-0-100µA	£3.60
200µA	£3.40
500µA	£3.20
1mA	£3.20
5 amp.	£3.20
10 amp.	£3.20
50V d.c.	£3.20
20V d.c.	£3.20
50V d.c.	£3.20
300V a.c.	£3.25
VU Meter	£3.85

**\*MOVING IRON—ALL OTHERS MOVING COIL**  
 Please add postage

**MP7 MIXER PREAMPLIFIER**

Battery operated. 9 1/4" x 5 1/4" x 3 1/4". Input: Mic: 3 x 3m. 50K. 2.3mV. 600 ohm. Phone mag. 4mV 50K. Phono ceramic 100mV 1 neq. Output 250mV 100K.


**OUR PRICE £8.97 P. & P. 20p**

**AUDIOTRONIC AM101 STEREO HEADPHONE AMPLIFIER**

All silicon transistor amplifier operates from magnetic ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Input 5mV/100mV. Output 50mW per channel.

**OUR PRICE £7.50 P. & P. 20p**

**"Sew" Educational Meters**

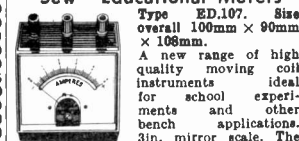

Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3 1/4" mirror scale. The meter movement is easily accessible to demonstrate internal working. Available in the following ranges:

15V d.c.	£5.95
20V d.c.	£5.95
50V d.c.	£5.95
300V d.c.	£5.95
Dual range	£7.00
500mA/5A d.c.	£7.00
15A d.c.	£5.95
5A d.c.	£5.95
5V/15V d.c.	£7.00
5V/15V d.c.	£7.00

**"Sew" Bakelite Panel Meters**

**Type MR.65. 3 1/4" square Fronts.**

1 amp.	£2.60
2 amp.	£2.60
5 amp.	£2.60
15 amp.	£2.60
30 amp.	£2.60
50 amp.	£2.60
5V d.c.	£2.60
10V d.c.	£2.60
20V d.c.	£2.60
50V d.c.	£2.60
150V d.c.	£2.60
300V d.c.	£2.60
500µA	£2.60
500-0-500µA	£2.60
1mA	£2.60
1-0-1mA	£2.60
5mA	£2.60
10mA	£2.60
50mA	£2.60
100mA	£2.60
500mA	£2.60

**Type MR.65. 3 1/4" square Fronts.**

1 amp.	£2.60
2 amp.	£2.60
5 amp.	£2.60
15 amp.	£2.60
30 amp.	£2.60
50 amp.	£2.60
5V d.c.	£2.60
10V d.c.	£2.60
20V d.c.	£2.60
50V d.c.	£2.60
150V d.c.	£2.60
300V d.c.	£2.60
500µA	£2.60
500-0-500µA	£2.60
1mA	£2.60
1-0-1mA	£2.60

# G.W.S. G.W.SMITH & CO (RADIO) LTD

## TRIO TR2000 TRANSCIEVER

Fully transistorised portable VHF Transceiver. Will transmit and receive on 6 channels between 144-146MHz. 1W transmitter. 12V d.c. internal or external supply. Built in charger for ni-cad cells. Power/volume switch, squelch control, channel selector, mike socket, earphone/external speaker socket. Complete with microphone. 144.48, 144.72 and 145.32 crystals.

OUR PRICE **£79.50** Carr. Paid

## TRIO 9R59DS RECEIVER



4 bands covering 550kHz-30MHz continuous and electrical bandspread on 10, 15, 20, 40 and 80 metres. 8 valve plus 7 diode circuit. 4/8 ohm output and phone jack. SSB-CW. ANL. Variable BFO. 8 meter. Sep. bandspread dial. IF frequency 445kHz audio output 1.5W. Variable RF and AF gain controls 115/250V a.c. Size: 7in x 13in x 10in with instruction manual.

OUR PRICE **£49.50** Carr. Paid  
FULL RANGE OF TRIO STOCKED

## UR-1A RECEIVER



4 Bands covering 550kHz-30MHz. FET, 8 Meter. Variable BFO for SSB. Built-in Speaker. Bandspread. Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2 x 4 1/2 in x 7in. Brand new with instructions.

OUR PRICE **£25.00** Carr. Paid 37p

## UNR 30 RECEIVER



4 Bands covering 550kHz-30MHz. BFO Built-in Speaker 220/240V a.c. Brand new with instructions.

OUR PRICE **£15.75** Carr. Paid 37p

## TRIO JR310 SSB RECEIVER



Covers 3-5, 7, 14, 21, 28, 28.5 and 29.1MHz bands, and WWV 15MHz. SSB, AM and CW. AF output more than 1W. Crystal controlled BFO for SSB. 8 meter. ANL, etc. A.c. 110/120-220/240V. Size 330 x 179 x 310mm.

OUR PRICE **£75.00** Carr. Paid



## TRIO JR599 RECEIVER



9 wavebands covering 1.8-29.7MHz. 144-146MHz and 10-00MHz WWV. SSB, CW, AM and FM. AF output more than 1W. 8 Meter. Squelch control. BFO. Variable RF and AF controls. 4-16 ohm output and phone jack. Power requirements 100/240V a.c. 12-14V d.c.

OUR PRICE **£155.00** Carr. Paid

## TRIO TS515/PS515 TRANSCIEVER



High quality TS515 SSB/CW amateur band receiver covering 80, 40, 20, 15 and 10 metre bands with PS515 power supply and speaker unit. Transmit/receive frequency 3.5-29.7MHz. Output 1.5W. Power requirements 110-120/220-240V a.c.

OUR PRICE **£210.00** Carr. Paid


## BELTEK WS400 CAR TRANSCIEVER



Solid state mobile transceiver for 12V d.c. neg. use. Transmits and Receives on any 12 of 28 channels between 144 and 146MHz. Power output 10W and 1W switchable. Controls: Volume/on/off, squelch, channel selector, Internal 3m speaker. Complete with dynamic mike, PTT switch, three sets of crystals for 144.48MHz, 144.60MHz, 145.00MHz, mounting bracket and instructions.

OUR PRICE **£75.00** Carr. Paid

## LAFAYETTE HA-600 RECEIVER

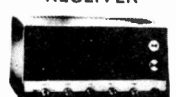

General coverage 150-400kHz. 550kHz-30MHz. FET front end. 2 mech. filters, product detector, variable BFO, noise limiter, 8 Meter. Bandspread. RF Gain. 16in x 9 1/2in x 8 1/2in. 18 lb. 220/240V a.c. or 12V d.c. Brand new with instructions.

OUR PRICE **£50.00** Carr. Paid 50p



Battery operation. Volume and squelch controls. Call button and press to talk button. Telescopic Aerial. Complete with carrying cases. SKYFON 100mW, £24.95 pair, post 50p. P302 2 CHANNEL 300mW, £52.50 pair, post 50p. P1003 3 CHANNEL 1 watt, £71.25 pair, post 50p. LICENSE REQUIRED IN U.K.

## AUDIOTRONIC AHP8A 8 TRACK STEREO TAPE PLAYER

Incorporates built in amplifiers giving 2 1/2 + 2 1/2 W r.m.s. output. Push-button track selector, illuminated track indicators, slider controls for volume, balance and tone. Attractive cabinet with black and silver trim. Output impedance 8 ohms. 220/240V a.c.

OUR PRICE **£17.25** P. & P. 50p, plus V.A.T.

## AUDIOTRONIC AHP8D 8 TRACK STEREO TAPE DECK

Can be used with most hi-fi amplifiers. Push button track selector and illuminated track indicators. Attractive cabinet with black and silver trim. Output level 750mV. 220/240V a.c.

OUR PRICE **£11.95** P. & P. 50p, plus V.A.T.

## AUDIOTRONIC ACD660 STEREO CASSETTE DECK

A beautifully styled & remarkably low price. Incorporates a host of features including switchable noise filter, normal/chrome tape selector, twin VU meter, slider record/playback level controls, front panel headphone socket, recording indicator lamp, phono/Din line input sockets, 3.5mm mike input sockets, etc. Frequency response 100-8kHz (100-12kHz CrO2). S/N -45dB. Crosstalk -45dB. Separation -35dB. Noise limiter -60dB at 10kHz. Complete with 10 pin connecting leads.

OUR PRICE **£39.50** Carr. Paid 50p

## AUDIOTRONIC STEREO HEADPHONES

- LSH20. Individual volume controls. Stereo mono switch. 8 ohms. 40-19,000Hz. **£3.50 P. & P. 30p**
- LSH30. Open back type. Individual tone and volume controls. 8 ohms. 30-20,000Hz. **£5.50 P. & P. 30p**
- LSH40. Two way speaker system. Individual volume controls. 8 ohms. 20-20,000Hz. **£6.95 P. & P. 30p**
- LSH60. 3in speaker units. 8 ohms. 20-20,000Hz. Complete with zippered carrying case. **£8.50 P. & P. 30p**
- LQH400. 4-channel dynamic headphones. Each earpiece has 4 drive units. 4-32 ohms. 20-20,000Hz. **£9.95 P. & P. 30p**
- LSH50. Electrostatic with self powered energiser and control unit with headphone/ speaker selector. 4-32 ohms. 20-24,000Hz. **£15.95 P. & P. 30p**

## SPECIAL BARGAIN! PHONIC 10, TWO-WAY SPEAKER SYSTEM

Matched pair of compact bookshelf speakers of unique design incorporating 2in. high frequency tweeter and 6in. woofer. 8 ohms impedance. 10 watts power handling. Size 345 x 228 x 110mm.

GWS SPECIAL PRICE **£9.85** per pair P. & P. 50p, plus VAT

## FERGUSON 3416 STEREO TAPE DECK

4 track, 7 1/2, 3 1/2, 1 1/2 i.p.s. Stereo mono record/play. 7in reels. Inputs for dynamic mikes, radiogram. Complete with cover.

OUR PRICE **£41.95** Carr. Paid 75p

## AUDIOTRONIC ACR3500 CAR RADIO



Manual tuning of Medium and Long waves. 12V pos. or neg. earth. Complete with speaker, mounting brackets and instructions.

OUR PRICE **£6.50** P. & P. 50p

## AUDIOTRONIC ACP8 8-TRACK CAR PLAYER



12V neg. earth. Slider controls for Volume, Tone and Balance. Channel selector button with pilot lamp. With speakers, mounting brackets and instructions.

OUR PRICE **£12.50** P. & P. 40p

## BSR 8-TRACK PLAYER CHASSIS

Famous BSR 8 track chassis as used in Model 8 S complete with silver and black escutcheon ready to fit into cabinet. Output 125mV A.C. 240V. Overall size approx. 185 x 215 x 80mm.

OUR PRICE **£8.95** P. & P. 50p

## EMI LOUDSPEAKERS

Model 350. 13in x 8in with single tweeter / crossover. 20-20,000Hz. 15W RMS. Available 8 or 15 ohms. £7.25 each. P. & P. 37p. Model 450. 13in x 8in with twin tweeters / crossover. 55-13,000Hz. 5W RMS. Available 8 or 15 ohms. £3.62 each. P. & P. 25p.

## BINATONE DS100 DIGITAL CLOCK

240V mains operation. Ivory case with large clear numbers for hours, minutes and seconds. Approx. size 6 1/2in x 3in x 3 1/2in. OUR PRICE **£4.50** P. & P. 30p

## AUDIOTRONIC AMR-9000 GLOBAL AM/FM PORTABLE

10 wavebands covering A.M.: 535-1605kHz; L.W.: 150-380kHz; M.B.: 1.8-4.0MHz; S.W.1.: 4.0-8.0MHz; S.W.2.: 8.0-16.0MHz; S.W.3.: 16-24MHz; P.S.B.1.: 30-50MHz; P.S.B.2.: 148-174MHz; F.M.: 88-108MHz; A.I.R.: 105-136MHz. Features time zone map and timing dial. Large clear scale. Telescopic aerial and built-in aerial. A.F.C. on F.M. 6in x 4in speaker and personal earpiece. Battery/mains operation. Size 345 x 133 x 305mm.

OUR PRICE **£36.00** P. & P. 50p

## AUDIOTRONIC AMB500 MULTI BAND RADIO

5 wavebands covering MW 535-1605kHz and F.M. 88-175MHz. All transistor. Battery or mains operation. Built-in aerial and 8 section telescopic aerial. Complete with batteries, shoulder strap and earpiece.

OUR PRICE **£6.95** P. & P. 35p

## AUDIOTRONIC ARI1000 Sportsman AM/FM Portable

5 wavebands covering A.M.: 535-1605kHz; F.M.: 88-175MHz; A.I.R.: 105-136MHz; P.B.: 147-174MHz; W.B.: 162-5MHz Large horizontal slide dial with logging scale. Slide volume and squelch controls. 7 section telescopic aerial for F.M. and built in ferrite bar for A.M. A.F.C. 3in speaker. Earpiece socket. Green leatherette covering cabinet with 219mm slide panel. Size 135 x 79 x 219mm. Battery/mains operation. OUR PRICE **£11.50** P. & P. 35p

## AUDIOTRONIC AM/FM PORTABLE RADIO AR3000

4 wavebands covering FM 87-108MHz, MW 510-1605kHz, L.W. 145-285kHz, SW 5.8-12.5MHz. Push button wave change plus AFC and on/off. Thumbwheel tuning. Slider volume and tone controls. Earphone socket. Built in and telescopic aerials. Car aerial socket. Battery/Mains operation. OUR PRICE **£14.95** P. & P. 57p

## AUDIOTRONIC DIGITAL CLOCK / AM-FM RADIO

ADC. I Covers AM 540-1600kHz. FM 88-108MHz with AFC. 24 hour fast type digital clock with one minute division. Time change. Illuminated dial. 24 hour alarm setting. Wake up to the sound of music or loud buzzer. Unique sleep switch will automatically turn off radio when you have gone to sleep. Slider volume control. Internal speaker plus socket for earpiece or pillow speaker. A.C. 240V. Size 254 x 92 x 178mm. Complete with earpiece, and operating instructions. OUR PRICE **£12.50** P. & P. 50p

# SAVE UP TO 33 1/3% OR MORE! GWS

## SH028 STEREO HEADPHONES



Outstanding value. Soft earpads, adjustable headband. 8-16 ohms. 20-20,000 Hz. Complete with lead and stereo plug.

**OUR PRICE £1.87 P. & P. 30p**

## LHO2S STEREO HEADPHONES



Lightweight headphones with padded earpieces. 4-16 ohms. 20-20,000 Hz. Complete with 6 ft cord and plug.

**OUR PRICE £1.97 P. & P. 30p**

## TE1018 DE-LUXE MONO HIGH IMPEDANCE HEADSET



Sensitive magnetic headset with soft earpads. Impedance 2,600 ohms (d.c. 600 ohms). Frequency response 200-4,000 Hz.

**OUR PRICE £2.25 P. & P. 30p**

## DHO2S STEREO HEADPHONES

Wonderful value and excellent performance combined. Adjustable headband. 8 ohm impedance. 20-12,000 cps. Complete with lead and plug.



**OUR PRICE £2.25 P. & P. 30p**

## BH001 HEADSET AND BOOM MICROPHONE



Moving coil. Headphone imp. 16 ohms. Mike imp. 200 ohms. Ideal for language teaching, communications etc. Complete with leads and plugs.

**OUR PRICE £4.95 P. & P. 30p**


## STEREOSOUND SPEAKERS



Matched pair of bookshelf speakers. Deluxe teak veneered finish. Size 14 1/2 in x 9 1/2 in x 8 3/4 in. 8W RMS. 16W peak. Complete with DIN lead.

**OUR PRICE £12.95 Carr. Paid**

## SUPER AKAI HI FI CASSETTE BARGAIN

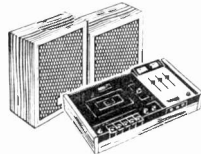

## STEREO CASSETTE RECORDER

For conventional or Chromium Dioxide tape. 4 track recording. Playback. Volume and tone controls. Frequency response 40-16kHz (using CrO<sub>2</sub> tape), distortion better than 2%, wow and flutter better than 0.3% RMS. Complete with pair of matching Akai CS88 speakers. Rec. Price £96-10.

**OUR PRICE £56.50 P. & P. 50p**

**MICROPHONES (P. & P. 50p) ADM Dynamic (pair) £7.50.**

## AUDIOTRONIC ACR14 BATTERY MAINS CASSETTE RECORDER

Portable twin track mono recorder with automatic recording level control. Built in speaker. Ear piece. Input for radio or record player. Fast forward and rewind. Output 500mW; 220/240V a.c. or 6V d.c. operation. Complete with remote control microphone, mains lead, earpiece and batteries.

**OUR PRICE £10.50 P. & P. 50p**

## FANTASTIC OFFER! PORTABLE CASSETTE RECORDER CT5050

Instant recording and playing. Piano key controls. Automatic level control. Built in speaker. Complete with remote control, microphone, carrying case and shoulder strap.

**OUR PRICE £8.50 P. & P. 50p**

## AUDIOTRONIC LOW NOISE CASSETTES

Top Hi-Fi quality in library cases

TYPE	5	10	25
C60	£1.29	£2.53	£5.99
C90	£1.95	£3.82	£9.59
C120	£2.99	£4.48	£10.88

P. & P. 15p Post Free

## RECORD DECK PACKAGES

Carriage and Packing 75p  
Complete units with Stereo cartridge ready wired in plinth and cover.

GARRARD	
2025 TC/9TAHCD	£11.35
SP25 111/G800	£16.50
SP25 111/M44E	£17.95
SP25 111/M44-7	£17.50
SP25 111/M55E	£18.50
SP25 111 Module/M75-6	£19.45
AP76/G800	£26.45
AP76/G800E	£28.65
AP76/M44E	£27.70
AP76/M44-7	£27.20
AP76/M55E	£28.30
AP76/M75E	£34.90
AP76/M75EJ	£30.90
AP76 Module M75-6	£29.10
AP76 Module (less cartridge)	£23.75

868B Module/M70-68M	£32.30
AP96 Module M75-6	£33.20
ZERO 1008 Module/M93E	£44.15
ZERO 1008B Module/M70-68M	£44.20

B.S.R. McDONALD	
210/SC7M	£7.40
MP60/G800	£16.60
MP60/TPD1/ADC K8	£16.80
MP60/M44-7	£17.50
HT70/TPD1/G800	£18.20
HT70/TPD1/ADC K8	£18.10

## RECORD DECKS

Carriage & Packing 50p	
B.S.R. McDONALD	
C114 Mini	£3.95
C129 Mono	£5.60
C137	£7.00
510/TPD1	£18.95
610	£15.45
610/TPD1	£15.45
710	£21.15
810	£28.30
MP60	£28.25
MP60/G800	£10.90
MP60/TPD1	£18.50
MP60/TPD2	£13.55
HT70	£11.60
HT70/G800	£14.25
HT70/TPD1	£16.85

CONNOISSEUR	
BD1 KK	£9.10
BD1 Chassis	£11.35
BD2/SAL2/Plinth/Cover.	£28.70

GARRARD	
2025 T/C Less Cartridge	£6.35
2025 TC/K840A	£6.95
SP25 111	£9.25
SP23111/G800	£10.95
SP25/M75-6	£13.90
AP76	£18.00
SL65B	£11.15
SL72B	£17.75
SL95B	£31.15
401	£24.35
ZERO 1008	£34.90
ZERO 1008B	£27.00

GOLDRING	£22.50
(499)	£22.50
G101P/C	£22.50
GL69/2	£16.75
GL72	£25.45
GL79P	£38.75
GL75P	£41.85
GL78 P/C	£58.25
GL85P/C	£72.00

THORENS	
TD125/11	£59.40
TD125AD/11	£92.05
TL165	£55.80
TL165	£48.80

## SINCLAIR CAMBRIDGE CALCULATOR

To build yourself. Complete kit of parts with step by step instructions to build a full specification pocket sized calculator.

**OUR PRICE £24.95**

P. & P. 50p (Also available ready built (Rec. Price £29.95).

**OUR PRICE £27.20 P. & P. 25p**

## MINUTEMAN MM3 POCKET CALCULATOR

Size only 4 1/2 in x 3 in x 1 in. 8 digit display with overflow and error indicators. Floating decimal. Adds, subtracts, multiplies and divides. Chain and mixed calculations. Constant factor for series multiplication or division. Complete with batteries, instructions and case.

**OUR PRICE £23.95 P. & P. 25p**

**OUR PRICE £28.50 P. & P. 25p**

as above with addition of memory key, percent key and a fixed or floating decimal. Complete with rechargeable batteries, a.c. adaptor, instructions and case.

**OUR PRICE £28.50 P. & P. 25p**

## AUDIOTRONIC DOLBY UNITS

**OUTSTANDING VALUE!**

Reduce tape hiss by 3dB at 600Hz, 6dB at 1200Hz and 10dB for all frequencies above 3000Hz. Size 1 1/2 in x 5 in x 3 1/2 in. a.c. 00/250V2.

**PROCESS TWO**  
For use with cassette and tape recorders. Freq. res. 30Hz—20kHz ±2dB. 8/N of tape monitoring. Switchable multiplex filter. Two Dolby calibration meters. 8/N better than 70dB. Supplied with test cassette or tape as required.

**OUR PRICE £34.50 P. & P. 50p**

**PROCESS FOUR**  
For use with semi professional tape recorders. Freq. res. 30Hz—20kHz ±2dB. 8/N better than 70dB. Full source tape monitoring. Record/Replay metering. Switchable multiplex filter. Supplied with test tape.

**OUR PRICE £50.00 P. & P. 50p**


## NEW FROM SINCLAIR!

**PROJECT 80 HI FI MODULES**

Stereo 80 pre-amp	£9.50
Z40 power amplifier	£4.30
Z60 power amplifier	£5.50
Active filter unit	£5.50
FM tuner	£9.50
Stereo decoder	£3.50
PZ5	£3.95
PZ6	£6.30
PZ8	£6.30
PZ8 mains transformer	£4.05

All other SINCLAIR products in stock including:  
2000 amplifier (improved) £31.25  
4000 amplifier £39.00  
2000 FM tuner (improved) £31.25  
4000 FM tuner £31.25  
Q16 speaker £6.10  
Q30 speaker £19.95

## FM TUNER CHASSIS

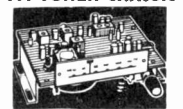

**6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in x 4in x 2 1/2in** 3 I.F. stages. Double tuned discriminator. Simple output to most amplifiers. Operates on 9V battery. Coverage 88-108MHz. Ready built ready for use.

**OUR PRICE £5.95 P. & P. 20p**

**Stereo Multiplex Adaptor £4.97.**

## A1018 FM TUNER

Specification as above but complete in cabinet with on/off switch. Size 7 1/2 in x 3 1/2 in x 5 in.

**OUR PRICE £9.65 P. & P. 30p**

**Stereo Multiplex Adaptor £4.97.**

## SPECIAL OFFER! FRUSTRATED EXPORT ORDER

Philco Ford Model 5245  
Mains Tape Recorder  
2 track BSR deck with push button controls for easy operation. Tape counter and volume control. Complete with hand microphone, direct recording lead, 1,200 ft. reel of tape and spare spool. 200/250V a.c. operation. Fully guaranteed. **OUR PRICE £17.60 C. & P. 75p.**

Philco Ford Model 5248  
Mains Tape Recorder  
4 track 2 speeds (31 i.p.s. & 1 1/2 i.p.s.) piano key type controls, tape counter, recording level meter.

Complete with hand microphone, direct recording lead, 1,800 ft. of tape with spare spool. 200/250V a.c. operation. Fully guaranteed. **OUR PRICE £27.50 C. & P. 75p.**

## LONDON'S LARGEST STOCKS INCLUDING PRODUCTS BY-



ARMSTRONG  
CAMBRIDGE  
KEF-LUX-NIKKO  
SANSUI-SANYO  
SONY-TEAC  
TRANSCRIPTORS  
TRIO-UHER  
YAMAHA

Prices on request or send S.A.E. for full Discount List

ALL EQUIPMENT IS FULLY GUARANTEED AND COVERED BY 12 MONTHS FREE SERVICE!

# G.W.S. SMITH & CO (RADIO) LTD

PERSONAL CALLERS WELCOME AT ANY OF OUR RETAIL BRANCHES

**CENTRAL LONDON**  
257/8, Tottenham Court Rd. W.1.  
10, Tottenham Court Rd. W.1.  
27, Tottenham Court Rd. W.1.  
67, Tottenham Court Rd. W.1.  
21, Old Compton Street. W.1.  
3, Lisle Street, W. C. 2.  
34, Lisle Street, W. C. 2.  
118, Edgware Road, W. 2.  
193, Edgware Road, W. 2.

Tel: 01-580 0670  
Tel: 01-637 2232  
Tel: 01-636 3715  
Tel: 01-580 3729  
Tel: 01-437 9369  
Tel: 01-437 8204  
Tel: 01-437 9155  
Tel: 01-723 9789  
Tel: 01-723 8211

311, Edgware Road, W. 2. Tel: 01-262 0387  
382, Edgware Road, W. 2. Tel: 01-723 4194  
152/3, Fleet Street, E. C. 4. Tel: 01-353 2833  
378, Harrow Road, W. 9. Tel: 01-286 9530  
535/3  
86, South Street, Romford. Tel: Romford 20218  
1046, Whitgift Centre, Croydon. Tel: 01-681 3027  
27, Eden Street, Kingston. Tel: 01-546 7845  
32, Hill Street, Richmond. Tel: 01-948 1441

ALL BRANCHES OPEN 9 a.m. - 6 p.m. MONDAY TO SATURDAY

HEAD OFFICE AND MAIL ORDER DEPARTMENT  
UNIT 4, THE HYDE INDUSTRIAL ESTATE, THE HYDE, LONDON NW9 6JJ  
TELEPHONE 01-205 3735

## PRICES SUBJECT TO 10% VAT

Order with confidence by Post—but remember to add 10% VAT to total value of order including carriage and packing and send cash with order. PLEASE PRINT NAME & ADDRESS CLEARLY IN CAPITALS.



TELEPHONED ORDERS ACCEPTED FROM ACCESS and BARCLAYCARD HOLDERS




CREDIT TERMS FOR PERSONAL CALLERS (on sales of £50 and over)

All prices correct at 1-11-73 but subject to change without notice. E. & O.E.

Among the 240 pages of the famous HOME RADIO COMPONENTS Catalogue, are seven pages listing Resistors . . .

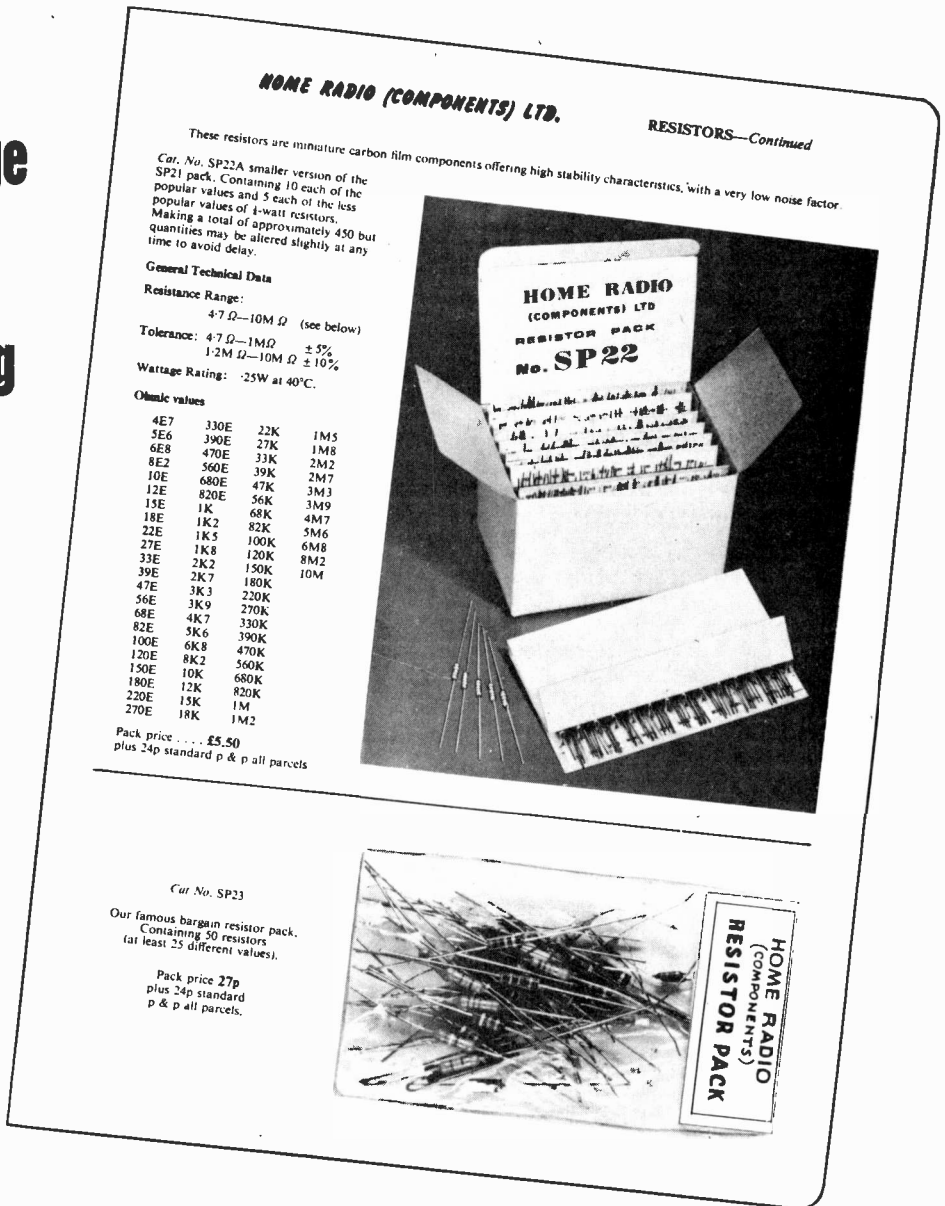Here is a page showing 2 of our unique money saving RESISTOR PACKS



\*The famous Home Radio Components Catalogue lists 6,800 items—1,770 of them illustrated

The Catalogue costs 55p plus 22p post and packing. Every copy contains ten vouchers each worth 5 pence when used as directed. Regularly up-dated price lists are supplied to you free

\*Send now for catalogue

**POST THIS COUPON**  
with cheque or P.O. for 77p.

The price of 77p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses

Please write your Name and Address in block capitals

NAME

ADDRESS



HOME RADIO (Components) LTD.  
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

Regd. No.  
912966  
London

## TWENTY-FIVE YEARS ON

**T**HE 25th year of the transistor draws to its close. A quarter century of exciting and rapid technological growth justifiably referred to as a revolution, and unlikely to be paralleled within the seeable future.

In this issue appears a final article in our special series marking this anniversary of the dawn of the new solid state era. It is written, most fittingly, by a well known contributor and dwells on those now far off days when the transistor was still much of a curiosity and just beginning to cause an upheaval in constructor circles. Established methods of building clearly had to change, but it was far from clear just how.

Much water has flowed under the bridge since then . . . but those early experiments with transistors are worth recalling, though it will all sound very strange to a fair proportion of our readers since there is now a whole generation of constructors brought up entirely on semiconductors.

Yet even our younger post-valve-era readers are not denied the excitement of being involved in great changes in technology. Right at this present moment we are witnessing a "quiet revolution." With hindsight, we know that the discrete semiconductor device represented but the opening phase of this solid state revolution; the culminating achievement has been the creation of the integrated circuit.

So let us turn now from the past and consider what the future holds for the constructor. It will be a future dominated by the i.c., that is obvious. Until, of course, another spectacular discovery leads to the obsolescence of semiconductors—a development not entirely improbable but sufficiently remote in time to be left out of any sensible prognostications at this particular moment.

The i.c. is, in circuit terms, a very large building block and is tending to become even bigger, thanks to l.s.i. This type of device influences very considerably, if it does not dominate entirely, the general pattern of any design in which it is called upon to play a part.

In the future, the drift towards more custom designed i.c.'s may well limit the total number of new devices suitable for constructor applications. Yet amongst the balance there are bound to be an abundance of types than can be usefully employed by the amateur. In this respect, particularly noteworthy at the present time are phase-locked loops. These i.c.'s are beginning to mould the pattern of many equipment designs. They are opening up new fields and revolutionising some traditional designs, especially in the radio receiver area.

Immediately following its introduction, the i.c. was thought by some to represent a threat to home construction activities. Such a pessimistic view has already been proved ill-founded. Looking ahead, there is no reason to suppose any drying up of individual enterprise and ability to extract the maximum advantage from monolithic devices yet to emerge from the microelectronics plants.

F.E.B.

**Editor**  
F. E. BENNETT

**Editorial**  
R. D. RAILTON *Assistant Editor*  
D. BARRINGTON *Production Editor*  
G. GODBOLD *Technical Editor*  
S. R. LEWIS B.Sc.

**Art Dept.**  
J. D. POUNTNEY *Art Editor*  
J. A. HADLEY  
R. J. GOODMAN  
K. A. WOODRUFF

**Advertisement Manager**  
D. W. B. TILLEARD  
Phone: 01-634 4202


P. J. MEW  
Phone: 01-634 4210

C. R. BROWN, *Classified*  
Phone: 01-634 4301

**Editorial & Advertising Offices:**  
Fleetway House, Farringdon St.,  
London EC4A 4AD  
Phone: *Editorial* 01-634 4452  
*Advertisements* 01-634 4202

# PARTY STROBE LIGHT

BY M. HUGHES

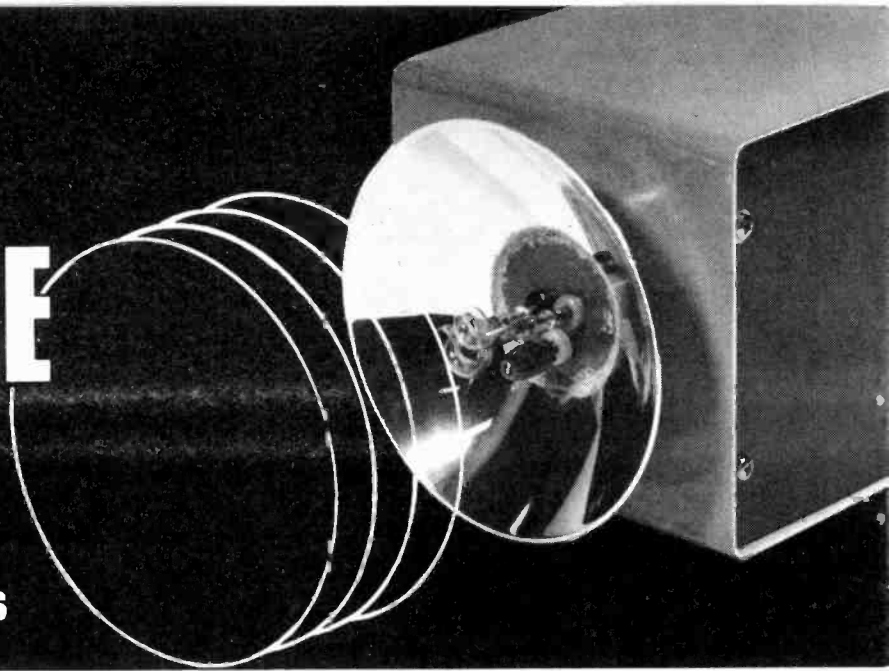

**T**HIS strobe is designed primarily for use as a lighting effect for parties and discotheques. Its flashing rate is continuously variable from about 2Hz to 20Hz. It can be used—with limitations—for specialised photography but the output power (about half a joule) limits it to use with only medium to high speed black and white films at distances of a few feet. For discotheque work, however, it can be classified as of medium power.

## SOME WARNINGS

Those who intend building the equipment should be fully aware at the outset of their social responsibilities in the operation of such equipment; strobing in the frequency range of 10 to 20Hz can, in some instances, produce hypnotic effects. Excessive use of the strobe should thus be avoided; however, if handled carefully and used in moderation some particularly pleasing lighting effects can be produced.

A further word of warning regarding the construction. Very high voltages are used to charge up high value capacitors—these can be lethal if mis-handled. When testing it is not sufficient simply to switch off the power; the plug should be completely removed from the socket and all capacitors shorted out with an insulated handled screwdriver before any attempt is made to handle the circuitry.

## OPERATION

The principle of operation is quite simple. All we have to do is apply a high voltage across a Xenon gas filled tube from a reasonably high value capacitor. This voltage is arranged to be below the breakdown voltage of the tube so initially no electrical discharge takes place. At some pre-determined time a very high voltage pulse (at low current) is applied to a third electrode fixed to the outside

of the tube—this is called the trigger electrode—and we cause a localised electrical breakdown of the gas between the trigger and one of the primary electrodes. The gas in that locality becomes electrically conducting (or ionised), and the ions produced move rapidly throughout the length of the tube and cause main conduction between the primary electrodes.

For a fraction of a second the tube becomes a short circuit across the capacitor and the full charge held on the latter flows through the tube giving rise to the very bright short duration flash. As soon as the capacitor has fully discharged the tube is extinguished and a fraction of a second later the residual ions of gas revert to their non-conducting state and the tube once more becomes inert. The capacitor can now be recharged and a second trigger pulse applied for the next flash.

## FLASH ENERGY

The energy of the flash is measured in joules and is equivalent to the amount of electrical energy stored in the main capacitor (C4 in Fig. 1). This energy is calculated by using the formula:—

$$\text{Energy} = \frac{1}{2}CV^2 \text{ joules}$$

where C is the value of the capacitor in farads and V is the voltage to which it is charged. In Fig. 1 C4 charges up through a half wave rectifier (D2) and limiting resistor, R3, direct from 250V r.m.s. mains; this means the peak voltage on the capacitor when it is fully charged is about 350V. The energy produced in each flash for the capacity used will be about 0.48 joules.

## LIMITED OUTPUT

Because of the tube rating, if it is flashed too often at too high an energy it will get extremely hot. The tube specified is made of hard glass that has a



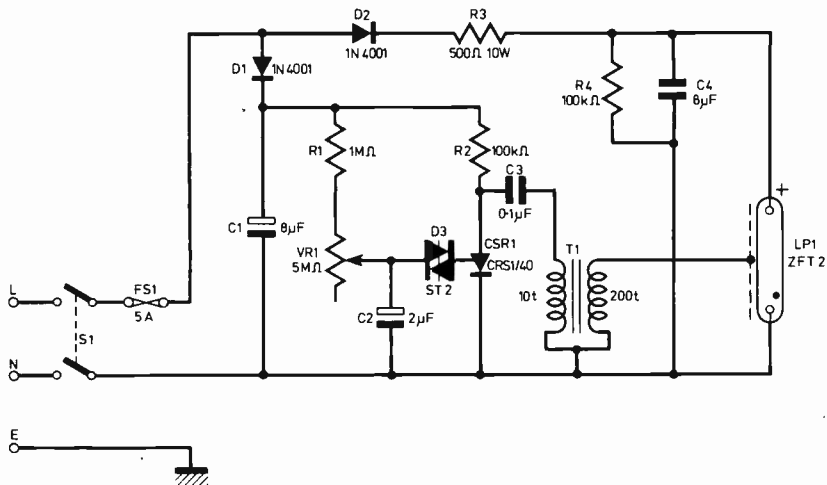


Fig. 1. Circuit diagram of the Party Stroboscope. Note that the case is connected to mains earth

maximum dissipation of 10 watts. It is possible to obtain tubes having a high permitted dissipation but these are quite expensive, particularly those made from quartz.

We can calculate dissipation by multiplying flash energy by the maximum frequency of flashing, with the stroboscope this is  $0.48 \times 20 = 9.6$  watts.

Since this represents nearly the limit of the tube, experimenters should not try to get more light output by increasing the value of C4 without limiting the maximum flash rate proportionally.

Before describing the trigger system, which forms most of the circuitry, a word about R3. The value is reasonably important because it prevents the main capacitor charging before the discharge tube is completely de-ionised; at the same time it must be of low enough a value to ensure that C4 is fully charged before the next trigger pulse. Quite high peak currents flow through this resistor so it should be of at least 10 watts rating and even so will get quite warm in use.

## TRIGGER SYSTEM

To produce the trigger pulses there must be a timing circuit that is adjustable in the range from  $\frac{1}{2}$  second to  $\frac{1}{20}$  second. D1 and C1 form a simple auxiliary d.c. supply of about 350V. C2 will charge up towards 350V and the rate of charge is controlled by the value of R1 and VR1—as the latter is adjustable we can vary the charging rate. In actual fact the potential across C2 will never reach 350V because as soon as it reaches about 25V the diac D3 will start to conduct and any charge held on C2 is applied to the gate electrode of the thyristor.

As soon as C2 is completely discharged the diac becomes non conducting and C2 is able to charge back up towards the 350V. This is a repetitive cycle and the timing is controlled, as we have already said, by the time constant of C2 with the charging resistors but also by the differential between the breakdown voltage of the diac and the potential towards which C2 is charging. Different diacs—particularly the cheaper ones—may have slightly different breakdown voltages so there may be some

variance in timing between different assemblies. This can be compensated for in practice by increasing or decreasing the value of C2. Increase its value if you require a slower repetitive cycle and vice versa.


It is most important that you do not exceed a flash rate of 20Hz because you might exceed the power rating of the tube.

## TURN ON

The discharge current from C2 through D3 into the gate of the thyristor causes the thyristor to turn on. C3 has been charged to 350V through R2 and when the thyristor turns on this is discharged through the circuit C3, CSR1, and the primary of T1. The instantaneous current is quite high and the rate of change of flux in the primary of T1 causes a very high voltage pulse across the secondary windings (approximately 7,000V). This pulse is fed to the trigger electrode of the discharge tube.

Component values have all been carefully chosen so that everything happens in the correct time sequence, e.g. C4 and C3 must be fully charged before the highest rate of trigger pulse is generated by C2 and the diac circuitry so do not use values other than those specified.

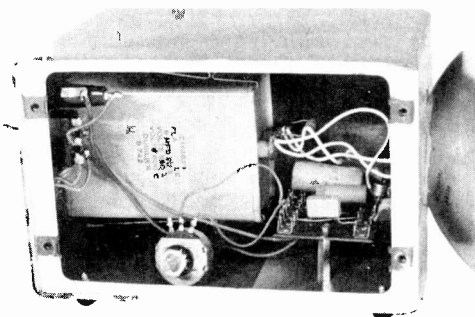R4 is a bleed resistor across the main capacitor to ensure that when the unit is switched off any



The strobe unit with a panel removed showing the large paper capacitor (C4)

## COMPONENTS . . .

### Resistors

- R1 1M $\Omega$
- R2 100k $\Omega$
- R3 500 $\Omega$  10W wirewound
- R4 100k $\Omega$  1W
- All 10%  $\frac{1}{4}$ W except where otherwise stated

### Capacitors


- C1 8 $\mu$ F elect. 500V
- C2 2 $\mu$ F elect. 200V
- C3 0.1 $\mu$ F 400V polyester
- C4 8 $\mu$ F 500V paper

### Diodes

- D1-D2 IN4001 (2 off)
- D3 ST2 Diac (G. W. Smith)
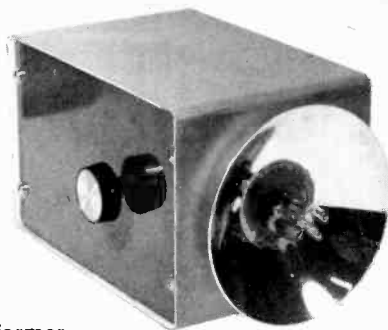
### Xenon Tube

- LP1 Hivac ZFT2 (Townsend and Coates Ltd., Coleman Rd., Leicester)



### Transformer

- T1 Primary, 10 turns 18 s.w.g. enamelled wire; secondary, 200 turns 36 s.w.g. enamelled wire both layer wound on 2in length,  $\frac{1}{4}$ in dia. ferrite rod

### Miscellaneous

- S1 Double pole mains switch; FS1—5A fuse with panel mounted holder; group board; stand off spacers; 3 wander plug sockets; 1 wander plug

high charge stored on C4 is reduced over a short period of time. Do not, however, rely on this—it is always safer to discharge high value capacitors with a screwdriver before touching them.

C4 must be a paper dielectric capacitor rated in excess of 500V. An electrolytic must not be used in any circumstance.

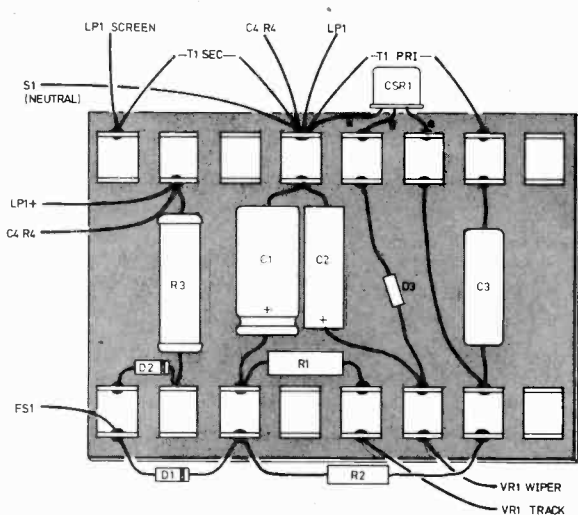


Fig. 2. Component wiring and assembly on group board. Stand-off spacers should be used when connecting to case.

## CONSTRUCTION

Nearly all the circuitry is mounted on a length of group board (Fig. 2) and the only precautions necessary in the layout are that the secondary of T1 (winding details given in Fig. 3) should not be routed too close to any other wiring and R3 should not touch any other components as it gets quite warm. As the discharge current from C4 is very high, fairly heavy gauge wire should be used to connect its terminals to the discharge tube to prevent excessive line drop.

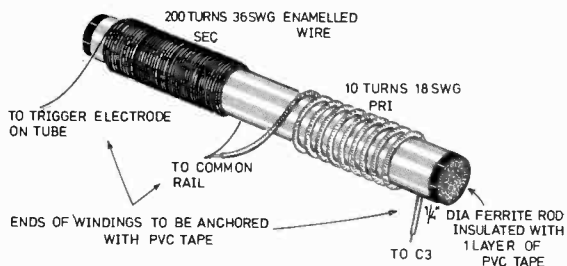




Fig. 3. Winding details of trigger transformer. Both windings are wound in the same sense

All the components should be mounted in a metal case that can be properly earthed; this is essential as all the wiring is live to mains. Wander plug sockets form a convenient way of mounting the tube within the reflector and enable easy change of tubes which have a life expectancy of about a million flashes (this is equivalent to about 25-30 hours of operation at 10 flashes per second).
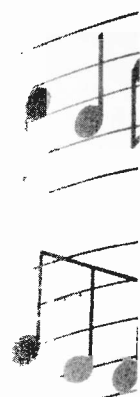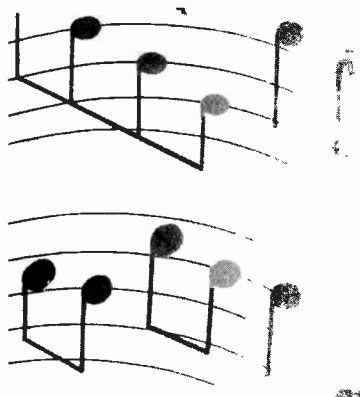
## REFLECTOR

The reflector was the hardest single item to find. In the end a tour round surplus shops solved the problem where a reflector from an old projector system was found for a few pence. An old car headlight reflector (pre sealed-beam era) would be ideal.

The reflector should be bolted or stuck on the main box and the tube sockets fixed through the rear of the reflector and the case—these add extra mechanical support to the reflector. To make the unit tamper proof it would be advisable to place a clear Perspex guard in front of the tube—if different coloured lighting was required tinted Perspex could be used for this purpose. ★



**T**HIS FADER unit was developed for use in a Discotheque console where it will automatically fade out the music being played when the D.J. makes an announcement *via* the microphone. When the announcement is finished the music is then restored to its original volume.

As the finished unit in its original form measures only 3.75 x 2.5 x 0.5in, it should fit easily into the corner of a Discotheque console.

Whilst no complicated adjustments of the console wiring are required the unit will require some form of power supply as it consumes some 7mA at 9V. This could be taken from the Discotheque supply or be provided by a battery if required.

## CIRCUIT

The circuit is shown in Fig. 1 and, as can be seen, is constructed around the Motorola integrated circuit MFC 6040 which is used as an electronic attenuator. It provides zero attenuation for control voltages below 3.5V and about 90dB attenuation for a 6V control voltage. Thus to give the required control effect we have to derive a rising and falling d.c. level from the microphone signal to fade the deck signal in and out.

TR1 and its associated resistors form an emitter follower which gives the input a high impedance and thus prevents undue loading of the console pre-amplifier. TR2 forms a simple amplifier the output of which goes to the base of TR3 *via* diodes D1 and D2 and VR1. The diodes clamp and rectify the amplified microphone signal and VR1 controls the amount of signal applied to the base of TR3. Thus it controls the sensitivity of the unit.

When there is an input signal at the microphone of sufficient amplitude TR3 is turned hard on and the collector is thus at 0V. C4 prevents this voltage rising appreciably during any short breaks in speech which might occur such as between words or sentences.

Without an input signal TR4 conducts and the collector lies about 2V above earth potential. When TR3 turns on TR4 turns off and C5 charges up *via* R7, providing a rising potential at the control input of IC1.

This in turn attenuates, at a rising rate, the signal from the deck. The initial attenuation must be fairly rapid if the initial part of the announcement is not to be drowned in music.

When TR3 turns off again TR4 turns on and C5 discharges to earth through TR4 and R8 until it reaches a steady level. This gives a falling voltage level to decrease the attenuation provided by IC1.

## POWER SUPPLY

As mentioned, a 9V supply giving about 7mA is needed. If such is already available within the console, all well and good. If not then it is simply a matter of dropping and stabilising the console pre-amplifier supply and this may be done simply by using the circuit of Fig. 2.

In Fig. 2, the resistor R9 drops the supply voltage from the console rail value to 9 volts at which it is clamped by the Zener D3. Capacitor C9 gives smoothing of the output. Using Ohms Law, and given a pre-amplifier voltage of V volts then:—

$$R9 = \frac{(V-9)}{11} \text{ k}\Omega$$
, where R9 is  $\frac{1}{4}$  watt if V is less than 30V or otherwise  $\frac{1}{2}$  watt.

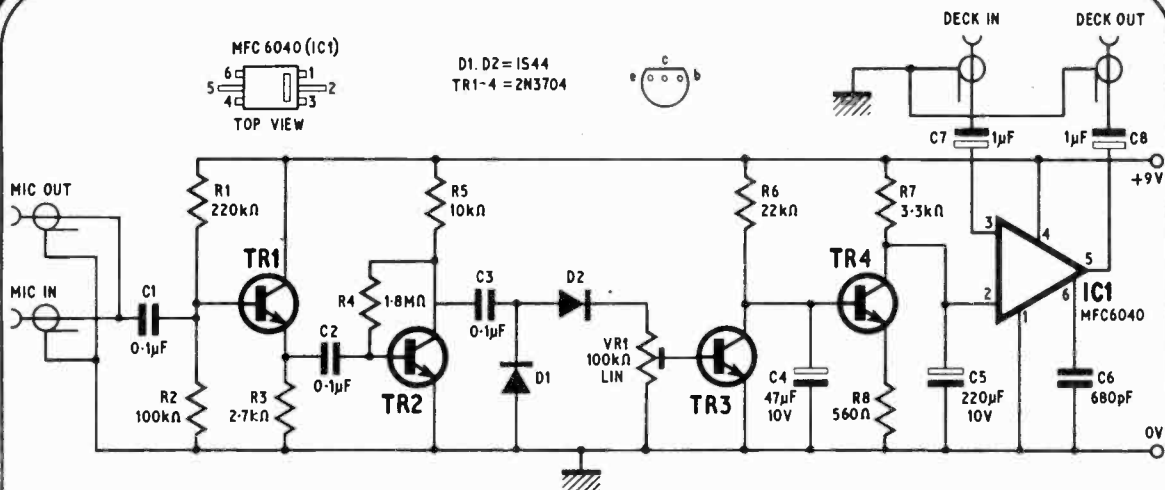


Fig. 1. Circuit diagram of the complete fader which is based on the Motorola MFC 6040 attenuator integrated circuit

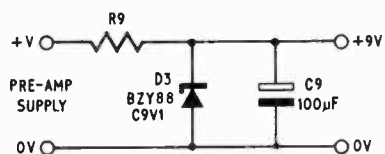


Fig. 2. Circuit of a simple power supply for use with the fader

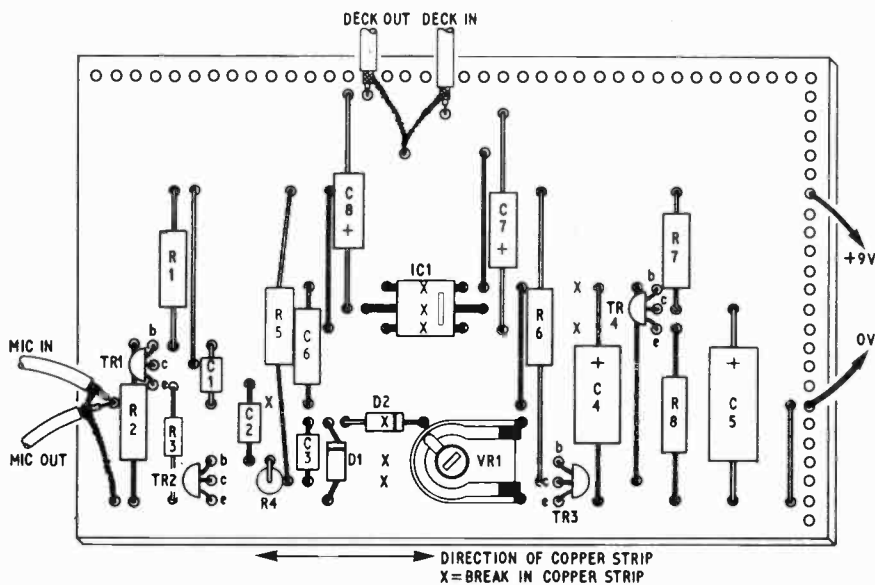


Fig. 3. Component layout and 0.1 in track Veroboard cutting details

## COMPONENTS . . .

### VOICE OPERATED FADER

#### Resistors

R1	220k $\Omega$
R2	100k $\Omega$
R3	2.7k $\Omega$
R4	1.8M $\Omega$
R5	10k $\Omega$
R6	22k $\Omega$
R7	3.3k $\Omega$
R8	560 $\Omega$
R9	See text

#### Capacitors

C1-C3	0.1 $\mu$ F Mylar film
C4	47 $\mu$ F, 10V elect.
C5	220 $\mu$ F 10V elect.
C6	680pF polystyrene
C7, C8	1 $\mu$ F 16V elect.
C9	100 $\mu$ F 10V elect.

#### Semiconductors

TR1-TR4	2N3704
D1, D2	1S44
D3	BZY88 C9V1, 9.1V Zener
IC1	MFC 6040 (Motorola). Available from Jermyn or Arrow Electronics

#### Potentiometers

VR1 100k $\Omega$  linear horizontal mounting pre-set

#### Miscellaneous

0.1in Matrix Veroboard measuring 3.75in  $\times$  2.75in  
Wire and coaxial cable as needed

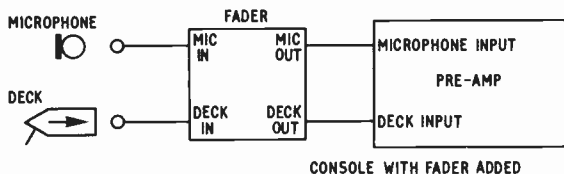
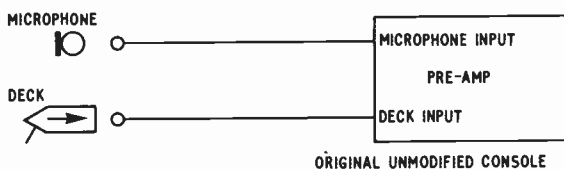


Fig. 4. Discotheque console circuit with and without voice operated fader

### CONSTRUCTION

The unit is quite simple to construct as can be seen from Fig. 3. Using standard 0.1in matrix Veroboard 3.75  $\times$  2.5in the layout of Fig. 3 may be followed. Coaxial cable should be used for the microphone leads to avoid hum pick-up.

Equally, circuit installation is simple as is shown in Fig. 4.

If the circuit of Fig. 2 is to be used, this may be added to the board carrying the main components or simply suspended in the wiring since it consists of so few components. ★

# NEXT MONTH...



## IGNITION TIMING LIGHT


By simply flashing the light from this portable unit on your car crankcase and pulley the state of ignition timing can be seen.

## I.C. POWER SUPPLY

A dual power supply giving all the common voltages for linear and T.T.L. integrated circuits. Each supply gives 100mA with variable overcurrent protection.

## PE RONDO

## LOUDSPEAKER ENCLOSURE

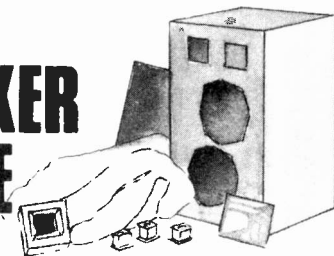

Construct your own Hi-Fi loudspeakers for the P.E. Rondo Quadraphonic System. (Equally suitable for use with other audio systems, of course.)

Infinite baffle enclosure, with four 8 ohm units and a six-element crossover network.

Design and constructional details given.

# PRACTICAL ELECTRONICS

JANUARY ISSUE ON SALE DECEMBER 14, 1973

# PHASE LOCKED LOOPS

BY J.B. DANCE M.Sc.

THE BASIC theory of phase locked loops has been reviewed in a non-mathematical way in the previous articles in this series. We will now consider in detail the types of phase locked loops which are currently available together with examples of the types of circuit in which they can be used.

Monolithic phase locked loops are necessarily fairly complex devices. In general the various manufacturers have evolved devices which are quite different from one another and they must therefore be considered separately.

## SIGNETICS H.F. LOOPS

The Signetics International Corporation manufacture three rather similar monolithic phase locked loops which can operate at high frequencies. They are the NE560B, the NE561B and the NE562B devices.

These three phase locked loops all employ the same phase detector, the same voltage controlled oscillator and the same voltage regulator stages. The basic parameters are therefore very similar for all the three devices, but there are differences in the metallic interconnections which make some types especially suitable for certain applications.

## NE560B

The NE560B can be regarded as the most fundamental of the three devices. It has the basic phase locked loop structure shown in the block diagram of Fig. 3.1. This device is suitable for high linearity f.m. demodulation, for telemetry decoding, for use in signal generators, in frequency shift keying receivers, in tracking filters, in circuits for exact frequency duplication in a high noise environment, etc.

The voltage controlled oscillator in this device provides two outputs of opposite polarity to each other.

## NE561B

The NE561B contains all the circuitry of the NE560B, but also has an analogue multiplier which can be used as a quadrature detector. This allows the device to be employed for the synchronous

detection of amplitude modulated signals if an external 90 degree phase shift network is added.

The NE561B can also be employed in a.m./f.m. i.f. strips, in signal generators, in telemetry decoders, in tracking filters, etc.

## NE562B

The NE562B is similar to the NE560B, but the loop is broken between the voltage controlled oscillator and the phase comparator. A frequency dividing circuit can therefore be inserted in the loop at this point if it is desired that the voltage controlled oscillator shall operate at a harmonic of the input frequency.

The NE562B is therefore especially useful in frequency synthesisers and for frequency multiplication and division. In addition, it can also be used in f.m. i.f. strips and for most of the other applications for which the NE560B is suitable.

## SUMMARY OF DATA

Each of these three phase locked loops can be operated over a frequency range from less than 1Hz to over 15MHz, the centre or free-running frequency being set by the value of a capacitor connected between two pins of the voltage con-


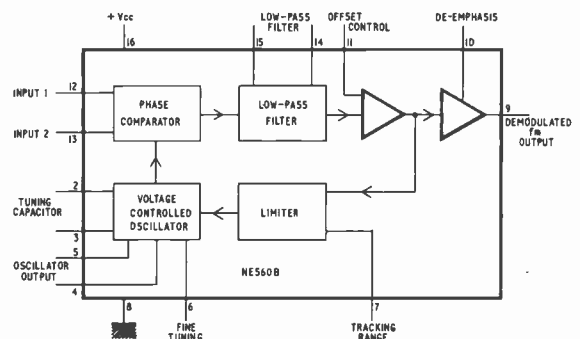


Fig. 3.1. Block diagram of the NE560B phase locked loop. The numbers refer to pins on the dual-in-line versions
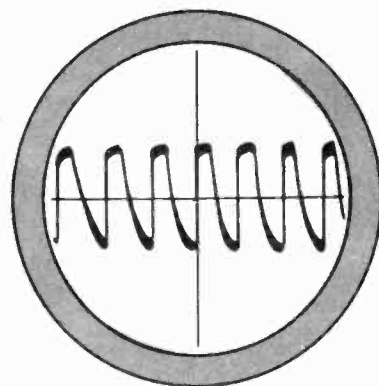
# look! electronics really mastered

**... practical  
... visual  
... exciting!**

no previous knowledge  
no unnecessary theory  
no "maths"



RAPY


## BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

### 1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.
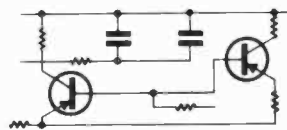
### 2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

### 3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to: we do not employ representatives

NAME


BLOCK CAPS

ADDRESS

PLEASE EL123

**special free gift also to all our students**
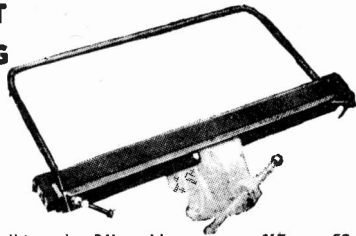
# PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



With Bevelled Former Bars

No. 1. Capacity 18 gauge mild steel x 36in. wide ... £17 carr. 50p  
 No. 2. Capacity 18 gauge mild steel x 24in. wide ... £12 carr. 38p  
 No. 3. Capacity 16 gauge mild steel x 18in. wide ... £12 carr. 38p  
 Also new bench models. Capacities 36in. x 18 gauge £35. 24in. x 16 gauge £32.  
 Carriage 75p. Add 10% VAT to total price of machine and carriage.  
 End folding attachments for radio chassis. Tray and Box making for 36in.  
 model, 27p per ft. Other models 17p. The two smaller models will form  
 flanges. As supplied to Government Departments, Universities, Hospitals.


One year's guarantee. Money refunded if not satisfied. Send for details.  
 A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

# ELECTRONIC DETECTOR for GAS & SMOKE

COMPLETE MAINS OPERATED parts kit &  
 flush or surface mounting box £8.45 P&P 20p.  
 parts available separately;  
 TGS 105 sensor ..... £1.80 P&P 10p.  
 Transformer ..... £1.50 P&P 20p.  
 PCB and circuit diagram ..... £0.55 P&P 10p.

PLEASE ADD 10% VAT TO THE ABOVE

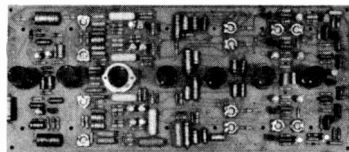ELECTROMECH Ltd, Ruckinge, Ashford, Kent TN26 2EF



**AURORA**  
 Multichannel Sound Controlled Light (PE Apr./Aug. 71). S/c's (excl. SCR's), Rs, Cs, Pots, Cores—8 ch. £17.50; 4 ch. £9.95. Reg. PSU £3.65. PCB £4.40. 4 ch. control (4 1/2in x 10 1/2in) Mk. 2—also holds rotary or slider pots £2.20. P/A (4 1/2in x 5in) Mk. 2—for PSU, Sync Gen. 8 cores, 8 SCR's, £1.10. SCR's—1A, 50p.

**A. F. SIGNAL GENERATOR**  
 (PE Nov. 72). S/c's, Rs, Cs, Pots, Sw's, PCB (2 1/2in x 4in) also holds Sw's, £3.15.

**LOUD-HALER AND SIREN**  
 (Pre-amp and Siren Generator) (PW Dec. 72). S/c's, Rs, Cs, Pot, PCB (2 1/2in x 2 1/2in). £2.20 (White stocks last). Main Amp Module PCS+ obtainable to special order, £6.

**GEMINI STEREO AMPLIFIER**  
 (PE Nov. 70/Mar. 71) Stereo Sets & PCBs. Pre-amp—S/c's, £1.80. Rs, Cs, Pots, Maka-Sw's—with 1/2W MO Rs, £10.90—with 1/2W C.F. Rs, £8.90. PCB (3 1/2in x 10 1/2in) for sets with MO and 1/2W Rs, also holds rotary or slider pots and Maka-Sw's, £1.90. Main Amp—Rs, Cs, Pots, £5.20. PCB (3 1/2in x 5in), £1.15. PSU—Rs, Cs, Pot, £3.70. PCB (2 1/2in x 4in), 65p.

**GEMINI STEREO TUNER**  
 (PE Apr./Jun. 72). Rs, Cs, Pot, £3.80. PCB as publ., £1.50.

**MICROPHONE MIXER**  
 (PE Apr. 69). S/c's, Rs, Cs, Pots, £2.60. PCB (3 1/2in x 4 1/2in) also holds 6 rotary or 4 slider pots, £1.10.


**LOGICAL RADIO CONTROL AND MODEL SERVO CONTROL**  
 (PE Feb./Jun. 72)—Details in lists—Hurry not many left!

**BIOLOGICAL AMPLIFIER**  
 (PE Jan./Feb. 73). P/A Set—S/c's, i.c.'s, Rs, Cs, Pots, PCB (1 1/2in x 3 1/2in), £3.50. O/P Stages (S/c's, Rs, Cs, Pots and Sw's as reqd.). Alphaphone 53p, Cardiophone 66p, Freq. Meter £1.60, Vis-Feedback 55p. Audio Amp PC7 avail. to order £5.20.

**ELECTRONIC PIANO**  
 (PE Sep. 72/Jan. 73). PCB PRICES DOWN. Details in lists.

**8 WATT AMPLIFIER**  
 (PW Nov./Dec. 72). Pre-amp—S/c's, Rs, Cs, Pots, Sw—Mono, £2.50; Stereo, £5.20. PCB (3 1/2in x 7 1/2in) (Stereo) also holds rotary or slider pots and Sw, £1.50. Main Amp—S/c's, Rs, Cs, Pot—Mono, £3.65; Stereo, £7.30. PCB (2 1/2in x 3in) Mono, 60p.
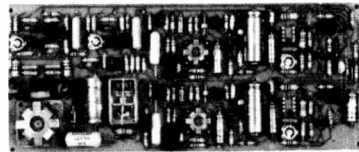
# PHONOSONICS NEW LOW PRICES FOR MANY PCB'S AND KITS



**HI-FI TAPE LINK**  
 (PE Mar./Apr. 73). S/c's, i.c.'s, Rs, Cs, Relay and pe-base, Pot, Cores and pe-bases. Sw's, Pots, Panel Lamp—Mono, £11.80; Stereo, £18.70. PSU, £2.50. PCB—Main Circuit (3 1/2in x 9in) (Stereo) also £2.50. PCB—Sub-Assembly. (2 1/2in x 6 1/2in) (Stereo) Mk. 2 holds Sw, Rs, Cs, Presets and mounts on Sw's, 80p.

**REVERBERATION UNIT**  
 (PW Nov./Dec. 72). S/c's, Rs, Cs, Slider Pots, T/fmr, £6.80. PCB (2in x 1 1/2in) also holds sliders, £1.20. 9in Spring Unit avail. to order, £3.75.

**VIBRASONIC GUITAR PRE-AMP**  
 (PW Sept. 70). Incl. Mic P/A, 2-Guitar P/A, Trem and Tone Controls, Master Volume. S/c's, Rs, Cs, LDR, Rotary Pots, Lamp, Coupling T/fmr, £6.65. PSU, £2.80. PCB (3 1/2in x 10 1/2in) Mk. 2, also holds 7 rotary or slider pots, £1.75.

**ULTRASONIC TRANSMITTER-RECEIVER**  
 (PE May 72). S/c's, Rs, Cs, Pot, Relay, Dual PCB (2in x 5 1/2in), £3.90. T/ducers avail. to order, £6.30 per pair.

**ALSO**  
 PCBs as published (while stocks last) for:  
 DIGITAL PSU (PE Aug. 72), 50p  
 OSCILLOSCOPE P/A (PE Aug. 72), 33p  
 SCORPIO (PE Nov./Dec. 71), 60p  
 TRIFFID (PE Feb. 73), 60p

**AND**  
 DIGITRONIC (PW Mar. 73). Read-out PCB (1 1/2in x 3 1/2in), 60p.

**TAPE NOISE LIMITER**  
 (PE Feb. 72). S/c's, Rs, Cs, Pot, PCB (1 1/2in x 3in), £3.20. Reg. PSU and PCB (1 1/2in x 2 1/2in), £3.10.

**VERSATILE LIGHT EFFECTS UNIT**  
 Single Channel Sound Controlled Light with built-in variable strobe, (PE June 72). S/c's, Rs, Cs, Pots, T/fmrs, Keyswitch, £8.85. PCB (3 1/2in x 7 1/2in) Mk. 2, also holds pots, Sw, T/T7 T/fmr, £1.50. SCR's—1A, 50p.

**PHOTOPRINT PROCESS CONTROL**  
 (PE Jan./Feb. 72). For colour and B & W—finds exposure, controls timing, stabs, mains voltage. S/c's, SCR, LDR, Rs, Cs, Pots, Relay, Keyswitch, T/fmr, £7.50 PCB (3 1/2in x 5 1/2in) also holds pots, Sw, Relay, £1.20.

**SOUND SYNTHESIZER**  
 (PE 1973)  
 Details of PCB's & Components in lists. SOME PRICES DOWN.

## SEMICONDUCTORS

AC128	20p	ZTX531	22p
AC176	20p	ZN706	13p
AD161	20p	ZN914	22p
BC107	9p	ZN1304	20p
BC108	9p	ZN2905	23p
BC109	9p	ZN2907	22p
BC147	11p	ZN3702	10p
BC148	11p	ZN3704	10p
BC149	11p	ZN3823E	31p
BC157	12p	ZN5777	40p
BC158	12p	IN914	4p
BC159	12p	IN4001	9p
BC204	14p	IN4002	7p
BCY71	23p	IN4004	8p
BFY51	16p	IN4005	10p
BSY95A	12p	BA145	17p
OC28	45p	OA91	7p
OC71	12p	OA200	6p
OC84	24p	Z11	50p
ORP12	48p	741C	36p
TS43	24p	(8-pin DIL)	100/63
ZTX107	9p	UA7815	£2.47
ZTX503	14p	(TO3 can)	150/63

## CAPACITORS

ELECTROLYTIC		(µF/V)		TANTALUM BEAD		(µF/V)		POLYESTER		C280AE	
220/10	6p	220/16	6p	0.1/35	12p	0.01	3p	250V(µF)			
220/25	6p	220/25	10p	0.22/25	12p	0.015	3p				
220/40	6p	220/40	12p	0.47/35	12p	0.022	3p				
220/50	6p	226/63	18p	1.0/35	12p	0.033	3p				
330/10	6p	330/10	6p	1.5/35	12p	0.047	3p				
470/6.3	6p	470/25	12p	2.2/35	12p	0.068	3p				
470/16	6p	470/40	16p	4.7/35	12p	0.1	4p				
500/6.3	6p	500/6.3	10p	10/25	16p	0.15	3p				
680/6.3	10p	680/6.3	10p	15/6.3	16p	0.22	3p				
1000/10	12p	1000/25	20p	22/16	16p	0.33	7p				
1000/25	20p	1000/40	40p	47/6.3	16p	0.47	9p				
1000/50	20p	1000/50	40p	47/16	25p	0.68	11p				
2200/25	45p	2200/25	45p			1.0	14p				
2200/40	50p	2200/40	50p								
3300/63	110p	3300/63	110p								
3300/100	£3	3300/100	£3								
4700/16	60p	4700/16	60p								
4700/25	75p	4700/25	75p								
4700/40	93p	4700/40	93p								

## SWITCHES

Makaswitch:	
Shaft assembly	48p
Wafers	33p
Screens (per	
pk of 5)	12p
Spacers (per	
pk of 10)	8p
Rotary:	
3P4W	30p
Multipole	
Lever:	
4CL/4CL	£1.30
4CL/4CN	£1.30
Knobs	6p
Slide:	
DRPT	24p

## NEW!

**RONDO** (PE current series)  
**PHASING UNIT** (PE Sept. 73)  
**ENLARGER EXPOSURE METER AND THERMOMETER**  
 (PE SEPT. 73)  
**SEMICONDUCTOR TESTER**  
 (PE OCT. 73)  
**WIND AND RAIN EFFECTS**  
 (PE OCT. 73)  
 DETAILS IN LISTS

## TRANSFORMERS (MAINS)

Sub-min 12V-0.12V 50mA	£1.50
Min 0-6V 0-6V 6VA	£1.30
Min 0-12V 0-12V 6VA	£1.30
Min 0-20V 0-20V 6VA	£1.30
17 1/2V 1-6A	£1.88
0-25-30 0-25-30V 1.5A	£3.60

**RELAYS**  
 2PCO 12V £1  
 4PCO 12V £1.30  
 Relay base & Clip 20p  
 Reed Relay 85p  
 6-9V

## V.A.T.

U.K. Orders only—add 10% to total cost or order.

## LIST


S.A.E. for free itemised list and with all enquiries please.

**GENERAL**  
 All PCB's Fibreglass, Drilled, Roller-Tinned. Layout and Circuit Diagrams Free with each PCB. Unless stated "as published", PCB's are designed by Phonosonics. Pots are rotary unless stated as slider. All components are brand new, top quality, guaranteed. Prices and deliveries of individual components subject to stock availability.

PHONOSONICS, DEPT. PE12, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW

MAIL ORDER ONLY



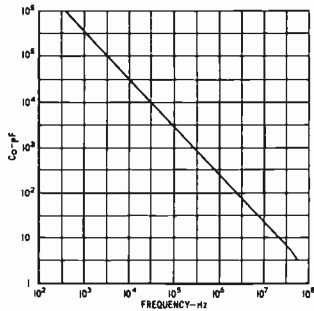

**Fig. 3.2. Graph showing the relationship between the centre frequency and the value of the timing capacitor**

trolled oscillator. The variation of this frequency with the value of the capacitor is shown in Fig. 3.2.

The control voltage is prevented from exceeding a preset level by a limiter between the control voltage amplifier and the voltage controlled oscillator. This range is known as the tracking range and is set by a control current into pin 7 of the i.c.

The typical operating voltage of these devices is 18V. The NE560B consumes less than 11mA, the NE561B less than 12mA and the NE562B less than 14mA.

The NE560B and the NE561B require a minimum of 100 $\mu$ V for locking, and can take 1V r.m.s. maximum. The corresponding figures for the NE562B are 200 $\mu$ V minimum and 3V r.m.s. maximum.

The maximum output voltage swing is 4V peak-to-peak.

If one applies a 1mV, 10.7MHz f.m. input signal which has a  $\pm 75$ kHz deviation and a 50 ohm source impedance, the demodulated output is typically 60mV in amplitude with a total harmonic distortion of 0.3% (typical).

When one of these loops is used for demodulating f.m. signals a capacitor may be connected from pin 10 to ground to provide de-emphasis.

At operating frequencies below 5MHz the low pass filter may be formed by connecting a capacitor (or capacitor and resistor in series) across the low pass filter terminals. At higher frequencies a capacitor from each terminal to ground should be used to ensure loop stability.

## APPLICATIONS


In order to illustrate the usefulness of phase locked loops some circuit diagrams will be given. Whilst it is not possible to give sufficient detail for the systems to be built it is hoped that the information given will give the reader an appreciation of the practical aspects of phase locked loop i.c.s.

## F.M. DEMODULATION


A phase locked loop can replace almost the whole i.f. strip, limiter and f.m. detector of a conventional receiver. A typical circuit using the NE560B as f.m. demodulator with an i.f. amplifier and limiter is shown in Fig. 3.3.

The input from the f.m. tuner unit is first amplified by the two sections of a Signetics NE510A dual high frequency differential amplifier. The low output impedance signal from the NE510A is coupled by C4 to pin 12 of the NE560B. The other input (pin 13) of the phase comparator is grounded with respect to radio frequencies by C5. The capacitors C4 and C5 may each have a value of 20pF when the signal frequency is 10.7MHz.


The frequency of the loop is set by the variable capacitor C9 which is connected between pins 2 and 3 so that the centre frequency becomes approximately equal to the signal frequency. The value of C9 may be estimated from Fig. 3.2.

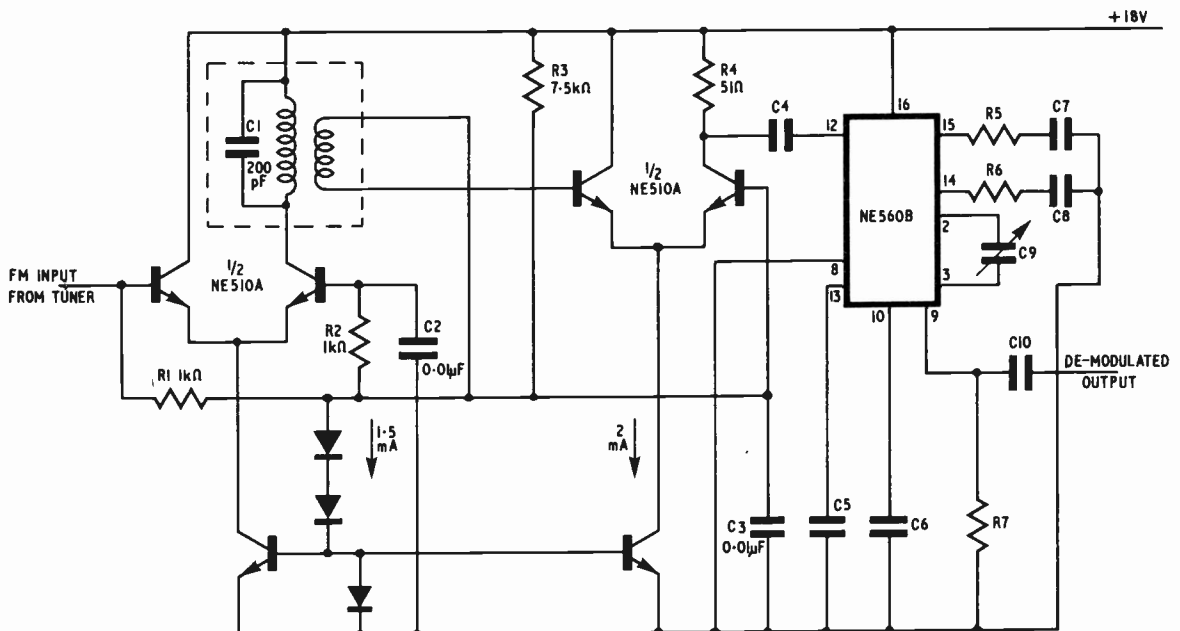

**Fig. 3.3. Circuit diagram of the NE560B used in an f.m. demodulator**

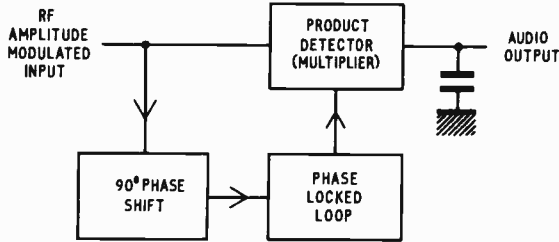

**Fig. 3.4a. Block diagram showing the NE561B used as an a.m. demodulator**

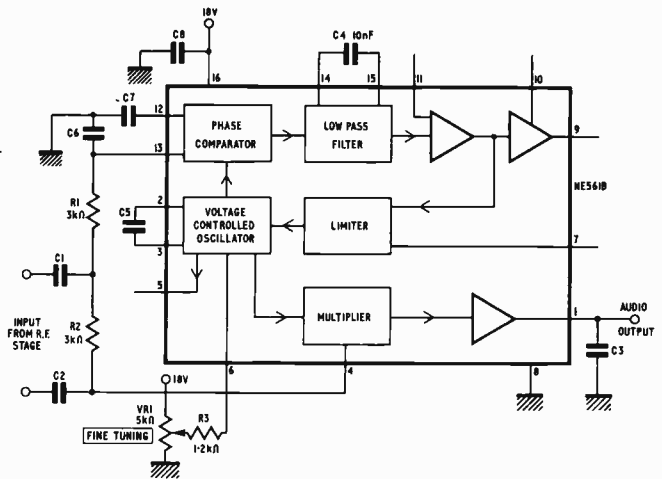

**Fig. 3.4b. Practical circuit of the a.m. demodulator**

Fine tuning is easily accomplished by using a variable capacitor for C9. However, a potentiometer connected between the power supply lines with the slider connected to pin 6 via a 200 ohm current limiting resistor may be employed.

Components R5, R6, C7 and C8 form the low-pass filter which controls the capture range and the selectivity. The value of the capacitors in microfarads is approximately 2660 divided by the required bandwidth in hertz.

### DE-EMPHASIS

The de-emphasis is introduced by merely connecting pin 10 via a capacitor to ground. The value of this capacitor multiplied by the internal eight kilohm resistance should produce a time constant of about 50µs for the standard f.m. broadcasts in the U.K. Thus  $C_6 = 50 \times 10^{-6} / 8000 = 6.25\text{nF}$ , but this value is in no way critical.

### THE NE561B FOR A.M. RECEPTION

The NE561B can be connected as in the block diagram of Fig. 3.4a for the detection of a.m. signals.

The 90 degree phase shift circuit changes the phase of the input signal so that the voltage controlled oscillator in the phase locked loop operates in phase with the input signal. The output from this oscillator is fed to the product detector where it provides the local oscillator signal.

A practical a.m. detector circuit using the NE561B is shown in Fig. 3.4b. It can be used over a fairly wide frequency range, but component values will be quoted for the medium wave band (550kHz to 1.6MHz).

The values of the by-pass and coupling capacitors should be chosen for a low impedance at the operating frequencies. For medium wave use C2, C7 and C8 may therefore be 0.1µF.

### CAPACITOR TUNING

The value of C5 must be selected so that the voltage controlled oscillator operates at the required input signal frequency. If desired, the capacitor C5

may be a variable one, in which case the connections to pin 6 (R3 and VR1) may be omitted.

When a variable capacitor is employed for C5, its value will be approximately 300 divided by the input signal frequency in megahertz at the capacitor setting concerned. For the 550kHz to 1.6MHz range, the value of C5 should range from about 550pF to about 180pF.

### RESISTOR TUNING

If the tuning is to be carried out by the variable resistor VR1, the value of C5 should be chosen so that when no current is injected or removed from pin 6, the voltage controlled oscillator operates at the geometric mean frequency of the band to be received. This geometric mean is equal to the square root of the product of the lowest and highest frequencies in the band. In the case of the 550kHz to 1.6MHz receiver, this mean frequency works out as 940kHz.

The complete medium wave band may be tuned by VR1; this potentiometer may be a ten-turn helical type to permit accurate setting. The value of R3 is selected to give the desired tuning range and will be about 1.2 kilohm when an 18V power supply is employed.

### PHASE SHIFT

The component values of the phase shift circuit may be determined in the following way.

If  $R_1 = R_2 = 3\text{k}\Omega$ , the  $C_1 = C_6 = (1.3 \times 10^{-4} / f)\text{F}$  where  $f$  is the midband frequency. In the medium wave receiver,  $f$  is 0.94MHz and  $C_1 = C_6 = 1.35 \times 10^{-10}\text{F} = 135\text{pF}$ .

### LOW-PASS FILTER

The value of the low-pass filter capacitor, C4, is not at all critical, since no information is derived directly from the loop error signal. One merely requires to establish stable operation. A 10nF capacitor is suitable for C4.

## TAPE RECORDER FLUTTER METER

A circuit devised by R. Blair of Houston using the NE561B in a tape recorder flutter meter is shown in Fig. 3.5. A 3kHz sinewave is fed to the recording head. The output from the replay head is fed to the phase locked loop which detects any variations in frequency from the 3kHz value.

The NE561B circuit is set to a nominal value of 3kHz using the fine tuning control. The demodulated output is capacitively coupled to an amplifier of high input impedance. The output level changes with any change in the frequency of the signal applied to the phase locked loop.

An oscilloscope may be employed to measure the peak deviations and a true r.m.s. voltmeter to make r.m.s. flutter measurements. (The waveform is complex and therefore meters which read the peak or average value will not give true readings.) The output can be filtered to study any selected bands of frequencies.

## THE 565


One of the best known low frequency phase locked loops is the 565 device. This is available as the Signetics NE565A device and as the National Semiconductor LM565CN device in a 14 pin dual-in-line encapsulation. The NE565K and the LM565CH are electrically equivalent devices in a TO-99 circular encapsulation.

The basic circuit for all of these devices together with the pin connections is shown in block form in Fig. 3.6.

The loop is broken between the output of the voltage controlled oscillator and the input to the phase comparator (pins 4 and 5 respectively) so that frequency divider circuits can be inserted at this point for frequency synthesis applications. The low-pass filter is formed by the internal resistor marked RA in Fig. 3.6 and the external capacitor C2.

## FREQUENCY RANGE

The maximum frequency at which the voltage controlled oscillator of the 565 devices can operate is

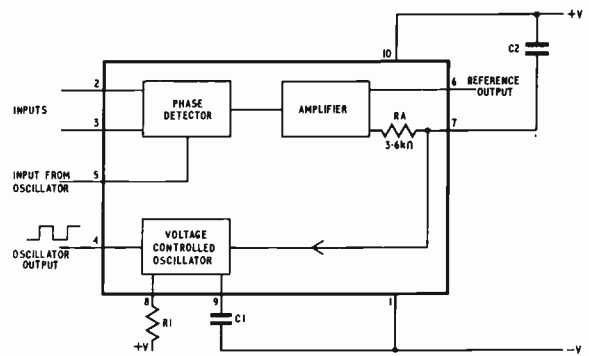


**Fig. 3.6. Block diagram of the 565 low frequency phase locked loop. This is the pin numbering for the NE565A (Signetics) and the LM565CN (National Semiconductor), both 14 pin dual-in-line**

about 500kHz. The minimum practical operating frequency is set by the maximum value of the timing capacitor (C1 in Fig. 3.6) which can reasonably be used. If one decides that this maximum value is  $10,000\mu\text{F}$ , one can obtain a frequency as low as 0.001Hz.


The free-running frequency of the voltage controlled oscillator is only partly determined by the value of the timing capacitor C1. The frequency can be changed over a range of at least 10:1 using a single value of C1 by varying the value of R1 in the pin 8 circuit; alternatively the value of the current fed to pin 8 may be varied.

The typical variation of the free-running frequency with the value of R1 for four values of the timing capacitor is shown in Fig. 3.7. For any given value of the timing capacitor, the free-running frequency is about an order of magnitude lower than that of the high frequency loops.

The free-running frequency of the 565 oscillator is given by the approximate equation  $f = 1.2 / (4R_1C_1)$  where R1 and C1 are the timing components shown in Fig. 3.6.

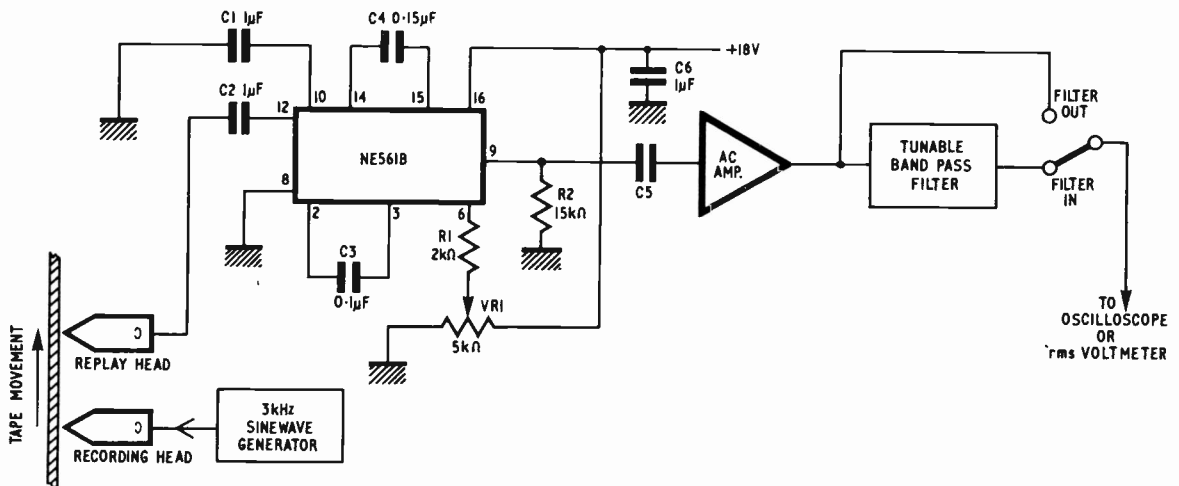

**Fig. 3.5. A tape recorder flutter meter using the NE561B phase locked loop**

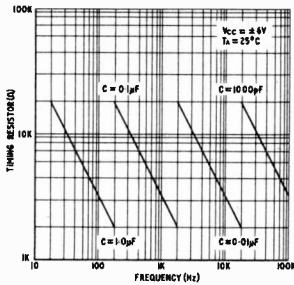

**Fig. 3.7. Relationship between the centre frequency and the timing components for the 565 integrated circuit**

The value of the timing capacitor C1 can vary over wide limits, but the resistor R1 should have a value of between 2k $\Omega$  and 20k $\Omega$ , the optimum being about 4k $\Omega$ .

When using power supply lines which are symmetrical with respect to ground, the range of voltages which may be employed is  $\pm 5V$  to  $\pm 12V$ . When  $\pm 6V$  power supplies are employed, the typical current taken is 8mA with a maximum value of 12mA. The maximum permissible power dissipation is 300mW.

## THE OSCILLATOR

The voltage controlled oscillator circuit used in the 565 devices can be obtained as a separate integrated circuit type 566. It is available as the Signetics 8 pin dual-in-line device type NE566V and the similar National Semiconductor device type LM566CN. The circular TO-99 equivalents are types NE566T and LM566CH. The SE566T and LM566H are close tolerance devices.

In the 565 phase locked loops, triangular and square waves are generated by the voltage controlled oscillator, but no buffer stage is provided to give a triangular wave output as in the 566. The square wave output (about 5.4V peak-to-peak) is available at pin 4 of the 565.

The output of the low-pass filter (pin 7 of Fig. 3.6) is connected internally to the voltage control input of the oscillator. The oscillator frequency can therefore be controlled by a signal fed to the demodulated output terminal (pin 7).

## LOCKING RANGE

The range of input frequencies over which the loop will remain in lock on each side of the centre frequency is given by the approximate expression  $\pm 8f/V$  where  $f$  is the centre frequency and  $V$  is the total voltage between the power supply lines.

The 565 can therefore track the input frequency over a very wide range (typically  $\pm 60\%$  of the centre frequency). Locking can be obtained over a greater fraction of the input frequency than in the case of high frequency loops.

The 565 input impedance is typically 10 kilohm (minimum 5 kilohm). The minimum input signal required to produce tracking is typically 1mV r.m.s.

The linearity of the f.m. response is very good (typically about 0.2%).

## FREQUENCY MULTIPLICATION

In the circuit of Fig. 3.8, a frequency divider circuit has been inserted in the loop between pins 4 and 5. The output of the voltage controlled oscillator is divided in frequency by a certain factor and the frequency divided circuit locks with the input signal. The oscillator therefore operates at a higher frequency than the input signal.

The value of C2 should be adequate to eliminate variations in the demodulated output voltage at pin 7 in order to stabilise the voltage controlled oscillator frequency.

The square wave output frequency can be taken from pin 4.

## METAL DETECTOR


Phase locked loops can be used to detect changes of frequency. Such changes can be produced when the coil of a tuned circuit approaches a piece of metal. Phase locked loops can therefore be used in metal detectors.

A circuit of this type which has been designed by J. Blecksmith of California is shown in Fig. 3.9. The 8in diameter search coil comprises 30 turns of copper wire (26 s.w.g.) and has an inductance of about 0.5mH. It is connected in the Colpitts oscillator circuit of TR1 which operates at about 100kHz.


This oscillator is coupled by C3 into the input of the 565 circuit (pin 2). A current source (TR2 and TR3) is employed to supply most of the current of about 2.5mA which passes to pin 8 and which equals the charging and discharging current of C4. The use of this current source increases the output of the loop at pin 7 to about 0.5V for a 1% frequency deviation. (This follows from the fact that the 20k $\Omega$  resistor R7 will produce a change in the current to pin 8 of  $0.5/20,000 = 0.025\text{mA}$  for a 0.5V change. In other words a change of 0.5V produces about 1% change in the pin 8 current.)

The output voltage at pin 7 is compared with the reference voltage at pin 6 by the differential amplifier of TR4 and TR5. The output of this amplifier drives a centre reading meter which has a  $\pm 100\mu\text{A}$  scale. The meter zero is set by VR2 and the sensitivity by VR3.

When the search coil is brought near to a non-ferrous metal object, the frequency of the TR1 oscillator circuit will rise and so will the meter indication. Any object containing iron will increase the inductance of the loop and reduce the frequency of oscillation; the meter reading will therefore fall.

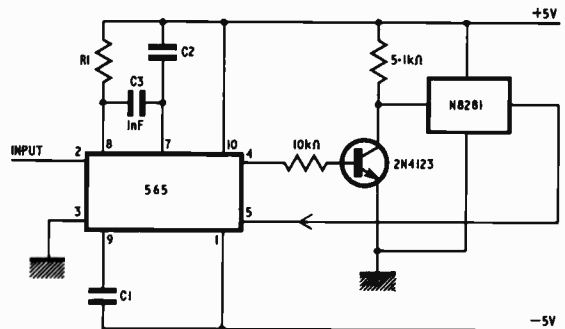

**Fig. 3.8. A frequency multiplier using the 565 and a divider**

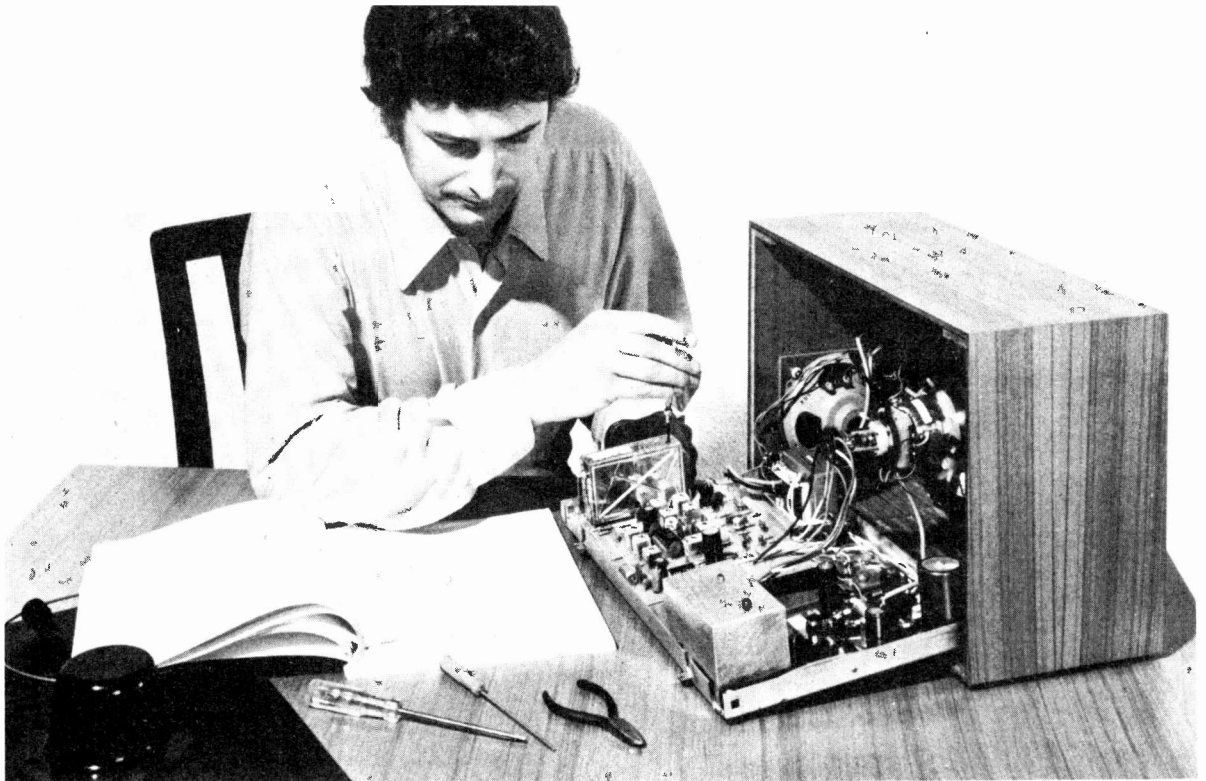

## LEARN about MODERN TV Design by building this Heathkit 12" B/W Portable

the new Heathkit GR-9900 portable 12" UHF Monochrome Television kit. A unique chance to double the pleasure available from any other television set — because you build this yourself.

We've used the latest modular construction and advanced design concepts to produce an outstandingly high performance TV worthy of the Heathkit name. All the main electronics are mounted on two easy-to-assemble printed circuit boards—this plus the use of no less than four integrated circuits perform the complex function of IF, video, sound, line frame and scan. Factory pre-aligned coils make alignment very easy and there are four presettable pushbutton controls for channel tuning—a luxury found in very few other models. The quality and fidelity is therefore excellent, and of a far higher standard than most ready-built televisions in the shops.

The GR-9900 is portable too—equally at home on

the mains or off your 12 volt battery for car, boat or caravan use. Add to this Heath's world renowned experience in the design of equipment for first-time kit builders, and you will be impressed on all counts of engineering, styling, and performance.


The instruction manual is surprisingly simple with big, clear illustrations to map out your way. Would-be TV engineer? Here's your chance to learn—by actually building a television yourself. The manual not only shows you how to get 100% personalised quality control on your own; in the event of anything going wrong, a Trouble-Shooting section enables you to find the fault—and, in most cases, to put it right unaided.

The GR-9900 is a kit you'll be proud to build and own. You have a choice of fully finished cabinets in teak or modern white and the kit price, £62.70 (carriage extra), includes a FREE high performance indoor aerial.
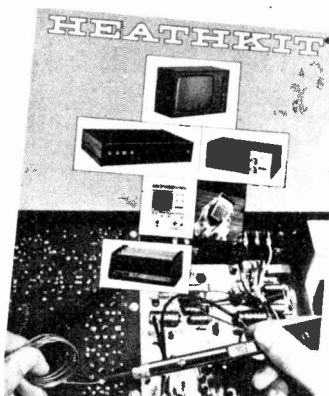
## FREE Heathkit Catalogue

Contains something for everyone: Hi-Fi Stereo, Testers & Instruments, SWL Metal Detectors... even a Battery charger Kit. Mail the coupon... Today! Heath (Gloucester) Limited, Gloucester GL2 6EE.

LONDON showroom  
233 Tottenham Court Road  
Tel 636 7349



## Choose cash or Heath Monthly Budget Plan

(Mail order prices and specifications subject to change without notice)

Please send me a FREE Heathkit catalogue

Name \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

HEATH  
Schlumberger

Heath (Gloucester) Limited, Dept. PE/12/73  
Gloucester GL2 6EE. Telephone 0452 29451

# TRANNIES

1 Dockyard Station Road,  
Old Harlow,  
Essex

All prices  
inclusive  
of V.A.T.

P/P 12½p.

Catalogue 10p.

(Saturday callers welcome)

## 74 Series TTL



SN7400	0.17	0.16	SN7426	0.50	0.46	SN7454	0.17	0.16	SN7494	0.85	0.82
SN7401	0.17	0.16	SN7427	0.50	0.46	SN7460	0.17	0.16	SN7495	0.85	0.82
SN7402	0.17	0.16	SN7428	0.77	0.76	SN7470	0.32	0.29	SN7496	0.98	0.93
SN7403	0.17	0.16	SN7430	0.17	0.16	SN7472	0.32	0.29	SN74100	£1.82	£1.76
SN7404	0.17	0.16	SN7432	0.50	0.46	SN7473	0.41	0.39	SN74104	£1.07	£1.04
SN7405	0.17	0.16	SN7433	0.98	0.93	SN7474	0.41	0.39	SN74105	£1.07	£1.04
SN7406	0.39	0.34	SN7437	0.71	0.68	SN7475	0.50	0.48	SN74107	0.44	0.42
SN7407	0.39	0.34	SN7438	0.71	0.68	SN7476	0.44	0.43	SN74110	0.61	0.59
SN7408	0.20	0.19	SN7440	0.17	0.16	SN7480	0.74	0.71	SN74111	£1.38	£1.27
SN7409	0.20	0.19	SN7441	0.74	0.71	SN7481	£1.32	£1.27	SN74119	£1.10	£1.05
SN7410	0.17	0.16	SN7442	0.74	0.71	SN7482	0.96	0.95	SN74121	0.44	0.43
SN7411	0.25	0.27	SN7443	£1.43	£1.38	SN7483	£1.21	£1.16	SN74122	£1.54	£1.43
SN7412	0.39	0.34	SN7444	£1.43	£1.38	SN7484	£1.10	£1.05	SN74123	£3.08	£2.97
SN7413	0.32	0.29	SN7445	£1.98	£1.95	SN7485	£3.96	£2.85			
SN7416	0.48	0.44	SN7446	£1.07	£1.04	SN7486	0.35	0.34			
SN7417	0.48	0.44	SN7447	0.98	0.88	SN7489	£6.05	£5.78			
SN7420	0.17	0.16	SN7448	£1.10	£1.07	SN7490	0.68	0.60			
SN7422	0.55	0.53	SN7450	0.17	0.16	SN7491	£1.10	£1.05			
SN7423	0.55	0.53	SN7451	0.17	0.16	SN7492	0.74	0.71			
SN7425	0.55	0.53	SN7453	0.17	0.16	SN7493	0.74	0.71			

## Volume controls POTENTIOMETERS

Carbon track 500 Ω to 2.2 meg Ω  
Log or Linear.  
Single 13p. Dual ganged (stereo) 44p.  
Single type with D.F. switch 25p.

## Carbon skeleton presets

Small high quality type (linear only)  
All values 100—5 meg ohms.  
0.1 watt 6p each  
0.25 watt 7p each

## Resistors

100 plus  
½ watt 5% carbon 1p 0.7p  
½ watt 5% carbon 1p 0.7p  
½ watt 10% carbon 2ip 2p  
range 10 ohms to 4.7 megohms.  
½ watt m/o 2% 3p 2.4p  
range 10 ohms to 1 megohms.

## Vereoboard

24 × 31	matrix	17p	22p
24 × 5	matrix	22p	24p
34 × 31	matrix	22p	24p
34 × 5	matrix	28p	28p
24 × 17	matrix	60p	78p
34 × 17	matrix	81p	£1.05
Pin insertion tool			82p
Spot face cutter		52p	62p
Pack of 36 pins		42p	42p
		20p	20p

## Linear Integrated Circuits

301 DIL	0.50	307 TO99	0.69	710C TO99	0.46	748C DIL	0.52
301 TO99	0.55	307 8 Pin DIL	0.88	723C DIL	0.89	748C TO99	0.42
301 8 Pin DIL	0.48	308 TO99	26.90	723C TO99	£1.00	1437 DIL	£1.30
301A DIL	0.89	308A TO99	27.40	741C 8 Pin DIL	0.35	1458 TO99	£1.30
301A TO99	0.88	709C DIL	0.35	741C 14 Pin DIL	0.36	3046 DIL	0.84
301A 8 Pin DIL	0.68	709C TO99	0.34	741C TO99	0.38		
307 DIL	0.69	710C DIL	0.44	747C DIL	0.80		

## Electrolytic Capacitors

4 VOLT		10 VOLT		16 VOLT		25 VOLT		63 VOLT	
47µF	6½p	22µF	6½p	1000µF	17p	2200µF	39p	1µF	6½p
100µF	6½p	47µF	6½p	1500µF	25p	5000µF	68p	2.2µF	6½p
220µF	6½p	100µF	6½p	2000µF	43p			4.7µF	6½p
330µF	6½p	220µF	8p	3300µF	38p			6.8µF	6½p
1000µF	13p	330µF	10p	6800µF	65p	40 VOLT		10µF	6½p
4700µF	29p	470µF	10p			6.8µF	6½p	22µF	6½p
		1000µF	11p	25 VOLT		15µF	6½p	68µF	10p
		1500µF	20p	10µF	6½p	33µF	6½p	100µF	11p
		2200µF	24p	22µF	6½p	47µF	6½p	150µF	13p
				47µF	6½p	100µF	9p	220µF	19p
		16 VOLT		100µF	8p	220µF	11p	330µF	22p
		15µF	6½p	150µF	8p	470µF	19p	470µF	26p
		33µF	6½p	220µF	10p	680µF	25p	1000µF	44p
		68µF	6½p	470µF	13p	1000µF	25p		
		150µF	18p	680µF	20p	2200µF	44p		
		2200µF	18p	1000µF	22p	3300µF	65p		
		3300µF	26p						
		6800µF	40p						

## Mullard Polyester's

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
250V P.C. mounting: 0.01µF, 0.015µF, 0.22µF, 3ip, 0.33µF, 0.047µF, 0.068µF, 4p, 0.1µF, 4ip, 0.15µF, 0.22µF, 5ip, 0.33µF, 7p, 0.47µF, 9ip, 0.68µF, 12p, 1.0µF, 14p, 1.5µF, 22p, 2.2µF, 27p.

**MULLARD POLYESTER CAPACITORS C296 SERIES**  
400V - 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 2ip, 0.068µF, 0.1µF, 0.015µF, 0.022µF, 0.033µF, 3ip, 0.047µF, 0.068µF, 1µF, 4ip, 0.15µF, 6ip, 0.22µF, 8ip, 0.33µF, 12p, 0.47µF, 14p, 0.68µF, 0.01µF, 0.015µF, 0.22µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 4ip, 0.22µF, 5ip, 0.33µF, 6ip, 0.47µF, 8ip, 0.68µF, 12p, 1.0µF, 14ip.

## Popular Transistors and Diodes

(Many other types stocked)

AC107	16p	AD149	40p	BC157	13p	BFY50	17p	2N3053	26p	40636	86p	OA47	9p
AC126	14p	AD161	32p	BC158	12p	BFY61	17p	2N3054	52p			OA81	9p
AC127	14p	AD192	32p	BC159	13p	BFY52	17p	2N3055	52p	<b>DIODES</b>		OA85	11p
AC128	14p	AD114	15p	BC168	11p	MP811	35p	2N3702	11p	1N914	8p	OA90	8p
AC142K	25p	AF115	15p	BC169	11p	OC29	40p	2N3703	11p	1N916	8p	OA91	8p
AC141K	28p	AF116	15p	BC182	12p	OC35	40p	2N3704	11p	1N4148	5p	OA95	8p
AC176	15p	AF117	15p	BC183	12p	OC36	45p	2N3705	11p	1N4001	4p		
AC187	14p	BC107	9p	BC184	12p	OC44	14p	2N3706	11p	1N4002	4ip		
AC188	14p	BC108	9p	BC212	12p	OC45	14p	2N3707	11p	1N4003	5ip		
AC187K	25p	BC109	10p	BC213	12p	OC71	14p	2N3708	11p	1N4004	6ip		
AC188K	25p	BC147	11p	BC214	12p	OC81	14p	2N3709	11p	1N4005	8p		
ACV20	22p	BC148	11p	BF194	15p	TTP41A	79p	2N3710	11p	1N4006	9p		
AD140	40p	BC149	12p	BF195	17p	TTP42A	91p	2N3819	28p	1N4007	10p		

## Volume controls POTENTIOMETERS

Carbon track 500 Ω to 2.2 meg Ω  
Log or Linear.  
Single 13p. Dual ganged (stereo) 44p.  
Single type with D.F. switch 25p.

## Carbon skeleton presets

Small high quality type (linear only)  
All values 100—5 meg ohms.  
0.1 watt 6p each  
0.25 watt 7p each

## Resistors

100 plus  
½ watt 5% carbon 1p 0.7p  
½ watt 5% carbon 1p 0.7p  
½ watt 10% carbon 2ip 2p  
range 10 ohms to 4.7 megohms.  
½ watt m/o 2% 3p 2.4p  
range 10 ohms to 1 megohms.

## Vereoboard

24 × 31	matrix	17p	22p
24 × 5	matrix	22p	24p
34 × 31	matrix	22p	24p
34 × 5	matrix	28p	28p
24 × 17	matrix	60p	78p
34 × 17	matrix	81p	£1.05
Pin insertion tool			82p
Spot face cutter		52p	62p
Pack of 36 pins		42p	42p
		20p	20p

## P.E. RONDO KITS

Supplied to full specifications complete with top quality P.C. boards, components and solder.

CBS SQ Matrix Decoder (including licence fees) £8.00 + 80p VAT.

Preamplifier Board £3.00 + 30p VAT.

Master Volume/Tone Controls/4 channel Balance Control Board £8.50 + 85p VAT.

Power Amplifier Board and Heat Sink (each board contains a stereo pair of amplifiers) £7.50 + 75p VAT.

Power Supply Board	£5.00 + 50p VAT.
Mains Smoother Capacitor	75p + 7p VAT.
Mains Transformer	£6.25 + 62p VAT.
Patched Chassis	£2.25 + 22p VAT.
Wooded Case	£1.75 + 17p VAT.
Hardware Pack	£2.00 + 20p VAT.
Control Section Facia	£3.50 + 35p VAT.

All other kits and components used in the P.E. Rondo will be available as they appear in this series.

## Transformers

12-24 volt Secondary		Amps	Volts	Amps	Part No.	Price Inc. P/P	
12	500mA	24	250mA	MT111		£1.20	
12	1	24	500mA	MT213		£1.26	
12	2	24	1	MT71		£1.89	
30 volt Secondary 12, 15, 20, 24, 30v		Amps	Part No.	Price Inc. P/P			
1	MT79			£2.02	1	MT103	£2.54
2	MT3			£2.78	2	MT104	£3.75
5	MT51			£5.21	4	MT106	£6.00
50 volt Secondary 19, 25, 33, 40, 50v		Amps	Part No.	Price Inc. P/P			

Many other types available See our Catalogue.



We are now Stockists of AMTRON High Quality Construction Kits (S.A.E. for full list)

UK65	Transistor Tester	£2.50
UK92	Telephone Amplifier	7.91
UK110	Stereo Amplifier 5 + 5w	11.07
UK115	Hi-Fi Amplifier 8w	4.31
UK120	Hi-Fi Amplifier 12w	5.20
UK125	Stereo Control Unit	6.30
UK160	I.C. Amplifier 8w	11.07
UK220	Signal Injector	2.57
UK235	Acoustic Alarm for Absent-minded Drivers	7.39
UK240	Parking Lights Automatic Switch	8.66
UK500	LW/MW/FM Radio Receiver	35.30
UK515	MW Radio Receiver	9.86
UK640	200mw Light Dimmer	7.24
UK790	Capacitive Burglar Alarm	7.57
UK840	Adjustable time lag car Burglar Alarm	6.81
UK875	Capacitive Discharge Electronic Ignition for internal Combustion Engines	14.51
TRA I	24-hour Digital Clock	40.50

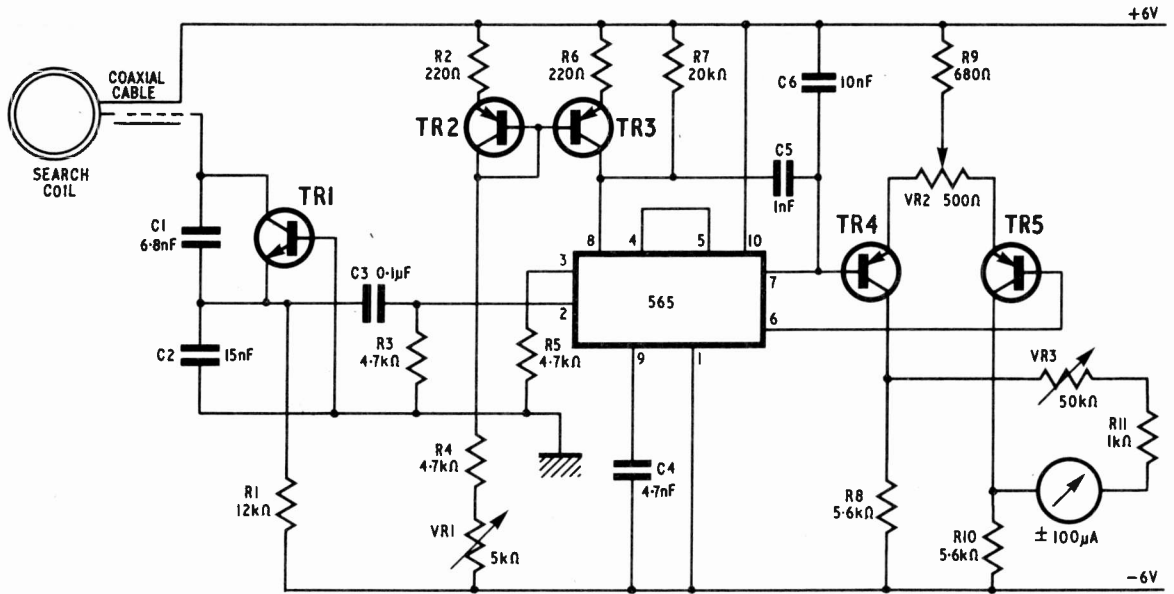


Fig. 3.9. A metal detector using the 565

### WEATHER SATELLITE APPLICATION

As an example of a very different application of the 565, its use in a weather satellite picture demodulator will be outlined.

Weather satellites continually photograph the earth from a distance of typically a few hundred miles. The pictures are stored in an electrostatic Vidicon tube and are read out during the succeeding 200 seconds.

The signal is transmitted on a 137.5MHz carrier frequency modulated with a 2.4kHz sub-carrier; the latter contains the picture information. The demodulated 2.4kHz tone is normally recorded on tape at the receiving station for subsequent processing.

When the tape is replayed, it is desirable to reproduce the 2.4kHz sub-carrier using a phase locked loop, since the latter will effectively filter out most of the noise and will track any flutter in the magnetic tape mechanism.

The basic circuit used in this application is shown in Fig. 3.10. The loop locks at the 2.4kHz frequency. If this is also the centre frequency of the loop, the square wave output from pin 4 of the 565 will be 90 degree out of phase with the input.

However, the zero crossing times of the triangular wave across the timing capacitor may be applied to the LM1596 doubled balanced modulator so that switching occurs in phase with the 2.4kHz sub-carrier.

The picture may be reproduced on a cathode ray tube. Detailed circuit information is available in the National Semiconductor report AN-46.

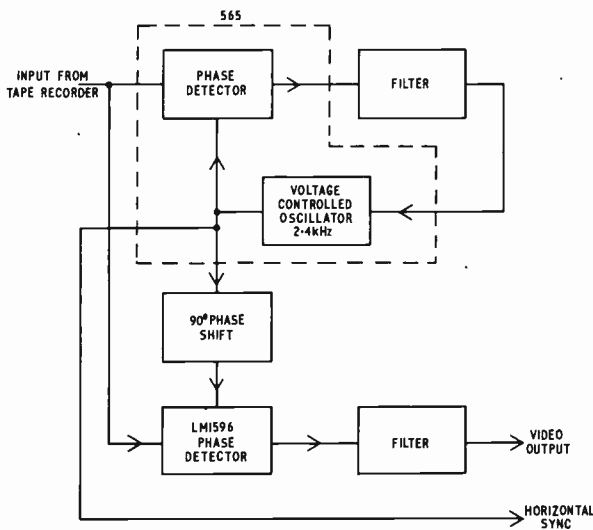


Fig. 3.10. A system for demodulating video signals from the 2.4kHz sub-carrier which is used by weather satellites

### AVAILABILITY

The Signetics phase locked loops are about the most widely available type at the present time and are available from many of the advertisers in PRACTICAL ELECTRONICS. The NE560B, NE561B and NE562B are available from S.D.S. Components Ltd., Portsmouth PO3 5JW at about £4.20 in small quantities. The Signetics 565, 566 and 567 are obtainable from the same source at about £4, £1.44 and £3.25 respectively.

National Semiconductor devices can be obtained from Semiconductor Specialists, Farfield Road, West Drayton.

Further information on these devices may be obtained from the Signetics Linear Integrated Circuit book and in data and applications notes from Signetics and National Semiconductors.

**Next month: more applications of phase locked loop integrated circuits will be described including stereo decoding**

# LOGIC TUTOR EXPERIMENTS..



## THE FULL ADDER

**I**N PRACTICE we must be able to add together two multi-digit numbers and as we saw last month the HALF ADDER does not go quite far enough to doing this. We have to design a circuit that is capable of accepting the two digits of the column (A with B) and incorporate a possible carry over from the previous (less significant) column.

### TWO STAGES

The simplest way of doing this is to carry out the operation in two stages; first add together the digits that are in the higher significance column—this is done in the HALF ADDER 1 of Fig. 8.1.

If the digits were 0 and 0 we would get a partial sum of 0 and a carry of 0. If either of the digits were 1 we would get a partial sum of 1 and a carry of 0 but if both digits were 1 we would get a partial sum of 0 and a carry of 1.

We shall come back to this carry in a moment but remember that if we get a carry, at all, at the output of HALF ADDER 1 the sum output of it is *bound* to be 0.

We now take the partial sum from the first HALF ADDER and combine it with the carry digit—that might have been generated by the previous column. This is done in HALF ADDER 2. This will generate a final sum and *could* generate a carry.

If you think about it you will see that if a carry is generated at the output of HALF ADDER 1 it is not possible to get a carry from HALF ADDER 2 (because the sum from the first stage would have been bound to be 0). However, if the sum from the first stage was 1 it *might* be that there was a carry in from the previous column and these combine in the second stage to give a carry out as well as the final sum. Whatever happens it is not possible to get a carry out of both stages at the same time so there is no question of having to add two carries together.

### FULL ADDER

Thus to generate a final carry out of the complete unit we only have to OR together the two possible sources of carry. This circuit is called a FULL ADDER and can be made using the building blocks we have already described in NAND form. We need two HALF ADDERS and an OR gate.

An unsimplified circuit showing the discrete stages in NAND logic appears in Fig. 8.2. Do not make this on Logic Tutor because we can simplify the circuit a little. Notice that we have double inversion on the two lines feeding the final NAND gate of the OR block. These negate each other and we are left with a complete FULL ADDER using nine NAND gates in Fig. 8.3. This you can make on Logic Tutor.

Using the switches and lamps and a piece of paper and a pencil show that the circuit truthfully follows the rules of arithmetic necessary to add the three input digits together.

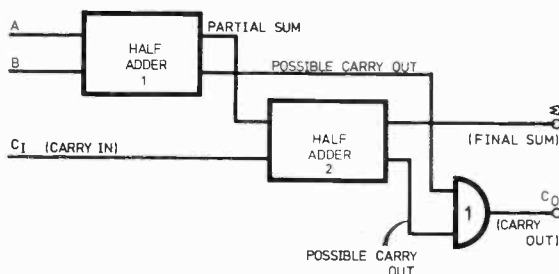


Fig. 8.1. Two HALF ADDERS are combined to form a FULL ADDER.

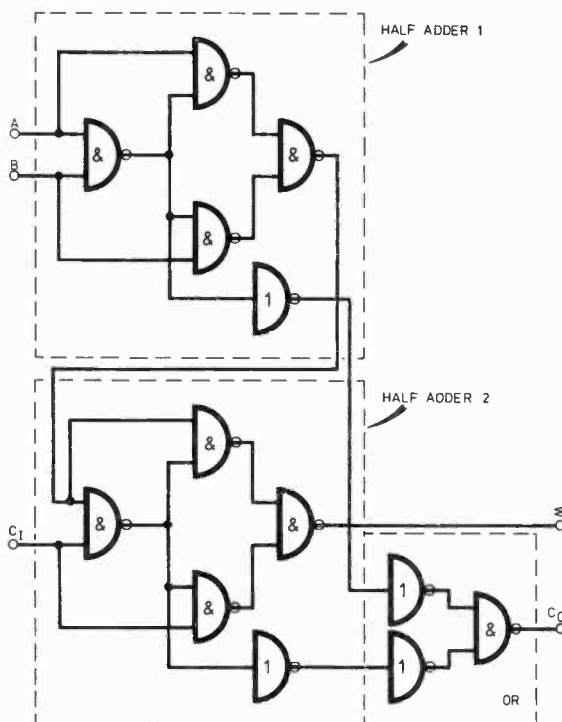


Fig. 8.2. A FULL ADDER using blocks of logic in unsimplified form. Note the two sets of double inversion before the final NAND gate in the  $C_0$  line.





# BOOK REVIEWS

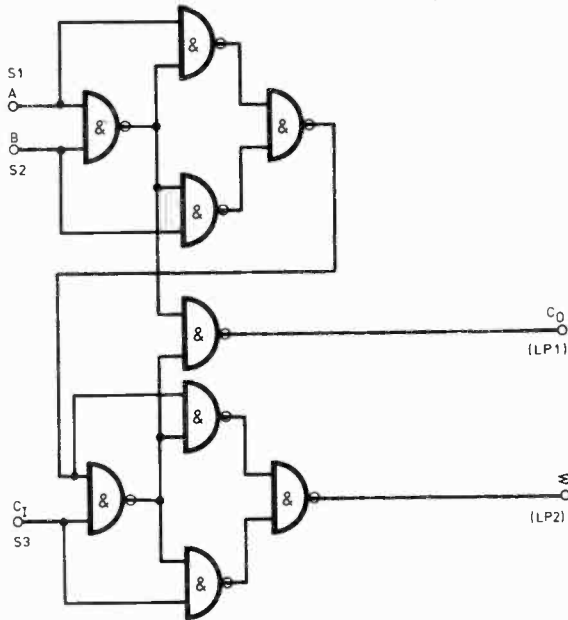


Fig. 8.3. A FULL ADDER that can be built on the Logic Tutor

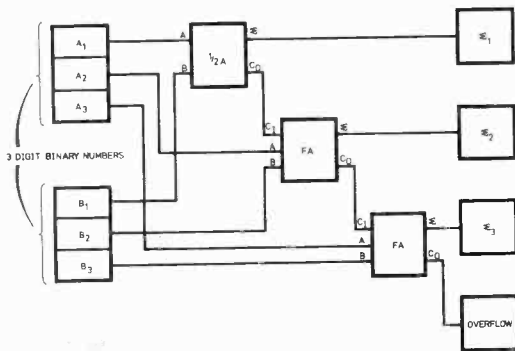


Fig. 8.4. Block diagram of a parallel adder capable of summing two, three-digit binary numbers to give a three- or four-digit answer

## MULTIDIGIT NUMBERS

In practice we have to add multidigit numbers together and the simplest way of doing this is to cascade FULL ADDERS—one after the other. The carry out from the previous column is connected directly to the carry in of the next. Fig. 8.4 is a block diagram of such a summing unit.

A<sub>1</sub> and B<sub>1</sub> are the least significant digits of the respective multidigit numbers and because of this they only need a HALF ADDER to produce a true sum and carry; however, all higher order digits have to be combined in FULL ADDERS.

You would need as many adding stages as there are digits when carrying out the process in parallel form consequently a parallel adder can be quite expensive but it is very fast in operation. A cheaper form is the serial adder (not shown in this series) but there is rather more complexity in handling the carry signals.

★  
by M. J. Hughes

## HOW TO LISTEN TO THE WORLD. 7th EDITION

By J. M. Frost  
Published in the U.K. by Fountain Press  
160 pages, 9in × 6in. Price £1.90

WHILST not exactly filled with "do it yourself" information on the making and using of radio receiving equipment, it does contain considerable information of general interest.

For example, how many people know the frequencies and addresses of a variety of Irish "pirate" stations currently in operation? A section of this volume provides details of a number of revolutionary stations throughout the World and gives information on their mode of operation.

On the technical side there is some interesting discussion on the use of front-end tuners for RX equipment, together with details of some the reader can make. Other chapters cover medium wave working, improving a second-hand set, working South America and a listing of the major broadcast stations.

R.D.R.

## PHOTOCELL APPLICATIONS

Published by English Universities Press  
52 pages, 11½in × 8½in. Price £1.05

AS AN introduction to electronics, photocells of various types provide an excellent starting point as they are easy to understand, they have a multitude of applications and are relatively cheap.

Only a basic knowledge of electronic principles is assumed and practical points such as resistor colour code and circuit symbols are fully covered. The projects range in complexity from a simple exposure meter to a modulated light transmitter and receiver.

Through this book the reader can obtain not only a knowledge of photocells but also other electronic components such as transistors, and thus can discover some of the fascination of electronics.

S.R.L.

## IBA TECHNICAL REVIEW—DIGITAL TELEVISION

Published by the IBA  
64 pages, 9in × 7½in

IN THIS the third of the IBA's Technical Reviews an extremely interesting account of the IBA Engineering Section and its work on digital television is presented. The book includes descriptions of the recent work of the IBA in developing digital standards converters, among them the first digital intercontinental conversion equipment (DICE) now in operational service at Independent Television News.

This book is written by members of the IBA Engineering staff and provides a valuable insight into the design techniques and philosophy behind some interesting projects.

Copies of this book may be obtained on request from: IBA Engineering Information Service, 70 Brompton Road, London, SW3 1EY.

S.R.L.



# PE RONDO PART 4

## MECHANICAL ASSEMBLY & INTERWIRING

BY R. A. COLE

### FACIA

### SURROUND

### INTERWIRING & HARNESS

IN THE previous parts of the RONDO series we have discussed the construction of the main chassis member which forms a trough-like carrier for the power sections of the system. Now we come to a discussion of the general mechanical assembly and the wiring of the system.

#### GENERAL CONSTRUCTION

The facia of the RONDO system supports both the controls and the r.f. tuning unit, whilst the remainder of the boards are assembled in the chassis pan itself. Thus, as can be seen from Fig. 4.1 the facia consists of an aluminium framework supported on four columns which are held in the main chassis by screws.

The columns support two crossmembers (Fig. 4.1b) made from aluminium angle ( $\frac{1}{4}$ in  $\times$  1in) which in turn support two sections of aluminium extrusion made specially for the RONDO system and available from a number of kit suppliers. The two sections are separated by an inverted "U" section of brushed aluminium provided with ventilation louvres.

For those who wish to make their own facia this may be made up from sheet material bent up into the form at Fig. 4.1a, again supported on the columns and drilled so as to carry a simple aluminium facia in plain sheet. Drilling for this is identical to that for the pre-form material with the addition of master tone board mounting screw holes added.

The plain face area shown above the four input selector push-buttons on the left of the RONDO is allocated to the tuner section, yet to be described.

The final main part of the mechanical assembly is the "wrap-round" or surround which forms the sides of the RONDO. This is made from wood, veneered chipboard, or the like according to taste.

From Fig. 4.2 which shows the surround it will be seen that there are two alternative methods of fixing between the surround and the basic trough chassis. The first is to make use of the natural spring in the bent-up chassis by springing the two longer sides apart slightly such that when the surround is finally lowered over the facia to abut the two flanges on the trough, these are pushed in against the spring action. As the surround is lowered further they will then spring out to engage with the two grooves cut in the inner long surfaces of the surround.

If the constructor prefers, he may replace this method with one in which the surround is reduced in depth by the distance between the lower edge and the grooves and is supported on an extension bolted to the two trough flanges as shown in Fig. 4.2.

#### WIRING DETAILS


The P.E. RONDO quadraphonic system is quite complex and, if not carefully wired, will result in an untidy maze. It is therefore strongly recommended that a prefabricated wiring harness, or cableform, be made to cover the bulk of the inter-unit wiring.

This cableform is constructed by means of a simple jig illustrated in Fig. 4.3 and made from a suitable piece of wood into which a pattern of "pins" is fixed;  $1\frac{1}{2}$ in panel pins are ideal for this purpose. They are hammered into the appropriate points as shown and the heads are then clipped off and the sharp ends smoothed.


When assembling the cableform make certain that each wire or cable is inserted in the order given in Table 4.1, since otherwise both simple mechanical and electrical problems can arise.



# SURROUND & LOOM

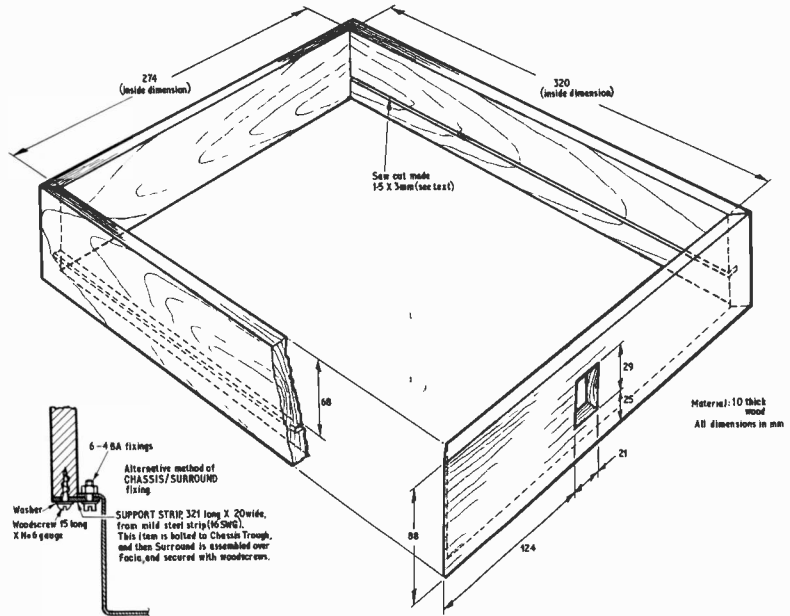

**Fig. 4.2. Construction of the wooden surround with details of the two methods of fixing the trough**

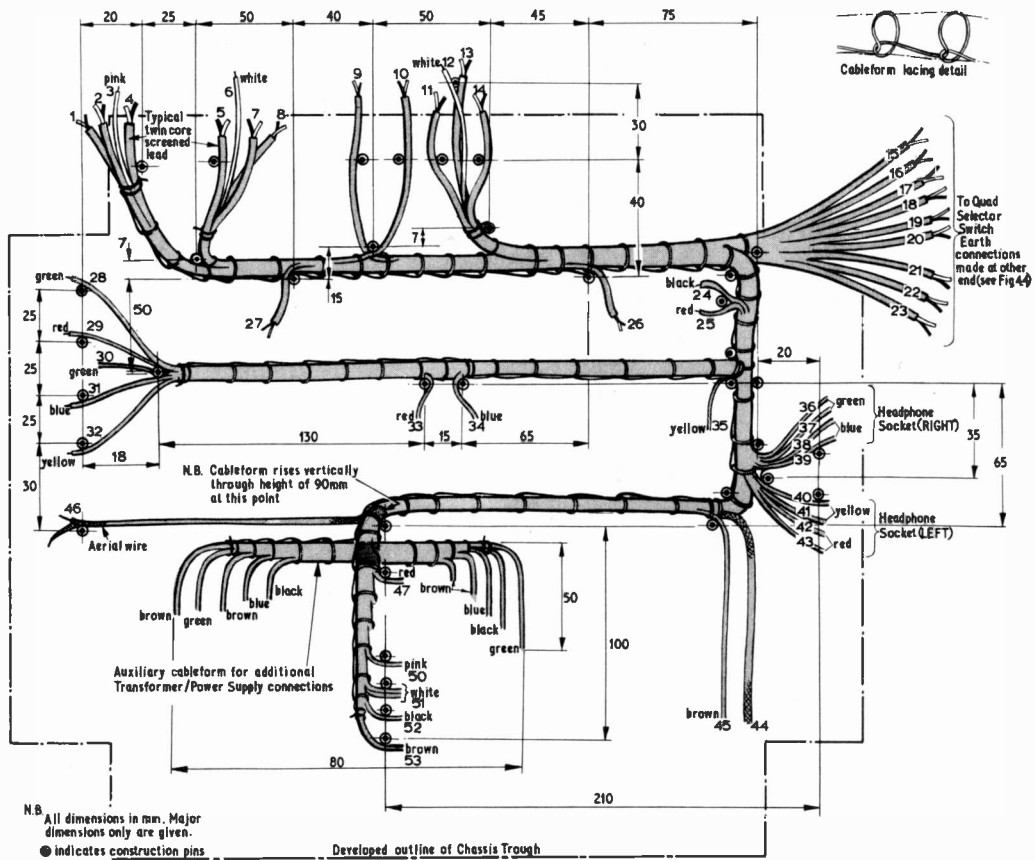

**Fig. 4.3. Details of the cableform wiring harness. Interwiring between the units is greatly simplified if a cableform system is constructed as shown here**

Each piece of wire is firmly secured by wrapping its start end round the first pin and then laying it along the route shown in Fig. 4.3 and the point-to-point wiring and assembly diagram of Fig. 4.4.

The intermediate pins along a route are used as guides and gentle tension is applied to each wire in order to produce a neat and tidy result. At the termination point the wire is again secured to the adjacent pin by wrapping. With the heavier wires it may be found necessary to knot the wire around the pin.

A "tail" some two to three inches long should be left at each end of each wire for later circuit connecting.

The cableform may now be "laced" up using lacing twine or, failing the availability of this, a waxed heavy thread or light nylon line. A simple form of lacing is shown in Fig. 4.3 from which it will be seen that this is merely a matter of tying the cableform into one cohesive unit by using a series of loops around the cables every  $\frac{3}{4}$ in or so.


After lacing, the cableform is gently eased from the pins and is now ready for positioning in the trough.

### MECHANICAL ASSEMBLY

The two power amplifiers, already assembled complete with heat sinks, are laid side by side, copper side upwards on the bench. The power rails and earth rails are connected and flying leads are soldered as shown in Fig. 4.6.

The next step is to fit all sockets, rubber feet and mains lead grommet to the chassis as shown in Fig. 4.4. The wiring harness is then laid in the bottom of the main chassis as shown.

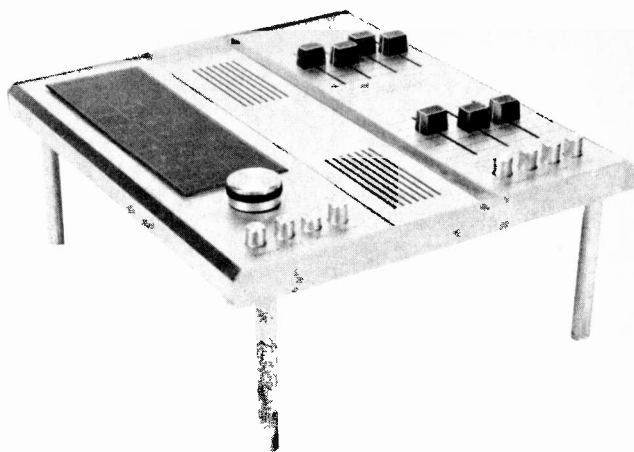Starting at the rear of the chassis carefully identify each wire and its connecting point. Cut the wire tails to length and carefully strip the ends, wrap round and then solder. Repeat this procedure until



all wires that are shown to be terminated are soldered.

The remaining wires and their terminations are associated with the tuner unit which is to be the subject of a separate article and they will be described in detail then.

The two power amplifier boards, now joined together, are placed component side upwards in the chassis. The two right-hand limbs of the wiring harness (as seen from the front of the chassis) should be under the boards and the left-hand limb along the edge of the heat sink.

Ensure that the yellow, blue, red and green wires, in the centre limb of the harness, protrude above the boards at the appropriate outlet points. Cut, strip, wrap and solder them. Similarly treat the red and black wires in the right-hand limb, soldering them to the positive and negative 15 V rails on the power amplifier board.

The two rails are duplicated on the rear power amplifier board and the two boards are joined with short lengths of red and black wire interconnecting the rails.

Table 4.1

Start	Finish	Signal	Cable Type												
1	15	CD4	} Twin screened												
2	16	"													
4	17	"													
5	18	SQ													
7	19	"													
8	20	"													
11	21	QS													
13	22	"													
14	23	"													
9	26	L <sub>A</sub> I/P		} 14/0-0076 Pink											
10	27	R <sub>A</sub> I/P			} White										
3	50	+24V Rail				} "									
6	51	+20V Rail					} Black								
12	51	- 15V "						} Red							
24	52	+15V Rail	} Yellow												
25	47	L <sub>F</sub> O/P							} "						
35	40	"								} Blue					
40	32	L <sub>B</sub> O/P									} "				
34	39	"										} Red			
39	31	R <sub>F</sub> O/P											} Green		
33	43	"												} "	
43	29	"													} Brown
30	36	R <sub>B</sub> O/P													
36	28	+18V Rail													
53	45	"													
46	44	Aerial													

### HEADPHONE SOCKETS

A group of four pairs of wires, each pair of one colour, namely yellow, blue, red and green, protrudes from the front of the harness in line with the headphone sockets. These wires are connected to the headphone sockets, as shown, ensuring that the leads from the power amplifiers go to the appropriate tags on the *right* side of the headphone sockets as viewed from the front of the chassis. If these connections are not correctly made the headphones will not function correctly.

The headphone sockets shown are of the normal three-wire type which can exhibit problems with the amplifiers set to high output levels. It is possible to either damage the headphones or the ear-drums if care is not taken when plugging the headset in.


It is therefore recommended that the constructor either takes great care under these circumstances or adopts the use of a new style of socket which has just come onto the market. The new socket interposes a load in series with the headphones in order to limit the output level and current to a safe value.


Using the new sockets, a suitable load resistor for most applications is 220Ω,  $\frac{1}{4}$ W.

# SYSTEM INTERWIRING

**Fig. 4.4. Main wiring diagram of the PE RONDO.**  
Wires are separated for clarity but should be grouped together as indicated in Fig. 4.3

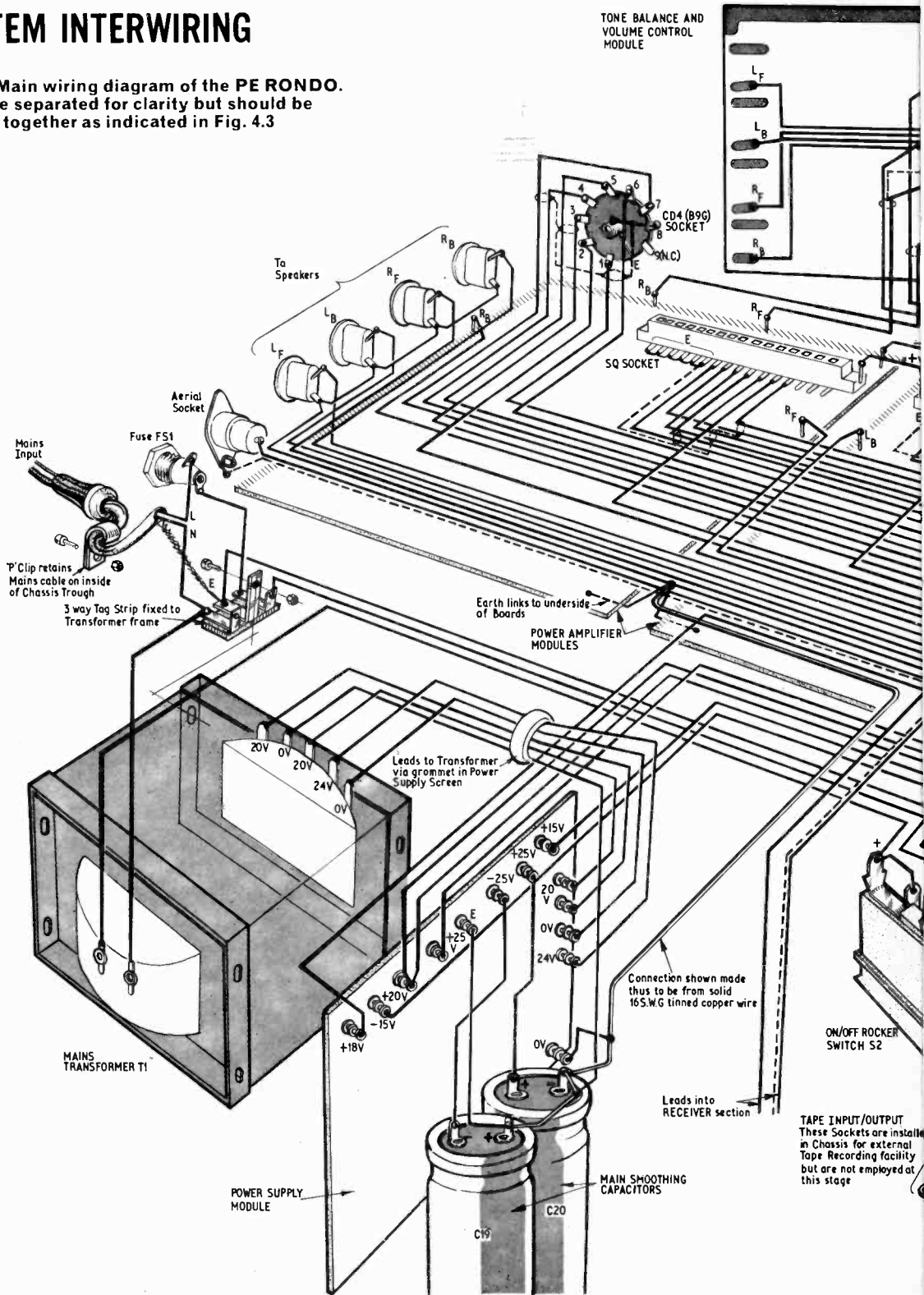TONE BALANCE AND  
VOLUME CONTROL  
MODULE



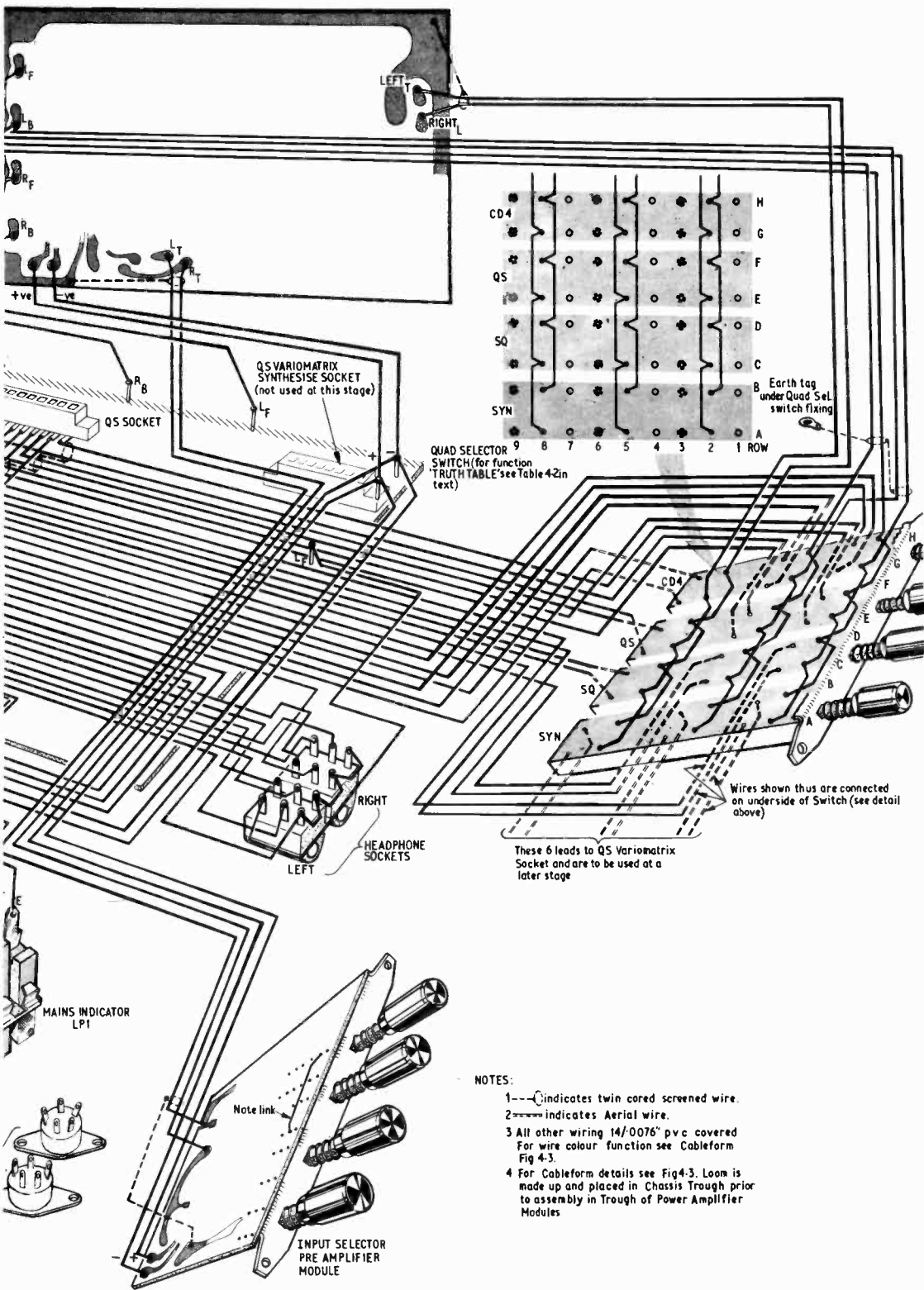

QUAD SELECTOR SWITCH (for function 'TRUTH TABLE' see Table 4-2 in text)

QS VARIOMATRIX SYNTHESISE SOCKET (not used at this stage)

Wires shown thus are connected on underside of Switch (see detail above)

These 6 leads to QS Variomatrix Socket and are to be used at a later stage

NOTES:

- 1 --- indicates twin cored screened wire.
- 2 - - - indicates Aerial wire.
- 3 All other wiring 14/0076" pvc covered For wire colour function see Cableform Fig 4-3.
- 4 For Cableform details see Fig 4-3. Loom is made up and placed in Chassis Trough prior to assembly in Trough of Power Amplifier Modules

## POWER SUPPLY SUB-ASSEMBLY

Returning now to the power supply sub-assembly; fit the complete sub-assembly to the chassis with four  $\frac{1}{2}$ in round-head 4BA screws, plain washers, lock washers and nuts. Similarly secure the power amplifiers to the chassis by means of the heat sinks. Fit the main smoothing capacitors to the chassis by means of capacitor clips.

The power supply includes transformer, power board and main smoothing capacitors and is shielded by means of two steel screens. The smaller of these screens, shown in Fig. 3.6, acts as a supporting baffle for the power supply board.

It is first fastened to one end of the mains transformer by four  $\frac{1}{2}$ in round-head 4BA screws, each fitted with one plain washer, one lock washer and a nut. The board is then secured to this baffle by three  $\frac{1}{2}$ in round-head 6BA screws, washers and nuts and, in each case, a  $\frac{1}{2}$ in spacer is interposed between the board and the baffle.

The larger of the two steel screens is now fitted to the chassis.

Refer to Fig. 4.4 and connect the leads to the power supply coming from the harness. Connect the mains lead and switch/pilot light as shown in Fig. 4.4.

Prepare the pre-amplifier board with flying leads

for connection to the main chassis components. Similarly connect the master volume/tone/balance control board. Reference to Fig. 4.4 will give the necessary guidance.

The four-way, six-change-over, pushbutton bank is now pre-wired in accordance with Fig. 4.4 and Table 4.2.


The nine pairs of screened leads protruding from the right-hand front of the wiring harness are carefully stripped and identified. Connection of these leads to the switch bank is carried out with reference to the figure.

Please note that no wiring is provided for the SYNTHESISE position on the pushbutton bank. Details of this facility will be given in a later article together with the wiring of the tape sockets.

Fuses are now inserted into the holders on the power amplifier boards and into the mains fuse holder. See components list for ratings.
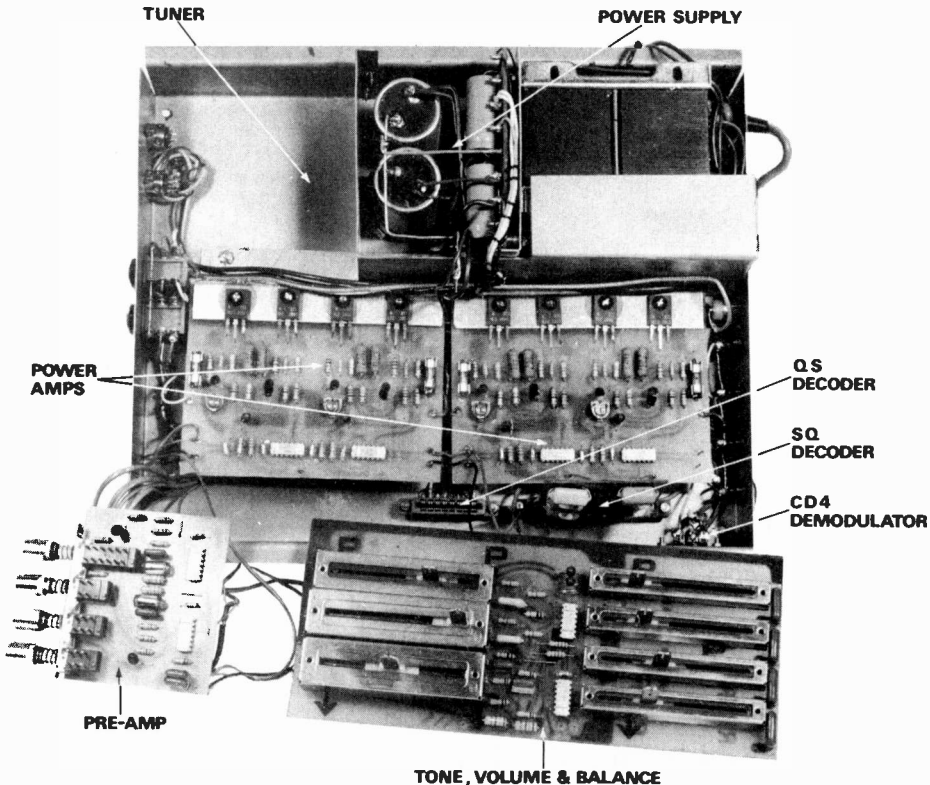
## AMPLIFIER CHECKING

Before commencing, carefully check the accuracy and completeness of the wiring. Extra time spent here can save expensive components coming to undue harm. Ideally, a parallel check between the unit, layout drawings and theoretical circuit should be performed.





Connect the speaker outlets to dummy  $8\Omega$  loads. The dummy load may be made up from 15,  $120\Omega$   $\frac{1}{2}W$  carbon resistors connected in parallel. Only one load need be made as each amplifier is tested individually.

As the initial output power will be fairly low on setting up, 2W resistors are adequate. If a cheap  $8\Omega$  loudspeaker is available to monitor each channel as it is set up, so much the better. Do not, however, risk a good loudspeaker at this stage.

Turn the presets on all power amplifier channels to maximum, that is clockwise. Reduce all level and balance controls on the master board to minimum and set the tone controls mid-way.

## COMPONENTS . . .

### Resistors

Headphone load resistors  $220\Omega$   $\frac{1}{2}W$  (4 off)  
Dummy load for testing  $120\Omega$   $\frac{1}{2}W$  (15 off)

### Plugs and Sockets

Speaker sockets 2 pin DIN (4 off)  
Tape in/out sockets 5 pin  $180^\circ$  DIN (2 off)  
Aerial socket Coaxial recessed  
Headphone sockets Switched stereo headphone sockets (2 off)  
CD4 connector B9G valve base  
SQ edge connector 16 way 0.15in pitch edge connector  
QS Variomatrix  
Synthesise socket 8 way 0.15in pitch edge connector  
QS edge connector  
Fuse holder 8 way edge connector  
20mm chassis type

### Switches

Push button bank, 4 bank, 17.5mm spacing, with each bank  
6-changeover per bank

### Wiring


32ft 14/0-0076in stranded single p.v.c. (yellow 3ft, blue 3ft, red 5ft, green 5ft, white 5ft, pink 3ft, brown 6ft, black 2ft)  
20ft twin screened lightweight audio wire  
2ft single screened light co-ax.  
8ft lacing cord  
Mains lead 3-core to suit  
2ft tinned copper 16 s.w.g. wire

### Materials

Aluminium extrusion for facia (available from Sonax Electronics) or plain 18 gauge sheet aluminium if alternative construction method is used. Aluminium "L" or "U" form and  $\frac{3}{8}$ in rod for support members for facia. Boxform surround (from Sonax) or wood to make
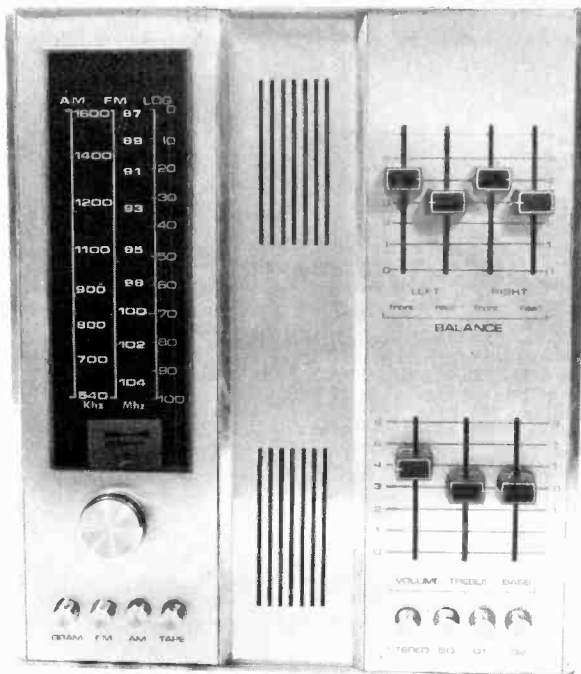
### Miscellaneous

3-way terminal tag strip  
Rubber feet (4 off)  
Grommet  $\frac{1}{2}$ in  $\times$   $\frac{1}{4}$ in, sleeved grommet for mains lead  
 $\frac{1}{2}$ in 4BA roundhead screws (17 off)  
4BA nuts, plain washers and lock washers (17 off)  
 $\frac{3}{8}$ in 6BA roundhead bolts (16 off)  
 $\frac{1}{2}$ in 6BA roundhead bolts (6 off)  
 $\frac{3}{8}$ in 6BA roundhead bolts (3 off)  
6BA nuts, plain and lock washers (25 off)



Connect a d.c. millivoltmeter across resistors R29 and R30 as shown in Fig. 4.6 on one power stage. The sum of these two resistors is approximately  $1\Omega$ . Switch on the complete system.

At this stage a variable input transformer (Variac) to adjust the mains supply slowly is very useful, but not essential.

The millivoltmeter should now read from 2 to 10mV d.c.

If the reading is more than 50mV switch off and check wiring again. If all is well, slowly rotate the preset VR8 anticlockwise until a reading of approximately 20mV is obtained. This reading corresponds to approximately 20mA quiescent current.

Disconnect the meter and repeat the procedure on all the remaining power amplifiers in turn.

The main amplifiers are now set for optimum quiescent current conditions and should not require re-setting at all.

## FINAL MECHANICAL ASSEMBLY

The master volume and tone board, preamplifier board and quadraphonic selector switch are all assembled on the facia as shown in Fig. 4.1. It must be remembered that the wiring to these boards should be kept as short as possible to avoid interference and hum. However, they must be sufficiently long to allow both initial assembly and possible later disassembly.

The facia may now be attached to the trough by its pillars and 4BA screws inserted upwards from beneath the trough in the holes provided.

The surround may now be placed over the facia and dropped down to engage with the lips on the trough for either of the two fixing methods described earlier to be effected.

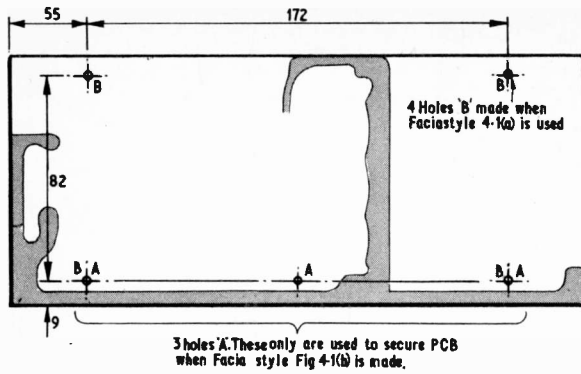


Fig. 4.5. Drilling details of the Tone/Master volume board to suit the facia of Fig. 4.4a.

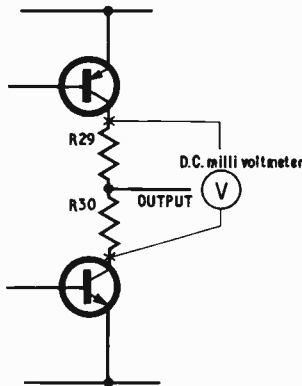


Fig. 4.6. Location of the test points for measurement of the quiescent current in the power amplifiers

Where "spring" locating method is used to retain the surround the exact fit is adjusted as required by applying a slight set to the sprung chassis sides. Be careful not to overdo the tension as this will make subsequent removal of the surround difficult.

Ideally the springing should just cause the flanges to "bite" the surround as it is lowered into position and adjustment can be made in small steps until correct setting is achieved.

To remove the surround using the same method it is simply a matter of placing the finger tips against the long sides from below and pressing lightly inwards until the lips of the flanges release from the grooves. The approach from below is important as working from above is rather difficult. Thus it is simplest to place the unit on a box or other object first so that the hands can be positioned lower than the bottom of the unit.

After releasing from the grooves a gentle upward pressure will slide the surround free for removal.

## EARTHING

The use of a wiring loom reduces the problems encountered with hum and stray pickup and it is for this reason that we have described a loom here. Further steps can be taken to minimise these unwanted signals.

Firstly, ensure that both screens are electrically connected to the main chassis which must be itself

Table 4.1 WIRING OF QUAD SELECTOR SWITCH

TOP SIDE WIRING			
Join A8, C8, E8, G8 =	R <sub>T</sub> input		
Join B8, D8, F8, H8 =	L <sub>T</sub> input		
Join A5, C5, E5, G5 =	L <sub>F</sub>		
Join B5, D5, F5, H5 =	L <sub>B</sub>		
Join A2, C2, E2, G2 =	R <sub>F</sub>		
Join B2, D2, F2, H2 =	R <sub>B</sub>		
} To Fader Inputs			
UNDERSIDE WIRING			
Synthesise	R <sub>F</sub> =3A	L <sub>F</sub> =6A	R <sub>T</sub> =9A
	R <sub>B</sub> =3B	L <sub>B</sub> =6B	L <sub>T</sub> =9B
SQ	R <sub>F</sub> =3C	L <sub>F</sub> =6C	R <sub>T</sub> =9C
	R <sub>B</sub> =3D	L <sub>B</sub> =6D	L <sub>T</sub> =9D
QS	R <sub>F</sub> =3E	L <sub>F</sub> =6E	R <sub>T</sub> =9E
	R <sub>B</sub> =3F	L <sub>B</sub> =6F	L <sub>T</sub> =9F
CD4	R <sub>F</sub> =3G	L <sub>F</sub> =6G	R <sub>T</sub> =9G
	R <sub>B</sub> =3H	L <sub>B</sub> =6H	L <sub>T</sub> =9H
Rows 1, 4 and 7 have no connections			

connected to mains earth. Thus if there is any doubt about good conduction between the screens and chassis it is advisable to either insert a wire link or clean the adjoining faces thoroughly before assembly.

Secondly, there is a very useful technique which can be applied to the RONDO screened leads. Simply make certain that all screens are earthed at the end nearest to the signal source for that particular length of lead. With a system as complex as the RONDO this does make for complexity in deciding which end must be earthed but the results bear out the effort. The constructor may find Fig. 1.15 in the September issue of PRACTICAL ELECTRONICS useful in this context.

If hum is experienced and the circuitry in the area of the decoders is suspected it is advisable to remove the earth connections from both ends of the screened leads between the boards and the selector switch and replace each connection in turn until the hum loop is isolated. This may involve connecting from either end of a cable.

## NOTE.

The output transistors in the power amplifiers should be MJE 3055K and MJE 2955K.

## Next Month: Loudspeaker enclosure design and construction



## RADIO STARS

In the early days of radio astronomy astronomers were constantly pointing out that there were radio sources but no known radio stars. In consequence the actual discovery on rare occasions of a radio star made headlines. Now, however, particularly over the last few months, quite a number have been added to the list. The chance discoveries have now been supplemented by those discovered as a result of a definite programme of search.

Theory suggested that an early type of star which shows emission lines and an excess of infra-red would be a candidate. It is maintained that the infra-red occurs in the surrounding dust and gas. This was the place to look for radio emission.

It is quite a neat piece of work by a team from the Algonquin Radio Observatory in Canada since a comparatively small telescope was used. The telescope operates at a wavelength of 2.8 centimetres and the dish is a mere 46 metres in diameter. Drs Feldman, Marsh and Purton have managed to secure this scoop with apparent ease.

Now, no doubt, the larger telescopes will turn their attention to the matter. Since the astronomers will now know what to look for and where to look, it is to be expected that more will be found and new data will be obtained. It could mean that a new and more successful model of infra-red stars will emerge.

## ANOTHER INTERPRETATION OF THE SIBERIAN METEORITE

The spectacular terrestrial catastrophe that took place in Siberia in 1908, has led to much speculation. No remnants of the meteorite have ever been found so many quite bizarre explanations have been forthcoming, from a crashed space vehicle to a lump of anti-matter.

The force that produced the blast is said to have had an energy output of 0.2 to 20 megatons. The physical effect of this is observable even after many years. There is no crater as such for it is a swampy area.

Dr Stephen Hawking has suggested, in the last year or so, that if black holes do exist they would be of all sizes. Many of these could be quite tiny and may well have been formed after a "big bang" start to the universe.

Since in their travels these small units would suck into themselves matter through which they passed they may well be at the centre of stars and even galaxies. Perhaps here might be found a solution to the problem of gravitational waves.

From the University of Texas comes a suggestion by Dr A. A. Jackson and Dr M. Ryan. They put



forward the idea that one of the small black holes moving at high speed and passing through the atmosphere would produce temperatures of the order of  $10^5$  degrees K.

This would cause ultraviolet radiation and a plasma column would be formed. The black hole would pass right through the Earth because of its small size but would have the mass of an asteroid. This energy would carry it onwards into space.

The plasma column would be dissipated in the surrounding area of entry. This plasma column would be of a deep blue colour. Is it perhaps significant that the many eyewitnesses described the appearance of the sighting as a "bright blue tube".

## EXTRA VEHICULAR ACTIVITY

A new method of control for astronauts is under development by the RCA Company. The astronaut's voice is used to control movements.

This is a truly significant move. It means that the actual movements required can be initiated by voice commands only. There are 12 basic commands that operate the manoeuvring and propulsion system. Thus right, left, up, down, etc. can be brought to any situation. A dream come true for many applications. It is surely not far from this point to the control of vehicles in terrestrial situations.

Other activities planned for the future concern two satellites to be launched in 1975. Some of the instruments to be carried are for the determination of the immediate Earth environment. More data will be made available from the higher levels of the atmosphere particularly the thermosphere. The sort of instrumentation that is required for this work includes an electron tem-

perature probe as well as the usual photometers and spectrometers.

The data to be gathered will be neutral particle and ion compositions, ion and the natural gas temperature, information about the air-glow and the detection of thermal electrons and photoelectrons.

The satellite will weigh about 1,300 pounds and will carry a momentum wheel for stabilisation.

## SKYLAB PRELIMINARY RESULTS

So much data has been gathered on the second *Skylab* period of observation, that it will take some years to evaluate it all.

Perhaps the most consistent of the findings relate to the Sun. The better observation of the structure of the atmosphere of the Sun and in particular the great hole that has been found in the corona may unlock secrets far away from the Sun.

Recently Dr C. H. Barrow of the University of the West Indies has been trying a new correlation of micropulsations from the Sun and those observed in the radiations from Jupiter.

It could well be that the information returned from the Jupiter probe, which should be close to the planet on December 10th, will help to establish a positive result. The micropulsations have been known for some years but because of lack of data from the Sun the matter was only spasmodically reviewed.

The hypothesis involved is an important one for, though there have been a number of models evolved, all lack the sort of confirmation required to establish the facts.

## COMET KOHOUTEK

*Skylab* will have a special mission with respect to the comet *Kohoutek*. The next mission (*Skylab 4*) is the last in the projected series and begins on November 9th.

Seven of the existing instruments will be brought to bear on the comet and the astronauts will have with them a new far-ultraviolet camera. It should be possible to photograph the neutral hydrogen cloud which is estimated to surround the comet and extend to more than six million miles.

Initially the plans are for the *Skylab* mission to be completed by January 4th. It would be a pity if this could not be extended to January 14th to allow further observation. Such a unique opportunity to study the period immediately after the perihelion passage may never come again.

The best time to view the comet for Earth-based observers is at about 12.00 to 14.00 hrs, right ascension, in the morning sky near the area of the bright star *Spica*. This will be around December 4th.

# PE Sound Synthesiser 11

## KEYBOARD

By G.D. SHAW



THE article this month deals with the remainder of the electronics sited within the keyboard unit and details the divider system, the analogue memory or hold circuits, modulation amplifiers, envelope shaper/v.c.a.s and mixer. The overall system has been extensively redesigned to take maximum advantage of the greater versatility of the logarithmic v.c.o.s and with the aim of improving the live performance capability of the instrument.

### BLOCK SCHEMATIC

A block schematic arrangement of the keyboard unit is shown in Fig. 11.1 and the unit has been designed to accommodate a four-octave Kimber-Allen keyboard. The specified keyboard may be obtained through the Electronic Organ Constructors Society at 4 Lees Barn Road, Radcliffe-on-Trent, Nottingham NG12 2DS. The E.O.C.S are also able to supply the contact assemblies and mounting strips. The type of contact assembly required is the G.B.-2 paired contact unit, also by Kimber-Allen.

Although a four-octave keyboard is specified it should be made clear that smaller—or larger—units may be employed with no changes to the circuitry other than the adjustment to the number of divider resistors employed. With respect to the use of smaller keyboards, the E.O.C.S. have informed the author that they have a limited number of two-octave organ keyboards by Herrburger Brooks.

These are full sized timber keys faced with plastic and mounted on a hardwood frame. The keys themselves are in reverse colours with black naturals and white sharps, and although they will require to be sprung by the constructor, the additional work required is reflected in the attractive pricing of £5 per keyboard.

Reverting again to Fig. 11.1 it will be seen that the keying system is divided into two channels each channel having its own electronic assemblies and signal path. Signals from both channels join together in the final circuit, a simple virtual-earth mixer. The purpose of this arrangement is to allow a rhythm accompaniment and melody line to be programmed at the same time, channel 1 programmed by the upper 31 keys and channel 2 by the remainder.

The tuning arrangement allows the transition between the two channels to be musically consecutive. Spread apart by one or more octaves or the channels juxtaposed in terms of frequency with the 31 note channel providing a bass line to a treble channel 2. Since the combined effect of the tuning controls is continuously variable there are a number of intermediate possibilities such as channel 2 dupli-

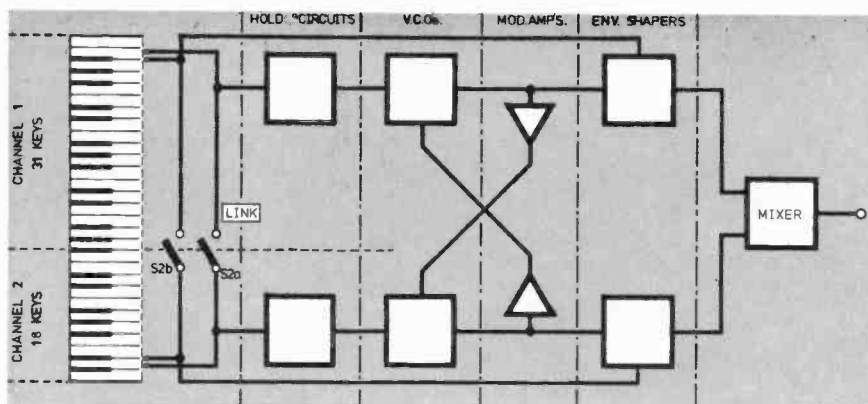


Fig. 11.1. Block schematic of keyboard unit

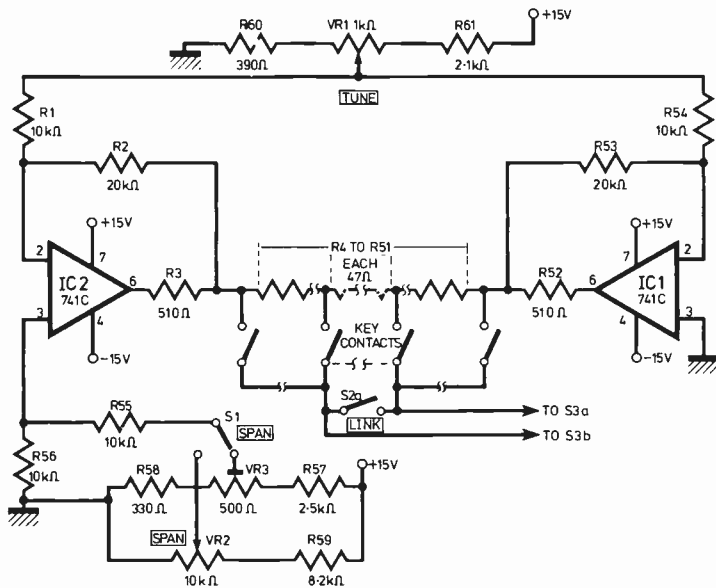


Fig. 11.2. Keyboard divider network

cating sections of channel 1 or, in more bizarre terms, both channels programmed in different keys.

The programming voltage from the keyboard is led to a memory circuit which holds the last voltage entered until such time as a new voltage is programmed or until the hold circuits are grounded. The output voltage from the hold circuit is used to program its respective v.c.o. to the desired frequency which is then amplitude modulated in the envelope shaper/v.c.a. Triggering of the envelope shaper takes place each time a key is depressed in the appropriate channel and each envelope shaper is provided with separate attack and decay controls together with an additional percussive attack facility which may be switched in as desired.

Frequency modulation between oscillators may be achieved by means of the modulation amplifiers which have sufficient gain to swing the frequency of the v.c.o.s through the entire audio spectrum. Finally, a link switch is provided to enable both channels of the system to be programmed in parallel.

## THE DIVIDER NETWORK

Fig. 11.2 shows the theoretical circuit of the keyboard divider network in which resistors R4-R51 inclusive form the actual divider which is "floated" between the outputs of two operational amplifiers. The output of IC1 is coupled to the high frequency end of the divider and IC2 to the low frequency end. R60, VR1 and R61 together form an adjustable divider which is coupled to the inverting inputs of both i.c.s. Thus, by means of VR1, the main tuning control, the voltage on output of

the i.c.s may be swung through a range of rather more than 8 volts.

Since this latter effect will be equal at both ends of the keyboard it is necessary to apply an offset to one of the i.c.s in order that a voltage differential will exist across the divider chain. The offset is applied to the non-inverting input of IC2 through the medium of either one of two divider chains.

## SPAN FACILITY

R57, VR3, R58 provide what has been termed the fixed span facility with the preset VR3 having sufficient swing to enable the V/Octave range to be adjusted between about 400mV/octave to rather more than 1V/octave. R59, VR2 provide the variable span facility which is adjustable over a range of about 8.0V. The setting of VR3 is normally adjusted so that one octave width on the keyboard spans precisely one frequency-octave. VR2 on the other hand enables the frequency spread of one keyboard-octave to be varied between a fraction of a semitone (micro-tones) to several tens of semitones (macro-tones). The actual effect, in terms of frequency range, resulting from the swing on both VR2 and VR3 will depend very much on the requirements demanded by the v.c.o. as a result of the "Law Adjust" setting.

The exact value of the divider resistors R4 to R51 is not too critical except that they should be of sufficiently low a value so that the combined loading of the v.c.o.s does not cause a measurable change in the voltage at any point on the divider. Values between 10 and 60 ohms should meet all the necessary criteria. For best results, however, it is important that, whatever the nominal value of divider resistor chosen, the individual resistors are

## COMPONENTS . . .

### DIVIDER

#### Resistors

- R1 10kΩ
- R2 20kΩ
- R3 510Ω
- R4-R51 47Ω (48 off)
- R52 510Ω
- R53 20kΩ
- R54-R56 10kΩ (3 off)
- R57 2.5kΩ
- R58 330Ω
- R59 8.2kΩ
- R60 390Ω
- R61 2.1kΩ

All 2% metal oxide

#### Integrated circuits

- IC1-IC2 741C (2 off)

#### Potentiometers

- VR1 1kΩ semi-precision wire-wound
- VR2 10kΩ midget moulded linear carbon
- VR3 500Ω cermet

#### Switches

- S1 s.p.c.o. miniature toggle
- S2 d.p.c.o. miniature toggle

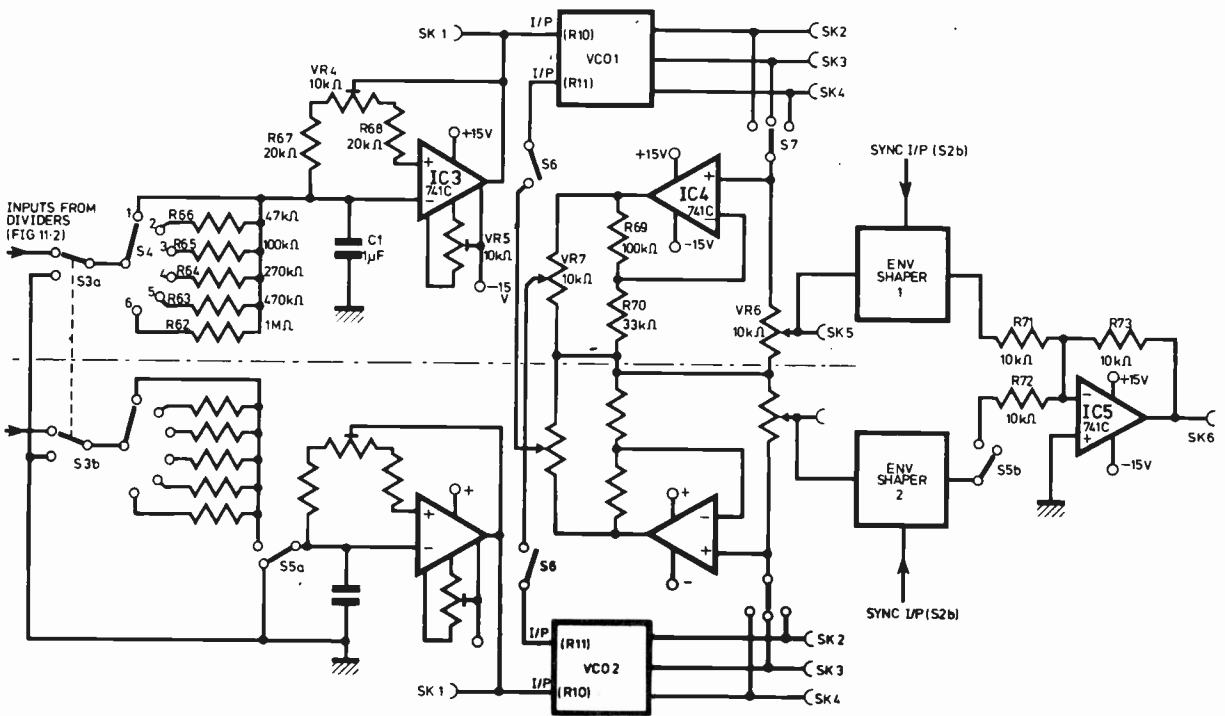


Fig. 11.3. Circuit of hold, modulation amplifier and mixer for both channels with v.c.o. interconnections. The component values for the mirrored hold and modulation amplifier circuits are identical

## COMPONENTS . . .

### HOLD CIRCUIT (2 off)

#### Resistors

R62 1M $\Omega$  5% carbon  
 R63 470k $\Omega$  5% carbon  
 R64 270k $\Omega$  5% carbon  
 R65 100k $\Omega$  5% carbon  
 R66 47k $\Omega$  5% carbon  
 R67 20k $\Omega$  2% metal oxide  
 R68 20k $\Omega$  2% metal oxide

#### Potentiometers

VR4-VR6 10k $\Omega$  15 turn cermet

#### Capacitor

C1 1 $\mu$ F 63V polyester

#### Integrated Circuits

IC3-IC4 741C

#### Switches

S3 2-pole 6-way  
 S4 d.p.c.o. toggle  
 S5 d.p.c.o. toggle

### MODULATION AMPLIFIER (2 off)

#### Resistors

R69 100k $\Omega$   
 R70 33k $\Omega$

#### Integrated Circuit

IC4 741C

#### Potentiometer

VR7 10k $\Omega$  midget moulded linear carbon

#### Switches

S6 s.p.c.o. miniature toggle  
 S7 2-pole 3-way

### MIXER

#### Resistors

R71-R73 10k $\Omega$  (3 off) 5% metal oxide

#### Integrated Circuit

IC5 741C

as closely matched to the nominal value as possible. It is particularly important that the ohmic value of any 12 consecutive resistors in the divider should be a close match with any other selection of 12 consecutive resistors.

The junctions between individual resistors in the divider are hard wired to the moving contact of their respective contact assemblies mounted below the keyboard, the fixed contacts being joined into two bus-bar units which can be joined by means of a link switch. A similar arrangement is employed for the second pair of contacts which serve to provide the sync pulse necessary for the envelope shapers.

## ANALOGUE MEMORY

The divider voltage resulting from the depression of any particular key is routed into the analogue memory circuits via S3 and S4 as shown in Fig. 11.3. The purpose of the hold circuit is to retain the last programmed keyboard voltage for sufficient time to enable the desired tone processing to be completed. For example, with S4 in position 1, the depression of a key is sufficient to cause C1 to become charged to the value associated with that particular key. At the same time a sync-pulse is routed to the envelope shaper which, if it is set to provide a rapid attack, will turn on the v.c.a. and allow the oscillator tone to be heard. If the envelope shaper is also set to provide a long decay, the oscillator tone will immediately begin to die away.

In operation the hold circuit utilises the common-mode rejection of the 741 operational amplifier to provide a very high input impedance. Positive and negative feedback are applied by means of R67 and R68 with VR4 serving to provide a balance between the respective levels of feedback to the inverting and non-inverting inputs of the amplifier. C1 is the reservoir capacitor and is coupled directly to the non-inverting input.

The input impedance of the circuit is given by the paralleled value of R67 + part of VR4, and R68 + part of VR4 times the open loop gain of the amplifier. Thus depending on component tolerances the input impedance can be anywhere within the range 250 to 2,500 megohms and since a 1.0 $\mu$ F capacitor is specified the leakage time constant of the network will similarly vary between 250 and 2,500 seconds.

## PORTAMENTO

When keyboard voltages are routed direct to C1 in the hold circuit the change in level of the charge on C1 is virtually instantaneous. However, if a resistance is interposed between the keyboard and C1 the rate of change of charge is inversely proportional to the value of the resistor. This provides a very convenient means of adding a portamento facility and R62-R66 are included for this purpose, being switched in as required by S4.

Portamento is the name given to the effect when the transition between two successive notes in a musical piece is accomplished in a gliding manner encompassing all the intermediate frequencies.

The nature of the hold circuit requires that the setting-up procedure be followed with great care

since any output offset voltage present will inevitably cause the holding ability of the circuit to wander. With VR4 in its electrical mid position, and with the wiper grounded, a 10 megohm resistor is connected between the output and inverting input of the amplifier. With power on, VR5 is then adjusted so that the output is precisely zero when observed on the most sensitive setting of the oscilloscope. When satisfied that the initial setting up has been correctly accomplished the circuit connections may be made as generally shown in Fig. 11.3 but omitting the connections to the v.c.o. and portamento resistors. With power on again, and observing the output of IC3 on the oscilloscope, apply about -6V transiently to the junction of R67 and C1. Careful adjustment of VR4 will result in virtually negligible drift and, in the prototype, it was found that a drift of 6mV/20 minutes was quite easily attainable.

The -6V charge on C1 during the setting-up procedure is also quite an important value since it will be found that the circuit will have a much greater degree of drift if the applied voltage is significantly higher or lower than this value. For this reason S5 is provided to ground the input of the hold circuit during switch-on or when the keyboard is "idling" for any length of time thus ensuring that the v.c.o. is not over or under driven.

The output of the hold circuit is routed directly to the R10 input of the v.c.o. the three output waveforms of which are, in turn, routed to a selector switch, S7.

## MODULATION AMPLIFIERS

The wiper of S7 is coupled to the v.c.o. level control VR6 and also directly to the non-inverting input of what has been termed the modulation amplifier. The output of the modulation amplifier driven by VCO1 is then routed to the R11 input of VCO2 through S6, a similar arrangement existing between VCO2 and the R11 input of VCO1.

The net result of this arrangement is that each oscillator can frequency modulate the other either separately or at the same time. Although simple in concept this system is capable of generating waveforms having very complex harmonic structures and is thus able to produce an enormously wide range of sounds and effects.

In the modulation amplifiers R69 and R70 set the gain at about 4.5 and VR7 provides a modulation depth control. S5a/b provide a means of turning VCO2 off in the sense that its input and output are isolated and its frequency controllable either by its own manual frequency control or by its associated modulation amplifier or both. The main purpose of this arrangement is to allow VCO2 to provide a vibrato modulation to VCO1.

## ENVELOPE SHAPERS

From the wiper of VR6 the v.c.o. signal is routed into a v.c.a. based on the MFC6040 which is, in turn, controlled by an envelope shaper triggered by depression of any of the keys on the keyboard. The working of the circuit shown in Fig. 11.4 is as follows.

IC1-TR1 represent a current amplifier/follower with overall feedback. The output at the emitter normally is +4.5V under quiescent conditions thus

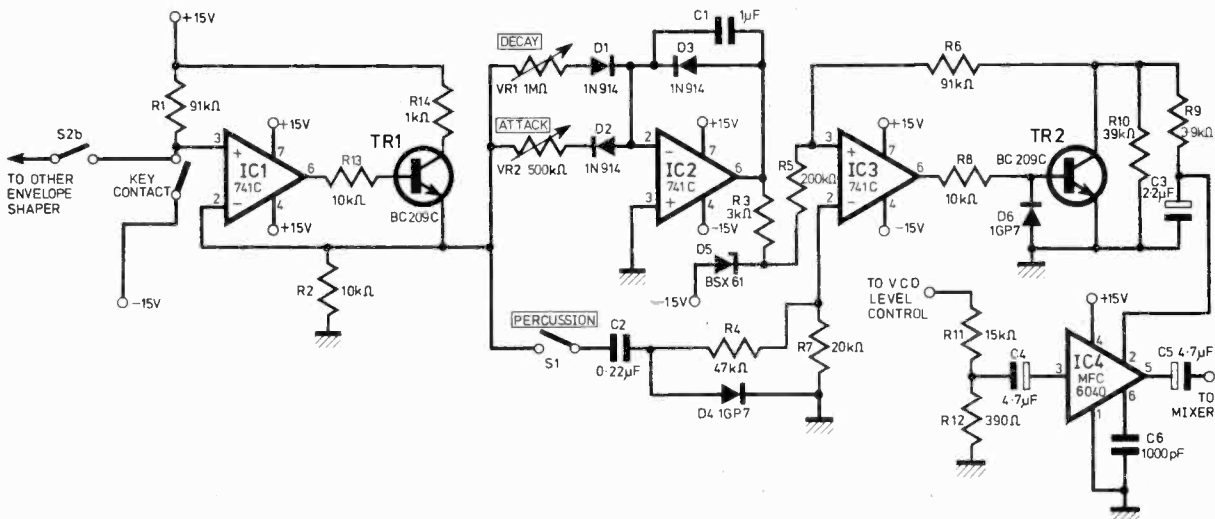


Fig. 11.4. Circuit of keyboard envelope shaper and voltage controlled amplifier

## COMPONENTS . . .

### ENVELOPE SHAPER (2 off)

#### Resistors

R1 91k $\Omega$	R8 10k $\Omega$
R2 10k $\Omega$	R9 3.9k $\Omega$
R3 3k $\Omega$	R10 39k $\Omega$
R4 47k $\Omega$	R11 15k $\Omega$
R5 200k $\Omega$	R12 390 $\Omega$
R6 91k $\Omega$	R13 10k $\Omega$
R7 20k $\Omega$	R14 1k $\Omega$

All 5%  $\frac{1}{2}$ W carbon

#### Transistors

TR1-TR2 BC209C (2 off)

#### Integrated Circuits

IC1-IC3 741C (3 off)  
IC4 MFC6040

#### Diodes

D1-D3 1N914 (3 off)  
D4 1GP7  
D5 BZX61 V Zener  
D6 1GP7

#### Capacitors

C1 1 $\mu$ F polyester  
C2 0.22 $\mu$ F polyester  
C3 2.2 $\mu$ F 35V tantalum  
C4 4.7 $\mu$ F 35V tantalum  
C5 4.7 $\mu$ F 35V tantalum  
C6 1,000pF polystyrene

#### Miscellaneous

S5 d.p.c.o. toggle, S7-4 pole 3 way rotary (2 required), VR6-10k $\Omega$  midget moulded carbon (2 off), 2mm miniature sockets (12 off), 1-4 octave keyboard, G.B-2 pair contacts (49 off) (see text), contact locating strip.

driving IC1 hard negative, or to  $-12.5$ V as determined by the divider R3-R5. With a negative input signal to the non-inverting input of IC2 the output of this device is also negative and TR1 is turned off. With TR2 off the control input of the MFC6040 rises to +6V and thus attenuates the audio input signal by about 77dB.

The application of a negative trigger pulse to the input of IC1 causes TR1 to turn off and the output at R2 to go to  $-15$ V. C1 thus discharges via D2/VR2 and the output of IC2 rises from  $-12.5$ V to about  $-4$ V. Under these conditions the non-inverting input of IC3 becomes positively biased, its output goes positive turning on TR2 which thus effectively short circuits R10 and causes the control voltage to IC4 to fall to about +4.3V. When the trigger pulse is removed C1 charges to a level again via D1/VR1 and the original situation is positive restored.

A separate percussive attack can be obtained by differentiating the trigger pulse to the envelope shaper by means of C2. The negative differentiated trigger pulse is applied to the inverting input of IC3 with the effect previously described except that in this case the magnitude of the pulse causes the v.c.a. control voltage to fall to +3.7V corresponding to an audio signal amplification of about 12dB. The percussive attack may be used on its own by advancing the trapezoid attack control to the slowest rate and playing the keys in a staccato manner. Alternatively the percussive attack may be mixed with the normal trapezoid control waveform or it may be switched out altogether by means of S1.

The audio signal outputs of the envelope shapers are led to a simple unity gain, virtual earth mixer shown in Fig. 11.3. The level of signal from each channel is controlled directly from VR6 on each of the oscillators.

**Next month: construction of the keyboard housing, wiring and tuning instructions. Details will also be given of a small p.s.u. which will enable the keyboard unit to be operated independently of the main synthesiser.**



# Strictly

by K. Lenton-Smith


**S**TUDENTS of the Hammond organ can usually detect aurally which models use tone wheels and which use integrated circuits. The "Concorde", introduced over a year ago, was the first Hammond drawbar organ not to use tone wheels. Using L.S.I. techniques it is now possible to synthesise the unique sounds produced by these electromagnetic devices.

Another novel feature of this organ is the multiple derivative divider which divides down the 12 top notes to the sub-octave frequencies giving locked tuning.

Both of these features are also found in the "Regent" cinema type organ which was released recently from the same stable. An adjunct to both instruments is the Automatic Rhythm 3 unit which is unusual in that the waltz may be selected with any other pattern for a rhythm variation (such as waltz/cha-cha!).
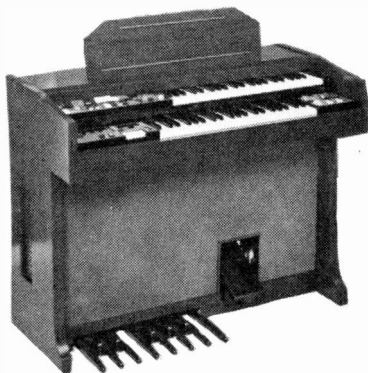
## NOTHING NEW

There seems to be nothing radically new in the manufacture of electronic instruments at present. The various makers appear to be using integrated circuits wherever possible, having relegated the transistor to "slave" duty.



The Lowrey Venus Stereo with a.o.c. and a Genie supplying rhythm patterns

Though R/C oscillators are usually considered to be less stable than L/C oscillators, manufacturers are now using carefully designed R/C master oscillators—presumably to reduce weight and the possibility of interaction on small printed circuit boards. The Lowrey "Genie" uses this system.

Lowrey are transistorising their automatic orchestra computer circuit, which hitherto used a diode matrix. Unless you play a Lowrey, a.o.c. will not mean much, but the sound is probably unconsciously recognised by those that enjoy light music. Harry Stoneham began to broadcast regularly some six years ago and has been featured by Sam Costa, in "Breakfast Special" and on the Pete Brady Show: more recently, he has appeared in Michael Parkinson's programme. His distinctive sound is usually produced on a Lowrey with the a.o.c. in action, though Harry also plays Hammond with equal dexterity.

A.o.c. allows the performer to play a single note melody on the upper manual (at the selected pitches) which is automatically harmonised with any chord played on the lower manual. Whilst this feature was probably designed with the beginner in mind, the experienced player can produce breathtaking runs of chords. Left hand chords must be sustained when using a.o.c. as the harmonising facility is lost when the accompaniment keys are released.

## REVERBERATION

An electronic instrument played in a public hall may not need reverberation, though a crowd of people will absorb both reverberation and output power. In a small room with fitted carpets and curtains, the instrument will be dead without some reverberation. Adding echo makes the sound source seem to come from deeper within the speaker enclosure and gives a more natural effect.

Tape, delay lines or spring units may be used, the latter still being the

simplest. Some commercial spring units are too small and consequently produce short delay times, often with too much "direct" signal that can only be reduced by going to work on the circuit board.

It is possible to add reverberation to an existing installation without running to the expense of a further power amplifier if some care is taken. The main amplifier loudspeaker signal is tapped off and fed to the secondary of a small output transformer. It is a good precaution to put a 100Ω resistor in series with one lead to prevent robbing, and a small 6V lamp in series with the other to act as a current limiter. The primary winding of this transformer feeds the driver coil of a magnetic unit such as the Gibbs-Hammond.

The driven coil produces only a few millivolts and requires a pre-amplifier with a gain of about 50. It is a fairly easy matter to arrange a pair of BC109 transistors, directly coupled, to recover the signal. Small capacitors should be used at both input and output of this pre-amplifier. The base of the first transistor should be biased by means of a resistor from the emitter of the second transistor.

A 50kΩ potentiometer across the pre-amp output is suggested, with a T attenuator from the slider followed by 250pF before feeding into the main amplifier at a point after the main volume/swell control. The small capacitor tends to accentuate top response. Needless to say, there is some danger of howl due to feedback and the 50kΩ variable should be kept near minimum while setting up. Ideally, the spring driver coil should be fed from a push-pull driver amplifier, but the method outlined above will probably give sufficient echo for most needs, and it has the merit of simplicity.



The Hammond Regent

# The Sinclair Cambridge... no other calculator is so powerful and so compact.

## Complete kit-£24.95! (PLUS VAT)

### The Cambridge – new from Sinclair

The Cambridge is a new electronic calculator from Sinclair, Europe's largest calculator manufacturer. It offers the power to handle the most complex calculations, in a compact, reliable package. No other calculator can approach the specification below at anything like the price – and by building it yourself you can save a further £5.50!

### Truly pocket-sized

With all its calculating capability, the Cambridge still measures just  $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$ . That means you can carry the Cambridge wherever you go without inconvenience – it fits in your pocket with barely a bulge. It runs on ordinary U16-type batteries which give weeks of life before replacement.

### Easy to assemble

All parts are supplied – all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our service department will back you throughout if you've any queries or problems.

### The cost? Just £27.45!

The Sinclair Cambridge kit is supplied to you direct from the manufacturer. Ready assembled, it costs £32.95 – so you're saving £5.50! Of course we'll be happy to supply you with one ready-assembled if you prefer – it's still far and away the best calculator value on the market.



### Features of the Sinclair Cambridge


- \* Uniquely handy package.  $4\frac{1}{2}'' \times 2'' \times \frac{11}{16}''$ , weight  $3\frac{1}{2}$  oz.
- \* Standard keyboard. All you need for complex calculations.
- \* Clear-last-entry feature.
- \* Fully-floating decimal point.
- \* Algebraic logic.
- \* Four operators (+, -, ×, ÷), with constant on all four.
- \* Constant acts as last entry in a calculation.
- \* Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £30.
- \* Calculates to 8 significant digits, with exponent range from  $10^{-20}$  to  $10^{79}$ .
- \* Clear, bright 8-digit display.
- \* Operates for weeks on four U16-type batteries. (MN 2400 recommended.)

# A complete kit!

The kit comes to you packaged in a heavy-duty polystyrene container. It contains all you need to assemble your Sinclair Cambridge. Assembly time is about 3 hours.

## Contents:

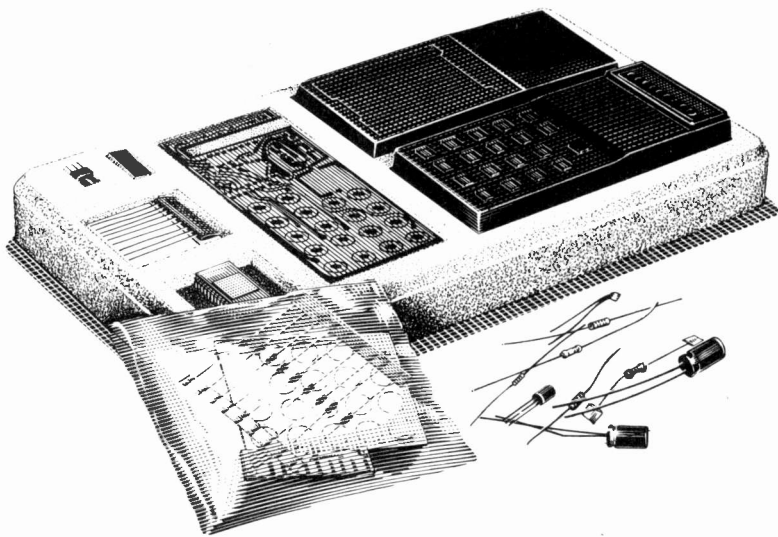
1. Coil.
2. Large-scale integrated circuit.
3. Interface chip.
4. Thick-film resistor pack.
5. Case mouldings, with buttons, window and light-up display in position.
6. Printed circuit board.
7. Keyboard panel.
8. Electronic components pack (diodes, resistors, capacitors, transistor).
9. Battery clips and on/off switch.
10. Soft wallet.


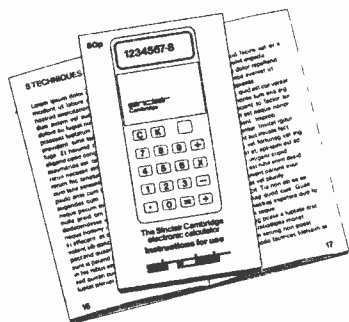
## This valuable book – free!

If you just use your Sinclair Cambridge for routine arithmetic – for shopping, conversions, percentages, accounting, tallying, and so on – then you'll get more than your money's worth.

But if you want to get even more out of it, you can go one step further and learn how to unlock the full potential of this piece of electronic technology.



How? It's all explained in this unique booklet, written by a leading calculator design consultant. In its fact-packed 32 pages it explains, step by step, how you can use the Sinclair Cambridge to carry out complex calculations like:

Logs Sines Cosines  
Tangents Reciprocals nth roots  
Currency Compound  
conversion interest  
and many others...

# sinclair

Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire  
Reg. no: 699483 England  
VAT Reg. no: 213 8170 88

## Why only Sinclair can make you this offer

The reason's simple: only Sinclair – Europe's largest electronic calculator manufacturer – have the necessary combination of skills and scale.

Sinclair Radionics are the makers of the Executive – the smallest electronic calculator in the world. In spite of being one of the more expensive of the small calculators, it was a runaway best-seller. The experience gained on the Executive has enabled us to design and produce the Cambridge at this remarkably low price. But that in itself wouldn't be enough. Sinclair also have a very long experience of producing and marketing electronic kits. You may have used one, and you've almost certainly heard of them – the Sinclair Project 60 stereo modules.

It seemed only logical to combine the knowledge of do-it-yourself kits with the knowledge of small calculator technology.

And *you* benefit!

## Take advantage of this money-back, no-risks offer today

The Sinclair Cambridge is fully guaranteed. Return your kit within 10 days, and we'll refund your money without question. All parts are tested and checked before despatch – and we guarantee a correctly-assembled calculator for one year.

Simply fill in the preferential order form below and slip it in the post today.

**Price in kit form: £24.95 + £2.50 VAT. (Total: £27.45)**

**Price fully built: £29.95 + £3.00 VAT. (Total: £32.95)**

To: Sinclair Radionics Ltd, London Road,  
St Ives, Huntingdonshire, PE17 4HJ

PE/12/73

Please send me

a Sinclair Cambridge calculator kit at  
£24.95 + £2.50 VAT (Total: £27.45)

a Sinclair Cambridge calculator ready  
built at £29.95 + £3.00 VAT  
(Total: £32.95)

\*I enclose cheque for £ \_\_\_\_\_, made  
out to Sinclair Radionics Ltd, and  
crossed.

\*Please debit my \*Barclaycard/Access  
account. Account number \_\_\_\_\_

\*Delete as required.


Name \_\_\_\_\_

Address \_\_\_\_\_

PLEASE PRINT

# 9V BATTERY ELIMINATOR

BY A.M. RUDKIN B.Sc.(Eng.)Hons.

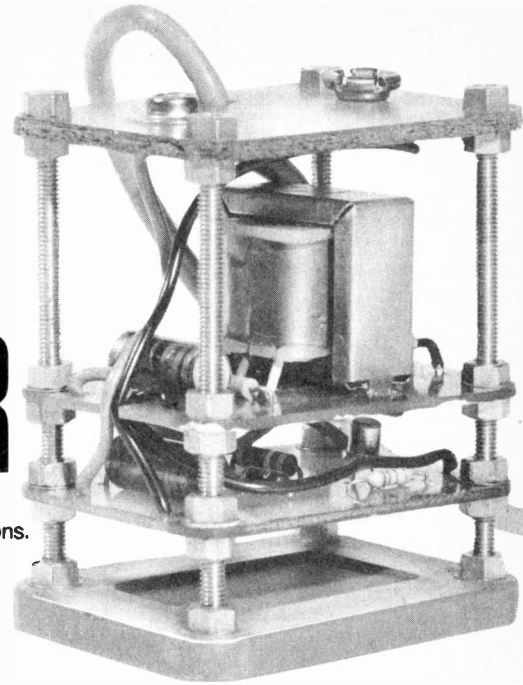

THERE are many battery operated transistor radios which are used almost entirely in the home, and with the rising cost of replacement batteries the question of a battery eliminator comes to mind. To the home constructor the thought of buying a ready-made unit goes against the grain, but it is not easy to achieve a professional finish in a home-made unit. Fortunately, the battery manufacturer provides us with an easily available case of exactly the right size. The current trend amongst manufacturers is to use a thin metal casing and a battery case of this type can be re-used quite successfully.

Most portable radios used in the home take PP9 batteries or an equivalent and this size is large enough to hold the necessary components to make the eliminator. With a component cost of about £1.50p the unit will pay for itself quite quickly and, of course, the eliminator can easily be removed whenever battery operation is required.

## CIRCUIT DESCRIPTION

As can be seen from Fig. 1, the circuit of the battery eliminator is relatively simple, but despite the simplicity the unit delivers a regulated output voltage and provides protection against overloading or short circuits.

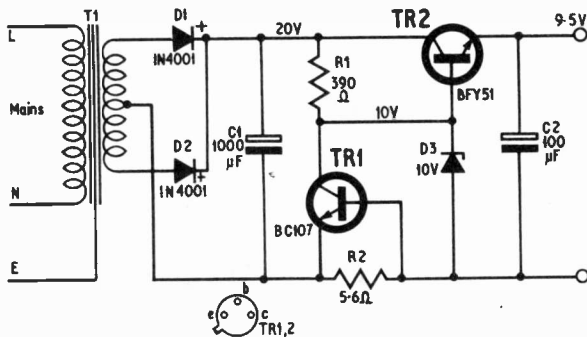


Fig. 1. Circuit diagram of the 9V Battery Eliminator

A miniature mains transformer with a centre-tapped secondary feeds a full-wave rectifier. The reservoir capacitor, C1, smooths the rectified output before it is applied to the series regulator circuit. A 10 volt Zener diode, D3, provides a fixed base voltage to transistor TR2, which in turn provides a fixed output voltage of about 9.5 volts at low impedance.

A second transistor, TR1, provides current limiting protection since its base-emitter junction is connected across a current sensing resistor, R2.

When the current flowing through the resistor exceeds 100mA the transistor begins to turn on and reduces the voltage across the Zener diode thereby reducing the output voltage so that even under short circuit conditions the current through the series regulator never exceeds a safe value.

## COMPONENTS . . .

### Resistors

- R1 390 Ω
- R2 5.6 Ω } ±10% ¼W carbon

### Capacitors

- C1, C2 100µF 25V elect. (2 off)

### Semiconductors

- TR1 BC107
- TR2 BFY51
- D1, D2 1N4001 (2 off)
- D3 10V 400mW Zener

### Transformer

- T1 Mains primary, 14-0-14 50mA secondary (Henry's type MT991)

### Miscellaneous

- Printed circuit board, 4BA studding, mains cable, nuts and washers, old PP9 battery case, interconnecting wire

The graph in Fig. 2 shows the way the output voltage varies with load current and the rapid drop in voltage as the current approaches the 120mA limit can clearly be seen.

An electronic "fuse" of this kind may seem a luxury but in fact it costs less than a fuse link and fuse holder whilst offering a high degree of protection. The simple regulator used in the battery eliminator is quite adequate for use with radio receivers and the ripple on the output is low enough not to cause any audible hum in the radio loud-speaker.

### MOUNTING COMPONENTS

The electronic components are mounted on two small boards which are supported by screwed rods and it is recommended that printed circuits are used. Dimensions of the boards and the track layouts are shown full size in Fig. 3 and Fig. 5. If facilities for making printed boards are not available then as an alternative 0.1in matrix board (without copper strip) may be used with point to point wiring.

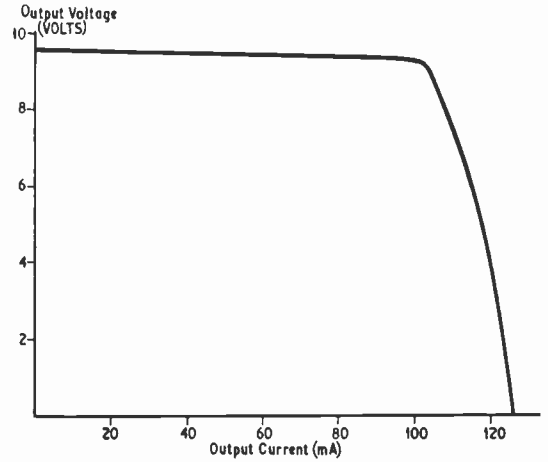


Fig. 2. Graph showing the variation of output voltage with current. The fall off at 100mA is due to the current limiting effect of TR1

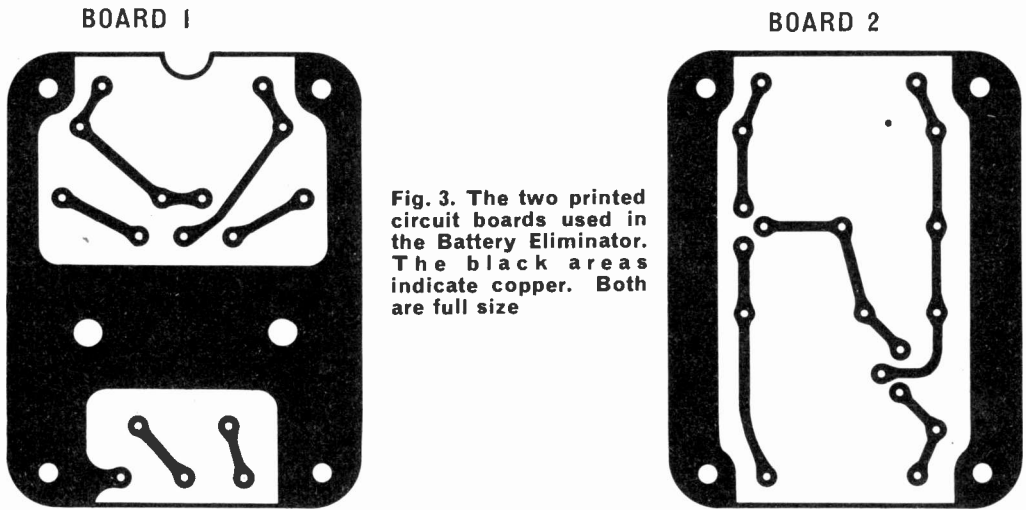


Fig. 3. The two printed circuit boards used in the Battery Eliminator. The black areas indicate copper. Both are full size


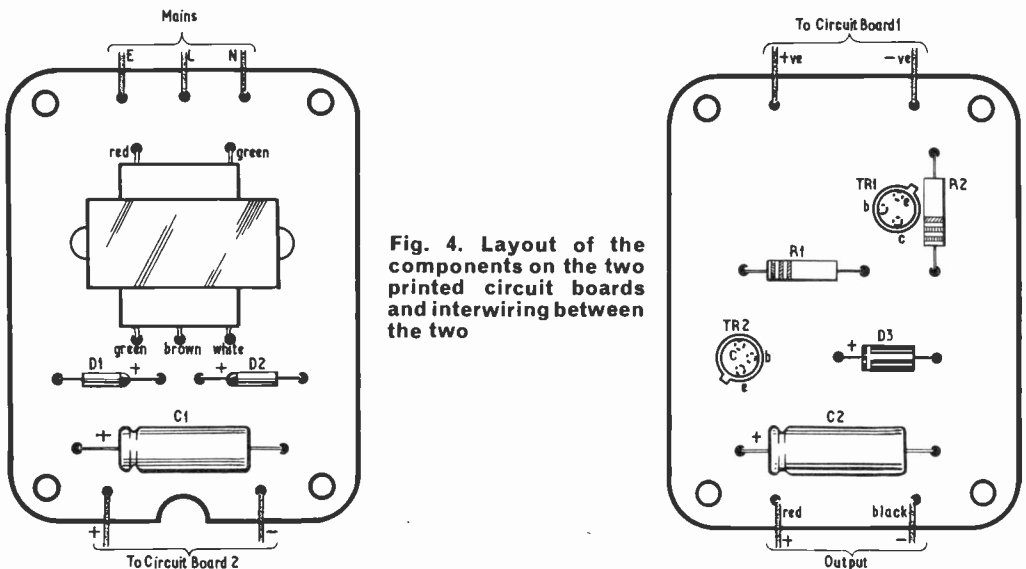


Fig. 4. Layout of the components on the two printed circuit boards and interwiring between the two

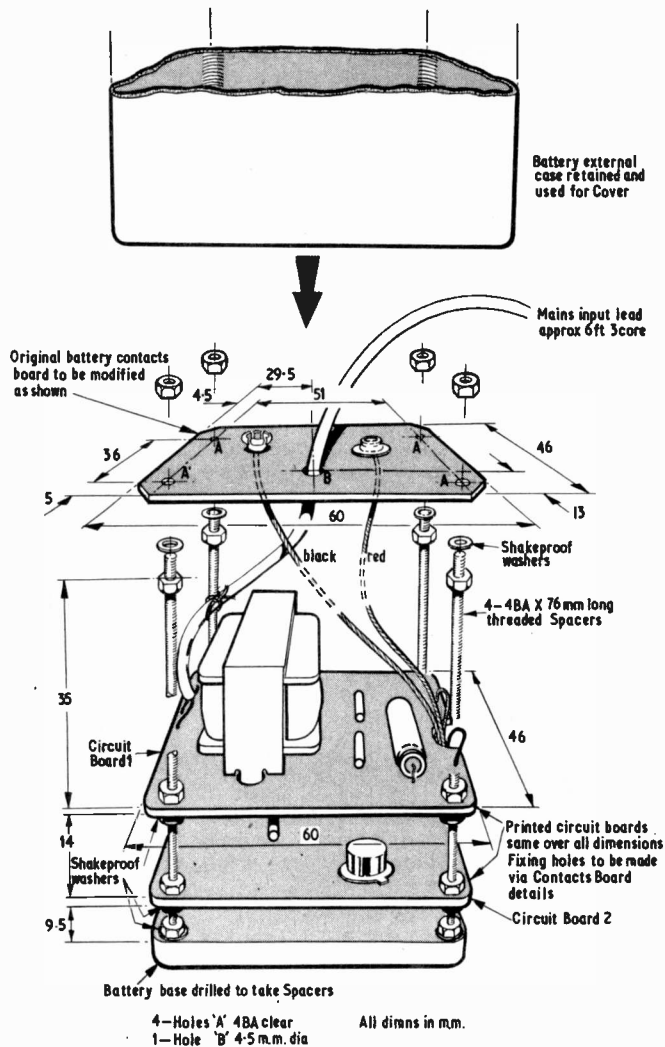

**FIG. 5  
EXPLODED  
VIEW**

Before mounting the mains transformer onto the printed circuit board shorten the leads to about  $\frac{1}{2}$  in and strip the sleeving back to expose  $\frac{1}{4}$  in of the wire. Mount the transformer on the board and bend back the fixing lugs to hold it securely in place. Fit the other components and interconnect the two boards as shown in Fig. 4.

Temporarily connect a mains lead and, as a safety precaution during testing, cover the mains connections with self adhesive p.v.c. tape. Apply the mains and check that the output voltage of the regulator board is approximately 9.5 volts. A voltage very different from this value indicates a fault condition and the voltages indicated on the circuit diagram (Fig. 1) may be used to aid in fault finding.

### USING AN OLD BATTERY CASE

It is quite easy to take a battery apart, but some care should be taken in order that the casing may be re-used. The battery should not be so old that the cells have started to leak or the case may be damaged.

In the battery used for the prototype the bottom plate was made of plastic and was held in place by

the metal jacket which was folded over the rim of the plate. This fold was carefully straightened by bending back the metal with a small pair of pliers. After this the contents of the battery can be removed by pressing the top plate of the battery downwards.

The six cells are, of course, no longer required, but the other parts should be kept. Contact between the cells and the top plate with the "snap" connectors is by a thin piece of brass strip and a spring contact. Cut off the brass strip and remove the piece of cardboard which separated the top plate from the cells by cutting around the contacts with a knife blade.

Drill holes in the top and bottom plates in accordance with the dimensions given in Fig. 5. The hole for the mains lead is drilled in the top plate only.

### ASSEMBLY

When the boards are functioning correctly they can be assembled onto the screwed rods. The distances between the boards and the plates are shown

*continued on page 1097*

# INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

## TRACE DOUBLER FOR TTL COMPATIBLE SIGNALS

THE diagram in Fig. 1 shows a circuit for a trace doubler, which displays the time relationship between two series of pulses.

Gate G1 and its associated diode plus two resistors and capacitor form a clock generator with a mark to space ratio of 1 to 1. Gate G3 provides an inverted clock waveform. One input of G4 is the signal input, "A". One input of G5 is the other signal input, "B". The other input of G4 is connected to the output of G3, the inverted clock. The other input of G5 is connected to the output of G2, the true clock.

These two clock signals are always the opposite of

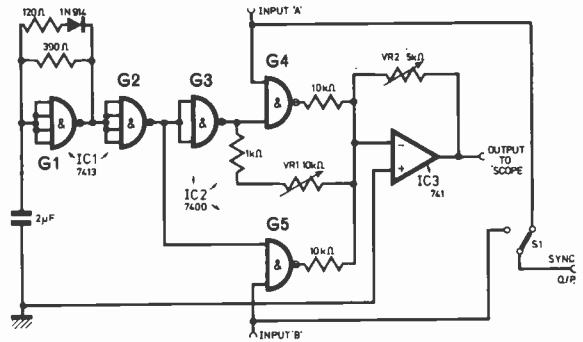


Fig. 1

each other, thus gates G4 and G5 are alternately enabled or disabled. Any output from G4 or G5 is fed to the summing junction of IC3, via a 10kΩ potentiometer and a 1kΩ resistor. The operational amplifier combines the signals and feeds them to the oscilloscope to be displayed.

The idea behind the operation of this circuit is that any signal information from input "A" is added to a constant voltage, the inverted clock and is then displayed below the trace for input "A".

The 10kΩ potentiometer VR1 varies the separation between the traces and VR2 in the operational amplifiers feedback path controls the overall gain of the instrument.

C. Nicol, Brixton, S.W.9.

## SIMPLE VARIABLE-DELAY PULSE CIRCUIT

VARIABLE delay time on a repetitive pulse is frequently required, particularly in those applications concerning transient phenomena. A simple, low cost, and easily constructed electronic circuit is described which enables continuously variable delayed times in the range 10µS to 80mS to be achieved.

The circuit, shown in Fig. 1, consists of two monostables, the first providing the controlled variable delay time and the second giving the delayed output pulse. The master pulse to be delayed is first differentiated by the R1C1 network. The negative-going spike obtained from this network is then used to turn the first monostable over. The turn-over period is given by:—

$$T = 0.7 VR_1 \times C_{2, 3, \text{ or } 4}$$

The positive pulse from the collector of TR1 is fed into the second monostable via another differentiating network. Again the negative-going spike turns the monostable over and a rectangular pulse can be taken from the collector off TR3.

A negative output pulse could be taken from the collector of TR4, but it would be of poor shape due to capacitance C7 charging up via the load R8 in the collector of TR4.

By both making VR1 variable from 100Ω to 10kΩ and by selecting the C2, C3, C4 capacitors having fixed values of 0.1, 1.0 and 10µF a continuously variable delayed output pulse in the range 10µS to 80mS has been obtained.

The delayed times are measured from the negative-going edge of the master pulse. Both shorter than 10µS, and

longer than 80mS can be obtained by suitable choice of the passive components VR1 and C2, C3, C4.

The minimum width of the output pulse is 2µS. This is varied using VR2 (100Ω to 10kΩ) and C7 (4000pF).

The sum of the delayed time and the pulse width must, of course, be shorter than the periodic time of the master pulse. The rise and fall times of the output pulse are respectively, 25 and 30nS.

The delay times of the present circuit have been calibrated against a standard time marker and found to be both reproducible and reliable.

Drs. R. Hackham and P. Johnston  
University of Sheffield.


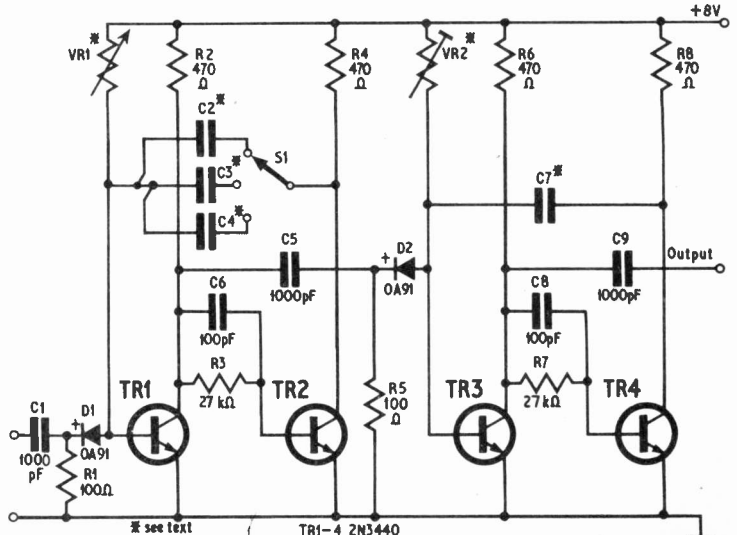


Fig. 1. Simple variable-delay pulse circuit

## SIMPLE TACHOMETER

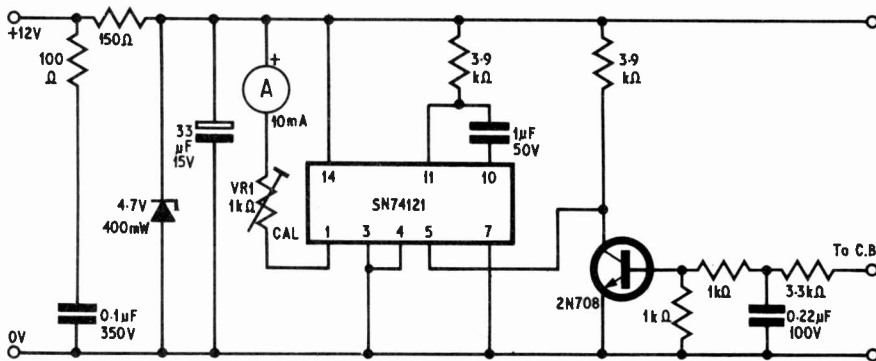

**TABLE 1:**  
Calibration Frequency corresponding to 1,000 r.p.m.

No. of Cylinders	2-stroke	4-stroke
	frequency	
1	16.7Hz	8.4Hz
2	33.4Hz	16.7Hz
3	50Hz	—
4	—	33.4Hz
6	—	50Hz
8	—	67Hz

THE CIRCUIT of a tachometer shown in Fig. 1 is based on the integrated circuit SN74121. This is a monostable device available for under 50 pence.

The circuit can be adapted for a wide range of meters up to 10mA f.s.d. by simply connecting a resistor in series with the meter if required. Initially the design was made for a 12V system but providing the 150Ω series dropper is altered there should be no difficulty in adapting for other voltages.

The timing components are the 3.9kΩ resistor and 1μF capacitor connected to pins 10 and 11, and the capacitor should preferably be a reasonable quality non-electrolytic type.

Meter movement at very low frequencies may be countered by connecting a capacitor across the meter but a good movement should not need this.

Calibration is *via* VR1 preferably against a pulse

generator of reasonable accuracy. Calibration frequencies are given in Table 1.

C. J. Nother,  
Portsmouth, Hants.

## SCREENWASHER TIMING UNIT

THE device to be described operates the electric screenwashers of a car for a period of up to 10 seconds after a single press of the switch so that one hand does not have to leave the steering wheel for more than a second or so.


Only two main components are used, a relay and a capacitor, and from Fig. 1 it can be seen that when the washer control button is pressed, C1 is immediately charged up to the full 12V battery voltage and discharges over a period of 10 to 15 seconds through the coil of RLA so closing the contacts RLA1 and operating the washer pump motor.

As C1 discharges through the relay, the current eventually falls to below the hold-in value for the relay, contacts RLA1 separate and the pump stops.

VR1 is used to set the operating time of the pump motor. By filing the copper rivet on the armature flat with the face, the hold-in time can be slightly increased and also has the advantage that the relay drops out suddenly so preventing arcing of the contacts which might occur if they separated more slowly.

The relay used is a PO 3000 type with a 1,000Ω coil with all the contacts removed except for one pair of "make" contacts to increase sensitivity, though if a second pair was fitted combined wash and wipe with "one shot" operation could be achieved.

The can of C1 should be completely insulated before mounting, using p.v.c. tape or tube and the

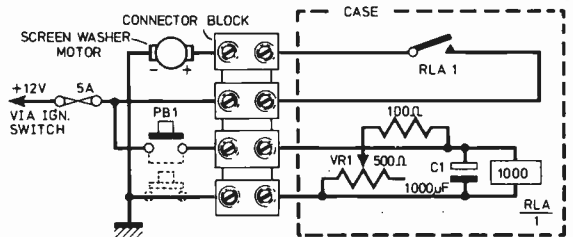

**Fig. 1. Arrangement of the screenwasher unit**

complete unit should be mounted in a closed steel case in a dry spot away from exhaust pipes. The prototype has functioned perfectly over 1,000 miles with no maintenance being required.

The circuit shown is for 12V negative earth systems. For positive earth the connections to C1 and the washer pump motor merely need to be reversed.

The dotted lines in Fig. 1 show a slight modification which is necessary where the existing switch operates the original washer circuit by shorting one side of the motor to earth, the other side being permanently live, as is often found in the horn circuit.

In both cases, connection to the supply should be *via* a 5A fuse to a "live when on" part of the ignition switch or terminal A4 on the fuse box.


A. Calder,  
Leigh, Lancs.





# VEROSTRIP

LENGTH 8'5"

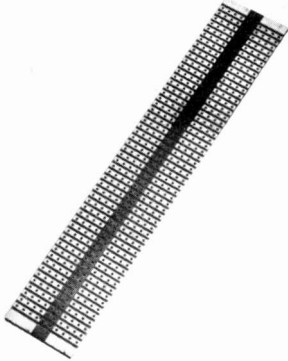

WIDTH 1'5"

Available from your Local Retailer

0-1 and 0-15 pitch Vero Strip is suitable for all applications where Tag Boards can be used



VERO ELECTRONICS LTD  
INDUSTRIAL ESTATE  
CHANDLERS FORD HANTS.

## 6 WATT STEREO AMPLIFIERS




High quality amplifiers giving 3W/channel RMS. With low distortion (0.2%). The circuit is designed around the Plessey Integrated Circuit Type SL414A.

There is a single and a two-tone control model each designed to accept a crystal pick up. Giving a frequency response from 50 to 15kHz with a load of 8 ohm impedance 3W/channel.

Transformers for above amplifiers ... £1-08  
Single Tone Controls ... £6-55 each  
Dual Tone Controls ... £8-25 each

### LOUDSPEAKER ENCLOSURE

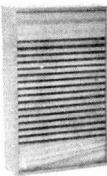

Incorporating 6 x 4in Fane speaker 10,000 Gauss. Voice coil impedance 8 ohm. Work 6ft of lead. Teak Vinyl covered enclosure with slotted Scandinavian type front. Size 12 1/2 x 7 1/2 x 3 1/2in. Ideal for extension speakers. Price, £4-60 each.

Plessey I.C.'s Type SL414A - complete with circuit diagram, £1-38.

Trade enquiries invited. Post and packing 40p for speakers and amplifiers.

ALL PRICES INCLUDE V.A.T.

**CIRTEC PRINTED CIRCUITS LTD**  
HIXON INDUSTRIAL ESTATE, HIXON  
STAFFORD

**PARTRIDGE MAINS ISOLATION TRANSFORMER.** Pri: 105-250V, 6V steps, Sec: 240V, 13 amps. £16, carr. pack. £1-50.

**FARNEKO MAINS TRANSFORMER** Isolated windings. Pri: 200-250V. Sec: 90-120V at 4.5 amp., £4, carr. pack. 75p.

**GARDNER'S POTTED TRANSFORMER, 0-250V.** Pri: 200-250V. Sec. Input: 18V 500mA, 50V 150mA, 6V 260mA output. Size: 3in x 2 1/2in x 2 1/2in, £1, p.p. 25p. Ex equip. tested.

**RIPLYE MAINS TRANSFORMER.** Pri: 110V-240V, Sec: 12-5V: 0.12-5V 750mA/4 7V:0.7 VIA, £1, p.p. 25p.

**MAINS TRANSFORMER.** Pri: 100-250V, Sec: 22:0-22 200mA/4. 22:0-22 100mA/4 0:24V 20mA/4, 80p, p.p. 25p.

**MAINS TRANSFORMER.** Pri: 230V. Sec: 14V, 120 amps. £15, p.p. £1-50.

**MAINS TRANSFORMER.** Pri: 100-240V a.c. 36-5-0-36-5V, 27 mA/A, 0-21-5, 260 mA/A, 80p, p.p. 25p.

**TRANSISTOR OUTPUT TRANSFORMER.** Ratio 8:1, 150mH. Centre tap 2 watts. output, 80p, p.p. 8p.

**SMOOTHING CHOKE, 11mH, 1 1/2in x 1 1/2in x 1 1/2in.** 80p, p.p. 8p.

**FINNED ALUMINIUM HEATSINK, 4 1/2in x 8in x 1in, 2 x 2N3055, £1, p.p. 13p.**

**GOODMANS 8in SPEAKERS 3 Ω £1-50, p.p. 28p.**

**FINNED ALUMINIUM HEATSINK. 9in x 8in x 1 1/2in. In C.: 4 x 2N3055, £2, p.p. 29p.**

**GARRARD MAG. TAPE DECKS: 1 1/2in.p.s., 50V, solenoid operated brakes, etc. Mains voltage motors £7-50 each, p.p. 60p.**

**MOYET 3 speed tape deck (1 1/2in x 3 1/2in x 7 1/2in)** reel to reel 7in mains operated, £7-50, p.p. 63p.

**10 REED SWITCHES** operated by push buttons and magnets, 60p, p.p. 25p.

**COMPONENT PANEL, 6 scr's (300V, 1-6A) 6 cond., 15 resistors, 6 diodes, 45p, p.p. 8p.**

**COMPONENT PANEL, 6 scr's (200V 4 amps), 6 condensers, 12 resistors, 30p, p.p. 8p.**

**COMPONENT PANEL (9 ICs FJH131) (1-CA30), 1 crystal 7-68kHz ± various other components, £1, p.p. 8p.**

**COMPONENT PANEL, 2 x 500mF 50V, 3 x 100mF 25V, cap. 1 x 2N2812, 2 x 2N404, 3 diodes plus various other components, 10p, p.p. 9p.**

**COMPONENT PANEL, 24 0A81 diodes, 10p, p.p. 8p.**

**VEEDED ROOT ELECTRICAL IMPULSE COUNTER NON-RESETABLE, A.C. 200-250V, £1-10, p.p. 13p.**

**GEV MAINS CIRCUIT BREAKERS, 2 amp or 3 amp, £1 each, p.p. 14p.**

**LEVER ACTION P.O. 1000 TYPE SWITCHES** Lock 4-pole changeover, 15p, p.p. 4p. Ex equip. Lock 2-pole changeover, 10p, p.p. 4p. Ex equip.

**MULLARD & MALLORY SCREW TERMINAL CAPACITORS 4,600µF 64V, 1,100µF 40V, 50p each. 20,000 30V, 25,000 25V, 35,000 15V, 30p each, p.p. 21p.**

**MULLARD FULLWAVE RECTIFIERS** 6-48V, 15 amp, 75p, p.p. 10p.

**BELLING LEE 1-5 amp in-line rubber covered interference suppressor, 25p, p.p. 8p.**

**RUBBER 3 PIN 5 AMP NON-REVERSIBLE CABLE CONNECTORS, 20p, p.p. 5p.**

**SOLENOIDS 12 VOLT PULL ACTION** 2in x 1in x 1in, 40p, p.p. 8p.

**SOLENOIDS 12-24V d.c. pull action 1 1/2in x 1 1/2in x 1 1/2in, 40p, p.p. 5p.**

**SOLENOIDS 240V a.c. pull action 2 1/2in x 1 1/2in x 1 1/2in, 50p, p.p. 9p.**

**BANGALOW WESTON TIME LAPPED METER** Mains operated. 1 1/2in x 1 1/2in x 2in, £1-50 p.p. 7p.

**ARROW RELAY, 240V a.c. coil, double pole change over, 1 make contact's 10A, 240V a.c., 25p, p.p. 9p.**

**OMRON MK2 MIDGET POWER RELAY, 12V d.c. Double pole changeover. New, 70p, p.p. 5p.**

**ETC VARLEY, miniature relays 700 Ω, 17-5-37V, persex cover, 4 pole changeover, 40p, p.p. 5p.**

**POTTER BRUMFIELD 12V d.c. 3 pole changeover with base, contacts rated 7A d.c., £1, p.p. 10p.**

**I.T.T. LOW PROFILE RELAYS. 4 pole c/overs. 600 Ω 12-18V, 75p, p.p. 8p.**

**MAINS RELAYS, 200-250V a.c. 2 makes. Heavy duty contacts, 50p, p.p. 7p.**

**TELESCOPIC AERIALS** Chromed 7in closed, 28in extended, 6 section ball jointed base, 25p, p.p. 5p new.

**PRINTED CIRCUIT BOARD/19 ACY 19's 10 0A200 Diodes: 1 reed relay: 1 AZ 229 zener ass. capacitor/resistors. Power supply 22V, 250 mA d.c. Output 240V a.c., £1, p.p. 25p. Ex equip.**

**WIRING CABLE** Size-1-020. Various colours. 350yds, 60p, p.p. 28p.

**TAPE POSITION INDICATOR** Re-settable 3 digits, 30p, p.p. 5p.

All orders add 10% V.A.T.

**FIELD ELECTRIC LIMITED**  
3 Shenley Road  
Borehamwood, Herts.  
Tel. 01-953 6009

# 0442:62757

THE NUMBER  
FOR CLOCKS,  
LSI CHIPS, KITS  
& DISPLAYS.

Choose a combination from the tables below. get out your Access card and ring the above number, or send us a cheque, MO, PO, etc.

BYWOOD for ADVICE, SERVICE and of course COMPONENTS.

Clock Code	12/24 Hour	4/8 Digit	BCD out	7seg out	MPX'd	1Hz out	AM/PM	Alarm	Date	Snooze	Sleep	Pwr Cnt	INTERFACES						Interface Key	Availability	PRICE
													TIL360	DL34	DL707	DL62	DG12	TA8055			
MM5311	Y	Y	Y	Y	Y							28	D	D	T	T	-	11-49	8	Stock	11.50
MM5314	Y	Y	Y	Y	Y							24	D	D	T	T	-	11-49	8	Days	11.00
MM5316	Y	4	Y	Y	Y	Y	Y	Y	Y	Y		40	-	-	L	D	K	8-29	4	Stock	16.00
5017AA	Y	6	Y	Y	Y	Y	Y	Y	Y	Y		24	T	T	T	K	-	11-18	16	Stock	14.00
5017BB	Y	6	Y	Y	Y	Y	Y	Y	Y	Y		24	T	T	T	K	-	11-18	16	Ltd	14.00
CT7001	Y	6	Y	Y	Y	Y	Y	Y	Y	Y		28	T	T	T	D	-	11-18	16	Feb74	18.00

Display Code	Type	Pack	Digs	Digit Size	Drive Req.	Common	Digit Cost £	Unit Cost £
TIL360	LED	16 DIL	6	0.1ins	2v 10mA	Cathode	2.50	15.00
DL707	LED	14 "	1	0.3ins	3v 30mA	Anode	2.00	2.00
DL34	LED	14 "	4	0.1ins	5v 10mA	Cathode	2.50	10.00
DL62	LED	16 "	1	0.6ins	6v 30mA	Anode	6.50	6.50
DG12H	Phosphor Diode.	TUBE	1	12.5mm	25v 1mA	Htr Anode	2.00	2.00
TA8055	Liq.Crys.	EDGE	4	0.6ins	30v125uA (A.C.)	N/A	3.25	13.00

Sockets - 24or28pin 115p, 40pin 135p. Case - Warm red Perspex 250p.

Kits 5017AA or BB + PCB + socket + 4 DG12s + Instructions £24.  
MM5316 + " + " + TA8055 + " £32.

CLOCK DATA SHEETS - SAE. ADVICE - PHONE 0442-62757 CATALOGUE 15p  
POST & PACKING - 10p. OVERSEAS (AIRMAIL) 50p. VAT - ALL PRICES EXCLUDE VAT.  
PAYMENT C.W.O. or ACCOUNT. ACCESS. ORDERS & PAYMENT BY PHONE ACCEPTED.  
QUANTITY DISCOUNTS ON MOST ITEMS - STATE REQUIREMENTS FOR QUOTATION.

# BYWOOD

Bywood Electronics  
181 Ebbwens Road  
Hemel Hempstead  
HP3 9RDB

## MAINS NEON FLASHER

THIS is a circuit which I have developed to remind you to un-plug mains appliances as well as switch them off. The neon glows when the appliance is switched on and flashes when it is switched off until it is unplugged.

With S1 (on/off switch of the appliance) closed (see Fig. 1) the neon lights, R2 dropping the mains voltage to the firing voltage of the neon. With S1 open C1 charges via R1 until it reaches the firing voltage of the neon and then discharges through it, thus making it flash until S1 is closed or the appliance is unplugged.

With such devices fitted to all appliances, a quick look round the room last thing at night will tell you that they are all off and unplugged.

M. J. Maynard,  
Wednesbury, Staffs.

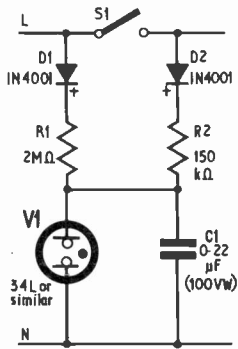


Fig. 1. Circuit diagram for the mains neon flasher

## 9V BATTERY ELIMINATOR

continued from page 1092

in Fig. 5, although the dimension between the connector plate and the mains transformer board may need to be varied slightly to ensure a snug fit inside the battery casing.

Before fitting the connector plate pass the output leads of the regulator board through the slot in the mains transformer board and solder them to the contacts. The plain contact is positive and the castellated contact is negative (on some modern batteries the castellated contact has been replaced by a split contact).

Pass the mains lead through the hole in the connector plate and fit the plate onto the rods. Using p.v.c. lacing cord or thin p.v.c. sleeving, tie the mains lead tightly to one of the screwed rods to prevent the soldered joints being stressed.

The length of the screwed rod is 3in where the battery has a plastic bottom plate, but a slightly longer rod will be needed if a different bottom plate is fitted. The rod is normally supplied in 3ft lengths and can be sawn very easily with a "junior" hacksaw.


One "trick of the trade" when sawing threaded rod is to thread a nut onto the length to be sawn. After cutting and deburring with a file the nut can be removed and this will automatically re-form the thread on the cut end. This simple procedure saves a good deal of time and temper.

### FINISHING OFF

When the power supply assembly fits the battery case satisfactorily the ends of the brass rod may be filed down level with the tops of the nuts. Finally fit the unit into the case ensuring that "+" marking on the case is closest to the plain contact and carefully re-fold the casing over the bottom plate.

The battery eliminator can then be fitted into the portable radio in place of the normal battery although a slot will need to be made in the radio casing to allow for the mains lead. On the few occasions that the radio is required as a true portable the mains unit can be removed and a battery inserted in exactly the same time as it would take to replace a flat battery. ★

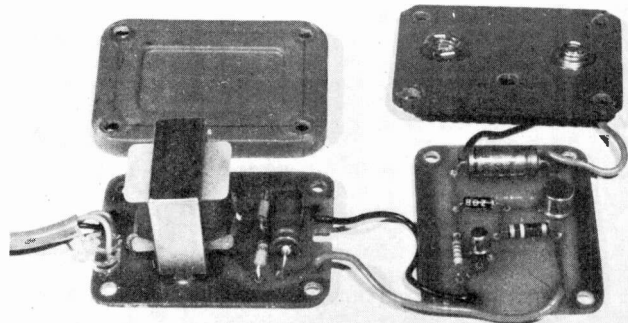Photograph showing the two component boards and the end plates of the battery before mounting on brass studding



# VIEWPOINT

Sir—Am I alone in thinking that quadraphony (and indeed stereo) is a "con"—or at least an attempt by the industry to create a demand?

I remember several years ago an article in this or a similar magazine, reporting a Continental idea whereby the orchestra performed in the wide end of a large exponential horn—the audience obtaining the effect of hearing a live orchestra through a metre-square hole!


Now this seems infinitely more sensible to me than quadraphony.

Surely the fact that an orchestra, or a pop-group, is ten metres wide is irrelevant. If width is necessary *per se*, why not spread the musicians out more? In fact musicians have always stood as close together as possible. Why?

A group of musicians constitutes a certain size purely because human beings are the size they are, and similarly with instruments.

"Stereo" and "quad" are NOT analogous to stereo pictures. Surely it follows that the industry should be putting the effort into improved colour, stereo pictures instead of the absurdities of "quad"! The present colour T.V. picture is on a par with a washed-out, amateur transparency viewed through a 50p lantern.

E. Wadsworth,  
Huddersfield, Yorks

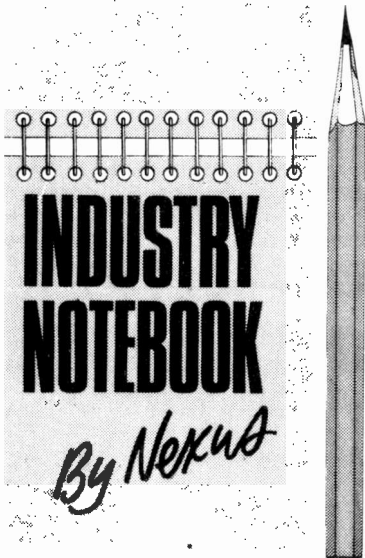

# INDUSTRY NOTEBOOK

By Nexus

## LIGHT FINGERS

Shop-lifting by well-heeled women in London's West End has been making the headlines. Not so well publicised is the wave of petty and not-so-petty pilfering in the electronic components industry since the upsurge in world demand created a component famine.

As usual, the incidence of crime appears greatest in the United States. Few of the semiconductor manufacturers are immune and hardest hit, according to reports, is Signetics with over £40,000 of goods mysteriously disappearing. Fairchild has also been hit.

It's not only straight pilfering that's worrying the industry. Huge quantities of below-standard products have been hived off onto the market at give-away prices in recent years and many of these are now re-appearing freshly remarked and not necessarily with the original manufacturer's name. These are being bought in good faith and equipment manufacturers have found performance not up to scratch. Motorola has been one company receiving back for replacement falsely marked semiconductors. Over in the States, the police have been sleuthing away and some arrests have been made.

The racketeers have not confined activities to the USA. The very nature of semiconductor devices with their small size, light weight and high intrinsic value makes them a natural for shipping round the world and Bill Richardson, Chairman of Britain's Association of Franchised Distributors of Electronic Components (AFDEC) has warned the industry against dishonest brokers.

Members of AFDEC are bound by constitution to guarantee all products they sell and this is the best protection. Richardson quotes a case where a UK manufacturer disposed of a bulk quantity of sub-standard products 12 years ago which have recently re-appeared on the UK market through sources which can be traced back through Tel Aviv and Geneva. Buyers beware!

## DEFENCE BOOM

The Royal Navy Equipment Exhibition at Greenwich showed defence equipment manufacturers in good shape, technically and economically. Defence exports have been booming and climbing in value every year. In 1968-69 exports were £150 million, in 1972-73 they had climbed to £345 million and this year will top £400 million, about 40 per cent of all defence equipment manufactured in the UK.

The sales success of recent years owes much to the pioneer work of Sir Raymond Brown who resigned his Chairmanship and business interests in Racal Electronics to become the first Head of Defence Sales in 1966. Present Head of Defence Sales is Sir Lester Sheffield.

The sales organisation does market research, organises exhibitions, assists industry with advice and generally smooths the path between initial enquiry and final sale. Even Royal Fleet Auxiliary vessels are pressed into use as floating exhibition centres. For the past three months RFA *Tarbatness* has been touring the Middle East and Far East on just such a mission.

## FIFTY YEARS ON

This has been a great year for Golden Jubilees marking the 50th anniversary of broadcasting and of many of the pioneering companies that sprang into existence to serve the needs of what was to become an industry in its own right. Of all the celebrations one of the cosiest, if not the biggest, was the informal party given by Eddystone Radio.

Although the company is now part of the giant GEC-Marconi complex, Eddystone's managing director Dick Carroll has managed to preserve the family atmosphere—perhaps not too difficult with so many of the staff having been around for more years than they care to remember.

Enough of the past. How is Eddystone shaping up to the future? Today's sets are all solid-state, modular, up-to-the-minute and selling well. Eddystone profits are buried deep in the corporate

accounts of the parent group but I can reveal that they are healthy in every way. Watch out for new models and an expanded component line in 1974.

## COMPUTERISED METROLOGY

Herbert Controls and Instruments Ltd. was formed in 1969 from three companies in the Alfred Herbert Group and started life with a 50-year background in measurement techniques stretching back to Sigma gas gauges, modern versions of which are still sold to the gas industry. But more recently HCIL moved into the field of mechanical inspection equipment and rapidly established a world reputation for solving difficult problems.

One of HCIL's most remarkable machines is the Sigmatrace designed specifically for inspection of the aerofoil profile of gas and steam turbine compressor blades. This was traditionally a skilled job which took a lot of time and involved lengthy written records which were passed to a blade polisher to iron out humps and hollows and get each blade right. The inspector would compare the workpiece under inspection with a perfect master.

Sigmatrace does the whole job in a minute, complete with a printed record of deviation. Moreover, no master blade is required because all the master profile information is fed into a computer store direct from the drawings. HCIL is doing a roaring trade world wide with this sort of electronic-based metrology and supplies most major automotive and aerospace manufacturers.

The chief engineer of HCIL, Dr. Colin Gaskell, sees computer-controlled gauging becoming really significant in engineering shops where more than 30 measurements are needed on a workpiece. When you get up to 80 measurements a computer is practically a necessity.

## DUCKS AND GROUSE

Mallard is dead—long live Ptarmigan. They are the code names for the army's trunk communications systems. Mallard died after endless discussion. Now Plessey has been appointed prime contractor for the new system, Ptarmigan, with Marconi and STC as subcontractors. Initial contracts are worth £17 million but the project could lead to £100 million of business over the years.

I marvel at the wit of those who invent code-names. Mallard always seemed a dead duck. And if Ptarmigan doesn't come up to scratch, we'll have something to grouse about.

## Come home to this fine 8 track stereo system

Elegantly styled in teak finished cabinets with satin aluminium trims and controls.

Automatic and manual channel selection with at-a-glance illuminated track indicator.

Separate bass treble and volume controls for exact tone balance.

Full 5 + 5 watt rating from latest integrated circuit amplifiers.

Solidly built bookshelf speaker units house high performance elliptical loudspeakers.

The complete package including mains and speaker leads is ready to play in minutes.

# Quentronic



Price Incl. VAT, P & P

**£28.50**

Manufactured and distributed by  
Quentronic Ltd., 4-6 Mill Lane, Brighouse, Yorks. Telephone: 048 47 4837

## RECORD PLAYBACK HEADS (TRUVOX)

Individual prices of these are:—  
2 track record playback heads 50p each.  
4 track record playback heads 79p each.  
Erase heads are also available separately—2 track 38p—4 track 56p.  
MV metal mounting slides 38p each.  
2 track-heads already fixed on heavy mounting plate with shield £1.22.


## CONTROL DRILL SPEEDS

### DRILL CONTROLLER NEW IKW MODEL

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.95. 13p post and p. Made up model also available. £2.95.
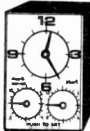
### MIGHTY MIDGET

Probably the finest possible radio, as described in *Practical Wireless*, January 73. All electronic parts £2.20 post paid.



### TIME SWITCH

Smith's mains driven clock with 15 amp switch, also notes showing how you can wake up with music playing, kettle boiling or come home to a warm house, warn off burglars, keep pets warm, halve your heating bills, etc. £1.95.

### I CHIP RADIO

Ferranti's latest device ZN414 gives results better than superhet. Supplied complete with technical notes and circuits. £1.98 each. 10 for £11.11.

### HI-Q TUNER COMPONENTS

For experimenting with the ZN414.  
KIT NO. 1. Fleesby Miniature Tuning Condenser with built-in LW switch and 3in Ferrite slab and litz wound MW coil, 72p.  
KIT NO. 2. Air spaced tuning condenser 6in ferrite rod litz wound MW and LW coils, 94p.  
KIT NO. 3. Air spaced TC with slow motion drive 8in ferrite rod, with litz wound LW and MW coils, £1.10.  
KIT NO. 4. Permeability tuner with fast and slow motion drive and LW loading coil, 50p.

### AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete when fitting instructions and ready wired dashboard switch. £6.35 plus 25p post and insurance.

### TELESCOPIC AERIAL

for portable, car radio or transmitter. Chrome plated—six sections, extends from 7 1/2 to 47in. Hole in bottom for 6BA screw. 42p. KNUCKLED MODEL FOR F.M. 55p.

### EXTRACTOR FAN

Cleans the air at the rate of 10,000 cubic ft. per hour. Suitable for kitchens, bathrooms, factories, changing rooms, etc. It's so quiet it can hardly be heard. Compact, 5 1/2in casing with 5 1/2in fan blades. Kit comprises motor, fan blades, sheet steel casing, pull switch, mains connector, and fixing brackets. £2.75 + 20p P. & P.

### MAINS OPERATED SOLENOIDS

Model 772 — small but powerful 11n pull—approx. size 1 1/2 x 1 1/2 x 1 1/2in. 68p.  
Model 4001—1in. pull. size 2 1/2 x 2 x 1 1/2in. 88p.  
Model 771—1 1/2in. pull. size 3 x 2 1/2 x 2in. £1.98 plus 20p post and insurance.

### MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v., 9v., 12 volts for up to 500mA (class B working). Takes the place of any of the following batteries: PF1, PF3, PF4, PF6, PF7, PF9, and others. Kit comprises: mains transformer rectifier, smoothing and load resistor condensers and instructions. Real snip at only £1.10. Plus 20p postage.

### DESK TELEPHONES

Ex G.P.O. Black standard model with dialing dial but no internal bell. Supplied with connection diagram £1 each. D150, with bell but without dialing dial £1.85. Model as illustrated with bell and dial £1.50 each plus 30p post for single then 65p per pair.



## SMOKE WILL KILL—GAS WILL KILL—FIRE WILL KILL

But, if you install SAGA (our smoke and gas alarm) your family will have the latest electronic protection against these killers. SAGA uses a fantastic electronic sensor which "smells" smoke and gas and sounds the alarm immediately, in a neat case measuring approx. 5in x 3 1/2in x 2 1/2in. It has its own internal alarm, also a connector for additional bells. You just plug it in to the mains and hang it near the ceiling. SAGA uses so little electricity that it will hardly move the meter, leave it on always to give night and day protection. One year's guarantee, also 7-day cash return offer, or kit of parts £5.99. Battery model kit only £4.99, £6.69 plus 30p post and service.



### CENTRIFUGAL FAN

Mains operated, turbo blow type. Pressed steel housing contains motor and impeller. Motor is 1/10th h.p. giving considerable air flows but virtually no noise. Approx. dimensions 10 1/2in wide x 12in dia. outlet into trunking 10 1/2 x 4 1/2in. £6.55 plus £1 post and insurance.




### STANDARD WATER SWITCHES

Standard size 1 1/2in waffer—silver-plated 5 amp contact, standard 1/2in spindle 2in long—with locking washer and nut.

No. of Poles	2way	3way	4way	6way	8way	9way	10way	12way
1 pole	44p	44p	44p	44p	44p	44p	44p	44p
2 poles	44p	44p	44p	44p	44p	44p	44p	44p
3 poles	44p	44p	44p	44p	44p	44p	44p	44p
4 poles	44p	44p	44p	44p	44p	44p	44p	44p
5 poles	44p	44p	44p	44p	44p	44p	44p	44p
6 poles	44p	44p	44p	44p	44p	44p	44p	44p
7 poles	44p	44p	44p	44p	44p	44p	44p	44p
8 poles	44p	44p	44p	44p	44p	44p	44p	44p
9 poles	44p	44p	44p	44p	44p	44p	44p	44p
10 poles	44p	44p	44p	44p	44p	44p	44p	44p
11 poles	44p	44p	44p	44p	44p	44p	44p	44p
12 poles	44p	44p	44p	44p	44p	44p	44p	44p

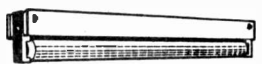
### THE TWENTYLITE

Fluorescent lighting units with polyester choke and finished white enamel. 2ft. model, ideal kitchen, bedroom, hallway, porch, lift, etc., with tube. Assembled ready to install. Price £2.20 + 40p P. & P.



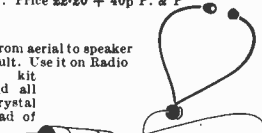
### RADIO STETHOSCOPE

Easiest way to fault find—traces signal from aerial to speaker—when signal stops you've found the fault. Use on Radio TV, amplifier, anything—complete kit comprises two special transistors and all parts including probe tube and crystal earpiece. £2.20—twin stethos instead of earpiece 88p extra—post and ins. 20p.


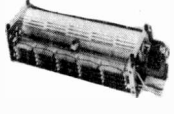
### TANGENTIAL HEATER UNIT


This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. £3.85. 2kW Model as above except 2kW £2.75. Don't miss this. Control Switch 44p. P. & P. 40p.



Room Thermostat made by the famous Smith's Company. 15 amp at 250V. Elegant white and beige case, size 4 1/2in long by 1 1/2in square approx. Adjustment is by slider (lockable), adjusts through range 30°-90°F. Special 8in price £1.65.

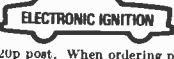
### CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the *Wireless World* about a year ago. We can supply kit of parts for an improved and even more efficient version (*Practical Wireless*, June). Price £2.55 plus 20p post. When ordering please state whether for positive or negative systems. De-luxe model including printed circuit board, etc. £7.95.


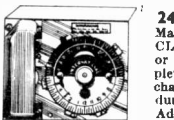
### 24-HOUR TIME SWITCH

Made by Smiths, these are A.C. mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Two completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. £2.75 post and ins. 25p. Additional time contacts 55p pair.




### PHOTO ELECTRIC KIT

Contains photo cell, relay, transistor and all parts to make light operated switch. £1.75 plus 20p post and ins.


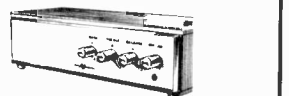
## MULLARD UNILEX STEREO AMPLIFIER

We demonstrate these daily and almost always a sale results; it really is a cracking amplifier. Only Mullard with their know-how could have made it possible at this low price. SPEC. Mains operated. 4 watts music or speech per channel. Double wired power supply eliminates cross talk. Harmonic distortion less than 2%. Frequency response 50Hz-15kHz. Input suitable for pick up tuner or microphone. 6-month guarantee. Only £11.30 post paid. Optional extras—Cabinet £2.20. Extra front plate £1. Pair of 15 ohm speakers £3.30.



TERMS: 10% discount if ten of an item ordered, send postage where quoted—other items, post free if order for these items is £6.00, otherwise add 20p.

## NEW ITEMS THIS MONTH

**White Rocker Switches.** Four types available, all snip in fixing through oblong hole approx 1 1/2in, all rated at 10A a.c. All have white rocker except 83, which is amber. Our ref R8 S1, push to make, spring return, 14p. Our ref R8 S2, push to break, spring return to on, 14p. Our ref R8 S3, change over contacts, luminous rocker, 28p. Our ref R8 S4, changeover contacts, normal rocker, 16p.

**Rocker Switches.** 15A Pritmac panel mounting, hole size 1 1/2in x 1 1/2in. Our ref R8 S5 price 11p each. 5A made by Mem, their type ref 1600, our ref R8 S6, price 11p each.

**Miniature Hand Microphone.** Dynamic, for tape recorders but equally suitable for amplifiers, good quality with lead and plug, price £1.37.

**Open Coil Relays.** All with 10A change over contacts, all brand new. Our ref REL S1, 12 volt d.c. coil, double pole, 44p. Our ref REL S2, 110 volt a.c. coil, treble pole, 44p. Our ref REL S3, 240 volt a.c. coil, treble pole, 55p.

**Photo Transistor Bargain.** First class maker but slightly reject, covered, however, by our normal six month guarantee, these respond to light or infra red. Will work a burglar alarm system, make detector counter, etc. Price £2p complete with three circuits.

**Mains Fuses.** Braided, circular cotton covered, overall 8in x (23-36) 100 yard coils. Price £2.75 plus 50p post.

**Mains Connector.** This serves the same purpose as a treble pole relay but owing to the more robust construction and more positive action it is much more reliable and very suitable for heavy duty mains circuits, for example, where a thermostat has to control a large number of heaters. The connector has four switches each in its own compartment separate from the others and each able to make and break 10A with complete safety. German made, these measure approx. 2 1/2in x 2 1/2in x 2 1/2in, price £2.20.

### GOOD COMPANION I.C. VERSION

We can now offer these again in I.C. version using Ferranti ZN414 and Mullard AF Module 1172. Cabinet size approx. 1 1/2in wide x 8in high x 3in deep. Complete assembly instruction—Excellent tone wood cabinet £5.75 plus 25p post and insurance.



### MOTORS FOR £1.50

As used in racing cars and power models. All battery operated and reversible.



**Mains Transformers.** All by first class makers, all with normal 230V primary and static screen. Our ref TR S1, 6.3V, 3A, with clamp and feet, 88p. Our ref TR S2, made by Finchley for Decca primary tapped 200/340 volt two secondaries 275-0-275 volt at 90MA and 6.4 volt at 3A, this is for above chassis mounting, open construction, price £1.75 plus 25p post. Our ref TR S3, upright mounting with metal shrouds, primary tapped 110 volt and 200/240 volt, two secondaries 50 volt at 2A and 6 volt at 1A, £5.50 plus 25p post.

### PC BOARD MARKER

Valve action fibre tipped marking pen filled with black etch resist—it's easy with this to make a perfect PC board, just draw straight on to the copper—allow 15 minutes to dry, then immerse in ferric chloride or other etchant on removal the circuit stand in high relief, 99p.

### EDUCATIONAL KITS — all with pictorial instructions


3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 44p each post paid. Special price for all 7 kits £3.00 with free balance kit.



- KA2 Lens Kit. Eleven parts, concave lens, one convex lens, stage and slit frame, etc.
- KA3 Water Pump Kit. Thirteen parts. Transparent so that operating parts may be observed. You can make Lift pump, Force pump and Force pump with reservoir and nozzle.
- KA4 Buzzer Kit. Eleven parts. Operation of buzzer seen.
- KA7 Electro-Magnet Kit. Fifteen parts, includes compass, showing how magnetism works.
- KA8 Current and Resistance Kit. Twenty-nine parts, including bench and light bulb. "OHMS LAW" etc.
- KA9 Bell Kit. Eight parts, including bell and push button switch. Build a complete electric bell.
- KA10 Morse Key buzzer and bell kit. 25 part kit easy to construct, simple to operate.
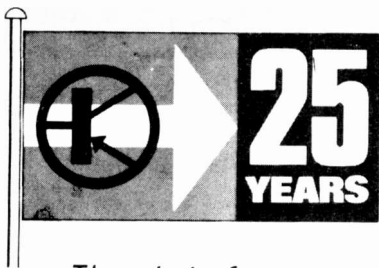
## J. BULL (ELECTRICAL) LTD.

(Dept. P.E.), 7 Park Street, Croydon CRO 1YD  
Callers to 102/3 Tamworth Road, Croydon



# Transistors & Constructors

## By D. Bollen

*The start of a great revolution in home construction is recalled by a well-known contributor in this article, which brings to a conclusion our special series commemorating the invention of the transistor*

IN THE TYPICAL home electronics workshop of twenty-five years ago the enthusiast would be surrounded by machines for bending, punching, drilling, and rending asunder sheet metal. Constructional techniques were based upon the chassis, a box-like structure full of holes into which were inserted spindles, screws, valveholders, grommets, and trapped fingers.

Sometimes, when the burden of bashing metal became tiresome, a piece of easily punctured Bakelite might be pressed into service as a breadboard, but this was considered very unprofessional, a throwback to the days of coil winding, capacitor building, and generally doing it yourself.

Components came from two main sources; sturdy ex-government equipment which was cannibalised, sometimes with the aid of a hammer and cold chisel, and the "junk box" where reposed an amorphous heap of very second-hand items, ranging from a leaking electrolytic capacitor dated 1941 to a speaker grille woven to depict a scene of nymphs and satyrs dancing in a woodland setting. These were the lean years just after the war, with no oriental imports, kits of parts or regular sources of "bits".

Into this man's world of hot cathodes and 100 watt soldering irons was born the sub-midget transistor, and the wonder is that it managed to survive at all, let alone replace valves, which everyone said it would never do.



### A TOUGH TIME

Transistor manufacturers were having a tough time trying to fabricate the new device, probably because they were ham-fisted too. In any event, if you were fortunate enough to get hold of a sample in the early fifties it was likely to be one that everybody else had rejected, with a leakage current of two or three milliamps, a current gain of five, and dying from slow contamination.

Compared with a valve this was a pathetic thing indeed!

Assume that you were the proud possessor of a device no bigger than a resistor with three wires sticking out of it. Where did you go from there? Published information was scanty and far from standardised. Maximum ratings were mere hearsay. At the devaluation equivalent of £2 to £4 each, the safest policy was to power the device at the lowest voltage and current at which it was capable of supplying useful work.

As far as circuits went, which was not very far, there was a limited choice between the upside down, thread-in-a-maze American sort, or the UK variety which favoured the powering of each transistor in a multi-stage circuit by its own personal 1.5V cell.

Apart from earth symbols and batteries floating all over the page, there was also a general tendency for transistor symbols to be shown doing a base-down nose dive into the earth rail, this being the only way they could be made to function above 10kHz.

### GREAT DIFFICULTIES


So, in the face of great difficulties you managed first of all to identify the leads on your transistor with an ohmmeter and then to find, or rashly devise a transistor circuit.

Were you supposed to solder the thing to a tag-strip, and mount the resulting assembly on the customary two acres of sheet aluminium? After all, we were here dealing with impedances of a very low order, for which electrolytic capacitors the size of milk bottles would have to be accommodated for coupling and decoupling purposes.
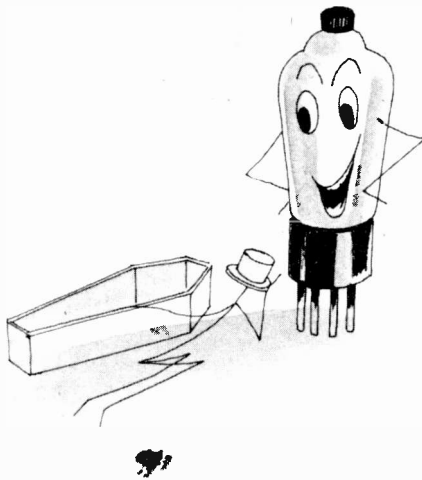
### DELICATELY SOLDERED

The delicately soldered transistor clings to its tag-strip. The scope (ex-government of course) displays a straight line on its axis. Several meters are linked to those parts of the circuit where a voltage or current might conceivably occur.

After inserting the power supply plug into the lowest voltage tap of a grid-bias battery . . . yes, we have oscillation!



True, it is but a crude imitation of what would normally pass as a sine wave from a valve circuit, but it is early days yet. A few more volts perhaps? Why is that meter reading creeping higher and higher? Should the transistor run hot? It has stopped oscillating.

"Grrr! They will never replace valves."

## AVAILABLE TO AMERICAN

The transistor was available to American enthusiasts for about \$18 in 1953. Over here, the ubiquitous OC71 and "red spot" transistors (the latter a polite name for manufacturer's reject) came on the scene in 1956 priced at 24/- and 10/- respectively. Full praise must be given to those suppliers who struggled to bring us the amplifying crystal less than eight years after its invention.

The silicon transistor also took only eight years to reach the home after being first manufactured in 1952.

More than one enterprising magazine contributor of the period went one better and gave full instructions for making a point-contact transistor from an old crystal diode, but the problem here was that an excess of audio signal or marital strife in the home could dislodge the triple catswhisker and thus degraded performance.

Another bright spark discovered that when the paint was scraped off the glass encapsulated OC71 it responded to light in the manner of a photo-transistor. The manufacturers quickly countered this cunning move by filling their transistors with opaque blue putty, labelling the clear putty variety OCP71 and charging more for it.

## NEST OF SNAKES

An innovation of the middle fifties was the transistor radio, which incorporated the new "nest of snakes" unrepairable printed circuit and the fragile ferrite rod aerial. Also at this point in time, the word "transistor" was press-ganged into common English usage to signify a radio receiver which could be employed to annoy people on beaches, and also render the user deaf in one ear by means of a simple unhygienic earphone.

The printed circuit defied all former rules of construction.

Components were held in position by solder alone, a practice which previously would have been considered very naughty. With the passing of the chassis, there was no longer anywhere to mount controls, and this caused quite a few headaches in constructional circles.

Eventually, it was tacitly agreed that serious projects would have their controls mounted on smart metal front panels, while silly projects could use sheet plastic or even wood. Alas, these attempts at standardisation failed miserably.

One breakaway group defiantly insisted on using metal tobacco tins for all projects, while another sect mounted their controls on the printed circuit itself! The latest trend seems to be to bung everything inside a transparent plastic cube or sphere and hope for the best, so confusion still persists.

## ADVANCED STAGE

Valve audio amplifiers had reached an advanced stage of development prior to the introduction of the "jump-a-groove" long-playing record in 1950, but with the coming of the difficult-to-tune f.m. radio in 1955, hi-fi purists were at last able to take time off to just sit and listen to the music, without having to bother about all that nasty distortion of former years.

Unfortunately, this idyllic state lasted only until 1961, when the easy-to-blow power transistor started to appear in output stages, accompanied by something called "the transistor sound".

This unusual effect was characterised by a rattling buzz from loudspeakers when gain controls were turned low. After a good deal of concentrated sleuthing, it transpired that transistor audio amplifiers were subject to crossover distortion, so the purists had to climb out of their armchairs and set about exorcising the demon with cabalistic circuitry.

Since then there has been no further opportunity to listen to music. Elimination of the output transformer led to severe difficulties in trying to match the then extant 15 ohm loudspeakers to amplifiers requiring a four to eight ohm load, and all problems were multiplied by two when stereo came along.

Now they are about to be multiplied by four.

## SURVIVE THE TRANSITION

What has the future in store for those who have managed to survive the transition from valve to transistor? Clearly, the introduction of a new device is often accompanied by unpleasant side-effects. For example, with i.c.s. we have already experienced circuits which are best understood if held upside down in front of a mirror, and the use of postal codes for device numbering is to be deprecated.

Above all, one thing is patently clear. A new device seems to take eight years to mature to amateur status. Furthermore, all information concerning a new device is automatically withheld for five years, or until it becomes obsolete, whichever period is shorter. So it follows that there is no need to get too agitated when a new device comes along, because the threat to one's peace of mind is not immediate.

NOTE: This last point is not quite true since it is the avowed object of PRACTICAL ELECTRONICS to ensure that the reader is informed of interesting developments as soon as possible. Indeed, the problem nowadays would be to avoid doing so—ED.





# PATENTS REVIEW...

## FUEL MONITOR

BP 1 320 039

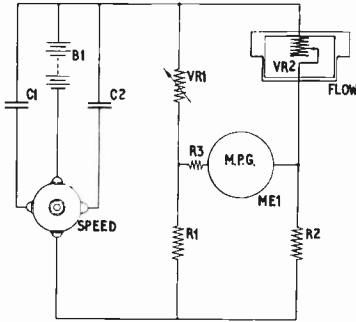


Fig. 1

With petrol likely to be very scarce or more expensive or both in future, devices for accurately measuring vehicle fuel consumption will become more popular.

In BP 1 320 039 Alan Westwood, Peter Davidson and Brian Dean describe and claim just such a device. The circuit Fig. 1 shows a vehicle speed measuring device, a flow meter to measure fuel rate of flow (and thus proportional rate of consumption) and an ammeter for reading m.p.g.

The meter is connected between opposite junctions of a Wheatstone bridge comprising VR2 (which forms part of the flow meter), R2, R1 and VR1 for pre-setting bridge balance. The use of R3 in series with the meter is only necessary with certain meters.

The opposite corners of the bridge are connected together by the vehicle speed measuring device. This includes a rotor geared to the vehicle transmission with brushes which alternately connect capacitors C1, C2 across the vehicle battery and discharge them through the bridge. The capacitors C1, C2 thus charge and discharge alternately to give a signal representative of the vehicle speed.

The flow meter will generally be in the form of a chamber with inlet and fuel outlet pipes and a bellows-type diaphragm. Fuel passing to the engine flows through the chamber to compress the diaphragm in dependence upon fuel flow rate. As the diaphragm is compressed, the value of VR2 resistance is varied by movement of the slider over its track. The value of VR2 resistance is in practice an inverse function of the fuel flow rate.

The reading given on the meter is approximately proportional to an arithmetical relationship between the two signals controlled respectively by the flowmeter and the speed measuring device, being approximately proportional to the current received from the rotor of the speed measuring device multiplied by the imbalance of the bridge circuit due to the flow meter. This reading represents an indication of distance travelled by the vehicle per unit of fuel consumed and the meter ME1 can be calibrated to provide direct readout in miles per gallon.

## NEW APPROACH TO TONE CONTROL

In BP 1 304 774 Wilfred Palmer of Dagenham, Essex, describes a three part tone control circuit for an audio amplifier. By way of example he gives a list of specific values for all the components, see Fig. 1.

The variable potentiometer VR1 and d.c. blocking capacitor C1 form a normal volume control. The slider of VR1 acts as a common input line to the three sections of the tone control, shown dotted.

The bass circuit includes R1 and R2 in series with VR2. The slider of VR2 is in series with R3 which feeds the output terminal.

The mid-range circuit has R4 and R5 in series with VR3, and the slider is also connected to the output via R6 and C2.

The high frequency circuit comprises VR4, the slider being connected to the output via C3.

The resistor R7 between C2 and C3 is intended to isolate the infinite variations of time constant of the treble circuit from the infinite variations of time constant of the mid-range circuit. Also, the resistor acts as an impedance to high frequencies from the bass and mid-range circuits. The inventor suggests that in this way the signals from the middle and treble circuits are cleanly and fully mixed.

The bass circuit presents a high impedance to high frequencies, thereby attenuating them but passing low and mid-range frequencies. This is due to the presence of resistors R1 and R2. The inventor points out that any resistor can be represented by a pure resistance in parallel with the self capacitance across the resistor terminals and there is thus attenuation of high frequency signals by the changes of self capacitance with increasing frequency. By using the resistors in series, total self capacitance is lowered.

The treble circuit presents an increasing impedance as the frequency decreases, thus attenuating low frequencies but passing the high and part of the mid-range frequencies.

The inventor claims that the circuit eliminates the need for attenuators in crossover units and allows infinite variations of the signal fed to loudspeakers over the whole audio spectrum.

BP 1 304 774

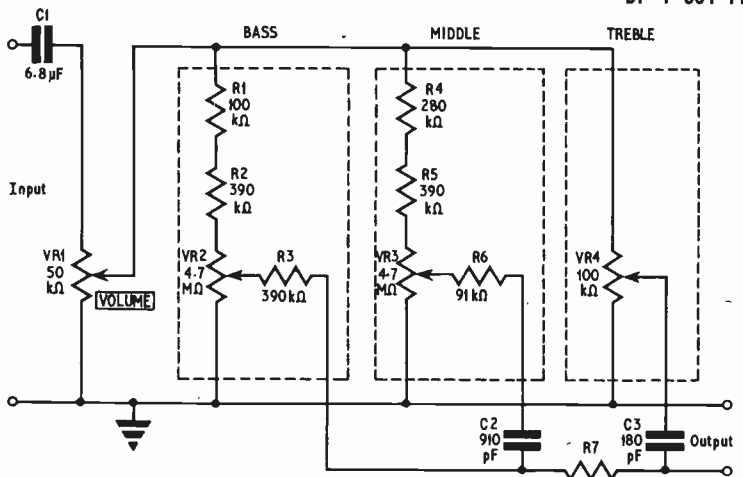


Fig. 1

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way.*

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s simplified study method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don’t know the first thing about Radio now, you’ll build your own Radio set within a month or so!

... and what’s more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.


**You LEARN—but it’s as fascinating as a hobby.**

Among many other interesting experiments, the Radio set you build—and it’s a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.
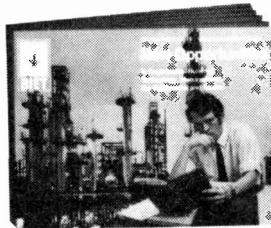
### Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of “NEW OPPORTUNITIES”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



## FREE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. BPE22, ALDERMASTON COURT, READING RG7 4PF

*Accredited by the Council for the Accreditation of Correspondence Colleges.*

**POST THIS COUPON FOR FREE BOOK**

**CL** **BPE22**

NAME (BLOCK CAPITALS) ..... AGE .....

ADDRESS .....

SUBJECT OF INTEREST .....

# P.C. BORED?

— not with the

## decon-dalo 33PC



A unique drafting aid for the electronics engineer enabling him to prepare in minutes a perfect PCB.

A fine-tipped marker charged with a free-flowing etch-resist ink. Simply draw the desired circuit onto copper laminated board—etch—clean.

The circuit is ready to use.

## NO MESS — NO MASKING

### A perfect circuit every time!

*The Decon-Dalo 33 PC marker is now available in France, Germany, Italy, Switzerland, Austria and all Scandinavian countries. Send for details of local supplier.*

Please send me further details on the 33PC:

Name .....

Address .....

PE12

Post to: **DECON LABORATORIES LTD.**

**FREEPOST**

**PORTSLADE, BRIGHTON, ENGLAND**


(No Stamp Needed) Phone 0273 414371

## parts for PRACTICAL ELECTRONICS projects. "One Source" buying makes sense—saves you time, money and postage.

After many requests, Electro Spares are now supplying lists of components for ALL the projects featured in "Practical Electronics" commencing July 1973 issue. Just forward a S.A.E. (preferably 9" x 4" minimum) stating which project is of interest to you—we will forward an individually priced list of components required. No need to buy a full kit—you need only purchase the parts you require at any one time. All Electro Spares supplied components are new, branded products of reputable manufacturers and carry full makers' guarantee. We regret we cannot supply lists for projects published before July 1973 issue.
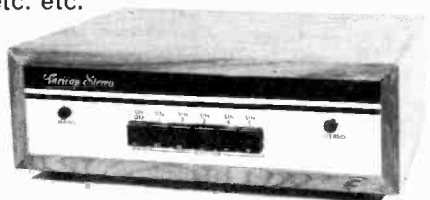
### "P.E. RONDO" QUADRAPHONIC SOUND SYSTEM

Complete kits for the entire P.E. Rondo Project will be available as this appears in the magazine. These contain top quality components with fibre glass p.c. board, etc. etc.



### "P.E." F.M. VARICAP STEREO TUNER

Electro Spares offer a kit of high quality parts to the published specification for this remarkable tuner, featured in "Practical Electronics", May 1973. Features include pushbutton "Spot On" tuning, with up to 5 pre-set stations (no difficult tuning dial and drive cord). Easy "no problem" construction requiring only a few simple setting up adjustments with a d.c. Voltmeter. Uses NEW pre-set modules for R.F. and I.F. circuits—no circuit alignment. High efficiency integrated circuit Phase Lock Loop Decoder for perfect stereo reception, with stereo lamp indicator. Fibre Glass P.C. Board, neat slim-line cabinet, with brushed aluminium front panel, pushbuttons, etc. etc.

IDEAL FOR USE WITH THE "TEXAN",  
"P.E. GEMINI" AND ANY GOOD  
QUALITY STEREO AMPLIFIER.

ALL PARTS for Varicap tuner and Gemini amplifier supplied separately.

Please send S.A.E. for full details of any of the above or call yourself. Visitors welcome—easy parking.

### "P.E. GEMINI" STEREO AMPLIFIER

QUALITY HI-FI FOR THE  
HOME CONSTRUCTOR. 30 Watts (R.M.S.)  
per Channel into 8 ohms!  
Total Harmonic Distortion 0.02%!  
Frequency Response (—3 dB) 20 Hz—  
100kHz!

We are still continuing to supply components for this fabulous amplifier, which is now recognised as practically the ultimate in High Fidelity. We know of no better unit for the home constructor, and can supply a booklet, containing full specification, complete constructional information, wiring diagrams, fault finding guide, etc. etc., price 55p plus 4p postage. Our new, low comprehensive price list is supplied with each booklet, or prices for components supplied separately on receipt of large S.A.E.

FOR PEOPLE WHO REQUIRE THE  
BEST—IT HAS TO BE THE "p.e. gemini"

# ELECTRO SPARES

The Component Centre of the North.


288 Ecclesall Road  
Sheffield S11 8PE  
Tel.: Sheffield (0742)  
668888

# es

NEW QUICK and EFFICIENT MAIL ORDER DEPARTMENT
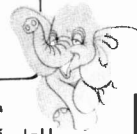
# Henry's

**UK'S LARGEST RANGE OF TRANSISTORS, IC'S RECTIFIERS, ALL SEMICONDUCTOR DEVICES**  
**BEST PRICES - RETAIL - TRADE - EXPORT & INDUSTRIAL**



## FREE BOOKLET

All types of TRANSISTORS • RECTIFIERS BRIDGES • SCR's • TRIACS INTEGRATED CIRCUITS F.E.T. • LIGHT DEVICES OVER 1500 DIFFERENT DEVICES



MORE DEVICES  
 NEW PRICES  
 NEW RANGES  
 THIS IS A MUST FOR ALL SEMI-CONDUCTOR USERS!

ENTIRELY NEW 1973 EDITION (ask for Booklet No. 36)  
**SEND FOR YOUR FREE COPY TODAY!**

INTEGRATED CIRCUITS, VERY IMPORTANT—ONLY BRANDED I.C.'s ARE TO THE FULL MANUFACTURERS' SPECIFICATIONS. ALL OTHERS ARE NOT. HENRY'S SELL ONLY BRANDED INTEGRATED CIRCUITS... FROM TEXAS... I.T.T. FAIRCHILD SIGNETICS... SO WHY BUY ALTERNATIVES OR UNDER SPEC. DEVICES WHEN YOU CAN PURCHASE THE GENUINE ARTICLE FROM US EX STOCK... NEED WE SAY MORE!

Type	1-	12-	30-	Type	1-	12-	30-
8N7400N	20	18	16	8N7446N	2-16	2-16	1-89
8N7401N	20	18	16	8N7447AN	1-80	1-80	1-57
8N7401AN	38	38	38	8N7448N	1-50	1-27	1-13
8N7402N	20	18	16	8N7450N	20	18	16
8N7403N	20	18	16	8N7451N	20	18	16
8N7403AN	38	38	38	8N7452N	20	18	16
8N7404AN	24	21	18	8N7454N	20	18	16
8N7405N	20	18	16	8N7460N	20	18	16
8N7405AN	44	44	38	8N7470N	33	30	27
8N7406N	40	38	35	8N7472N	33	30	27
8N7407N	40	38	35	8N7473N	44	41	37
8N7408N	25	22	19	8N7474N	48	48	42
8N7408AN	38	38	38	8N7475N	59	55	51
8N7409N	38	38	38	8N7476N	45	45	38
8N7409AN	44	44	38	8N7478N	80	70	60
8N7410N	20	18	16	8N7480N	40	30	27
8N7411N	25	23	21	8N7481N	1-25	1-10	95
8N7412N	28	28	28	8N7482N	87	80	72
8N7412AN	38	38	38	8N7483N	1-20	1-10	1-00
8N7413N	80	27	25	8N7485N	1-87	1-87	1-63
8N7414N	72	72	68	8N7486N	50	50	44
8N7416N	80	27	25	8N7489N	4-32	4-32	3-78
8N7417N	80	27	25	8N7490N	75	70	63
8N7420N	20	18	16	8N7491AN	1-10	1-00	90
8N7422N	28	28	28	8N7492N	75	70	63
8N7423AN	38	38	38	8N7493N	75	70	63
8N7425N	37	34	32	8N7494N	85	80	75
8N7426N	37	37	37	8N7495N	85	80	75
8N7427N	37	37	37	8N7496N	1-00	90	83
8N7428N	43	43	37	8N74100N	2-16	1-89	1-80
8N7430N	20	18	16	8N74104N	1-10	1-00	90
8N7432N	37	37	32	8N74105N	60	53	45
8N7433N	43	43	38	8N74107N	51	51	45
8N7433AN	57	57	50	8N74110N	57	57	50
8N7437N	48	43	37	8N74111N	86	86	75
8N7438N	48	43	37	8N74116N	2-16	2-16	1-89
8N7438AN	57	57	50	8N74119N	1-82	1-82	1-68
8N7440N	39	39	39	8N74120N	1-05	1-05	92
8N7441AN	85	79	73	8N74121N	57	57	50
8N7442N	85	79	73	8N74122N	80	80	70
8N7443N	1-50	1-27	1-13	8N74123N	1-44	1-44	1-28
8N7444N	1-50	1-27	1-13	8N74124N	69	69	60
8N7445N	2-16	2-16	1-89	8N74125N	80	80	70

PRICING OF 8N7400 SERIES IS CALCULATED ON THE TOTAL NUMBER ORDERED REGARDLESS OF MIX

5N74 (HIGH POWER), 5N74 (LOW POWER) series in stock. Send for List 36 free on request. Low Profile Sockets, 14 pin, 15p, 16 pin, 17p, 8 pin, 14p.

TBA 800 5 WATT I.C.  
 Suitable alternative to SL403D, 5/30 volt operated, 8/16 ohm 5 watt output.  
 With circuits and data £1.50.



SINCLAIR IC12  
 With circuits and data. 6 W IC with printed circuit board 28V operated, £1.80.



ZN414 IC  
 Integrated circuit radio as featured by many magazines. (PW Jan. 73 Reprint Ref. No. 19 for 10p), £1.20.




TOSHIBA POWER AND PREAMPLIFIER MODULES  
 TH9013P 20W power amplifier 22-0-22 or single 45V operated, £4.50.



TG9014P Stereo on two channel preamplifier, £1.50.  
 (Circuit book No. 42 price 10p).

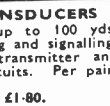ULTRASONIC TRANSDUCERS  
 Operate at 40kHz up to 100 yds. Ideal remote switching and signalling, complete with data transmitter and receiver, new I.C. circuits. Per pair, £5.90.  
 TA 960 I.C. with socket £1.80.



3015F 7 SEC.  
 IC size complete with data price £2 each or 4 for £7.  
 (Digital clock circuits Ref. No. 31, 15p).



TRANSISTORS—SPECIAL OFFERS  
 2N3055 25 47p each  
 100 100 42p each  
 500 500 39p each  
 1000 1000 34p each

AF117 25 15p each  
 100 100 13p each  
 500 500 12p each  
 1000 1000 10p each

ZENER DIODES  
 400m/w BZY88/ 702C (T05) 75  
 BZX83 From 709C (T05) 39  
 3.3V-33V, 10p 709C (DIL) 39  
 each. 723C (T09) 98  
 1-3W 5% Miniature Tubulars 723C (DIL) 90  
 728C (DIL) 45  
 IN4700 series. 728C (T09) 45  
 From 3.3V-33V, 741C (T05) 50  
 18p each. 741C (DIL) 50  
 10W. Std. 747C (T09) 1-00  
 Mounting ZS 747C (DIL) 1-00  
 5%, 40p each. 748C (DIL) 61

SILICON RECTIFIERS  
 1 amp series. IN4001 to IN4007. From 8p each.  
 1.5 amp. PL4001 to PL4007. From 8p each.  
 3 amp. PL7001/IN5400. From 14p each.  
 Send for full list 36.

MORE OF EVERYTHING AT HENRY'S  
 See pages 935, 936, and Back Cover of this magazine.  
**BEST VALUE**

TRIACS—Stud Mounting with accessories  
 3 AMP RANGE 1-11  
 Type P.I.V. Price ea.  
 SC35A 100V 80p  
 SC35B 200V 85p  
 SC35D 400V 90p  
 SC35E 500V £1.20

6 AMP RANGE  
 SC40A 100V 90p  
 SC40B 200V 95p  
 SC40D 400V £1.20  
 SC40E 500V £1.50

10 AMP RANGE  
 SC45A 100V £1.05  
 SC45B 200V £1.15  
 SC45D 400V £1.45  
 SC45E 500V £1.85

15 AMP RANGE  
 SC50A 100V £1.45  
 SC50B 200V £1.65  
 SC50D 400V £1.95  
 SC50E 500V £2.25

TRIACS—Additional Types  
 40430 TRIAC (T066) 85p  
 40669 TRIAC (Plastic) 90p  
 40486 TRIAC (T05) 75p

NEW RANGES BRIDGE RECTIFIERS  
 FEATURES SMALL SIZE & LOW COST  
 250 MA ± 5 AMP P.I.V.  
 B025/05 50V 16p  
 B025/10 100V 18p  
 ± x ± x in. dia.

1 AMP  
 Type P.I.V. Price ea.  
 B05/05 50V 20p  
 B05/10 100V 22p  
 B05/20 200V 23p  
 B05/40 400V 25p  
 B05/60 600V 27p  
 ± H x ± L x in. dia.

1 AMP  
 B1/05 50V 25p  
 B1/10 100V 25p  
 B1/20 200V 28p  
 B1/60 600V 30p  
 ± H x ± L x in. dia.

1 AMP  
 W005 50V 29p  
 W01 100V 30p  
 W02 200V 32p  
 W06 600V 35p  
 ± x in. tubular

2 AMPS  
 B2/05 50V 35p  
 B2/10 100V 40p  
 B2/20 200V 45p  
 B2/60 600V 50p  
 B2/100 1000V 55p  
 ± H x ± L x in. dia.

4 AMPS  
 B4/100 100V 55p  
 B4/200 200V 59p  
 B4/400 400V 65p  
 B4/600 600V 75p  
 B4/800 800V £1.00  
 ± H x ± L x in. dia.

6 AMPS  
 B6/05 50V 65p  
 B6/10 100V 70p  
 B6/20 200V 80p  
 B6/40 400V 90p  
 B6/60 600V £1.00  
 ± H x ± L x in. dia.

SILICON CONTROLLED RECTIFIERS  
 Type P.I.V. Price ea.  
 CR5 1/05AF 50V 30p  
 CR5 1/10AF 100V 30p  
 CR5 1/20AF 200V 35p  
 CR5 1/40AF 400V 45p  
 CR5 1/60AF 600V 55p

3 AMP (TO48)  
 CR5 3/05AF 50V 40p  
 CR5 3/10AF 100V 40p  
 CR5 3/20AF 200V 45p  
 CR5 3/40AF 400V 55p  
 CR5 3/60AF 600V 65p  
 5 AMP 400V 60p  
 CR5 5/400V 60p

7 AMP (TO48)  
 CR5 7/100 100V 60p  
 CR5 7/200 200V 67p  
 CR5 7/400 400V 85p  
 CR5 7/600 600V 95p

## TRANSISTORS—A selection

For full list send for booklet 36 today

£ p	£ p	£ p	£ p	£ p	£ p
AAZ13	10 BC169C	14 BY100	15 OC36	65 V405A	25 2N3614
AC107	35 BC182	12 BY127	15 OC44	18 ZX108	10 2N3702
AC128	20 BCY32	85 BZY13	35 OC45	18 ZX300	14 2N3714
AC187	20 BCY39	1-00 C106D	55 OC71	15 ZX302	18 2N3771
ACY17	35 BCY55	2-50 GET111	55 OC72	25 ZX500	15 2N3790
ACY39	65 BCY70	15 GET115	75 OC81	28 ZG301	40 2N3790
AD149	50 BCY82	13 L309K1	87 OC83	25 2N706	10 2N3866
AD161	39 BY12	80 MAT121	25 OC140	65 2N930	20 2N3903
AD162	39 BD124	80 MAT125	25 OC170	25 2N987	45 2N4062
AF117	20 BD131	45 MJE340	50 OC200	55 2N1132	25 2N4126
AF118	50 BF115	22 MJE520	65 OC202	60 2N1320	22 2N4126
AF139	33 BF180	33 MJE3055	75 OC210	60 2N1613	20 2N5457
AF186	44 BF194	13 MPF105	45 OC271	55 2N1671	100 25001
AF239	44 BF213	25 NP217	45 ORP12	45 2N2147	75 25026
AS737	30 BFX34	55 NKT404	60 ORP60	20 2N2160	69 25303
BA115	10 BFX88	22 OAS	60 P346A	25 2N2926	10 40230
BAX13	5 BFY50	20 OA81	10 TIL209	49 2N3053	20 40361
BC107	12 BFY51	20 OA200	8 TIP29A	29 2N3054	45 40361
BC108	12 BFY64	45 OA202	10 TIP30A	61 2N3055	45 40408
BC109	12 BFY90	75 OC210	85 TIP31A	61 2N3055	45 40408
BC109C	44 BFY36	6-25 OC20	1-25 TIP41A	74 2N3440	50 40486
BC113	16 BX520	15 OC28	65 TIP42A	90 2N3442	1-10 40636
BC147	12 BU105	2-20 OC35	55 TIS43	26 2N3525	80 40430

All types offered subject to availability. Prices correct at time of press. E. & O.E.

U.K. post, etc. 15p per order.

**Henry's RADIO LIMITED**  
 EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381  
 354-356 High Fidelity and Tape Equipment 01-402 5854/4736  
 309 PA-Disco-Lighting High Power Sound 01-723 6963  
 303 Special offers and bargains store  
 All mail to 303 Edgware Road, London W2 1BW

Open:-  
 9 am-6 pm  
 6 days a week  
 All stores open all day Saturday

# Henry's

PANEL METERS · TRANSFORMERS · CONTROLS · RELAYS  
IRONS · TOOLS · VALVES · POT CORES MOST TYPES OF COMPONENTS  
You need a catalogue! 55p post paid complete with Discount Vouchers



UK'S  
LARGEST RANGE  
OF KITS &  
GADGETS



## TEST EQUIPMENT MULTIMETERS

(carr., etc. 30p)  
200H (M210) 20k/V Slimline with case, £4.95  
THL33D 2k/V Robust with case, £4.95  
U437 10k/V Steel case. A.C. up to 40kHz, £4.95  
U4324 20k/V with A.C. current ranges, £8.00  
AF105 50k/V with leather case, £9.50  
U4313 20k/V A.C. current. Steel case, £10.50  
U4341 Plus built in transistor tester, £10.50  
Model 500 30k/V, £9.95

## OTHER EQUIPMENT

SE250B Pocket Signal Injector, £1.90, Carr. 15p  
SE500 Pocket Signal Tracer, £1.50, Carr. 15p  
TE15 Grid Dip Meter 440kHz—280MHz, £13.45, Carr. 30p  
TE40 A.C. Millivoltmeter 1-2MHz, £18.75, Carr. 35p  
TE65 28 Range Valve Voltmeter, £19.25, Carr. 40p  
TE20D 120kHz—500MHz RF Generator, £16.95, Carr. 40p  
TE22D 20Hz—200kHz Audio Generator, £18.75, Carr. 40p  
SE350A Deluxe Signal Tracer, £9.95, Carr. 20p  
SE400 Volt/ohms/R-C sub./RF field/RF gen., £11.25, Carr. 20p

## NEW REVOLUTIONARY SUPERTESTER 680R


680R Multi-tester, £18.50  
Accessories £

Transistor tester	11.00	Gauss meter	11.95
Electronic volt-meter	18.00	Signal Injector	5.95
Ampclamp	11.95	Phase sequence	5.95
Temperature probe	11.95	EHT Probe	5.95
		Shunts	4.50
		25/50/100A	each

## A SELECTION OF INTERESTING ITEMS

C3025 Compact transistor tester, £5.50, P. & P. 15p  
E1300 Mono mag cart preamp, £1.95, P. & P. 15p  
E1310 Stereo mag cart preamp, £4.95, P. & P. 25p  
Easiphone telephone amplifier, £6.15, P. & P. 25p  
LL1 Door Intercom with PU coil, £3.60, P. & P. 20p  
Chastalite (lights as you talk), £13.90, P. & P. 20p  
1kW Dimmer/controller, £3.00, P. & P. 10p  
9in Twin spring unit, for Reverbs, £2.75, P. & P. 15p  
16in Twin spring unit, for Reverbs, £6.50, P. & P. 25p  
Car Tachometer Electronic, £7.50, P. & P. 15p  
VHF Aircraft band corrector, £3.95, P. & P. 15p  
B2005 4 Ch. mic. mixer, £2.95, P. & P. 15p  
B2004 2 Ch. stereo mixer, £4.75, P. & P. 15p

## BUILD THIS RADIO

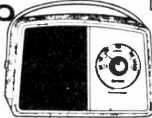

PORTABLE MW/LW RADIO KIT using Mullard RF/IF module. Features MW—bandsread for extra selectivity. Slow motion tuning. Fibre glass PVC cabinet. 600MW output. All parts £7.98 (battery 22p). Carr. etc. 32p.

## EXCLUSIVE: SPECIAL OFFERS

MW/LW CAR RADIO + or - earth with speaker and fixings. £6.50 carr/pack. 30p.  
8 TRACK CAR STEREO (- earth) with speakers, in pods and fixings. £12.50 carr/pack. 40p.  
HANIMAX HC1000 battery cassette recorder. £10.50 carr/pack. 25p.  
HANIMAX HC2000 battery/mains cassette recorder. £13.50 carr/pack. 30p.  
AKAI GXC40 stereo cassette recorder. £39.95 carr/pack. 50p

Pair Akai ADM microphones. £6.95 carr/pack. 20p.

5 WAVEBAND PORTABLE TWIN SPEAKER RADIO FM/MW/SW/ AIR-CRAFT — PUBLIC SERVICES. £10.45 carr/pack. 30p.

PORTABLE CASSETTE TAPE PLAYER—for car or carry around. £7.25 carr/pack. 20p.

HANIMAX POCKET CALCULATOR with % key. £33.50.

## SPECIAL PURCHASES

### AVOMETER MOVEMENTS

AVO 8 or 9 50mA MOVEMENTS. Ex Brand New AVO's. £3.50. Post 20p.

### UHF TV TUNERS CHANNELS 21 to 64

Brand new transistorised geared tuners for 625 Line Receiver IF output. £2.50. Post 20p.



## GARRARD BATTERY TAPE DECK

GARRARD 2 speed 9 volt tape decks. Fitted recorder/play and oscillator/erase heads. Wind and rewind controls. Takes up to 4in spools. Brand new complete with head circuits. £9.50. Carr. 30p.

### TOP QUALITY SLIDER CONTROLS

60mm stroke high quality controls complete with knobs (post, etc. 15p any quantity).  
Singles Log and Lin 5kΩ, 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ, 500kΩ, 1 Meg. 45p each.  
Ganged Log and Lin 10kΩ, 22kΩ, 50kΩ, 100kΩ, 250kΩ. 65p each.  
(Quantity discounts available). Complete with knobs.

### MARRIOT TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO '17' High Impedance, £2.00; '18' Med. Impedance, £2.00; Erase Heads for '17' and '18', 75p; '63' 2 track mono Hi imp., £1.75; '43' Erase Head for '63', 75p. (Post, etc. 15p any quantity).

R730/E73 2 Track Mono Record Erase Low Imp., 75p pair.

## SINCLAIR, MINIATURE AMPLIFIERS AND TUNER/DECODER

AMPLIFIERS (Carr. etc. 20p).


4-300	0.3 watt 9 volt	1.75
104	1 watt 9 volt	2.20
304	3 watt 9 volt	2.50
555	3 watt 12 volt	2.85
E1208	5 watt 12 volt	4.50
608	10 watt 24 volt	4.10
410	10 watt 28 volt	4.95
E1206	15 watt 30 volt	3.57
Z50	30 watt 45 volt	9.75
E1210	2 1/2 + 2 1/2 watt 12 volt	4.37
RE500	5 watt 1C mains operated Amplifier with controls	6.30
SAC14	7 + 7 watt Stereo with controls	8.00
SAC30	15 + 15 watt Stereo with controls	11.00

SINCLAIR PROJECT 60 (Carr. 20p)

Z30	3.57	Z50	4.37
Stereo 60	Preamplifier		7.97
PZ5			3.97
PZ6			6.37
PZ20	(for Z50)		4.77
TRANS			2.95
AFU			4.45

NEW SINCLAIR PROJECT 80

Stereo Preamplifier	9.50
Audio Filter Unit	5.50
£40 15 Watt Amplifier	4.30
Z60 25 Watt Amplifier	5.50
PZ5 Model for 1 on Z40	3.98
PZ6 Model (S. Tab.) 1 on Z40	6.25
PZ8 Model (S. Tab.) 1 on Z260	6.30
TRANSFORMER FOR PZ8	2.95

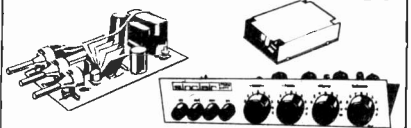


## POWER SUPPLIES FOR EVERY PURPOSE

(All cases unless stated chassis)

470C 6.7/9V 300mA, (Includes Multi-Adaptor for Tape Recorders etc.), £1.95, Post 20p  
Car Lighter Voltage Adaptors 300mA (State Voltage £1.95, Post 20p)  
SC202 3.16/7.5V 400mA, £3.25, Carr. 30p  
HC244R Stabilised version, £4.25, Carr. 30p  
P500 9V 500mA, £2.80, Post 20p  
P11 24V 500mA (chassis), £2.80, Post 20p  
P15 26/28V 1 amp (chassis), £2.70, Post 20p  
P1080 12V 1 amp (chassis), £3.25, Post 20p  
P1081 45V 0.9 amp (chassis), £4.40, Post 20p  
P12 4.5-12V 0.4-1 amp, £6.75, Post 30p  
SE101A 3.6/9/12V 1 amp (Stab.), £9.15, Post 25p  
RP164 6.7/9/12 1 amp (Stab.), £9.95, Post 30p


## EASY TO BUILD KITS BY AMTRON—EVERYTHING SUPPLIED

Model No.	£
310 Radio control receiver	2.98
300 4-channel R/C transmitter	5.95
345 Superhet R/C receiver	5.95
455 AM signal generator	12.33
65 Simple transistor tester	1.40
115 8W amplifier	1.40
120 12W amplifier	4.70
125 Stereo control unit	5.70
130 Mono control unit	3.60
605 Power supply for 115	4.55
610 Power supply for 120	4.55
615 Power supply for 2 x 120	5.73
230 AM/FM aerial amplifier	2.93
240 Auto packing light	5.90
275 Mic. preamplifier	6.08
570 LF generator 10Hz—1mHz	15.80
575 Sq. wave generator 20Hz—20kHz	14.60
590 SWR meter	12.85
620 Ni-CAD Charger 1-2-12V	8.00
630 STAB. Power supply 6-12V 0.25-0-1A	8.15
690 D.C. motor speed Gov.	2.87
700 Electronic Chaffinch	7.00
705 Windscreen wiper timer	10.70
760 Acoustic switch	6.85
780 Metal Detector (electronics only)	9.65
790 Capacitive burglar alarm	6.85
835 Guitar preamp	4.25
840 Delay car alarm	6.15
875 CAP. Discharge ignition for car engine (-Ve Earth)	13.15
80 Scope calibrator	2.25
255 Level indicator	6.15
525 120—160MHz VHF timer	11.30
715 Photo cell switch	7.70
795 Electronic continuity tester	4.30
860 Photo timer	13.25
871 Slide projector auto feed control	7.15
235 Acoustic alarm for driver	7.60
465 Quartz XTAL checker	8.75
220 Signal Injector	2.30
390 VOX	15.50
432 Testakit	19.30
670 Buffer Battery Charger	6.55
885 Capacitive Contact Alarm	6.25
850 Electronic Keyer	18.75
820 Electronic Digital Clock	58.50

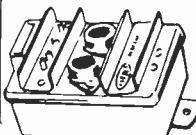

ALL KITS OFFERED  
SUBJECT TO STOCK  
AVAILABILITY

## BUILD THIS TUNER

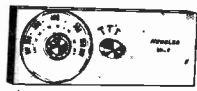

MW/LW Radio tuner to use with any amplifier. Features Mullard RF/IF module Ferrite aerial, built-in battery. Excellent results. Size: 7in x 2 1/2in x 3 1/2in. All parts £4.85. Carr. 15p.

## MULTI-USE AND RADIONIC KITS

10-1 10 Projects	£	3.60
50-1 50 Projects		8.00
150-1 150 Projects		13.20
Telephone Communicator		7.20
X20 20 (Elec.)		4.95
X40 40 (Radio) Projects		9.45
(Carr./Packing 40p)		

## ALL TRANSISTOR CIRCUITS WITH HANDBOOKS

All types offered subject to availability. Prices correct at time of press E & OE. 10% VAT to BE ADDED TO ALL ORDERS. UK post, etc. 15p per order unless stated.


# Henry's RADIO LIMITED

EDGWARE ROAD, W2

SEE FACING  
PAGE FOR  
ADDRESSES

## FIBRE OPTICS

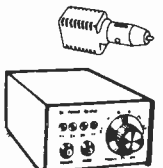0-01 dia. Mono Filament, £1.50 per 25 metre reel.  
0-13 dia. 64 Fibres Sheathed, £1.00 per metre, SP10Y—12V 0.4-1 amp, 15mm dia. Mares Tails, £9.50.



# Henry's

## DISCOUNT HI-FI, TV, TAPE AND CAR ENTERTAINMENT

Low prices means less VAT - Henry's give full guarantees and demonstrations for callers. Plus big savings. Also at Modern Electrics (Retail) Ltd., 120 Shaftesbury Avenue, W.1.—Your Sony dealer.

### STEREO AMPLIFIERS

(Carr./packing 50p)	£
AKAI: A45200	61.70
AA5500	78.50
AA5800	117.50
AMSTRAD: IC2000 Mk. II	29.50
4000 Mk. II	23.95
EAGLE: TSA149	25.10
TSA151	34.85
AA2	32.80
AA4	42.45
AA6	55.95
HOWLAND WEST: DA1000	22.45
HENELEC TEXAN: Kit	28.50
HENELEC TEXAN: Built	35.00
NIKKO: TRM300	25.95
TRM400	32.50
PIONEER: SA500A	34.25
ROTEL: RA211	32.65
RA311	41.15
RA611	60.80
RA810	75.75
RA1210	92.50
SINCLAIR: 2000	32.50
3000	28.95
TANDBERG: TA300	66.10
TELETON: SAQ206B	22.50
SAQ307	22.50
GA202	28.50

### STEREO RADIO TUNERS

(Carr./packing 50p)	£
AKAI: AT550	60.50
AT580	94.50
AMSTRAD: 3000	23.55
EAGLE: AA8	40.80
TS152	29.45
HENELEC: Stereo Kit	21.00
Built	24.95
HOWLAND WEST: DA1000T	25.35
PIONEER: TX500A	48.75
ROTEL: RT222	32.65
RT322	43.75
RT622	65.40
SINCLAIR: 2000	26.95
3000	26.95
TELETON: GT202	30.50

### DECODERS/SYNTHESIZERS

(Carr. etc. 30p)	£
DYNACO QUADRATOR	16.90
EAGLE: AA10	12.00
AA26	16.35
TATE 1	7.95
TATE 3 } Chassis	15.75
TATE 4	19.95
TATE 7 } Boxed	25.95

### MATCHED SPEAKER SYSTEMS

Recommended pairs 8 ohms	
RANK DOMUS	£
150	26.95 pair
175	33.75 pair
250	53.75 pair
MARSDEN HALL	£
110, 10W	22.50 pair
150, 15W	27.50 pair
200, 20W	34.50 pair
DYNACO	£
A10	43.00 pair
A25 } 20-60W	69.00 pair
A35	79.00 pair

WHARFEDALE  
Denton 2, 18W 27.20 pair  
Linton 2, 20W 32.65 pair  
Triton, 25W 40.80 pair  
Melton II 25 watts 51.80 pair  
LEAK  
150, 18W 32.65 pair  
250, 18W 44.30 pair  
CELESTION  
120, 20W 37.80 pair  
County, 25W 33.60 pair  
15, 30W 50.40 pair  
44, 44W 81.20 pair  
U.K.'s largest stockists for KEF Acoustic Research, Mordaunt Short and Cambridge audio speakers. In stock and on demonstration. Phone for keenest price

### STEREO MAGNETIC CARTRIDGES (Carr. etc. 15p)

SHURE	£								
M3Dm	£3.20; M44.7	£3.95; M44E	£4.25; M55E	£4.95; M44G	£4.20; M75/IB	£6.75; M75EDII	£8.50; M75EIII	£7.95; M75GII	£7.25.
GOLDRING	£								
G850	£2.85; G800	£3.95; G800H	£3.95; G800E	£5.95; G800SE	£10.00; G820	£6.70; G820E	£10.00; G820SE	£13.35.	
ADC	£								
Q36	£10.70; Q32	£8.70; Q30	£5.90.						
GRADO	£								
FTR	£5.25; F3E	£11.25; FTE	£8.25; MZ	£18.75.					

### EMPIRE

999REX 3-70; 999QUX 4-80; 999XEX 8-80; 999TEX £14.95.	
RONETTE	£
SM5007	4.60
SM5007E	4.60
SM500/E	6.95

### RECORD DECK PACKAGES

(Carr./packing 75p)	£
*Less cart. - rest with	
(HL): SP25 III/800 or H	15.95
(M): SP25 III/M7565	19.45
(HL): AP76/G800	25.35
(M): AP76/M7565	29.10
(HL): GL75 P/C	33.50
(HL): GL75 P/C G800	36.65
(HL): MP2615N	39.15
(HL): MP261 TPD1 G800	15.80
HT70(TPD) G800	19.50
RANK DOMUS	£
BD200	43.60
BD400	53.95
*Pioneer PL12D	31.75
*Thorens TD165	43.80
*Thorens TD 160C	50.80

### STEREO COMPACTS

complete with speakers	£
(Carr./packing £1-25)	
Fidelity: UA3	39.90
Sony: G2601K	125.50
Sony: G2615N	71.50
Sony: GX T4520KL	103.50
Sony: GX T4730KL	97.50
Philips GF908	102.75
GF825	159.95
RF836	57.20
GF826	41.75
RH81/RH421	84.95
RF839	55.95
GF829	39.95
GF815	47.75
GF808	68.75
RH814/RH411	96.75
GF603	19.95

### 8 TRACK STEREO HOME UNITS

(Carr./packing 70p)	£
Amerlec ACR301	£48.00
(With MW/FM stereo radio).	

### PORTABLE TV BATTERY-MAINS

(Carr./packing £1-00)	£
Elizabethan T9 (9in)	43.50
Crown 9TV (9in)	46.50
Elizabethan T12 (12in)	43.95
Teleton TW12 (12in)	46.95
Sony 10T150 (9/10in)	52.50

## CASSETTE PLAYER

FOR CAR - HOME AND AROUND



Actually the price far below the quality of the superb player. It is of beautiful quality both in sound and looks. Features wind-rewind volume and tone controls. Speaker is very good indeed. Comes complete with earphone, batteries. Full guarantee. Optional adaptor to run off car or mains.

MADE TO ORDER £12.50  
OUR PRICE £7.25  
CAR CIGAR LIGHTER £1.95  
PLUG-IN ADAPTOR £1.95  
MAINS ADAPTOR £1.95

### DOLBY/NRU

(Carr./packing 30p)	£
Teleton SNR100D	29.50
Philips N6720	15.00
Teac AN60/AN80/AN180 stocked.	

### BATTERY CASSETTE RECORDERS

(Carr. etc. 30p)	£
Amerlec 100	11.00
Wien ET1008	11.00
Philips EL3302	14.40
N2203	16.60
N2211	19.95
Sony M1101	14.65
M1102	12.95

### BATTERY/MAINS CASSETTE

(Carr. etc. 35p)	£
Wien RT452	13.65
Amerlec AC101	12.00
Elizabethan LZ315	12.25
Amerlec AC104	16.00
Philips N2204	20.75
N2205	29.50
Pye 9115	27.75
9118	21.20
Hitachi TRQ291	27.50
Sony M2000G	23.25
MR4010G	28.95
M4000G	49.50
BASF CC9201	37.25
Hitachi TRQ2335	49.50

### BATTERY/MAINS RADIO CASSETTE RECORDERS

(Carr. etc. 30p)	£
Amerlec ACR200	22.00
ACR201	30.00
Elizabethan LZ416	27.25
LZ516	29.10
BASF CC9301	30.75
Philips RR322	28.75
RR413	33.90
RR712	48.30
Sony M4141FG	43.20
M2400W	36.90
M2400FG	36.90
M4000S	65.15
Grundig C250	47.95
Hitachi TRK1240E	29.50
TR51161	35.00
KCT1210L	33.50

### STEREO RECORDER DECKS

(Carr./packing 50p)	£
Amerlec ACR301	£48.00
Philips N2506	44.50
Philips N2410	87.10
Pye 9145	44.50
Tandberg TCD3000	112.00
AKAI CS30D	50.65
CS33D	62.50
GC36D	65.15
GXC40D	57.40
GXC38D Dolby	81.45
GXC46D Dolby	89.15
GXC45D	74.30

TEAC: A250/A350/A450 stocked.


### Reel to Reel

AKAI 400DS	£2.50		
Tandberg 3321X/3341X	107.70		
Large range Akai/Tandberg/Revox/Teac stocked.			
8 Track	£		
AKAI CR81D	53.60		
CR80DS	93.65		
Pioneer: SE20A	£5.90;		
SE30A	£9.45; SE50	£10.95; PC51	£14.75;
SEL25	£7.90; SEL40	£18.60;	
SEL25	£11.15; SEL40	£18.60;	
Accessories:			
H1012/ JB3 Junction Box	£1.40;		
1B3DE Din Junction Box	£1.60;		
1B11D De Luxe Junction Box	£1.95; 0250		
Control Switch	£4.75.		
Control Boxes: G1301 (two phones) £2.62; G1305 Controller £2.15; FF17 2-pairs (Sliders) £6.25; Koss T4A £4.20; Koss T5A £4.95; Koss T10A £8.50; HW Mk.III Controller £6.90.			

### IN CAR ENTERTAINMENT

Car radios (carr./packg. 35p). MW/LW complete with speakers. Shira Touring £7; Shiramatic £9; Philips RN270 £13.65; RP305 £17.40; Pyle 2644 £26.75; 2062
--

BEST VALUE IN U.K.

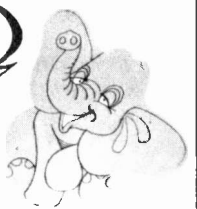

### STEREO RECORDERS

(Carr./packing 70p)	£
AKAI I721L	67.20
Cassette	
AKAI GXC40 Dolby	59.95
GXC46 Dolby	89.95
Philips N2400/RH411	63.75
N2401/RH411	74.50
N2401S/RH411	79.95
N2405/RH401	49.50
8 Track	
AKAI CR81	66.20
8 Track Player Decks (Carr./packing 35p)	
Elizabethan 8/LZI	£13.40
McDonald/BSR TDB85	12.75
TDB3V	15.25

### STEREO TUNER-AMPLIFIERS

(Carr./packing 75p)	£
AKAI AA8030	92.50
Goodmans Module 80	59.20
Goodmans Module 90	75.75
Goodmans One/Ten	88.50
Pioneer SX525	90.75
SX 626	124.75
Rotel RX150A	41.95
RX200A	53.95
RX400A	64.95
RX600A	90.00
RX800	114.50
RX154A	78.30
Tandberg TR200MPX	85.00
TR1000MPX	143.75
TR1010MPX	149.95
Teleton TSF55	57.70

**YOU CAN PAY BY BARCLAYCARD OR ACCESS**

For callers or by phone  
**01-402 4736**

Easy credit terms for callers to  
309 and 354-356

**ALSO STOCKED AND DEMONSTRATED**

Armstrong - Acoustic Research  
-Cambridge Audio - Leak - Lux  
-Marantz - Quad - Revox -  
-Sansui - Tandberg - Sugden -  
Wharfedale - Goodmans - Celestion  
Grundig - Kef - Teac - Bose -  
Sherwood

Call or phone 01-402 4736 for best prices

10% VAT to be added to ALL ORDERS. Prices and description correct at time of press E & OE. All goods offered subject to stock availability.

# Henry's RADIO LIMITED

**EDGWARE ROAD, W2**

404-406 Electronic Components and Equipment 01-402 8381  
354-356 High Fidelity and Tape Equipment 01-402 5854/4736  
309 PA - Disco - Lighting High Power Sound 01-723 6963  
303 Special offers and bargains store  
All mail to 303 Edgware Road, London W2 1BW

Open -  
9 am - 6 pm  
6 days a week  
All stores open  
all day Saturday

# ZIGGY'S 2001 ELECTRONICS Co. Ltd.



**SPECS. MULTIMETER U4324.** Sensitivity 20,000 OPV DC. Usually high current ranges. 3 amps a.c./d.c. Voltages AC3 to 900V d.c. 0-6 to 1200V. Resistance 500 ohms—20-200-2,000kΩ. Transmission level -10 to +12dB. This high quality instrument has diode protection. Complete with test leads, batteries, etc. £8.80 plus 25p P. & P.

**MULTIMETER 4313.** Similar to above but special features include 3 amp current range and instrument is housed in metal case with carrying handle. (Illustrated leaflet sent on request.) ONLY £10.45 plus 30p P. & P.



**SANWA JP-5D SPECS. 2000 OPV 1000V A.C.-D.C. 500 M/A current D.C.** A robust instrument with diode protection. Only £6.64. P. & P. 20p.

### MAINS TRANSFORMER

Eagle MT6, 6-0-6, 100 M/A, 95p plus 6p P. & P.  
MT12, 12-0-12, 50 M/A, 95p plus 10p P. & P.  
Eagle Type MT280 6-0-6, 250 M/A } All  
MT150 12-0-12, 150 M/A } £1.43 plus  
MT100 24-0-24, 100 M/A } 12p P. & P.  
R/S 13V 0.5 Amp C.T. } £1.40  
16-3V 0.3 Amp C.T. } plus 12p P. & P.  
Charger Types 9V, 17V.  
1 Amp £1.20 P. & P. 12p  
2 Amp £1.65 P. & P. 12p  
4 Amp £1.95 P. & P. 20p  
6 Amp £2.62 P. & P. 35p

### POTENTIOMETERS

log or lin less switch (& 1kΩ lin) 1-5 12p  
6-10 11p each. 11 plus 10p each.  
5kΩ 50kΩ 500kΩ }  
10kΩ 100kΩ 1mΩ }  
25kΩ 250kΩ 2mΩ }  
log or lin with switch 1-5 24p. 6-10 23p. 11 plus 20p.  
dual less switch 1-5 39p. 5-10 37p. 10 plus 35p.  
Any mix for Quantity Prices. P. & P. 7p.

### MINI LOUSPEAKERS

2 1/2 in 8Ω 50p. 5p P. & P.  
3 1/2 in 8Ω 50p. 5p P. & P.

### ENAMELLED COPPER WIRE

S.W.G. 16, 18, 20, 22, 24, 26, 2oz reels, 26p.  
28, 30, 32, 34, 36, 38, 40, 2oz reels, 36p.  
Postage 1-5, 10p. 6 plus, 15p.

### ANTEX SOLDERING IRON BITS

Chrome Type for 15 watt Models.  
1/2 in, 3/4 in, 1 in. All 26p each. Postage 5p.

### TELESCOPIC AERIAL

Six Section, Swivel Base. Only 20p. P. & P. 5p.

### TURNABLE SERVICES

**Headhells**  
Garrard SP25 Mk.I & II. Type M7 £1.10  
S.M.E. 52 Shell £2.77  
Thorens TP50 for TD150 £3.30  
Thorens TP60 for TD160 £3.30  
Golding PH7 for GL85 £3.80  
**Head Slides** Postage 5p. per item  
Garrard C1 for SL75 etc. 50p  
Garrard C2 for SP25 Mk.III, SL95 etc. 50p  
B.S.R. for MP60, 310, 510, 610 50p  
**Jockey Wheels**  
Garrard SP25 Type etc. 55p  
McDonald MP60 etc. 50p  
**Styls** Diamonds for Sonotone 65p  
9TA/HC LP/7B 95p  
9TA/HC LP/LP

### TRANSISTORS

BC107, 108, 109, all 9p each. Any six 50p.  
P. & P. 4p.

### EAGLE LT700 TRANSFORMER

40p. P. & P. 5p.  
NEW MULLARD DATA BOOK 1973/74  
30p. P. & P. 5p.


FOR SPEEDY DELIVERY OF THESE MINT CONDITION COMPONENTS PLEASE SEND C.V.O. TO ZIGGY'S 2001 ELECTRONICS CO. LTD., DEPT. P.E.3, 34 MABLEY STREET, LONDON, E.9. All prices include VAT, please add postage where indicated.

## JOSTY KITS SPECIAL OFFER

To celebrate our introduction to this famous range of Danish kits we are offering them free of VAT and postage. All models are available. For prices see the Radio Supplies advert or send a S.A.E. to us.
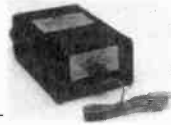
### BATTERY ELIMINATOR BARGAIN

The most versatile eliminator ever offered. Input from a.c. mains. Output selected by switch is 3, 4, 5, 6, 7, 5, 9 and 12V d.c. at 500mA. ONLY £3.60 (58p)



**NEW SINCLAIR CAMBRIDGE CALCULATOR** ONLY £26.45 (£3) Fully built

### SINCLAIR EQUIPMENT



Project 605 Stereo 80 Preamp £9.53 (£1 05)  
£18.90 (£2 30)  
Project 80 Tuner £8.95 (£1 10)  
Z40 £4.25 (63p)  
Project 80 Decoder £5.69 (77p)  
Z60 £5.38 (74p)  
Project 80 AFU £5.38 (74p)  
Z30 £3.50 (55p)  
Z50 £4.30 (65p)  
Z25 £3.47 (57p)  
Stereo 60 £7.80 (98p)  
Trans for PZ8 £2.95 (50p)  
2000 Amp £28 (£3)  
PZ6 £6.30 (83p)  
PZ8 £8.40 (84p)  
AFU £4.40 (65p)  
Q16 Speaker £5.90 (79p)


**PROJECT 60 KIT** £2.70 (49p)  
Our extremely popular kit contains the extra capacitors, din plugs and sockets, cable and fuseholder needed to complete Project 60.

**IC RADIO CHIP TBA651** £2.10 (32p)  
The world's most advanced IC radio chip. Contains RF Amp, oscillator, mixer, IF Amps, wide range AGC circuitry and voltage stabilizer. With data £2.10 (32p). Send S.A.E. for free leaflet. A kit of resistors, capacitors and IF filters is available to go with the chip for £1.75 (29p).
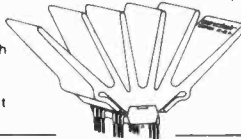
### SINCLAIR SUPER IC12

£2.10 (43p)

Supplied complete with free 44 page instruction booklet and printed circuit



### DE LUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.55 (26p). Stereo model with balance control £3.50 (46p).

### BASIC KIT FOR THE IC12

Contains components for P.C. board and volume and simple tone controls. Mono version £1.25 (24p). Stereo model with balance control £2.90 (40p).

### IC12 POWER KIT

A set of components to construct a 28V 0.5A power supply £2.47 (50p).

### LOUDSPEAKERS FOR THE IC12

5in 8 ohm £1.10 (27p). 5in x 8in 8 ohm £1.55 (37p)


### IC12 PREAMPLIFIER KITS

Type 1 for magnetic pickups, mics and tuners. Mono model £1.30 (24p). Stereo model £2.30 (34p). Type 2 for ceramic or crystal pickups. Mono model 60p (17p). Stereo £1.20 (23p).

SEND S.A.E. FOR FREE LEAFLET ON KITS
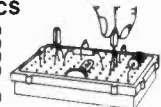
### S-DECS AND T-DECS

S-DECS £1.44 (25p)  
T-DECS £2.80 (40p)  
μ-DEC A £3.18 (43p)  
μ-DEC B £5.94 (71p)  
16 dit IC carriers £1.20 (17p)



## SWANLEY ELECTRONICS

32 Goldsel Road, Swanley, Kent

Please add the sum shown in brackets after the price to cover the cost of post and VAT. Official credit orders from local authorities and schools, etc., welcome. Lists 10p. Mail order only. No callers please.

# P.E. RONDO

## FULL SPECIFICATION KITS

Complete designer approved kits. Full data and even solder included. Top quality PCBs and components.

\* CBS-SQ MATRIX DECODER £8.00 Post Free + 80p VAT

\* PRE-AMP BOARD, COMPLETE £3.00 Post Free + 30p VAT

\* MASTER VOL/TONE/BAL. BD. £8.50 Post Free + 85p VAT

\* POWER AMP BOARD + HEAT-SINK £7.50 Post Free + 75p VAT

\* POWER SUPPLY BOARD £5.00 Post Free + 50p VAT

\* MAIN SMOOTHING CAPS £0.75 Post Free + 7p VAT

\* MAINS TRANSFORMER £6.25 Post Free + 62p VAT

\* PUNCHED CHASSIS £2.25 Post Free + 22p VAT

\* REAL WOOD CASE £1.75 Post Free + 17p VAT

\* HARDWARE PACK £2.00 Post Free + 20p VAT

\* CONTROL SECTION FASCIA £3.50 Post Free + 35p VAT

All other items will be offered as published  
TRADE ORDERS WELCOMED

## STUDIO ELECTRONICS

P.O. BOX No. 18, HARLOW, ESSEX CM18 6SH

Telephone: Harlow (02796) 25457

### ORDER—PLEASE SEND

CBS-SQ DEC.  ENCLOSED  
PRE-AMP   
MASTER VOL.  £.....  
POWER AMPS (2 for RONDO)  CHEQUE  
POWER SUPPLY CAPACITORS  P.O.  
TRANSFORMER  M.O.  
CHASSIS   
WOODEN CASE   
HARDWARE   
CONTROL FASCIA

NAME .....


ADDRESS .....

PE12

<p><b>NEW! NEW! NEW! NEW!</b></p> <p>An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.</p> <p><b>Method</b> Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light (No need to use ultra-violet) Spray with developer. Rinse and etch in normal manner.</p> <p>Light sensitive aerosol spray £1 Developer and Etchant 50p (plus postage)</p>		<p><b>SILICON P.N.P.</b></p> <table border="1"> <thead> <tr> <th>Part No.</th> <th>Voltage</th> <th>Frequency</th> <th>Price</th> </tr> </thead> <tbody> <tr><td>BCY71</td><td>45</td><td>200MHz</td><td>12p</td></tr> <tr><td>BFS92</td><td>100</td><td>70MHz</td><td>20p</td></tr> <tr><td>BFS95</td><td>40</td><td>70MHz</td><td>17p</td></tr> <tr><td>BFX12</td><td>25</td><td>210MHz</td><td>10p</td></tr> <tr><td>2N2906</td><td>60</td><td>200MHz</td><td>15p</td></tr> <tr><td>2N3702</td><td>40</td><td>100MHz</td><td>11p</td></tr> <tr><td>2N3703</td><td>50</td><td>100MHz</td><td>12p</td></tr> </tbody> </table>		Part No.	Voltage	Frequency	Price	BCY71	45	200MHz	12p	BFS92	100	70MHz	20p	BFS95	40	70MHz	17p	BFX12	25	210MHz	10p	2N2906	60	200MHz	15p	2N3702	40	100MHz	11p	2N3703	50	100MHz	12p	<table border="1"> <tbody> <tr><td>AF124</td><td>20</td><td>75MHz</td><td>20p</td></tr> <tr><td>AFY19</td><td>32</td><td>350MHz</td><td>20p</td></tr> <tr><td>ASY32</td><td>25</td><td>5MHz</td><td>10p</td></tr> <tr><td>ASZ21</td><td>15</td><td>450MHz</td><td>20p</td></tr> <tr><td>GET113</td><td>32</td><td>—</td><td>10p</td></tr> <tr><td>GET120</td><td>32</td><td>2 watts</td><td>10p</td></tr> <tr><td>OC123</td><td>50</td><td>1MHz</td><td>10p</td></tr> <tr><td>OCP70</td><td>Light-sensitive</td><td>—</td><td>20p</td></tr> <tr><td>2N1307</td><td>30</td><td>10MHz</td><td>15p</td></tr> <tr><td>2N1309</td><td>30</td><td>15MHz</td><td>15p</td></tr> <tr><td>2N443</td><td>60</td><td>150 watts</td><td>£1</td></tr> </tbody> </table>		AF124	20	75MHz	20p	AFY19	32	350MHz	20p	ASY32	25	5MHz	10p	ASZ21	15	450MHz	20p	GET113	32	—	10p	GET120	32	2 watts	10p	OC123	50	1MHz	10p	OCP70	Light-sensitive	—	20p	2N1307	30	10MHz	15p	2N1309	30	15MHz	15p	2N443	60	150 watts	£1	<table border="1"> <tbody> <tr><td>BXY27</td><td>Varactor Diode.</td><td>'S Band.</td><td>£1</td></tr> <tr><td></td><td>Cut-off.</td><td>70 GHz</td><td></td></tr> <tr><td>BXY28</td><td>Varactor Diode.</td><td>Cut-off.</td><td>£1</td></tr> <tr><td></td><td></td><td>100GHz</td><td></td></tr> <tr><td>BXY32</td><td>Frequency Multiplier.</td><td>'X Band.</td><td>£1</td></tr> <tr><td></td><td></td><td>150GHz</td><td></td></tr> <tr><td>BXY35A/C</td><td>Frequency Multiplier.</td><td>'X Band.</td><td>£1</td></tr> <tr><td></td><td></td><td>25GHz</td><td></td></tr> <tr><td>BXY36C/D</td><td>Frequency Multiplier.</td><td>'X Band.</td><td>£1</td></tr> <tr><td></td><td></td><td>75GHz</td><td></td></tr> <tr><td>BXY37C/D</td><td>Frequency Multiplier.</td><td>'X Band.</td><td>£1</td></tr> <tr><td></td><td></td><td>100GHz</td><td></td></tr> <tr><td>BXY38C/E</td><td>Frequency Multiplier.</td><td>'X Band.</td><td>£1</td></tr> <tr><td></td><td></td><td>120GHz</td><td></td></tr> <tr><td>BXY39C/D</td><td>Frequency Multiplier.</td><td>'X Band.</td><td>£1</td></tr> <tr><td></td><td></td><td>150GHz</td><td></td></tr> <tr><td>BXY40D/E</td><td>Frequency Multiplier.</td><td>'X Band.</td><td>£1</td></tr> <tr><td></td><td></td><td>180GHz</td><td></td></tr> <tr><td>BXY41C/D/E</td><td>Frequency Multiplier.</td><td>'X Band.</td><td>£1</td></tr> <tr><td></td><td></td><td>200 GHz</td><td></td></tr> </tbody> </table>		BXY27	Varactor Diode.	'S Band.	£1		Cut-off.	70 GHz		BXY28	Varactor Diode.	Cut-off.	£1			100GHz		BXY32	Frequency Multiplier.	'X Band.	£1			150GHz		BXY35A/C	Frequency Multiplier.	'X Band.	£1			25GHz		BXY36C/D	Frequency Multiplier.	'X Band.	£1			75GHz		BXY37C/D	Frequency Multiplier.	'X Band.	£1			100GHz		BXY38C/E	Frequency Multiplier.	'X Band.	£1			120GHz		BXY39C/D	Frequency Multiplier.	'X Band.	£1			150GHz		BXY40D/E	Frequency Multiplier.	'X Band.	£1			180GHz		BXY41C/D/E	Frequency Multiplier.	'X Band.	£1			200 GHz	
Part No.	Voltage	Frequency	Price																																																																																																																																																																
BCY71	45	200MHz	12p																																																																																																																																																																
BFS92	100	70MHz	20p																																																																																																																																																																
BFS95	40	70MHz	17p																																																																																																																																																																
BFX12	25	210MHz	10p																																																																																																																																																																
2N2906	60	200MHz	15p																																																																																																																																																																
2N3702	40	100MHz	11p																																																																																																																																																																
2N3703	50	100MHz	12p																																																																																																																																																																
AF124	20	75MHz	20p																																																																																																																																																																
AFY19	32	350MHz	20p																																																																																																																																																																
ASY32	25	5MHz	10p																																																																																																																																																																
ASZ21	15	450MHz	20p																																																																																																																																																																
GET113	32	—	10p																																																																																																																																																																
GET120	32	2 watts	10p																																																																																																																																																																
OC123	50	1MHz	10p																																																																																																																																																																
OCP70	Light-sensitive	—	20p																																																																																																																																																																
2N1307	30	10MHz	15p																																																																																																																																																																
2N1309	30	15MHz	15p																																																																																																																																																																
2N443	60	150 watts	£1																																																																																																																																																																
BXY27	Varactor Diode.	'S Band.	£1																																																																																																																																																																
	Cut-off.	70 GHz																																																																																																																																																																	
BXY28	Varactor Diode.	Cut-off.	£1																																																																																																																																																																
		100GHz																																																																																																																																																																	
BXY32	Frequency Multiplier.	'X Band.	£1																																																																																																																																																																
		150GHz																																																																																																																																																																	
BXY35A/C	Frequency Multiplier.	'X Band.	£1																																																																																																																																																																
		25GHz																																																																																																																																																																	
BXY36C/D	Frequency Multiplier.	'X Band.	£1																																																																																																																																																																
		75GHz																																																																																																																																																																	
BXY37C/D	Frequency Multiplier.	'X Band.	£1																																																																																																																																																																
		100GHz																																																																																																																																																																	
BXY38C/E	Frequency Multiplier.	'X Band.	£1																																																																																																																																																																
		120GHz																																																																																																																																																																	
BXY39C/D	Frequency Multiplier.	'X Band.	£1																																																																																																																																																																
		150GHz																																																																																																																																																																	
BXY40D/E	Frequency Multiplier.	'X Band.	£1																																																																																																																																																																
		180GHz																																																																																																																																																																	
BXY41C/D/E	Frequency Multiplier.	'X Band.	£1																																																																																																																																																																
		200 GHz																																																																																																																																																																	
<p><b>NEWER THAN NEW!!!</b></p> <p>Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.</p> <table border="1"> <tbody> <tr><td>75mm x 100mm</td><td>33p</td></tr> <tr><td>150mm x 100mm</td><td>66p</td></tr> <tr><td>150mm x 200mm</td><td>£1.32</td></tr> </tbody> </table>		75mm x 100mm	33p	150mm x 100mm	66p	150mm x 200mm	£1.32	<p><b>SILICON N.P.N.</b></p> <table border="1"> <tbody> <tr><td>BC108</td><td>30</td><td>150MHz</td><td>10p</td></tr> <tr><td>BC109</td><td>30</td><td>150MHz</td><td>10p</td></tr> <tr><td>BF179</td><td>225</td><td>125MHz</td><td>40p</td></tr> <tr><td>BF180</td><td>30</td><td>625MHz</td><td>25p</td></tr> <tr><td>BFW58</td><td>80</td><td>80MHz</td><td>15p</td></tr> <tr><td>BFX43</td><td>30</td><td>500MHz</td><td>20p</td></tr> <tr><td>BFX86</td><td>40</td><td>50MHz</td><td>17p</td></tr> <tr><td>BFY53</td><td>30</td><td>50MHz</td><td>10p</td></tr> <tr><td>BXS19</td><td>40</td><td>500MHz</td><td>10p</td></tr> <tr><td>BXS67</td><td>30</td><td>200MHz</td><td>12p</td></tr> <tr><td>2N697</td><td>60</td><td>40MHz</td><td>12p</td></tr> <tr><td>2N709</td><td>15</td><td>900MHz</td><td>30p</td></tr> <tr><td>2N718</td><td>60</td><td>60MHz</td><td>12p</td></tr> <tr><td>2N753</td><td>25</td><td>250MHz</td><td>12p</td></tr> <tr><td>2N744</td><td>20</td><td>300MHz</td><td>12p</td></tr> <tr><td>2N1613</td><td>75</td><td>60MHz</td><td>17p</td></tr> <tr><td>2N2220</td><td>60</td><td>250MHz</td><td>15p</td></tr> <tr><td>2N3053</td><td>60</td><td>100MHz</td><td>17p</td></tr> <tr><td>2N3707</td><td>30</td><td>—</td><td>12p</td></tr> <tr><td>2N5179</td><td>20</td><td>900MHz</td><td>40p</td></tr> </tbody> </table>		BC108	30	150MHz	10p	BC109	30	150MHz	10p	BF179	225	125MHz	40p	BF180	30	625MHz	25p	BFW58	80	80MHz	15p	BFX43	30	500MHz	20p	BFX86	40	50MHz	17p	BFY53	30	50MHz	10p	BXS19	40	500MHz	10p	BXS67	30	200MHz	12p	2N697	60	40MHz	12p	2N709	15	900MHz	30p	2N718	60	60MHz	12p	2N753	25	250MHz	12p	2N744	20	300MHz	12p	2N1613	75	60MHz	17p	2N2220	60	250MHz	15p	2N3053	60	100MHz	17p	2N3707	30	—	12p	2N5179	20	900MHz	40p	<p><b>HIGH FREQUENCY, POWER</b></p> <table border="1"> <tbody> <tr><td>BFR64</td><td>40</td><td>1200MHz</td><td>£1</td></tr> <tr><td>BLY89A</td><td>35</td><td>650MHz</td><td>£5</td></tr> <tr><td>BLY93A</td><td>60</td><td>500MHz</td><td>£5</td></tr> <tr><td>BLY218</td><td>36</td><td>1200MHz</td><td>£2</td></tr> <tr><td>2N709</td><td>15</td><td>800MHz</td><td>15p</td></tr> <tr><td>2N3926</td><td>36</td><td>250MHz</td><td>£1</td></tr> </tbody> </table>		BFR64	40	1200MHz	£1	BLY89A	35	650MHz	£5	BLY93A	60	500MHz	£5	BLY218	36	1200MHz	£2	2N709	15	800MHz	15p	2N3926	36	250MHz	£1	<p><b>MICROWAVE DEVICES</b></p> <table border="1"> <thead> <tr> <th>Part No.</th> <th>Price</th> </tr> </thead> <tbody> <tr><td>CL8300</td><td>Gunn effect oscillator.</td><td>£40</td></tr> <tr><td></td><td>9.4GHz</td><td>12p</td></tr> <tr><td>CL8370</td><td>Gunn effect oscillator.</td><td>£10</td></tr> <tr><td></td><td>9.5GHz</td><td>12p</td></tr> <tr><td>CL8380</td><td>Gunn effect oscillator.</td><td>£10</td></tr> <tr><td></td><td>10.5GHz</td><td>12p</td></tr> <tr><td>CL8390</td><td>Gunn effect oscillator.</td><td>£10</td></tr> <tr><td></td><td>11.5GHz</td><td>15p</td></tr> <tr><td>CL8430</td><td>Gunn effect oscillator.</td><td>£40</td></tr> <tr><td></td><td>9.35GHz</td><td>12p</td></tr> <tr><td>CL8450</td><td>Gunn effect oscillator.</td><td>£40</td></tr> <tr><td></td><td>9.35GHz</td><td>12p</td></tr> <tr><td>CL8470</td><td>Gunn effect oscillator.</td><td>£40</td></tr> <tr><td></td><td>9.35GHz</td><td>10p</td></tr> </tbody> </table>		Part No.	Price	CL8300	Gunn effect oscillator.	£40		9.4GHz	12p	CL8370	Gunn effect oscillator.	£10		9.5GHz	12p	CL8380	Gunn effect oscillator.	£10		10.5GHz	12p	CL8390	Gunn effect oscillator.	£10		11.5GHz	15p	CL8430	Gunn effect oscillator.	£40		9.35GHz	12p	CL8450	Gunn effect oscillator.	£40		9.35GHz	12p	CL8470	Gunn effect oscillator.	£40		9.35GHz	10p		
75mm x 100mm	33p																																																																																																																																																																		
150mm x 100mm	66p																																																																																																																																																																		
150mm x 200mm	£1.32																																																																																																																																																																		
BC108	30	150MHz	10p																																																																																																																																																																
BC109	30	150MHz	10p																																																																																																																																																																
BF179	225	125MHz	40p																																																																																																																																																																
BF180	30	625MHz	25p																																																																																																																																																																
BFW58	80	80MHz	15p																																																																																																																																																																
BFX43	30	500MHz	20p																																																																																																																																																																
BFX86	40	50MHz	17p																																																																																																																																																																
BFY53	30	50MHz	10p																																																																																																																																																																
BXS19	40	500MHz	10p																																																																																																																																																																
BXS67	30	200MHz	12p																																																																																																																																																																
2N697	60	40MHz	12p																																																																																																																																																																
2N709	15	900MHz	30p																																																																																																																																																																
2N718	60	60MHz	12p																																																																																																																																																																
2N753	25	250MHz	12p																																																																																																																																																																
2N744	20	300MHz	12p																																																																																																																																																																
2N1613	75	60MHz	17p																																																																																																																																																																
2N2220	60	250MHz	15p																																																																																																																																																																
2N3053	60	100MHz	17p																																																																																																																																																																
2N3707	30	—	12p																																																																																																																																																																
2N5179	20	900MHz	40p																																																																																																																																																																
BFR64	40	1200MHz	£1																																																																																																																																																																
BLY89A	35	650MHz	£5																																																																																																																																																																
BLY93A	60	500MHz	£5																																																																																																																																																																
BLY218	36	1200MHz	£2																																																																																																																																																																
2N709	15	800MHz	15p																																																																																																																																																																
2N3926	36	250MHz	£1																																																																																																																																																																
Part No.	Price																																																																																																																																																																		
CL8300	Gunn effect oscillator.	£40																																																																																																																																																																	
	9.4GHz	12p																																																																																																																																																																	
CL8370	Gunn effect oscillator.	£10																																																																																																																																																																	
	9.5GHz	12p																																																																																																																																																																	
CL8380	Gunn effect oscillator.	£10																																																																																																																																																																	
	10.5GHz	12p																																																																																																																																																																	
CL8390	Gunn effect oscillator.	£10																																																																																																																																																																	
	11.5GHz	15p																																																																																																																																																																	
CL8430	Gunn effect oscillator.	£40																																																																																																																																																																	
	9.35GHz	12p																																																																																																																																																																	
CL8450	Gunn effect oscillator.	£40																																																																																																																																																																	
	9.35GHz	12p																																																																																																																																																																	
CL8470	Gunn effect oscillator.	£40																																																																																																																																																																	
	9.35GHz	10p																																																																																																																																																																	
<p><b>SPECIAL OFFER</b></p> <p><b>UNI-JUNCTION TRANSISTOR SIMILAR TO 2N2646 25p</b></p>		<p><b>GERMANIUM P.N.P.</b></p> <table border="1"> <tbody> <tr><td>ACY44</td><td>50</td><td>1MHz</td><td>£1</td></tr> <tr><td>ADY26</td><td>80</td><td>75 watts</td><td>10p</td></tr> </tbody> </table>		ACY44	50	1MHz	£1	ADY26	80	75 watts	10p	<p><b>20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108, ETC.</b></p> <p>POSTAGE 20p      PACK No. 5</p>		<p><b>5 COMPUTER PANELS CONTAINING MASSES OF DIODES, TRANSISTORS, INDUCTORS, RESISTORS AND CAPACITORS</b></p> <p>POSTAGE 27p      PACK No. 7</p>																																																																																																																																																					
ACY44	50	1MHz	£1																																																																																																																																																																
ADY26	80	75 watts	10p																																																																																																																																																																
<p><b>£1</b> 100 1/2 WATT RESISTORS 100 CERAMIC CAPACITORS 100 DIODES</p> <p>POSTAGE 20p      PACK No. 1</p>		<p><b>£1</b> 1 VEROBOARD CUTTER 5 2 1/4" x 9" 15 BOARDS 50 SQ. IN. "ODD PIECES" VERO</p> <p>POSTAGE 20p      PACK No. 3</p>		<p><b>£1</b> 1 TRANSISTORISED SIGNAL TRACER KIT 1 TRANSISTORISED SIGNAL INJECTOR KIT</p> <p>POSTAGE 20p      PACK No. 6</p>		<p><b>£1</b> 100 RESISTORS 100 CERAMIC CAPACITORS 100 POLYSTYRENE CAPACITORS</p> <p>POSTAGE 20p      PACK No. 8</p>																																																																																																																																																													

POSTAGE (MINIMUM) 20P PER ORDER

ALL GOODS PLUS 10% V.A.T.

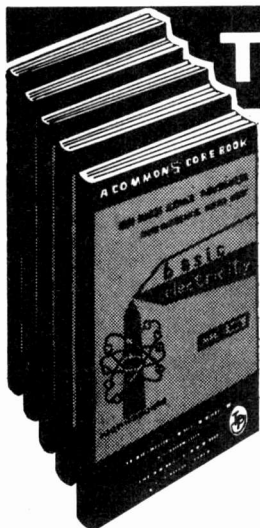

# The Pictorial Method

## BASIC ELECTRICITY (5 vols) ELECTRONICS (6 vols) TELEVISION (3 vols)

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

**YOUR 100% GUARANTEE**

Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

### WHAT READERS SAY

I am very pleased with the books for they are of great assistance to me in my employment.

S.A.K., Luton

These books are, without a doubt, the best explanatory books that I have ever possessed.

M. J., Sunderland

Basic Electronics received today. Excellent—would you now please send Basic Electricity.

E.Q., Blackpool

I am very pleased with these manuals: they give the best instruction I have ever had on the subject yet.

K.J., Grays

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £4.50

BASIC ELECTRONICS 6 parts £5.40

BASIC TELEVISION 3 parts £3.60

Tick Set(s) required.

Prices include Postage and Packing.

**YOUR 100% GUARANTEE.** If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME .....

BLOCK LETTERS


FULL POSTAL.....

ADDRESS .....

**POST NOW FOR THIS OFFER!**


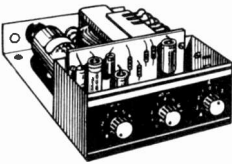
## PRICES NOW INCLUDE VAT SUPERSOUND 13 HI-FI MONO AMPLIFIER




A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz  $\pm$  3db. Fully integrated pre-amplifier stage with

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, esutechone panel, input and output plugs. Overall size 3in high  $\times$  6in wide  $\times$  7 1/2in deep. A.C. 200/250V. P. & P. 40p.

**PRICE £11.60**

## DE LUXE STEREO AMPLIFIER

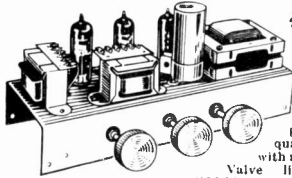

A.C. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up: -2  $\times$  ECL86 Triode Pentodes.

1  $\times$  E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 5 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in.  $\times$  4in.  $\times$  4in. Overall height including valves 5in. Ready built and tested to a high standard. **Price £9.90**, P. & P. 50p.

## NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 7 1/2V and 9V and 12V at 1 amp continuous (14 amp intermittent). Fully fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6"  $\times$  3 1/2"  $\times$  2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

**PRICE £5** P. & P. 35p.

**BLACK ANODISED 16g. ALUMINIUM HEAT SINKS.** For TO3, complete with mica's and bushes. Size 2 1/2in  $\times$  3in approx. 25p pair. P. & P. 6p.

**HIGH GRADE COPPER LAMINATE BOARDS.** 8"  $\times$  6". 5 for 55p. P. & P. 23p.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-13-20-25-30-35-40-60V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amp full wave. Size 3inL  $\times$  3 1/2inW  $\times$  3inD. Price £2.10 P. & P. 40p.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240V Sec. 9-0-9 at 500mA. £1 P. & P. 25p. Pri. 200/240V Sec. 12-0-12 at 1 amp. £1.10 P. & P. 26p. Pri. 200/240V Sec. 10-0-10 at 2 amp. £1.65 P. & P. 30p.

**GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER.** For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/4  $\times$  1 1/4  $\times$  1/2in. Brand new complete with instructions. Price £1.1 P. & P. 15p.

**3 REFERENCE ENCYCLOPEDIAS FOR ELECTRONIC ENGINEERS AND DESIGNERS,** covering between them, transistor characteristics, diode and transistor equivalents. Many thousands of up-to-date European types listed.

Diode Equivalents 80p  
Transistor Equivalents 80p  
Transistor Characteristics 11-90  
All three together 42-80  
POST FREE

## HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A trust for servicemen and home constructors. Includes many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.  
**NEW ISSUE - Thyristor, Triac, Diac, etc. encyclopedias** 95p Post Free.

Open 9-5.30 Mon. to Fri.  
9-5 Sat. Early closing Wed.

A few minutes from South Wimbledon Tube Station.

**CENTRE ZERO MINIATURE MOVING COIL METER.** 100uA for balance or tuning. Approx. size 1in  $\times$  1in  $\times$  1/2in. Limited number 88p. P. & P. 12p.

**RECORD PLAYER BARGAINS**  
Mains models. All brand new in maker's packing.  
**LATEST B.B.R. C109/C129 AUTOCHANGER UNITS.** With latest stereo/mono compatible cartridge £7.60 plus 50p P. & P.  
**Garrard SP25 Mk. III** with heavy precision machined die cast turntable. £10.56. Carr. 55p.

**PRECISION ENGINEERED PLINTHS**  
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025ST, 2500, 3000, 3500, 5100, SP25 II and III, SL65B, AT50, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12 1/2in  $\times$  14 1/2in  $\times$  3 1/2in high (approx. 7 1/2in high, including rigid smoked acrylic cover). P. & P. 70p. **Now only £4.95**

**LATEST ACOS GP91/15C Mono Compatible Cartridge** with T/O stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 15p.

**SONOTONE STEREO COMPATIBLE STEREO CARTRIDGE** T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.80. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.80. P. & P. 15p.  
**LATEST RONETTE T/O Stereo Compatible Cartridge** for EP/LP/Stereo/78. £1.63. P. & P. 15p.  
**LATEST RONETTE T/O Mono Compatible Cartridge** for EP/LP/78 mono/stereo records on mono equipment £1.50. P. & P. 15p.

**QUALITY RECORD PLAYER AMPLIFIER MK II**  
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w.  $\times$  5 1/2 in. h. Ready built and tested. **PRICE £4.40**. P. & P. 50p. **ALSO AVAILABLE** mounted on board with output transformer and speaker. **PRICE £5.85**. P. & P. 60p.

## SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Teganlyn front panel. Size 16in high  $\times$  10 1/2in wide  $\times$  6in deep. Fitted with E.M.I. Ceramic Magnet 13in  $\times$  8in bass unit, two H.F. tweeter units and crossover. Max. power handling 10W. Available 3, 8 or 15 ohm impedance.

**Our Price £9.25** Carr. 75p.

**CABINET AVAILABLE SEPARATELY £4.95**, Carr. 65p. Also available in 8 ohm with EMI 13in  $\times$  8in, bass speaker with parasitic tweeter. £7.15. Carr. 75p.

## HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide  $\times$  3in. deep  $\times$  6in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer.

**OUR ROCK BOTTOM BARGAIN PRICE £3.30** P. & P. 40p.

## LOUDSPEAKER BARGAINS

5in 3 ohm £1.05, P. & P. 15p. 7  $\times$  4in 3 ohm £1.15, P. & P. 20p. 10  $\times$  6in 3 or 15 ohm £1.90, P. & P. 30p. E.M.I. 8  $\times$  3in 3 ohm with high flux magnet £1.62, P. & P. 20p. E.M.I. 13  $\times$  8in with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £2.50, P. & P. 30p. E.M.I. 13  $\times$  8in, 3 or 8 or 15 ohm with twin inbuilt tweeters and crossover network £4.65. P. & P. 30p.

**EMI CERAMIC MAGNET HEAVY DUTY TWEETER.** approx. 3 1/2in. Av. 3 or 8 or 15 ohms. £1.25 plus 20p P. & P. **BRAND NEW.** 12in 15W H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiFiLux ceramic ferroba magnet assembly £7.50. (Guitar models: 25w £7.50, 35w £8.55. P. & P. 45p each).



## SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUDSPEAKERS. With large ceramic magnet and plasticised cone surround. 3 ohm impedance. £2.70. P. & P. 35p.

Also available specification as above but size 10"  $\times$  6" £2.70 and size 8" round £2.60 P. & P. 35p.

LIMITED NUMBER - EM1 2 1/2" 8 ohm Tweeters. Mounted on flat bracket, size 2 1/2" wide  $\times$  7 1/2" long. 70p per pair plus 15p P. & P. Exp equipment but new and tested. 70p per pair plus 15p P. & P.

12in "RA" TWIN CONE LOUDSPEAKER 10 watts peak handling, 3, 8 or 15 ohm, £2.45. P. & P. 36p. 35 ohm SPEAKERS 3". ONLY 70p. P. & P. 25p.


"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 1 1/2in  $\times$  14 1/2in  $\times$  1 1/2in deep. Weight 1lb2oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only 36-55 each. P. & P. 34p.

## HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo jn jack plug. Frequency response 30-16,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. **PRICE £8.30**. P. & P. 25p.
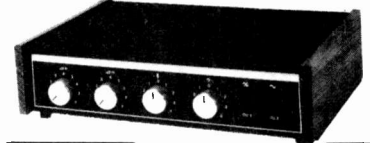
## HAVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



**NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EASIER CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 16 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 8 ohms. Frequency response  $\pm$  3dB 20-20,000Hz. Sensitivity better than 80mV into 16 Ohm. Full power bandwidth  $\pm$  3dB 12-15,000Hz. Bass boost approx. to  $\pm$  12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide  $\times$  8" deep  $\times$  2 1/2" high.


Fully tested 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

**PRICES AMPLIFIER KIT, £11.55** P. & P. 25p. (Magnetic input components 33p extra)

**POWER PACK KIT, £3.30** P. & P. 35p. **CABINET, £3.30** P. & P. 35p.

(Post Free if all units purchased at same time). Full sales service. Also available ready built and tested, £28-10. Post Free.

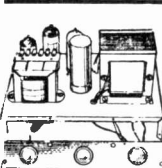Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque use, etc.



## 3-VALVE AUDIO AMP. HA3 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in.  $\times$  4in.  $\times$  4 1/2in. h. Incorporates ECC83, PL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel, fully drilled and lends itself to remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only **£5.50**. P. & P. 45p.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA3A above but employs entirely different and advanced circuitry. Complete set of parts, etc. **£4.50**. P. & P. 45p.

## 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 ohm speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 15p plus S.A.E. (Free with parts). All parts sold separately. ONLY **£3.50**. P. & P. 60p. Also available ready built and tested **£18.10**. P. & P. 70p.

**VYNAIR & BEKINE SPEAKERS & CABINET FABRICS** app. 5 1/2in. wide. Our Price 85p yd. length. P. & P. 25p per yd. (min. 1 yd.). S.A.E. for samples.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

## HARVERSON SURPLUS CO. LTD.

Dept. PE, 170 High St., Merton, London, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

# YATES ELECTRONICS

(FLITWICK) LTD.

DEPT. PE, ELSTOW STORAGE DEPOT  
KEMPSTON HARDWICK  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the  
components listed will be sent free on request.  
10p stamp appreciated.

CALLERS WELCOME Mon.-Sat. 9 a.m.-5 p.m.  
PLEASE ADD 10% VAT

## RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.  
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.  
1W 2% ELECTROSIL TR5

Power watts	Tolerance	Range	Values available	Price
↓	5%	4.7Ω-2.2MΩ	E24	1-99 100+
↓	10%	3.3MΩ-10MΩ	E12	1p 0-8p
↓	2%	10Ω-1MΩ	E24	1p 0-8p
↓	10%	1Ω-3.9Ω	E12	1p 0-8p
↓	5%	4.7Ω-1MΩ	E12	1p 0-8p
↓	10%	1Ω-10Ω	E12	6p 5.5p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ±W, lin ±W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.  
mounting (0.1 matrix).  
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 7p each.

## TRANSISTORS

AC107	15p	AF139	32p	BF177	20p	OC45	12p	2N3710	11p
AC126	12p	AF178	32p	BF178	32p	OC70	12p	2N3711	11p
AC127	15p	AF180	40p	BF179	32p	OC71	12p	2N3819	32p
AC128	15p	AF181	40p	BF180	32p	OC72	12p	2N4062	12p
AC131	12p	BC107	12p	BF181	32p	OC81	12p	2N4286	20p
AC132	12p	BC108	12p	BF194	14p	OC82D	12p	2N4289	20p
AC176	15p	BC109	12p	BF195	14p	2N2646	60p	40360	35p
AC187	22p	BC147	12p	BF197	15p	2N2904	20p	40361	35p
AC188	22p	BC148	12p	BF200	32p	2N2926	10p	40362	40p
AD140	50p	BC149	12p	BFY50	20p	2N3054	50p	40408	40p
AD149	45p	BC157	14p	BFY51	20p	2N3055	60p	ZTX108	15p
AD161	33p	BC158	14p	BFY52	20p	2N3702	13p	ZTX300	15p
AD162	36p	BC159	14p	BUY105		2N3703	12p	ZTX302	20p
AF114	20p	BC187	22p		£2.25	2N3704	12p	ZTX500	15p
AF115	20p	BD131	75p	OC26	45p	2N3705	12p	ZTX503	20p
AF116	20p	BD132	75p	OC28	50p	2N3706	11p		
AF117	20p	BD133	75p	OC35	50p	2N3707	12p		
AF118	38p	BF115	25p	OC42	12p	2N3708	10p		
AF126	20p	BF173	20p	OC44	12p	2N3709	11p		

## ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

## WIRE WOUND POTS, 3W, 10, 25,

50Ω and decades to 100kΩ, 35p.

## DIODES

### RECTIFIER

BY127	1250V	1A	12p
IN4001	50V	1A	7p
IN4002	100V	1A	8p
IN4004	400V	1A	8p
IN4006	800V	1A	10p
IN4007	1000V	1A	10p

### SIGNAL

OA85	7p
OA90	5p
OA91	5p
QA202	7p
IN4148	8p
BA114	8p

## BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2 1/2in = 10p; 9in x 2in = 7p

## SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm.

SINGLE 10K, 25K, 100K log, or lin, 40p.

DUAL GANG, 10K + 10K etc. log, or lin, 60p.

KNOB FOR ABOVE 12p.

FRONT PANEL 65p.

18 Gauge panel 12in x 4in with slots cut for use with slider pots. Grey or matt black finish complete with fixings for 4 pots.

## THERMISTORS

VA10555	15p
VA10665	15p
VA1077	15p
R53	£1.35

## THYRISTORS

2N5060 50V 0.8A	30p.
2N5064 200V 0.8A	47p.
CRS1/40 400V 1A	25p.
106F 50V 4A 40p, 106D 400V 4A 65p.	

## MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2p. 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 3p. 0.047μF, 0.068μF, 0.1μF, 4p. 0.15μF, 6p. 0.22μF, 7p. 0.33μF, 10p. 0.47μF, 13p.

160V: 0.1μF, 0.15μF, 0.22μF, 0.33μF, 0.47μF, 0.68μF, 3p. 0.1μF 3p. 0.15μF 4p. 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 7p. 0.68μF, 11p. 1.0μF, 13p.

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p. 0.033μF, 0.047μF, 0.068μF, 3p. 0.1μF, 4p. 0.15μF, 0.22μF, 5p. 0.33μF, 6p. 0.47μF, 8p. 0.68μF, 11p. 1.0μF, 13p. 1.5μF, 20p. 2.2μF, 24p.

## ELECTROLYTIC CAPACITORS—MULLARD O15/6/7

(μF/V) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/6, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6, 68/16, 100/4, 100/10, 100/25, 330/10, 470/6, 3, 7p. 68/63, 150/40, 220/4, 220/6, 3, 220/16, 330/4, 6p. 47/63, 100/40, 150/25, 220/25, 330/10, 470/6, 3, 7p. 68/63, 150/40, 220/4, 330/16, 1.000/4, 10p. 470/10, 470/25, 330/10, 100/63, 150/63, 220/63, 1.000/10, 12p. 470/25, 680/16, 1.500/6, 13p. 470/40, 680/25, 1.000/16, 1.500/10, 2.200/6, 3, 18p. 330/63, 680/40, 1.000/25, 1.500/16, 2.200/10, 3.300/6, 3, 4.700/4, 21p.

## SOLID TANTALUM BEAD CAPACITORS

0.1μF	35V	2.2μF	35V	22μF	16V	12p
0.22μF	35V	4.7μF	35V	33μF	10V	
0.47μF	35V	6.8μF	25V	47μF	6.3V	
1.0μF	35V	10μF	25V	100μF	3V	

## VEROBOARD

2 1/2 x 3 1/2	0-1	0-15
2 1/2 x 5	24p	24p
2 1/2 x 8	24p	24p
3 1/2 x 5	27p	27p
17 x 2 1/2	75p	57p
17 x 3 1/2	100p	78p
17 x 5 (plain)	—	82p
17 x 3 1/2 (plain)	—	60p
17 x 2 1/2 (plain)	—	60p
2 1/2 x 5 (plain)	—	11p
2 1/2 x 3 1/2 (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

## JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	3p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240° 6 pin  
Plug 12p. Socket 8p.  
4 way screened cable, 15p/metre.  
6 way screened cable 22p/metre.

## BATTERY ELIMINATOR

£1.50  
9V mains power supply. Same size as PP9 battery.

## LARGE (CAN) ELECTROLYTICS

1600μF 64V	74p	2500μF 64V	80p	4500μF 16V	50p
2500μF 100V	74p	2800μF 100V	£2.60	4500μF 25V	£1.68
2500μF 50V	58p	3200μF 16V	50p	5000μF 50V	£1.10

## HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF	10p	0.047μF	13p	0.22μF	20p
0.022μF	12p	0.1μF	13p	0.47μF	22p

## POLYSTYRENE CAPACITORS 160V 2 1/2%

10pF to 1,000pF E12 Series Values 4p each.

## SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector.  
excluding cases. Mains operated detector £5.20. 12 or 24V battery operated audible alarm £7.30. As above for PP9 battery, £6.40.

## PRINTED BOARD MARKER

97p  
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

# LARGE RANGE ITT/TEXAS IC's NOW IN STOCK

PRICES ARE CALCULATED ON TOTAL NUMBER ORDERED REGARDLESS OF MIX

	1-11	12-24	25-99	100+	7448	185	175	170	165	74118	100	82	73	64
7400	18	16	14	13	7450	18	16	14	13	74121	43	40	38	36
7401	18	16	14	13	7451	18	16	14	13	74141	100	95	90	85
7402	18	16	14	13	7453	18	16	14	13	74145	150	140	135	130
7403	18	16	14	13	7454	18	16	14	13	74150	330	280	250	220
7404	18	16	14	13	7460	18	16	14	13	74151	110	100	95	89
7405	20	18	16	14	7470	30	28	25	24	74153	120	110	105	95
7406	50	45	40	35	7472	30	28	27	23	74154	200	180	170	160
7407	56	50	44	38	7473	40	38	36	30	74155	150	120	100	86
7408	36	30	27	23	7474	40	36	32	28	74156	130	120	100	86
7409	36	30	27	23	7475	55	52	50	49	74180	155	136	112	96
7410	18	16	14	13	7476	40	36	32	30	74190	195	190	185	180
7411	18	16	14	13	7480	100	95	90	85	74191	185	190	185	180
74118	23	21	20	18	7481	125	115	110	105	74192	200	190	180	164
7412	36	30	27	23	7482	100	96	90	85	74193	200	180	170	150
7413	34	28	26	22	7483	100	97	95	92	74196	200	190	180	170
7416	45	43	39	34	7484	120	115	110	105	74197	200	195	180	170
7420	18	16	14	13	7485	250	245	240	230					
7421	36	30	27	23	7486	45	42	37	33					
7426	32	25	23	20	7490	75	67	60	52					
7430	20	18	16	14	7491A	100	92	85	79	709	14 pin DIL			40p
7432	40	36	32	28	7492	75	70	65	60	741	8 pin DIL			

# SAXON ENTERTAINMENTS LTD.

STANDARD & CUSTOM-BUILT AUDIO & ELECTRONIC EQUIPMENT. NEW & SECONDHAND MUSICAL INSTRUMENTS. DISTRIBUTORS FOR A.K.G. HIGH QUALITY MICROPHONES

**Better built  
Better performance  
Better value**

## SAXON HI-FI POWER AMPS FOR DOMESTIC & COMMERCIAL USE

New Versions using 3A "Plastic Power" Driver Transistors now available.

To meet demand, we have included a more powerful module in our well-established and proven range. All these power amplifiers are carefully assembled, tested and guaranteed. They offer superb value for reliability and versatility.



**SA35** 35W RMS uses 7 transistors and 7 diodes. Carr. paid. **£4.45**

## A NEW ADDITION IS THE SA50 at £5.65

Carr. paid. A rugged, well built unit, capable of 50W RMS out, with all the advantages of Saxon Amplifier design and quality. Ready now.

## SA100 makes an ideal unit in disco assemblies

A real glutton for work. Reliable, tough and compact. 11 transistors, 6 diodes. Carr. paid. **£10.90**

### BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000Hz ± 1dB	All modules incorporate OPEN AND SHORT CIRCUIT PROTECTION, plus proof against over-dissipation and faulty inductive loads in its SA100
Distortion	0.2% at 1kHz	
Loads	4 to 16 ohms	
Quiescent current	15mA	
Noise	Better than -75dB	
Supply voltage	SA35-45V SA50 45/65V SA100 40-70V	
Size	4 1/2in x 4in x 1in (SA100) 4in x 3in x 1in (SA35/SA50)	

Circuits, connecting instruction and application data are supplied free with all modules.

### POWER SUPPLIES FOR THE SA35, SA50 AND SA100 POWER AMPS. ABOVE

PU45	Unstabilised supply for 2 SA35's	£4.90
P070	Unstabilised supply for one or two SA50 or SA100	£7.75 carr. 40p
PS45	Stabilised module for two SA35's	£3.50 carr. free
MT45	Transformer for above, heavy duty	£2.85 carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted	£3.50 carr. 20p
PS70	Stabilised supply module for one or two SA100's	£4.90 carr. free
MT70	Transformer for PS70	£4.90 carr. 40p

**ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD AND SUPPLIED FULLY TESTED**

Order and personal shoppers to:

**SAXON ENTERTAINMENTS LTD., 329 Whitehorse Road, W. Croydon, Surrey CR0 2HS**

Telephone 01-684 6385  
From 9.30 a.m.-5.30 p.m.

Prices quoted do not include V.A.T. 10% must be added on total value of order for V.A.T.

**TRADE AND EXPORT ENQUIRIES INVITED**

### TERMS OF BUSINESS


Cash with order (C.W.O.). For C.O.D. please add 35p extra, cash by regd. letter please.

## SAXON PA MIXER-CONTROL UNITS

In extra slimline easy-fit case.

Using grouped pairs of inputs (high Z and low Z inputs) with individual bass, treble and volume controls on each pair, plus master controls. These low-noise units will feed all makes of amplifiers, making them ideal for clubs, discos, etc. Standard jack sockets, compact design. In strong metal cases. All Units guaranteed for 3 years.

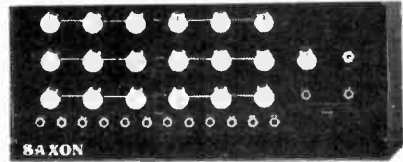- HIGH AND LOW IMPEDANCE INPUTS
- BASS/TREBLE/VOLUME ON EACH PAIR
- MASTER CONTROL ON OUTPUT



### M4H

4 high Z, 4 low Z inputs, 4 sets of controls. Case 10" x 8" and only 2 1/2in deep. Carr. paid.

**£18.50 + V.A.T.**

### M6HL

12 inputs (6 high Z, 6 low Z) 18" x 8" x 2 1/2". Carr. paid

**£27.50 + V.A.T.**

Channel section modules, for building your own: gain—16 x (24dB). Tone controls—18dB swing. Carr. paid.

**£3.50 + V.A.T.**

## CONTROL UNITS

Mono (as shown): **£6.50**

Carr. 20p.

For 9v battery operation. As stereo model, less mic. input.

Stereo. Carr. 30p. **£15.80**



Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2in x 3in x 4in deep and is finished with a smart white on black fascia. The controls are: Left/Right deck fader, volume, bass, treble, Headphone Selector and volume, Microphone volume, bass treble, mains on/off.

**COMPARABLE TO UNITS AT OVER TWICE THE PRICE.**

PLEASE ADD 10% FOR V.A.T. TO TOTAL VALUE OF YOUR ORDER

S.A.E. brings Saxon equipment and bargains list

● 160 watts version with power supply **£27.90** (Carr. 50p)

## 120 W HEAVY DUTY MODULE

Rugged class A driver stage. This module will run from all our mixers, etc., and most other makes. Delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.

### SPECIFICATION

Power output, 120W into 8 ohms  
Freq. response, 20-20,000Hz ± 2dB  
Input sensitivity, 200mV into 10K  
Construction, Fibreglass board  
Size, 8in x 4in x 4in (5in with supply)  
Low distortion parallel push-pull output stage.


Module and power supply (Carr. 40p)

**£18.95**

Another Saxon winner!
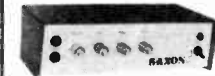
## SOUND AND LIGHT UNITS

Our popular 3 channel model handles up to 3kW (3,000W) of lighting and incorporates versatile sound control arrangement to enable professional standards to be achieved. Both units are excellent examples of Saxon quality and value.



### 3 CHANNEL UNIT

Includes bass, middle and treble as well as master controls, 2 amplifier sockets eliminate need for split leads. Up to 3kW lighting load. Smartly finished steel case. Carr. 30p. **£19.75**


### SINGLE CHANNEL UNIT

Operates from 5-100W amplifiers. Supplied for bass note operation, is easily adapted for treble or mid-range at a cost of about 5p. Carr. pd. **£8.90**

## COMPLETE AMPLIFIERS

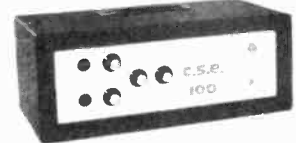**CSE 100 £34.90 carr. free**

This versatile unit is now available in a black vynide case and so represents even better value than ever delivering speech and music powers of up to 100W RMS and continuous signal outputs of 70W. Two individually controlled inputs with wide range bass and treble controls.



**SAXON 100 £48.50 carr. free**



With an RMS output of 120W speech and music, 100W continuous power, four individually controlled FET input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

**LOUDSPEAKERS British made bargains!!**

12in 25W 8/15 ohms £5.95 carr. 30p. 15in 50W 8/15 ohm £14.50 carr.

50p. 12in 40W 15,000 gauss magnet system 8/15 ohm £11.50 carr. 40p.

600 Watt 3 colour Light Boxes. Prices subject to alteration without notice E. & O.E.

# KEEP WARM AT A COOL PRICE.

Slash central heating costs with **AMKIT.**

If you can put in electric wiring, you can install Amkit. The unique nylon pipe hot water central heating system, that you install yourself in hours.

Look at these advantages:

- No soldering
- No 'T' junctions
- No special equipment
- No leaks, no lagging, no corrosion
- No structural upheaval

Just reliable, effective central heating (Guaranteed 25 years) at a saving of between £150 & £250. This famous system has been successfully marketed since 1968.

Clip the coupon, and we'll tell you more.

To Autocon Manufacturing Co.

Spring House, 10, Spring Place, London, NW5, 3BH  
Please send your brochure telling me all about Amkit.

Name .....

Address .....



or see for yourself at: THE AMKIT D.I.Y. CENTRE,  
15, Procter St., London, W.C.1. (opp Holborn Undgnd).  
Open Mon-Fri 9.30 am-5.30 pm, Sat 9 am-1 p.m.

**SPECIAL 40 MHZ SCOPE—SOLARTRON CD112 ONLY £50.** Has to be a snag. There are no plug-in Y amps available.

**TB**—100 nanosecs per cm to 5 secs per cm in 24 calibrated ranges. 20 nanosecs per cm with times 5 expansion. 5in flat faced tube. Trace locator. 0.2 microsec signal delay. Built-in calibrator 1kHz square wave. 200 micro volts to 100 volts in 18 calibrated ranges. Tube sensitivity 3 V/cm. Main Frame Y Amp boosts this to better than 200 MV per cm at 40 MHz. 240V 50 Hz input. Complete with full manual including plug-in circuits. Come and see one working or Carriage £1.50.

**MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR LOW PRICED SOLID STATE SWITCH.** 2 Hz to 8 MHz. Hook up a 9 volt battery and connect to your scope and have two traces for **ONLY £5.50.** P. & P. 25p. (Not cased, not calibrated.)

**NEW WIDE RANGE WOBBLATOR** 5 MHz to 150 MHz up to 15 MHz sweep width. Only 3 controls, preset RF level, sweep width and frequency. Ideal for 10.7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V A.C. and use within minutes of receiving. All this for **ONLY £5.75p.** P. & P. 25p. (Not cased, not calibrated.)

**20 Hz to 200 kHz WB.**

**SINE and SQUARE GENERATOR.** Four ranges. Independent amplitude controls, thermostat stabilised. Ready to use. 9V supply required. £7.85 each. P. & P. 25p (Not cased, not calibrated.)

**GRATICULES.** 12cm x 14cm high quality plastic 15p each. P. & P. 5p. 12" Long Persistence CRT, full spec. Price £12.50 to include V.A.T. & carr.

PLEASE ADD 10% V.A.T.

OPEN 9 a.m. to 6.30 p.m. ANY DAY

**CHILTMHEAD LTD**

7/9 ARTHUR ROAD, READING, BERKS.  
(rear Tech. College) Tel.: Reading 582605/65916

**COMPONENT PACK** consisting of 5 pots, various, brand new; 250 resistors  $\frac{1}{2}$  and  $\frac{1}{4}$  watt; many high stabs, etc. Fine value at **50p.** P. & P. 17p.

**P.C.B. PACKS** & D. Quantity 2sqft—no tiny pieces. 50p plus P. & P. 20p. **FIBRE GLASS** as above £1 plus P. & P. 20p.

**5 CRYSTALS** 70 to 90kHz. Our choice. 25p. P. & P. 15p. **5 MOVING COIL METERS** various £2. P. & P. 37p.

**CAPACITOR PACK**—50 Brand new components only 50p. P. & P. 17p.

**POTS**—10 different values. Brand new—50p. P. & P. 17p. **TRIMMER PACK.** 2 Twin 50/200pF ceramic 2 Twin 10/60pF ceramic; 2 min. strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW, 25p the lot. P. & P. 10p.

**FLAT FACED 4" Twin Beam Tube,** type CV2193. Green trace. Brand new £4 each. P. & P. 37p. **LIGHT EMITTING DIODES** (Red) from Hewlett-Packard. Brand New 38p each. Holder 1p each. Information 5p.

**PHOTOCELL** equ. OCP71, 13p each. **PHOTO RESISTOR** type Clare 703. Two for 50p.

**MODERN TELEPHONES** type 706. Two-tone grey, £3.75 each. The same but black, £2.75 each. P. & P. 25p each. Also **TOPAZ YELLOW** £4.50 each. P. & P. 25p.

**IDEAL EXTENSION** Telephones with standard GPO type dial, bell and lead coding. £1.75 each. P. & P. 25p.

**DELIVERED TO YOUR DOOR** 1 cwt of Electronic Scrap chassis, boards, etc. No Rubbish. FOR ONLY £3.50.

# Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Training Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

Ring

**01-637 2171**

between 9 a.m. and 9 p.m. and ask for Mr PLATT

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name .....

Address .....

Age .....

Phone .....

PE8

**CONTROL DATA INSTITUTE**


**CONTROL DATA LIMITED**

The Training Division of one of the world's largest Computer manufacturers.

# ALL OUR PRICES INCLUDE V.A.T.
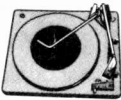
## BSR HI-FI AUTOCHANGER STEREO AND MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 2 months' guarantee. A.C. 200/250V. Size 13" x 11 1/2". Above motor board 3 1/2". below motor board 2 1/2".



with STEREO and MONO XTAL £6.25 Post 25p.

## PORTABLE PLAYER CABINET

Modern design. Black rexine covered. Silver front grille. Chrome fittings.

Motor board cut for BSR deck £4.50 Post 25p

## COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 1 1/2" x 10" x 3 1/2". Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2" x 10" x 8 1/2". 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls 240V a.c. mains.



Attractive Teak finish Weight 13 lb. Bargain Price £25 85p carriage

## SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH

Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Two types available 0 to 60 minutes Type A or 0 to 8 hours Type B. Makers' last list price £4.50. Brand new and fully guaranteed. Fully insulated. OUR PRICE £1.85 or £3 pair. Post 25p (PLEASE STATE TYPE A OR B WHEN ORDERING)



## WEYRAD P50 — TRANSISTOR COILS

R2W Ferrite Aerial 85p  
Osc. P50/1A/C 40p  
I.F. P50/2CC 470 k/c/s 40p  
3 r.f. P50/3CC 40p  
Spare Cores 3p  
Mullard Ferrite Rod 8 x 1/2", 20p. 6 x 1/2", 20p. 3 x 1/2", 10p.  
Driver Trans. LFDT4 85p  
Printed Circuit, PCA1 85p  
J.B. Tuning Gang 85p  
Weyrad Booklet 10p  
OPT1 85p

**VOLUME CONTROLS**  
5 K. ohms to 2 Meg. LOG or LIN. L/S 15p. D.P. 25p.  
STEREO L/S 55p. D.P. 75p.  
Edge 5K.S.P. Transistor 25p.  
**80 ohm Coax 4p yd.**  
BRITISH AERIALITE  
AERAXIAL-AIR SPACED  
40 yd. £1.40; 80 yd. £2.  
FRINGE LOW LOSS  
Ideal 625 and colour 10p yd

## 8in. or 10in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-18,000 c/s. Bass resonance 55 c/s, 8 ohm. Impedance 8in 10 watt, 10in 12 watt music power. £3.75 Post 25p



## E.M.I. 1 1/2" x 8in. SPEAKER SALE!

With twin tweeters. And crossover. 10 watt. Stereo 3 or 8 or 15 ohm. As illustrated. Post 25p



With flared tweeter cone and ceramic magnet. 10 watt. Bass res. 45-60 c/s. Flux 10,000 gauss. Stereo 3 or 8 or 15 ohm. Post 25p

Bookshelf Cabinet 16 x 10 x 8in. £5.50 Teak finish Post 25p

## SET OF 3 MOTORS FOR COLLARO STUDIO TAPE DECK

£2.50 Post 50p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2in sides 6 x 4in 53p; 8 x 6in 53p; 10 x 7in 85p; 12 x 8in 85p; 14 x 9in 90p; 16 x 8in 90p; 12 x 3in 50p; 16 x 10in £1.  
ALUMINIUM BOXES, 3 x 3 x 3in 60p; 4 x 4 x 4in 70p; 6 x 4 x 4in 80p; 9 x 4 x 4in £1; 12 x 4 x 4in £1.30.  
ALUMINIUM PANELS 18 s.w.g. 6 x 4in 8p; 8 x 6in 15p; 14 x 3in 16p; 10 x 7in 16p; 12 x 5in 20p; 12 x 8in 20p; 16 x 8in 20p; 14 x 8in 34p; 12 x 12in 40p; 16 x 10in 50p.  
PAXOLIN PANEL 10 x 8in 15p.

## ANOTHER R.C.S. BARGAIN! 4 TRANSISTOR MONO AMPLIFIER

Powerful 3 watt output, 15 ohm. AC mains operated with transformer. 3-Controls, volume, treble, bass and On/Off switch with knobs. Ready made on printed circuit board. Fused inputs and outputs. Famous make, size 8in wide x 4 1/2" x 3 1/2". £5.95 Post 20p

**R.C.S. STABILISED POWER PACK KITS**  
All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA a.c.  
PLEASE STATE VOLTAGE REQUIRED. £2.20 Post 25p Details S.A.E. Size 3 1/2 x 1 1/2 x 1 1/2in.

## R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. Line 200-300V d.c. operation. Size: 1 1/2 x 1 1/2 x 1 in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. £9.9p Post 20p Full instructions supplied. Details S.A.E.

## E.M.I. WOOFER AND TWEETER KIT

Woofers 10 1/2 x 6 1/2in. Ceramic Magnet, 44oz. 13,000 lines. Tweeter 3 1/2in. square, 10,000 lines. Crossover condenser, full instructions supplied. Impedance 3 ohms, power 12 watts. £5.75 Post 25p

## BRITISH FM/VHF TUNING HEART

88 to 108 M/C/S British made. 2 Transistors ready aligned requires 10-7 M/C/S I.F. Complete with tuning gang. Connections supplied but some technical experience essential. Our price £3.95 1 Post 20p

## MAINS TRANSFORMERS ALL POST 25p each

Eagle MT12 12-0-12V 50 mA 90p  
250-0-250 80 mA, 6-3V 3-5A 6-3V 1A or 5V 2A £2.50  
350-0-350 80 mA, 6-3V 3-5A, 6-3V 1A or 5V 2A £3.00  
300-0-300V 120 mA, 6-3V 4A, 6-3V 2A £3.25  
MINIATURE 200V 20 mA, 6-3V 1A x 2 1/2 x 2in £2.50  
MIDGET 220V 45 mA, 6-3V 2A 2 1/2 x 2 1/2 in. 80p  
HEATER TRANS. 6-3V 3A 80p  
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp. 3, 4, 5, 8, 9, 10, 12, 15, 18, 24 and 30V £2.80  
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £2.25  
2 amp. 12, 15, 25V 23p; 50V 24p; 30, 36, 40, 48, 60 £3.80  
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £3.75  
3 amp. 5, 8 and 13V £1.00; Dito 5 amp £1.20. 3 amp. 3, 5, 8, 10, 13 and 5-0-5V £1.30. Dito 5 amp. £1.50.  
6-0-6V 500mA 90p 9V 1 amp 85p, 12V 300mA 75p, 12V 500mA 85p, 12V 750mA 85p, 40V 1 amp £1.75.  
AUTO TRANSFORMERS: 115V to 230V or 230V to 115V 150W £2.25; 500W £2.25; 500V £1.00 £1.00 £1.00  
CHARGER TRANSFORMERS. Input 200/250V, for 6 or 12V, 1 1/2 amp £1.50; 2 amp £1.80; 4 amp £2.50  
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4.50.  
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs, 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.

## MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V. 3A. 720W. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. OUR PRICE £10 10p Carr. Famous make. (Valve £18). 60p Can be used as 800W auto transformers 240-110V. IDEAL FOR COLOUR T.V. OR GARDEN TOOLS.

**NEW ELECTROLYTIC CONDENSERS**  
2/350V 14p 250/25V 14p 50-50/300V 50p  
4/350V 14p 500/25V 20p 80-100/350V 85p  
6/450V 18p 1000/25V 35p 32-32/250V 20p  
16/450V 22p 1000/50V 47p 32-32/250V 45p  
32/450V 35p 8-8/450V 22p 350-50/325V 55p  
25/25V 10p 8-16/450V 25p 32-32-32/350V 55p  
50/50V 10p 16-16/450V 40p 100-50-50/350V 55p  
100/25V 10p 32-32/350V 40p

**LOW VOLTAGE ELECTROLYTICS.**  
1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
500mF 12V 15p; 25V 20p; 50V 20p; 100V 20p.  
1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.  
2000mF 6V 25p; 25V 42p; 50V 57p.  
2500mF 50V 62p; 3000mF 25V 47p; 50V 85p.  
5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.

CERAMIC, 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0-1 4p, 0-5 13p; 1mF 15V 15p. 500V-0.001 to 0.05 4p; 0-1 5p; 0.25 8p; 0-47 25p. SILVER MICA. Close tolerance 1%, 2.2-500pF sp. 50-2.200pF 10p; 2.700-5.800 pF 20p; 8.800pF-0.01, mfd 30p each. TWIN GANG, "0-0" 280pF-170pF, 85p; 500pF standard 45p. 365pF-365pF with 25pF+25pF, Slow motion drive 50p. SHORT WAVE SINGLE, 10pF, 30p, 25pF, 50p, 50pF, 55p. NEON PANEL INDICATORS 250V AC/DC. Amber 20p. RESISTORS, 1W 1/4W 20%, 1/2W, 5p, 100 to 10M. HIGH STABILITY W 2%, 10 ohms to 6 meg., 10p. Dito 5%. Preferred values 10 ohms to 10 meg., 4p. WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 0.5 ohm to 8.2 ohms 10p. TAPE OSCILLATOR COIL Valve type 35p.

## NEW MODEL "BAKER LOUDSPEAKER", 12IN 50 WATT. GROUP 50/12. 8 OR 15 OHM HIGH POWER. FULL RANGE PROFESSIONAL QUALITY. £17.60

## BAKER MAJOR 12" £9.90

Post free 30-14,500 c/s, 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwell. Bass resonance 40 c/s. Rated 20W. NOTE: 3 or 8 or 15 ohms must be stated.



Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. £12.50 Please state 3 or 8 or 15 ohms. Post free

## BAKER "BIG-SOUND" SPEAKERS Post free

'Group 25' 'Group 35' 'Group 50'  
12in. £8.80 12in. £9.90 15in. £22  
25W 35W 50W  
3 or 8 or 15 ohm 3 or 8 or 15 ohm 8 or 15 ohm

TEAK VENEERED HI-FI SPEAKER & CABINETS  
For 12in or 10in dia. speaker 20 x 13 x 8in, £3.90. Post 25p  
For 13 x 8in or 8in speaker 16 x 10 x 8in, £3.50. Post 25p  
For 8 x 5in speaker 16 x 8 x 8in, £4.40. Post 25p  
For 8in and tweeter 12 x 8 x 8in, £4.00. Post 25p  
LOUDSPEAKER CABINET WADDING 18in wide, 15p ft.

## GOODMANS 6 1/2in. HI-FI WOOFER

8 ohm. 10W. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 c/s. Ideal for P.A. Columns, Hi-Fi Enclosure Systems, etc. Suitable Cabinet 12 x 8 x 6 £4 Suitable Tweeter £2 £4

**ELAC CONE TWEETER**  
The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 18,000 c/s. Size 3 1/2 x 2 1/2in deep. Rating 10W, 2 ohm. Crossover 95p £1.90 Post 20p.

**SPEAKER COVERING MATERIALS. Samples Large S.A.E.**  
Horn Tweeters 2-18kc/s, 10W 8 ohm or 15 ohm £1.95.  
De Luxe Horn Tweeters 2-18kc/s, 15W, 15 ohm £3.  
CROSSOVERS, TWO-WAY, 3,000 c/s 3 or 8 or 15 ohm 95p.  
LOUDSPEAKERS P.M. 3 OHMS, 7 x 4in, £1.25; 6 1/2in, £1.50; 8 x 5in, £1.80; 10in, £2.00; 8in, £1.75; 10 x 8in, £1.90.  
SPECIAL OFFER! 60 ohm, 2 1/2in, 2 1/2in; 35 ohm, 2 1/2in, 3in, 25 ohm, 2 1/2in dia, 3 1/2in dia, 5in dia. £1 TYPE EACH 15 ohm, 3 1/2in dia, 8 1/2in, 7 x 4in, 8 x 5in. 3 ohm, 2 1/2in, 2 1/2in, 3 1/2in dia, (6 x 4in 8 ohm £1.50).  
RICHARD ALLAN TWIN CONE LOUDSPEAKERS, 8in, DIAMETER 4W £2.50, 10in diameter 5W £2.50; 12in diameter, 8W, £2.85.  
VALVE OUTPUT TRANS. 25, 15p; MIKE TRANS. 50:1 25p. 5 WATT MULTI-RATIO, 3, 8 and 15 ohms 80p. Mike trans. mu metal 100:1 £1.25.

## MAJOR 100 WATT ALL PURPOSE GROUP AMPLIFIER

All purpose transistorised. P.A. for Groups, Diaco and P.A. 4 inputs speech and music, 4 way mixing. Output 8/15 ohm. a.c. Mains. Separate treble and bass controls. Guaranteed. Details SAE. £49 Carr. SUPER VALVE MODEL, 100W, callers only, £39.



## BARGAIN AM TUNER. Medium Wave. Transistor Superhet, Ferrite aerial. 9 volt. £4.95

**BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.** Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. £3.95  
**TWO CHANNEL STEREO VERSION** £5.95

**BARGAIN 3 WATT AMPLIFIER.** 4 Transistor Push-Pull Ready built, with volume, 18 volt. D.C. Treble and bass controls. £4.50

COAXIAL PLUG 10p. PANEL SOCKETS 10p. LINE 18p. CABLE BOXES, SURFACE OR FLUSH 25p.  
BALANCED TWIN RIBBON FEEDER 300 ohms. 5p yd.  
JACK SOCKET Std. open-circuit 14p, closed circuit 23p;  
Chrome Lead-Socket 45p. Phono Plug sp. Phono Socket 5p.  
JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 12p. DIN SOCKETS Chassis 3-pin 10p; 3-pin 10p. DIN SOCKETS lead 3-pin 15p; 3-pin 15p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMICS 8p; CANS 5p.

## REVERSIBLE 4 POLE MOTOR

1,400 r.p.m. Reversible 42 Watt, spindle 1 1/2" x 3/4", size 3" x 3", As £1.95 illustrated. With Cooling Fan. a.c. 240V. Post 25p

## ONE RPM GEARED MOTOR 95p

240V a.c. mains. Ideal for displays/diaco light wheels. Post 25p.

## E.M.I. GRAM. MOTOR. £1

2,400 r.p.m. 2 pole 70mA. Size 2 1/2 x 2 1/2in. Post 25p.

## WHITEHORN ROAD, CROYDON

Open 9-6. Wed. 9-1, Sat. 9-5 (Closed for lunch 1.15-2.30) Buses 50, 68, 159. Rail Selhurst. Tel. 01-684 1665

# RADIO COMPONENT SPECIALISTS

Illustrated Colour Brochure, Radio Books and Component Lists 10p. (Minimum posting charge 20p.)

# SPECIAL COMPONENTS OFFER!

ALL NEW GOODS  
FULLY GUARANTEED

Please add 10% VAT to  
Total Order including P. & P.

**HILLS DYNAMIC HEADPHONE MODEL H-707 VS DE-LUXE**  
An extremely high quality head-phone supplied with Padded Headphone and Earcups together with SLIDER volume controls for precise listening levels. Specially offered at an unbeatable price. 8 ohms. 20-20,000Hz.  
Retail Price OUR PRICE **£5.75** P. & P. 25p



**VEROBOARD** (P. & P. 12p)  
2.5in x 3.75in 19p 16p 10p  
2.5in x 5in 23p 22p 11p  
3.75in x 3.75in 24p 22p —  
3.75in x 5in 26p 26p 17p  
Spot Face Cutter 39p 38p  
Pin Insertion Tool 50p 50p  
Pins—single or double sided. 0.1 or 0.15 pitch. 18p (per pkt. 36).

### ANTEX BITS

(P. & P. 12p)  
Our Price  
1100 for CCN240 1/4in 25p  
1101 for CCN240 1/2in 25p  
1102 for CCN240 3/4in 25p  
50 for X25 1/4in 33p  
51 for X25 1/2in 33p  
52 for X25 3/4in 33p  
Antex Heat Sink 10p

(P. & P. 12p)

**PLINTH AND COVER FOR GARRARD SP-25 III or BSR MP60. Our Price £2.75 (P. & P. 65p)**

**ANTEX SOLDERING IRONS** Rec. Our Price  
(P. & P. 12p) Retail Price  
X25 25 watt £1.92 £1.40  
CCN240 15 watt £2.14 £1.60  
S73 Stand 84p  
X25E Replacement 25W Element £1.06  
CCN240E Replacement 15W Element £1.06

**HILLS DYNAMIC HEADPHONE MODEL H-101 VSM**  
Offered at a remarkably low price supplied with padded Headband and Earcups adjustable volume controls with stereo and mono switch. 8 ohms imp. 30-18,000Hz.  
Rec. Retail Price OUR PRICE **£3.75** P. & P. 25p




**PLUGS AND SOCKETS** (P. & P. 12p)  
Plain Chassis Sockets  
DIN 2 pin (SPK) 10p 5p  
DIN 3 pin 11p 9p  
DIN 5 pin (180°) 13p 9p  
DIN 5 pin (240°) 13p 9p  
3.5mm Plastic 9p \*9p  
1/2in Mono Plastic 12p \*12p  
1/2in Mono Chrome 16p \*13p  
1/2in Stereo Plastic 20p 22p  
\*Switched

### AUDIO EXTENSION CABLES

(P. & P. 12p)  
HH-101 Straight Headphone Cable 99p  
HH-102 15ft Coiled Headphone Extension Cable £1.45  
GL20 20ft Coiled Guitar Cable, Straight Jackplug to Angled Jackplug £1.30  
SEND FOR OUR FREE CATALOGUE (ENCLOSING 5p STAMP)
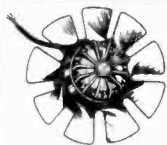
## HILLS COMPONENTS LTD.

DEPT. PE12, UNIT No. 6, MELINITE INDUSTRIAL ESTATE, BRIXTON ROAD, WATFORD, HERTS. WD2 5SL. Tel. Watford 27711



### FAN/BLOWER

Precision-built in Germany. Dynamically balanced mains unit (200/240) continuous rated, reversible 60mA on run. Size 5 1/2" dia x 2 1/2" deep. Back plate is tapped for 4 fixing screws (supplied). Well under maker's price at £3. P. & P. 20p. Similar unit to above but 7 1/2" dia. x 3" deep. £3.30. P. & P. 25p.



### SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1 min. divisions, approximately 1" between divisions. Panel mounting with chrome bezel 3 1/2" dia. £1.40. P. & P. 15p.




### GEARED MOTORS

"Parvalux" Reversible 100 rpm geared motor. Type 8D14, 230/250V a.c., 22 lb/in. 3" spindle. BRAND NEW £13.70 each. P. & P. 50p.

REVERSIBLE Parvalux type 8D19. 240V a.c. 30rpm. 40 lb/in. Variable angle drive shaft. Ex-equipment in good condition. £7. P. & P. 50p.

SHADED POLE Mains motor. 1 1/2" x 1 1/4" x 2" high. Double ended A shaft projecting 1 1/2" each side of motor. £1. P. & P. 20p.

### OPEN FRAME shaded pole GEARED MOTORS

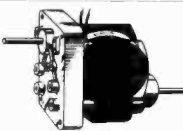


(Dural gear case) 240 a.c., 28rpm. NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 3 1/2" spindle 1 1/2" dia. as illustrated. £3. P. & P. 30p. Similar to above, 19rpm. £2.70. P. & P. 30p. 110rpm with pressed steel gear case (similar to above but slightly smaller). £2.70. P. & P. 30p.


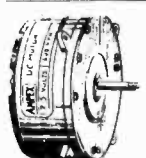
### SPIT MOTOR

51rpm. 2 1/2" x 1 1/2" x 6 1/2" high. 240V a.c. Shaft 1/2" o/d, 1 1/2" length with hexagon socket inside. £2. P. & P. 30p.



### AMPEX 7.5v. DC MOTOR

This is an ultra precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500mA. Draws 60mA on run. 600rpm speed adjustment. Internal A/R/F suppression. 1 1/2" dia. x 1 1/2" spindle, motor 3" dia. x 1 1/2". Original cost £16.50. OUR PRICE £3.30. P. & P. 25p. Large quantities available (special quotations). Mu-metal enclosure available. 75p each. P. & P. FREE.

"DAVENSEY" MAINS SOLENOID 1" travel, 8lb pull (approx.). Size: 2 1/2" long x 23/16" x 2" high. Similar in appearance to "SORENG". £1.65 P. & P. 20p.

### MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged "elbow". Bracket incorporates 2 fixing screws. Length of arm, 2 1/2". 240V a.c. Pull at coil is approximately 1lb. £1. P. & P. FREE. Special quotes for quantities.

### SOLENOIDS by WESTOOL

240 a.c. type MM6. 3lb. pull. 2 1/2" x 1 x 1 1/2". Travel 1". 90p each. P. & P. 10p.  
240 a.c. type MM4. 2lb. pull. 1 1/2" x 1 1/2" x 1". Travel 1/2". 70p each. P. & P. 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.

### "DECCO" MAINS SOLENOID

Compact and very powerful. 16lb. pull. 1/2" travel which can be increased to 1" by removing captive-end-plate. Overall size: 2" x 2 1/2" x 2 1/2" high. £2.20. P. & P. 20p.

### MAINS SOLENOID by MAGNETIC DEVICES LTD.

A beautifully constructed solenoid at half normal price. A 2-sided bracket is incorporated for vertical or horizontal mounting. Size: 2" x 1 1/4" x 1 1/4". Pull is approximately 2lb, plunger travel 1 1/4". Fixing eye takes up to 1" bolt, plunger non-captive. NEW in original maker's boxes. £1.20. P. & P. 20p. Large number available, special price for quantity.

### "CROUZET" MOTORS

Type 965 115/240V. 50Hz. 48W. Stoutly constructed, 2 1/16" dia. x 3 1/2" long plus spindle 1" x 1/2" dia. Anti-clock. £3.30 each. P. & P. 25p.

### "RE CIRK IT" Mains 10amp cut-out

by "Neimman Electric" Germany. Eliminates fuses. Size: 2" x 1" x 1 1/2" deep. 75p each. P. & P. 10p. 4 or more 55p each. P. & P. 20p.

### KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, hearing devices, etc. Size (60 DB) 7/32" x 5/32" x 1/4"; (80 DB) 1/2" x 3/32" x 1/4". Equipment, all tested. £1.40 each. P. & P. FREE.

### UNLESS OTHERWISE STATED

all items are NEW and UNUSED. Postal or carriage charges are for Gt. Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50. C.W.O., please. Company orders under £2.50, surcharge 60p, unless C.W.O.

### PLUG-IN RELAYS by SCHRACK (Perspex enclosed)

OCTAL (2c/o) 6 amp contacts at following voltages: 48 d.c., 60 d.c., 60 a.c., 110 d.c., 380 a.c. PRICE EACH £1-10.  
11 pin (3 c/o) 6 amp contacts: 12 a.c., 48 d.c., 48 a.c., 60 a.c., 60 d.c., 110 d.c., 115 a.c., 240 a.c. PRICE EACH £1.40.  
RA and RN Series (4 c/o) 3 amp Gold Plated Contacts. Handsome modern construction. 1/2" x 3/4" x 1 1/2" high. Following voltages: 6 a.c., 12 a.c., 24 a.c., 48 a.c., 48 d.c., 60 a.c., 110 d.c., 115 a.c., 120 a.c. PRICE EACH £1.  
Base sockets for all above types 15p. Please add 10p towards P. & P. on all orders.

From JAPAN. TAKAMISAWA Perspex enclosed relay. Type MQ308 24V d.c. 600 ohm (4 c/o). Complete with base socket. 80p. P. & P. 10p.

### SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!  
A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3 amp at 250V. 1 1/2" high at 240V. Size: (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems, etc. and wherever non-mechanical switching is required. 10 for £2. P. & P. 15p; 50 for £8.80; 100 for £16.50. P. & P. FREE over 10.

### NORPLEX

The famous American fibre-glass copper-clad laminate. Finest quality with woven glass of Epoxy-resin. Excellent Mech. and Elec. conductive properties. Heat resistant, ideal for P.C.'s, etc. TH18 IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST! Size: 12" x 22" x 1/8" x 1/8" x 24"; FULL SHEET 43" x 37" (11 sq.ft.). Single-sided Copper with thickness of 1/32", 3/64", 3/32". Also double-sided 1/32", 1/16", 3/32". £1 per sq.ft. Cut sizes (1-10 sq.ft. P. & P. 25p. Full Sheet £8 each. Carr. £1 for 1st sheet plus 25p each additional sheet.

### TANGENTIAL HEATER

Silently driven by shaded pole Mylex motor, powerful and smooth running with aluminium impeller (outlet 3/4" x 1 1/2"). mains voltage PLUS matching heater unit with spiral element. May be switched for 500 or 1,000W. £2.20. P. & P. 30p.

ALL PRICES NOW INCLUDE V.A.T.


# ELECTRO-TECH COMPONENTS LTD.

315/317 EDGWARE ROAD LONDON, W.2  
Tel. 01-723 5667 01-402 5580


now...
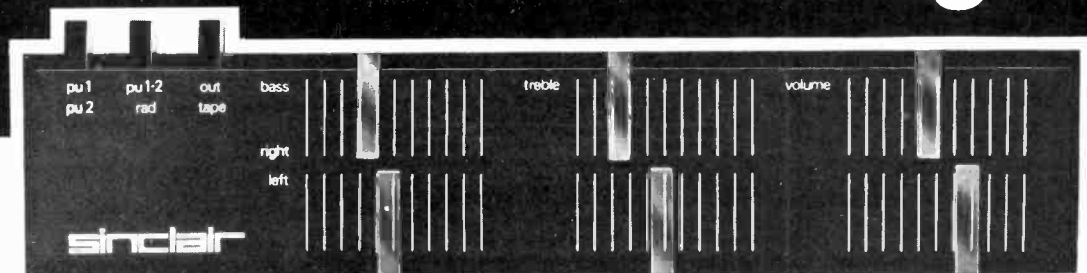
# Project 80

... exciting new thinking  
in modular hi-fi design



Stereo 80 pre-amplifier/control unit

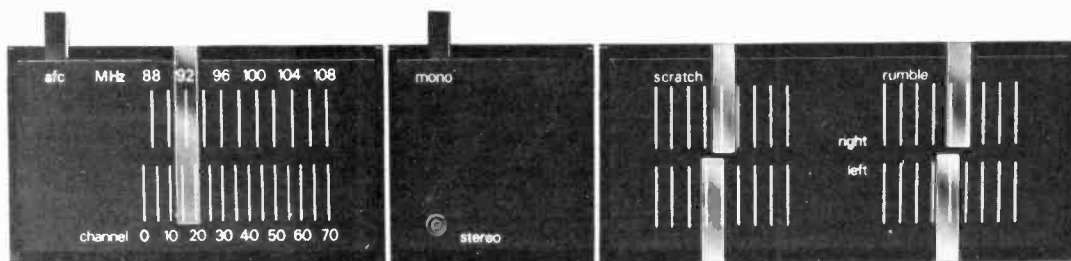

Project 80 tuner

Stereo decoder

Project 80 Active Filter Unit (AFU)

**the slimmest, most elegant hi-fi modules ever made**



Living with hi-fi takes on new meaning now that Project 80 is here. These amazing new modules mark a brilliant technical advance all round; their size and presentation bring exciting new opportunities to install systems in ways hitherto only dreamed about but never before made practical. You can build a Project 80 system virtually anywhere and it is unbelievably simple to install and connect up. Everything that could possibly be wanted in a top quality do-it-yourself domestic hi-fi system will be found in Project 80 – compactness, elegantly ultra-modern styling, ease of fixing and operation, new control methods, and above all superb performance. New as well as popular established ideas on installation are featured on page four of this announcement to provide just a few examples of the system's fantastic versatility.

# sincor

# Project 80 new modules

## Stereo 80 pre-amplifier and control unit

As with other Project 80 units, the Stereo 80 is mounted by means of two bolts fixed at the rear which pass through holes drilled in the wood or plastic on which modules are to be mounted. *All the electronics are contained within the  $\frac{3}{4}$ " deep front panel!* Connecting leads are taken away similarly out of sight. Each channel in the Stereo 80 has its own independent tone and volume controls operated by sliders. This enables exceptionally good environmental matching to be obtained. Provision is made for magnetic and ceramic pick-ups, radio and tape in and out. A virtual earth input stage forms part of the up-dated circuitry of the Stereo 80 to ensure the finest possible quality from all signal sources. Generous overload margins are allowed on all inputs. Clear instructions with template are supplied.

### TECHNICAL SPECIFICATIONS

Size - 260 x 50 x 20mm ( $10\frac{1}{2}$  x 2 x  $\frac{3}{4}$  ins)  
 Finish - Black, with white markings  
 Inputs - Mag P.U. 3mV RIAA corrected; Ceramic P.U. 300 mV  
 Radio 300 mV, Tape 30 mV  
 S/N ratio - 60db  
 Frequency range - 20Hz to 15KHz  $\pm 1$ dB; 10Hz to 25KHz  $\pm 3$ dB  
 Power requirements - 20 to 35 volts  
 Outputs - 100mV  $\pm$  AB monitoring for tape  
 Controls - Press button for tape, radio and P.U. selection Volume, Bass  $\pm 12$ dB to  $\pm 14$ dB at 100Hz, Treble  $\pm 11$ dB to  $\pm 12$ dB at 10KHz

## Project 80 FM tuner smaller, more efficient

A truly remarkable tuner in every way - its unbelievably compact size - its original circuitry - its dependable performance - all this in a boldly designed modern case measuring 85 x 50 x 20mm ( $3\frac{1}{2}$  x 2 x  $\frac{3}{4}$  ins). Greater adaptability (and possibly financial convenience) results from the tuner and stereo decoder section being made available separately.

### TECHNICAL SPECIFICATIONS


Size - 85 x 50 x 20mm (approx  $3\frac{1}{2}$  x 2 x  $\frac{3}{4}$  ins)  
 Tuning range - 87 to 108 MHz  
 Detector - I.C. balanced coincidence, for good A.M. rejection  
 AFC - Switchable, with thermistor control to prevent from drift  
 One 26 transistor I.C.  
 Twin dual varicap tuning  
 Distortion - 0.3% at 1KHz for 75KHz deviation  
 Ceramic filter in I.F. section  
 Aerial impedance - 75  $\Omega$  or 240-300  $\Omega$   
 Sensitivity - 4 microvolts for 30dB quieting  
 Power requirements - 12 to 45 volts

## Project 80 stereo decoder

Making the Project 80 decoder separate from the F.M. tuner gives the constructor a wider choice of systems as well as saving money in cases where stereo reception may not be required. This unit gives a 40dB channel separation with an output of 150mV per channel. The gallium arsenide light emitting beacon automatically lights up to show when a stereo transmission is tuned in. Designed essentially as an integral part of Project 80 systems, this multiplex stereo demodulator may be used in many cases with existing single channel frequency modulated tuners to provide stereo reception.


Size - 47 x 50 x 20mm ( $1\frac{3}{4}$  x 2 x  $\frac{3}{4}$  ins)  
 One 19 transistor I.C.

# NEW

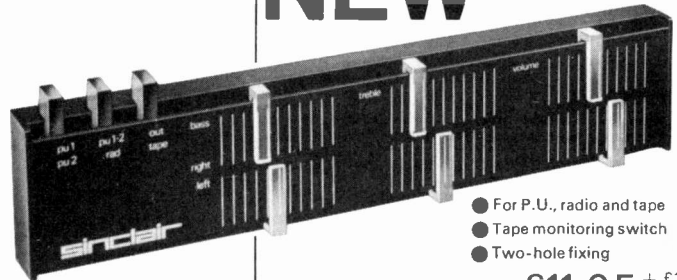


- For P.U., radio and tape
- Tape monitoring switch
- Two-hole fixing

R.R.P. **£11.95** + £1.19 V.A.T.

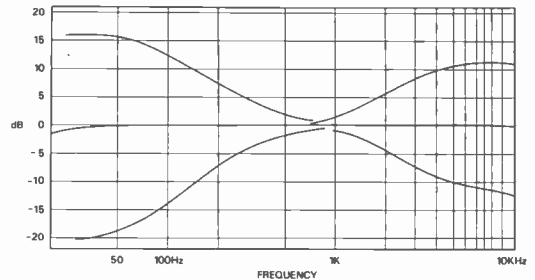


# NEW

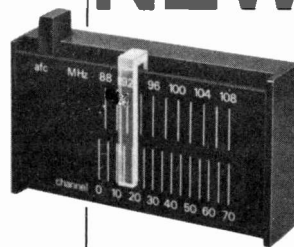

- AFC switch
- Twin dual varicap tuning
- 4-hole ceramic filter
- Slider tuning

R.R.P. **£11.95** + £1.19 V.A.T.

# NEW

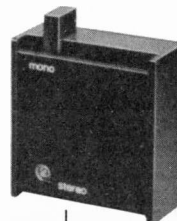

- Solid-state stereo indicating beacon
- Readily adaptable for use with other tuners

R.R.P. **£7.45** + 0.74p V.A.T.



# new constructional techniques

## ...and again Sinclair leads the world

- 1962 Micro-miniature power amp small enough to stand on a 10p. piece. Slimline pocket receiver smaller than a 20 cigarette pack
- 1963 Micro-6 receiver, smaller than a matchbox
- 1964 Pocket F.M. receiver; PWM amp.
- 1965 Z.12 power amplifier module; PZ.3 power supply
- 1966 Stereo 25 pre-amp/control unit
- 1967 Micromatic: Q.14 loudspeaker; the first Neoteric
- 1968 IC.10, the first ever integrated circuit for constructors' use


- 1969 Q.16 - improved version of Q.14 Systems 2000 and 3000: Project 60 launched
- 1970 IC.12 Project 60S
- 1971 Project 60 stereo FM tuner Z.50; PZ.8
- 1972 Improvements to Project 60 with Z.50 MK.2 and PZ.8 Mk.3 The Executive Calculator: Digital multi-meter. Q.30 speaker
- 1973 Cambridge Calculator  
PROJECT 80 LAUNCHED  
... and next?

## Project 80 active filter unit

This efficiently designed unit makes a highly desirable part of any worthwhile system where inputs may be from record, radio or tape. As with Stereo 80, separate controls are applied to each channel thereby making it easier to obtain ideal stereo balance in any kind of indoor environment.
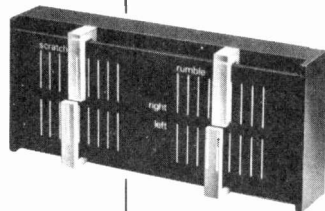
### TECHNICAL SPECIFICATIONS

Size - 108 x 50 x 20mm (4 1/4 x 2 x 3/4 ins)  
Voltage gain - minus 0.2dB  
Frequency response - 36Hz to 22KHz, controls minimum  
Distortion - at 1 KHz - 0.03% using 30V supply  
HF cut off (scratch) - 22KHz to 5.5KHz, 12dB/oct slope  
L.F. cut off (rumble) - 28dB at 20Hz, 9dB/oct. slope



# NEW

- For scratch and rumble control
- Transistorised active circuitry

R.R.P. **£6.95** + 0.69p V.A.T.

## Z.40 & Z.60 power amplifiers totally short-circuit proof



Either of these entirely new power amplifiers is intended for use in Project 80 installations although, of course, they are readily adaptable to an even wider range of applications. Both Z.40 and Z.60 incorporate built-in protection against shortcircuiting and risk of damage arising from mis-use is greatly reduced. Comprehensive instructions are supplied with each of the modules.

### Z.40 Technical Specifications

Size - 55 x 80 x 20mm  
(2 1/8 x 3 1/8 x 3/4 ins) 9 transistors  
Input sensitivity - 100mV  
Output - 15 watts RMS continuous into 8 Ω (35V), 30 watts music power into 4 Ω (30V)  
Frequency response - 10Hz - 100KHz ± 1dB  
Signal to noise ratio - 64dB  
Distortion - at 10 watts into 8 Ω less than 0.1%  
Power requirements - 12-35 volts
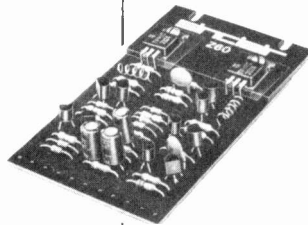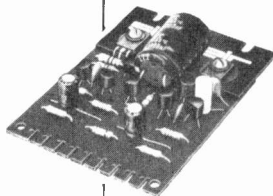
### Z.60 Technical Specifications

Size - 55 x 98 x 20mm  
(2 1/8 x 3 3/8 x 3/4 ins) 12 transistors  
Input sensitivity - 100-250mV  
Output - 25 watts RMS into 8 Ω (45V), 50 watts music power into 4 Ω (50V)  
Distortion - typically 0.03%  
Frequency response - 10Hz to more than 200KHz ± 1dB  
Signal to noise ratio - better than 70dB  
Built-in protection against transient overload and short circuit  
Load impedance - 4Ω min; max safe on open circuit



# NEW

### Z.40

R.R.P. **£5.45** + 0.54p V.A.T.


### Z.60

R.R.P. **£6.95** + 0.69p V.A.T.
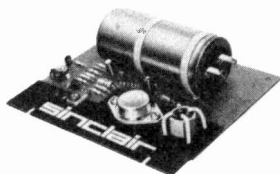
## Sinclair power supply units PZ.8

the worlds most advanced unit in its class

Stabilised power supply unit. Re-entrant current limiting makes damage from overload or even direct shorting impossible, a principle never before incorporated in a commercially available constructor module. Normal working voltage (adjustable) 45V.  
R.R.P. £7.98 + 0.79p V.A.T.  
Without mains transformer  
PZ.5 30V unbalanced  
R.R.P. £4.98 + 0.49p V.A.T.  
PZ.6 35V, stabilised  
R.R.P. £7.98 + 0.79p V.A.T.




## Recommended Project 80 applications

System	The Units to use	Units cost
Simple battery record player	Z.40	<b>£5.45</b> + £0.54p V.A.T.
Mains powered record player	Z.40, PZ.5	<b>£10.43</b> + £1.04 V.A.T.
30W RMS continuous sine wave stereo amp.	2 x Z.40s, Stereo 80; PZ.6	<b>£30.83</b> + £3.08 V.A.T.
50W (8 Ω) RMS continuous sine wave de luxe stereo	2 x Z.60s, Stereo 80; PZ.8	<b>£33.83</b> + £3.38 V.A.T.
amplifier Indoor P.A.	Z.60, PZ.8	<b>£14.93</b> + £1.49 V.A.T.
Car Radio	F.M. tuner, Z.40	<b>£16.40</b> + £1.64 V.A.T.


**sinclair**  
R.O. London Rd., St. Ives, Huntingdon PE17 4HS Reg. England 699483

# From Sinclair the worlds most advanced hi-fi modules

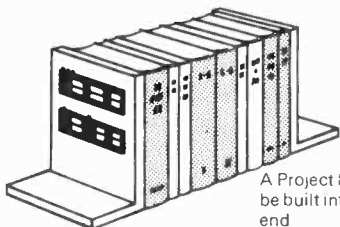
## Sinclair Project 80 the ultra-modern non-obtrusive hi-fi



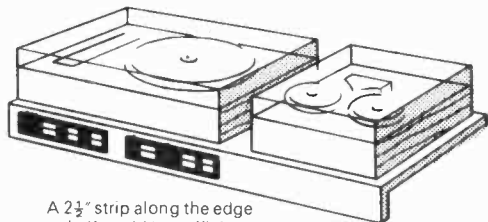
A Project 80 system could be built into a book-shelf end



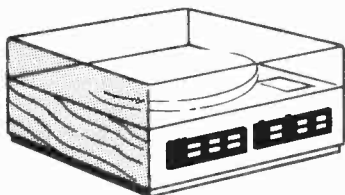
A 2½" strip along the edge a shelf could be sufficient to contain a complete system



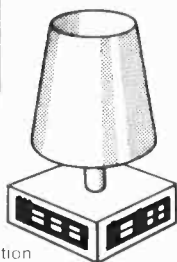
The modules mount very easily onto a playing plinth



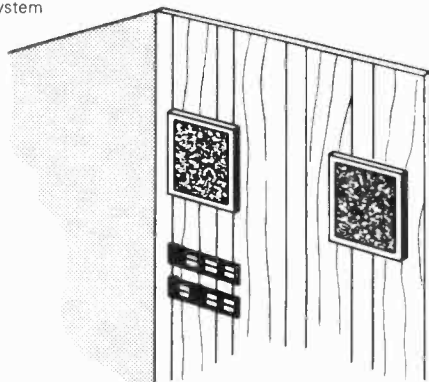
A novel application would be to build around the base of a lampshade



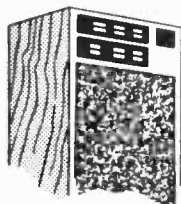Two Sinclair Q.16 loudspeakers suitably positioned together with Project 80 could be mounted on to a false wall.



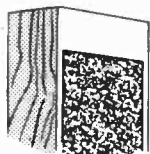Project 80 could be easily mounted onto a loudspeaker cabinet



When you have seen for yourself how fantastically slim and cleverly designed these modules are, further ways will suggest themselves in which they can become a pleasing part of your particular domestic environment.

To SINCLAIR RADIONICS LTD. ST. IVES, HUNTINGDON PE17 4HJ

Please send post paid \_\_\_\_\_

for which I enclose Cash/Cheque for £ \_\_\_\_\_ including V.A.T.

Name \_\_\_\_\_

Address \_\_\_\_\_

PE12

### Guarantee

If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair appointed Stockists also offer this guarantee.

*Should any defect arise in normal use, we will service it without charge. For damage arising from mis-use a small charge (typically £1.00) will be made.*

# sinclair

Sinclair Radionics Ltd.  
London Road, St. Ives,  
Huntingdon PE17 4HJ  
Telephone St. Ives (0480) 64311

## VARIABLE VOLTAGE TRANSFORMERS

**INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V**

All Types from ½ to 50 amp from stock.

### SHROUDED TYPE

1A £8.75, Post 50p  
2.5A £10.10, Post 60p  
5A £14.60, Post 75p  
10A £28.15  
15A £31.25  
20A £61.25  
37.5A £102.50  
50A £122.50

### CARRIAGE AND PACKING

EXTRA unless shown (Panel Mounting)  
1 amp £8.75, Post 50p. 2½ amp £10.10, Post 60p.



2.5 amp OPEN TYPE

## RING TRANSFORMERS

Functional Versatile Educational

These multi-purpose Auto Transformers, with large centre aperture, can be used as a Double wound current Transformer, Auto Transformer, H.T. or L.T. Transformer, by simply hand winding the required number of turns through the centre opening. Eg. using the RT.100 VA Model the output could be wound to give 8V @ 12½A, 4V @ 25A or 2V @ 50A, etc. Price:

RT.100VA 3/18 turns per V. £3.00, Post 35p.  
RT.1KVVA 1/82 turns per V. £8.60, Post 50p.  
RT.2KVA 1/5 turns per V. £14.00, Post 75p.  
RT.3KVA 1/5 turns per V. £19.00, Post £1.



## VOLTAGE CHANGING TRANSFORMER

M.f.g. to highest W.D. spec. Auto wound, and tapped 0-130-160-200-250 at least 2kVA. Can also be used as 230-240V input, 115V out for U.S.A. equipment, or reverse to obtain 240V from 115V. The ideal transformer for making up solid state constant voltage unit, by use of taps the following voltages may be obtained 30-40-50-70-90V at 10 amps. Weight 40lb, length, 260mm, height 190mm, width 230mm. In original maker's wooden case, £8, Carr. £1.

## BLOWER UNIT

200-240 Volt A.C. Precision German built. Dynamically balanced, quiet, continuously rated, reversible motor. Consumption 60mA. Size 120 mm. dia. x 60 mm. deep. Price £3, Post 30p.




## 4 BANK 3c/o PUSH BUTTON ASSEMBLY

Black rectangular buttons. 5 units (min. order) 85p, Post 15p.


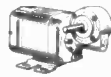
## PARVALUX Type: SDI.

S/86896/OJ  
230/250V A.C. 50 r.p.m. 7 lb/in. Continuously rated. £6, Post 30p incl. base.



## 600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £2.75, Post 25p.



## 2000 WATT POWER CONTROL

For Power Lamps, Heating, Sewing Machines, Lighting, etc. £8.00, Post 27p.



## VENNER TIME SWITCH TYPE MSQP

200/250 Volt 2-ON/2-OFF every 24 hours at any manually pre-set time. 20 amp contacts. Fitted diecast case. Tested and in perfect condition £4.75, Post 25p.




## FOOT SWITCH

Suitable for Motors, Drills, etc., etc. 5 amp, 250 volt. Price 75p, Post 15p.


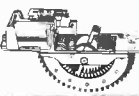
## UNISELECTOR SWITCHES

NEW 4 Bank 25 Way, 24V d.c. operation. £6.90, Post 30p. 6 Bank 25 Way, 24V d.c. £7.90, Post 30p. 8 Bank 25 Way, 24V d.c. operation. £9.50, Post 40p.



## TRIACS

GENERAL ELECTRIC POWER-GLAS TRIACS 10 amp. Glass passivated plastic triac. Latest design from U.S.A. Long term reliability. Type SC146D 10 amp, 400 PIV. £1, Post 5p. Type SC146E 10 amp, 500 PIV. £1.30, Post 5p. (Inclusive of data and application sheet.) Suitable Diac 18p.

All Mail Orders—Callers—Ample Parking  
Dept. PE11, 57 BRIDGMAN ROAD  
CHISWICK, LONDON W4 5BB  
Phone 01-995 1560  
Showroom open Mon.-Fri.

## STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation. **EXPERIMENTERS' ECONOMY KIT** Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30, Post 30p.

**NEW INDUSTRIAL KIT** Ideally suitable for schools, laboratories, etc. Speed adjustable 1-90 f.p.s. Approx. 2 output of Hy-Light. Price £10.50, Post 50p.

**HY-LIGHT STROBE MK III** For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £12, Post 50p.

## THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.

● Variable speed from 1-3 flash per sec.  
● Reactor control circuit producing an intense white light. ONLY £20, Post 75p.

**ROBUST, FULLY VENTILATED METAL CASE.** For Hy-Light Kit including reflector £4.75, Post 25p.  
Super Hy-Light Kit including reflector £7, Post 60p.


**7-INCH POLISHED REFLECTOR** Ideally suited for above Strobe kits. Price 55p, Post 15p.

## RAINBOW STROBE FOUR LIGHT CONTROL MODULE

Will operate four of our Hy-Light or Super Hy-Light Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Thoroughly tested and reliable. Complete with full connection instructions. Price: £18, Post 50p. Send S.A.E. for details.
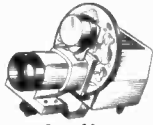
## COLOUR WHEEL PROJECTOR

Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18.50, Post 50p.



**6 INCH COLOUR WHEEL** As used for Disco lighting effects, etc. Price £5, Post 30p.

**1 R.P.M. MOTOR** 220/240 volt a.c., 1 r.p.m. synchronous motor. 2 watt. A/clock. Spindle 10mm long, 3mm dia. Motor only 20mm deep. Fixing centres 44mm. Price £1.10, Post 5p. Suitable for above wheel.

## BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. Innumerable industrial applications also ideal for stage display, discos, etc. P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16, Post £1. Spare bulb £7, Post 40p.



## BLACK LIGHT FLUORESCENT U.V. TUBES

4ft 40 watt. Price £5.50, Post 30p. 2ft 20 watt. £4.25, Post 25p. (For use in stan. bi-pin fittings.)

**MINI.** 12in 8 watt, £1.60, Post 15p. 9in 6 watt, £1.30, Post 15p. Complete ballast unit and holders for 9in and 12in tube. £1.70, Post 25p. (9in and 12in measures approx.)

## ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.75, Post 35p.

## 50 IN 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75, P. & P. 25p.

All prices are subject to 10% VAT. (10p in the L)  
To all orders add 10% VAT to total value of goods including carriage/packaging.

# SERVICE TRADING CO

## Superior Quality Precision Made

## NEW POWER RHEOSTATS

New ceramic construction, vitreous enamel embedded winding, heavy duty brush assembly, continuously rated.



2.5 WATT 1/25/50/100/250/300/500/1k/ohm  
£1.15, Post 10p.  
50 WATT 1/5/10/25/50/100/250/500/1k/1.5k/ohm £1.60, Post 10p.  
100 WATT 1/5/10/25/50/100/250/500/1k/1.5k/2.5k/3.5k/5k ohm £2.35, Post 15p.  
Black Silver, Skirted knob calibrated in Nos. 1-9. 1¼in. dia. brass bush. Ideal for above Rheostats. 22p each.

## RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col.(1)	1	2	3	4
Coil ohms	52	4-6	6M	60p*
Col. (2)	150	6-12	4 c/o	80p*
Working	185	8-12	6M	60p*
d.c. volts	280	8-16	2 c/o	70p*
Col. 3	410	10-18	4 c/o	60p*
Contracts	700	16-24	4M 2B	80p*
Col. (4)	700	15-35	2 c/o HD	70p*
Price	700	16-24	6M	60p*
	700	6-12	1 c/o HD	50p*
HD=	700	20-30	6 c/o	80p*
Heavy duty	1,250	24-36	4 c/o	60p*
	2,500	36-45	6M	60p*
*Incl. Base	2,400	30-48	4 c/o	60p
	5,800	24-26	2 c/o	60p
	9,000	40-70	4 c/o	60p*
All prices incl. P. & P.	15k	85-110	6M	60p

6 VOLT D.C. 2 make contacts 75p, Post 5p.  
9 VOLT D.C. RELAY  
3 c/o 5 amp contacts. 70 ohm coil. 75p, Post 5p.  
12 VOLT D.C. RELAY  
3 c/o 5 amp contacts. 75p, Post 5p.  
24 VOLT D.C. 3 c/o 75p, Post 5p.

230 VOLT A.C. 'DIAMOND H' RELAYS (Unused)  
Three sets c/o contacts rated at 5 amps. PRICE: 55p, Post 5p.



100 VOLT A.C.  
2 c/o seated type, octal base £1, Post 10p.  
24 VOLT A.C. 3 c/o 55p, Post 5p.


MINIATURE LATCHING RELAY  
Manufactured by Clare-Elliott Ltd. Type F. 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size 1¼ high, ¾ wide, ¾ thick. Complete with 3in. leads. New 65p, Post 5p.

230/240 VOLT A.C. HEAVY DUTY SEALED RELAY  
2 c/o 20 amp contacts £1.25, Post 10p.



DRY REED RELAYS  
Mfg. by ERG, 12 volt d.c. encapsulated. Two c/o 85p, post paid. Single c/o 65p, post paid. STC280 ohm coil 6/12V d.c. 3 make metal shrouded 60p, post paid. Large range of other types, details on request.

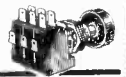"HONEYWELL" PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY  
Each bank comprises a c/o rated at 10 amps 240V A.C. Black knob 1in. Fixing hole ½ in. ONE bank 30p; TWO bank 40p; THREE bank 50p. Quote for quantity.



VERY SPECIAL OFFER  
Micro Switch, 5 amp c/o contacts. M.f.g. by Honeywell. NEW. Twenty for £1.50, Post 10p (min. 20).



'HONEYWELL' LEVER OPERATED MICROSWITCH  
15 amps 250 volt A.C. c/o contacts. In maker's carton. PRICE: 10 for £1.90, Post 15p.



## INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.8in. W.4in. H.6in, weight 6lb. 1,000V, 1,000 megohms, £34, Post 60p. 500V, 500 megohms, £28, Post 60p.



BALANCE/LEVEL METERS  
100-0-100 Micro Amp. Size 1½in x 1½in x ½in. Price only 70p, Post 5p.



METERS NEW! 2½in. Flush round. Available in D.C. Amps 1, 5, 10, 15, 20 or A.C. Amps 1, 5, 10, 15, 20, both types £2.00, Post 15p. Voltmeter 0-300V A.C. £2, Post 15p.



Personal callers only. Open Sat.  
9 LITTLE NEWPORT STREET  
LONDON WC2H 7JJ  
Phone 01-437 0576

# Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4H 4AD

## SITUATIONS VACANT

**YOUR TALENT CAN EARN YOU MONEY**

as a

**T.V. Engineer**

with

**Radio Rentals**

**Britain's No. 1 T.V. Rental Company**

Are you on the right lines in your present job? Switch to Radio Rentals and be assured a good future. Here are 5 star reasons for joining us.

- ★ Full Training given for Colour T.V.
- ★ 5-day week
- ★ Private use of a Company Vehicle or generous car allowance
- ★ 3 weeks' holiday per year, rising to 4 weeks
- ★ Good salary (up to £34.95 per week after 2 years)

Your present holiday arrangements will be honoured. Work towards a better future, better chances of promotion and more security. Telephone Mr. Mann, 01-540 1304 or write to:

**RADIO RENTALS**

**86 The Broadway • Wimbledon • London • S.W.19**

### FOR SALE

#### TV LINE OUT-PUT TRANSFORMERS

Tidman Mail Order Ltd., 236 Sandycombe Road, Richmond, Surrey TW9 2EQ  
01-948 3702

**CATALOGUE NO. 18**, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

**SEEN MY CAT?** 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

### MORSE MADE EASY!!

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only £8.90, complete course £4.50 P.P.I., etc., plus 10%.

(Overseas £1 extra) details only, 4p stamp. 01-680 2898  
**G8HSC** (Box 19), 45 GREEN LANE, FURLEY, SURREY

**SMALL ELECTRONIC MANUFACTURING COMPANY** (mixers) with excellent record for sale. Ideal opportunity for technically experienced entrepreneurs. Approx. £2,000. Box No. 53.

**HEATHKIT** aural/visual signal tracer in perfect condition. Complete with instruction manual, £15 o.n.o. Tel. 01-735 4698.

**MEN!**  
**£50 p.w.**  
**can be yours**

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a.

After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you **FREE** to world-wide opportunities. Write or 'phone **TODAY**, without obligation.

London Computer Operators

Training Centre  
M92, Oxford House  
9-15 Oxford Street, W.1  
Telephone 01-734 2874

### Department of Atmospheric Physics

### UNIVERSITY OF OXFORD

Applications are invited for a technician (prototype wireman) to work on electronic equipment for a satellite project. Experience in wiring solid state circuits would be an advantage. University salary scale rising to £1,794 p.a. according to age and experience. Apply in writing, giving full details of education, training, qualifications and experience to Dr. C. D. Walshaw, Clarendon Laboratory, Oxford OX1 3PU.

**LADDERS.** "Special Offer" Unvarnished Triples, 9ft 7in closed—24ft 7in extended. **£13.20** delivered. **HOME SALES LADDER CENTRE** (PEE2), Haldane (North), Halesfield (1), Telford, Shropshire. Tel. 0952 586644.

### FIBRE OPTICS

**Flexible Light Pipe** for conveying lights to inaccessible positions. Fibroflex Type 1. Glass 1.14mm effective dia. PVC sheathed. 44p per metre. (VAT inc.), P. & P. 10p. Any quantity.

**Polariser Sheet** up to 1 sq. ft. max. size. 161p per sq. in. (VAT inc.), P. & P. up to 6 in. square 10p; over 6 in. square 30p

- ★ Cut down glare
- ★ See those nixie tubes
- ★ Cross them for light control
- ★ Make your own strain gauge for plastics and glass

**Circuit Board Etching Kits.** Full instructions. £1.37½ (VAT inc.), P. & P. 20p

**Photographic CDS Light Cells**—used (with part of original circuit free), 33p (VAT inc.), Post free.

All items are strictly C.W.O.

From: **ARVIN SERVICE COMPANY**  
12 CAMBRIDGE ROAD  
ST. ALBANS

# T.V. Studio Engineer

The Road Transport Industry Training Board has in operation at its Wembley Headquarters, a 3 camera broadcast-quality colour television studio with full telecine and video recording facilities which includes R.C.A. TR 50 and 1" Helical Scan Systems. We now wish to appoint an experienced studio engineer to join a small team working on the production of training and educational television programmes.

The applicant should not be less than 24 years of age and have a good working knowledge of the above equipment. Salary will be negotiable depending on qualifications and experience. Three weeks holiday, contributory pension and life assurance scheme.

Please send all relevant personal history stating how the above requirements are met, and quoting reference GEA335, to:



Mrs. H. M. Brown  
Personnel Manager  
Road Transport Industry Training Board  
Capitol House, Empire Way  
Wembley, Middlesex HA9 0NG

## SERVICE SHEETS

### SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. ★ SERVICE SHEET CATALOGUE 25p  
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS  
RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

#### NEW BOOKS & PUBLICATIONS

- |  |       |
|--|-------|
| HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER by P.J.Guy. 142 pp.....                      | PRICE |
| CREATIVE TAPE RECORDING by Vivian Capel. 183 pp. Shows advanced techniques.                | £3.50 |
| TAPE RECORDERS by H.W.Hellier. 239 pp. A must for the enthusiast.....                      | £2.25 |
| UNDERSTANDING ELECTRONIC COMPONENTS by Ian R. Sinclair. 204 pp. 127 illus.....             | £3.50 |
| UNDERSTANDING ELECTRONIC COMPONENTS by Ian R. Sinclair. 218 pp. 130 illus.....             | £3.50 |
| FAULT LOCATION EXERCISES in Radio & TV Servicing by K.J.Bohman. VOL.1.....                 | £0.80 |
| FAULT LOCATION EXERCISES in Radio & TV Servicing by K.J.Bohman. VOL.2.....                 | £1.35 |
| WORLD RADIO TV HANDBOOK 1972. 26th Edition. 384 pp. Special reduced offer.....             | £1.10 |
| WORLD RADIO TV HANDBOOK 1973. 27th Edition. 400 pp.....                                    | £3.00 |
| TRANSISTOR AUDIO & RADIO CIRCUITS by Mullard Ltd. 283 pp. 2nd Edition.....                 | £1.80 |
| TRANSISTOR AUDIO & RADIO CIRCUITS by Mullard Ltd. Vol.1. 228 pp.....                       | £1.50 |
| POWER ENGINEERING USING TRANSISTORS by H.W.Hellier. 218 pp. 131 illustrations.....         | £3.50 |
| RADIO TECHNICIANS BENCH MANUAL by H.W.Hellier. 182 pp. 114 illustrations.....              | £3.00 |
| AUDIO TECHNICIANS BENCH MANUAL by John Earl. 182 pp. 114 illustrations.....                | £3.00 |
| MOBILE RADIO TELEPHONE EQUIPMENT HANDBOOK. Ccts. diagrams for PYE mods                     | £4.00 |
| ELECTRONICS IN MUSIC by F.C.Judd. 169 pp. Circuit designs and operation.....               | £3.15 |
| HANDBOOK OF TRANSISTOR EQUIVALENTS & SUBSTITUTES by B.B.Babani.....                        | £0.40 |
| HANDBOOK OF RADIO, TV, TUBE AND VALVE EQUIVALENTS by B.B.Babani.....                       | £0.40 |
| HI-FI PA, GUITAR & DISCOTIQUE AMPLIFIER DESIGN HANDBOOK by Babani.....                     | £0.75 |
| RADIO AMATEURS OPERATORS HANDBOOK by Data Publications Ltd. 80 pp.....                     | £0.45 |
| SIMPLE SHORT WAVE RECEIVERS by Data Publications Ltd. 140 pp.....                          | £0.80 |
| SERVICING TRANSISTOR RADIO RECEIVERS by F.R.Pettit. 3rd Edition. 88 pp.....                | £0.75 |
| USING AN OSCILLOSCOPE by D.W.Easterling. 108 pp.....                                       | £0.70 |
| SERVICING WITH THE OSCILLOSCOPE by G.J.King. 176 pp. Illustrated.....                      | £1.80 |
| BEGINNERS GUIDE TO RADIO by G.J.King. 7th Edition. 204 pp. Illustrated.....                | £1.00 |
| RADIO VALVE AND TRANSISTOR DATA by A.M.Bell. 9th Edition. 240 pp.....                      | £0.75 |
| NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good prices paid.      |       |
| Send large S.A.E. for FREE booklists. Postage on above books is 5p in the £1.00 (UK only). |       |

## BELL'S TELEVISION SERVICES

ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

**SERVICE SHEETS** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p with free Fault-Finding Guide. S.A.E. orders/enquiries. Catalogue 15p. HAMILTON ROAD, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

**SERVICE SHEETS**, Radio, TV, etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

### RECEIVERS AND COMPONENTS

**TUNBRIDGE WELLS.** Components from TELESERVICE, 108 Camden Road, Tunbridge Wells, Kent. Telephone 31803.

### 5-N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc.  
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

**REDHAWK SALES LTD.**  
45 Station Road, Gerrards Cross, Bucks.  
MAIL ORDER ONLY

**RADIO & TELEVISION AERIAL BOOSTERS** £2.95, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7.50. Carr. £1.50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.

## Trampus electronic

Add 10% VAT (h) to all prices. All brand new, no rejects. Money Back Warranty.  
**5V DIGITAL INDICATOR:** 0-9DP socket and filter £1.29.  
**LED TYPE 1'** 0-9DP DIL £1.75 each; 6x £1.69 each. 4 digit type £1.  
**LIGHT EMITTING DIODES.** All with data and panel clip. TTL 209 1" dia. 22p. Red 1" dia. type 28p. Green 55p. INFRA RED beam LED £1.10.  
**GAS detector** £1.69. Ultrasonic transducer £2.  
**DALO PCB resist marking pen** 69p. Copper board 12" x 6" SRBP 40p. FeC etch PAK 18p.  
**INTEGRATED CIRCUITS:** with data if required.  
**IC LITE SWITCH:** Photo amplifier 40mA/11-20V relay or TTL 87p. DIL relay £1.09.

## IC digital clock

MOS/LSI type. 28 pin, 4 or 6 digit, 12/24hr. chip with socket £13. PCB £1.69; KIT £20. DVM voltmeter £12. Data 89p. 3W AF amp £1.24.  
741 DIL 8 pin 28p; 709 19p. DIL 29p; 748 29p; mono 710 33p. 555 TIMER/mono/astable osc. clock 89p.  
**REGULATORS:** 1A 5 to 20V £1.49; 723 67p.  
**RECEIVER** 2N414 £1.19. Mini Rx Kit £1.90.  
1310 stereo decoder for tuner £2.69, KIT £3.45.

## NEW LOW PRICES

GATES 7400/1/2/3/4/5/10/20/30/40/50. etc. 14p each 7413 27p; 7441 73p; 7447 £1.09; 7470. 7472 28p; 7473. 7474 36p; 7475 60p; 7476 32p; 7490 59p; 7492 67p; 7480 69p; 7483 £1.10; 7486 37p; 7493 78p; 7494 83p; 7495 83p; 7496 89p; 74121 46p; 74141 98p; 74190/91/92/93/96 £2.39. DIL Plugs/IC case 10mm high 16 pin 85p.  
**DIL SOCKETS:** low or high profile 8/14/16 pin 13p.  
**SEMICONDUCTORS:**  
2N3055 40p; BC107 8p; BC108 8p; BC109 8p; BC147/8/9 10p; BC167/8/9 13p; BC177/8/9 15p; BC182/3/4 10p; BC212/3/4 11p; BCY70/72 13p; BD131/2 55p; BFY70/51/52 13p; B718/48 UJT 84p; 2N2369 11p; 2N2369 12p; 2N2369 8p; 2N664 40p; 2N3053 17p; 2N3055 40p; 2N3614 55p; 2N3702/3/4/5/6/7/8/9/10/11 All 9p each.  
**FETS:** 2N3819 27p; 2N3823 29p; SCR 400V: 1A 28p; 4A 55p. TRANSFORMER: 1A 6 and 12V £1.  
**CAPACITORS:** Disc 22pF to 0.1µF 4p. 25V electrolytic 10, 50, 100µF 5p. 1,000µF 35p. PRESETS each. RESISTORS 1W 5% 11p each. CARBON POTS 12p each. Dual 40p. Switch+12p. All Din Plugs 13p; sockets 9p; Vero RRP.

## FLUORESCENT LIGHTS 12VOLT £2.79

13" 8 watt fully built with diffuser.  
TRIO and GODAR communications and Hi-Fi retailer. ELECTRONIC ORGANS from 487.  
PW ELECTRONIC CAR IGNITION KIT £6.67.  
VAT: YOU MUST ADD 10% (h) to all prices.  
FREE CAT. S.A.E. Data sheets 8p each. P. & P. Sp. C.W.O. P.O. BOX 29, BRACKNELL, BERKS.

**LARGE COMPUTER PANELS** E42 18 trans, 44p. E44 12 trans, 33p. E46 16 trans, 44p (post 12p each).  
**M.C. METERS. THREE ASSORTED** 2.3in. £1.15 (2P). 5 FIGURE 2.3in. £1.15 (2P).  
18/22V. works on 12V, £2.20 (20p). **SILICON DIODES** 650V 1A. 10 on tagboard 35p (5p). NEW 800V 1A. 6 for 25p (5p). **STABILISED MAINS POWER SUPPLY** variable output. 13-26V 4A. d.c. 10x 7x 7in £8-50 (60p). **COPPER CLAD PAX. PANELS** 5 1/2x5 1/2 in for 45p c.p. 7 1/2x9in 25p c.p. 6 for £1.25 c.p. 8 1/2x9 1/2 in for 35p c.p. 10x9in 35p c.p. 6 for £1.45 c.p. **WIRE ENDED NEONS** 10 for 50p (8p). Bank of five with 5x C407 driver trans. 50p (8p). **COPPER CLAD FIBRE GLASS PANELS** 15x3 1/2in or 12x4 1/2in 30p c.p. **FOUR WAY PLANO KEY SWITCH WITH INTERLOCK** 35p (7p). **SILVER MICA CAPACITORS** 100 assorted 55p c.p. **POLYETHYLENE CAPACITORS** 100 assorted 75p c.p. Your choice 2p each.  
7lb ASSORTED COMPONENTS £1.65 c.p.  
2lb ASSORTED COMPUTER PANELS £1.65 c.p.  
List of computer panels, etc. 10p stamps, refunded on purchase.

**J.W.B. RADIO**  
2 BARNFIELD CRESCENT  
SALE, CHESHIRE M38 1NL  
Postage in brackets. Mail order only

**BRAND NEW COMPONENTS** by return, Electrolytics 10V, 25V. 50V—0.47, 1, 2, 2, 4.7, 10 mF. 4p; 22, 47, 47p (50V, 5p); 100, 51p (50V, 7p); 220, 6p (50V, 9p). Subminiature bead-type tantalums 0.1/35V, 0.22/35V, 0.47/35V, 1/35V, 2.2/35V, 4.7/35V, 10/16V, 8p. Mylar Film 100V—0.001, 0.002, 0.005, 0.01, 0.02, 2p; 0.04, 0.05, 3p; 0.068, 0.1, 34p. Polystyrene 63V E12 series 10-1,000pF, 2p; 1,200-10,000pF, 3p. Miniature highstab resistors, 5%, E12 series—Carbon Film 4W, 1Ω-10MΩ (10% over 1 MΩ). Metal Film 1/4W, 10Ω-2.2MΩ and 1W, 27Ω-10MΩ all 4p each. Postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

## PRECISION POLYCARBONATE CAPACITORS

Close tolerance. High stability. All 63V d.c.

0.47μF:	±5%	30p:	±2%	40p:	±1%	50p:
1.0μF:	±5%	40p:	±2%	50p:	±1%	60p:
2.2μF:	±5%	50p:	±2%	60p:	±1%	75p:
4.7μF:	±5%	60p:	±2%	75p:	±1%	11.1μF:
6.8μF:	±5%	75p:	±2%	11.1μF:	±1%	15.0μF:
10μF:	±5%	11.1μF:	±2%	15.0μF:	±1%	22.0μF:
15μF:	±5%	15.0μF:	±2%	22.0μF:	±1%	33.0μF:

**TANTALUM BEAD CAPACITORS.** Values available 0.1, 0.22, 0.47, 1.0, 2.2, 4.7, 6.8μF at 35V, 10μF 25V, 15μF 20V, 22μF 15V, 33μF 10V, 47μF 6V, 100μF 3V—all at 8p each; 6 for 45p; 14 for 95p. Special pack 6 off each value (78 capacitors) £4.50.

**NEW TRANSISTORS.** BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices. AF178 at 35p each or 3 for 95p.

**POPULAR DIODES.** IN914, 6p each; 8 for 45p; 18 for 90p. IN916, 8p each; 6 for 45p; 14 for 90p. IS44, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

**NEW LOW PRICE—400 mW Zeners.** Values available 4.7, 5.6, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5mA. All new and marked. Price 7p each; 6 for 39p; 14 for 84p. Special offer 6 off each voltage (66 zeners) £3.65.

**RESISTORS.** Carbon film 5%, 1/4W at 40°C, 1/2W at 70°C. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

**440V A.C. CAPACITORS.** 0.1μF, size 1 1/2in x 1/2in, 25p; 0.25μF, size 1 1/2in x 1/2in, 30p; 0.47 and 0.5μF, size 1 1/2in x 1/2in, 35p; 1.0μF, size 2in x 1/2in, 45p; 2.0μF, size 2in x 1/2in 75p.

**SILICON PLASTIC RECTIFIERS 1.5A.** Brand new wire-ended DO27, 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

7p post and packing on all orders below £5. Please add 10% VAT to all orders

**MARCO TRADING**  
Dept. E12, The Maltings, Station Road  
Wern, Shropshire

## TELORADIO ELECTRONICS ARE STOCKING THE MODULES FOR THE P.E. RONDO QUADRAPHONIC SYSTEM

Matrix Decoder £8-80  
Pre-Amplifier £3-30  
Stereo Amplifier £8-25  
Controls & balance panel £9-35

Prices include VAT and Post

Further information gladly supplied on request

**TELORADIO**  
325-7 Fore Street, London N9 0PE  
01-807 3719

## DIGITAL CLOCK COMPONENTS

4/6 Digit Clock Chip £9-00; 6 Minitron Displays £6-00; Kit of Discrete Driver Transistors and Diodes £3-50; Minitron Sockets 25p each, 2N 7447 drivers £1-20 each.

## LOW COST LED LAMPS

Red 3mm dia. 20p each; Red 4.45mm dia. 23p each; Green 3mm dia. 55p each; Green 4.45mm dia. 55p each.

## CALCULATOR DISPLAY

0-12 inches Character Height Flatpack £2-00 each.

## SLIDER SWITCHES

1 pole 2 position—Miniature 14p each; 2 pole 2 position 14p each; 2 pole 3 position 21p each; 1 pole 4 position 23p each. U.K. Postage and packing 10p. Overseas 25p. ADD VAT 10%

## PERDIX COMPONENTS LTD.

Dept. PE73, 31 Green Lane, Chislehurst, Kent.

**COMPONENTS GALORE.** Pack of 500 mixed components. Manufacturers' surplus plus once used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers, etc. Send £1 + 10p P. & P. C.W.O. to: CALEDONIAN COMPONENTS, Strathore Road, Thornton, Fife.

## DRY REED INSERTS

Overall length 1.85" (Body length 1.1"). Diameter 0.14". Max. ratings 250V D.C. and 500 mA. Gold clad normally open contacts. 69p per dozen; £4-12 per 100; £30-25 per 1,000; £275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.

40/42 Portland Road, Worthing, Sussex BN9 34897

## NEW ELECTROLYTIC CAPACITORS

3V, 450mF; 6V, 200, 250, 320, 500, 640, 1,000mF; 10V, 125, 160, 400, 1,000mF; 12V, 50, 100, 200, 250, 350mF; 15V, 100, 500mF; 16V, 25, 30, 40, 50, 80, 100, 250, 500, 1,000mF; 20V, 40mF; 25V, 10, 12, 16, 25, 50, 100, 160, 200, 250, 500, 1,000mF; 40V, 16mF; 50V, 12, 50, 100, 120, 175, 200, 250, 500mF; 64V, 6.4mF. 0.1/500mF 3p each; 1,500/3,000mF 4p; 3,000+mF 5p. Postage 15p, over £3 free; Discount £5/£25 15%; £25+ 20%; No VAT.

## W.E.B. ELECTRONICS

P.O. BOX 4, MALVERN, WORCS. WR14 3HX

## MINIATURE HIGH STAB RESISTORS

5% 1/4W 22Ω to 2.2MΩ E12 series 10 each value. Total 610, £3.

## ANTEX X25 25W SOLDERING IRON

R.R.P. £1-92. Our price £1-57.

BC107, 10p; BC108, 9p; BC109, 10p; IN914, 4p; 8 pin 741, 39p.

## NEK ELECTRONICS (P4)

28 Carnegie Road, St. Albans, Herts. Please add 10p P. & P. Mail order only.

**CERAMIC SPACERS.** 250 PCB stand-off 0-270 high, 0-070 bore, 30p. GOODHART, 8 Beltinge Road, Herne Bay, Kent CT6 6DB.

## R.T. SERVICES

(MAIL ORDER ONLY)

77 Hayfield Rd., Salford 6, Lancs.

Veroboard 6x5 0-1 Matrix, 2 for £1. 4x4 1/2 0-1 Matrix, 4 for £1. 12x3 1/2 0-1 Matrix, 75p each.

Mullard A.M. Module. I.F. Strip, LP1166, £1-10 inc. P.P.

FM Tuner with R.F. Stage and A.G.C., 3 transistors, neg. earth, 2 1/2 x 2 x 1 1/2 in with circuit, £1-37 1/2 inc. P.P.

Crouzet Geared Motors, 30-60 r.p.m. New, £1-54 inc. P.P.

UHF TV Tuners. Transistorised, £1-65 inc. P.P.

VCR138 CRT. New, boxed, £3-30 inc. P.P.

Transformers. 7-5V + 7.5V 1A, 66p inc. P.P. 18-0-18V, 200mA + 24V, 77p inc. P.P.

9-0-9V, 100mA, 69p inc. P.P. 12-0-12V, 100mA 69p P.P. 20V, 1A 88p inc. P.P.

Transformers. 52-0-52V, 1A + 22-0-22V, 200mA, £2-20 inc. P.P.

P.C. Board. 5/5, 5 1/2 x 5 1/2 in, 10 for 70p inc. P.P.

Panel with 5-200 PIV 1A SCRs + 14 OA200 diodes plus components 70p inc. P.P.

2,500 mfd 100V/V capacitor 4 1/2" x 1 1/2". New, 85p inc. P.P.

Panel with 2 SN7490, 2 SN7441 counting circuit with end connector, £2-20 inc. P.P.

Panel with 2 min. nixie tubes to slot in, £2 inc. P.P.

Transistorised Timer. Variable delay. 110 or 250V A.C. input. With instructions. Brand new, £2 inc. P.P. Size 3" x 2" x 2".

**FOR BARGAIN LISTS** worth seeing, plus FREE SAMPLES send S.A.E., 2 Richmond Terrace, Uxvretton, Lancs.

## WANTED

**TOP PRICES PAID**  
NEW VALVES AND TRANSISTORS  
Popular T.V. and Radio types  
**KENSINGTON SUPPLIES (B)**  
367 Kensington Street  
Bradford 8, Yorks.

**NEWNES RADIO** and TV Servicing Books wanted. From 1960-1966, £2 paid per copy by return post. Any quantity bought. BELL'S TELEVISION SERVICES, Albert Place, Harrogate, Yorks. Tel. 0423 86844.

**PRACTICAL ELECTRONICS—June 1969, any condition.** STEED, 60 Brock Hill, Wickford, Essex.

## EDUCATIONAL

# A SUCCESSFUL CAREER IN RADIO

Get the success you deserve—take an ICS home study course. Pass C&G, M.P.T. exams FIRST TIME! Free books. Low cost. Personal tuition. Send TODAY for FREE Guide on Radio, TV, Electronics. Electrical Engineering.

Name \_\_\_\_\_

Address \_\_\_\_\_

**ICS**

Dept. 730A  
Stewart's Road,  
London SW8 4UJ

## MISCELLANEOUS

## ENAMELED COPPER WIRE

S.W.G.	1lb Reel	1/2lb Reel
10-14	£1-27	72p
15-19	£1-27	72p
20-24	£1-30	75p
25-29	£1-38	83p
30-34	£1-43	88p
35-40	£1-54	91p

Please add 10% to all above prices to cover VAT  
The above prices cover P. & P. in U.K. Supplied by  
**INDUSTRIAL SUPPLIES**  
102 Farnsworth Rd., Withington, Manchester 20  
Telephone No. 061-224 3553

## NEW FROM ELBON

**L.E.D.'s** (Red Emitting) Ideally suited for panel indicators  
Price only: 33p each or £2-50 for 10

## Light SENSITIVE SWITCHES

Two types available giving wide operating voltages:

LITE-IC2 11V-20V working—£1 each—£8-50 for 10

LITE-IC3 20V-30V working—£1 each—£8-50 for 10

Applications include: Relay, Trac or Logic Drive, automatic light switching and door control, beam/break detector—burglar alarm, batch counting and code reading.

## BARGAIN PACK!

2 LITE-IC2, 2 LITE-IC3 and 5 LED's all for £5-00

ALL PRICES INCLUDE VAT, PACKING AND CARRIAGE

Please send C.W.O. to:

LITE-IC, ELBON, SUMMERFIELD,  
THE CRESCENT, WEST WITTERING, SUSSEX

**CONSTRUCTION AIDS.** Screws, nuts, spacers, etc., in small quantities. Aluminium panels punched to spec. or plain sheet supplied. Fascia panels etched aluminium to individual requirements. Printed circuit boards—masters, negatives and boards, one-off or small numbers Send 6p for list. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

**CLEARING LABORATORY,** scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, MC relays, components, etc. Lower Beeding 236.

**METER REPAIRS.** Ammeters, Voltmeters, Multi-Range meters, etc., also Linear scale Transistorised Ohmmeters for sale. METER REPAIRS, 39 Chesham Rd., London N16 0DS.

## fibre optic suppliers

LOW COST LED-MLED 500, MV 54 MLED 500 is in TO92 case, for PC board mounting MV 54 is T<sub>2</sub> size, 2mm, miniature. Both emit visible red light. Current requirement 20mA, 150Ω resistors available for 5V d.c. (TTL) operation.

2N5777—SILICON PHOTO DARLINGTON AMPLIFIER Economical, high sensitivity, TO92, LIGHT DETECTOR

	1	2	5	10	25
MLED500	22p	44p	£1-10	£2-20	£3-74
MV54	22p	44p	£1-10	£2-09	£3-52
150Ω	—	—	—	—	11p
2N5777	55p	£1-10	£2-53	£4-62	£9-90

ULTRASONIC TRANSDUCERS—TRANSMITTER RECEIVER PAIR 40kHz for burglar alarm, remote control, novelties. Great value at £3-85 per transducer pair.

HNCP 37—NEUTRAL CIRCULAR POLARISER

Reduce glare on crt's, meters, displays, panels. 50mm x 50mm (2in), 66p; 75mm x 75mm, £1-21; 150mm x 150mm, £4-40.

CROFON 1610—64 FILAMENT LIGHT CONDUIT

1.8mm active dia., 3.3mm o.d. Simply cut to length and conduct light where required. For displays, internal illumination, multiple point lighting. 1 metre, £1-32; 2m, £2-64; 5m, £5-50; 10m, £10-45.

FP40—PLASTIC OPTICAL MONO-FIBRE, 1mm DIAMETER

Single strand unjacketed light guide, simple to use. 5 metres, £1-10; 10m, £1-98; 25m, £3-85. FP20 (0.5mm) and FP60 (1.5mm) also available.

MARE'S TAILS FOR DECORATIVE DISPLAYS

7,000 fibres, professionally finished, beautiful. Add lamp, stand, cover to make a Fibre Optic Lamp. Eye catching in boardroom, hall or foyer, £11-00 each.

All prices shown include P. & P., VAT, C.W.O. please. For full information on our complete range, send 9in x 6in S.A.E. to

FIBRE OPTIC SUPPLIERS (PE)  
P.O. Box 702 London W10 6SL

SPAIN is behind in electronics. Rent a shop in Torremolinos. Meet Spanish directors in London. Details—PAWLAK & NONS, 98 St. John's Road, SW11. Tel. 01-228 4466.

## DON'T LOOK

unless you can resist the temptation to get these super 'attention-getters':

★ POCKET-SIZED MAXI-VOLT Big ½ inch Spark Generator (instant 15,000 volts!) Ready-made, needs no batteries. Carry it around anywhere. Only weighs about 3 oz (85g). Send £1-35 for your Maxi-volt now!

★ UNIQUE TRANSMITTER/RECEIVER KIT. No licence examinations or tests required to operate this transistorised equipment. Easy to build. Get transmitting. Send £5-90 for yours now!

★ PSYCHEDELIC MINI-STROBE KIT. Take a pocket-sized lightning storm to Disco's and Parties. "BRAIN-FREEZE" 'EM with vari-speed stop-motion flashes. Includes super case, too. Send £2-20 now!

(All prices include VAT, packing & postage)

Send remittance to:

BOFFIN PROJECTS  
4 Cunliffe Road, Stoneleigh  
Ewell, Surrey (Mail order only)

Or for more details, send 15p for lists, plus free design project sheet

A  
L  
S

A.L.S. PRESENTS OUR

E.C. 100 Watt Hi-Fi Amplifier ready drilled P.C.B. with full instructions only £2 plus 10p post.

We also supply:  
Service Sheets, Manuals, Books, etc.  
See our main advert in 'TELEVISION' or send S.A.E. for details.

10 DRYDEN CHAMBERS, 119 OXFORD ST., LONDON W1R 1PA (B).

BUILD THE



## TREASURE TRACER MK III Metal Locator

- Varicap tuning
- Excellent sensitivity and stability
- Weighs only 22oz.
- Speaker and earphone operation
- Knocks down to only 17in.
- Prebuilt search coil assembly
- Ministry approved design
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- Completely new design
- Send s.a.e. for leaflet

Complete kit Post 35p **£9-80**

Built, tested and guaranteed Post 35p **£13-75**

MINIKITS ELECTRONICS, 35 LANGLEY DRIVE, WANSTEAD LONDON E11 2LN (Mail order only)

	<b>BA NUTS BOLTS AND WASHERS</b>	Size	PER 100	W/rs	
	Assorted length bolts, shake-proof washers	0	53p	75p	29p
		2	46p	53p	22p
		4	35p	46p	18p
6		29p	35p	18p	
	<b>SELF TAPPING SCREWS</b>	Box of 100 Assrt	29p		
		<b>FASTENERS</b>	Box of 100 Assrt	51p	
		<b>5in SIDE CUTTERS</b>	Insulated Handles	59p	
		<b>5in PLIERS</b>	Insulated Handles	59p	
PVC 100 GROMMETS 1/4in dia or 1/2in hole Slate size		44p			
Post free over £2		Orders under £2 add P. & P. 15p		All prices include VAT	
<b>SILHILL PRODUCTS</b> Dept PE1 226 Mary Street, Birmingham B12 9RJ Tel. 021-440 3600					

## FM TUNER

NELSON-JONES

### PUSH BUTTON VARICAP

Tuning now available.

Six Position variable push button unit with individual frequency scales. Teak case and full metalwork matches the Texan amp.

Approved parts of this outstanding design. Featuring 0.75μV sensitivity. Mosfet front end. Ceramic I.F. strip. Triple gang tuning. S.A.E. please for lists.

### PE RONDO

We are kit stockists for this excellent design

SQ Decoder £8-00 Pre-Amp £3-00

Vol/Tone board £8-50 Power Amp board & H/S £7-50

### LIGHT EMITTING DIODES

RED only 29p each 10 + 23p

GREEN only 69p each 10 + 59p

### 7 SEGMENT LED DISPLAY

0.325in Characters 0-9 and nine letters. TTL, DTL compatible. ONLY £2-46 each, p.p. 10p.

Please add 10% V.A.T. for U.K. orders.

**INTEGREX LIMITED, DEPT. P.E.**

P.O. BOX 45, DERBY DE1 1TW

Tel.: Repton (0283 89) 3580

# LASKY'S 1974 CATALOGUE

## FREE

Send this coupon today for your free copy of Lasky's famous Hi-Fi, Audio and Electronics catalogue.

NAME .....

ADDRESS .....

AUDIOTRONIC HOUSE, THE HYDE, LONDON, NW9 6JJ

**MICROJET WELDER**  
A TINY FLAME UP TO 5000°F!  
WELDS-BRAZES SOLDERERS



INC. £12.65  
FLAME TIPS

A precision tool using a combination of butane and compressed oxygen or micro-nox. Gives a flame of pencil lead thickness. Adjustable temperatures up to 5,000°F. Lights instantly, no priming. Cuts metals, welds, brazes and solders, etc., gold and silver. Ideal for electrical work, jewellers, clockmakers, silversmiths. Up to 40 minutes' operation using fuel supplied. Replacement set of 2 micronox and 1 butane cylinders £1.45 extra inc. post. Complete with instructions.

Our price £12.65 + 35p p. & p. Send £13.00.  
JOHN DUDLEY & CO. LTD., Dept. P28  
301 Cricklewood Lane, Child's Hill, London, N.W.2  
Tel. 01-458 5917. Callers welcome.

## SWITCHES UNUSUAL

**PRESSURE MAT**—flexible, hard-wearing plastic mat containing 180 contacts. Contacts close when pressed, open when released. Rating 50V, 1A. Size 30in x 24in. £3.50.

**MINI MAT**—size 24in x 7in. £2. (Construction as above but more sensitive). Both items suitable for burglar alarm, counter, foot switch, games, seat belt indicator, alarm, door opener. Uses limited by imagination.

POSTAGE 15p PER ITEM. C.W.O.

**ELECTRONIC SWITCH DEVICES**  
P.O. Box 10, Aspley, P.D.O. Nottingham  
For further details send S.A.E.

## Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual (also available separately at 76p)

SEND 5" 7" S.A.E. FOR DETAILS TO:

**CROFTON ELECTRONICS**  
15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

**ALUMINIUM SHEET** to individual sizes or in standard packs, 3p stamp for details. RAMAR CONSTRUCTOR SERVICES, 29 Shelbourne Road, Stratford-on-Avon, Warwks.

**UFO's**. Wave Prediction Chart, 49p. TV Notes for Detection, 2 Optical Circuits, 55p. UFO Map, 42p. Daily Flight Pattern, 42p. Transistor Optical Circuit, 66p. Optical/Radiation Detector Circuit, 44p. Microdetector Circuits, with Memory, LSI, 75p. R. & E. Highlands, Needham, Suffolk.

**GLASS FIBRE P.C. BOARD**—large supplies available. 1/4 in single sided one ounce copper, 2p per sq in (under 1ft); 75p per sq ft (over 1ft). 1/2 in double sided one ounce copper, 1p per sq in (under 1ft); 81p per sq ft (over 1ft). Please add 10p per sq ft postage and packing. We can cut to your size at 1p per cut. **SOLID STATE LIGHTING**, The Firs, Smallworth Lane, Garboldisham, Diss, Norfolk.

**HARDWARE**—Screws, nuts, washers and other useful items in small quantities. Sheet aluminium to individual requirements, punched/drilled. Send 6p for list. **RAMAR CONSTRUCTOR SERVICES**, 29 Shelbourne Road, Stratford-on-Avon, Warwickshire.

## OSMABET LTD.

We make transformers amongst other things.  
**AUTO-TRANSFORMERS**, 110/200/220/240V. 500W, 20-50; 750W, 12-75; 1000W, 15-75; 2000W, 20-50; 3000W, 25-00; 4000W, 25-00, etc.  
**LOW VOLTAGE TRANSFORMERS**  
Prim. 200/240V a.c. 6.3V 6A CT, 22-10; 12V 1.5A, 22-15; 3A 22-15; 6A CT, 22-30; 18V 1.5A CT, 22-15; 24V 1.5A CT, 22-15; 3A CT, 22-85; 5A, 24-30; 8A, 26-75; 12A 29-40; 40V 3A CT, 22-75; 50V 6A CT, 21-25; 25V 2A, 4-25V 2A, 24-15.  
**L.T. TRANSFORMERS TAPPED 50V** Prim. 200/240V 0-10-12-14-16-18V 2A, 22-25; 4A, 22-40; 0-12-15-20-24-30V 2A, 22-30; 4A, 24-05; 0-6-20-30-40-60V 1A, 22-00; 2A, 24-20; 0-40-50-60-80-90-100-110V 1A, 24-20.

**MIDGHT RECTIFIER TRANSFORMERS**  
For PW rect.: 200/240V a.c. 0-0-9V 0.3A, 12-0-12V 0.25A or 20-0-20V 0.15A, £1.45 each; 9-0-9V 1A, £1.80; 12-0-12V 1A or 20-0-20V 0.75A, £1.85 each.  
**MAINS TRANSFORMERS FOR POWER AMPLIFIERS**  
Prim. 200/240V a.c. TX6 sec., 425-0-425 500 Ma, 6.3V CT 6A, 6.3V CT 6A, 9-5-6.3V 3A, £15-00; TX1 425-0-425V 250 Ma, 6.3V CT 4A, 6.3V CT 4A, 0-5-6.3V 3A, 29-40; MT3 Prim. 01-110-240V. Sec. 250V, 100 Min Amp. 6.3V 2A E-F £1.60.


**O/P TRANSFORMERS FOR POWER AMPLIFIERS**  
P.P. sec, tapped 3-8-15ohms, A-A 6.6kΩ 30W, 24-80; A-A 3kΩ 50W, 28-00; 100W (EL34 KT88, etc.) £18-50; tapped Multi 0/9 10W, 22-25.  
**G.E.O. MANUAL OF POWER AMPLIFIERS**  
Covering valve amplifiers of 30 to 400W, 80p.  
**LOUDSPEAKERS FOR POWER AMPLIFIERS**  
BAKER 25W, 26-40; 35W, 27-30; HI-FI, Major Module 20W w/ tweeter Xover, 29-20; Baker speaker lists: FANZ 50W, 110-80; 60W, 115-50; EMI 13 x 8in 3 or 15Ω, 21-80; speakers for HI-FI 5in 8Ω, 21-18; 8 x 5in 3, 8 or 15Ω 21-75.

**LOUDSPEAKERS**  
2 1/2in 3, 8, 16 or 75Ω, 2 1/2in 25Ω, 3in, 3, 8 or 25Ω, 3 1/2in 8, 16 or 80Ω, 80p; 5in 3, 8, 15, 25 or 36Ω, 5 x 3in 3, 8 or 25Ω 21-05; 6 1/2in 3Ω, 6 x 4in 25Ω, 7 x 4in 3, 15 or 25Ω, 8 x 2 1/2in 3Ω 21-28; 8 x 5in 15 or 25Ω 21-50; 10 x 6in 3Ω 21-50.  
**SPEAKER MATCHING TRANSFORMERS**  
12W 3 to 8 or 15Ω up or down, 21-15.  
**BULK TAPE ERASERS**  
Instant erasure, tape spools, cassettes, demagnetises tape heads a.c. 200/240V a.c. 22-50 plus P. & P.

**CONDENSERS**  
Paper, tubular W/E 2-2mtd 250V Xovers, etc. 15p, 25p per 100; Block 4mtd 800V, 75p; 8mtd 750V, 75p; Electrolytic, 900mtd 360V, 50p; 200+100+100/360V, 80p. V.A.T. extra on all orders.

Carriage extra on all orders.  
**S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY**  
46 Kenilworth Road, Edgware, Middx. HA8 6YG  
Tel. 01-958 9314
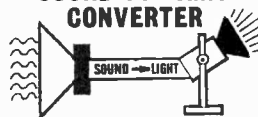
## SINGLE CHANNEL SOUND-TO-LIGHT CONVERTER



**WITH LIGHT DIMMER**  
Max. Load 2kW at 250V a.c.


Price includes ready built and tested module, edge connector/mounting bracket, dimmer potentiometer, audio sensitivity potentiometer, full connecting data. Price £7.90 inc. VAT + 25p P. & P.  
**EXTRA FACILITIES**. Push-button for Manual Pulsing, 25p extra. Photocell for turning on the lights as the ambient light decreases, 75p extra.

## THREE CHANNEL FILTER UNIT

When used with three single channel modules this unit filters the sound into bass, middle and top frequencies enabling three coloured light displays to be shown. Independent sensitivity controls on each channel. Ready built and tested.

Price £23.40 inc. VAT + 15p P. & P.

## OIL WHEEL PROJECTOR

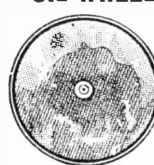

Build your own using our **MULTI-COLOURED OIL WHEEL AND MOTOR KIT**. Suitable for mounting on virtually all Slide Projectors.

Kit contains:

- ★ 6in dia. or 4in dia. OIL WHEEL (please state size required when ordering).
- ★ Suitable Miniature mains motor.
- ★ Full instructions.
- ★ For Professional Discotheque use or home enjoyment. Price £7.15 inc. VAT & P. & P.

## ELECTRONIC COMPONENTS BARGAIN COMPONENT PACKS

- Pack No.
- 1 500 Carbon resistors, 1%, 1, 1, 2W.
  - 2 100 Electrolytic Condensers.
  - 3 250 Ceramic, Polystyrene, Silver Mica, etc. Condensers.
  - 4 250 Polyester, Polycarbonate, Paper, etc. Condensers.
  - 5 25 Potentiometers, assorted.
  - 6 250 High-stab. 1%, 2%, 5% resistors.
  - 7 30 Assorted Tagstrip.
  - 8 110 wt. Assorted Nuts, bolts, washers, spacers, etc.
  - 9 25 Assorted switches, rotary, lever, micro, toggle, etc.
  - 10 50 Preset Potentiometers.

ALL COMPONENTS NEW AND UNUSED  
£1 + 25p P. & P. per pack 25 for 5 packs post free.

## G.T. ELECTRONICS

267 Acton Lane, London W4 5DG  
01-994 6275

## Dimmit


range of light dimmers

Illustrated is the popular PMSD1000 module. A 1000W quality dimmer, linear operation; interference suppression, 60mm slider range; size 12 x 5 x 4 cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studios, etc. Complete with scale plate, fixing screws and full instructions. £5.50 inc. VAT, add 10p P. & P.

Also available in 2kW, with separate heatsink. The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for use on lamps, heaters, motors, etc. Rotary and Slider control versions. Ratings: 400W, 1,000W, 2,000W.

**NEW** addition to Dimmit range—Model SL800 sound to light converter. Modulates the light in time with sound. Built-in microphone. Just place unit near any sound source—radio, hi-fi, tv, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Black A1 case—size 12 x 4 x 7cm. Full instructions. £6.50 inc. VAT, add 10p P. & P. Send 10p for complete illustrated catalogue and price list.

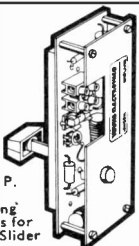**YOUNG ELECTRONICS** Mail Order Dept.  
54 Lawford Road, London NW5 2LN. Telephone 01-267 0201



## DEEPPATCH SYSTEM

for **EDUCATION - EXPERIMENT - DESIGN**  
BUILD A CIRCUIT IN SECONDS. NO SOLDERING. CONNECTION BY MINIATURE GOLD PLATED STACKING PLUGS.

- Unit 1 £3.50 will carry 3 D.I.L. 14 PIN IC's
- Unit 2 £3.50 will carry 2 D.I.L. 16 PIN IC's
- Unit 3 £4.60 6 L.E.D. indicators with driver
- Unit 4 £3.90 OP 'AMP' with variable resistor and discrete components wired in
- Unit 5 £3.80 Dual clock generator and monostable
- Unit 6 £3.90 Output stage for audio or D.C. amplification with transistors and relay sockets
- Unit 15 £0.75 Logic indicator probe
- Unit 13 £0.60 Set of stack plug links. 4 each short, medium, long and stack plug—croc clip links
- Unit 10 £7.90 5V regulated power supply with circuit protection Post and packing 10p per order. Please add 10% VAT to total cost of order including postage.

Other units, components and accessories available. Send for details to:

**D. WOOD - ELECTRONICS**  
17 Wellmeadow Lane, Uppermill, Oldham, Lancs. Tel.: Saddleworth 5177



**BRAND NEW**

**SEMICONDUCTORS AND COMPONENTS**

**GUARANTEED**

WE SUPPLY NEARLY ALL THE COMPONENTS FOR PROJECTS ADVERTISED IN THIS MAGAZINE

**TRANSISTORS**

2G901	0-15	2N3414	0-10
2G902	0-15	2N3415	0-10
2G903	0-25	2N3416	0-15
2G906	0-80	2N3417	0-81
2G909	0-80	2N3570	1-25
2G948B	0-25	2N3571	1-12
2G971	0-15	2N3572	0-17
2G974	0-15	2N3702	0-11
2N174	1-40	2N3703	0-10
2N404	0-48	2N3704	0-14
2N456	0-75	2N3705	0-10
2N466A	0-75	2N3706	0-09
2N467A	0-80	2N3707	0-13
2N491	8-25	2N3708	0-07
2N896	1-18	2N3709	0-09
2N897	1-21	2N3710	0-12
2N898	0-25	2N3711	0-10
2N899	0-52	2N3712	0-08
2N706	0-16	2N3713	1-95
2N706A	0-18	2N3714	2-29
2N708	0-18	2N3715	1-23
2N711	0-80	2N3716	3-00
2N718	0-21	2N3773	3-15
2N718A	0-49	2N3779	3-15
2N720	0-50	2N3790	4-01
2N721	0-55	2N3794	2-06
2N914	0-22	2N3791	2-08
2N916	0-41	2N3792	2-20
2N918	1-50	2N3794	0-10
2N929	0-18	2N3813	0-82
2N930	0-48	2N3820	0-47
2N1090	0-23	2N3823	1-42
2N1091	0-24	2N3824	1-33
2N1131	2-82	2N3826	0-23
2N1132	0-58	2N3854	0-18
2N1302	0-16	2N3854A	0-19
2N1303	0-16	2N3855	0-19
2N1304	0-20	2N3856	0-19
2N1305	0-20	2N3856A	0-20
2N1306	0-22	2N3858	0-17
2N1307	0-25	2N3858A	0-19
2N1308	0-25	2N3859	0-18
2N1483	0-90	2N3859A	0-18
2N1607	0-24	2N3860	0-20
2N1613	0-33	2N3866	1-69
2N1631	0-36	2N3877	0-25
2N1637	0-36	2N3877A	0-28
2N1701	1-32	2N3900	0-20
2N1702	2-15	2N3900A	0-21
2N1711	0-45	2N3901	0-32
2N1893	0-81	2N3903	0-24
2N2102	0-30	2N3915	0-27
2N2147	0-70	2N3905	0-24
2N2148	0-94	2N3906	0-27
2N2192	0-40	2N4036	0-46
2N2192A	1-21	2N4037	0-40
2N2193	0-40	2N4038	0-18
2N2193A	0-81	2N4039	0-20
2N2194	0-78	2N4040	0-11
2N2194A	0-80	2N4061	0-11
2N2195	0-87	2N4062	0-11
2N2196A	0-18	2N4302	0-25
2N2218A	0-88	2N4303	0-47
2N2219	0-57	2N4916	0-20
2N2219A	0-88	2N4917	0-17
2N2220	0-45	2N4918	0-75
2N2221	0-41	2N4919	0-84
2N2221A	0-83	2N4920	0-99
2N2222	0-60	2N4921	0-73
2N2222A	0-81	2N4922	0-84
2N2368	0-21	2N4923	0-83
2N2369	0-37	2N5172	0-12
2N2369A	0-43	2N5174	0-23
2N2646	0-77	2N5175	0-26
2N2647	1-20	2N5176	0-32
2N2711	0-30	2N5190	0-92
2N2712	0-12	2N5191	0-98
2N2713	0-17	2N5192	1-24
2N2714	0-18	2N5193	1-01
2N2904	0-58	2N5194	1-10
2N2904A	0-70	2N5195	1-40
2N2905	0-71	2N5245	0-43
2N2906A	0-88	2N5245	0-49
2N2906	0-86	2N5458	0-46
2N2906A	0-70	2N5459	0-49
2N2907	0-79	3N128	0-73
2N2907A	0-88	3N136	0-82
2N2923	0-12	3N138	1-42
2N2924	0-14	3N140	0-92
2N2925	0-17	3N141	0-81
2N2926	0-26	3N142	0-58
Green	0-12	3N143	0-75
Yellow	0-10	3N152	0-82
Orange	0-10	3N153	0-81
2N3053	0-32	3N154	0-84
2N3054	0-76	3N159	1-17
2N3055	0-85	3N187	1-55
2N3390	0-28	3N200	2-49
2N3391	0-28	3N201	1-05
2N3391A	0-29		
2N3392	0-13		
2N3393	0-18		
2N3394	0-17	40050	0-78
2N3402	0-18	40251	0-81
2N3403	0-19	40309	0-30
2N3404	0-24	40310	0-50
2N3405	0-27	40313	0-62

**KELLNER CONSTRUCTION KITS**

**WE ARE THE SOLE DISTRIBUTORS IN U.K.**

ES3	3 watt Mono Transistor Amplifier Kit	£4.00
ES15	15 watt Hi-Fi Transistor Amplifier Kit [two for stereo] with Tone Control and Pre-Amp	£11.94
ES30	30 watt Mono Hi-Fi Power Amplifier	£8.32
ES50	50 watt Mono Hi-Fi Power Amplifier	£9.53
EV3	Distortion Compensated Pre-Amplifier	£3.00
AV7	Aerial Amplifier. LW, SW, MW, VHF. TV Channels 2-12	£1.83
UH87M	FM Transmitter Kit. 65mHz-145mHz. A GPO Licence is required	£2.52
MUE7	Short Wave and VHF Receiver Kit. Companion to UH870	£2.83
EW18	Electronic Dice Kit	£5.91
EW20	Electronic Dice with Sensor Button	£6.84
ST800	Strobe Light Kit, 120W/8	£7.11
LO1000	Psychelidic Light Control, single channel	£7.00
LO350	Psychelidic Light Control, three channel	£13.50
NT15	Power Supply—4 to 30V, 1.5W	£6.75
NT85	Professional Stabilized Power Supply, 5 to 70V, 2A	£11.34
D800	800W Light Dimmer Speed Control	£2.70
WT7	Aircraft Communications Tuner 110-130mHz. Built and aligned	£14.00
WT9	Transmitter VFO for 2 meters [144mHz-146mHz]. Built and aligned	£14.00

**TTL LOGIC I.C.'s**

SN7400	28p	SN7430	28p	SN7472	40p
SN7401	38p	SN7432	48p	SN7473	40p
SN7402	28p	SN7433	62p	SN7474	48p
SN7403	56p	SN7434	52p	SN7475	96p
SN7410	22p	SN7441	75p	SN7476	64p
SN7411	22p	SN7442	79p	SN7481	£1.25
SN7413	48p	SN7443	£1.04	SN7483	£1.00
SN7420	20p	SN7444	£1.04	SN7484	95p
SN7421	22p	SN7445	£1.85	SN7485	£1.20
SN7422	48p	SN7446	£2.00	SN7489	£1.00
SN7423	52p	SN7447	£1.30	SN7491	£1.00
SN7425	32p	SN7450	20p	SN7493	£1.00
SN7427	48p	SN7451	20p	SN7494	85p
SN7428	48p	SN7452	20p	SN7495	80p
SN7428	50p	SN7454	28p	SN7496	£1.00

We also stock the unusual numbers as follows:

SN74100	2-50	SN74153	1-63	SN74176	1-50
SN74107	0-43	SN74154	2-00	SN74180	1-55
SN74118	1-00	SN74155	1-55	SN74181	7-00
SN74119	1-92	SN74157	1-80	SN74180	1-95
SN74121	0-60	SN74161	2-60	SN74192	1-90
SN74122	1-35	SN74161	2-60	SN74192	1-90
SN74123	1-35	SN74164	2-20	SN74173	1-90
SN74141	0-90	SN74165	4-00	SN74196	1-60
SN74145	1-50	SN74167	6-25	SN74198	4-60
SN74150	3-35	SN74174	1-80	SN74199	4-00
SN74151	1-10	SN74175	3-00		

**BRIDGE RECTIFIERS**

PIV	50	100	200	400	600
1A	24p	26p	35p	45p	40p
2A	32p	37p	41p	46p	52p
4A	80p	70p	75p	85p	95p
6A	62p	75p	80p	£1.10	£1.25

**DIODES AND RECTIFIERS**

IN5171 (1.5A 50pV)	8d	IN5402 (3A 200pV)	80p
IN5172 (1.5A 100pV)	9p	IN5404 (3A 400pV)	82p
IN5173 (1.5A 200pV)	10p	CL7000 (3A 600pV)	25p
IN5174 (1.5A 400pV)	11p	CL7006 (3A 800pV)	27p
IN5176 (1.5A 600pV)	12p	CL7007 (3A 1000pV)	30p
IN5177 (1.5A 800pV)	15p	CL1002 (10A 100pV)	85p
PL4007 (1.5A 1000pV)	20p	CL1003 (10A 200pV)	47p
IN5400 (3A 50pV)	15p	CL1004 (10A 400pV)	47p
IN5401 (3A 100pV)	17p	CL1005 (10A 600pV)	56p

NE555 TIMER I.C. 90p.  
NE560 PHASE LOCKED LOOP, £4.48.  
SCORPIO IGNITION KIT for improved performance £10 + 50p P. & P.

**ANODE AND CATHODE STUD**

IN1183 (35A 50pV)	92p	IN1188 (35A 400pV)	£2.66
IN1184 (35A 100pV)	£1.12	IN1190 (35A 600pV)	£2.16
IN1186 (35A 200pV)	£1.57		

**CATHODE STUD ONLY**

IN3766 (35A 800pV)	£3.65	IN3768 (35A 1000pV)	£4.20
IN384	10p	BA141	17p
IN384	7p	BA142	17p
IN384	7p	BA143	17p
IN384	7p	BA144	12p
AA119	7p	BA145	17p
AA129	15p	BA154	12p
BA100	15p	BY100	15p
BA102	25p	BY126	15p
BA110	25p	BY127	17p
BA113	7p	BY140	£1
BY237	12p	OA79	7p
BY211	35p	OA81	8p
BY211	32p	OA85	10p
BY212	80p	OA90	7p
OA9	10p	OA91	7p
OA10	20p	OA95	7p
OA47	71p	OA200	7p
OA70	71p	OA202	10p
OA73	10p	OA210	27p

**All prices plus 10% VAT and plus 15p post & packing.**  
**All kits with easy to follow instructions and covered by a full guarantee.**

BC301	0-34	BFS21A	2-30	MJ421	0-88
BC302	0-27	BFS28	0-82	MJ430	0-75
BC303	0-54	BFS91	0-27	MJ440	0-71
BC303	0-54	BFS98	0-28	MJ480	0-75
BC307	0-10	BFW10	0-61	MJ481	0-85
BC307A	0-10	BFW11	0-61	MJ490	0-84
BC308	0-09	BFX13	0-23	MJ491	1-10
BC308A	0-09	BFX29	0-30	MJ802	4-12
BC308B	0-09	BFX30	0-25	MJ901	4-85
BC309	0-10	BFX37	0-30	MJ1001	2-34
BC309A	0-10	BFX44	0-33	MJ1800	1-88
BC327	0-24	BFX63	0-28	MJ2500	2-82
BC327	0-24	BFX68	0-68	MJ2501	3-25
BC328	0-22	BFX84	0-24	MJ2855	1-00
BC337	0-19	BFX85	0-29	MJ3000	2-47
BC338	0-19	BFX98	0-20	MJ3001	2-79
BCY30	0-43	BFX87	0-28	MJ3701	0-93
BCY31	0-51	BFX88	0-25	MJ4502	4-44
BCY32	1-15	BFX89	0-45	MJ4504	0-47
BCY33	0-34	BFY10	0-35	MJ4570	0-73
BCY34	0-35	BFY11	0-46	MJ4571	0-60
BCY38	0-53	BFY17	0-60	MJ4572	0-69
BCY39	0-05	BFY18	0-35	MJ4573	0-72
BCY40	0-81	BFY19	0-36	MJ4574	1-93
BCY42	0-15	BFY20	0-50	MJ4575	1-57
BCY43	0-15	BFY29	0-40	MJ4580	1-19
BCY58	0-21	BFY37	0-20	MJ4590	1-58
BCY59	0-22	BFY44	0-43	MJ4595	1-65
BCY70	0-17	BFY43	0-65	MJ4595	0-83
BCY71	0-22	BFY50	0-22	MM1613	0-43
BCY72	0-13	BFY51	0-18	MM1711	0-49
BCY87	3-47	BFY52	0-20	MM1712	0-64
BCY88	2-40	BFY53	0-15	MM2712	0-84
BCY89	0-87	BFY56	0-34	MPF102	0-81
BCY90	0-85	BFY64	0-41	MP8111	0-32
BD111	0-50	BFY76	0-22	MP8112	0-40
BD115	0-75	BFY77	0-24	MP8113	0-47
BD116	0-50	BFY78	0-36	MPSA05	0-25
BD121	0-75	BFY90	0-60	MPSA06	0-20
BD123	0-82	BFY99	0-38	MPSA12	0-40
BD124					

# BUILD A CHORDING PROFESSIONAL SYNTHESISER



The Synthesiser shown above is the Dewtron "Apollo" A.1, which we sell ready-built to professionals. Believe it or not, it uses the SAME precision modules as we sell to you, the Constructor, to build any kind you like. The revolutionary Modumatrix system of routing makes old-fashioned patching a thing of the past. VCO-2 voltage-controlled oscillator module has accurate built-in log-law for chording and other professional effects. 3 and 4 octave keyboards and contacts. **VCO-2 STABLE, PRECISION V/C OSCILLATOR** gives SINE, TRIANGULAR AND SQUAREWAVE outputs, 1 volt/octave voltage control. £24 each or £27 each 2 or more matched. **SHE-1 SAMPLE, HOLD AND ENVELOPE MODULE** gives variable attack, sustain, touch sensitive playing when used with VCO-2 signals. £17. OFT-1 chording module £9. Modules (except VCO-1) guaranteed two years.

With over 7 years' unblemished reputation in these pages, Dewtron continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to leading groups. Our modules are used in professional equipment by other manufacturers and in our own built synthesisers, e.g. "Gipsy" G.I. Approved by a Musical Association. Send 15p for full catalogue of our famous musical effects.

## D.E.W. LTD.

254 Ringwood Road, FERNDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

**PROFESSIONAL MODULES CASH SAVINGS**

by buying modules and parts in bulk! All modules are available separately: Ring Modulator RM2, £8. Voltage-controlled Oscillator VCO1, £10.50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £10. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £13. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £10. etc., etc. ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE. Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £5.50. REVERB Module and spring unit £15. V.A.T. 10% extra. V.A.T. paid orders over £75.

# CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER DEPT. No. 11 MAYES RD. LONDON N22 6TL

**COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR**  
OUR SHOPS ARE OPEN ALL DAY FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY (WE CLOSE ALL DAY THURSDAY)  
13 SOUTH MALL, EDMONTON, N.9 803 1685

### "CRESCENT" BUBBLE LIGHT SHOW

A new and exciting feature for the professional disc jockey or to give the private party an electric atmosphere, a projected kaleidoscope of colour makes the music you produce more interesting and will appeal to the visual as well as the audio senses. This budget system compares very favourably with the more sophisticated and much higher priced models. Specification—Projector: 150W, convection cooled, at 30ft the projected image = 16ft; Motor: 1 rev per 2 min. Liquid Wheel: 6in diameter multicolour. The Motor is fitted to the Projector and can only be purchased as a single unit. The Liquid Wheel, however, is our very popular standard model & may be purchased separately. A bargain—Projector with Motor ready for instant use. £15; 6in Liquid Wheel, £5 = £20 + 75p carr.

### TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7.1 or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Our Price £2.75 plus 10p P. & P. Same model suitably wired for the Philips Cassette £3 plus 10p P. & P.

### TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. x 3 1/2in. x 1 1/2in. This converter supplies 6, 7.1 or 9 volts and is transistor regulated. A real money saving device for £2.50 plus 10p P. & P.

### MINI LOUDSPEAKERS

2 1/2in 80 ohm, 50p; 2 1/2in 40 ohm, 50p. Please include 5p P. & P. on each L.S.

### DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. £29.50 + 50p P. & P. Please send S.A.E. if you require more information.

V.A.T. From 1st April, 1973, will you please include on your Total (Goods plus Postage and Packing) Value Added Tax at the Standard Stated Rate.

### "CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U.BUILD.IT

We supply the three modules for you to build this Disco Group-P.A. amplifier into the cabinet of your choice. ★ THE POWER AMP MODULE TP100W 170W R.M.S. sq. wave 300V instantaneous peak into 8 ohm (60W into 16 ohm). £14.25, carr. 45p. ★ THE PRE-AMP MODULE Four control pre-amp. Vol., Bass, Treble, Middle controls. Designed to drive most amplifiers using F.E.T. first stage. £3.96, carr. 25p. ★ THE POWER SUPPLY MODULE PS100

is supplied complete with the mains transformer. £9.96, carr. 50p. Complete firing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. If you purchase all three modules, £25, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

### TWO WAY STEREO ADAPTOR

Stereo Jack plug to two stereo free sockets, complete with 110mm cable. For connecting two stereo inputs into one. A bargain at 65p. plus 5p P. & P.

### EMI LOUDSPEAKER 450

10W 13in x 8in x two 2 1/2in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. £3.75 plus 38p P. & P. each.

### 7in x 4in LOUDSPEAKER

A top quality speaker ideal where small size is important. Manufactured by E.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1.80. Free postage on this item.

### CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 25p, C90 35p, C120 45p plus 5p P. & P.

### 3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) £18.50 plus 38p P. & P. If you require more information please send S.A.E.

### "CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT

This fantastic little box approx. 4" x 3" x 2 1/2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fused and cannot harm your amplifier. A Bargain at £7.50 plus 10p.

### LOW VOLTAGE AMPLIFIER

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier. £1.75 plus 13p P. & P.

# FREE!

## Over 150 ways to engineer a better future

**HIGHER PAY**      **A BETTER JOB**

**SECURITY**

### find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained thousands of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

#### Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course". - Student D.L.B., Yorks.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects". - Student J.A.O., Dublin.

"My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold". - Student C.C.P., Bucks.


#### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to **B.I.E.T. Dept. BPE11, Aldermaston Court, Reading RG7 4PF.**

Published approximately once each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Anlover, Hants. Sole Agents for Australia and New Zealand: The Bookery (A/sia) Ltd., South Africa - Central News Agency Ltd. Publishers: Subscription Rate (including postage): For one year to any part of the world £27.50. Practical Electronics is sold subject to the following conditions, namely: (A) It shall not be lent, resold or hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown; (B) It shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover; (C) It shall not be used for advertising or other promotional purposes; (D) It shall not be used for any other purpose without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover or by way of Trade, or for any other purpose whatsoever.

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

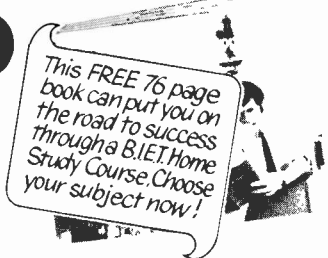Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.



**CUT OUT THIS COUPON**

Tick or state subject of interest. Post to address below.

<input type="checkbox"/> MECHANICAL Society of Engineers— A.M.S.E. (Mech.) Institute of Engineers & Technicians (A.M.I.E.) CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding Gen. Diesel Eng. Sheet Metal Work. Eng. Inspection Eng. Metallurgy	<input type="checkbox"/> DRAUGHTSMANSHIP Institute of Engineering Designers (A.M.I.E.D.) General Draughtsmanship Elec. Draughtsmanship Architectural Draughtsmanship Technical Drawing	<input type="checkbox"/> A.B.T. Clerk of Works Construction Surveyors Institute—(C.S.I.) CITY & GUILDS General Building (all branches) Heating & Vent. Inst. Clerk of Works Site Surveying Health Engineering Road Construction Quantities, Estimates Hydraulics Structural Eng.
<input type="checkbox"/> ELECTRICAL & ELECTRONIC Society of Engineers— A.M.S.E. (Elec.) CITY & GUILDS Gen. Electrical Engineering Electrical Installations Electrical Maths Computer Electronics Electronic Eng. Practical Radio & Electronics (with kit)	<input type="checkbox"/> RADIO & TELE-COMMUNICATIONS CITY & GUILDS, Radio, TV Electronics CITY & GUILDS Telecoms. Gen. Radio & TV Eng. Radio Amateurs Exam Radio Servicing TV Servicing Colour TV	<input type="checkbox"/> GENERAL Agricultural Eng. Council of Eng. Institutions Farm Science Plastics
<input type="checkbox"/> MANAGEMENT & PRODUCTION Institute of Cost & Management Accntnts. Computer Programming Works M'nt. Work Study Gen. Production Eng. Estimating & Planning Storekeeping Management Skills Quality Control	<input type="checkbox"/> AUTOMOBILE & AERONAUTICAL Institute of the Motor Industry A.M.I. MAA IMI CITY & GUILDS Auto Eng. Gen. Auto Eng. Motor Mechanics Auto Diesel Eng. Garage M'nt. ARB Aero Engineering Certs. Gen. Aero Eng	<input type="checkbox"/> Supplementary courses for Nat. Certificates.
<input type="checkbox"/> CONSTRUCTIONAL Society of Engineers— A.M.S.E. (Civ.) Institute of Building—L.I.O.B.		<input type="checkbox"/> <b>G.C.E.</b> - choose from 58 'O' & 'A' level subjects.

*Teaching for many years, and using C.A. and other modern methods.*

## POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. BPE11 Aldermaston Court, Reading RG7 4PF QN BPE11

NAME \_\_\_\_\_  
Block Capitals Please  
ADDRESS \_\_\_\_\_


OTHER SUBJECTS \_\_\_\_\_

AGE \_\_\_\_\_

Accredited by C.A.C.P.  
**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**
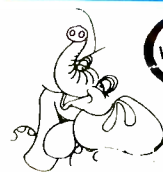
# Henry's

**DONT RELY ON YOUR MEMORY**  
**BUY NOW AT BARGAIN PRICES**  
 Order your latest Henry's Catalogue Price 55p post paid  
 complete with Discount Vouchers



You pay less  
 VAT with Henry's  
 Low Prices

Now built and  
 used by thousands of  
 satisfied cus-  
 tomers.

**FEATURES:** slim  
 design, covers size in  
 cabinet 15 1/2in x 2 1/2in x 6 1/2in

6-IC's, 10 transistors, stabilisers,  
 Gardners low field transformer, Fibre  
 Glass P.C. Panel, complete chassis work.  
 Now available built and tested as well  
 as in kit form.

**HIGH QUALITY & STABILITY ARE  
 PREDOMINATE FEATURES—DEVELOPED  
 TEXAS ENGINEERS FOR PERFORMANCE, BY  
 RELIABILITY AND EASE OF CONSTRUCTION.**

**FACILITIES.** On/off switch indicator, headphones  
 socket, separate treble, bass, volume and balance controls,  
 scratch and rumble filters, mono/stereo switch, input selector;  
 Mag. P.U., Radio Tuner, Aux. Can be altered for Mic, Tape, Tape-head, etc.  
 Constructional details Ref. No. 21, 30p.  
 Distributed by Henry's throughout UK.


**FREE** Teak cabinet with complete kit.

**KIT** (+ VAT + 50p  
**PRICE** £28.50 carr/packing) or  
**built and** (+ VAT + 50p  
**tested** £35.00 carr/packing)  
 as illustrated
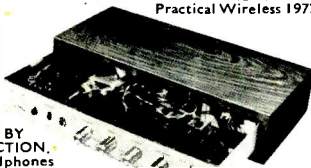
## BUILD THE TEXAN

**20 + 20 WATT IC STEREO  
 AMPLIFIER**

As featured by  
 Practical Wireless 1972



## TEXAN STEREO SYSTEM

**PLUS Price Savings**



The Texan Stereo Systems include  
 the high quality Texan Stereo  
 amplifier assembled and ready to  
 use. A pair of Type 200 20 watt  
 Speaker-Tweeter systems, size  
 12.12 x 10in and a choice of  
 Garrard players built into a  
 plinth with cover with Goldring  
 G800 magnetic cartridge. System  
 25 uses Garrard SP25 Mk.III and  
 system 76 the Garrard AP76 de  
 luxe turntable. All necessary  
 leads are supplied.

**SYSTEM 25** (list approx. £109)  
 £79.50  
**SYSTEM 76** (list approx. £117)  
 £89.50  
 (plus 10% VAT and plus £1.45  
 carr/packing).

### BARCLAYCARD/ACCESS

Call, write or phone your order  
 01-402 4736.  
**EASY TERMS FOR CALLERS**

Stereo Preamplifier .. £11.95  
 Audio Filter Unit .. £6.95  
 Z40 15 watt Amplifier .. £5.45  
 Z60 25 watt Amplifier .. £6.95  
 PZ6 Mod. for 1 on 2 Z40 .. £4.98  
 PZ Mod. (S Tab) 1 on 2 .. £7.98  
 Z40 .. £7.98  
 PZ8 Mod. (S Tab) 1 on 2 .. £7.98  
 Z60 .. £7.98  
**TRANSFORMER FOR**  
**PZ8** .. £2.95  
**NEW FM TUNER** .. £11.95  
**STEREO DECODER** .. £7.45  
 All items post paid—Best price  
 on request.

## BUILD THE NEW HENELEC STEREO FM TUNER

A completely new high stability stereo FM tuner. Features variable  
 capacity diode tuning, stabiliser power supply, IC Decoder, high gain  
 low noise, IF stages, LED  
 indicators, Tuning meter, AFC.

Easy to construct and use.

Mains operated. Slim

modern design with fibre

glass PC, teak cabinet,

etc. Available as a kit to

build or ready built.

Overall size: 8in x 2 1/2in

x 6 1/2in. Produced to give


high performance with a

realistic price. (Parts list

and constructional details

Ref. No. 5, 30p.) Henry's

are sole distributors UK and Europe.

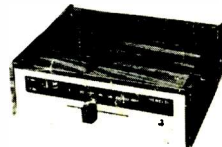

**Kit Price** £21.00 (+ VAT)  
 or built and tested £24.95 (+ VAT)

**LIVING SOUND LOW NOISE TOP QUALITY CASSETTES  
 MADE BY EMI TAPES LTD. TO INTERNATIONAL  
 STANDARDS ESPECIALLY FOR HENRY'S. ALL POST PAID  
 LESS THAN 1 REC. PRICES. COMPLETE WITH LIBRARY  
 CASES.**

	3 for	6 for	10 for	25 for
C60	£1.00	£1.80	£2.80	£6.75
C90	£1.33	£2.57	£4.20	£10.25
C120	£1.62	£3.15	£5.00	£12.25



Quantity and trade enquiries invited.

**LEARN A LANGUAGE**—complete with phrase book. German,  
 French, Spanish, Italian. £1.36 per course. £5 for any 4.

## LOW COST HI-FI SPEAKERS SPECIAL OFFERS

EMI 13in x 8in—full range speakers (post 20p each or 30p pair);  
 \*150TC—8 ohms Twin Cone 10 watt, £2.20 each or £4.40 pair; \*450 10  
 watt c/o Twin Tweeters 3, 8 or 15 ohms, £3.50 each or £7.00 pair; EVV  
 15 watt 8 ohms c/o Tweeter, £4.30 each or £7.90 pair; 350 20 watt  
 c/o Tweeters 8 or 15 ohms, £7.50 each or £14.20 pair

\* Polished wood cabinet £4.60, post 35p.

**8 ohms full range (post 20p)**  
 FR4 4in 5 watt, £4; FR65 6 1/2in 10 watt, £5.50;  
 FR8 8in 15 watt, £7.60; FR23 9 x 6in 15 watt,  
 £6.00.

**BASS AND MID RANGE—8 ohms (post 20p)**  
 A112 5in 15 watt, £3.20; B110 5 1/2in 15 watt,  
 £5.60; R200 8in 15 watt, £6.45; B139/2 13in x 8in  
 30 watt LF, £10.25.

**TWEETERS AND CROSSOVERS (post 20p)**  
 K2006 10 watt 8 or 15 ohms, £1.90; FHT6 15 watt 8 ohms, £3.20; K2011  
 30 watt 8 ohms, £3.75; T27 KEF, £4.25; Axcnet 100 30 watt 8 ohms,  
 £4.90; K4009 1kHz/5kHz c/o, £2; SN75 3kHz var. c/o, £1.75.

**SPEAKER KITS (carr. etc. 35p)**  
 20-2 8in 30 watt, £10 each; 20-3 8in 40 watt, £15 each; LINTON 2  
 20 watt, £15.95 pair; GLENDALE 3 30 watt, £28.95 pair; DOVEDALE 3  
 50 watt, £42 pair; KEF KK2, £20.40 each; KEF KK3, £32 each

## BUILD YOURSELF A POCKET CALCULATOR

A complete kit, packaged in a polystyrene con-  
 tainer and taking about 3 hours to assemble—  
 that's the Sinclair Cambridge pocket calculator  
 from Henry's. Some of the many features include  
 interface chip, pick-film resistor pack, printed  
 circuit board, electronic components pack.  
 Size: 4 1/2in long x 2in wide x 1 1/2in deep.  
 Free of charge with the kit for the more advanced  
 technologist is a 32-page booklet explaining how  
 to calculate Logs, Tangents, Sines, etc.



**Price** £24.95 (+ VAT)

Also assembled £27.22 (+ VAT)  
 ready to use

## EARN YOURSELF EASY MONEY, WITH PORTABLE DISCO EQUIPMENT



**DISCO MINI:** A complete portable disco,  
 fitted mixer/preamp, 2 decks all facilities... £98.50  
 As above but with Slider Controls... £118.50  
 100 watt amplifier for above... £42.50  
**SL100:** 100 watt mixer/amplifier with  
 slider controls... £69.00  
**R50:** 50 watt mixer/amplifier... £49.50  
**R100:** 100 watt mixer/amplifier... £57.50  
**DISCO AMP:** 100 watt mixer/amplifier  
 chassis unit... £69.50  
**DISCO MIXER/PREAMPLIFIERS (O/P**  
**for up to 6-100 watt amplifiers):**  
**SDL1** (rotary controls):... £49.50  
**SDL11** (slider controls):... £58.50  
**DISCO VOX** (slider controls): The complete  
 disco preamp... £69.50  
**DJ100:** 100 watt power amplifier for above... £42.50  
**DJ30L:** 3 channel 3kV sound to light... £31.50  
**DJ40L:** as 30L plus built-in microphone... £38.75  
**DIMAMATIC:** 1kV adjustable speed auto  
 dimmer... £25.00  
**Carlsbro Reverberation Unit**... £44.00  
**SCENE STROBE**... £19.00  
**ROAD STROBE**... £25.00  
**SUPER STROBE**... £45.00  
 Disco anti-feedback microphone... £11.95  
 Cole 150 watt liquid wheel projector... £22.50  
 150 watt QI liquid wheel projector... £50.00  
 150 watt QI cassette wheel projector... £50.00  
 Spare Effects and Liquid cassettes, large  
 range of patterns... £6.00  
 Mini spot bank fitted 3 lamps... £12.95  
 Auto Trilite (mini with flashers)... £17.00  
 Bubblemaster with 1 gal. liquid... £41.15  
**MIXERS/MICS/SPEAKERS/LIGHTING**  
 U.K.'s largest range of Disco lighting  
 6in liquid wheels... £5.00  
**FREE** stock list Ref. No. 18 on request.  
**AKG/RESLO/DJ/CARLSBRO/EAGLE**  
**CHASSIS AND COMPLETE SPEAKER**  
**SYSTEMS, MEGAPHONES, TURNTABLES,**  
**PUBLIC ADDRESS COMPONENTS, MICS.,**  
**STANDS, MIXERS, CABINETS**



All prices carr. paid (UK) (VAT EXTRA).  
 Barclaycard/Access call, write or phone your order  
 01-723 6963—easy terms for callers.

**10% VAT TO BE ADDED TO ALL ORDERS.**

Prices and descriptions correct at time of press E & OE. See pages 1106, 1107, and 1108 of this  
 magazine. Like a permanent job at Henry's? Experience and trainee salesmen required. Tel. 01-402 8791.

**Henry's** RADIO  
 LIMITED  
 EDGWARE ROAD, W2

404-406 Electronic Components and Equipment 01-402 8381  
 354-356 High Fidelity and Tape Equipment 01-402 5854, 4736  
 309 P.A. Disco Lighting High Power Sound 01-723 6963  
 303 Special offers and bargains store  
 All mail to 303 Edgware Road, London W2 1BW

Open 7 days a week  
 10.30am to 6.00pm  
 Mon-Sat all day  
 Saturday