

**ADC081S051,ADC081S101,ADC101S051,  
ADC101S101,ADC121S051,ADC121S101,  
LMP2011,LMP2012,LMP7711,LMP7712**

*Amplifier Closed-Loop Bandwidth Considerations in High Resolution A/D  
Converter Applications*



Literature Number: SNOA829



## Amplifier Closed-Loop Bandwidth Considerations in High Resolution A/D Converter Applications

By Jerry Freeman, Applications Engineer

### Amplifier Bandwidth Limitations

**A**mplifier closed-loop bandwidth-limited accuracy considerations are critical when driving high resolution A/D Converters (ADCs). It is useful to be able to predict, for any closed loop gain, the required gain-bandwidth (GBW) product of an op amp to achieve a specified level of accuracy in terms of the minimum ADC resolution. Other sources of error include offset, noise, and distortion, which are beyond the scope of this article. A simple equation will be developed below that relates the minimum closed-loop bandwidth of an op amp to the resolution requirements of a given ADC.

### Amplifier Response


Assuming a single pole roll-off, the frequency dependence of an amplifier's closed-loop gain,  $A_{CL}$ , is given by:

$$A_{CL} = \frac{A_{CLDC}}{\sqrt{1 + \left(\frac{f}{f_{-3dB}}\right)^2}} \quad \text{Equation 1}$$

where  $A_{CLDC}$  is the amplifier's DC gain, and  $f_{-3dB}$  is its corner frequency.

This equation describes the op amp's closed-loop gain at frequency  $f$ , in terms of the amplifier's corner frequency.

The vast majority of op amps employ internal lag compensation with a single dominant pole that rolls off the open-loop gain, from its cut-off frequency, to unity gain (zero dB) at a 20 dB per decade rate. The frequency response of such an amplifier with feedback is therefore also the same as for an RC low-pass filter. The frequency where the open-loop gain crosses unity gain is routinely called the GBW product in op amp datasheets. The GBW product for an amplifier is the product of its open loop gain (constant for a given amplifier)

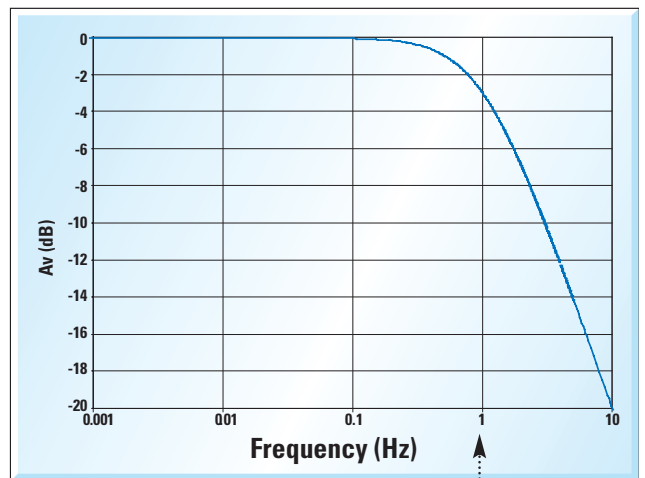

-3 dB cut-off frequency,  $f_U$

**Figure 1. Normalized bandwidth curve for an op amp in unity gain (Curve assumes an open loop gain with a single pole roll-off.)**

and its -3 dB bandwidth (GBW product = gain x -3 dB bandwidth). Given the GBW product and the open-loop gain roll-off of -20 dB per decade, the -3 dB bandwidth for any closed loop gain can be easily calculated, from

$$BW = GBW / A_{CL} \quad \text{Equation 2}$$

For example, the LMP2011 with a GBW product of 3 MHz will have a bandwidth of 300 kHz when configured with an  $A_{CL}$  of 10 V/V. However, at -3 dB the closed-loop gain has a 29.3% gain error. In reality, the gain expression starts rolling off long before the -3 dB pole frequency is reached. It is important to determine the frequency at which the closed-loop gain error increases above the maximum error allowed for a given data error. The maximum error in data

**NEXT ISSUE:**

**Dithered Switching Frequency**

# Featured Products

## Single/Dual, High Precision, Rail-to-Rail Output Operational Amplifier

The LMP2011/12/14 (single/dual/quad) are part of the LMP™ family of precision amplifiers that offer an industry leading gain bandwidth of 3 MHz, while maintaining high precision and low drift over time. These amplifiers deliver excellent CMRR (130 dB) and PSRR (120 dB) ratings without frequency related noise (no 1/f). The high CMRR allows for high accuracy across voltages.

The LMP2011/12/14 deliver a very low input offset voltage which offers high accuracy measurements with continued accuracy over temperature. The low voltage noise increases signal accuracy during low frequency measurements. No external capacitors are required.

### Features

- Low guaranteed  $V_{OS}$  over temperature 60  $\mu$ V
- Low noise with no 1/f, 35 nV/ $\sqrt{\text{Hz}}$
- High CMRR 130 dB
- High PSRR 120 dB
- High  $A_{VOL}$  130 dB
- Wide gain-bandwidth product 3 MHz
- High slew rate 4 V/ $\mu$ s
- Low supply current 930  $\mu$ A
- Rail-to-rail output 30 mV from rails



The extended temperature range of -40°C to 125°C allows for operation in demanding industrial and automotive applications, as well as in precision instrumentation amplifiers, thermocouple amplifiers, and strain gauge bridge amplifiers. The LMP2011 is offered in SOIC-8 and SOT23-5 packaging. The LMP2012 is offered in SOIC-8 and mini SOIC-8 packaging. The LMP2014 is offered in TSSOP-14 packaging.

For FREE samples, datasheets, and more, visit  
[www.national.com/pf/LM/LMP2011.html](http://www.national.com/pf/LM/LMP2011.html)  
[www.national.com/pf/LM/LMP2012.html](http://www.national.com/pf/LM/LMP2012.html)  
[www.national.com/pf/LM/LMP2014MT.html](http://www.national.com/pf/LM/LMP2014MT.html)



## Low Power, 200 kSPS to 500 kSPS, 8/10/12-Bit A/D Converters

The ADC081S051, ADC101S051, and ADC121S051 are low-power, single channel, CMOS 8/10/12-bit Analog-to-Digital Converters (ADCs) with a high-speed serial interface. Unlike the conventional practice of specifying performance at a single sample rate only, these ADCs are fully specified over a sample rate range of 200 kSPS to 500 kSPS.

Operation with a single supply can range from +2.7V to +5.25V. Normal power consumption for the ADC121S051 using a +3.6V or +5.25V supply is 1.7 mW and 8.7 mW, respectively. The power-down feature reduces the power consumption to as low as 2.6  $\mu$ W using a +5.25V supply.

### Features

- Speed range: 200 kSPS to 500 kSPS
- Integral Non-Linearity (INL):
  - +0.45, -0.40 LSB (ADC121S051)
  - +0.15, -0.09 LSB (ADC101S051)
  - +0.06, -0.05 LSB (ADC081S051)
- Differential Non-Linearity (DNL):
  - +0.5, -0.25 LSB (ADC121S051)
  - +0.15, -0.11 LSB (ADC101S051)
  - +0.06, -0.045 LSB (ADC081S051)
- Signal-to-Noise Ratio (SNR):
  - 72.0 dB (ADC121S051)
  - 61.6 dB (ADC101S051)
  - 49.6 dB (ADC081S051)

The ADC081S051, ADC101S051, and ADC121S051 are ideal for use in applications including portable systems, remote data acquisitions, and instrumentation and control systems. These low power ADCs are offered in LLP-6 and SOT23-6 packaging.

For FREE samples, datasheets, and more, visit  
[www.national.com/pf/DC/ADC081S051.html](http://www.national.com/pf/DC/ADC081S051.html)  
[www.national.com/pf/DC/ADC101S051.html](http://www.national.com/pf/DC/ADC101S051.html)  
[www.national.com/pf/DC/ADC121S051.html](http://www.national.com/pf/DC/ADC121S051.html)

## Amplifier Closed-Loop Bandwidth Considerations in High Resolution A/D Converter Applications

converters is usually expressed in terms of the Least Significant Bit (LSB). Ideally, all error sources should be well below this level. An LSB of an ADC is defined as the finest resolution of which the ADC is capable. Quantitatively this is equal to the full scale voltage divided by the resolution of the ADC ( $V_{FS}/2^N$ ) for one LSB, where N is the number of bits. Thus for an 8-bit converter, the error would be  $V_{FS}/256$ . If  $1/2$  LSB is set as the required system accuracy, the acceptable accuracy limit would be:

**Accuracy ( $\delta$ ) = 100% - gain error (%)**,

where gain error =  $1/2 (1/2^N) * 100\%$ , *Equation 3*

which gives  $\delta = 100\% - 1/2 (1/2^N) * 100\%$ , or 99.8%

The accuracy is calculated based on the -3 dB cut-off frequency at a particular close-loop gain. Approximating the frequency response of an op amp to that of a single pole filter, we get the frequency vs gain curve of such a system as shown in *Figure 1*.

Because the curve is normalized to 1 for a frequency  $f_U$  (-3 dB at unity gain), the expression for this curve, for any  $f$ , from *Equation 1* is

$$A_{cl} = \frac{1}{\sqrt{1 + (f)^2}} \quad \text{Equation 4}$$

Solving for  $f$  gives

$$f = \sqrt{\frac{1}{(A_{cl})^2} - 1} \quad \text{Equation 5}$$

The question is now, for any ACL, what is the maximum signal frequency that does not exceed the specified error? From *Equation 1*, *Equation 3*, and *Equation 5*, and the example for 8-bit accuracy, the normalized frequency,  $f_{MAX}$ , for an amplifier requiring 99.8% accuracy, is the frequency where the gain roll off is less than  $1/2$  LSB is expressed as

$$f_{max} = \sqrt{\frac{1}{(0.998)^2} - 1} \times f_U = 0.062 \times f_U \quad \text{Equation 6}$$

for the case of unity gain.

Thus, the maximum frequency at which it is still possible to get at least 99.8% ( $1/2$  LSB) accuracy in an 8-bit system, is 0.062 of the op amp's -3 dB frequency. In the case of the LMP2011 example, the available bandwidth for 99.8% accuracy is

$$0.062 \times f_{-3dB} \text{ kHz} = 0.062 \times 300 \text{ kHz} = 18.6 \text{ kHz}$$

In general, the normalized  $f_{MAX}$  for  $1/2$  LSB error for ADCs of various resolutions can be calculated as

$$\text{Normalized } f_{MAX} = \sqrt{\frac{1}{\left(1 - \frac{1}{2^{n+1}}\right)^2} - 1} \quad \text{Equation 7}$$

Using this equation, a list of normalized bandwidths for system resolutions up to 16 bits have been calculated (*Table 1*).

System Resolution	Normalized Bandwidth for $<1/2$ LSB Error
8-bit	0.062592
9-bit	0.044227
10-bit	0.031261
11-bit	0.022101
12-bit	0.015626
13-bit	0.011049
14-bit	0.007813
15-bit	0.005524
16-bit	0.003906

**Table 1. Calculated maximum frequency with an error less than  $1/2$  LSB at the specified resolution**

### Conclusion

Obtaining dynamic performance compatibility between an amplifier and an ADC in data acquisition designs requires careful analysis of the amplifier's bandwidth capability. Choosing an amplifier that satisfies the bandwidth requirements of the system on the basis of its GBW product specification can introduce an excessive amount of error into the system. The amplifier must be chosen such that its closed-loop bandwidth matches the resolution needs of the ADC. This dictates the need for a much wider bandwidth amplifier than would be suggested by the specified signal bandwidth in the amplifier's datasheet. ■

View over 50 design seminars by industry experts at [www.national.com/onlineseminars](http://www.national.com/onlineseminars)

## Featured Products



### Low Power, High Precision 8/10/12-Bit, 1 MSPS A/D Converters

The ADC081S101, ADC101S101, and ADC121S101 are low-power, single channel, CMOS 8/10/12-bit Analog-to-Digital Converters (ADCs) with a high-speed serial interface. Operation with a single supply can range from +2.7V to +5.25V. Normal power consumption using a +3V or +5V supply is 2 mW and 10 mW, respectively. The power-down feature reduces the power consumption to as low as 2.5  $\mu$ W using a +5V supply.

#### Features

- Speed range: 500 kSPS to 1 MSPS
- Integral Non-Linearity (INL):
  - $\pm 0.4$  LSB (ADC121S101)
  - $\pm 0.2$  LSB (ADC101S101)
  - $\pm 0.05$  LSB (ADC081S101)
- Differential Non-Linearity (DNL):
  - +0.5, -0.3 LSB (ADC121S101)
  - +0.3, -0.2 LSB (ADC101S101)
  - $\pm 0.07$  LSB (ADC081S101)
- Signal-to-Noise Ratio (SNR):
  - 72.5 dB (ADC121S101)
  - 62 dB (ADC101S101)
  - 49.7 dB (ADC081S101)

The ADC081S101, ADC101S101, and ADC121S101 are ideal for use in applications including portable systems, remote data acquisitions, instrumentation, and control systems. These ADCs are offered LLP-6 and SOT23-6 packaging.

For FREE samples, datasheets, and more, visit [www.national.com/pf/DC/ADC081S101.html](http://www.national.com/pf/DC/ADC081S101.html)  
[www.national.com/pf/DC/ADC101S101.html](http://www.national.com/pf/DC/ADC101S101.html)  
[www.national.com/pf/DC/ADC121S101.html](http://www.national.com/pf/DC/ADC121S101.html)

### Precision, 17 MHz, Low Noise, CMOS Input Op Amps

The LMP7711/12 (single/dual) are low-noise, low offset, CMOS input, rail-to-rail output precision amplifiers with a high gain bandwidth and an enable pin. These precision amplifiers achieve an input bias current of 100 fA, an input referred voltage noise of 5.8 nV/ $\sqrt{\text{Hz}}$  and an input offset voltage of less than  $\pm 150$   $\mu$ V, using a CMOS input stage.

These features make the LMP7711/12 superior choices for precision applications. Consuming only 1.15 mA of supply current, the LMP7711 offers a high gain bandwidth product of 17 MHz, enabling accurate amplification at high closed loop gains. The high PSRR (100 dB) and CMRR (100 dB) ensure high accuracy with noisy supplies, and high accuracy over a wide input range.



#### Features

- $\pm 150$   $\mu$ V (max) input offset voltage
- 100 fA input bias current
- 5.8 nV/ $\sqrt{\text{Hz}}$  input voltage noise
- 17 MHz gain bandwidth product
- 1.15 mA supply current (LMP7711)
- 1.30 mA supply current (LMP7712)
- 0.001% THD+N at f = 1 kHz
- Rail-to-rail output swing

Operating at  $-40^{\circ}\text{C}$  to  $+125^{\circ}\text{C}$ , these precision amplifiers are ideal for use in sensor interface applications, transimpedance amplifiers, and active filters and buffers. The LMP7711 is offered in Thin SOT23-6 packaging and the LMP7712 is offered in a MSOP-10 packaging.

For FREE samples, datasheets, and more, visit [www.national.com/pf/LM/LMP7711.html](http://www.national.com/pf/LM/LMP7711.html)  
[www.national.com/pf/LM/LMP7712.html](http://www.national.com/pf/LM/LMP7712.html)



## IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

### Products

Audio	<a href="http://www.ti.com/audio">www.ti.com/audio</a>
Amplifiers	<a href="http://amplifier.ti.com">amplifier.ti.com</a>
Data Converters	<a href="http://dataconverter.ti.com">dataconverter.ti.com</a>
DLP® Products	<a href="http://www.dlp.com">www.dlp.com</a>
DSP	<a href="http://dsp.ti.com">dsp.ti.com</a>
Clocks and Timers	<a href="http://www.ti.com/clocks">www.ti.com/clocks</a>
Interface	<a href="http://interface.ti.com">interface.ti.com</a>
Logic	<a href="http://logic.ti.com">logic.ti.com</a>
Power Mgmt	<a href="http://power.ti.com">power.ti.com</a>
Microcontrollers	<a href="http://microcontroller.ti.com">microcontroller.ti.com</a>
RFID	<a href="http://www.ti-rfid.com">www.ti-rfid.com</a>
OMAP Mobile Processors	<a href="http://www.ti.com/omap">www.ti.com/omap</a>
Wireless Connectivity	<a href="http://www.ti.com/wirelessconnectivity">www.ti.com/wirelessconnectivity</a>

### Applications

Communications and Telecom	<a href="http://www.ti.com/communications">www.ti.com/communications</a>
Computers and Peripherals	<a href="http://www.ti.com/computers">www.ti.com/computers</a>
Consumer Electronics	<a href="http://www.ti.com/consumer-apps">www.ti.com/consumer-apps</a>
Energy and Lighting	<a href="http://www.ti.com/energy">www.ti.com/energy</a>
Industrial	<a href="http://www.ti.com/industrial">www.ti.com/industrial</a>
Medical	<a href="http://www.ti.com/medical">www.ti.com/medical</a>
Security	<a href="http://www.ti.com/security">www.ti.com/security</a>
Space, Avionics and Defense	<a href="http://www.ti.com/space-avionics-defense">www.ti.com/space-avionics-defense</a>
Transportation and Automotive	<a href="http://www.ti.com/automotive">www.ti.com/automotive</a>
Video and Imaging	<a href="http://www.ti.com/video">www.ti.com/video</a>

TI E2E Community Home Page

[e2e.ti.com](http://e2e.ti.com)

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265  
Copyright © 2011, Texas Instruments Incorporated