

Using the TPS5430 as an Inverting Buck-Boost Converter

John Tucker

PMP Systems Power

ABSTRACT

The wide input voltage range SWIFT™ (Switcher With Integrated FET) dc/dc converters are typically used as step-down converters where the derived output is a positive voltage less than the input voltage source. In some cases, it may be required to generate a negative voltage from the input voltage source. In such instances, it is possible to configure the TPS5430/20/10 devices in an inverting buck-boost topology, where the output voltage is negative with respect to ground.

Contents

1	Basic Buck Topology	1
2	Inverting Buck-Boost Topology	2
3	Design Considerations	2
4	Circuit Performance	4
5	Conclusion	7

List of Figures

1	Buck Topology	1
2	Inverting Buck-Boost Topology	2
3	TPS5430 Buck-Boost Application	3
4	Closed Loop Response	4
5	Transient Response	5
6	Output Voltage Ripple and PH Node Voltage	5
7	Efficiency	6
8	Load Regulation	6

1 Basic Buck Topology

To understand the circuit operation, consider the basic topology of the buck converter as shown in Figure 1.

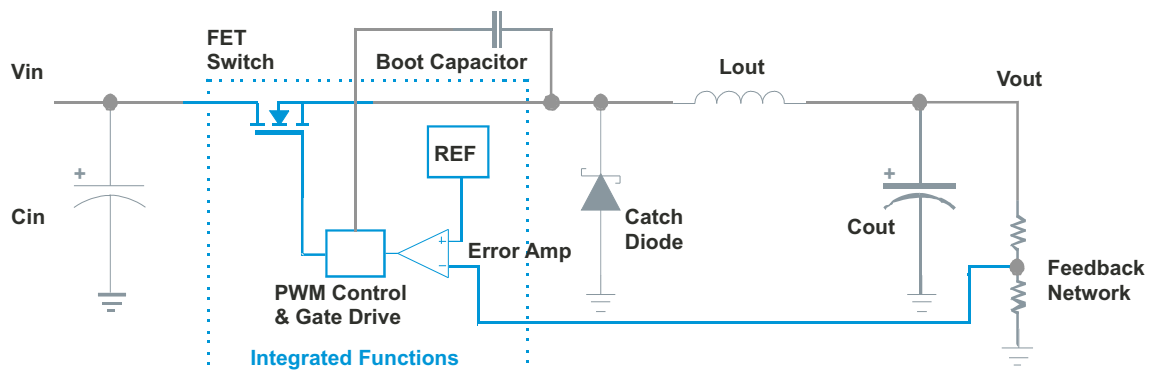


Figure 1. Buck Topology

SWIFT, PowerPAD are trademarks of Texas Instruments.

Inverting Buck-Boost Topology

When the FET switch is on, the voltage across the inductor is $V_{in} - V_{out}$, and the current through the inductor increases at a rate of $di/dt = (V_{in} - V_{out}) / L$. When the switch is off, the inductor voltage reverses to keep the inductor current continuous. Assuming that the voltage drop across the diode is small, the inductor current ramps down at a rate of $di/dt = (V_{out}) / L$. The steady-state load current is always carried by the inductor during both the on and off times of the FET switch. The average inductor current is equal to the load current, and the peak-to-peak inductor ripple current is $I_{L\ p-p} = ((V_{in} - V_{out}) D) / (f_{sw} \times L)$. Where V_{in} is the input voltage, V_{out} is the output voltage, the duty cycle $D = V_{out} / V_{in}$, f_{sw} is the switching frequency and L is the inductor value.

2 Inverting Buck-Boost Topology

Compare the above operation to that of the buck-boost topology shown in [Figure 2](#).

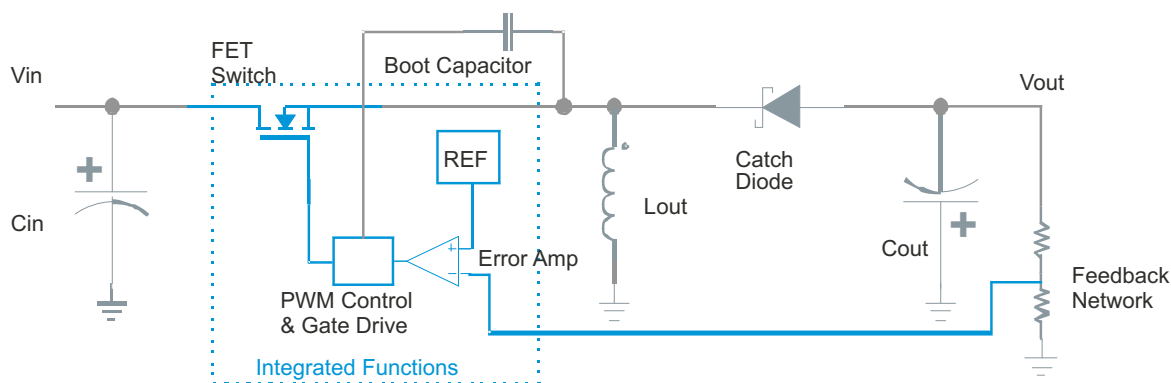


Figure 2. Inverting Buck-Boost Topology

The inductor and catch diode have switched places relative to the buck converter of [Figure 1](#). Also, the output capacitor is reversed in polarity as the output voltage is negative. During operation, when the FET switch is on, the voltage across the inductor is V_{in} , and the current ramps up at a rate of $di/dt = V_{in} / L$. While the FET switch is on, all of the load current is supplied by energy stored in the output capacitor. When the FET switch turns off, the inductor reverses polarity to keep the inductor current continuous. The voltage across the inductor is approximately V_{out} and the inductor current decreases at a rate of $di/dt = -V_{out} / L$. During the off-time, the inductor supplies both the current to the load and also current to replenish the energy lost by the capacitor during the on-time. So, for the buck-boost circuit, the average inductor current is $I_L = I_{out} / (1 - D)$, and the peak-to-peak inductor current is $I_{L\ p-p} = (V_{in} \times D) / (F_{sw} \times L)$. The duty cycle D is approximately $D = V_{out} / (V_{out} - V_{in})$. These basic differences in circuit operation are important when using the TPS5430 as a buck-boost converter.

3 Design Considerations

Consider the circuit of [Figure 3](#). In this design, the TPS5430 is designed as an inverting buck-boost converter with a 15-V input voltage and a -5-V output voltage. The design equations are presented in simplified form with the semiconductors idealized and other component losses neglected. To implement the buck-boost topology of [Figure 2](#), connect the TPS5430 GND pin to V_{out} and connect the positive terminal of the output capacitor to the V_{out} return, which is the circuit ground.

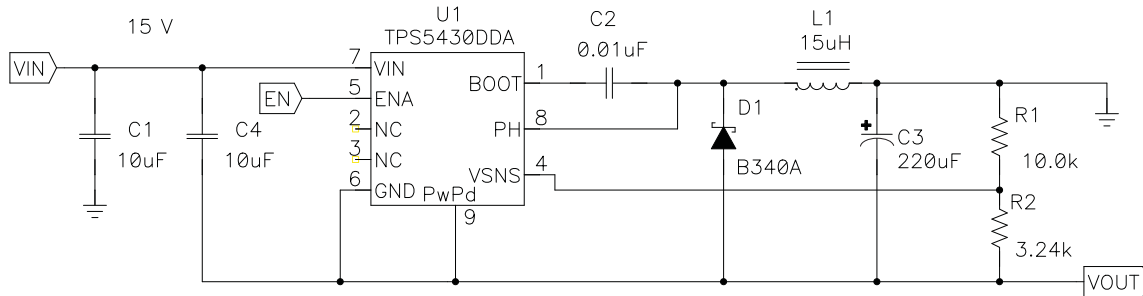


Figure 3. TPS5430 Buck-Boost Application

The input voltage across the device VIN pin to GND is now $V_{in} - V_{out}$, or $15 - (-5) = 20\text{ V}$.

The operating duty cycle is:

$$D = V_{out} / (V_{out} - V_{in}) = -5 / (-5 - 15) = 0.25$$

The average inductor current is:

$$I_{l\text{ avg}} = I_{out} / (1-D)$$

The average output current cannot exceed the TPS5430 rated output of 3 A, so the available load current is reduced by a factor of $1 - D$. For this design, the maximum available dc load current is:

$$3 \times (1 - D) = 2.25\text{ A}$$

Also, the inductor ac ripple current should be kept small for several reasons. The peak inductor current is the average inductor current plus one-half the peak-to-peak ac current. This must be below the internal current limit of 4 A. The inductor ac ripple current also determines the dc output current below which the circuit begins to operate in the discontinuous conduction mode. This point is when the dc output current is equal to one-half the peak-to-peak ac current. This circuit is designed to operate in the continuous mode; therefore, the inductor ripple current should be less than 2 times the minimum output current. In general, this is a more severe restriction than the current limit. Additionally, the ripple current contributes significantly to the output voltage ripple. Lower inductor ripple currents provide cleaner output voltages.

For the inverting buck-boost converter, there are significant operating differences between discontinuous and continuous mode operation. Designs that are stable in the discontinuous mode of operation often will become unstable when increased load current causes them to operate in the continuous mode as the feedback loop now contains a right-half-plane zero. This example is designed to be stable in continuous conduction mode, and should be operated in that mode. The inductor value is chosen so that the converter will work in the continuous conduction mode at any output above 0.25 A. If the load current drops below 0.25 A the output will continue to regulate and remain stable in this design.

For this design, the inductor value is calculated based on maintaining continuous conduction with a minimum load of 250 mA. The maximum switch current is $3 + (0.500 / 2) = 3.25\text{ A}$, which is below the 4-A minimum current limit of the TPS5430; the minimum inductor size is given by:

$$L_{min} = (V_{in} \times D) / (f_{sw} \times 2 \times I_{omin}) = (15 \times 0.25) / (500000 \times 2 \times 0.25) = 15\ \mu\text{H}$$

Choose the inductor so that RMS and saturation current ratings are not exceeded. The peak current of 3.25 A should be lower than the saturation current. The RMS current is given by:

$$I_{lrms} = \sqrt{I_{avg}^2 + (1/12 \times I_{l\text{p-p}}^2)} = 3.003\text{ A}$$

Choose the output capacitor so that the circuit will work well with the internal compensation of the TPS5430. The internal compensation for the TPS5430 contains an integrator pole at the origin and two additional poles and zeros. These are located at the frequencies shown:

- Fint = 2165 Hz
- Fz1 = 2170 Hz
- Fz2 = 2590 Hz
- Fp1 = 24 kHz
- Fp2 = 54 kHz

The capacitor value is chosen based on the output inductor so that the LC resonant frequency is situated near in frequency to the internal zeros of the internal compensation. The LC resonant frequency should be at or just above the Fz2 frequency. The ESR of the output capacitor then is chosen so that the ESR zero is located near (+/-10 kHz) to the first internal pole in the compensation network. For this circuit, the output capacitor is a 220- μ F POSCAP with an ESR of 40 m Ω . The resultant LC resonant frequency and ESR zero are:

$$F_{lc} = 1 / (2 \times \pi \times \sqrt{L \times C}) = 2770 \text{ Hz}$$

$$F_{esr} = 1 / (2 \times \pi \times C \times R_{esr}) = 18 \text{ kHz}$$

This assures stable operation with an optimal closed-loop crossover frequency.

On the input, be sure to use both a bypass capacitor from Vin to ground (C1) and from Vin to Vout (C4). The bypass from Vin to Vout is across the device voltage input. These can be of equal value and should meet the ripple current and voltage rating of the circuit.

The buck-boost circuit shown in [Figure 3](#) is available as an evaluation module. See the [TPS5430](#) product folder or send an e-mail to tps5430buckboost@ti.com to request an evaluation module.

4 Circuit Performance

The performance characteristics of the circuit are depicted in [Figure 4](#) through [Figure 8](#). All performance data is for an ambient temperature of 25°C. The measured closed-loop response is shown in [Figure 4](#). The closed-loop crossover frequency is approximately 20 kHz and the phase margin is 59 degrees.

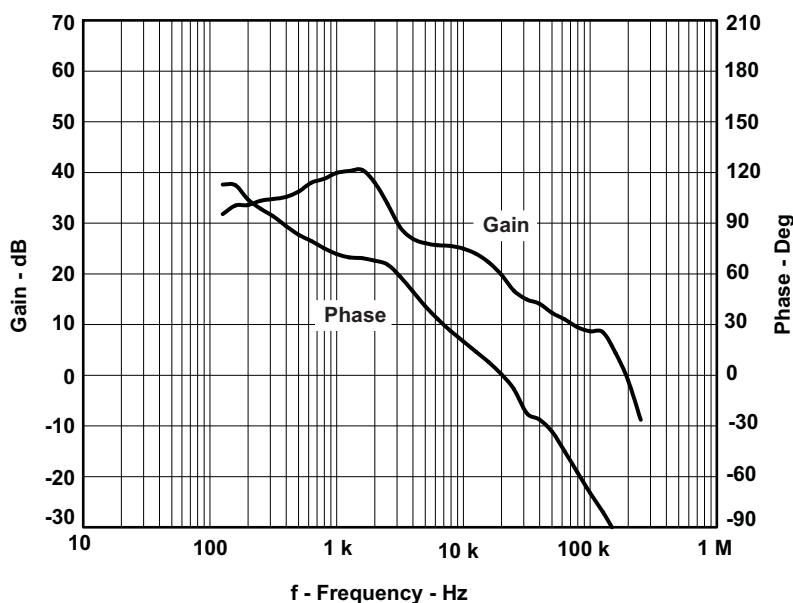


Figure 4. Closed Loop Response

The output voltage response to a load transient is shown in [Figure 5](#). The output current step is from the minimum current of 0.25 A to 2 A then back to 0.25 A. The peak-to-peak voltage deviation in response to the step load change is ± 50 mV.

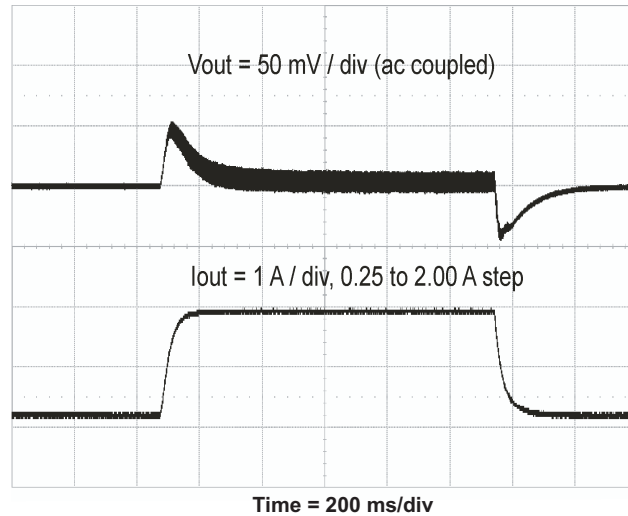


Figure 5. Transient Response

Output voltage ripple and PH node waveform is shown in [Figure 6](#). Note that the PH node switching waveform varies from V_{in} to V_{out} , or from 15 V to -5 V. The ground reference line is indicated in the figure. Also observe that the output voltage ripple does not show the linear ramp characteristic typical for the buck converter. In the buck converter, the average inductor current is delivered to the load while the ac portion is shunted to ground through the output filter capacitor. The primary component of the ripple voltage is the ac ripple current times the esr of the output capacitor, resulting in a waveform resembling a ramp that rises during the FET with on time and falls during the switch-off time. For the inverting buck-boost converter, the output capacitor supplies the load current during the switch-on time, and is recharged during the switch-off time. This charge and discharge cycle is superimposed with the ac ripple current to create a more complex ripple current as shown in [Figure 6](#). Remember that the output voltage is negative; so, the positive portions of the waveform represent the output going less negative or the discharge portion of the cycle.

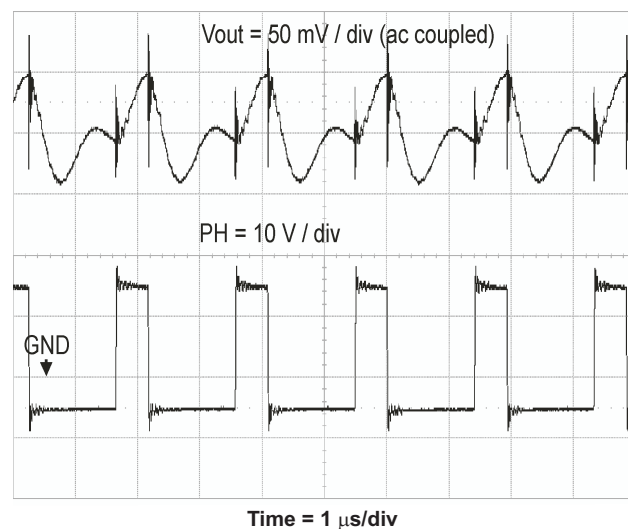


Figure 6. Output Voltage Ripple and PH Node Voltage

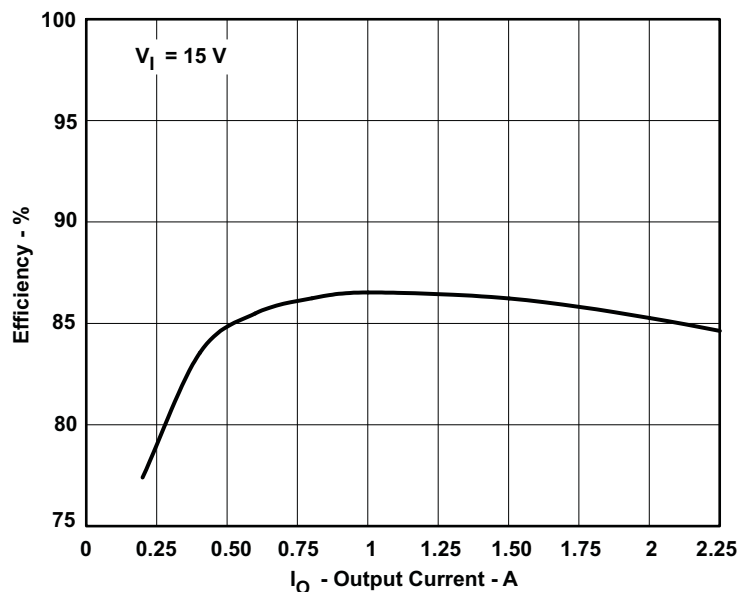


Figure 7. Efficiency

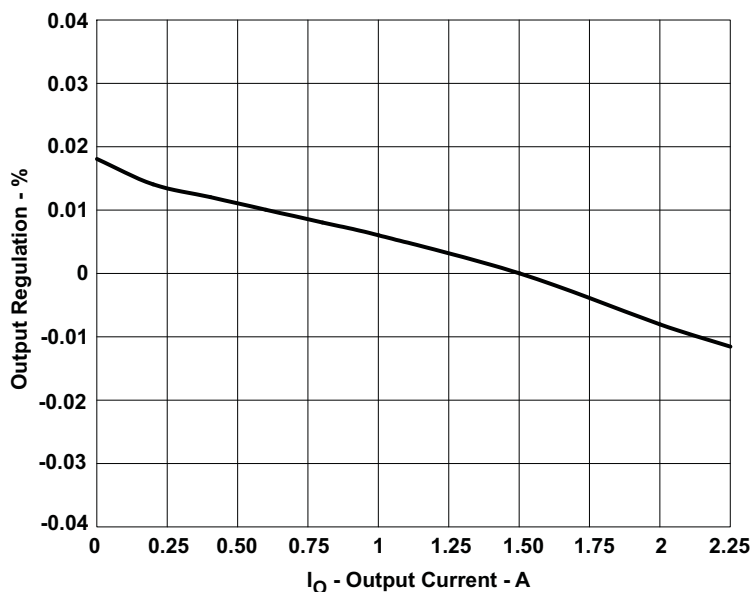


Figure 8. Load Regulation

The efficiency curve is shown in [Figure 7](#). The low on-resistance of the internal FET switch makes high efficiency of 87 percent maximum possible for this design. The output voltage variation with respect to load current is shown in [Figure 8](#). Note the tight voltage regulation across the entire load current range of which this circuit is capable.

5 Conclusion

The TPS5430 can be used to generate a negative output voltage from a positive input voltage by configuring the circuit as a buck-boost design. The circuit design is straight-forward, but remember these important points. The output current is less than the average inductor current by a factor of $1-D$; thus, the available output current will be less than the device rating. The output voltage is negative and is available at the device ground pin; so, the effective voltage across the input of the device is $V_{in} - V_{out}$. This difference must not exceed the input voltage rating of the device. Make sure not to tie the ground of the device or the exposed PowerPAD™ package to the system ground.

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products		Applications	
Amplifiers	amplifier.ti.com	Audio	www.ti.com/audio
Data Converters	dataconverter.ti.com	Automotive	www.ti.com/automotive
DSP	dsp.ti.com	Broadband	www.ti.com/broadband
Interface	interface.ti.com	Digital Control	www.ti.com/digitalcontrol
Logic	logic.ti.com	Military	www.ti.com/military
Power Mgmt	power.ti.com	Optical Networking	www.ti.com/opticalnetwork
Microcontrollers	microcontroller.ti.com	Security	www.ti.com/security
RFID	www.ti-rfid.com	Telephony	www.ti.com/telephony
Low Power Wireless	www.ti.com/lpw	Video & Imaging	www.ti.com/video
		Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2007, Texas Instruments Incorporated